

This is it! You can't get any newer in theory and practice than this matching device you can put together now.

A Multimatch Unun

BY JERRY SEVICK*, W2FMI

Broadband multimatch ununs (unbalanced-to-unbalanced transformers) capable of high-power applications have been the goal of many designers throughout the years. Some have resorted to using conventional autotransformers with tapped windings to obtain the many impedance transformation ratios. These met with little success, however, because of their limited bandwidths and efficiencies. Others (including the author's¹) have tried tapping a bifilar Ruthroff unun.² Although these designs yielded the high efficiencies of transmission-line transformers, they too had limited bandwidths. Furthermore, their best bandwidths (for the various ratios) occurred at odd impedance levels. In other words, they didn't meet the objective of broadband operation with one of the input or output ports being at 50 ohms.

This article describes a design³ that is capable of broadband operation from 1.7 MHz to 30 MHz with the following five ratios (which are close to): 1.5:1, 2:1, 4:1, 6:1,

and 9:1. Since the two lower ratios work well in either direction (that is, stepping up or down from 50 ohms), this design can match 50 ohm cable to impedances as high as 100 ohms (actually, 112.5 ohms) and as low as 5.6 ohms over the frequency range. Furthermore, since this is a transmission-line transformer which cancels out the flux in the core, losses (in a matched condition) of only 0.04 dB to 0.08 dB can be expected.

The novelty in the design is the use of a trifilar winding (with one winding tapped) on a very small ferrite toroid, resulting in the shortest possible lengths of transmission lines. The windings are also connected in such a manner as to optimize the characteristic impedances of the windings from an overall standpoint. Since the transmission-line transformer is a choke (which limits the low-frequency response) and a configuration of transmission lines, the high-frequency response is not limited by leakage inductance or shunting capacitance (as some say), but by *standing waves*.

Therefore, the combination of using small ferrite toroids with the maximum allowable permeability (less than 300) for high efficiency,¹ and with sufficient turns


to meet the low-frequency objective, results in the excellent performance exhibited by the designs in this article.

For those interested in the design considerations of this broadband multimatch transformer, a brief review is presented in the first section. It is then followed by a section describing a high-power design capable of handling the full legal limit of amateur radio power. And finally, the last section includes a low-power design capable of handling the output of any HF transceiver. Since transmission-line transformers can be made so efficient in matching 50 ohms to 100 ohms or less, their small sizes will surprise many readers.

The Circuit


Fig. 1(A) is presented here because it is the easiest form of the trifilar-wound unun to explain. For example, if the input voltage to ground, V_1 , is connected to terminal H, the output terminal B has a voltage to ground of $3/2V_1$. This results in a transformation ratio, ρ , of $(3/2)^2$, or 2.25:1. This should satisfy most 2:1 requirements. If the

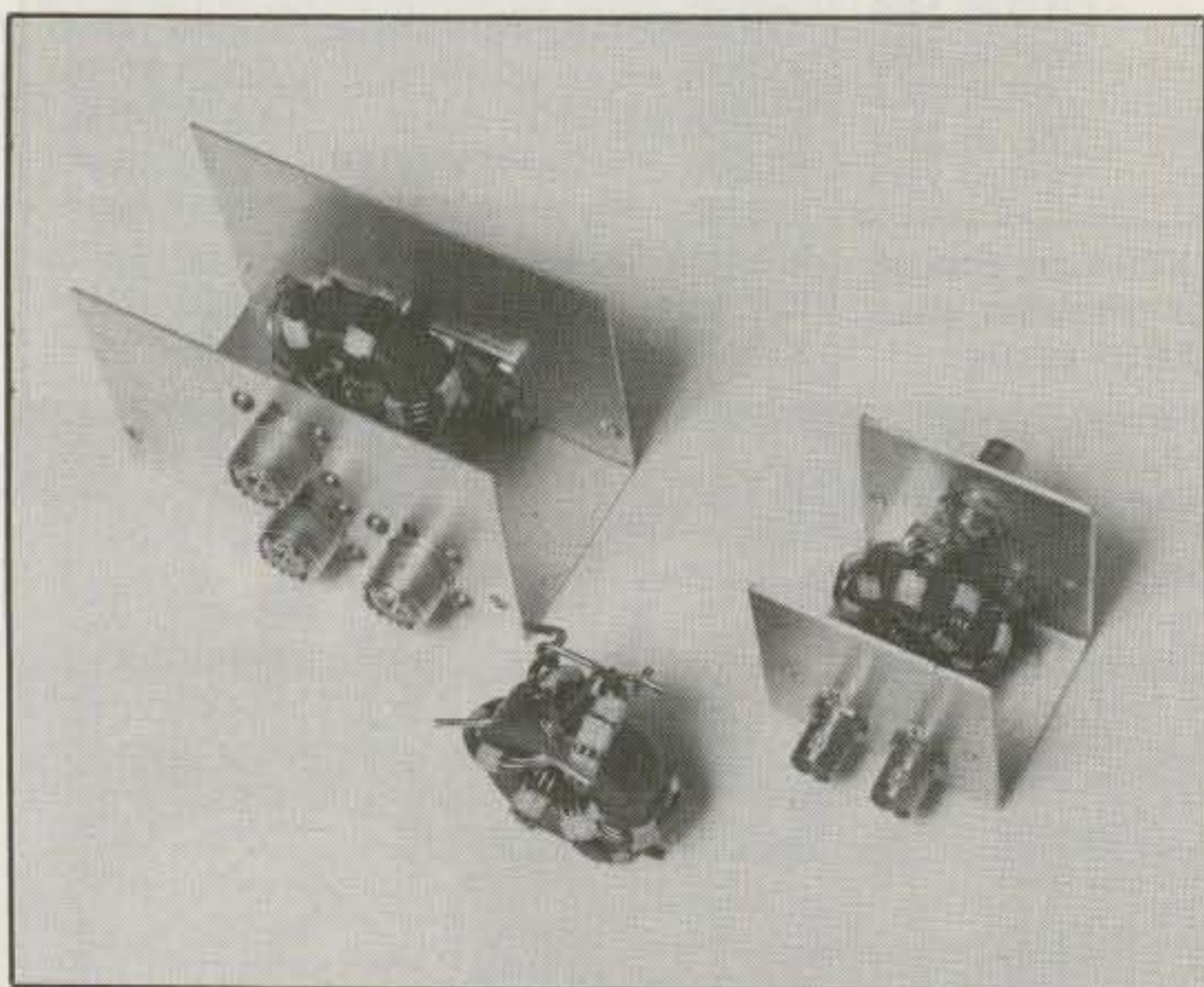*32 Granville Way, Basking Ridge, NJ 07920



From left to right, the high-power unit, the 5-ratio unun, and the low-power unit. (See text for details.)

Fig. 1—Circuit diagrams for the 5-ratio unun: (A) diagram for analysis; (B) transposed windings for best overall performance.

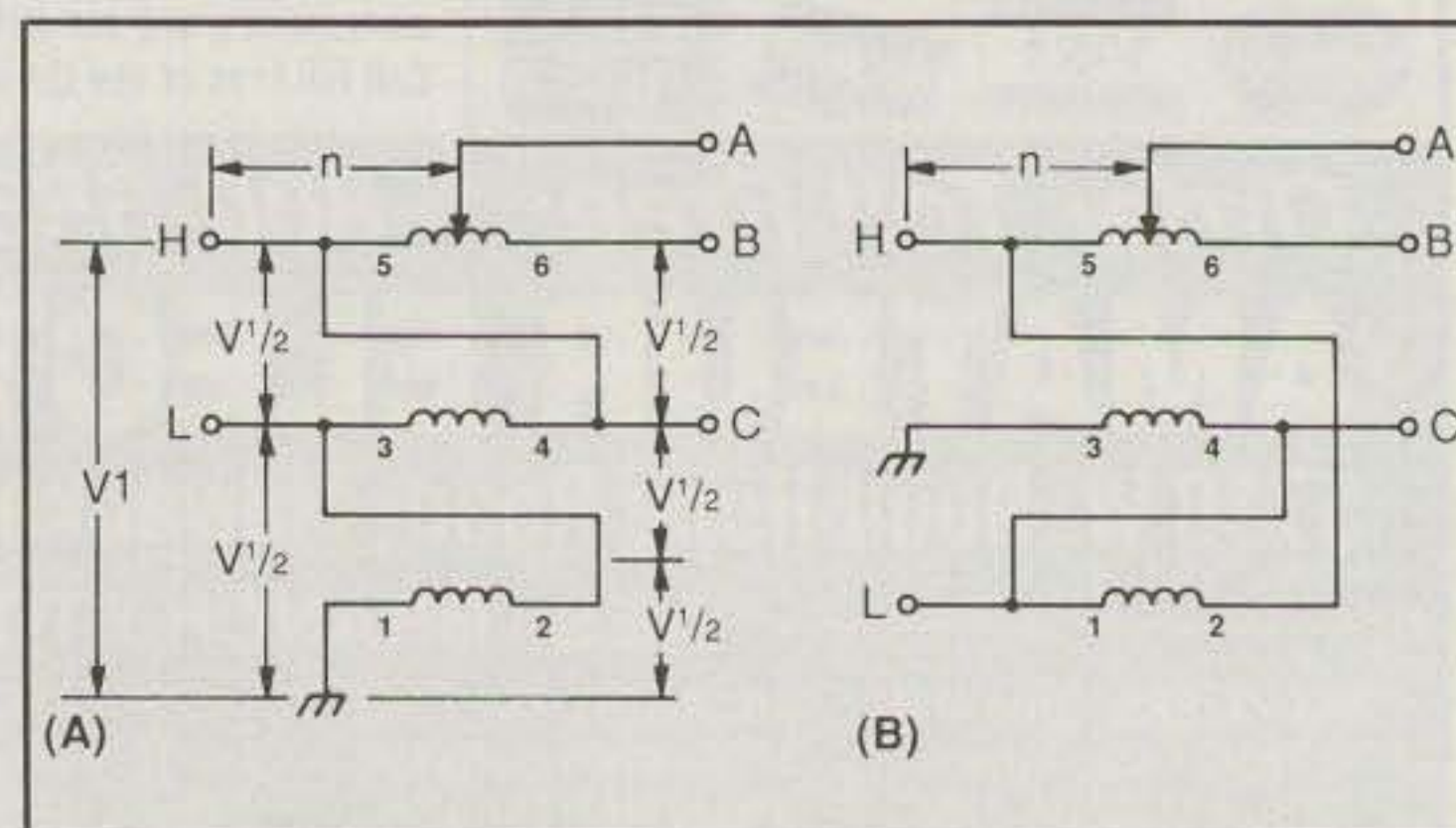

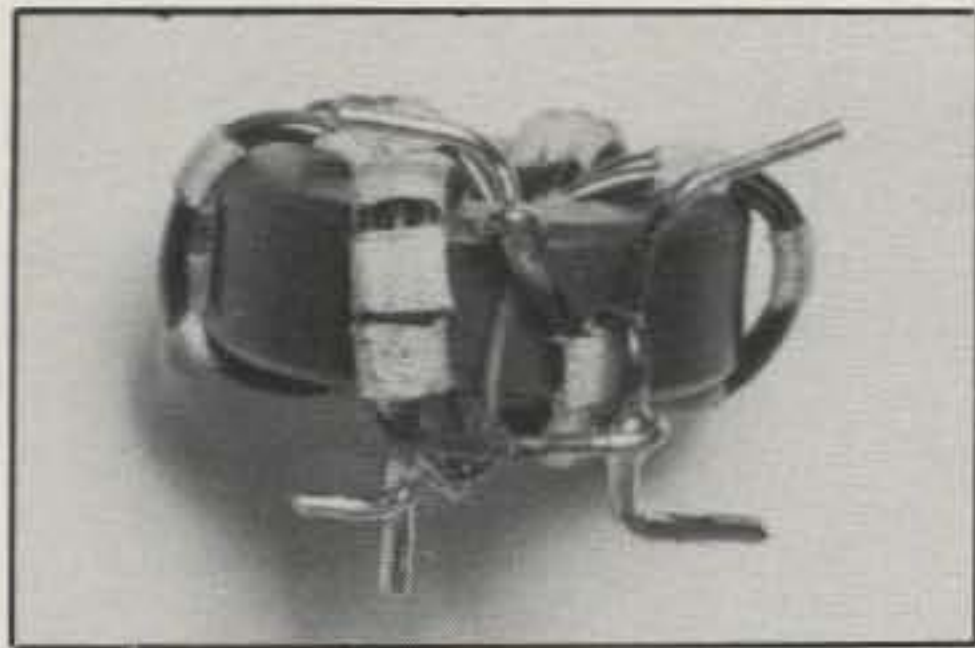


Fig. 2- Bottom view of the 5-ratio unun of fig. 1(B). The upper-left lead is terminal C. The upper-right lead is terminal B. The lower-left lead is terminal H. The straight-downward lead is grounded (terminal 3). The lower-right lead is terminal L.

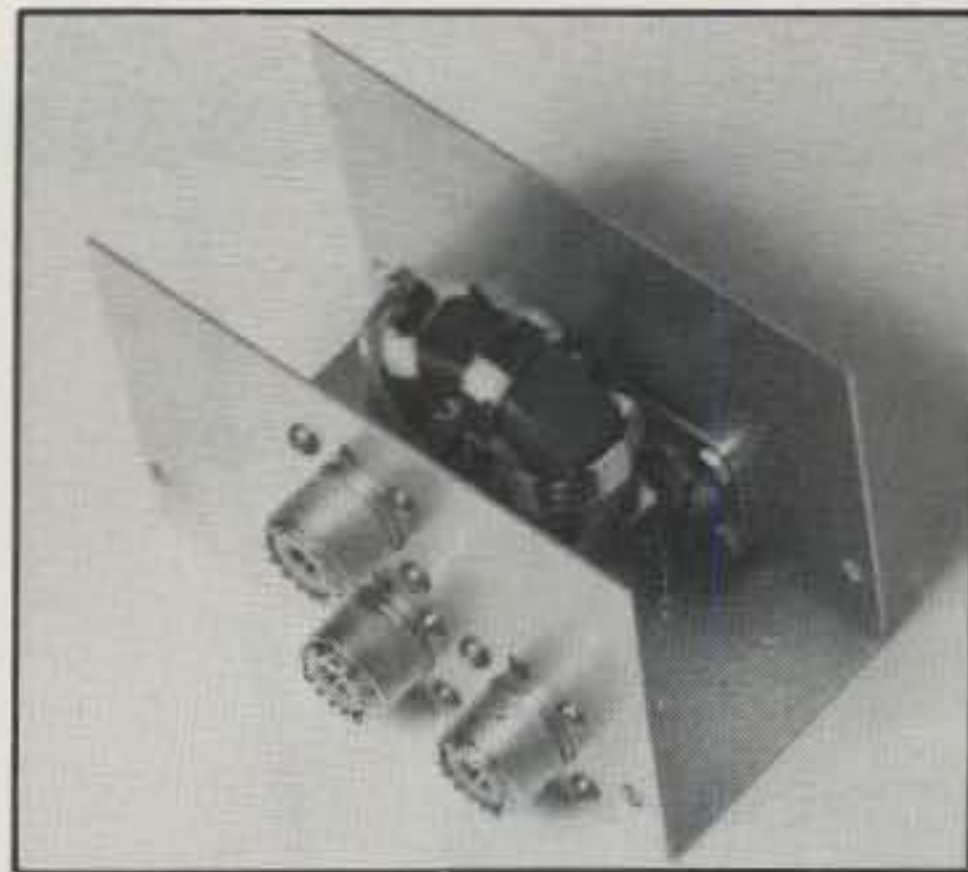


Fig. 3- High-power unit mounted in a 4" L x 2" W x 2.75" H CU-3015A minibox.

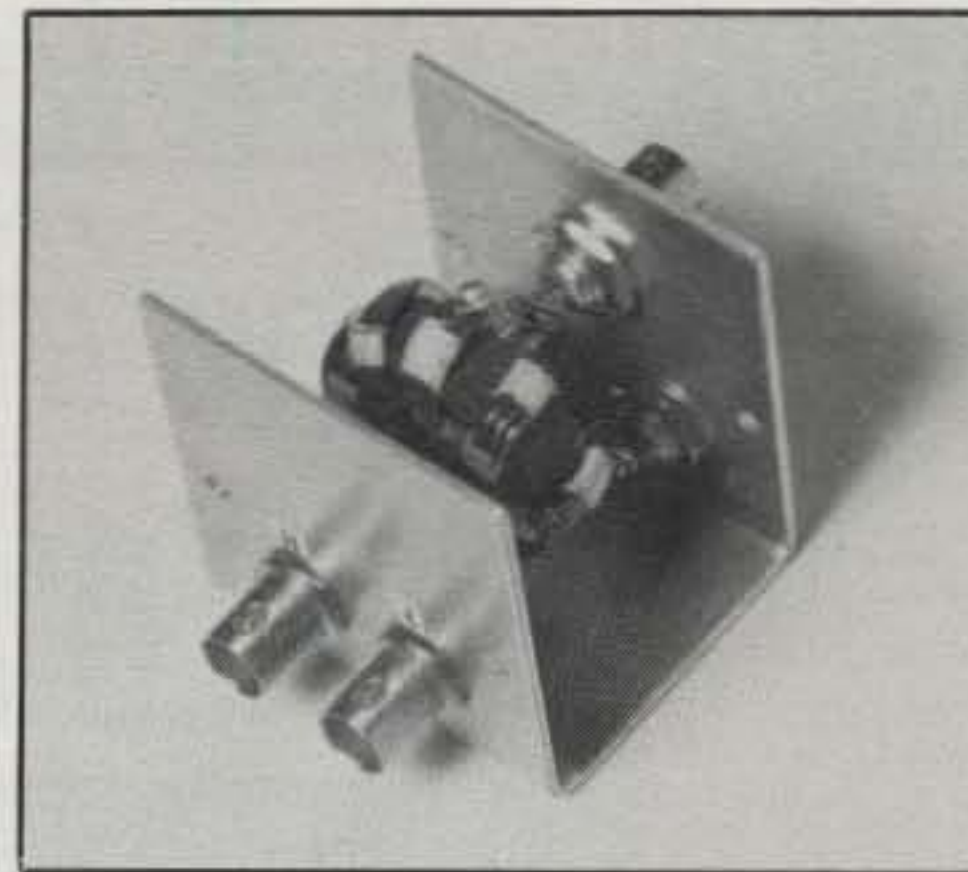


Fig. 4- Low-power unit mounted in a home-made 2" L x 1.5" W x 2.25" H minibox.

output is at terminal A to ground, then the output voltage is

$$V_o = V_i + V_i(n/2N) = V_i(1 + n/2N) \quad (\text{Eq 1})$$

where

N = the total number of turns on the winding

n = the number of turns from terminal 5

The transformation ratio, e , then becomes

$$e = (V_o/V_i)^2 = (1 + n/2N)^2 \quad (\text{Eq 2})$$

If the input voltage to ground, V_i , is connected to terminal L, then terminal C has twice the voltage of V_i , resulting in a 4:1 ratio. Terminal B has three times the voltage, resulting in a 9:1 ratio. With terminal A, the output voltage is

$$V_o = 2V_i + V_i(n/N) = V_i(2 + n/N) \quad (\text{Eq 3})$$

The transformation ratio, e , then becomes

$$e = (2 + n/N)^2 \quad (\text{Eq 4})$$

A High-Power 5-Ratio Unun

After several attempts at rearranging the windings of fig. 1(A) for best overall performance (optimizing the effective characteristic impedances of the windings), fig. 1(B) evolved. Fig. 2 shows the bottom view of an unun, using the circuit of fig. 1(B), capable of handling the full legal limit of amateur radio power. Fig. 3 shows the unit mounted in a CU-3015A minibox. It has five trifilar turns on a 1.5 inch OD ferrite toroid with a permeability of 250. Winding 5-6 is tapped at two turns ($n = 2$) from terminal 5.

If the 9:1 ratio matching 50 ohms to 5.6 ohms (connection B-L) is to be used at full power, then winding 3-4 should be No. 12 H Thermaleze wire. If not, then all windings can be No. 14 H Thermaleze wire.

A listing of the expected performance across the band from 1.7 MHz to 30 MHz, with the various ratios, is as follows:

9:1 (B-L); 50:5.6 ohms
Ratio is within 1 percent!

the Original ULTIMATE PADDLE
We Didn't invent CW. We Perfected It.

- Non-Skid Feet
- Stainless Steel Adjustable Spring for Different Fists
- Nylon & Stainless Self Adjusting Needle Bearings
- Gold Plated Solid Silver Contact Points
- Large Clear Plastic Handles
- Unmatched Responsiveness

Write or Call for Brochure

BENCHER, INC.
831 N. Central Ave., Wood Dale, IL 60191
708/238-1183 FAX 708/238-1186

Made in U.S.A.

CIRCLE 54 ON READER SERVICE CARD

SURVEILLANCE
COUNTER SURVEILLANCE Electronic Devices
Mini Transmitter Kits.. \$39.95 ppd., Voice Changers, Vehicle Tracking, Touch Tone Decoders, Phone Scramblers, Caller ID's, Scanners, Bug & Phone Tap Detectors & More!

TELEPHONE RECORDING SYSTEM • 10 hour extended play (5 hours per side), complete \$149.95 ppd.

FOR CATALOG SEND \$5.00 TO...
E D E P.O. Box 337, Buffalo, NY 14226 (716) 691-3476

SATELLITE T.V.
Factory Direct to Your Door
EchoStar • Startrak • Houston Tracker • Orbitron

24 Hr. Pricing Hotline 516-763-6842

- Call for FREE Huge Color Catalog
- Domestic & International Systems
- Huge Savings!

Info & Orders **ECHOTRAK™ 305-344-6000**
4749 NW 98th Lane • Coral Springs, FL 33076

New Amateur Publications

Radio/Tech Modifications 5A & 5B
Expanded RX /TX Modifications & alignment controls
Vol 5A for Kenwood, Icom & Scanners
Vol 5B for Alinco, Standard, Yaesu,
\$ 19.95 each CB's & others

Federal Government Frequency Assignments
A must for scanner listeners
Frequency use assignments for Departments of Agriculture, Air Force, Army, Commerce, Defense, Energy, Health and Human Services, Housing and Urban Development, Interior, Justice, Labor, Navy, State, Treasury, and Transportation. Also 29 Independent Agencies \$ 24.95

North American Shortwave Frequency Guide
.5 - 30 MHz listing of all shortwave activity, listed in frequency order.
International Broadcasts from around the world, Military and Public services. All broadcast modes. The most handy reference \$ 19.95 book for the band scanner.

artsci
Add \$ 4.00 Shipping to all orders in USA

3rd Edition \$ 24.95
Federal Government Frequency Assignments
This has all the stuff you would want to read. This has all the stuff you would want to hear. This has all the stuff you would want to hear.

CLASSIFIED

Artsci inc
P.O. Box 1848
Burbank, CA 91507
(818) 843-4080
Fax (818) 846-2298

CIRCLE 140 ON READER SERVICE CARD

**PERFORMANCE, FEATURES
AND QUALITY...**

FROM

TOKYO HY-POWER

WORLD'S FIRST!

3 HF Bands in ONE Handheld

Enjoy operating 7, 21, and 50MHz SSB/CW with the HT-750. Now you can truly take HF with you anywhere! Many features include:

- 3W Out on 40M and 15M
- 2W Out on 6M
- Digital Readout
- Noise Blanker
- Internal CPU Controller
- RX Preamplifier
- RIT Knob
- S-RF Meter
- Uses Common Batteries
- Size 2.5(W)x7.4(H)x1.8"(D)



VHF AMPLIFIERS

HL-37Vsx 2 Meter amplifier for FM/SSB HT's. Puts out 30W. Built-in variable RX preamplifier. LED power level indicator. Only .5 to 5W of input required. Other 2M models up to 350W output available.



UHF AMPLIFIERS

HL-36U All mode 30W amplifier for 70 cm. GaAs FET preamplifier built-in. LED power level indicator. Input power is 1 to 12W. Other models up to 230W output available.



DUAL BAND AMPLIFIERS

HL-724D 2M and 70 cm dual band amplifier. Output power is 25W. Built-in RX preamplifier. Advanced cross-band full duplex function. Input power is .3 to 6W. Model HL-728D with 100W output is available.



TRANSVERTERS

HX-650 Connect to transverter terminal of your HF transceiver to convert from 28MHz to 50MHz. Output power is 50W. Dual function RX preamplifier built-in. Model HX-240 converts 2M to HF bands.



**ORION
BUSINESS
INTERNATIONAL, INC.™**

360 W. Bedford Ave. Suite 111 Fresno, CA 93711

Tel: **209-432-4155**

Fax: **209-261-0662**

Contact your dealer or Orion for more information. Full line catalog available.

5.75:1 (A-L); 50:8.7 ohms

Ratio decreases by 5 percent.

4:1 (C-L); 50:12.5 ohms

Ratio increases by 15 percent (the greatest deviation of all the ratios).

2.25:1

a. (B-H); 50:22.22 ohms

Ratio decreases by 4 percent.

b. (H-B); 50:112.5 ohms

Ratio increases by 8 percent.

1.44:1

a. (A-H); 50:35 ohms

Ratio decreases by 10 percent.

b. (H-A); 50:72 ohms

Ratio increases by 2 percent.

Several comments should be made regarding the expected results shown above. First of all, the greatest deviation from a flat response at any ratio occurs when matching 50 ohms to 12.5 ohms (connection C-L; a 4:1 ratio). If an accurate insertion-loss measurement was made at this ratio and impedance level, the result would show an insignificant difference across the band. Second, the major part of the deviations for all ratios occurs beyond 15 MHz (the effect of standing waves). And finally, the higher ratios should never be used to match 50 ohms to 450 ohms, 288 ohms, and 200 ohms, respectively. The characteristic impedances and choking reactances do not allow for broadband operation under these conditions.

A Low-Power 5-Ratio Unun

Fig. 4 shows a low-power unit mounted in a homemade 2"L x 1.5"W x 2.25"H mini-box. It has six trifilar turns of No. 16 H Thermaleze wire on a 1.25 inch OD ferrite toroid with a permeability of 250. The tap on winding 5-6 is at three turns from terminal 5, yielding ratios of 6.25:1 and 1.56:1 instead of the 5.75:1 and 1.44:1 ratios of the high-power unit. In actual use, these differences should be negligible.

Since this unun has shorter transmission lines than its high-power counterpart, the deviations of the ratios across the band are even less. Also, it is interesting to note that if No. 14 H Thermaleze wire was used in winding 3-4, this very small unun could well be rated at 500 watts of continuous power!

Footnotes

1. Sevick, J., *Transmission Line Transformers*, 2nd ed., Newington: ARRL, 1990.

2. Ruthroff, C. L., "Some Broadband Transformers," *Proceedings of the IRE*, Volume 47, August 1959, pages 1337-1342.

3. Kits and finished units available from Amidon Associates, Inc., 2216 East Gladwick Street, Dominguez Hills, CA 90220.