

Fig. 1. The two high-Q loading coils shown here are important factors in the operation of this versatile antenna.

a Six Band Mobile Antenna

HARTLAND B. SMITH, W8VVD

467 Park Ave., Birmingham, Mich.

In This Article a Well Known Author Describes the Step by Step Construction of a Novel and Efficient Multi-Band Antenna

The number of amateur mobile installations which include band-switching transmitters has recently shown a marked increase. However, despite the ease with which gear of this type can be shifted from one frequency to another most mobileers still operate on only one band. This is true because the process of altering the resonant frequency of a loaded mobile antenna is usually so complicated that the average Ham shies away from the task.

After building a multi-band transmitter and installing it in my car I was faced with this same dilemma. I wanted to work several different bands, but I didn't care to load the trunk compartment with numerous coils and wrenches just so I could change the operating frequency of the antenna.

The most convenient way to have solved the problem would have been to construct an antenna with a remotely operated bandswitch controllable from the driver's seat. Unfortunately, most switching schemes that I could devise put too much metal near the loading coil and seriously reduced its Q. Although not remotely switched, the mobile antenna I finally settled for is relatively inexpensive to construct, works well on all Ham bands from 3.7 Mc. to

29.7 Mc. and can be changed from one frequency range to another with a minimum of inconvenience. It is truly a six-band mobile antenna.

The most efficient mounting position for a mobile antenna is reputed to be in the center of the car's roof. Trees, trolley wires and XYL's, however, make it impossible for the majority of amateurs to utilize such a location. Bumper mounting may be slightly less efficient, but it was decided on because it is certainly much more practical.

Total length, including loading coils, is slightly more than 8 feet. Although a longer antenna would work somewhat better on 75 meters, the 8-foot length was chosen as a good compromise between performance and appearance.

The Base Sections

As shown in *Fig. 2*, the lower part of the antenna is a 13" length of $\frac{3}{4}$ " galvanized pipe which is fastened, by means of fiber insulators, to a bumper bracket of aluminum angle. A floor flange on the threaded top of this pipe provides a solid foundation for a body-mount style of antenna spring. Placing the spring

part way up the antenna results in greater mechanical stability, thus reducing antenna sway while the car is in motion. This is an important factor when two loading coils are made a part of the radiating system.

Threaded into the spring is the bottom 4½" of an Army surplus AN-131-A antenna. Although the lower portion of any mobile whip can be used at this point, the section of AN-131-A works out nicely because its fairly large diameter helps to provide good support for the rest of the antenna.

One end of a 12" length of 1" diameter polystyrene rod is drilled to a depth of 2" to accept the short piece of AN-131-A. A 14" section of ⅜" dural tubing is next cut and fitted into a hole drilled for it in the top end of the 12" poly rod. Another poly rod, 11" long, is drilled on the lower end to provide a tight fit with the dural tubing. The top 4 feet of a good spring steel mobile whip is then placed in a hole drilled at the top of the 11" poly rod. To insure that the sections of antenna are held firmly together, a number of 6-32 set screws are placed in holes drilled and tapped for them in the poly rods, as shown in Fig. 5.

The operating frequency of the antenna can

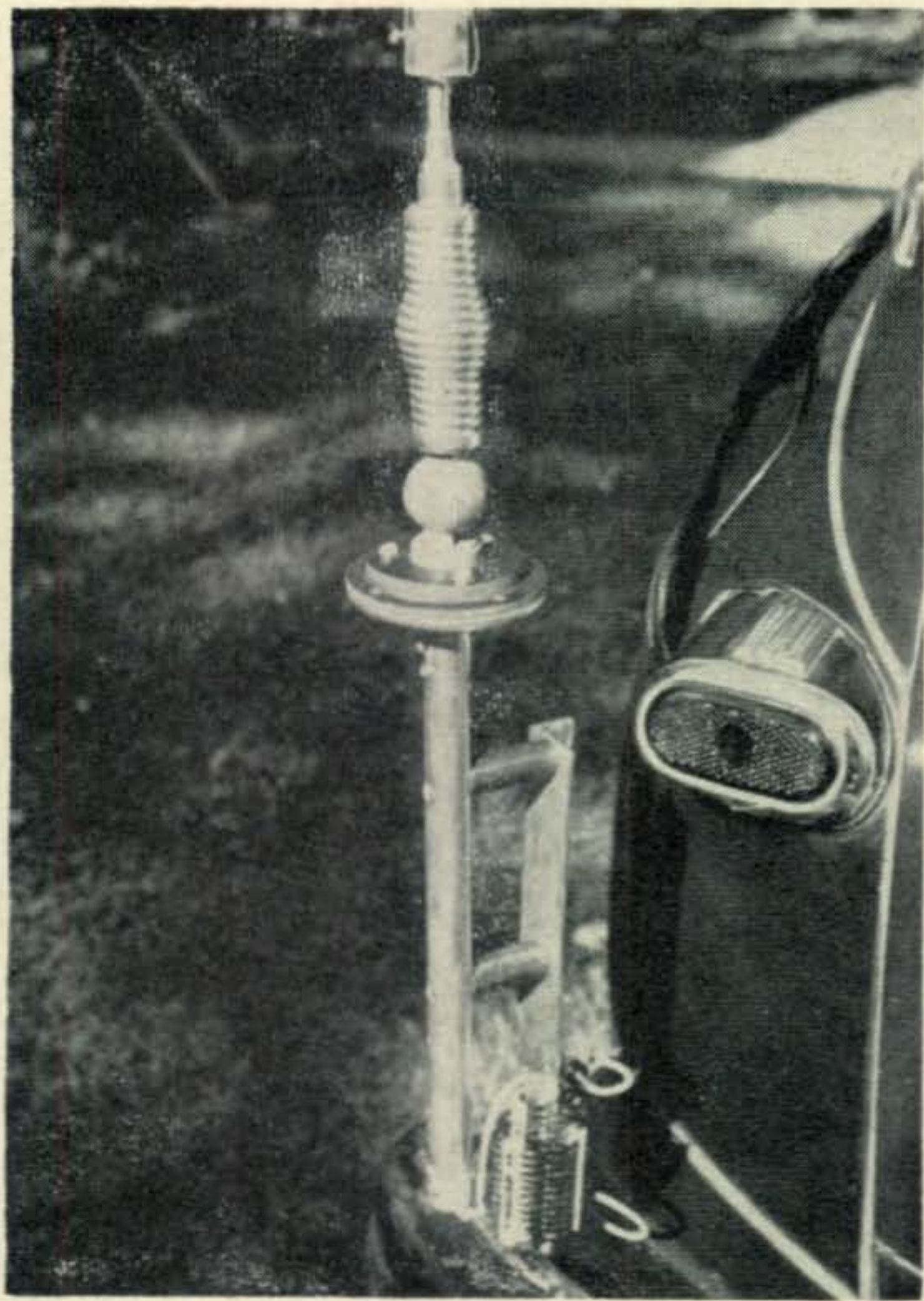


Fig. 2. A floor flange, atop a 13-inch length of ¾-inch galvanized pipe, provides a suitable location for the body mount type of antenna spring. A ¼-inch thick fiber disc acts as a shim between the spring mount and the flange to provide adequate clearance for the stud protruding from the bottom of the mount.

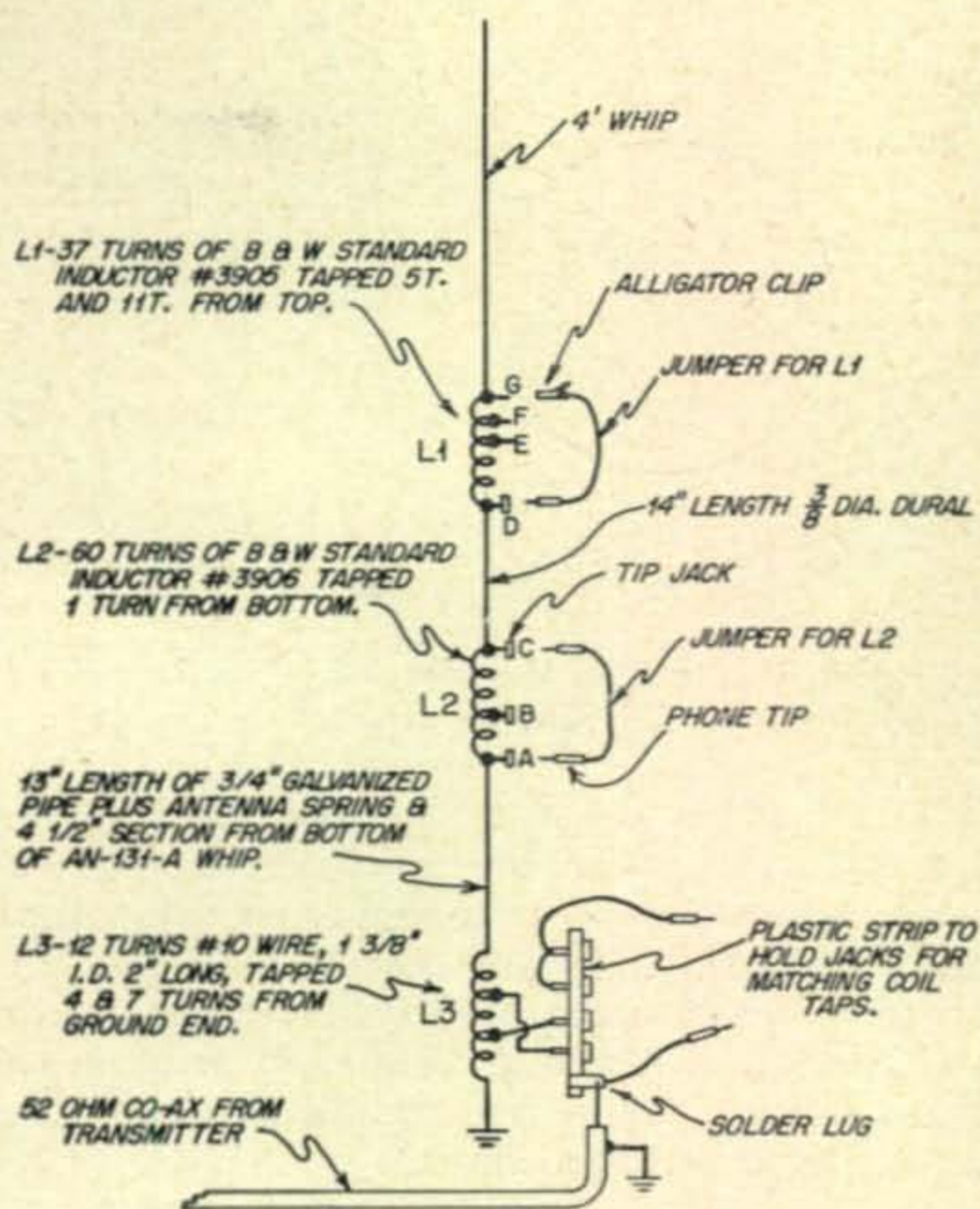


Fig. 3. Wiring schematic of the antenna.

be changed by shorting either $L1$ or $L2$ with a couple of 12" jumpers made from test lead wire. One jumper should have phone tips on both ends while the other jumper should have a phone tip on one end and an alligator clip on the opposite end. The jumper with two phone tips is for use with $L2$. The one with an alligator clip is for $L1$.

Making the Coil Formers

Four 2 ⅝" diameter discs with 1" center holes are cut from ¼" sheet polystyrene. The discs slip over the poly rods and help to hold the loading coils in place. Holes must be drilled in the discs for the screws that fasten the plastic mounts of the shorting jumper tip jacks. These mounts can be 4 pieces of ¼" polystyrene, ¾" by 1" in size. A hole just large enough to accommodate a tip jack should be drilled in each of these pieces. A smaller hole that can be tapped to take the 6-32 screw which fastens the mount to the plastic disc should be drilled in one edge of each mount. A drop of polystyrene cement put on this edge of the mount, just before it is screwed to the disc will provide a good strong bond between the two pieces of plastic. The tip jacks, by the way, should contain strong springs which firmly grip the tips of the shorting jumpers to provide good, low resistance contacts.

When working with polystyrene, patience is very important. Without it, Ole Man Friction will heat your tools to the point where the plastic melts into a sticky, unmanageable goo. A supply of water should be kept on hand for cooling drills and saws.

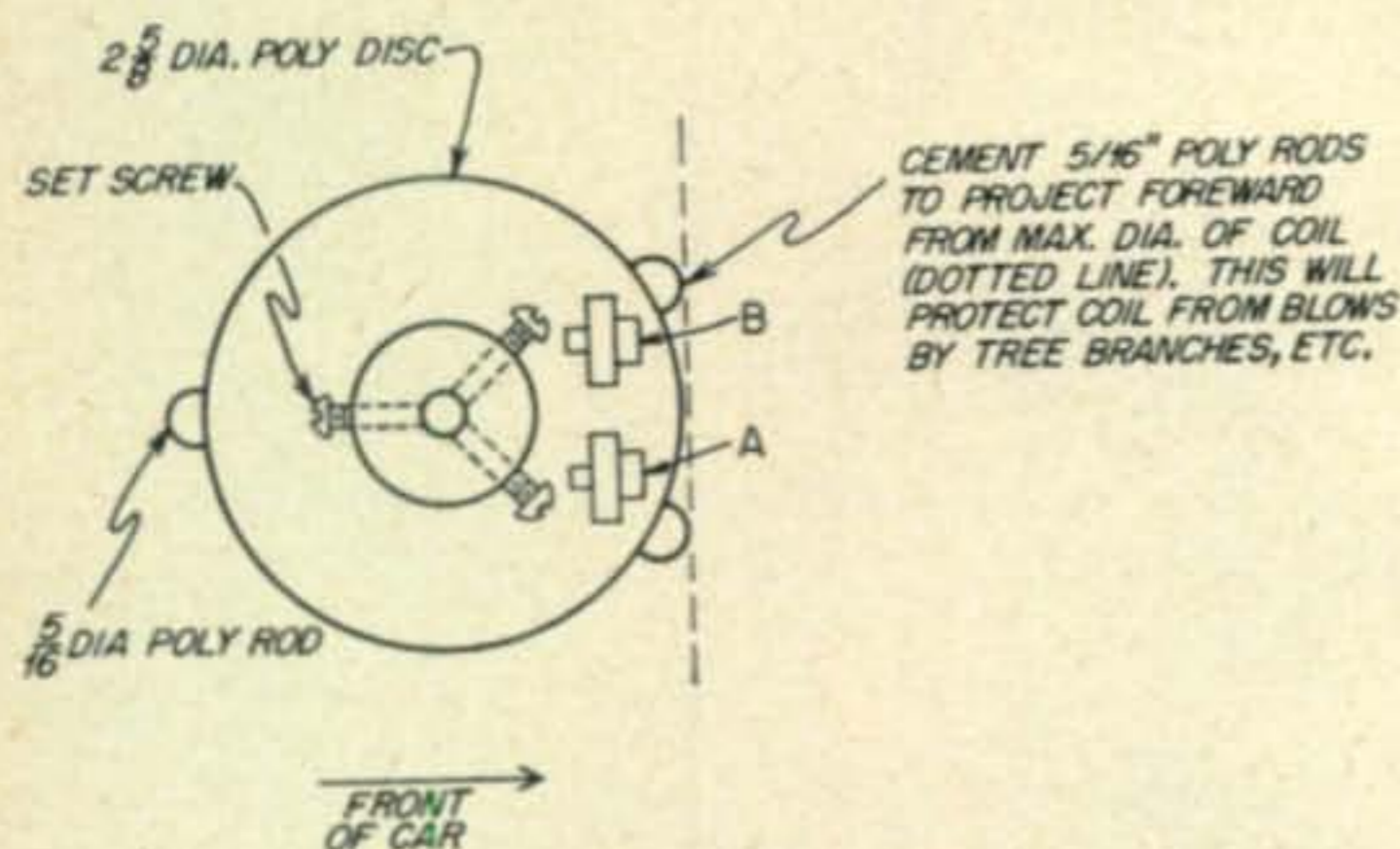


Fig. 5. This is a bottom view of L2 to show the positions of the rods to strengthen the coils.

The loading coils are modified B&W standard inductors. For preliminary tune-up purposes, be on the safe side and leave a few more turns on them than are shown in Fig. 3. The exact inductance required differs with each installation, and it is much easier to prune a coil that's too long than it is to add turns to a coil that's just a little too short.

Matching the Antenna

Matching the antenna to the coaxial feed line is accomplished by means of a small tapped coil, L3, connected between the base of the antenna and the car body ground. This coil can be closewound with 12 turns of #10 wire using a size D flashlight cell as a form. After the coil is wound, remove it from the battery and carefully stretch it to a length of 2". The coil may then be strengthened, as shown in Fig. 4, by cementing thin plastic strips to it.

The importance of this base matching coil can hardly be overemphasized. It answers the problem of incorrect loading which so often is encountered with pi-network finals operating on 40 and 75 meters. Furthermore, a matching coil makes possible the use of an inexpensive standing wave bridge to correctly resonate the antenna and produce a very low standing wave ratio on the feed line.

As can be seen in the photographs, the matching and loading coils are exposed to the weather. Normal precipitation has had little effect on the antenna and so no protective covering appears necessary for the inductance. It takes a very heavy downpour to put the unit so far out of resonance that it is no longer possible to load the transmitter on 75. Operation on the other bands is little affected by anything short of a deluge.

All exposed metal parts should be protected from the weather. The 3/4" pipe and pipe flange can be given a coat of aluminum paint. The screws, and other pieces of hardware may be protected by spraying them with Krylon. The plating of these items isn't always too good and so the liquid plastic is used to help keep them from rusting.

Do not attempt to tune the antenna by

guesswork. Either a standing wave bridge¹ or an Antennascope² must be employed during the process of adjustment if satisfactory performance is to be obtained.

Mount the antenna on the car with the loading coils temporarily held in position between the plastic discs by means of Scotch tape. The discs, in turn, should be taped to the plastic rods to keep them from slipping down during the preliminary tune-up. Once the antenna is working properly, the discs and coils may be permanently cemented in place. At the same time three 5/16" polystyrene rods should be cemented to each coil as shown in Fig. 5 to provide a certain amount of mechanical protection. The rods can be so positioned that they will help to absorb any blow from a tree branch or other obstruction which may be encountered when the car is in motion.

One satisfactory method of antenna tune-up employs a standing wave bridge as shown in Fig. 6. With the antenna temporarily disconnected from the output of the bridge, feed in just enough r.f. to give a full scale reading on the indicator meter. If your mobile rig can't be decoupled sufficiently to prevent overloading the meter, some other source of low power

1. "Bridge Construction," p. 480, The Radio Amateur's Handbook, 30th edition, 1953.
2. Scherer, W. M.: "Building and Using The Antennascope," CQ, September, 1950.


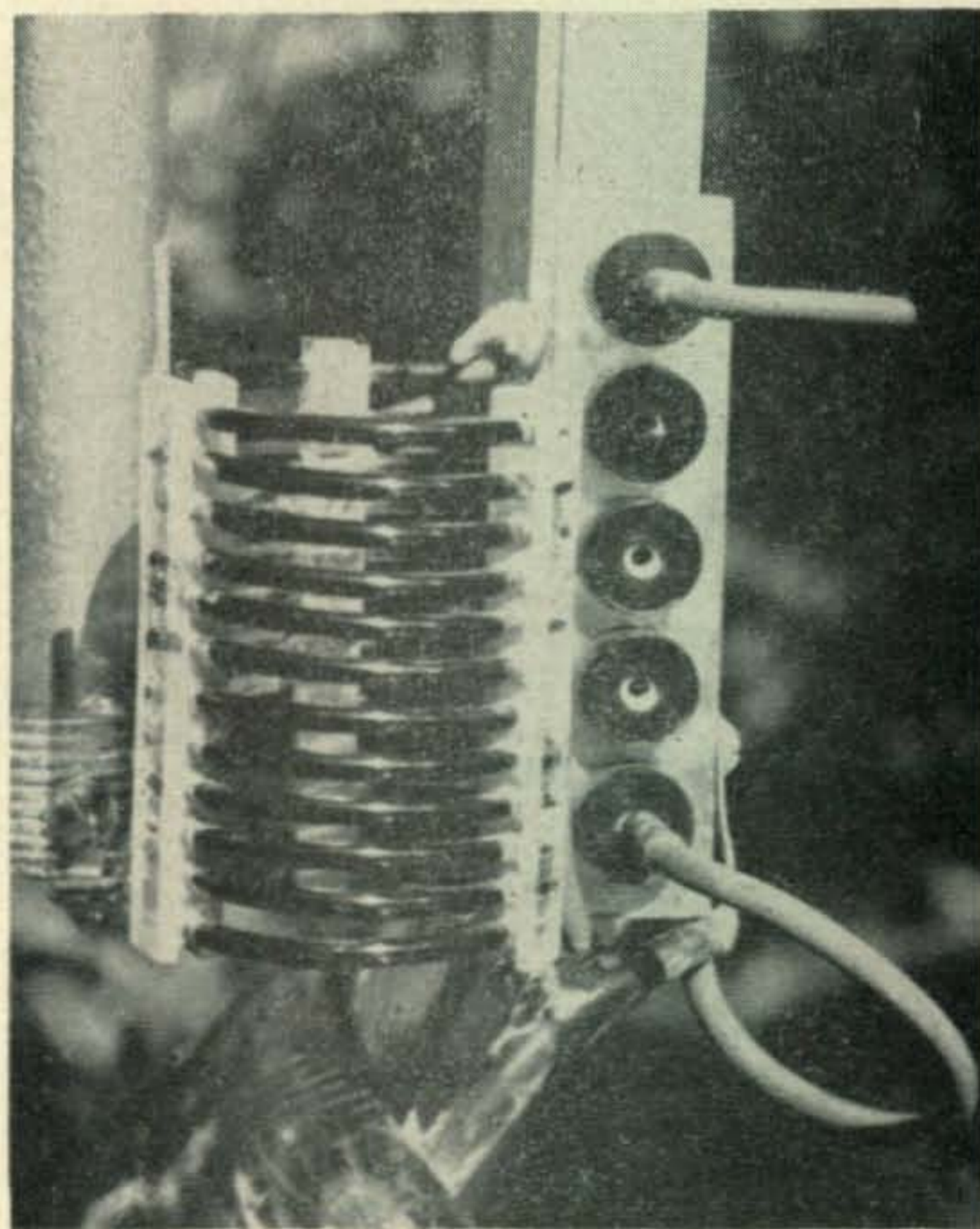


Fig. 4. Careful examination of this closeup will reveal that matching coil, L3, is mounted upside down. The top is grounded to the aluminum angle mounting bracket, while the bottom is connected to the base of the antenna. The center tip jack on the plastic strip to the right of L3 is not used, and so may be omitted by the constructor.

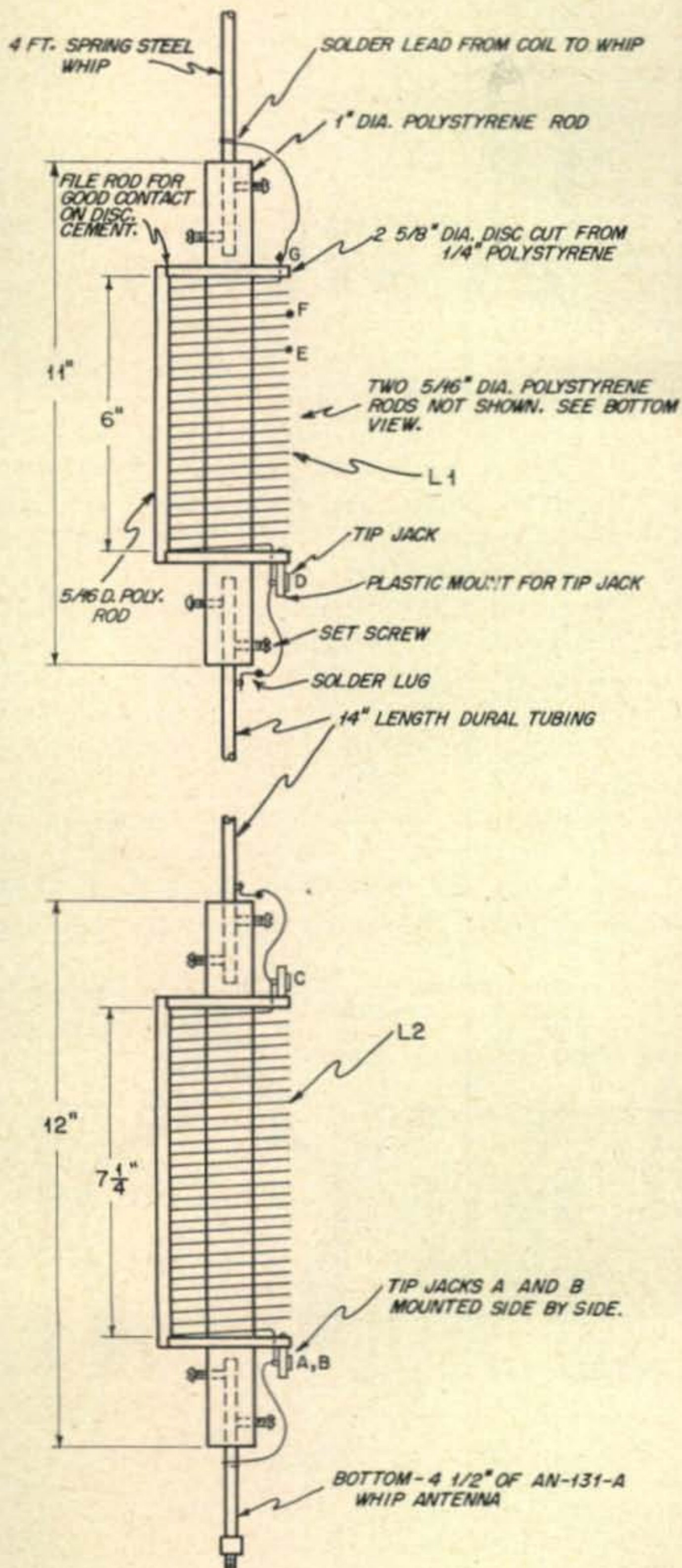

Mechanical assembly details of the antenna.

r.f. will have to be found. In my case, Command transmitters, a BC-458 for 75 and a BC-459 for 40 and 20, were pressed into service. When powered with a small a-c supply, the output from one of these rigs can be made very low by reducing the coupling to minimum and, at the same time, slightly detuning the final plate condenser.

Once the indicator reads full scale, the coaxial lead from the antenna may be attached to the output terminal of the bridge. The meter reading will drop, but it won't go to zero. Short the bottom loading coil, L_2 , and set the matching coil for 40 meters. Plug the jumper with an alligator clip into the jack in the base of the upper loading coil, L_1 . Using the jumper,

start at the bottom of L_1 and short out a turn or two. Note the reading on the standing wave indicator and then short out a few more turns. After several trials, some point will be found where the reading on the meter will drop to zero. This denotes antenna resonance and a correct match between the feed point resistance of the antenna and the coaxial line. If no position can be found where the meter goes all the way to zero, move the 40-meter tap on the matching coil, L_3 , up or down a turn or two and repeat the shorting process on L_1 . When the meter finally reads zero, disconnect the alligator jumper and remove almost all turns which had to be shorted out on L_1 . Then, carefully prune the coil a turn at a time until the antenna is resonant at 7250 kc. as shown by a zero reading on the standing wave meter.

Tuning Up on 75 Meters

Disconnect the antenna and feed enough power at 3850 kc. to the bridge to produce a full scale reading. Reconnect the antenna and set matching coil, L_3 , for 75 meters. Leave L_1 unshorted, and plug the alligator clip jumper into the jack at the bottom of L_2 . Proceed to tap up on this coil until a resonant condition is noted. As with the 40-meter adjustment, it may be necessary to make a slight change in the position of the matching coil tap before exact resonance can be achieved.

If you wish to operate at a higher frequency in this band, you can tap up one or two turns from the bottom of L_2 and bring this tap out to another tip jack at the coil's base. By plugging a jumper between this tap and the bottom of L_2 the resonant frequency of the system will be raised a number of kilocycles. Another method for QSYing on 75 is to resonate the antenna near the high frequency end of the band. Then a short pigtail may be clipped to the whip where it emerges from the top of L_1 . The added capacity of the pigtail will lower the resonant frequency by a significant amount.

To tune the radiator for 20 meters, disconnect the antenna and feed r.f. to the bridge at

(Continued on page 62)

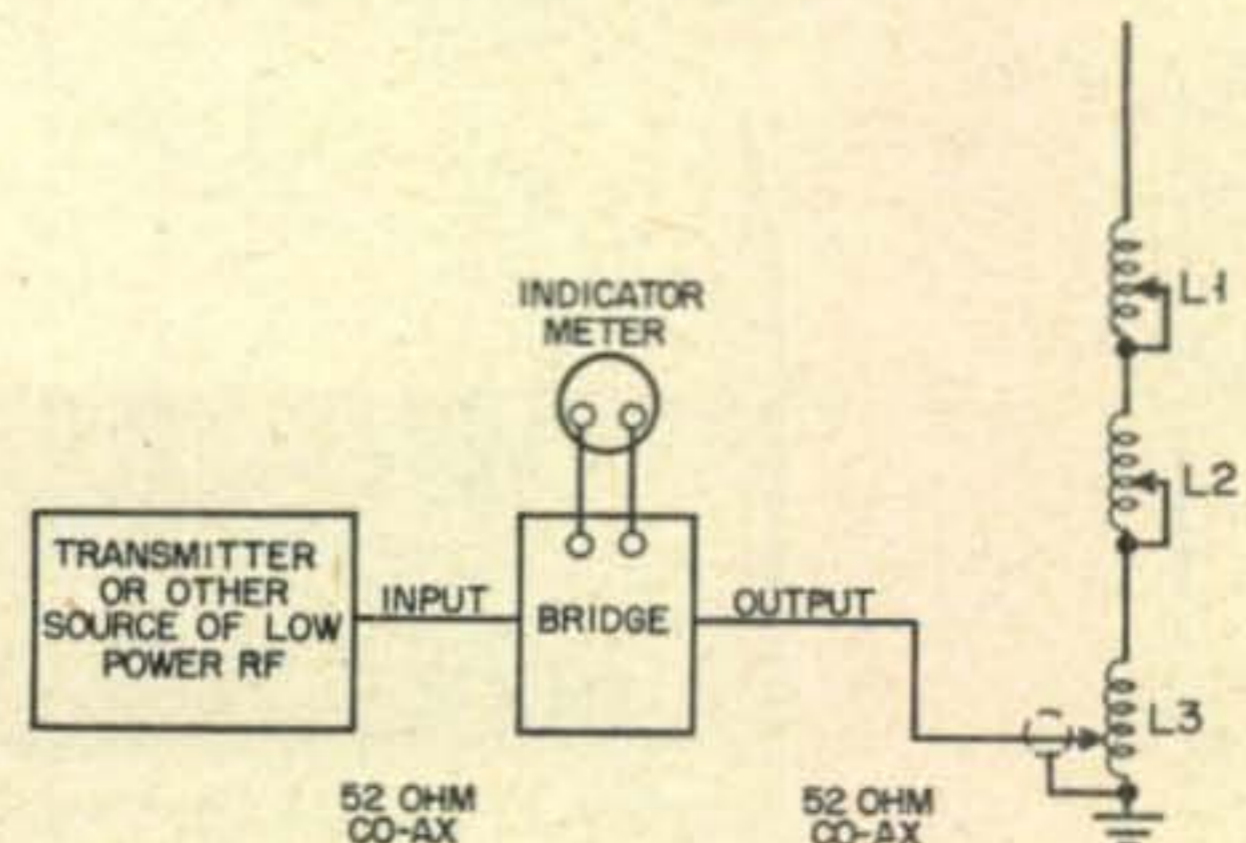


Fig. 6. Block diagram showing the connections to VSWR bridge during the tune-up process.

EVANS RADIO

10 Hills Avenue
Concord, New Hampshire

has **hallicrafters**



- 10 Kc to 250 cycles in six steps!
- The most stable receiver made!
- Single Side Band Suppressed Carrier!

The Hottest Ham News in Years!

See complete details on pages 4-5


THE HALLICRAFTERS CO • CHICAGO 24, ILL.

6 - BAND ANTENNA

(from page 31)

a frequency of 14,250 kc. Reconnect the antenna and short *L2* with the appropriate jumper. Plug the alligator jumper into the jack on *L1* and set the matching coil, *L3*, for 20 meters. Run the alligator clip up and down *L1* until resonance is indicated by a zero reading on the bridge indicator. As soon as the optimum tap position is located, solder a loop of wire on *L1* at this point. Then, whenever 20-meter operation is desired, the alligator may be clipped to the same spot with no difficulty.

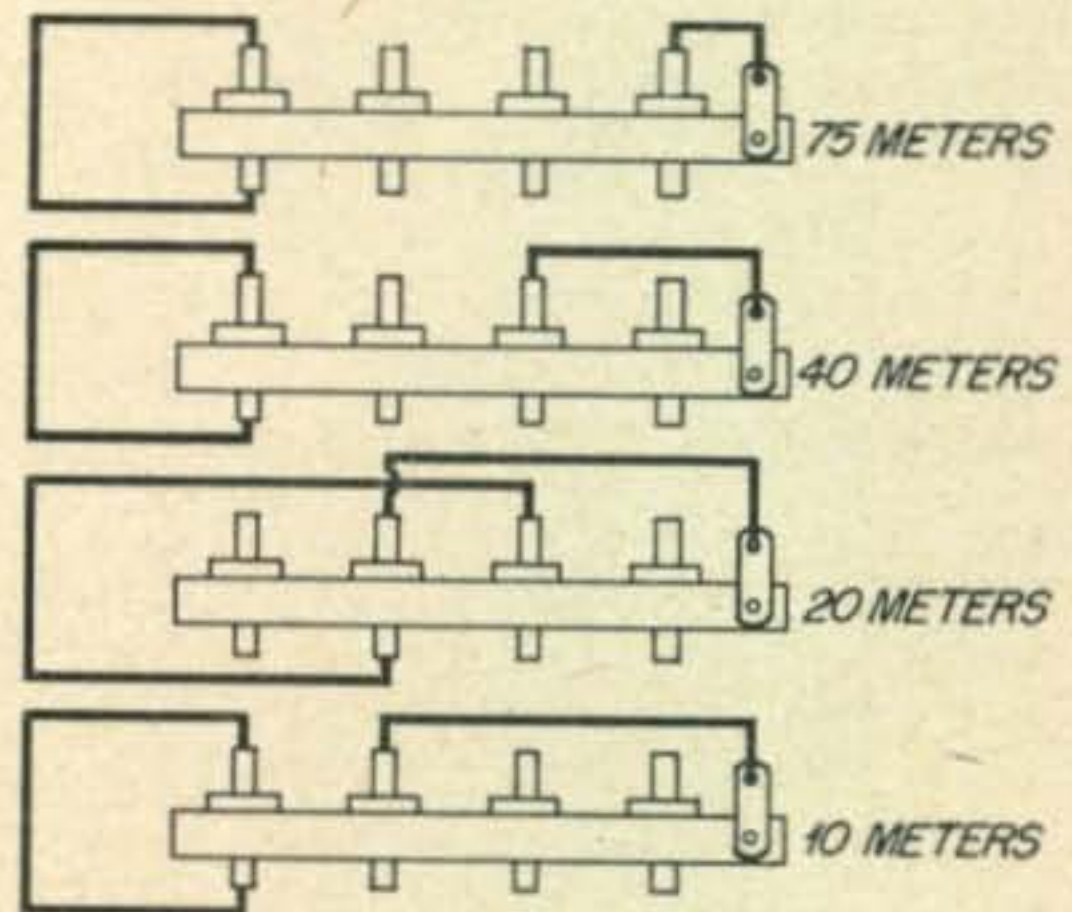The adjustment for 15 meters is quite simple. Put the matching coil on the 10-11-15 meter position. Remove the bridge from the circuit and feed 15-meter energy directly from the transmitter to the antenna. Find the tap position on the top coil which provides maximum



This sketch shows the correct positions of the jumpers on *L3*, the matching coil at the base of the antenna. Compare this drawing with Figures 3 and 4.

field strength as shown on a nearby sensitive field strength meter tuned to 21 Mc. As with the 20-meter tap, solder a loop of wire at this point so that it may be easily identified in the future.

No loading coil adjustment is required for either 10 or 11 meters. On both of these bands *L1* and *L2* are completely shorted out.

A word of caution regarding the foregoing adjustments is in order. Before tuning the antenna make sure that the trunk lid is closed and that the whip is fairly well in the clear—well away from power wires and tree limbs.

Since installing this multi-band antenna, I've overheard numerous comments regarding it and have been asked a great many questions about it. Wide-eyed youngsters inquire if I have TV in my car, while curious Hams are anxious to know if the contraption works.

(Continued on page 64)

QUARTZ CRYSTALS

Low Frequency — FT-241A for SSB, Lattice Filter etc., .093" Pins, .486" SPC, marked in Channel Nos. 0 to 79, 54th Harmonic and 270 to 389, 72nd Harmonic. Listed below by Fundamental Frequencies, fractions omitted.

49¢ each—10 for \$4.00						99¢ each—10 for \$8.00	
370	393	414	436	498	520	400	459
372	394	415	437	501	522	440	461
374	395	416	438	502	523	441	462
375	396	418	481	503	525	442	463
376	397	419	483	504	526	444	464
377	398	420	484	505	527	445	465
379	401	422	485	506	529	446	466
380	402	423	486	507	530	447	468
381	403	424	487	508	531	448	469
383	404	425	488	509	533	450	470
384	405	426	490	511	534	451	472
385	406	427	491	512	536	452	473
386	407	429	492	513	537	453	474
387	408	430	493	514	538	454	475
388	409	431	494	515		455	476
390	411	433	495	516		456	477
391	412	434	496	518		457	479
392	413	435	497	519		458	480

99¢ each—10 for only \$8.00

CR-1A SCR 522— $\frac{1}{8}$ " Pin, $\frac{1}{2}$ " SP	FT-171B — BC-610 Banana Plugs, $\frac{3}{4}$ " SPC					
5910	7350	2030	2220	2390	3120	3520
6370	7380	2045	2258	2415	3150	3550
6450	7390	2052	2260	2435	3155	3570
6470	7480	2065	2280	2442	3202	3580
6497	7580	2082	2282	2532	3215	3945
6522	7810	2105	2290	2545	3232	3955
6547	7930	2125	2300	2557	3237	3970
6610		2131	2305	2660	3250	3995
		2145	2320	2940	3322	
		2155	2360	3035	3510	

BC 746 TUNING UNITS—
foundation coils and condensers
for 80 meter VFO or exciter—
less xtals 98¢



520 TENTH ST., N.W.—Wash., D. C. Dept. C

FT-243—.093" Pin Dia.—
.486" Pin SPC for Ham and
General Use

49¢ each—10 for \$4.00

4035	5500	5950	6725	7525	7840
4080	5675	5973	6740	7540	7850
4110	5677	5975	6750	7550	7873
4165	5700	6225	6773	7573	7875
4190	5706	6240	6775	7575	7900
4255	5725	6250	6800	7600	7906
4280	5740	6255	6806	7606	7925
4300	5750	6273	6825	7610	7940
4397	5760	6275	6840	7625	7950
4450	5773	6300	6850	7640	7973
4490	5775	6306	6873	7641	7975
4495	5800	6325	6875	7650	8206
4780	5806	6335	6900	7673	8225
4845	5825	6340	6906	7675	8240
4930	5840	6350	6925	7700	8250
5030	5850	6373	6940	7706	8273
5205	5852	6375	6950	7720	8275
5235	5873	6400	6973	7725	8300
5250	5875	6406	6975	7740	8306
5300	5880	6425	7450	7750	8325
5305	5900	6673	7473	7773	8630
5333	5906	6675	7475	7775	8683
5385	5925	6700	7500	7800	8690
5485	5940	6706	7506	7825	

99¢ each—10 for \$8.00

1015	2605	3995	6575	7273	8175
1110	2738	6000	6600	7275	8200
1150	2785	6025	6606	7300	8340
1525	2895	6050	6625	7306	8350
1915	2940	6073	6640	7325	8375
1930	3005	6075	6650	7340	8380
1940	3010	6100	7000	7350	8400
1950	3202	6106	7006	7375	8425
2065	3215	6125	7025	7400	8430
2105	3237	6140	7040	7425	8450
2118	3245	6150	7050	7440	8460
2125	3250	6173	7073	8000	8475
2140	3460	6175	7075	8006	8483
2145	3500	6200	7100	8025	8500
2305	3540	6440	7106	8040	8525
2320	3590	6450	7125	8050	8550
2390	3640	6473	7140	8073	8575
2415	3680	6475	7150	8075	8583
2430	3720	6500	7173	8100	8600
2442	3735	6506	7175	8106	8625
2460	3760	6525	7200	8125	8650
2532	3800	6540	7206	8140	8700
2545	3840	6550	7225	8150	8733
2557	3885	6573	7240	8173	

add 20¢ post. for ea. 10
xtals (or less)

R.C. & L.F. HALL, INC.

Radio & Television Parts

Distributors of Electronic Equipment Supplies

HOUSTON GALVESTON TEXAS CITY BEAUMONT
 1301 Polk at Caroline 4414 Broadway 523 7th Ave. 1135 Park
 Phone: Capital 9731 Phone: 3-1656 Phone: 4-7740 Phone: 5-7577

has **hallicrafters**



- 10 Kc to 250 cycles in six steps!
- The most stable receiver made!
- Single Side Band Suppressed Carrier!

The Hottest Ham News in Years!

See complete details on pages 4-5

THE HALLICRAFTERS CO • CHICAGO 24, ILL.



110V, AC POWER SUPPLY FOR ANY 274-N RECEIVER

Just plug it into the rear of your 274-N RECEIVER . . . any model. Complete kit and black metal case, with ALL parts and diagrams. Simple and easy to build in a jiffy. Delivers 24 volts plus B voltage. No wiring changes to be made. Designed especially for the 274-N receiver. **Only \$8.95.**

Filament trans. for 274N receivers. Pri. 110V, 60 cy. AC. Sec. 24V @ .6A. An excellent buy at **\$1.95 ea.**

SPLINED TUNING KNOB FOR 274N RECEIVERS

An exclusive O-R item manufactured for us. Fits BC-453, BC-454 and other 274N receivers. This is a really hard-to-obtain item. **Only .89c ea.**



OFFENBACH-REIMUS

1564 Market Street, San Francisco, Calif.

LEARN WITH AMECO COURSES

BECOME A RADIO AMATEUR

Simple, Low Cost, Home-Study Courses prepare you to pass F.C.C. Code and Theory Examinations for Amateur license and Code for Commercial license. Sold at leading distributors or write for information to

AMERICAN ELECTRONICS CO.
 (Dept. C-2) New York 59, N. Y.

1203 Bryant Ave.

(from page 62)

Despite a transmitter input of only 15 watts, the antenna does a good job on the bands for which it is designed. Most contacts made on 75 are of a ground wave nature with reports equal to or better than those given nearby mobiles employing single-band commercially built trans-

FREQ. KCS	L1	L2
3850	NO JUMPER	NO JUMPER
3950	NO JUMPER	JUMPER FROM A TO B
7250	NO JUMPER	JUMPER FROM A TO C
14250	JUMPER FROM D TO E	JUMPER FROM A TO C
21350	JUMPER FROM D TO F	JUMPER FROM A TO C
27000	JUMPER FROM D TO G	JUMPER FROM A TO C
28750	JUMPER FROM D TO G	JUMPER FROM A TO C

Loading coil tap positions for various frequencies in the six amateur bands.

mitting antennas. When conditions have been favorable, satisfactory 75 meter QSO's have been made at distances up to 250 miles.

Almost all 40-meter contacts are with stations more than 300 miles away. Reports have ranged from S5 to S9. Although not too much 20-meter operation has been attempted, a number of excellent ground wave contacts have been made. Little skip has so far been worked. It seems as though every time I try 20 it is either dead or else is loaded with DX. Neither condition is good for long haul mobile work.

At those times when 15 and 10 are open, QSO's via skip can be had with little difficulty. Due to lack of activity on the band, no 11-meter work has, up to now, been attempted.

If you've been looking for an inexpensive, efficient and highly versatile mobile antenna—one which can be constructed with ordinary hand tools—this 6-band job should adequately meet your requirements. Build it and enjoy the fun denied those unfortunate fellows whose antennas restrict them to one narrow segment of the radio spectrum.

TEST EQUIPMENT

(from page 29)

the coils, for overlapping bands, and the calibration. The coil winding problem can be reduced somewhat by the use of a circuit such as that shown in Fig. 1. With this type of circuit the coils require no taps or secondaries, which makes pruning easy. For the low ranges almost any pie or bank wound r-f chokes may be used as tuning coils. To isolate the output and give greater stability the oscillator may be followed by a cathode-follower type amplifier.

Calibration

Even though we have reduced the headache of coil winding, calibration is still a difficult