Number 18 on your Feedback card

Five-Band Magnetic Loop Antenna

Build a loop for QRP, and tune it up just right!

Francis Y. Kelson K2KSY/HL9BK PSC 450, Box 0826 APO AP 96206-0826

many years, but one of the problems faced by builders today is the acquisition of suitable variable capacitors. Having tried ARCO trimmer caps which overheated on the higher frequencies, I decided to use coaxial cable, since it has the inherent capacity and voltage

he magnetic loop has been used | protection needed for a 5 W-plus QRP successfully worldwide for signal. All coaxial cable has a specific capacitance per foot value, so it's a simple matter to calculate the length needed for a given capacitance. Also, its light weight maintains the loop's integrity. With propagation conditions getting better by the day, this little device should lend itself quite well to the

QRP purist, or to the person who just wants to SWL or listen to his favorite net. Supplemented with a long wire antenna for the 3.5, 7.0 MHz bands, its noise-canceling ability should make for a good copy.

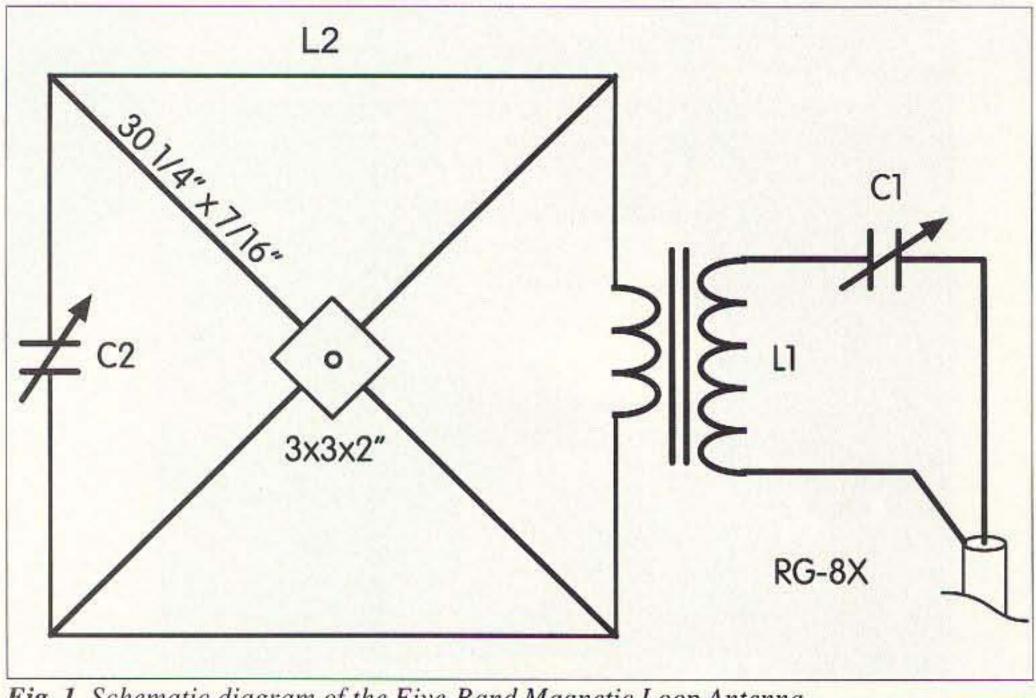


Fig. 1. Schematic diagram of the Five-Band Magnetic Loop Antenna.

18 73 Amateur Radio Today • January 1998

Construction

The loop consists of three parts. Printed circuit board 1 (PCB1) tunes the loop to the coaxial input. PCB2 mounts the desired capacitance on the other side of the loop. The loop itself (L2) is supported on a framework of crossed dowels.

Cut four 7/16-inch dowels to 31.5 inches each, and make a 1/16-inch slot in one end of each dowel. Shellac the dowels and set them aside to dry.

You'll need a block of wood for the hub, three inches square and two inches thick. Drill a 7/16-inch-diameter hole into the middle of each side of the block, to a depth of 1-1/4 inches. I also drilled a 1/4-inch hole through the center of the block for mounting. Shellac the block and set it aside to dry.

When the unslotted ends of the dowels are inserted into the hub, they should measure 30-1/4 inches from the hub's outer edge to the dowel tips.

Cut two segments of #22 audio wire, each 7 feet, 4-1/4 inches long. Strip 1/8 inch of insulation from each of the wires' four ends; tin each end with solder. Solder a Caltern[™] ring terminal, common to auto wiring (the #22-18 Red are suitable), to each end of the wires.

Prepare two single-clad PCBs as depicted in **Figs. 2** and **3**. You may use something else, just as long as you keep the separation for L2 the same as shown, or else you may have trouble keeping L2 taut with the dimensions shown.

The coaxial input is L1, toroid T 68-7 White, wound with #24 enamel wire 25 turns, spaced approximately one millimeter apart. The secondary winding is prepared by winding the #24 enamel wire for a total of six turns, encompassing at least three-quarters of the toroid's primary. This will approximate a 75-ohm input, which is easily matched up with the RG-8X coax.

Remove the insulation from the toroids' four leads, and solder to PCB 1 (**Fig. 2**). Solder C1 across the copper traces on PCB1 as shown.

At this time you may want to apply coil dope or clear fingernail polish to coil L1.



Note that the negative PCB trace continues along a path beneath C1, so don't mount C1 flush against the PCB.

Mount the ring terminals of the audio wire to PCB1 and PCB2, using 6-32 x 1" screws, nuts, and washers. Use three nuts on each PCB, so that removal of L2 will be easy later on.

Insert the dowels into the hub, and align the wire on the dowels as shown in Fig 1.

You may remark on the fact that, worked out by the formula for determining cross-arm lengths, one quarter of L/ 7071 = 63.50 inches, but ours is 64 inches. This gives us a slight bow to the loop for rigidity—and it also looks nicer that way.

To build the various capacitors, you will need approximately five feet of RG-174U mini coaxial cable, plus a little extra to play with. Cut all coax as specified by the chart for your frequency of choice.

On each piece of coax, measure off one inch, and remove the outer insulation. Bend the coax at the point where

				Amps		
a state and	NE	The second value of		mhz 400watts		
	3 3	1	220	nhz 225watts		
			440	nhz 185watts		
Pin	Pout	IC _	Gain/N	F (+13.8V)		
(W)	(W) ((A) (dB) (dB) Type		
1.5	10.50	E	15/0 7	LPA		
1-5				Standard		
1		1000	15/0.7	CnDty/cc		
10	1000		15/07	Standard		
	10000	111 A	-	CnDty/cc		
	2010.04		15/0.7	HPA		
	171 C 1 175		-	CnDty/fan		
and the second		1.00	15/0.7	HPA		
1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1			-	CnDty/fan		
1-5	10-50	6	15/0.7	LPA		
1-2	100	14	15/0.7	Standard		
5-10 1	60-200	28	15/0.7	Standard		
5-10 1	60-200	28		CnDty/cc		
25-45 1	60-200	22	15/0.7	Standard		
25-45 1	60-200	22	-	CnDty/cc		
.255 1		29	-	CnDty/fan		
5-10	and the second s		15/0.7	HPA		
				CnDty/fan		
				HPA		
			-	CnDty/fan		
50-80	350+	40	-	CnDty/fan		
1-5	8-35	5	14/0.8	LPA		
				Standard		
			-	CnDty/cc		
			14/0.8	Standard		
			1000	CnDty/cc		
			14/0.8	HPA		
			Sec. 1	CnDty/fan		
10-25			14/0.8	HPA		
10-25	225	36		CnDty/fan		
75	225	32		HPA		
75	255	32		CnDty/fan		
Sarde 1	TENNER		-	The section of the se		
				LPA		
			12/1.2	Standard		
				CnDty/cc		
			12/1.2	Standard		
			-	CnDty/cc		
			12/1.2	HPA		
			1011.0	CnDty/cc		
			12/1.2	HPA CoDtu/loo		
			104 0	CnDty/fan HPA		
			121.2			
			22	CnDty/fan		
1. 1. The State of				CnDty/fan		
Description Size Wt Connector LPA=Low-power amp 3x6x5 4lbs UHF						
Standard=Mobile/Base 3x6x11 6lbs UHF or M						
HPA=High-power amplifier 3x10x11 9lbs UHF or N						
CnDty/cc=Cont-duty/rack-mt 4x12x19 17lbs UHF or N						
	and the second se			/forced-air		
	Pin (W) 1-5 1 10 10 5-10 2-6 25-40 25-40 25-40 25-40 25-40 25-40 25-40 25-40 25-45 5-10 25-45 5-10 2-6 10-25 10-25 50-80 1-5 5-10 2-6 10-25 10-25 50-80 1-5 5-10 2-6 10-25 10-25 50-80 15-10 25-45 5-10 2-6 10-25 10-25 50-80 15-10 25-45 5-10 2-6 10-25 10-25 50-80 10-25 10-25 50-80 10-25 50-80 10-25 10-25 50-80 10-25 10-25 50-80 10-25 10-25 10-25 50-80 10-25	Pin Pout WW WW 1-5 10-50 1 170 1 170 1 170 10 170 10 170 10 170 10 170 10 170 10 170 10 170 10 170 10 170 10 170 10 170 10 170 10 170 5-10 375 25-40 375 25-40 375 25-40 375 25-40 375 25-40 375 25-40 375 25-45 160-200 25-45 160-200 25-45 160-200 5-10 350+ 10-25 350+ 10-25 350+ 10-25 225	Pin Pout Ic (W) (W) (A) 1-5 10-50 6 1 170 28 1 170 28 10 170 25 10 170 25 5-10 375 59 2-6 375 54 25-40 375 54 25-40 375 54 25-40 375 54 25-40 375 54 25-40 375 54 510 160-200 28 25-45 160-200 22 25-45 160-200 22 25-5 160-200 22 25-45 130 20 5-10 350+ 56 10-25 350+ 50 10-25 350+ 50 5-10 130 20 25-45 130 16 25-45 130 16	PLIFIERS 220 Pin Pout Ic Gain/N (W) (W) (A) (dB) (dB) 1-5 10-50 6 15/0.7 1 170 28 - 10 170 25 15/0.7 10 170 25 - 5-10 375 59 15/0.7 2-6 375 59 - 25-40 375 54 15/0.7 2-6 375 54 - 1-5 10-50 6 15/0.7 25-40 375 54 - 1-5 10-50 6 15/0.7 25-40 375 54 - 15/0.7 2-6 350+ 5 25-45 160-200 22 - 25-5 160-200 22 - 25-5 160-200 22 - 5-10 350+ 5 14/0.		

3/4" -L1 COAX IN

Fig. 2. PCB1 (approximately 2-1/4" x 1-1/2") provides mounting for the input circuit.

the outer insulation now meets the braid. With a sharp-pointed instrument, push aside the braid until the center conductor is exposed; extract it from the braid, leaving two terminal leads each one inch in length. Tin each tip lead, and solder on a ring terminal.

According to **Table 1**, measure off the specified length, from the junction of the braid and center conductor to the coax tip. Hold it! Despite what the chart specifies, add one inch to each coax. You will use this extra length to compensate for the area density (capacitive effect) in which you will place your loop for operation. I tuned mine in the shack. When I moved it out to the patio there was no change, but this will vary depending on your own surroundings. A 500 pF trimmer was used for the 3.5 MHz band, since the length of coax needed would have been quite long enough. However, this limits the power on this band to only a couple of watts.

If you elect to use the trimmer capacitors for all bands and are going to use two watts or less, just drop me an SASE if you're unsure of values and tuning, and I will be glad to explain it.

Tuning the loop

Connect your RG-8X mini coax to the loop's input as in Fig 2. You can use just about any length—I've used 16 to 50 feet in various situations. Connect the free end of this coax to an MFJ-249 SWR Analyzer. At this point you should have the capacitor of choice mounted securely to PCB2.

Search the analyzer for a frequency that obtains a dip. With the added one inch of coax, your frequency should be somewhat lower than expected. Then adjust C1 for the best dip possible. C1 will pull the loop's resonance point a little higher in frequency, so adjust the analyzer a little higher in frequency, and you will note that the SWR is getting lower. Start to trim your RG-174 coax, about 1/8 of an inch at a time, until you are very close to the frequency selected, and repeat the procedure:





Model 1410G

Model 1452G

Description: All amplifiers (non-rptr) are linear, all-mode with fully automatic T/R switching and PTT capability. The receive preamps use GaAs FET devices rated at .5 db NF with +18dbm 3rd order IP. LPA, Standard and HPA amps are intermittent duty design suitable for base and mobile operation. Continuous-Duty(repeater amps) are class C and convection-cooled(cc) or fan-cooled(fan).

Amplifier capabilities: High-power, narrow or wideband; 100-200 MHz, 225-400MHz, 1-2 GHz Military (28v). Also full Commercial line available - consult factory.

RX Preamplifiers(Low-Noise)

Freq	Model	NF (dB)	Gain (dB)	Connector
50 MHz	0520B	0.5	25	BNC
50 MHz	0520N	0.5	25	N
144 MHz	1420B	0.5	24	BNC
144 MHz	1420N	0.5	24	N
220MHz	2220B	0.5	22	BNC
220MHz	2220N	0.5	22	N
440MHz	4420B	0.5	18	BNC
440MHz	4420N	0.5	18	N
1.2GHz	1020B	0.9	14	BNC
1.2Ghz	1020N	0.9	14	N Send for Catalog
				d directly for further products made in USA
-	Concession in	TESY	STEMS	TEL (310)478-059

TE P.O. Box 25845 FAX (310)473-4038 Los Angeles, CA 90025

CIRCLE 232 ON READER SERVICE CARD

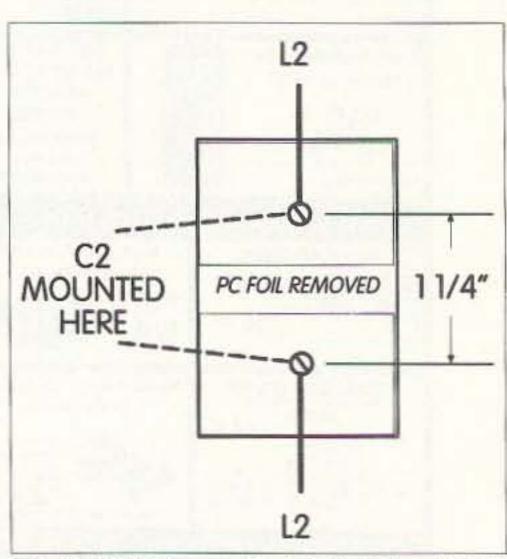


Fig. 3. PCB2 (approximately 2-1/4" x 1-3/4") connects the various capacitors to loop L2.

1. Check frequency for a dip.

2. Adjust C1 for a dip.

3. Check frequency again.

4. Trim coax, recheck frequency. Repeat steps 1 through 4.

Once all your coax caps are resonant, simply roll the larger lengths of coax over two fingers and secure with a rubber band or tie-wrap. The 18 and 21 MHz capacitors are short enough to just hang freely.

Once C1 is optimized, for purity an antenna coupler can be used despite C1 being in series. Since the loop's bandwidth is about 50 kHz, the antenna coupler will allow wider frequency variations.

Desired Frequency	Length of Coaxial Cable
7.0 MHz	26-1/8 inches
14.0 MHz	5-3/4 inches
18 MHz	3-1/8 inches
21 MHz	1-5/8 inches
3.5 MHz	1 each Arco trimmer 500 pF

Table 1. RG-174U chart.

A wattmeter or SWR meter placed at the input of the loop should reveal a flat SWR when full power is applied. If it doesn't, retune the coupler and retouch C1. Proper tuning is the key to success when using an antenna of this type. Use of a field-strength meter or neon lamp is a great help, too. For operation outdoors, a couple of plastic pill bottles can be slipped over PCBs 1 and 2.

Seal the coax caps with Shoe $Goop^{TM}$, or cement, at their tips and terminal junctions.

If you cannot beg, borrow, or acquire an MFJ-249 SWR Analyzer, you could use a grid dip meter to acquire resonance, and with the application of very little RF power, obtain a roughly suitable SWR.

I have accomplished QRP DXCC, WAC QRP, and 1,000 miles per watt with Argentina using one watt of power. I also have 40 states confirmed, using mostly wire and loop antennas.

See the FUN you've been missing!



Every day more and more hams are enhancing their enjoyment of ham radio by adding images to their conversations. Join the fun!

new Pasokon TV Lite \$30 + \$3 shipping. *Pasokon TV* Classic \$200 + \$5 shipping.

> Absolute Value Systems 115 Stedman St. #7 Chelmsford, MA 01824-1823 (508) 250 0611

http://www.ultranet.com/~sstv

CIRCLE 351 ON READER SERVICE CARD

