


Here's a good weekend project that will get you up and running on 30 meters.

How To Build a 80 And 30 Meter Trapped Dipole


BY CHARLES C. BURKE*, WA2SLK

A few weeks ago I picked up my soldering pencil and went to work on my rig to add the 10 MHz, 30 meter band to it. The conversion was a success, but now an antenna was needed to go with it. I tried running it on my 80 meter dipole, using a tuner, but the results left a great deal to be desired. So, out came the reference texts and a calculator and within a few minutes a trap was designed which, if it worked, would permit operation on both 80 and 30 meters without a tuner. From the calculations it appeared that a good trap could be fabricated by building a tank circuit that would resonate on 10 MHz. This called for an 80 pf capacitor and a 3.2 uh coil. With these figures in mind an expedition was launched into the archaeological junk heap which is made up of old parts and items one buys at hamfests, then can't figure out what to do with them later. Armed now with a fist full of parts, and the plan, a simple prototype trap was fabricated and installed on the 80 meter dipole. The results were good and after a few trial runs the SWR readings were around 1.5-1 on both 30 and 80 meters. The unit was then encapsulated in plastic tubing and installed permanently on the dipole. The total cost ran under \$7.00 and actual fabrication time ran around two hours. Even if you had to buy everything the entire project could be completed for under \$15.00.

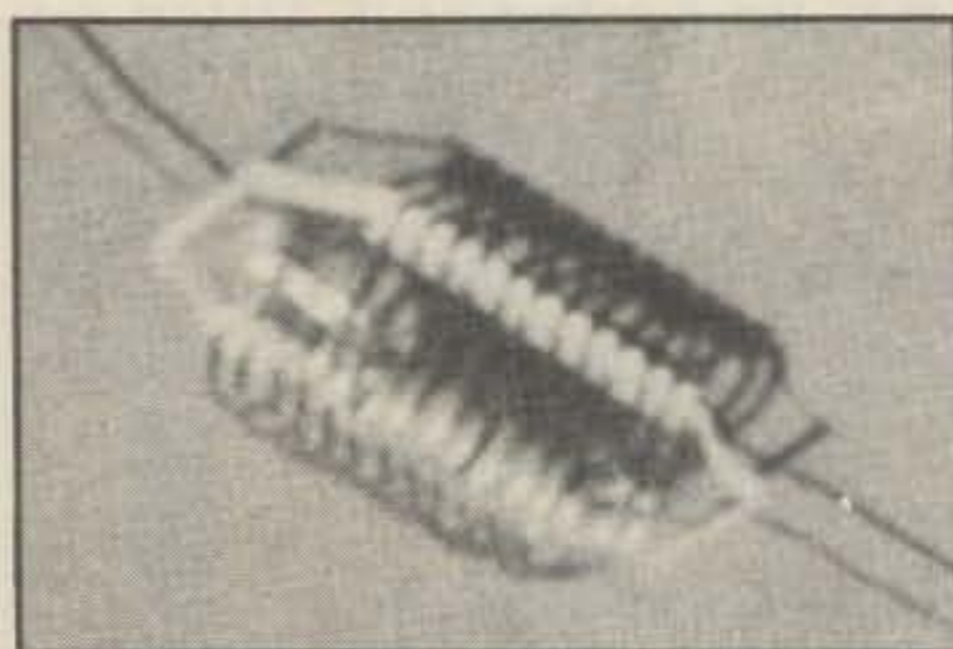The steps needed to build the traps are simple and can be altered to meet the parts you have on hand. Start off by laying




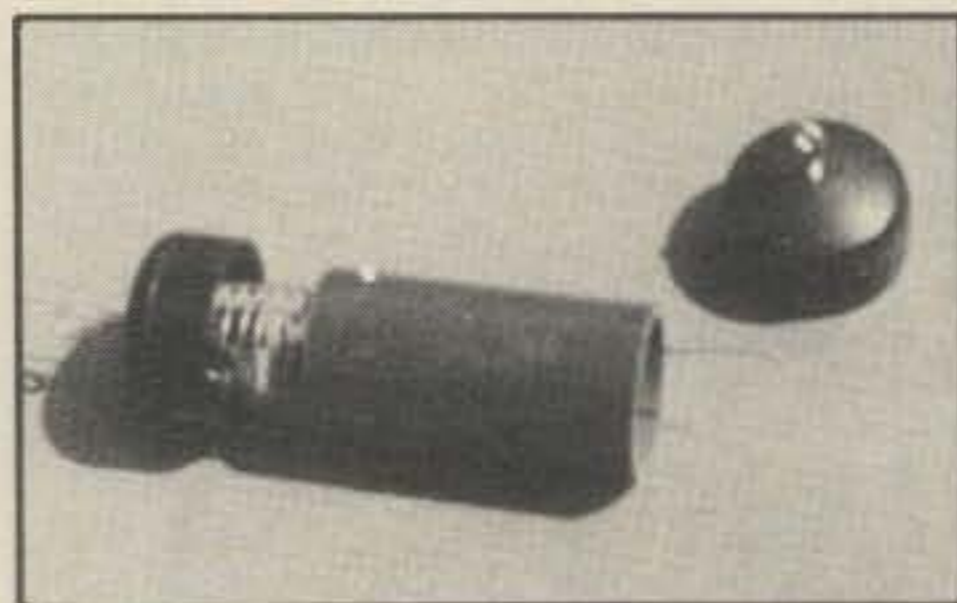The completed coil and capacitor combination.



The coils are inserted in the plastic tubing as shown.

out the pattern on the $\frac{1}{4}$ " plexiglass. The $\frac{1}{2}$ " radius cuts are added only to make treading the coil onto the form easier. Care should be taken to get the grooves even and safety glasses should be worn when doing the actual cutting. I made the slots on a table saw with a blade that was $\frac{1}{8}$ " wide. The coil is fabricated by wrapping the wire tightly around a $1\frac{1}{8}$ " cyclinder. The wire was obtained by stripping some 14 gauge Romex house-wire and the winding form was a bedpost in my daughters room. It is suggested that you

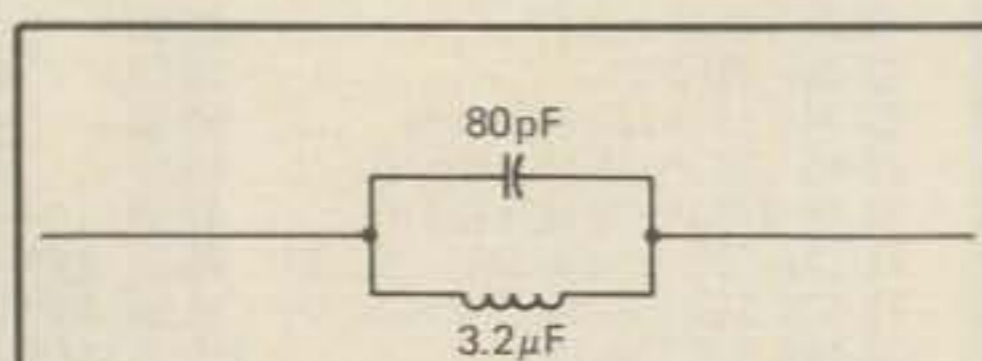

BILL OF MATERIALS

- 2- $\frac{1}{4}$ " \times $4\frac{1}{2}$ " \times 2" plexiglass
- 2-80 pf, 1.5 KV or higher transmitting capacitors (in the unit I built I used a 200 pf and a 150 pf capacitor in series to get approximately 80 pf. This is why two are seen in the picture.)
- 2- $4\frac{1}{2}$ ' lengths of 14 gauge copper wire, solid.
- 4-#6-32 \times 1" round or pan head screws
- 4-#6-32 nuts
- 4- #6 flat washers
- 4-6" lengths of wire about the same gauge as your antenna wire
- 2-4" length of 2" ID plastic pipe
- 4-End caps for 2" plastic pipe AR-Pipe cement
- 4-#8 eye bolts and nuts

Fig. 1- Schematic diagram for the antenna trap. Two traps are required.

get the wire as straight and as smooth as possible, as the coil will be hard to form if the wire is kinked. One way to get it smooth is to pull it over a slightly round edge several times. once you have made about 15 turns let the wire go and it should spring open just a bit. If the coil has about a $1\frac{1}{4}$ " inside diameter then you're in the ball park.

The coil can be easily threaded onto the plexiglass-form by simply turning it. If it doesn't go on easily, try winding the coil in the opposite direction. Once it is in

*RR1 Box 164A
Farmingdale, NJ 07727


NEW from BARKER & WILLIAMSON!

1.8 - 30 MHz. Continuous Coverage Antenna for Commercial and Amateur Service

Model AC 1.8 - 30

The AC 1.8 - 30 Antenna uses only 80 feet horizontally, and, when space is limited, can be shortened even further with only slight loss of radiation efficiency.

Patent Pending

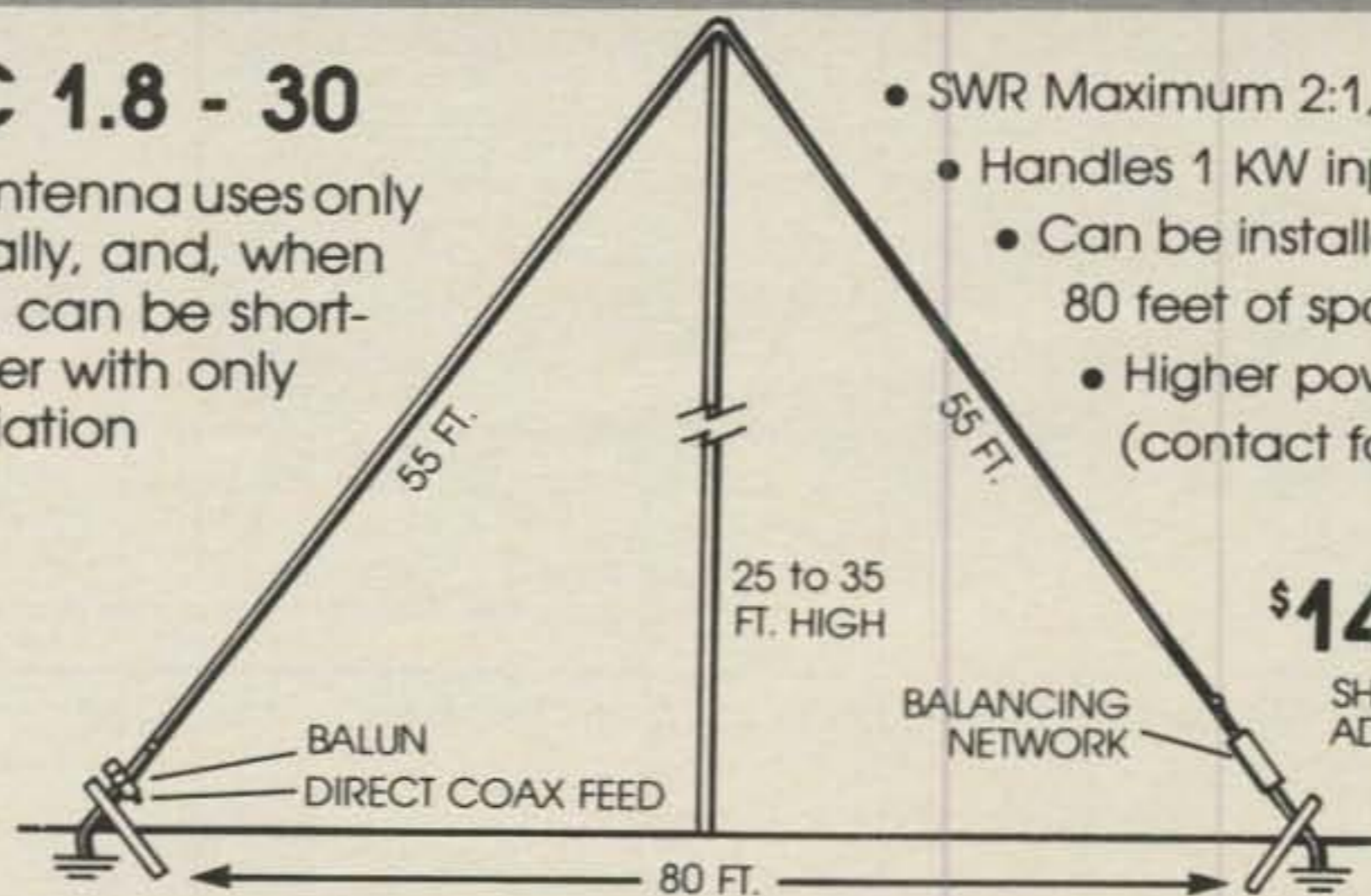

- SWR Maximum 2:1, 1.4:1 Average
- Handles 1 KW input ICAS
- Can be installed in approximately 80 feet of space
- Higher power models available (contact factory)

\$149.50

SHIPPING AND HANDLING ADD \$4.00



BARKER & WILLIAMSON

ALL OUR PRODUCTS MADE IN USA

Quality Communication Products Since 1932

At your Distributors write or call, 10 Canal Street, Bristol PA 19007

(215) 788-5581



FREE new bulletin contains information... to improve your signal coverage...



by eliminating distortion caused by re-radiated signals.

Flexible, electrically transparent Phillystran® guys completely isolate a tower-guy system from the antenna field

These high-performance tower guys eliminate maintenance and the hidden damage caused by white-noise arcing.

They also provide a neater tower appearance with no troublesome ceramic insulators.

Name _____

Street or P.O. Box _____

City _____

State _____

Zip _____



Phillystran®


UNITED ROPEWORKS (U.S.A.) INC.
20 COMMERCE DRIVE, P.O. BOX 306
MONTGOMERYVILLE, PA 18936 U.S.A.
(215) 368-6611 TELEX: 846342

CIRCLE 120 ON READER SERVICE CARD

Say You Saw It In CQ

QUALITY PARTS AT DISCOUNT PRICES!


SUB-MINIATURE D TYPE CONNECTOR

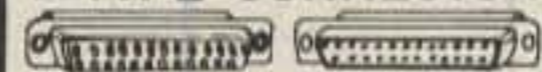

SOLDER TYPE SUB-MINIATURE CONNECTORS USED FOR COMPUTER HOOK UPS.

DB-15 PLUG	\$2.75
DB-15 SOCKET	\$4.00
DB-15 HOOD	\$1.50
DB-25 PLUG	\$2.75
DB-25 SOCKET	\$3.50
DB-25 HOOD	\$1.25

"PARALLEL" PRINTER CONNECTOR

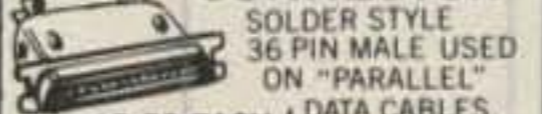

SOLDER STYLE 36 PIN MALE USED ON "PARALLEL" DATA CABLES.

\$5.50 EACH

L.E.D.'S STANDARD JUMBO DIFFUSED

RED	10 FOR \$1.50
GREEN	10 FOR \$2.00
YELLOW	10 FOR \$2.00

FLASHER LED 5 VOLT OPERATION RED JUMBO SIZE \$1.00 EACH

BI POLAR LED 2 FOR \$1.70

CRYSTAL

CASE STYLE HC33/U COLORBURST 3579.545 KC \$1.00 EACH

2 MHZ \$3.50 EA

8" P.A. SPEAKERS



C.T.S. MODEL 8B3079. 8 OHMS COIL. 3.0 OZ FERRITE MAGNET.

TYPICAL RESPONSE RANGE: 100 - 10,000 HZ. POWER: 15 Watt MAX. DRILLED TO MOUNT LINE MATCHING TRANSFORMERS.

\$5.00 EACH. CASE OF 8 SPEAKERS, \$32.00.

SEND FOR **NEW 1985** 48 PAGE CATALOG FREE!

MINIATURE TOGGLE SWITCHES

ALL ARE RATED 5 AMPS @ 125 VAC

S.P.D.T. (on-on) P.C. STYLE. NON-THREADED BUSHING. 75¢ EACH 10 FOR \$7.00	S.P.D.T. (on-on) SOLDER LUG TERMINALS. \$1.00 EACH 10 FOR \$9.00 100 FOR \$80.00
S.P.D.T. (on-off-on) P.C. LUGS. THREADED BUSHING. 75¢ EACH 10 FOR \$7.00	S.P.D.T. (on-on) P.C. LUGS. THREADED BUSHING. \$1.00 EACH 10 FOR \$9.00 100 FOR \$80.00

SOLID STATE BUZZER

STAR #SMB-06L 6 VDC. TTL COMPATIBLE \$1.00 EACH 10 FOR \$9.00

120V INDICATOR

NEON INDICATOR. RATED 120 V 1/3 W. MOUNTS IN 5/16" HOLE 75¢ EACH RED LENS. 10 FOR \$7.00 100 FOR \$65.00

EDGE CONNECTORS

22/44 22/44 GOLD PLATED CONTACTS 156 CONTACT SPACING. \$2.00 EACH 10 FOR \$18.00

13 VDC RELAY

CONTACT: S.P.N.C. 10 AMP @ 120 VAC ENERGIZE COIL TO OPEN CONTACT COIL: 13 VDC 650 OHMS SPECIAL \$1.00 EACH

SWITCHING POWER SUPPLY

INPUT: 14 Vac-25.5 Vac OUTPUT: +12 Vdc @ 350 ma + 5 Vdc @ 1.2 amp - 5 Vdc @ 200 ma SIZE: 4 1/4" x 4 1/4" x 1 1/4" high \$5.00 each

ALL ELECTRONICS CORP.

905 S. VERMONT • P.O. BOX 20406 • LOS ANGELES, CA 90006

TOLL FREE ORDERS • 1-800-826-5432 (IN CA: 1-800-258-6666) INFO • (213) 380-8000 TWX - 5101010163 ALL ELECTRONIC

- QUANTITIES LIMITED
- FOREIGN ORDERS INCLUDE SUFFICIENT SHIPPING
- USA \$300 SHIPPING NO C.O.D.
- CALIF. RES. ADD 8 1/2%

CIRCLE 119 ON READER SERVICE CARD

