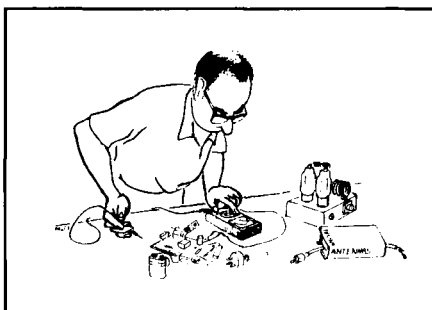


Ham Radio Techniques

Bill Orr, W6SAI



THE GAMMA MATCH: AN UPDATE

When the 88 to 108-MHz FM broadcast band was authorized shortly after World War II, a VHF transmitting antenna using an off-center feed system was introduced. Adapted for Amateur use, the system was termed the "gamma match" and was featured in *QST*, September 1949. The builder, H. Washburn, W3MTE, remarked that the device worked well, permitting him to achieve an SWR value as low as 1.75:1. His arrangement is shown in Figure 1.

Several other antenna experimenters and I worked with the W3MTE gamma match. We soon determined that to lower the SWR appreciably below 2:1 a variable capacitor had to be placed in series with the gamma rod (see Figure 2).

Little information was available on optimum rod-to-antenna spacing, rod length, or rod diameter. It was strictly a cut-and-try situation. Some Amateurs had good luck with the device; others couldn't get it to work. The gamma match soon got the reputation as a tricky device that was hard to adjust. In time, it became apparent that the gamma rod had to be small in diameter compared with the driven element, and that the spacing of the gamma rod to the element had to be quite large compared with rod diameter, in order to make the system work properly.

Some attempts were made to analyze the gamma match using transmission line equations. But it wasn't until Harold Tolles, W7ITB, analyzed the device¹ that a computer program was derived that would predict gamma dimensions accurately for a particular antenna.²

The gamma match program

The gamma program, written in BASIC by Richard Nelson, WBØIKN, is


based upon W7ITB's analysis and designed for the Apple II+. It can be modified to work equally well with many microcomputers.³

I put the program to use designing a gamma match for a three-element, 10-meter Yagi. I took beam dimensions from my *Beam Antenna Handbook*.⁴

Design frequency was 28.5 MHz. I planned to use a 1-inch diameter element, a 1/4-inch diameter gamma rod, 3-inch center-to-center spacing, and a 100-pF series capacitor (refer to Figure 3). Feedpoint impedance was estimated to be 18 ohms and I wanted to match to a 50-ohm line. When I plugged these values into the computer program, it indicated a gamma rod length of 22 inches and a series capacitance of 180 pF.


These results immediately rang an alarm bell. Our experiments had indicated that the series gamma capacitor should be about six times the operating frequency in meters and the gamma rod

FIGURE 1

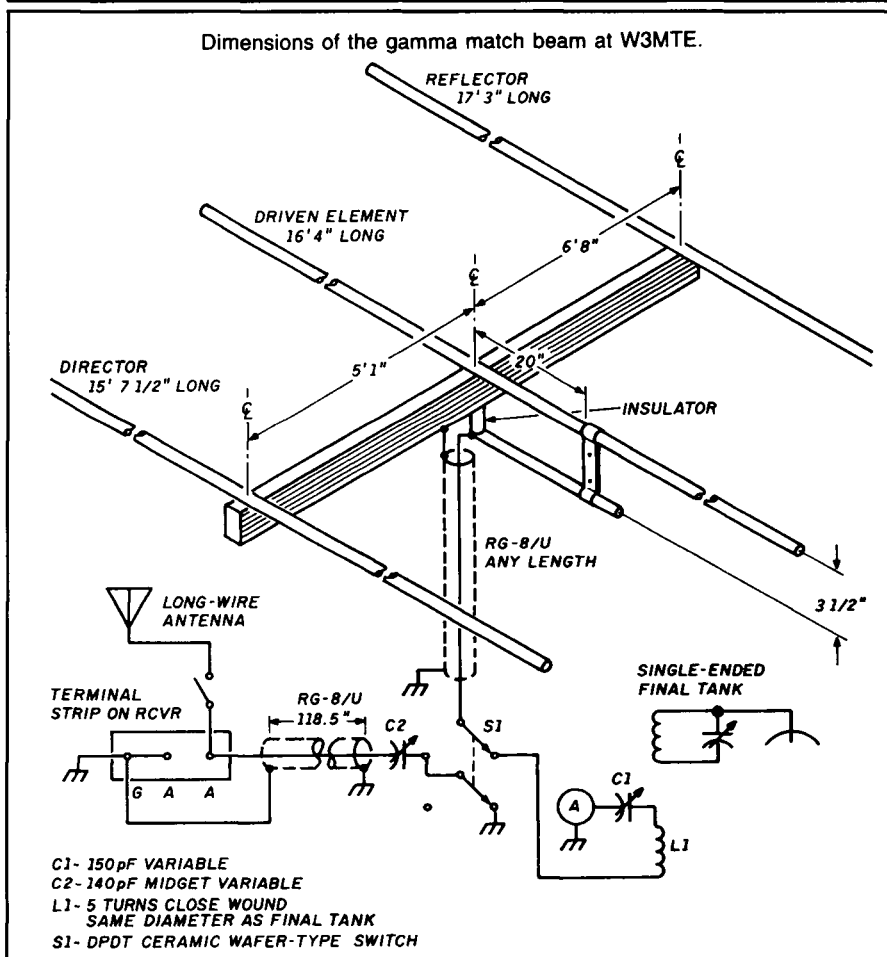


The early gamma match described by W3MTE (*QST*, September 1948).

FIGURE 2

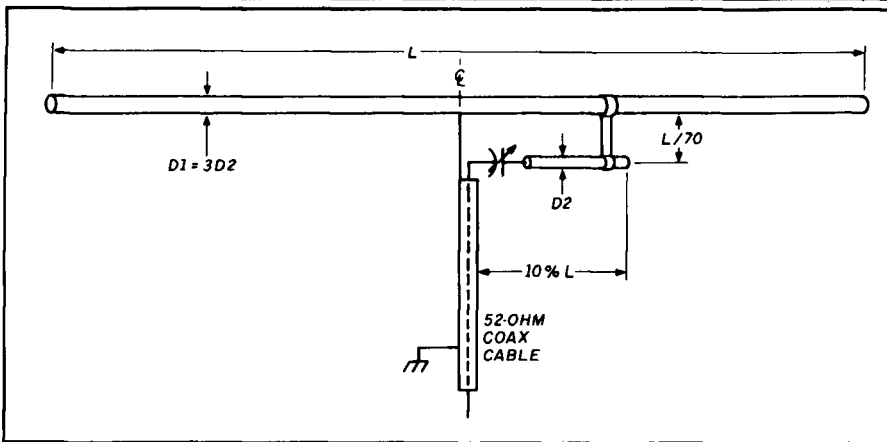

Early *Radio Handbook* shows series gamma capacitor and approximate dimensions for gamma match.

FIGURE 3

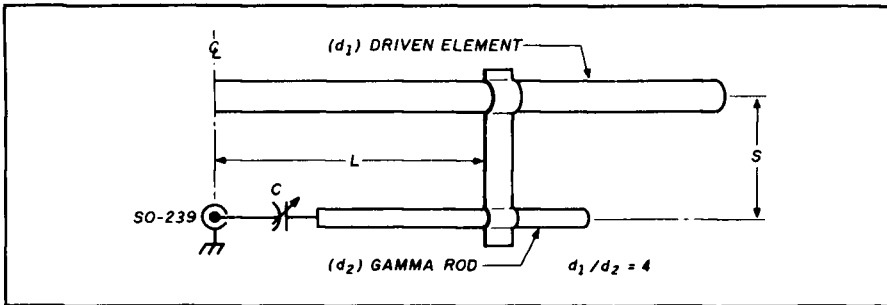

W6SAI's 10-meter gamma match. Diameter $d_1 =$ one inch, $d_2 =$ 1/4 inch. Center-to-center spacing = 3 inches.

should be about 0.04 wavelength long. For the 10-meter band, this works out to a capacitor of 60 pF and a rod length of about 16 inches. To back up my assumption, I found a commercially produced 10-meter beam with substantially the same dimensions as my design, using a 19-inch gamma rod and a 45-pF capacitor. Not too close, but a lot closer than the answer ground out by the computer program!

Obviously, there was some factor I hadn't taken into account that influenced gamma dimensions. There was more to the gamma match than met the eye!

Gamma match computation

I found the answer to the puzzle in a short remark (almost an afterthought) in the text of the W7ITB computer program article.¹ Harold worked out gamma dimensions for a sample antenna and then mentioned that if the drive point impedance of the antenna had capacitive reactance, the value of the gamma capacitor would decrease, as would the length of the gamma rod. Armed with

this morsel of information, I read the WBØIKN computer program again. At the end of the article the author mentioned that a smaller gamma capacitor may be used if radiator reactance is made capacitive (negative) by reducing its overall length.

Aha! Here was the missing clue. With a given value of drive point resistance, and a given gamma to driven element spacing, what would happen to the rod length and series capacitance values when different amounts of negative reactance were introduced into the driven element?

Varying the driven element reactance

For a given frequency, an antenna element may exhibit either positive or negative reactance at its drive point when the antenna is simply made longer or shorter than the resonant length. Shortening the element produces negative reactance; that's what I was interested in! I reran the WBØIKN program, plugging in various

NEW! No Tune Microwave Linear Converters

Board level RX/TX transverter modules and local oscillator: kit or assembled/tested. Linear operation allows all modes, ATV, SSB, Digital, Packet, FM.

Available for: 903, 1269, 1296, 2304, 3456 MHz

COMPLETE KITS

SHF 900 K	with integral LO for 902 MHz	\$110
SHF 1240 K	for 1240-1300 MHz - specify 1269 or 1296 base	\$135
SHF 2304 K	for 2300-2450 MHz - MODE S downlink package available	\$185
SHF 3456 K	for 3456 MHz	\$185
SHF-LO	LO kit only, with XTL, 540-580 MHz, +10 - +14 dBm out	\$ 60

Call or write for details on complete transverters and options

SHF Systems
P.O. Box 666
Nashua, NH 03061
(603) 673-1973
John Molnar, WA9MTD



Down East Microwave
Box 2310, RR#1
Troy, ME 04987
(207) 948-3741
Bill Olson, W3HQZ

✓ 136

DOWN EAST MICROWAVE



MICROWAVE ANTENNAS AND EQUIPMENT

- Loop Yagis • Power Dividers • Linear Amplifiers • Complete Arrays • Microwave Transverters • GaAs FET Preamps
- TROPO • EME • Weak Signal • OSCAR • 902 • 1269 • 1296 • 2304 • 2400 • 3456 MHz
- 2345 LY 45el loop Yagi 1296 MHz 20dBi \$99
- 1345 LY 45el loop Yagi 2304 MHz 20dBi \$80
- 3333 LY 33el loop Yagi 902 MHz 18.5dBi \$99

Above antennas assembled and tested. Kits available.

Add \$8 UPS S/H, \$11 West of the Mississippi

MICROWAVE LINEAR AMPLIFIERS SSB, ATV, REPEATER, OSCAR

2316 PA	1w in 18w out	1240-1300 MHz	13.8V	\$265
2335 PA	10w in 35w out	1240-1300 MHz	13.8V	\$315
3318 PA	1w in 20w out	900-930 MHz	13.8V	\$265
3335 PA	10w in 40w out	900-930 MHz	13.8V	\$320
23LNA preamp	0.7dB N.F.	1296 MHz		\$ 90
33LNA preamp	0.9dB N.F.	902 MHz		\$ 90

Add \$5 shipping UPS/48

LHM 1296 & 2304 MHz transverter/kits in stock

Write for free catalog



DOWN EAST MICROWAVE
Bill Olson, W3HQZ
Box 2310, RR 1, Troy, ME 04987
(207) 948-3741



✓ 137

MOVING?

Let circulation know 60 days in advance.

Ham Radio
Greenville, NH 03048-0498
603-878-1441

values of negative reactance from $j=0$ to $j=-50$ (see Figure 4).

The plot shows that the series capacitance value peaks at the element resonant frequency ($j=0$) and decreases in value either side of resonance. The length of the gamma rod, however, follows a different curve. It exhibits the shortest length when the antenna exhibits negative reactance ($-j15$).

A practical gamma match system (one that can be built cheaply and adjusted easily) calls for the shortest gamma rod and the least amount of capacitance. It's no fun to hang from the top of a tower and try to adjust a gamma rod whose shorting bar isn't quite within reach!

You can build a small gamma capacitor inexpensively with a coaxial gamma rod that has the inner conductor serving as one capacitance element as shown in Figure 5.

In my case, a 22-inch adjustable gamma rod would work over a range of antenna reactance from $j0$ to $-j50$. However, as the antenna element approached resonance, the value of the gamma capacitance rose sharply, and the coaxial rod length didn't provide sufficient capacitance. From the plot, it was obvious that the designer of the manufactured antenna had cut his driven element shorter than resonance to provide a negative value of reactance (about $-j30$ ohms) in order to have reasonable gamma dimensions.


Gamma rod spacing

My next question was: what is the effect on gamma dimensions when element-to-rod spacing is varied? I used the computer program for the 10-meter beam element diameters; the results are summarized in Table 1. Rod length compared with spacing is given for four values of antenna reactance: $j=0$ (resonance), $j=-15$, $j=-30$ and $j=-50$ ohms.

Larger values of element-to-gamma spacing require a shorter rod length, but greater gamma capacitance. The shortest rod length is achieved when the driven element has a reactive value between $-j15$ and $-j30$, with an element-to-gamma spacing of 3 to 4 inches.


Gamma capacitance increases with element-to-gamma spacing, and decreases as the driven element exhibits greater values of negative reactance. Practical (small) values of capac-

FIGURE 4

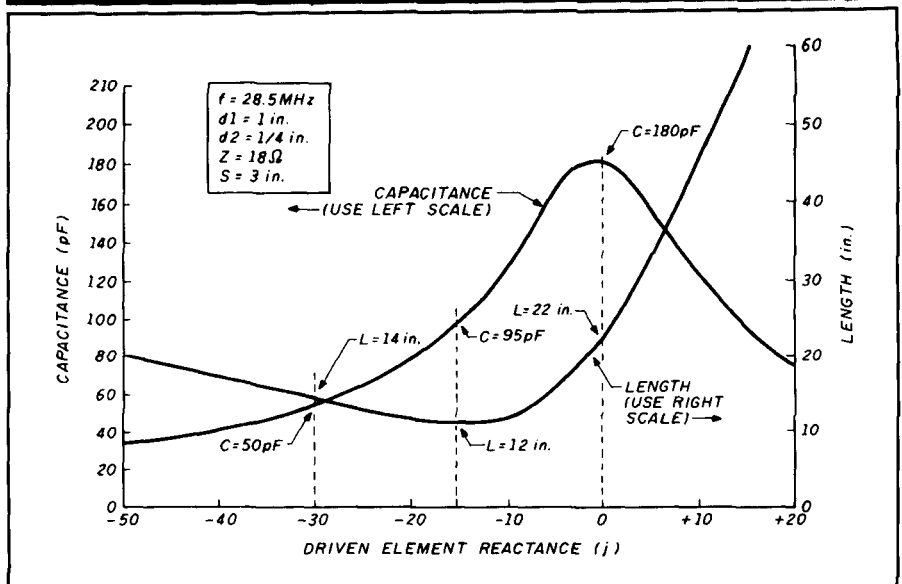

Graph for determining design lengths of the gamma match.

FIGURE 5

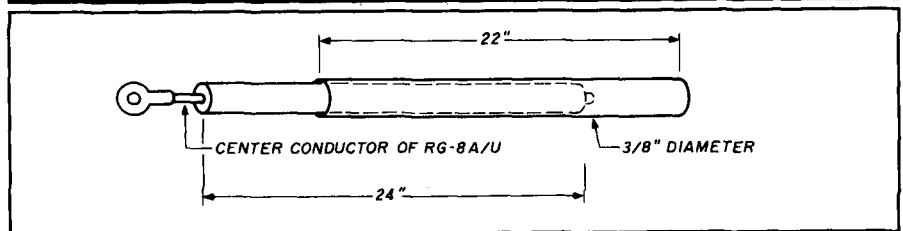

Coaxial gamma-rod capacitor for 10-meter beam. Maximum capacitance is about 55 pF.

TABLE 1

Various gamma and series capacitance values for different length driven elements.			
j	Spacing inches	Rod Length inches	Capacitance pF
j0	1	39	83
	2	25	145
	3	23	180
	4	22	212
-j15	1	33.5	57
	2	15	80
	3	12	95
	4	11	105
-j30	1	36	24
	2	18	31
	3	13	52
	4	12	58
-j50	1	36	22
	2	22	31
	3	20.5	32
	4	17	35

itance are reached in the reactive region between $-j30$ and $-j50$.


Because shortening the driven element has minimal effect on beam performance, it would be helpful to choose a

length providing a negative reactance of 30 to 50 ohms.

Element shortening

How much physical shortening is

FIGURE 6

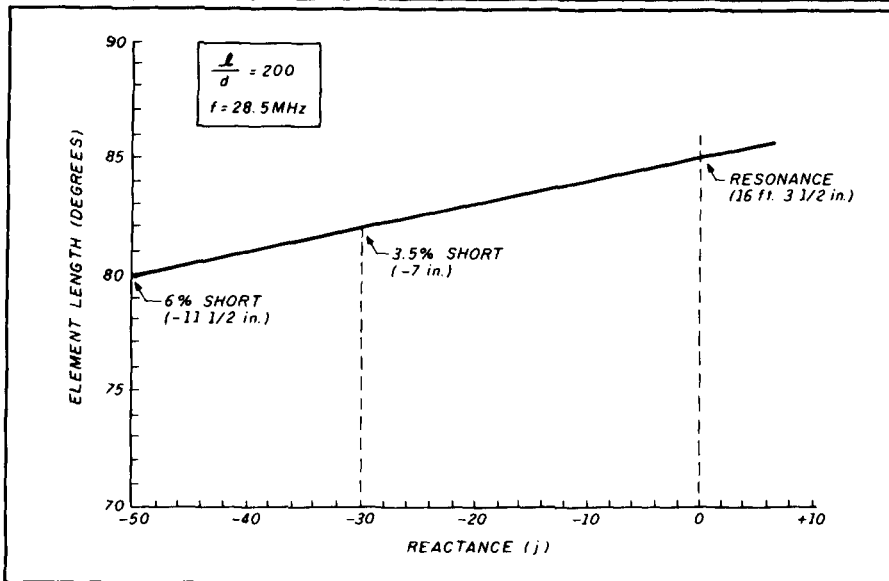

Tip-to-tip shortening required for various values of driven element reactance for 1-inch diameter element.

shows that gamma rod length increases by an inch, and that the series capacitance decreases by 3 pF from the values determined for a feedpoint value of 18 ohms. This indicates that the actual feedpoint resistance isn't critical, and that the feedpoint values given in the literature for multi-element Yagi beams hold well for use in the gamma computer program.

Gamma rod diameter

The computer program provides interesting information about gamma rod diameters (see Figures 7 and 8). The curves show the importance of having a shorter than resonant driven element. With the $-j30$ element length, gamma rod length changes less than 2 inches as the rod diameter is varied from 0.05 to 0.5 inches. The gamma capacitor, given the same rod diameters, varies from 36 to 65 pF. When the driven element is resonant, the values of rod length and series capacitance vary largely. This gives further proof that adjustment of driven element length is of paramount importance in making the gamma match work.


Frequency scaling

If all the dimensions of a 28.5-MHz beam and gamma match system are doubled, the computed results will be identical at half the frequency — or 14.25 MHz. This scaling isn't practical for my 10-meter beam; it would result in a 20-meter driven element diameter of 2 inches. I prefer a diameter of about 1.25 inches, all else being equal. I would probably also build a tapered element. The gamma match computer program doesn't consider this element, but there are programs that compute an equivalent element length for a tapered element.⁶ This equivalent element can then be used with the gamma program once its length is readjusted to provide a reactive termination. Someday the Yagi computer program will be modified for frequency scaling. It will also accommodate the gamma match, as well as other matching systems requiring adjustment of the driven element length.

Is there pattern distortion with the gamma match?

The gamma match feeds only half the driven element. What happens to voltages and currents in the other half? Does the unbalanced feed system upset the beam pattern? Tests run by

FIGURE 7

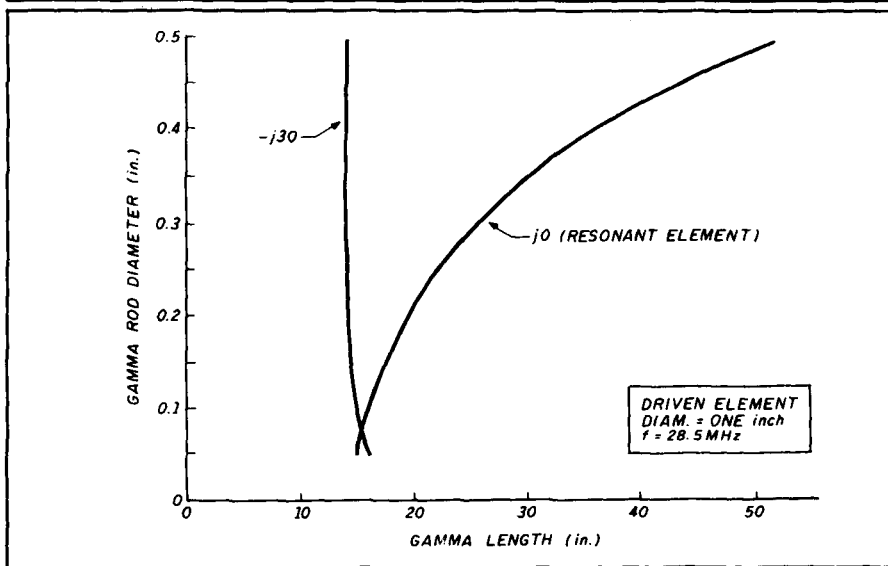

The length of the gamma rod with a shorter than resonant driven element ($-j30$) is nearly independent of gamma rod diameter.

required to provide a reactance of -30 to -50 ohms? It depends upon the ratio of element length to diameter. Such ratios have been computed and measured,⁵ and a simplified plot for a length-to-diameter ratio of 200 is shown in Figure 6. This corresponds to a 1-inch diameter element at 28.5 MHz. To achieve a reactance value of $-j30$, you must shorten the driven element about 7 inches (tip to tip). For a reactance of $-j50$, you'll need a shortening of 11.5 inches.

Drive point impedance and element length

What happens to the 18-ohm figure if the driven element has a drive point value of 18 ohms at resonance and is shortened to provide a negative reactance? It decreases in value. The reduction depends upon the amount of shortening and the element diameter, as discussed previously. Assuming that the new resistance value is 15 ohms at a reactance value of $-j50$, a computer run

MADISON SHOPPER

CALL FOR ORDERS

1 (800) 231-3057

1 (713) 520-7300 OR 1 (713) 520-0550

TEXAS ORDERS CALL COLLECT

FAX 1 (713) 771-7759

ALL ITEMS ARE GUARANTEED OR SALES PRICE REFUNDED



New Icom IC 781

Kenwood TH215A, TH25AT

TS440 S/AT

Trades wanted

Trade in your old HT

Call



Kenwood TS 140S

New Kenwood TM 721A, mobile

ICOM 228H/TTM

Call for trade

Call

449.00



TS 790A Superior 2 Meter 70 cm Rig,

1.2 GHz Option Available

Icom 765

Kenwood MC 60A + Heil HC 5 cartridge

Icom IC 725

NYE MBSA Tuner

Alpha Delta Transtrap HV

CSI Private Patch V

Ameco PT 3 Pre Amp

Larsen 2-meter on glass

Anteco 2M, 5/8, Mag. Mount, Comp

Van Gordon Window WA2

Bird 43, elements/stock

Thousands of panel meters

Belden 9913, 8267, 8214 Stock

MICA Capacitors

Arista SWR Bridge 3-30 MHz

831SP-PL259 Silverplate (Amphenol)

82-61 N Male (Amphenol)

82-202-1006 N Male (9913)

Double Female UHF

UG176 RGBX

Surplus Elbow PL259 SO239

Receiving tubes 50-90% off list price

Santec Boom Mike/Headset (fits ICOM)

STUPH

RF Amp Meters

25 pF/10KV Doorknob Cap

Throat Mike (new mil. surplus)

ANBH 1 600 Ω Headphones (new mil. surplus)

New Demo Units for Sale

Kenwood R-5000

3.95 up CALL

Call

Call

Call

19.95

1.50

3.50

1.00

each 40

each \$1

Call

20.00

Call

each

5.00

5.00

5.00

Call

849.00

USED EQUIPMENT

All equipment, used, clean, with 90 day warranty and 30 day trial. Six months full trade against new equipment. Sale price refunded if not satisfied.

(800) 231-3057

POLICIES

Minimum order \$10.00. Mastercard, VISA, or C.O.D. All prices FOB Houston, except as noted. Prices subject to change without notice. Items subject to prior sale. Call anytime to check the status of your order. Texas residents add sales tax. All items full factory warranty plus Madison warranty.


Bird and Belden products in stock. Call today.

MADISON Electronics Supply

3621 FANNIN HOUSTON, TEXAS 77004



FIGURE 8

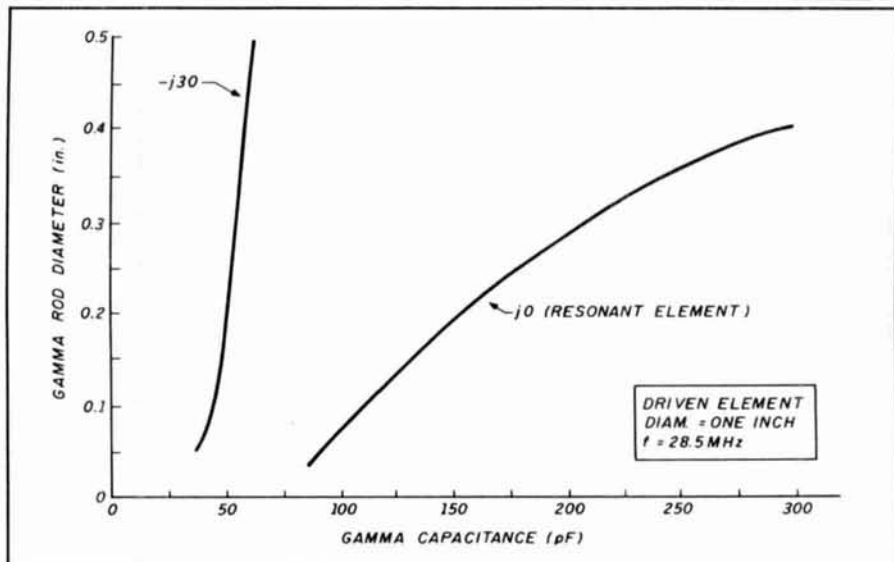

Gamma capacitance is nearly independent of gamma length when shorter than resonant driven element ($-j30$) is used.

Katashi Nose, KH6IJ, show that voltage at the driven element tips of a 20-meter Yagi isn't equal when a gamma match is used.⁷ Even so, the azimuth pattern seemed balanced. Nose concluded that the voltage imbalance wasn't important.

Later tests run by Bob Sutherland, W6PO, a VHF "moonbounce" enthusiast, on a large array of 220-MHz gamma-fed Yagis showed that the array's pattern was normal with no noticeable "squint" or distortion that could be attributed to the gamma matches.

Gamma match summary

The gamma match provides a mechanically simple and easily adjusted network for matching a Yagi to a coaxial transmission line, provided the driven element of the array is somewhat shorter than the resonant length. This point has often been overlooked or not emphasized in the literature, leading to puzzling results.

For the best mechanical arrangement, make the capacitor part of the gamma rod, as shown in Figure 5. As they say in the world of computers, the gamma match is "user friendly." Information provided in this article, along with the gamma computer program, should make life easier for those contemplating using this interesting match system.

Electric stove RFI! (What next?)

My friend Wyn Wagener, W6VQD, called me the other evening to give me the latest news on the continuing RFI battle. He was concerned about the new electric ranges.

Old-style electric stoves have a multiple circuit heating element. The circuits are selected by a rotary switch that cuts the heating coils in and out, depending upon the cooking heat required. The newer electric ranges have dispensed with this common sense idea in favor of modern gimmicks and the results are questionable, to say the least.

The new brand of electric range has only one coil in the heating element and the circuit is cycled on and off by a continuously variable heat control, instead of a multicontact switch. The control mechanism consists of a small rheostat in series with a low wattage heating element and bimetallic strip heat sensor. As you advance the control, the heater warms up and the strip cycles on and off. The strip controls the main heating element which, in turn, cycles on and off. Wyn discovered that some ovens created copious RFI during the cycling process, which can run in a sequence of 3 to 20-second on/off bursts.

Before he bought a new range for his home, Wyn took a portable receiver to the appliance store and monitored several ovens. Although there seem to