


# Trouble Shoot Your Antenna from Indoors

Neil Johnson, W2OLU  
74 Pine Tree Lane  
Tappan, New York 10983

Would you like to shoot trouble on your TV or short-wave antenna without going outdoors? It can be done, without the need for any complex instruments. The cost? Just a few cents. Here's how it's done. Assuming your antenna feeds into a transmission line of the 300-ohm type—this applies to most installations—the trouble shooting setup becomes simplicity itself: two carbon resistors, plus an ordinary ohmmeter (Fig. 1).

Two composition resistors, of values approximating 100K ohms each, are connected in series. This combination is then connected to the "top" end of the twin lead, where it joins to the antenna proper. Now...the twin lead is disconnected from the equipment which it feeds, such as TV receiver or short-wave apparatus. The normal reading for a "folded-dipole" type antenna installation will be in the order of a few ohms, possibly as high as 5 or 10 ohms at most. Should a break occur in the antenna or "flat-top" portion, the ohmmeter will read in the neighborhood of 200,000 ohms. On the other hand, if the meter readings should be extremely high, it is safe to assume that the twin lead coming down from the antenna has a break in it somewhere. Through this simple process of elimination, the experimenter quickly pinpoints the area of trouble. This reduces the total time needed for diagnosis and repair. It will also eliminate, or reduce, the need to climb over hazardous rooftops, thus cutting down on a few bruises, or possibly broken bones.

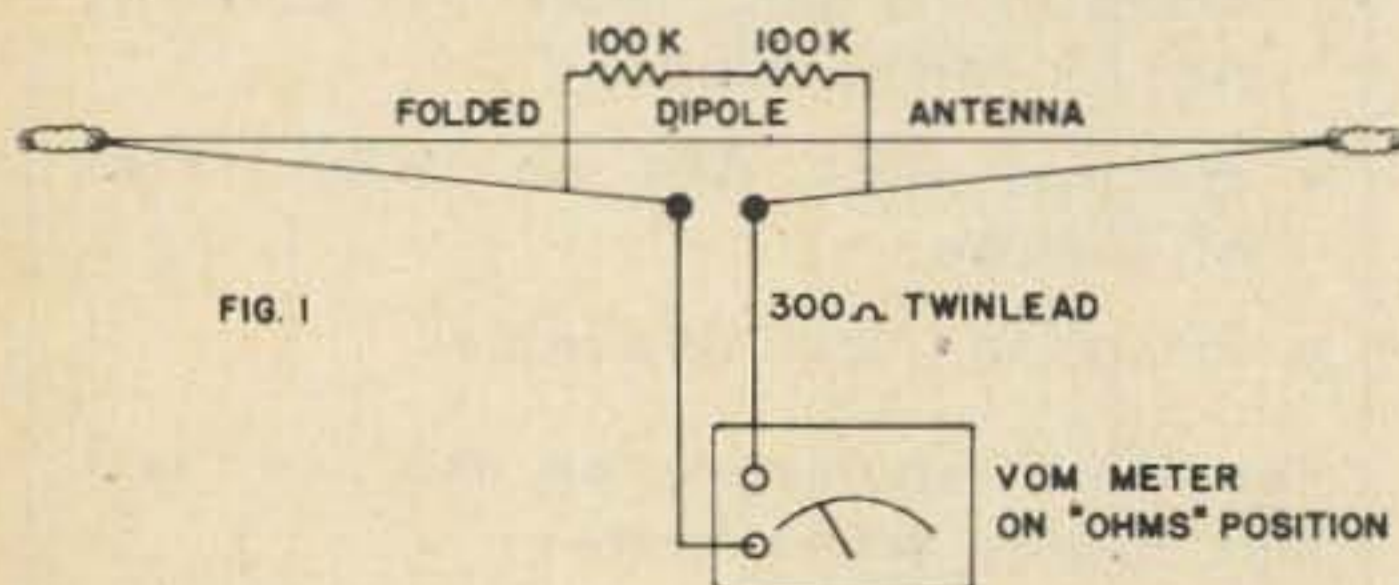This scheme, using resistors, is not confin-



#1 Possibility: Ohmmeter reads "low ohms," 5-10 ohms maximum. System OK.

#2 Possibility: Ohmmeter reads 200K ohms, folded dipole section of system disconnected from feedline; or, folded dipole "open."


#3 Possibility: Ohmmeter reads much higher than 200K ohms, the feedline has an "open circuit" before it joins the antenna section.

ed to antennas of the folded-dipole type. Many short-wave and TV antennas have a single conductor for the flat-top, such as a copper wire or an aluminum rod or tube. Breakage in the antenna proper is thus easily spotted. But twin-lead breakage, concealed inside a plastic overlay, cannot be detected without a minute and close-up inspection. Rather than needlessly risk a broken arm or leg, why not put two ten cent resistors to work? (Fig. 2).


In the case of "intermittents," one of the hardest of all radio troubles to spot, sometimes the fault may be determined by placing the ohmmeter terminals across the lower end of the down-lead, while at the same time keeping a sharp eye on the ohmmeter and simultaneously shaking the twin lead. The few check-points in this elementary "system" are not a 100% cure-all, but each only takes a few minutes' time; and in the majority of cases, diagnosis can be completed while the experimenter stands on "terra firma." Half watt resistors will suffice for all receiving set-ups, and 1 watt resistors will work out fine for all low-power amateur applications, both receiving and transmitting. Two watt resistors should be used for high-powered "ham" applications. In any case, very little power loss takes place through the resistors, since their total of 200,000 ohms is approximately 3,000 times the nominal impedance of a resonant dipole, or 70 ohms. The reason for using two resistors in series is mechanical, rather than electrical. Located as they are shown in the diagram, there is no physical strain on the resistors, and no chance for them to "open up." To avoid any chance of trouble, clean all connections thoroughly, and then solder them.

In addition to connecting the resistors to the antenna, trouble can be avoided by using twin-lead that is made with copperweld steel. The cost is no more, and it is far stronger than ordinary twin-lead, which is made with copper. Several manufacturers produce this "long life" variety of twin-lead. Belden offers these under several designations, such as type 8285 Permohm, type 8275 Celluline, and type 8230 Weldohm. Of these three, the last mentioned is least expensive. Amphenol makes


# LET DOW-KEY HELP SOLVE YOUR ANTENNA SWITCHING PROBLEMS . . .

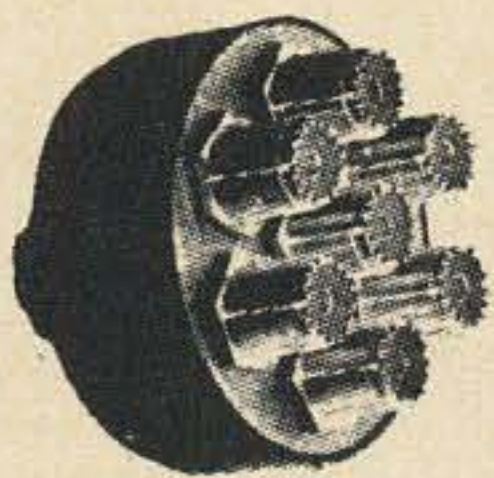

SP6T  
MANUAL  
78-0604

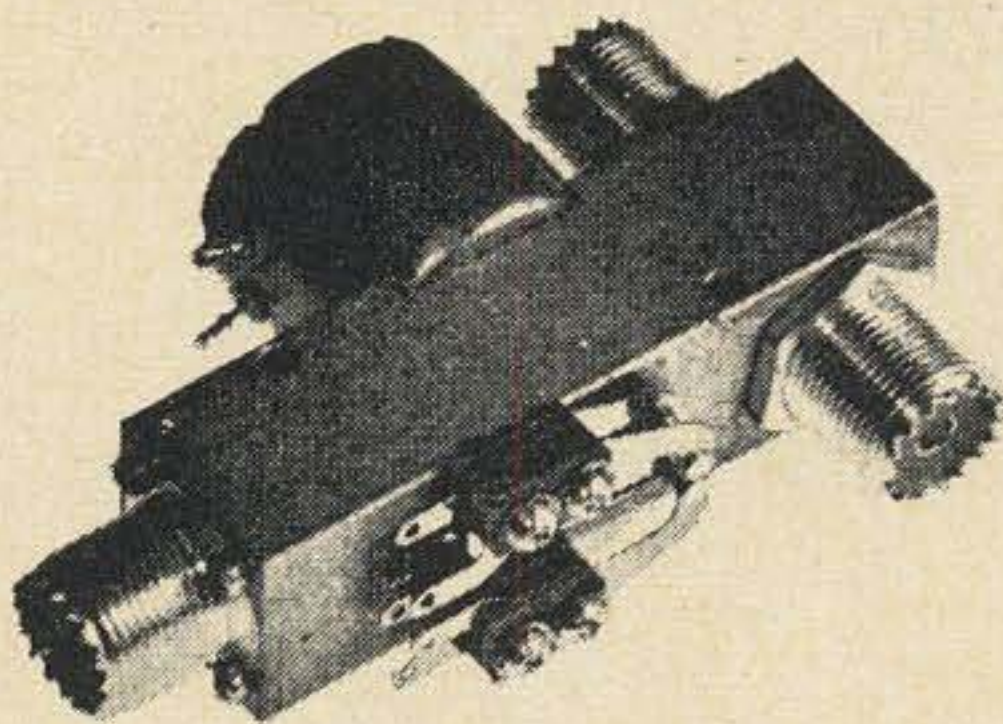

SPDT  
REMOTE 115V ac  
60-262842

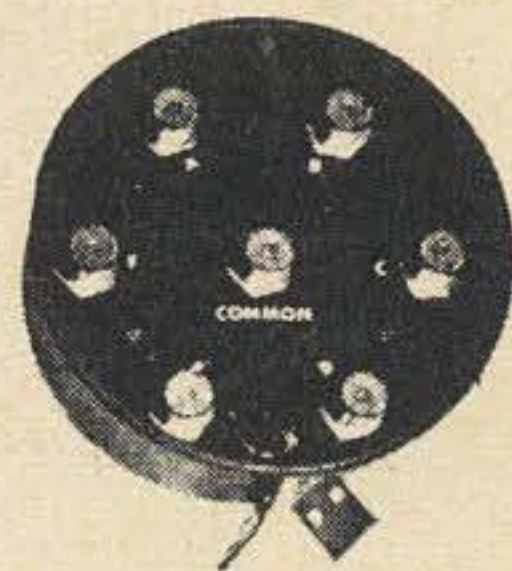

SP6T  
REMOTE 115V ac  
71-260401

**SERIES 78** The series 78 coaxial switches are manually operated with true coaxial switching members (not wafer switches). They are offered in 2, 3, 4 & 6 position (illustrated) types, plus a transfer or crossover and DPDT. The useful frequency range is 0-1 Ghz except 500 Mhz using UHF connectors. The unused positions are open circuited or non-shorting. Also available with other type connectors such as N, BNC, TNC or C.

**SERIES 60** The series 60 are remote operated, of rugged construction and designed for low-level to 1 KW use. The unit illustrated is equipped with a special high isolation connector ("G" type) at the normally closed or receive position. This "G" connector increases the isolation to greater than -100db at frequencies up to 500 Mhz, although it reduces the power rating through this connector to 20 watts. This is also available with other type connectors such as BNC, N, TNC, C or solder terminals.

**SERIES 71** High power 6 position switches commonly used for switching antennas, transmitters or receivers at frequencies up to 500 Mhz. The unit is weatherproof and can be mast mounted. The illustrated unit has the unused input shorted to ground. It is also available with a wide range of connectors, different coil voltages and non-shorting contacts or resistor terminations. Each of the six inputs has its own actuating coil for alternate or simultaneous switching.


## DOW - KEY

### ORDERING INFORMATION:

COMPANY

Contact your local electronics distributor or Dow-Key sales representative, or write direct to the factory.

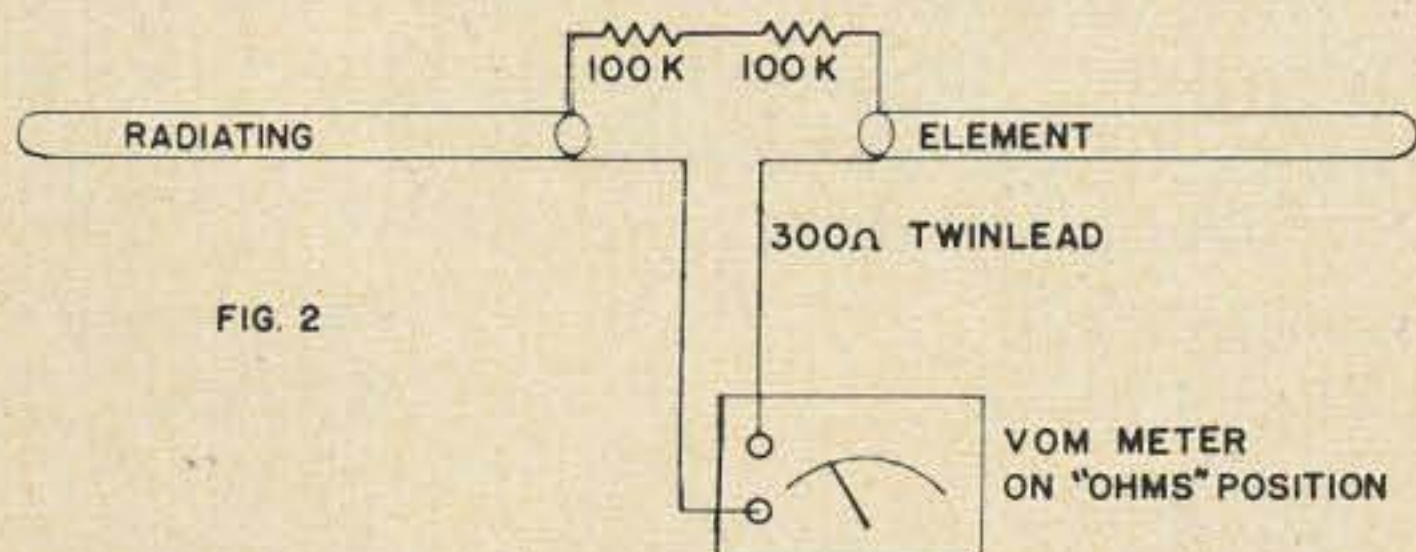2260 INDUSTRIAL LANE • BROOMFIELD, COLORADO 80020  
TELEPHONE AREA CODE 303/466-7303 • P. O. BOX 348



#1 Possibility: Ohmmeter reads approximately 200K ohms. System is OK.

#2 Possibility: Ohmmeter reads very high, in megohms. Twin lead is "open."

a similar flat line, "Steelcore," number 214-559. A somewhat more expensive line by Amphenol is their number 214-022, which has two number 16 conductors and is suitable for transmitting amateurs. Other makers offer copperweld twin-lead under such names as "lifeline." If doubt should exist as to the wire's having a steel center or core, a small magnet will give an indication of the wire's being copperweld. If you have been having trouble with ordinary twin-lead breaking frequently, why not give one of these copperweld lines a trial? You will be impressed by their relatively greater durability. Through the utilization of long-life twin-lead, plus the resistor scheme, it should not be necessary to make that dangerous trip to the roof so often.

...W2OLU

## MORE RANGE . . . with NO NOISE

FOR ALL  
MOBILE UNITS

ENGINEERING  
ESTES  
COMPANY

CUSTOM SYSTEMS  
KITS • ACCESSORIES

ELECTRO-  
SHIELD

ELIMINATE IGNITION NOISE  
ELECTRO-SHIELD®  
YOUR ENGINE

FROM \$44.95

ESTES ENGINEERING CO.

543 W. 184th St., Gardena, Calif. 90247

