

High Voltage Current Buffer

INTRODUCTION

Many high voltage op amps cannot deliver more than 200mA of output current. For applications requiring as much as 1A of current, you can include the current buffer described here. The current buffer is designed to provide approximately unity voltage gain and is inserted between the output of the high voltage op amp and the load. The current buffer is included in the feedback loop of the operational amplifier and creating a composite op amp.

One of the design challenges with a current buffer is the output stage bias circuit. A Class B output stage may be adequate for some applications, but it has characteristic crossover distortion as the lower device output current transitions to the high side device. A Class AB output stage is usually preferred as the crossover distortion is much lower and the feedback loop remains closed during the transition. Setting the quiescent current of the Class AB output stage is difficult because of output device variations and sensitivities.

The current buffer design approach proposed here avoids many of the difficulties of output stage biasing by incorporating a depletion mode MOSFET as the high side driver. This circuit topology exploits the MOSFET's ability to be used as a current source to provide the bias current. The depletion mode MOSFET serves as the bias current generator as well as the high side driver.

TYPICAL CURRENT BUFFER TOPOLOGIES

 


Figure 1: Class B Current Buffer

The Class B circuit shown in Figure 1 illustrates one common method of implementing a current buffer. The resistor R1 provides a current path to the load from the op amp and is selected to limit the maximum gate voltage of M1 and M2 to 10V. The resistor RCL1 sets the current limit value of the PA341 so that the current in R1 creates a voltage drop of 10 Volts. The op amp current limit value should be set as low as possible to minimize power dissipation of the op amp. Resistors RCL2 and RCL3 are included as a method of current limiting the output MOSFETs M1 and M2. This provides a level of protection for the output devices.

The output current flows through RCL2 and RCL3 creating a voltage across the base to the emitter of Q1 and Q2. Once this voltage reaches approximately 0.7V, the transistors Q1 and Q2 begin conducting current to the load thus clamping the gate drive voltage at M1 and M2 as the PA341 enters current limit mode.

 


Figure 2: Conventional Class AB Current Buffer

Figure 2 is a simplified schematic diagram of the conventional circuit topology used for a Class AB output stage. The VGS multiplier composed of M3, R1 and R2 sets the required voltage at the gates of M1 and M2 which provides the desired quiescent current through the output devices, M1 and M2. Constant current sources I1 and I2 provide the required current to the VGS multiplier. The transistors Q1 and Q2 are used for current limiting as described in the previous example of the Class B stage.

This design approach is much more complex and problematic than the Class B stage design. The current sources I1 and I2 require additional components in the actual implementation. The voltage swing will be less than the voltage swing of the PA341 because of the drive requirements of the output MOSFETs. Setting the quiescent current through M1 and M2 is difficult because of the high sensitivity between VGS and ID. The VGS multiplier, consisting of M3, R1 and R2 must be individually adjusted for every unit. Preventing thermal runaway relies on device matching and tight thermal coupling between M1, M2 and M3. Thermal stability is difficult to achieve. Because of the circuit complexity, temperature instability and sensitivity in setting the quiescent current, the actual implementation of this circuit topology is much more challenging than that of the Class B version

ALTERNATE CLASS AB CIRCUIT DESCRIPTION

A conceptual simplified circuit diagram of the proposed topology is shown in Figure 3. To demonstrate the mechanism for establishing the flow of quiescent current, assume the output voltage is at zero V. The base of Q1 must be approximately -0.7V. The Gate of M1 is also at -0.7V forcing the MOSFET to conduct. The resistor RS, is selected to adjust the quiescent current to the desired value. This circuit functions in a self-biasing mode and does not require the current sources and Vgs multiplier of the conventional Class AB stage.

 


Figure 3 Alternative Class AB Current Buffer

The simulation plots of Figure 5 illustrate circuit operation under light load conditions. The output voltage is 100V p-p across a load resistor of approximately 7KΩ. The plots indicate a quiescent current of approximately 9mA. Since the current through the transistors, M1, Q2 and Q3 is always greater than zero for the entire cycle, the output stage is operating in Class A mode.

 


Figure 5: Output Stage Behavior in Class A Mode (light load)

The simulation plots of Figure 6 illustrate circuit operation under full load conditions. The power supply voltage is $\pm 160\text{V}$. The output voltage is 200V p-p across a load resistor of 100Ω . The output stage is operating in Class AB mode.

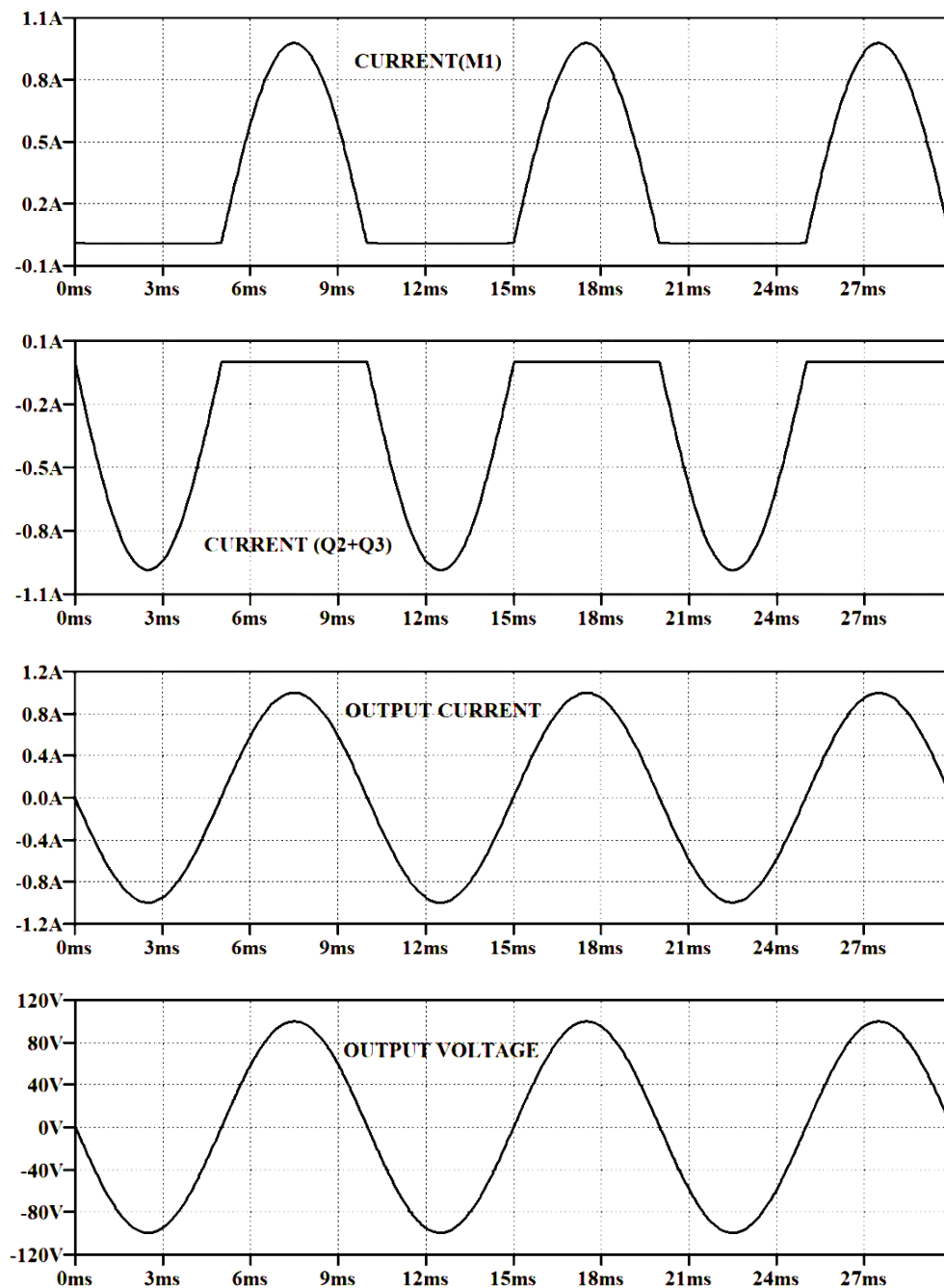


Figure 6: Output Stage Behavior in Class AB Mode (full load)

Figures 7, 8, 9 and 10 are oscilloscope screen shots taken during bench testing showing the actual circuit behavior. Power supply voltage is $\pm 160V$, signal frequency is $10KHz$ with the amplifier configured for an inverting gain of 10. The actual circuit configuration is shown in Figure 4. Channel one is the output voltage and channel two is the input voltage.

 


Figure 7: Oscilloscope Waveforms of Output voltage with Capacitive load of $0.1\mu F$ in Series with 10Ω

 


Figure 8: Oscilloscope Waveforms of Output Voltage with Resistive Load of 100Ω

 


Figure 9: Oscilloscope Waveform of Output Voltage Showing Current Limit Levels with Resistive load of 50Ω

 


Figure 10: Oscilloscope Waveform of Output Voltage Showing Voltage Swing Clipping. Power Supply Voltage is ±160V with Resistive Load of 150Ω (1AMP)

REFERENCES

1. Graeme, Tobey, Huelsman; OPERATIONAL AMPLIFIERS Design and Applications, 1971, McGraw-Hill
2. Steele, Eddlemon; Use High-Voltage Op Amps to Drive Power MOSFETs, Electronic Design, June 24, 1993
3. PA341U, Data Sheet, High Voltage Power Operational Amplifier, Apex Microtechnology: www.apexanalog.com
4. PA441U, Data Sheet, High Voltage Power Operational Amplifier, Apex Microtechnology: www.apexanalog.com

NEED TECHNICAL HELP? CONTACT APEX SUPPORT!

For all Apex Microtechnology product questions and inquiries, call toll free 800-546-2739 in North America.

For inquiries via email, please contact apex.support@apexanalog.com.

International customers can also request support by contacting their local Apex Microtechnology Sales Representative.

To find the one nearest to you, go to www.apexanalog.com

IMPORTANT NOTICE

Apex Microtechnology, Inc. has made every effort to insure the accuracy of the content contained in this document. However, the information is subject to change without notice and is provided "AS IS" without warranty of any kind (expressed or implied). Apex Microtechnology reserves the right to make changes without further notice to any specifications or products mentioned herein to improve reliability. This document is the property of Apex Microtechnology and by furnishing this information, Apex Microtechnology grants no license, expressed or implied under any patents, mask work rights, copyrights, trademarks, trade secrets or other intellectual property rights. Apex Microtechnology owns the copyrights associated with the information contained herein and gives consent for copies to be made of the information only for use within your organization with respect to Apex Microtechnology integrated circuits or other products of Apex Microtechnology. This consent does not extend to other copying such as copying for general distribution, advertising or promotional purposes, or for creating any work for resale.

APEX MICROTECHNOLOGY PRODUCTS ARE NOT DESIGNED, AUTHORIZED OR WARRANTED TO BE SUITABLE FOR USE IN PRODUCTS USED FOR LIFE SUPPORT, AUTOMOTIVE SAFETY, SECURITY DEVICES, OR OTHER CRITICAL APPLICATIONS. PRODUCTS IN SUCH APPLICATIONS ARE UNDERSTOOD TO BE FULLY AT THE CUSTOMER OR THE CUSTOMER'S RISK.

Apex Microtechnology, Apex and Apex Precision Power are trademarks of Apex Microtechnology, Inc. All other corporate names noted herein may be trademarks of their respective holders.