

Application Note

PWM Amplifier Output Power Calculator

by Randy Boudreaux

1. INTRODUCTION

The PWM amplifier output power calculator is used to determine the effective root mean square (rms) power for a given speaker load. The spreadsheet is configured to calculate the actual power delivered to the speaker load for three typical speaker-load configurations, half-bridge tied, full-bridge tied and parallel full-bridge tied. To access the spreadsheet, click on this link: <http://www.cirrus.com/en/support/AN268>. The PWM Amplifier Output Calculator is available in two forms. If a version of Microsoft® Excel is available on your local computer, then download the Excel spreadsheet version of the power output calculator. If not, then use the interactive power calculator located at the above web site.

2. AMPLIFIER OUTPUT CONFIGURATIONS

2.1 Half-Bridge

Half-bridge tied speaker loads are driven on a single side by the PWM output, with the other side of the load referenced to ground, see [Figure 1](#). For single voltage rail systems with a voltage of V_P , the amplifier output will contain a DC voltage offset equal to V_P divided by 2 that must be blocked from the speaker load. This is generally accomplished by using a large electrolytic capacitor (C) in series with the output following the 2-pole LC filter used to attenuate the PWM switching frequency. The electrolytic capacitor is usually polarized and care must be taken to wire the "+" terminal of the capacitor towards the output of the PWM output. For proper operation and increased circuit reliability, the maximum ripple current specification for the capacitor must be larger than the peak-to-peak current to the speaker load.

The capacitor (C) along with the speaker load (R), which is generally in the 4 ohm or less range for this configuration, form a high pass filter. The -3dB corner frequency is determined by the equation $F_s = 1/(6.28 \cdot R \cdot C)$. The particular speaker load supported and the desired corner frequency determines the size of the capacitor measured in microfarads.

To avoid loud pops in the speaker caused by the instantaneous voltage across the DC blocking capacitor at the beginning of the power on sequence, a voltage ramp up sequence should be used, such as the Ramp-up feature of the CS44800/44600. This feature will quickly bring the output of the PWM amplifier to the half rail voltage of V_P divided by 2 in a linear fashion without causing any loud pops.

 


Figure 1. Half-Bridge Output Configuration

2.2 Full-Bridge

With using the same VP voltage rail level as with the half-bridge configuration above, increased power to the speaker load is accomplished by using a pair of PWM outputs providing a differential signal to drive a full-bridge tied speaker load, see [Figure 2](#). In this configuration, the speaker load is not referenced to ground and is continuously driven by both the "+PWM Output" and "-PWM Output" signals from the amplifier. This effectively doubles the voltage across the load resulting in a quadrupling of the output power since the power is a function of the square of the voltage.

With full-bridge configurations, care must be taken not to exceed the maximum current specification limits for the components. This is accomplished by increasing the minimum speaker load over what was driven for the half-bridge example above (to 8 ohms versus 4 ohms). Since the power out is inversely proportional to the resistive speaker load, then instead of quadrupling the power output, now the power output is double and thereby lowering the maximum output current. Even though there are two L_{filt} components in series for the full-bridge configuration, the value for this inductor remains the same as for the half-bridge configuration since the speaker load is now doubled.

 


Figure 2. Full-Bridge Output Configuration

2.3 Parallel Full-Bridge

Parallel full-bridge tied loads are driven differentially similar to full-bridge tied loads, but can deliver more current to the speaker load, with more efficiency, see [Figure 3](#). Multiple PWM outputs are tied together in a parallel fashion which effectively causes the R_{ds_on} of these switches to also be in parallel, thereby dividing the R_{ds_on} as seen by the load current by a factor of 2. The benefit of doubling VP to the load is maintained and the current carrying capability is also doubled, allowing smaller speaker loads to be supported. This configuration is typically used when higher power levels are required such as when driving a subwoofer channel.

Since smaller speaker loads of 4 ohms or less, similar to the half-bridge output topology, are allowed to be driven in this configuration, the value for L_{filt} must be halved to maintain a comparable LC filter response to the half-bridge and full-bridge configurations. Also note that the parallel full-bridge configuration should only be attempted with power stage devices which integrate all MOSFET devices in a single package. In this case, the characteristics for each MOSFET switch are highly correlated and matched to the other MOSFET switches such as to avoid cross-conduction currents and high levels of distortion due to switching errors.

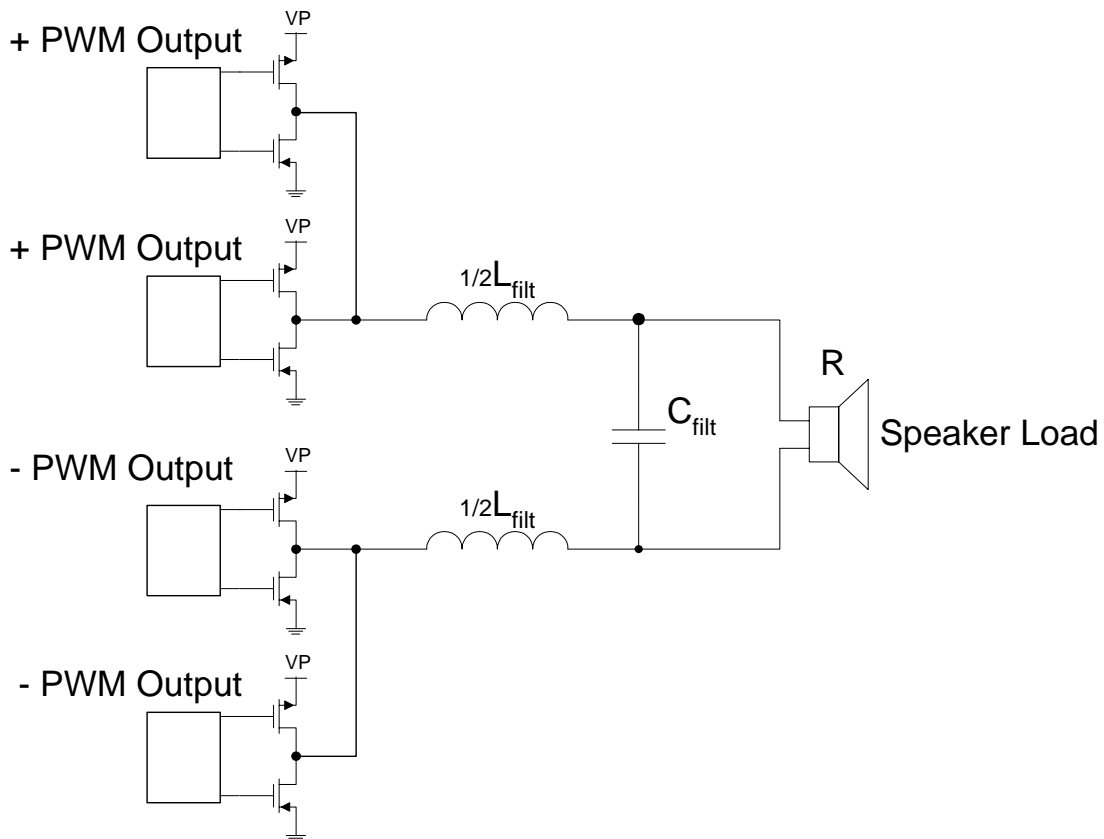


Figure 3. Parallel Full-Bridge Output Configuration

2.4 Power Calculations

A view of the downloaded spreadsheet is shown below. To modify the Assumptions or the Speaker Load in the calculations, double-click any cell with blue text within the spreadsheet. All parameters shown in blue can be modified with specific system or device parameters.

The Voltage Rail VP is the power supply nominal DC output expressed in volts. This value is taken at the input pin of the PWM power device.

The modulation index is the amount of full-scale signal that can be output from the PWM amplifier. This value is usually below 0.95 and is determined by both the modulator effectiveness and the ability of the PWM output power stage to handle small input pulse widths.

The PWM output Rds_on is the nominal series resistance of the MOSFET device as specified by the manufacturer. As the temperature of the power device rises, so will this value.

The inductor resistance is the resistance value of the inductor at DC. This value is specified by the inductor manufacturer and should be as low as possible. Typical values are between 0.05 and 0.15 ohms.

The capacitor's Equivalent Series Resistance (ESR) is specified by the component manufacturer. The capacitor ESR is only used in the half-bridge configurations when a capacitor is required to block any DC offset.

The "Power Out" calculation is the total power output for the specified channel. This is not the power delivered to the speaker load. The "Power Out" formula is: $\text{Power out} = (V_{\text{rms}})^2 / R_{\text{total}}$, where V_{rms} is the root mean square of the VP voltage rail multiplied by the modulation index. R_{total} is the sum of all the resistances along the amplifier

output path. In addition to the speaker load, these include the resistance of all the MOSFETs and filter inductors. Substituting gives:

$$\text{Power out} = (\text{VP} * \text{Mod. Index}/2.83)^2 / (\text{Spkr Load} + \text{PWM Rds}_{\text{on}} + \text{Ind. Resistance}).$$

The 2.83 value in the denominator converts the DC value of VP to an RMS value. For half-bridge configurations, the ESR of the capacitor is also added to the total resistance.

For full-bridge amplifier outputs, the current flow will actually incur the PWM Rds_on and the Inductor Resistance twice as it flows from one PWM output, through the load, and into the other PWM output. Because of the additional impedance, this configuration is a little less efficient than the others.

The parallel full-bridge amplifier is not only capable of supplying more current, it is more efficient than the full-bridge configuration. The reason is that since the two PWM outputs are in parallel, then the PWM Rds_on resistance of each output is also in parallel. This effectively cuts the total PWM Rds_on in half.

To calculate the actual power delivered to the speaker load, the "Total current" is calculated. The actual "Power at the load" is then the square of the "Total current" multiplied times the speaker load. This power level is somewhat lower than the "Power out" calculation due to the other resistive losses within the circuit. The 0.1% THD+N power number is the typical full scale, non-clipping output power at the load. The 1% THD+N power value represents a small amount of clipping when the output of the PWM modulator is brought above full scale and is approximately the 0.1% power output multiplied by 1.15. To approximate the generally specified 10% THD+N power value given by many amplifier manufacturers, multiply the 0.1% THD+N power output value by 1.75.

The "Power dissipation per channel" is the amount of power that will be dissipated within the MOSFETs for a single channel. The calculation is simply the square of the "Total current" multiplied by the PWM Rds_on for that channel. For bridge-tied channels, the effective PWM Rds_on is double that for a half-bridge channel. This increases the overall power dissipation for a channel which is configured for full-bridge operation. If multiple channels are contained within a single power output stage module, then the total power dissipation for all channels must be summed in order to calculate proper cooling requirements.

Assumptions	
Voltage Rail Vp (volts)	35
Modulation Index	0.87
PWM Output Rds_on (ohms)	0.25
Capacitor ESR (ohms)	0.05
Inductor Resistance (ohms)	0.05

Calculations									
	Half-Bridged Tied			Full-Bridge Tied			Parallel Full-Bridge Tied		
Speaker Load (ohms)	8	6	4	8	6	4	8	6	4
Power out (W)	13.86	18.23	26.61	53.85	70.16	100.67	55.46	72.93	106.46
Total current (rms)	1.29	1.69	2.47	2.50	3.26	4.68	2.58	3.39	4.95
Total current (peak)	1.82	2.40	3.50	3.54	4.61	6.61	3.64	4.79	7.00
Power at the Load (W)									
0.1% THD+N	13.28	17.23	24.47	50.09	63.79	87.54	53.13	68.91	97.89
1% THD+N (x1.15)	15.28	19.81	28.14	57.60	73.35	100.67	61.10	79.24	112.57
10% THD+N (x1.75)	23.25	30.15	42.83	87.66	111.63	153.19	92.99	120.59	171.31
Efficiency	0.96	0.94	0.92	0.93	0.91	0.87	0.96	0.94	0.92
Power Dissipation (W) per channel	0.42	0.72	1.53	3.13	5.32	10.94	1.66	2.87	6.12

3. REVISION HISTORY

Release	Date	Changes
Rev 1	May 2005	1st Preliminary Release

Table 1. Revision History

Contacting Cirrus Logic Support

For all product questions and inquiries contact a Cirrus Logic Sales Representative.

To find the one nearest to you go to www.cirrus.com

IMPORTANT NOTICE

Cirrus Logic, Inc. and its subsidiaries ("Cirrus") believe that the information contained in this document is accurate and reliable. However, the information is subject to change without notice and is provided "AS IS" without warranty of any kind (express or implied). Customers are advised to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current and complete. All products are sold subject to the terms and conditions of sale supplied at the time of order acknowledgment, including those pertaining to warranty, indemnification, and limitation of liability. No responsibility is assumed by Cirrus for the use of this information, including use of this information as the basis for manufacture or sale of any items, or for infringement of patents or other rights of third parties. This document is the property of Cirrus and by furnishing this information, Cirrus grants no license, express or implied under any patents, mask work rights, copyrights, trademarks, trade secrets or other intellectual property rights. Cirrus owns the copyrights associated with the information contained herein and gives consent for copies to be made of the information only for use within your organization with respect to Cirrus integrated circuits or other products of Cirrus. This consent does not extend to other copying such as copying for general distribution, advertising or promotional purposes, or for creating any work for resale.

CERTAIN APPLICATIONS USING SEMICONDUCTOR PRODUCTS MAY INVOLVE POTENTIAL RISKS OF DEATH, PERSONAL INJURY, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE ("CRITICAL APPLICATIONS"). CIRRUS PRODUCTS ARE NOT DESIGNED, AUTHORIZED OR WARRANTED FOR USE IN AIRCRAFT SYSTEMS, MILITARY APPLICATIONS, PRODUCTS SURGICALLY IMPLANTED INTO THE BODY, AUTOMOTIVE SAFETY OR SECURITY DEVICES, LIFE SUPPORT PRODUCTS OR OTHER CRITICAL APPLICATIONS. INCLUSION OF CIRRUS PRODUCTS IN SUCH APPLICATIONS IS UNDERSTOOD TO BE FULLY AT THE CUSTOMER'S RISK AND CIRRUS DISCLAIMS AND MAKES NO WARRANTY, EXPRESS, STATUTORY OR IMPLIED, INCLUDING THE IMPLIED WARRANTIES OF MERCHANTABILITY AND FITNESS FOR PARTICULAR PURPOSE, WITH REGARD TO ANY CIRRUS PRODUCT THAT IS USED IN SUCH A MANNER. IF THE CUSTOMER OR CUSTOMER'S CUSTOMER USES OR PERMITS THE USE OF CIRRUS PRODUCTS IN CRITICAL APPLICATIONS, CUSTOMER AGREES, BY SUCH USE, TO FULLY INDEMNIFY CIRRUS, ITS OFFICERS, DIRECTORS, EMPLOYEES, DISTRIBUTORS AND OTHER AGENTS FROM ANY AND ALL LIABILITY, INCLUDING ATTORNEYS' FEES AND COSTS, THAT MAY RESULT FROM OR ARISE IN CONNECTION WITH THESE USES.

Cirrus Logic, Cirrus, and the Cirrus Logic logo designs are trademarks of Cirrus Logic, Inc. All other brand and product names in this document may be trademarks or service marks of their respective owners.

Microsoft, is a registered trademark of Microsoft Corporation.