
Application Note

DESIGN CONSIDERATIONS WHEN USING THE CS7410 INTERNAL DAC

1. INTRODUCTION

The internal Delta-Sigma modulator inside the CS7410 allows the conversion of the digital PCM data inside the CS7410 to analog audio. The Delta-Sigma modulator inside the CS7410 converts the PCM data to over-sampled one-bit data. This data is output differentially on the LP/LN and RP/RN pins, low pass filtered and amplified to drive an external set of headphones. In the context of the familiar CMOS DAC, this approach separates the digital and analog portions of the DAC. The digital portion resides inside the CS7410 and the analog portion is implemented using discrete components.

2. DESIGN CONSIDERATIONS

In order to achieve the best possible performance from the internal Delta-Sigma modulator, the recommended circuit diagram shown in figure 4 or 6 and the recommended layout shown in figure 5 should be used. Failure to follow the recommended circuit design and layout can result in both poor overall dynamic range and distortion. There are several areas to pay careful attention to when designing your system.

2.1 Power Supply Routing and Filtering

For cost reasons, the analog output circuit operates from the digital 1.8 V and 3.3 V power supplies. Since these supplies are also used to power all the digital circuitry, they must

be carefully routed and filtered to prevent digital noise from corrupting the analog audio.

For best audio performance, the entire analog circuitry, including the 74AC74 logic part, should be connected to the same filtered 3.3 V supply and filtered ground. This filtered 3.3 V supply is identified as IDAC_3.3V in the attached schematic. The corresponding filtered analog ground node is identified as IDAC_GND in the attached schematic. The connecting traces for IDAC_3.3V and IDAC_GND should be routed straight from the 3.3 V regulator pins and not tapped anywhere near the CS7410 or any other logic circuit. The IDAC_3.3V/IDAC_GND filter components should be placed as close to the analog circuit as possible, not close to the 3.3 V regulator. Be careful to use high quality ferrite beads on leads as indicated in the attached circuit diagram. Failure to use the proper filtering will degrade the audio performance.

2.2 Reference Voltage Generation for the Op-Amp

The reference voltages for the headphone driver op-amps are generated from the 1.8 V digital supply and must be carefully designed and laid out. The filtered 1.8 V supply is identified as REF_VDD1 and REF_VDD2 in the attached schematic. It is very important to use separate filter circuits for each op-amp. Otherwise, the signal-to-idle-channel noise (or cross-talk) specification may degrade. Corresponding to REF_VDD1 and

REF_VDD2 are 2 other filtered ground nodes, called REF_GND1 and REF_GND2 that should be carefully treated. The connecting traces for REF_VDD1 / REF_GND1 and REF_VDD2 / REF_GND2 should be routed straight from the 1.8 V regulator pins and not tapped anywhere near the CS7410 or any other logic circuit. The filter components should be placed as close to the analog circuit as possible, not close to the 1.8 V regulator. Be careful to use high quality ferrite beads on leads as indicated in the attached circuit diagram. Failure to use the proper filtering will degrade the audio performance.

Each active device in the analog circuit requires good local power supply decoupling for correct operation. The 74AC74 requires a parallel 0.1/0.01 μ F capacitor pair placed as close to chip as possible and connected to the VCC and GND pins without vias. The op-amp requires a 0.1 μ F capacitor placed as close as possible to the chip and connected to the VDD/VSS pins without vias. The CS7410 also requires careful decoupling on its I/O supply pins. Each I/O supply pair should be decoupled with a 0.1 μ F capacitor placed as close to the chip as possible and connected to the chip pins with no vias.

2.3 Signal Routing

The high frequency one-bit data from the CS7410 DAC_LP, DAC_RP, and the PCM_XCLK signal must be routed carefully between the CS7410 and the 74AC74 to in order to preserve signal integrity. Excessive ringing, capacitive loading or jitter on these

signals can degrade the overall audio performance. In general, these signals should be kept as short as possible and routed over ground plane. Please refer to the attached layout diagram for preferred layout practices.

All the analog signals around the op-amp should be routed away from any digital signal traces. Analog routes should be short and routed on the top layer in a 2-layer design. The bottom layer should be flooded with continuous ground plane to create a low impedance ground return path and signal reference.

3. PERFORMANCE

Table 1 shows the performance of the reference design presented in this document as achieved with a modified SA03 development board. Plots corresponding to these measurements are shown in figures 1, 2, and 3 respectively. All measurements are taken using an Analog Precision System 2 with an AES-17 filter.

Parameter	Typical	Unit
THD+N (Note 1)	-75	dB
Dynamic Range (Note 2)	79	dB
Crosstalk (Note 3)	72	dB

Table 1: Performance of Reference Circuit 1

- 1) THD+N measured from 20-20kHz with an input of 1kHz, 0dBFS and the volume set to 1dB below output clipping.
- 2) Input signal of 1kHz, -60dBFS and volume setting same as in note 1.
- 3) Input on the left channel of 1kHz, 0dB and DC silence on the right and volume setting same as in note 1.

 


Figure 1. THD+N

 


Figure 2. Dynamic Range

 


Figure 3. Crosstalk

4. IMPLEMENTATION

Included in this application note is a recommended schematic and board layout for the entire internal DAC audio section for the CS7410. PADS / PowerLogic format schematics and PCB layout files are available from Cirrus Logic.

A second schematic detailing the use of a two-pole filter is also included. This filter design may increase the performance of the CS7410's converter beyond the numbers published here.

Important!

Please be aware that the performance of the circuit described here is dependent on the components used and board layout. The guidelines listed in previous sections of this document are absolutely critical to follow if one is to show similar results. Cirrus Logic provides **free** design review services for customers designing with any of our products, including schematic and board layout review. Please contact your local FAE or sales office to set up a formal review. For your convenience, our web site contains a Cirrus Logic sales office locator at <http://www.cirrus.com>.

 


Figure 5. PCB Stencil

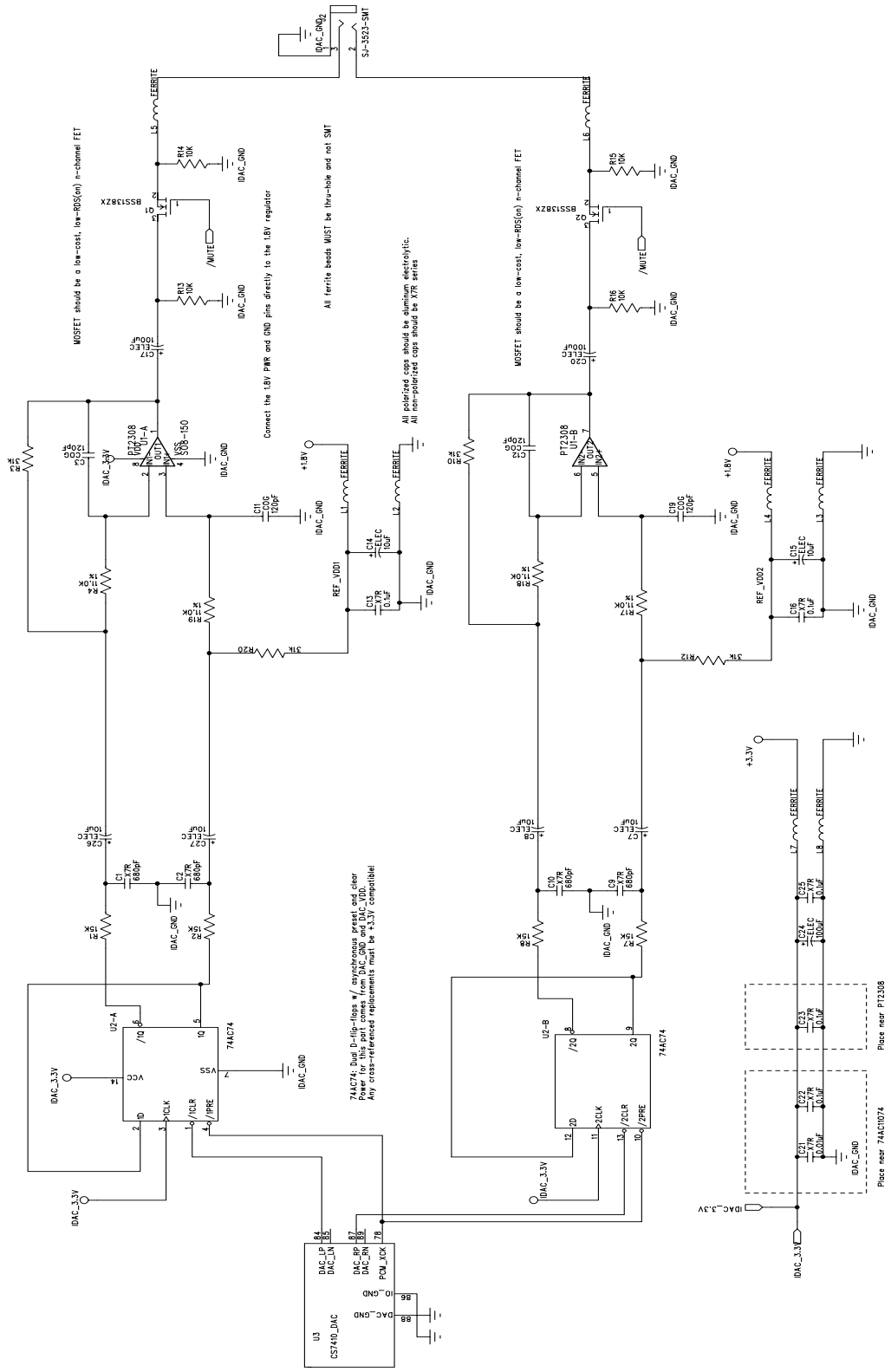


Figure 6. Alternative Schematic: 2-Pole Butterworth Filter at 30kHz with G=2.0

Contacting Cirrus Logic Support

For all product questions and inquiries contact a Cirrus Logic Sales Representative.
To find one nearest you go to www.cirrus.com

IMPORTANT NOTICE

"Preliminary" product information describes products that are in production, but for which full characterization data is not yet available. Cirrus Logic, Inc. and its subsidiaries ("Cirrus") believe that the information contained in this document is accurate and reliable. However, the information is subject to change without notice and is provided "AS IS" without warranty of any kind (express or implied). Customers are advised to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current and complete. All products are sold subject to the terms and conditions of sale supplied at the time of order acknowledgment, including those pertaining to warranty, patent infringement, and limitation of liability. No responsibility is assumed by Cirrus for the use of this information, including use of this information as the basis for manufacture or sale of any items, or for infringement of patents or other rights of third parties. This document is the property of Cirrus and by furnishing this information, Cirrus grants no license, express or implied under any patents, mask work rights, copyrights, trademarks, trade secrets or other intellectual property rights. Cirrus owns the copyrights associated with the information contained herein and gives consent for copies to be made of the information only for use within your organization with respect to Cirrus integrated circuits or other products of Cirrus. This consent does not extend to other copying such as copying for general distribution, advertising or promotional purposes, or for creating any work for resale.

An export permit needs to be obtained from the competent authorities of the Japanese Government if any of the products or technologies described in this material and controlled under the "Foreign Exchange and Foreign Trade Law" is to be exported or taken out of Japan. An export license and/or quota needs to be obtained from the competent authorities of the Chinese Government if any of the products or technologies described in this material is subject to the PRC Foreign Trade Law and is to be exported or taken out of the PRC.

CERTAIN APPLICATIONS USING SEMICONDUCTOR PRODUCTS MAY INVOLVE POTENTIAL RISKS OF DEATH, PERSONAL INJURY, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE ("CRITICAL APPLICATIONS"). CIRRUS PRODUCTS ARE NOT DESIGNED, AUTHORIZED OR WARRANTED FOR USE IN AIRCRAFT SYSTEMS, MILITARY APPLICATIONS, PRODUCTS SURGICALLY IMPLANTED INTO THE BODY, LIFE SUPPORT PRODUCTS OR OTHER CRITICAL APPLICATIONS (INCLUDING MEDICAL DEVICES, AIRCRAFT SYSTEMS OR COMPONENTS AND PERSONAL OR AUTOMOTIVE SAFETY OR SECURITY DEVICES). INCLUSION OF CIRRUS PRODUCTS IN SUCH APPLICATIONS IS UNDERSTOOD TO BE FULLY AT THE CUSTOMER'S RISK AND CIRRUS DISCLAIMS AND MAKES NO WARRANTY, EXPRESS, STATUTORY OR IMPLIED, INCLUDING THE IMPLIED WARRANTIES OF MERCHANTABILITY AND FITNESS FOR PARTICULAR PURPOSE, WITH REGARD TO ANY CIRRUS PRODUCT THAT IS USED IN SUCH A MANNER. IF THE CUSTOMER OR CUSTOMER'S CUSTOMER USES OR PERMITS THE USE OF CIRRUS PRODUCTS IN CRITICAL APPLICATIONS, CUSTOMER AGREES, BY SUCH USE, TO FULLY INDEMNIFY CIRRUS, ITS OFFICERS, DIRECTORS, EMPLOYEES, DISTRIBUTORS AND OTHER AGENTS FROM ANY AND ALL LIABILITY, INCLUDING ATTORNEYS' FEES AND COSTS, THAT MAY RESULT FROM OR ARISE IN CONNECTION WITH THESE USES.


Cirrus Logic, Cirrus, and the Cirrus Logic logo designs are trademarks of Cirrus Logic, Inc. All other brand and product names in this document may be trademarks or service marks of their respective owners.

MPEG Layer-3 (MP3) audio coding technology licensed from Fraunhofer Gesellschaft and Thomson multimedia. Supply of this product only conveys a license for personal, private and non-commercial use. Supply of this product does not convey a license under the relevant intellectual property of Thomson multimedia and/or Fraunhofer Gesellschaft nor imply any right to use this product in any finished end user or ready-to-use final product. An independent license for such use is required. For details, please visit <http://www.mp3licensing.com>.

Windows Media is a registered trademark of Microsoft Corporation. The product includes technology owned by Microsoft Corporation and cannot be used or distributed without a license from Microsoft Licensing, Inc.

Cirrus Logic, Cirrus, and the Cirrus Logic logo designs are trademarks of Cirrus Logic, Inc. All other brand and product names in this document may be trademarks or service marks of their respective owners.

• **Notes** •

 

CIRRUS LOGIC[®]