



Minimizing Start-up time After Coming out of Sleep

The CS5101A/CS5102A A/D converters include a sleep function to help reduce power consumption. The sleep function is a useful method of reducing the average power consumption in a data acquisition system if the converter need not be operated continuously. When power is first applied to the CS5101A/CS5102A, the device must be calibrated. Then if the sleep function is activated, the calibration register is maintained.


When the CS5101A/CS5102A comes out of sleep, how quickly the converter can perform its first conversion depends on several different factors. When in sleep, the gate (CLKIN-XOUT) used for the crystal oscillator is powered down. Therefore, when coming out of sleep, the oscillator must take some time to start up. The typical start-up time for a 2 to 8 MHz crystal oscillator is several milliseconds. The time it takes for the oscillator to start up can be eliminated if an external clock is used. Figure 1 illustrates a J-K flip-flop being used to control an external clock to the CS5102A.

A second source of delay when coming out of sleep, is that the REFBUF capacitor must be charged. While asleep the capacitor will discharge because the on-chip current source which normally keeps it charged is shut off. When coming out of sleep, the on-chip current source is powered up. It must then charge the REFBUF capacitor to a value nearly equal to the VREF voltage. The time it takes to charge the REFBUF capacitor is about 3 milliseconds in the CS5101A and about 50 milliseconds in the CS5102A. This time can be eliminated if the

REFBUF capacitor is kept precharged. This can be accomplished by keeping the external reference voltage powered up and connecting a 2 k Ω resistor between pins 20 and 21 (VREF and REFBUF). See Figure 1.

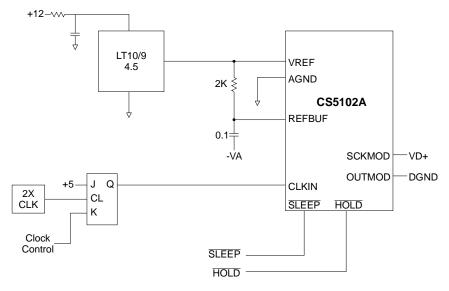By using an external clock and precharging the REFBUF capacitor, the start-up time after coming out of sleep can be minimized. Before performing the first conversion the internal circuitry must become stable after which the converter must go through a tracking cycle. The tracking cycle time is a function of the CLKIN rate (see CS5101A/2A Datasheet).





Note: Only pertinent pins are shown for simplicity

Figure 1. CS5102A Start-up Enhancements.

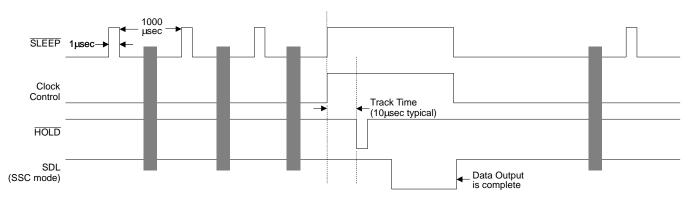


Figure 2. Timing for "shallow sleep" function (Timing segments not to scale).





Minimizing Start-up time After Coming out of Sleep

The CS5101A/CS5102A A/D converters include a sleep function to help reduce power consumption. The sleep function is a useful method of reducing the average power consumption in a data acquisition system if the converter need not be operated continuously. When power is first applied to the CS5101A/CS5102A, the device must be calibrated. Then if the sleep function is activated, the calibration register is maintained.


When the CS5101A/CS5102A comes out of sleep, how quickly the converter can perform its first conversion depends on several different factors. When in sleep, the gate (CLKIN-XOUT) used for the crystal oscillator is powered down. Therefore, when coming out of sleep, the oscillator must take some time to start up. The typical start-up time for a 2 to 8 MHz crystal oscillator is several milliseconds. The time it takes for the oscillator to start up can be eliminated if an external clock is used. Figure 1 illustrates a J-K flip-flop being used to control an external clock to the CS5102A.

A second source of delay when coming out of sleep, is that the REFBUF capacitor must be charged. While asleep the capacitor will discharge because the on-chip current source which normally keeps it charged is shut off. When coming out of sleep, the on-chip current source is powered up. It must then charge the REFBUF capacitor to a value nearly equal to the VREF voltage. The time it takes to charge the REFBUF capacitor is about 3 milliseconds in the CS5101A and about 50 milliseconds in the CS5102A. This time can be eliminated if the

REFBUF capacitor is kept precharged. This can be accomplished by keeping the external reference voltage powered up and connecting a 2 k Ω resistor between pins 20 and 21 (VREF and REFBUF). See Figure 1.

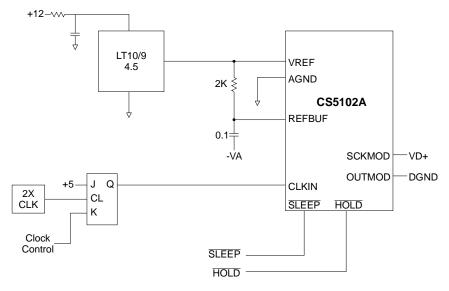By using an external clock and precharging the REFBUF capacitor, the start-up time after coming out of sleep can be minimized. Before performing the first conversion the internal circuitry must become stable after which the converter must go through a tracking cycle. The tracking cycle time is a function of the CLKIN rate (see CS5101A/2A Datasheet).





Note: Only pertinent pins are shown for simplicity

Figure 1. CS5102A Start-up Enhancements.

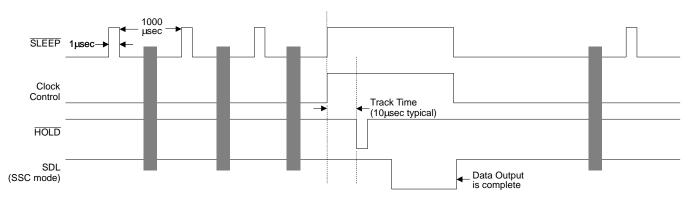


Figure 2. Timing for "shallow sleep" function (Timing segments not to scale).





Minimizing Start-up time After Coming out of Sleep

The CS5101A/CS5102A A/D converters include a sleep function to help reduce power consumption. The sleep function is a useful method of reducing the average power consumption in a data acquisition system if the converter need not be operated continuously. When power is first applied to the CS5101A/CS5102A, the device must be calibrated. Then if the sleep function is activated, the calibration register is maintained.


When the CS5101A/CS5102A comes out of sleep, how quickly the converter can perform its first conversion depends on several different factors. When in sleep, the gate (CLKIN-XOUT) used for the crystal oscillator is powered down. Therefore, when coming out of sleep, the oscillator must take some time to start up. The typical start-up time for a 2 to 8 MHz crystal oscillator is several milliseconds. The time it takes for the oscillator to start up can be eliminated if an external clock is used. Figure 1 illustrates a J-K flip-flop being used to control an external clock to the CS5102A.

A second source of delay when coming out of sleep, is that the REFBUF capacitor must be charged. While asleep the capacitor will discharge because the on-chip current source which normally keeps it charged is shut off. When coming out of sleep, the on-chip current source is powered up. It must then charge the REFBUF capacitor to a value nearly equal to the VREF voltage. The time it takes to charge the REFBUF capacitor is about 3 milliseconds in the CS5101A and about 50 milliseconds in the CS5102A. This time can be eliminated if the

REFBUF capacitor is kept precharged. This can be accomplished by keeping the external reference voltage powered up and connecting a 2 k Ω resistor between pins 20 and 21 (VREF and REFBUF). See Figure 1.

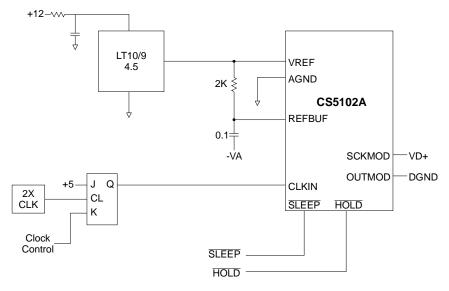By using an external clock and precharging the REFBUF capacitor, the start-up time after coming out of sleep can be minimized. Before performing the first conversion the internal circuitry must become stable after which the converter must go through a tracking cycle. The tracking cycle time is a function of the CLKIN rate (see CS5101A/2A Datasheet).





Note: Only pertinent pins are shown for simplicity

Figure 1. CS5102A Start-up Enhancements.

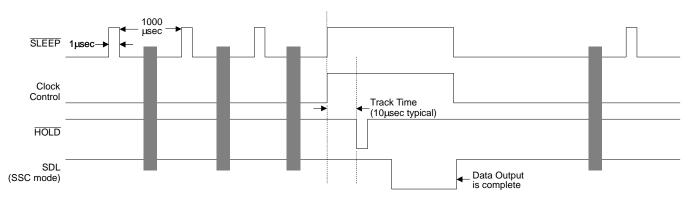


Figure 2. Timing for "shallow sleep" function (Timing segments not to scale).





Minimizing Start-up time After Coming out of Sleep

The CS5101A/CS5102A A/D converters include a sleep function to help reduce power consumption. The sleep function is a useful method of reducing the average power consumption in a data acquisition system if the converter need not be operated continuously. When power is first applied to the CS5101A/CS5102A, the device must be calibrated. Then if the sleep function is activated, the calibration register is maintained.


When the CS5101A/CS5102A comes out of sleep, how quickly the converter can perform its first conversion depends on several different factors. When in sleep, the gate (CLKIN-XOUT) used for the crystal oscillator is powered down. Therefore, when coming out of sleep, the oscillator must take some time to start up. The typical start-up time for a 2 to 8 MHz crystal oscillator is several milliseconds. The time it takes for the oscillator to start up can be eliminated if an external clock is used. Figure 1 illustrates a J-K flip-flop being used to control an external clock to the CS5102A.

A second source of delay when coming out of sleep, is that the REFBUF capacitor must be charged. While asleep the capacitor will discharge because the on-chip current source which normally keeps it charged is shut off. When coming out of sleep, the on-chip current source is powered up. It must then charge the REFBUF capacitor to a value nearly equal to the VREF voltage. The time it takes to charge the REFBUF capacitor is about 3 milliseconds in the CS5101A and about 50 milliseconds in the CS5102A. This time can be eliminated if the

REFBUF capacitor is kept precharged. This can be accomplished by keeping the external reference voltage powered up and connecting a 2 k Ω resistor between pins 20 and 21 (VREF and REFBUF). See Figure 1.

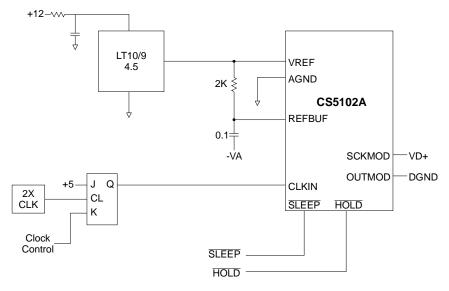By using an external clock and precharging the REFBUF capacitor, the start-up time after coming out of sleep can be minimized. Before performing the first conversion the internal circuitry must become stable after which the converter must go through a tracking cycle. The tracking cycle time is a function of the CLKIN rate (see CS5101A/2A Datasheet).





Note: Only pertinent pins are shown for simplicity

Figure 1. CS5102A Start-up Enhancements.

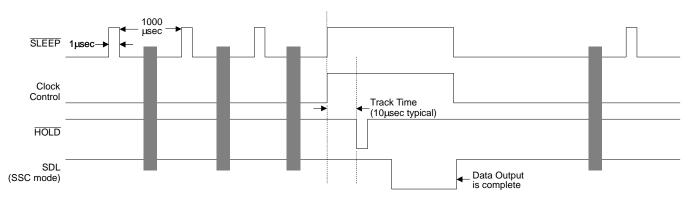


Figure 2. Timing for "shallow sleep" function (Timing segments not to scale).