

## Electroluminescent Lamp Driver Evaluation Board

### Introduction

This Application Note introduces an Evaluation Board for IMP EL driver ICs. It is supplied with the IMP803 but can also be used with the IMP560 and IMP525: all 3 have identical pinouts.

### EL Lamps and Drivers

An electroluminescent (EL) lamp consists of a phosphor coating on a dielectric that is sandwiched between two conductors. Electrically, it looks like a capacitor. Such a lamp requires drive from a high alternating voltage source in order to emit light. This can be obtained from IMP integrated circuits IMP803, IMP560 and IMP525 that convert low voltages into appropriate high-voltage waveforms.

Small EL lamps exhibit about 2 to 6nF/in<sup>2</sup>. IMP Driver ICs are capable of powering EL lamps that have total equivalent load capacitances up to 30nF, so this works out to a maximum of around 15 square inches. "Powering" in this context means enabling enough light for the application, which can range from LCD backlights (relatively bright in a handheld device) to pagers (medium-bright, in a poorly-lit room), to night-lights (faint, in a dark room).

### IMP Driver IC System Diagram

As shown in *Figure 1*, these ICs contain a high-voltage MOSFET switch, an output H-bridge, and oscillators to drive each. The switch, combined with an external inductor and diode, form a step-up (boost) converter that transforms the input voltage to 45-90 volts across capacitor  $C_S$ . This, in turn, is switched from one side of the load (the EL lamp) to the other by a commutating bridge, driven by its own oscillator. This action causes the lamp to experience twice the  $C_S$  value (i.e. 90-180 volts peak-to-peak) with no DC component.

A typical application uses a switch frequency of 80kHz and bridge commutation frequency of 360Hz. These frequencies are controllable via external resistors;  $R_{SW}$  for the boost converter and  $R_{EL}$  for the output driver.  $R_{EL}$  influences brightness, color and EL lamp life.  $R_{SW}$  controls converter efficiency. Both affect power consumption.

### IMP Driver IC System Diagram

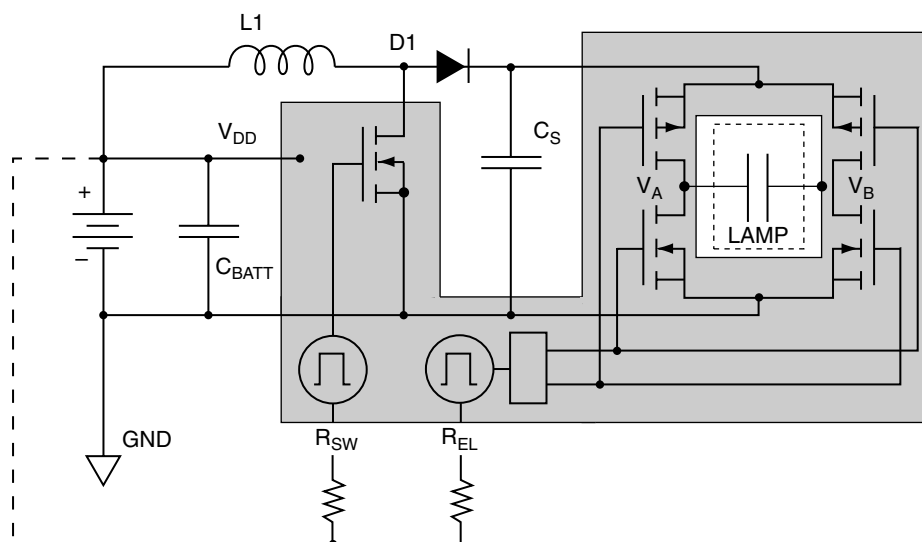


Figure 1. Circuitry in gray is on-chip.




## Basic Circuit, Plus Variations

In normal operation,  $V_{DD}$  is one or two 1.5V cells and  $L1$  is a tiny ferrite-bobbin inductor.  $R_{SW}$  and  $R_{EL}$  control their respective oscillators. If a logic-controllable shutdown is desired,  $R_{SW}$  may be switched between  $V_{DD}$  and GND ( $I_{DDQ} = 1\mu A$  max.). Conversely, if shutdown is via  $V_{DD}$ ,  $R_{SW}$  should then be connected to  $V_{DD}$  as shown by the dotted line in *Figure 3*.

$R_{CL}$  is included to protect the bridge against peak currents during commutation. A value of  $500\Omega$  to  $2k\Omega$  is suitable.

In use, the inductor current can reach several tens of milliamperes, so in single-battery applications it is recommended that the low-current shutdown capability of the driver IC be utilized. This is done by connecting  $R_{SW}$  (point A on the schematics) to either  $V_{DD}$  (ON) or GND (OFF). With power source(s) connected, shutdown (standby) current is typically much lower than  $1\mu A$ .

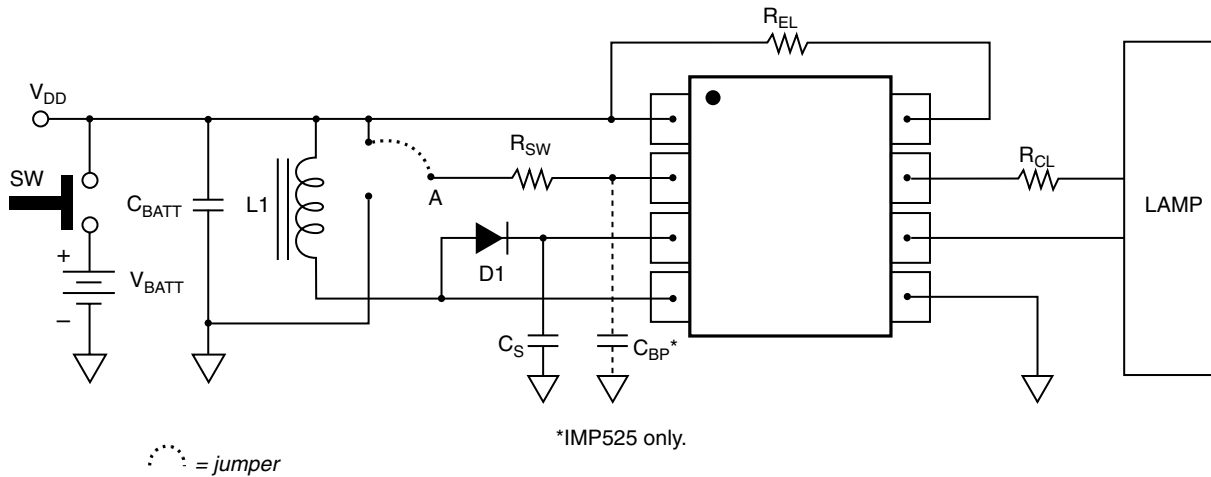


*Figure 3. Basic EL Lamp Driver.*

## Reducing Component Count

Having said that keeping  $R_{CL}$  is a good idea, it is true that removing as many components as possible may also be desirable. For the IMP803,  $R_{EL}$  and  $R_{SW}$  may be combined as shown in *Figure 4*. Varying  $R_{EL}$  causes a visible change in brightness and color, but a similar variation in  $R_{SW}$  (affecting oscillator frequency and power consumption) is much less noticeable. Combining the two is thus


a valid way to save a resistor. The bypass capacitor  $C_{BP}$  (IMP525 only) reduces display flicker in noisy environments, such as when there is no ground plane.

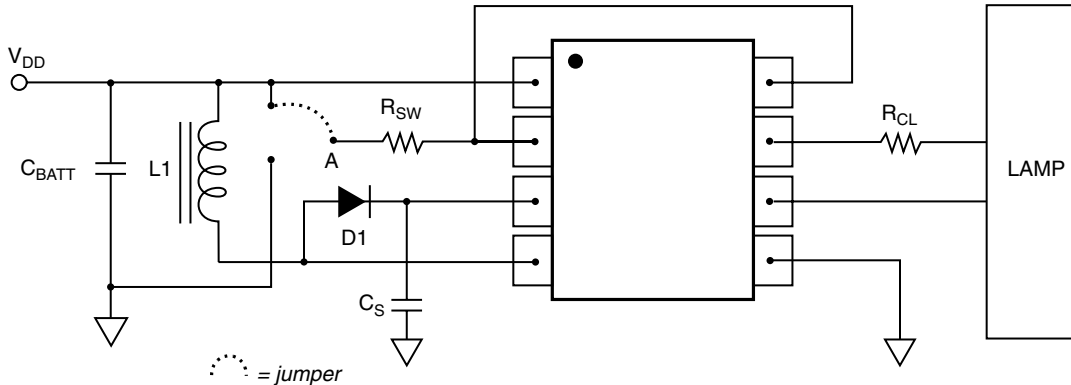

*Figure 4. Using  $R_{SW}$  to supply current for both switch and EL oscillators, and also serve as a low-current on/off switch (IMP803 only).*

Using the circuit in *Figure 5*, one can utilize an available  $V_{IN}$  that is higher or lower than the allowable  $V_{DD}$ . The logic shutdown may also be separated from  $V_{DD}$ . Such arrangements are helpful when the inductor supply is too low for the IC, or the display size requires a voltage that is too high for the IC.

A higher  $V_{IN}$  will need a higher switching frequency to keep the inductor out of saturation. In all cases, note the presence of HIGH VOLTAGE!

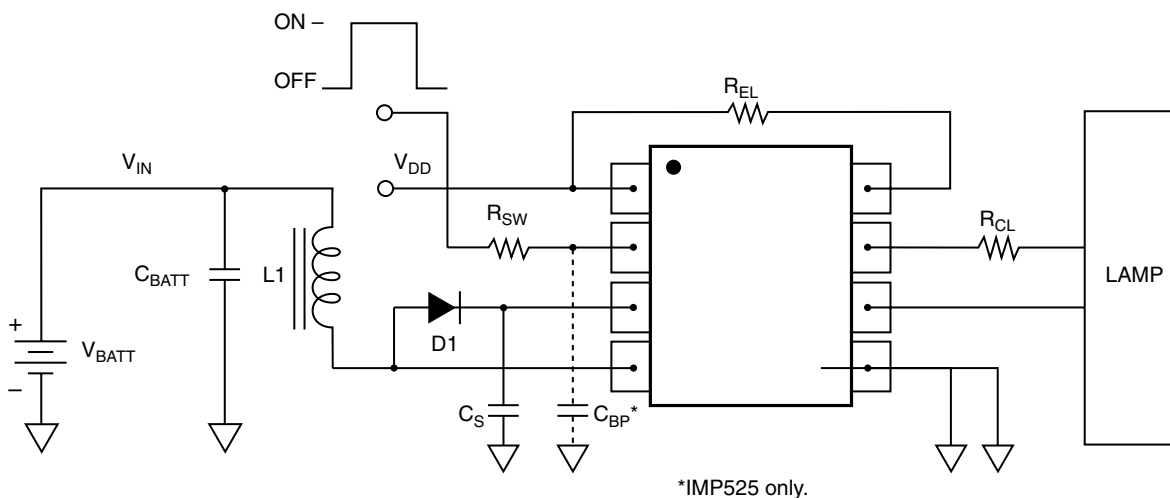

*Figure 5. General Circuit, where chip  $V_{DD}$ , on/off logic and  $V_{IN}$  are all different.*

## Evaluation Board

The ELD002 is a PC board for evaluation and experimentation purposes. More compact arrangements are easily achieved by using surface-mounted components exclusively. The various possible connections mirror the options discussed in the data sheet and the Application Note. While the IMP803 is supplied on the board, other pin-compatible drivers may be substituted.

The two dark patches are the connections for the EL lamp which are made using conductive double-sided tape. The display itself is held down with ordinary double-sided tape. Taping is advantageous for several reasons, among which are that lamps with

staked connecting terminals generally cost more, and they are a possible site for mechanical (and thus electrical) failure.

As a general precaution, note that HIGH VOLTAGE exists on the board; around 180V or so. The current level is low so there is no danger, except possible pain if a tender skin area or open cut contacts the HV sections.

There are extra holes for capacitors (if needed), and the hole spacings are wide enough to accommodate 1/4W resistors. Corner mounting holes have also been provided.

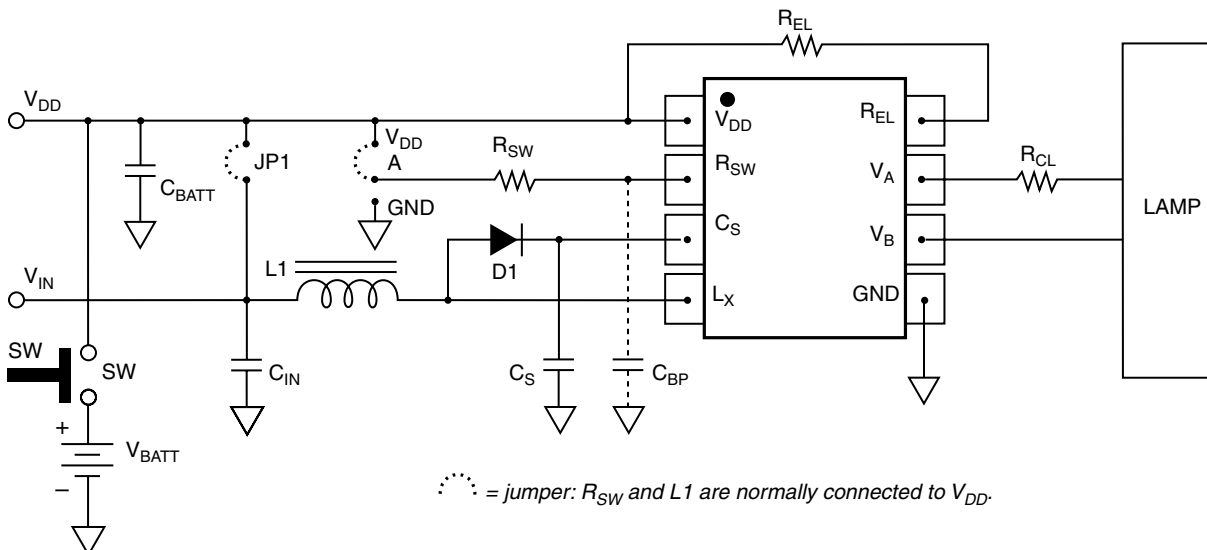
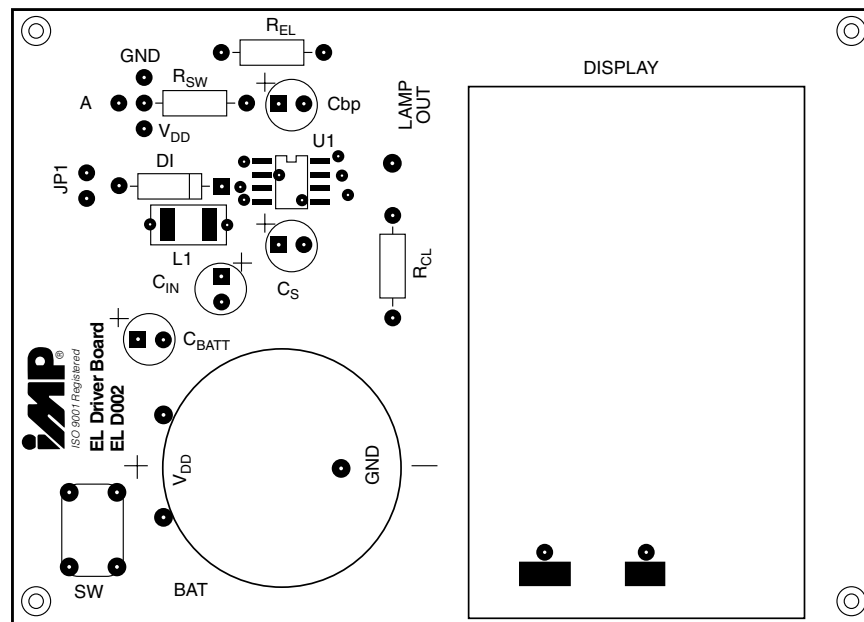


Figure 6. Evaluation Board Layout and Schematic.

## Some Battery Considerations

To keep the board light in weight, a Li-Mn power source was selected. When energized, the drain from the circuit is around 22mA, thus the CR battery chemistry is preferred over the BR for its superior pulse performance. If long-term continual illumination is anticipated and space is not an issue, alkaline batteries may be more economical.

With the IMP803 and 560 $\mu$ H inductor supplied, regulation begins at about 3-3.5V, but display illumination appears virtually

unchanged above 2.7V. When choosing the battery chemistry, it is a good idea to match the cell "plateau" voltages to this. For example, a typical NiCad plateau is 1.2V under load, so more than 2 cells would be needed. Alkaline plateaus are somewhat higher, and they differ with size, shape and duty, so 2 cells could suffice. Li-Mn coin cells have their voltage plateau under load at about 2.85 volts. They can drop lower, but they also return to close to 3V when the load is removed.

## Additional Points

- 1) To experiment with the *Figure 4* scheme, a jumper may be run from the rightmost pad of  $R_{EL}$  to the leftmost pad of  $C_{BP}$  (with the + above it). Start with an  $R_{SW}$  of 750k $\Omega$ . Short leads and a ground plane are more critical in this arrangement.
- 2)  $C_S$  should be 10nF - 100nF.
- 3) The IMP803, IMP560 and IMP525 datasheets show performance with different inductors. For example, high-voltage regulation is reached earlier with lower  $L$ , but this requires more current. This may be partially offset by adjustment of the oscillator resistors.
- 4) To experiment with multiple supplies, the appropriate jumpers may be removed.
- 5) The inclusion of  $R_{CL}$  should be stressed: while 500 $\Omega$  to 10k $\Omega$  has been used, 2k $\Omega$  is the best all-around value.

## Layout Rules for Other Arrangements

- 1) A ground plane is recommended to keep stray high frequencies confined. In a very small area, the need for a ground plane may be nil. A totally surface-mount arrangement would make such a plane difficult anyway.
- 2) Locate high voltages away from the high-impedance elements  $R_{EL}$  and  $R_{SW}$ .
- 3) Make sure that  $C_S$  has a rating of at least 100V.
- 4) The diode should have good reverse-recovery characteristics (the general-purpose 1N4148 is adequate) and should be rated for pulsed BV > 100V for the IMP803, and pulsed BV > 75V for the IMP560 and IMP525.
- 5) Shutdown by a logic-level signal is possible by connecting  $R_{SW}$  to ground ( $R_{SW}$  is normally connected to  $V_{DD}$ ). This on/off logic uses only 1 $\mu$ A max. when connected at this location.
- 7) Required voltage ratings for the capacitors other than  $C_S$  are flexible, and need only reflect actual stresses plus a safety margin.

## Bill of Materials for ELD001

Component	Description	Manufacturer	Part Number
Resistors ( $\pm 5\%$ )	See Table, below		
Capacitors ( $\pm 20\%$ )	See Table, below	Murata	RPE121/122 Series
Switch	SPST, momentary	Panasonic	P8008S
Battery	3.0V Li-Mn Coin	Sony Panasonic	CR2450-HE4 CR2354-IGU
Inductor	L1 = 560 $\mu$ H	Murata	LQH4N561K04
Diode	D1 = 1N4148		
Lamp	1.3" x 2.05"	MetroMark or other	
Conductive Tape	Connects display	Adhesives Research	ARclad 8001
Double-Sided Tape	Holds display down	3M	Type 665

## Key to Components and Ratings

Component	Value	Function	Comments
R <sub>SW</sub>	30k $\Omega$ to 3M $\Omega$	Sets switch osc. frequency.	Decrease R to increase frequency.
R <sub>EL</sub>	500k $\Omega$ to 10M $\Omega$	Sets bridge osc. frequency.	Decrease R to increase frequency.
R <sub>CL</sub>	500 $\Omega$ to 2k $\Omega$	Limits output current.	Protects IC.
C <sub>S</sub>	0.01 $\mu$ F to 0.1 $\mu$ F, 100V	Stores high voltage.	Use low values for large lamps.
C <sub>BATT</sub>	0.1 $\mu$ F, 10V	Supply bypass.	Keeps supply impedance low.
C <sub>BP</sub>	1nF, 10V	Lowers noise at R <sub>SW</sub> .	IMP525 only.
C <sub>IN</sub>	0.1 $\mu$ F to 22 $\mu$ F	Supply bypass.	Keeps supply impedance low.
L1	100 $\mu$ H to 1mH	Stores energy.	Small L, high f increases V <sub>OUT</sub> .
D1	100V, 10mA (1N4148)	Passes energy from L to C <sub>S</sub> .	Use fast recovery type.

## APPENDIX: Introduction to EL Lamps

Chemical compounds, called phosphors, glow when energy is applied to them. This excitation energy can come from conducted or radiated electrons, or an electric field. A common example of this process is found in the emitted (radiated) electrons that impinge on the dots and stripes of color monitors and TVs, whose phosphors emit everything from pure colors to white light, depending on their formulations.

Backlights and lamps generally are simpler, employing a manganese-activated zinc sulfide phosphor (ZnS:Mn) that is excited by a high-voltage (> 40V) AC electric field (DC can shorten the lamp life). Fabrication involves depositing the phosphor as a thin film onto a BaTiO<sub>3</sub> dielectric between conducting planes, like a capacitor: one of the planes is the transparent conductor, indium tin oxide (ITO). The lamp color depends on phosphor formulation, but also on its physical realization (i.e. encapsulation, resins, dyes, etc.), plus the characteristics of the drive circuitry.

The IMP line of drivers is targeted mainly at applications like backlight EL and stand-alone pre-printed or segmented lamps. Backlights are used with the Liquid-Crystal Displays found in cellular telephones, pagers, Personal Digital Assistants (PDAs), and general-purpose local lighting applications where low power consumption without heat is important (e.g. airline cockpits, medical instrumentation).

The excitation required for lamps ranges from tens to hundreds of volts, at frequencies from 60Hz to a few kHz. Each display has an optimum combination depending on size, color, efficiency and desired brightness.

In general, the changes in brightness with frequency and voltage are nearly linear. These facts allow tradeoffs. For example, if going above a certain voltage is not allowed, an increase in drive frequency may achieve the same result.


## Addendum

The new evaluation board ELD002 is now available and will be sent out to all new purchasers. This Addendum will serve to explain the differences and update the information in AN-1.

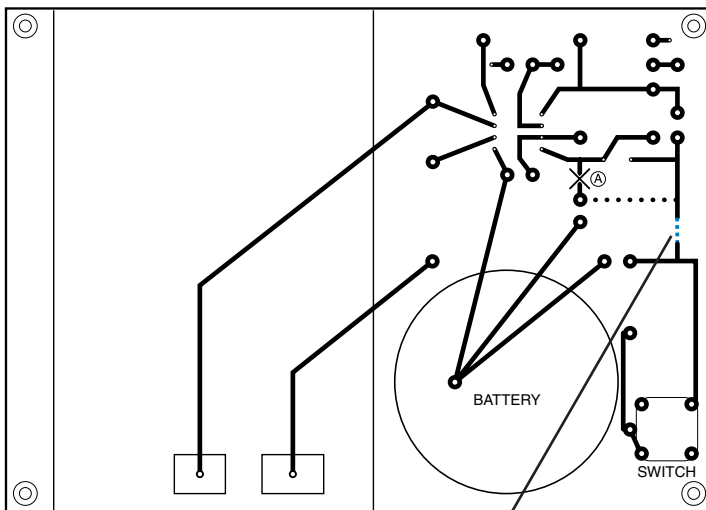
### Changes

The diagrams below show the basic wiring of ELD001 (see AN-1, Figure 6) on the left and ELD002 on the right. The difference is that, with ELD002, the 3V cell is switched to the  $V_{DD}$  pin, and this voltage only goes to the inductor if JP1 is connected. If JP1 is open, an alternate voltage can be used to power the inductor.


In contrast, the ELD001 switched power to the inductor, and to  $V_{DD}$  only if JP1 was connected. This was intended to demonstrate the logic-level shutdown ability of the IMP803: by using the pushbutton for the heavy current to the inductor, the  $V_{DD}$  pin could be tied to a voltage source and the chip enabled/disabled by a logic level of  $V_{DD}$  or ground applied to  $R_{SW}$ . The ELD002 board allows both features to be exercised. For ELD001 users who wish to modify their boards, the changes are shown below.




Cut the trace at this point.

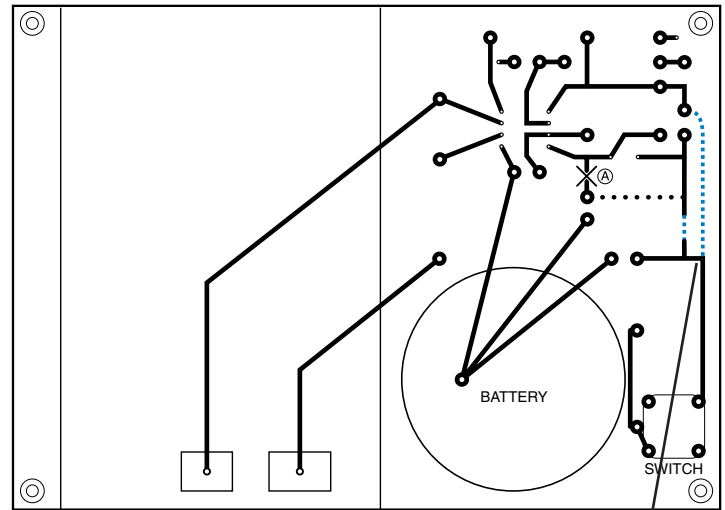

Extend the trace (using wire) and connect at this point.

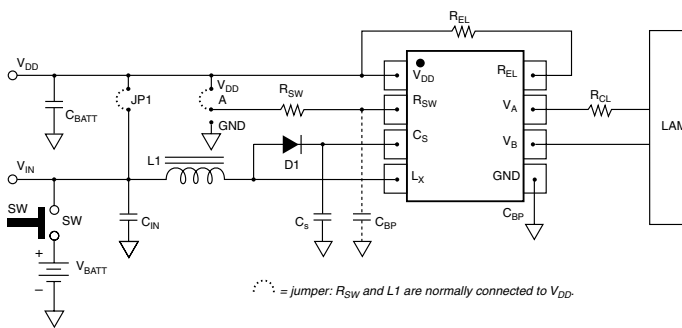

ELD001

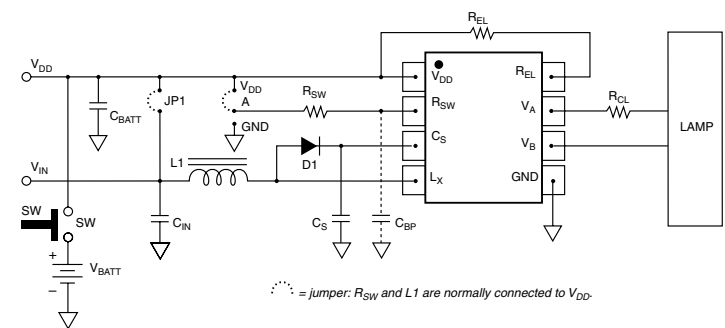

ELD002

### Updates

- 1)  $I_{DDQ}$  is listed as  $1\mu A$  max. (AN-1, pp 3, 6, 7). Extensive testing has shown this to be much too conservative:  $25nA$  is much more typical.
- 2) In using  $R_{SW}$  to shut-down the IMP803 (only  $25nA$ ),  $R_{EL}$  can remain connected to the  $V_{DD}$  pin; only 1 resistor then needs to be switched.
- 3) Under some circumstances,  $R_{CL}$  can be omitted. Consult IMP for details.
- 4) For single-battery systems (the vast majority), the capacitor shown on the diagram as  $C_{IN}$  is not needed. For cases where it is needed, further "surgery" is required: cut the trace shown as  $\textcircled{A}$  and reconnect it as per the dotted line.





IMP, Inc.  
Corporate Headquarters  
2830 N. First Street  
San Jose, CA 95134-2071  
Tel: 408-432-9100  
Tel: 800-438-3722  
Fax: 408-434-0335  
e-mail: [info@impinc.com](mailto:info@impinc.com)  
<http://www.impweb.com>

The IMP logo is a registered trademark of IMP, Inc.  
All other company and product names are trademarks of their respective owners.

© 1999 IMP, Inc.  
Printed in USA  
Publication #: 9001  
Revision: A  
Issue Date: 04/19/99  
Type: Preliminary