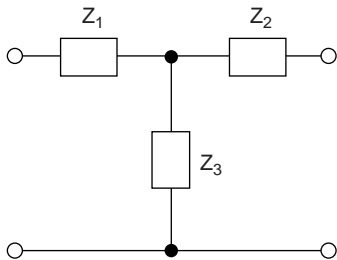


The objective of this application note is to (1) illustrate the idea of using digitally controlled potentiometers to form tee networks and (2) provide the design engineer with reference designs for using tee networks and their derivatives as building blocks in analog circuits and systems.


**Basic Ideas**

A tee network is a two-port network whose configuration, Figure 1, is in the form of the letter tee. The components used to implement the tee network can themselves be another network but they are usually single resistors and capacitors. Tee networks are used as building blocks in analog circuits including amplifiers, filters, oscillators, and convertors. The three-terminal potentiometer, along with passive parts, eases the implementation of the tee network. If a digitally-controlled potentiometer is used, Figure 2, the analog section will


provide variability to the circuit and the digital controls will provide programmability. The basic tee network can be expanded to include the bridged tee, twin tee, and  $\pi$  networks which are shown in Figure 3. The movement of the wiper of the potentiometer introduces a new degree of freedom  $k$  in the tee network where  $k$  is a number that varies from 0 to 1 and reflects the proportionate position of the wiper from one end of the pot (0) to the other end of the pot (1). The resistances from the wiper to the low terminal and the wiper to the high terminal are modeled as  $kR$  and  $(1-k)R$  and are shown in Figure 4. The resistance  $R$  is the same as the potentiometer's end to end resistance called  $R_{TOTAL}$ . In analyzing many analog circuits, the tee network is treated as a two port and its input-output relationship is described by the short-circuit admittance coefficients  $Y_{21}$  and  $Y_{12}$ .




**FIGURE 1. "T" NETWORK**

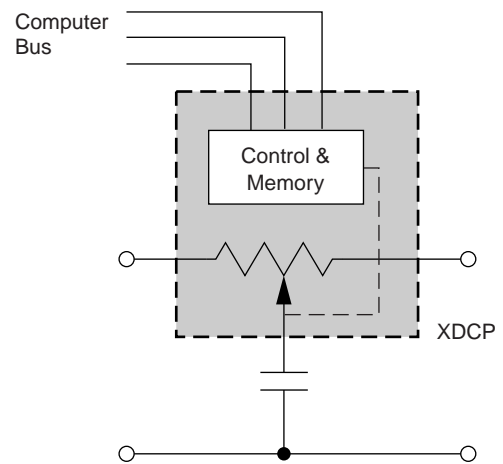

**FIGURE 2. PROGRAMMABLE TEE NETWORK**

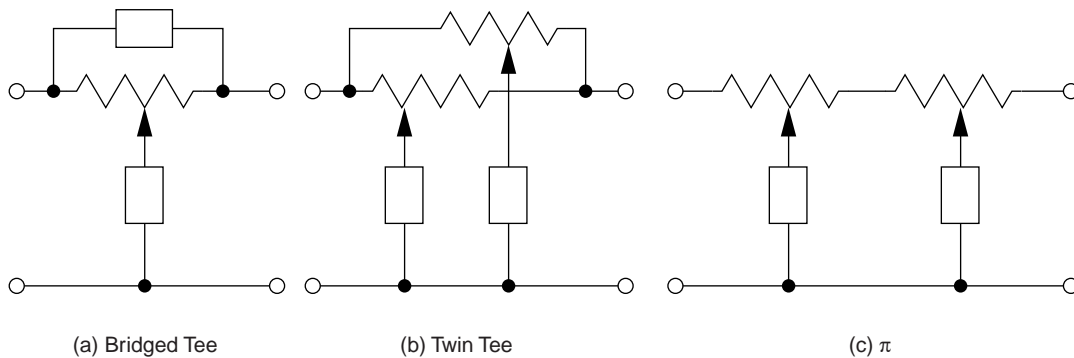

**FIGURE 3. TEE NETWORK PARAMETERS**

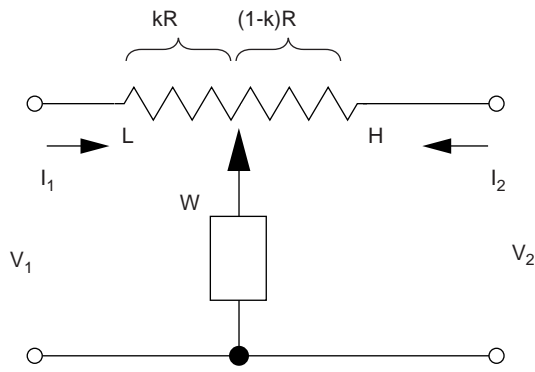

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2 = 0} \quad 0 \leq k \leq 1$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1 = 0} \quad R = R_{TOTAL}$$

FIGURE 4. TEE NETWORK PARAMETERS

The use of digitally-controlled potentiometers in programmable tee networks will be illustrated in several representative circuits including amplifiers, filters, and converters.

AMPLIFIERS: *Digitally Controlled Potentiometer Sets Cutoff Frequency*


FILTERS: *Programmable Tee Network Controls Sallen and Key Filter*  
*Programmable Tee Networks Control IGSF Filter*

CONVERTERS: *I to V Converter*

These basic analog circuits are used as universal building blocks in the design of analog systems and they also serve as models for more specialized analog functions. The following collection of independent articles and circuits are examples of using programmable tee networks in analog circuits. All of them have been breadboarded and tested.
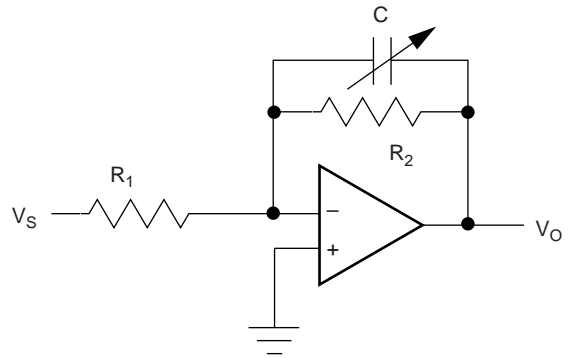
### Digitally Controlled Potentiometer Sets Cutoff Frequency

The traditional way of controlling the upper cutoff frequency in the basic inverting amplifier circuit of Figure 5 is to parallel  $R_2$  with a capacitor  $C$ . The cutoff frequency is controlled with the capacitor  $C$  and the magnitude of the circuit gain is independently established by  $R_2$  and  $R_1$  ( $=R_2/R_1$ ). If we need a variable cutoff frequency, we use a variable capacitor. This approach has two major problems: (1) the circuit does not lend itself to computer control and (2) availability of variable capacitors, especially in the nF region.



$$G_O = -\frac{R_2}{R_1}$$

$$f_c = \frac{1}{2\pi R_2 C}$$

FIGURE 5. TRADITIONAL INVERTING AMPLIFIER

The circuit in Figure 6 is an inverting amplifier that uses the digitally-controlled potentiometer and a fixed capacitor as an input 'tee' network. The magnitude of the gain for this inverting circuit is the same as the traditional circuit  $R_2/R_1$  but the cutoff frequency is established by  $R_1$ , capacitor  $C$ , and the location of the wiper along the resistor array of the potentiometer. Since the wiper of the digitally-controlled potentiometer is digitally or computer controlled, the upper cutoff frequency can then be programmed.

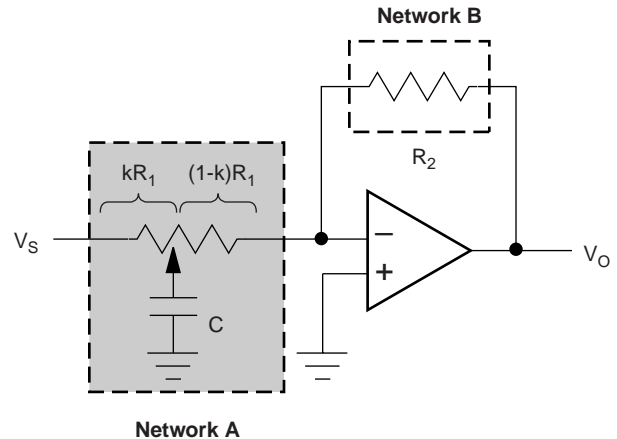


FIGURE 6. AMPLIFIER WITH INPUT TEE NETWORK

The circuit gain (as a function of frequency) can be determined using several analysis approaches. One approach is to use  $Y$  or admittance parameters. If network  $A$  and network  $B$  are treated as two-ports, the ratio of the short-circuit admittance coefficient  $Y_{21}$  for the input port to  $Y_{12}$  for the feedback port will produce the gain expression (Figure 6).

## Application Note 134

$$\frac{V_o}{V_s} = \frac{Y_{21A}}{Y_{12B}} = \frac{(R_2/R_1)(1/R_1 Ck(1-k))}{j\omega + (1/R_1 Ck(1-k))}$$

$$k \text{ is a number that varies from 0 to 1 and reflects the proportionate position of the wiper from one end (0) of the potentiometer to the other end (1).}$$

The circuit's gain expression is of the form

$$\frac{V_o}{V_s} = \frac{A_o \omega_c}{j\omega + \omega_c}$$

which is that of an amplifier or low pass filter with a gain  $G = -R_2/R_1$  and a cutoff frequency.

$$f_c = \frac{1}{2\pi R_1 Ck(1-k)}$$


As the wiper is programmed from one end of the potentiometer to the other,  $k$  varies from 0 to midscale (1/2) to 1, and the cutoff

frequency varies from infinite Hertz to a minimum frequency and back to infinite Hertz. The minimum frequency is:

$$f_c(\text{min}) = \frac{4}{(2\pi)R_1 C}$$

For the Intersil digitally-controlled potentiometer (XDCP),  $k$  will vary from 0 to 1 with a resolution determined by the number of taps or programmable wiper positions and  $R_1$  represents the  $R_{\text{TOTAL}}$  of the potentiometer. The number of taps varies from 32 to 256 and  $R_{\text{TOTAL}}$  varies from 1kΩ to 1MΩ depending on the particular potentiometer. A wiper or cutoff frequency setting can be stored in the XDCP's nonvolatile memory permitting the circuit's cutoff frequency to return to a predetermined value on power-up.

For the circuit values shown in Figure 7, the gain is -4.7 and the cutoff frequency varies from 6.4kHz to the frequency limited by the LT1007. The circuit uses Intersil's X9C103 which is a 10kΩ potentiometer with 100 taps and a three-wire interface. Other XDCPs are available with SPI and I<sup>2</sup>C interfaces. The circuit can be used in audio, control, and signal processing applications. (Published in EDN, June 10, 1999.)

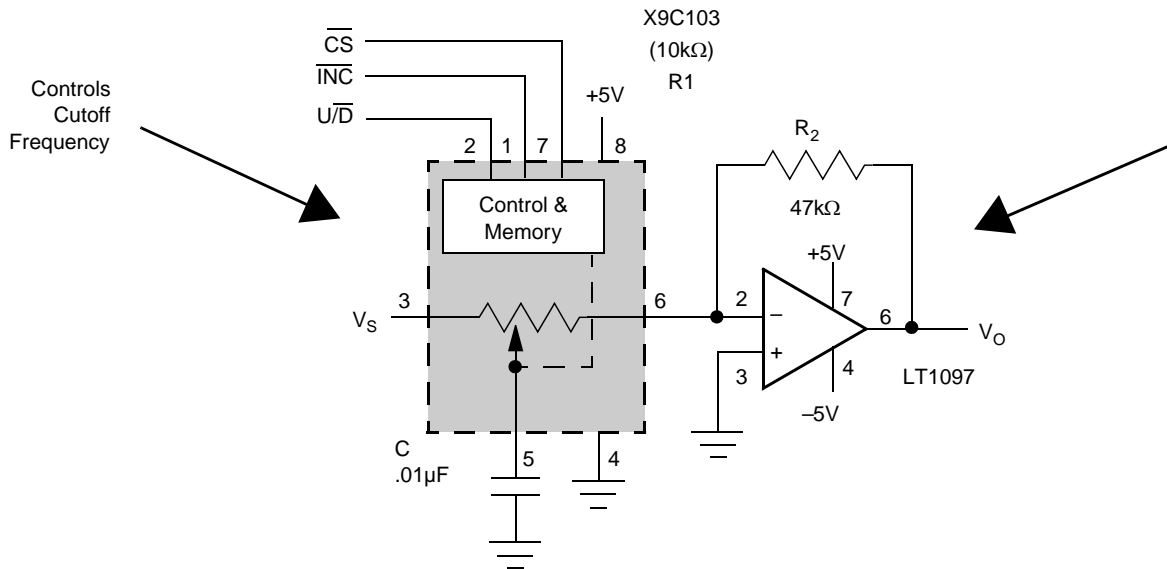

$$G = \frac{V_o}{V_s} = \frac{A_o \omega_c}{j\omega + \omega_c} = \frac{-(R_2/R_1)(1/R_1 Ck(1-k))}{j\omega + (1/R_1 Ck(1-k))}$$

$$A_o = -R_2/R_1 = -4.7$$

$$f_c = \frac{\omega_c}{2\pi} = \frac{1}{2\pi R_1 Ck(1-k)}$$

$$f_c(\text{min}) = \frac{4}{2\pi R_1 C} = 6.4 \text{ kHz}$$

**FIGURE 7. COMPUTER CONTROLLED AMPLIFIER**

## Programmable Tee Network Controls Sallen and Key Filter

The circuit in Figure 8 is a common way of implementing a second order, low pass filter. This Sallen and Key scheme provides a passband gain  $A_0$  of one and  $R_1$ ,  $R_2$ ,  $C_1$ , and  $C_2$  establish the characteristic frequency  $\omega_0$  and figure of merit  $Q$ . The circuit in Figure 9 replaces  $R_1$  and  $R_2$  with a digitally-controlled potentiometer and along with  $C_1$  is configured as a tee network. The location of the wiper changes the relative values of  $R_1$  and  $R_2$  and thus introduces another degree of freedom in the filter design. Since the wiper of the Intersil digitally-controlled potentiometer (XDCP) is computer controlled, this new degree of freedom  $k$  can be programmed.  $k$  is a number that varies from 0 to 1 and reflects the proportionate position of the wiper from one end (0) of the potentiometer to the other end (1). The resolution of  $k$  is determined by the number of taps or programmable wiper positions and  $R$  represents  $R_{TOTAL}$  or the end to end resistance of the potentiometer. The gain expression or transfer function for this circuit is:

$$\frac{V_o}{V_s} = \frac{1}{s^2 + s[1/k(1-k)RC_1] + 1/k(1-k)R^2C_1C_2}$$

$$\frac{V_o}{V_s} = \frac{A_0 \omega_0^2}{s^2 + s(\omega_0/Q) + \omega_0^2}$$

This is the classic expression for a second order low pass filter where

$A_0 = 1 =$  Pass Band Gain

$$\omega_0 = \sqrt{\frac{1}{k(1-k)R^2C_1C_2}},$$


and

$$Q = \sqrt{\frac{k(1-k)C_1}{C_2}}$$

The accuracy of filter parameters is dependent on the component sensitivities and the tolerance of the component values. Precise values of the parameters are difficult to achieve because precise values of capacitance are limited and expensive. This limitation of performance can be overcome using the programmable tee network. The characteristic frequency  $\omega_0$  or figure of merit  $Q$  can be precisely controlled depending on the critical need of the application.

For the values shown in Figure 9, the filter can be programmed for a theoretical maximally flat magnitude (MFM or Butterworth) response when  $k = 13/63$ . For this value of  $k$ ,  $Q = .704$  and  $f_0 = 6.85\text{kHz}$ . When the programmable tee network is at its limits ( $k = 0$  or  $k = 1$ ), the circuit reduces to a first order low pass filter whose cutoff frequency  $f_c = 1/2\pi RC_2$ . A second potentiometer can be used to control the noninverting, closed-loop gain of  $A_1$  and establish the passband gain  $A_0$  of the filter.

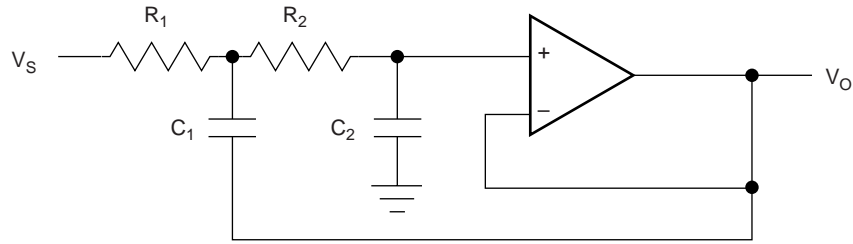
The electronic potentiometer adds variability to the filter circuit and its digital controls, though its computer-controlled serial bus, provide programmability. The X9418 has a 2-wire (I<sup>2</sup>C like) serial bus. An automated closed-loop calibration procedure to program the filter saves test time and provides enhanced performance and security. *(to be published in Electronics World [UK])*



$$T(s) = \frac{V_O}{V_S} = \frac{1}{R_1 R_2 C_1 C_2} \frac{1}{s^2 + \left( \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} + \frac{1}{R_1 C_1} \right) s + \frac{1}{R_1 R_2 C_1 C_2}}$$

$$= \frac{G_O \omega_0^2}{s^2 + (\omega_0/Q)s + \omega_0^2}$$

FIGURE 8. MODEL OF SALLEN AND KEY FILTER

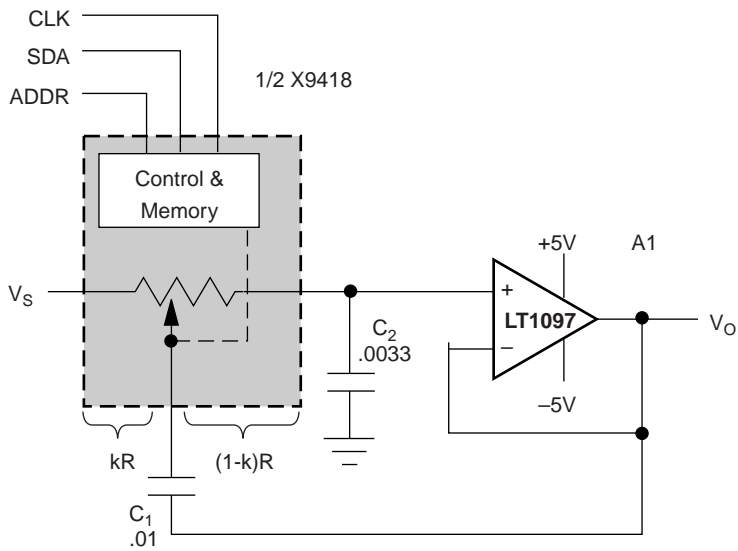

$$\frac{V_O}{V_S} = \frac{1}{k(1-k)R^2 C_1 C_2} \frac{1}{s^2 + s \left[ \frac{1}{k(1-k)RC_1} \right] + \frac{1}{k(1-k)R^2 C_1 C_2}}$$

$$A_O = G_O = -1$$

$$\omega_0 = \sqrt{\frac{1}{k(1-k)R^2 C_1 C_2}} \quad Q = \sqrt{\frac{k(1-k)C_1}{C_2}}$$

MFM (Marginally Flat Magnitude)

$$k = 13/63$$

$$Q = .704$$

$$f_0 = f_C = 6.85\text{kHz}$$

FIGURE 9. SALLEN AND KEY FILTER WITH THE TEE NETWORK

## Programmable Tee Networks Control IGSF Filter

The circuit in Figure 10 is a second order, low pass filter model that falls in the Infinite Gain, Single Feedback (IGSF) class. IGSF type filters are characterized by two-port input and feedback networks. Common two-ports used in filters are the tee network and its bridged tee and twin tee derivatives. If a digitally controlled potentiometer and a capacitor are used to implement the tee network, variability and programmability are added to the circuit.

The circuit in Figure 11 is basically an inverting amplifier where the input circuit A is a tee network and the feedback circuit B is a bridged tee network. The movement of the wiper of the potentiometer introduces a new degree of freedom  $k$  in the filter design where  $k$  is a number that varies from 0 to 1 and reflects the proportionate position of the wiper from one end of the pot (0) to the other end of the pot (1). The gain expression or transfer function of the filter is found by finding the ratio of the short-circuit admittance coefficients of the input and feedback networks. For this circuit,

$$\frac{V_o}{V_s} = -\frac{Y_{21A}}{Y_{12B}} = -\frac{1/kR(1-k)RC_1C_2}{s^2 + s[(1/k(1-k)RC_1] + 1/k(1-k)R^2C_1C_2}$$

This is the classic expression for a second order filter given by

$$\frac{V_o}{V_s} = \frac{A_o \omega_o^2}{s^2 + s(\omega_o/Q) + \omega_o^2}$$

where  $A_o$ ,  $\omega_o$ , and  $Q$  represent the passband gain, characteristic frequency, and figure of merit respectively.

From the gain expression,

$$A_o = 1,$$

$$\omega_o = \sqrt{\frac{1}{k(1-k)R^2C_1C_2}},$$

and

$$Q = \sqrt{\frac{k(1-k)C_1}{C_2}}$$

The movement of the wiper described by  $k(1-k)$  in the expressions for  $\omega_o$  and  $Q$  is parabolic. Depending on the application, the digitally controlled potentiometers can be programmed to optimize the characteristic frequency  $\omega_o$  or the quality factor  $Q$ . The accuracy of filter parameters is dependent on the component sensitivities and the tolerances of the component values. Precise values of the parameters are difficult to achieve because precise values of capacitance are limited and expensive. This limitation in performance can be overcome using the programmable tee network. The X9418 is dual potentiometer device with a 2-wire (I<sup>2</sup>C) interface and the ganging of the potentiometer wipers is done through the software.

For the circuit values shown in Figure 11, the filter can be programmed for a theoretical maximally flat magnitude (MFM or Butterworth) response when  $k=13/63$ . For this value of  $k$ ,  $Q=0.704$  and  $f_c = 6.85\text{kHz}$ . The measured response for this setting is shown in Figure 12. When the programmable tee network is at its limits ( $k=0$  or  $k=1$ ), the circuit reduces to a first order low pass RC filter whose cutoff frequency is determined by the  $10\text{k}\Omega$  resistance of the potentiometer and  $C_2$ .

The electronic potentiometer adds variability to the filter circuit and its digital controls, through its computer-controlled serial bus, provides programmability. An automated closed-loop calibration procedure to program or calibrate the filter saves test time and provides enhanced performance and security. (Published in *Electronic Design*, October 4, 1999.)


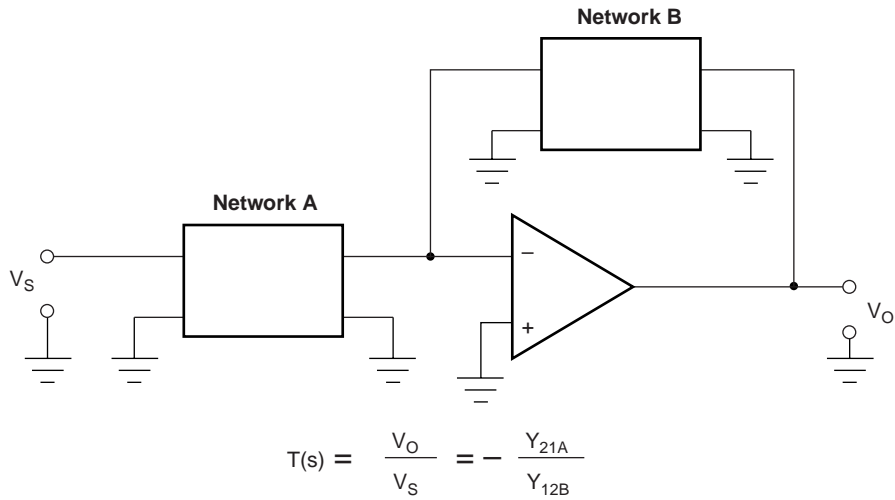


FIGURE 10. MODEL OF IGSF FILTER

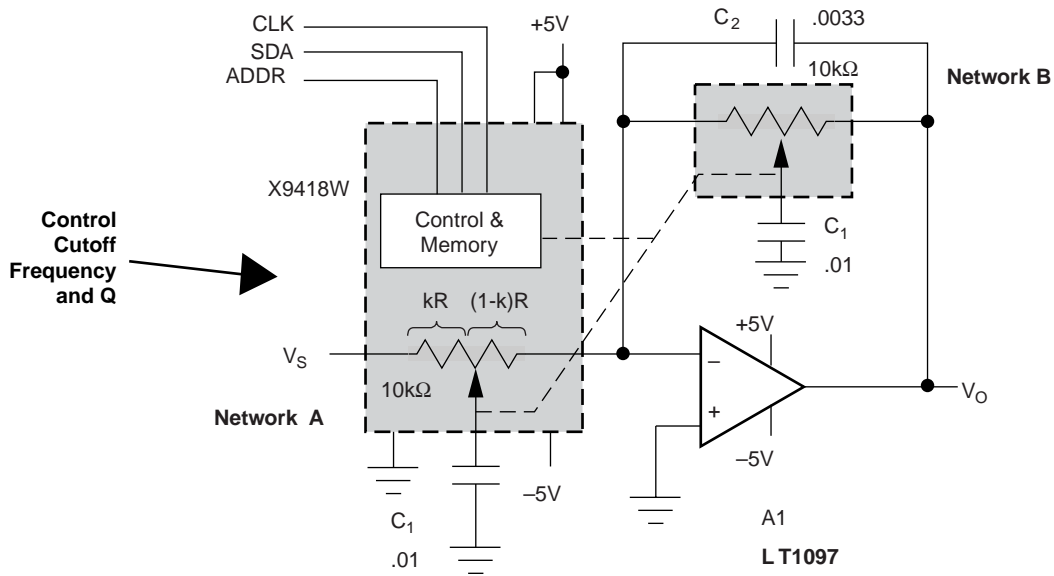

$$\frac{V_o}{V_s} = - \frac{Y_{21A}}{Y_{12B}} = \frac{-1/kR(1-k)RC_1C_2}{s^2 + s[1/k(1-k)RC_1] + 1/k(1-k)R^2 C_1C_2}$$

$$A_o = -1 \quad \omega_o = \sqrt{\frac{1}{k(1-k)R^2 C_1C_2}} \quad Q = \sqrt{\frac{k(1-k)C_1}{C_2}}$$

MFM RESPONSE:  $k = 13/63$ ,  $Q = .704$ ,  $f_c = 6.85\text{kHz}$

FIGURE 11. IGSF FILTER WITH TEE NETWORKS

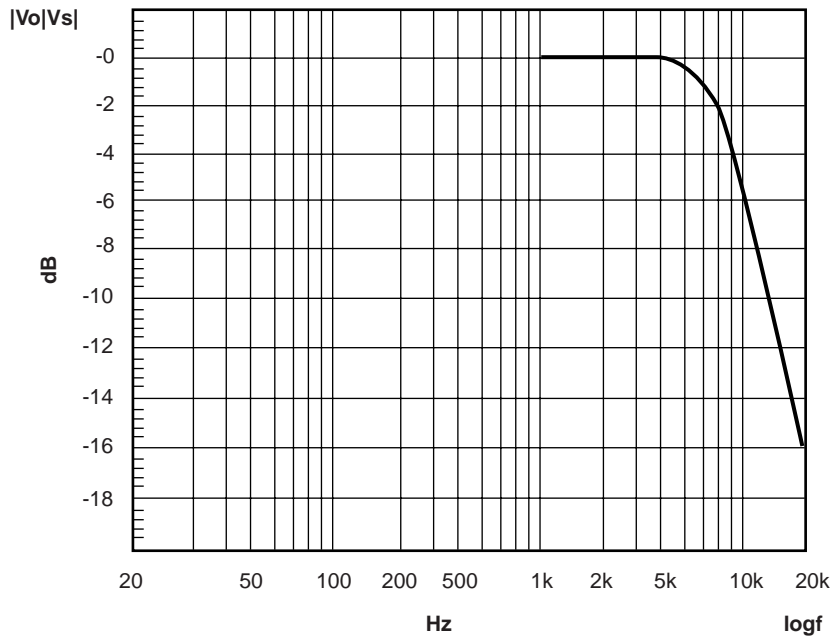


FIGURE 12. MFM RESPONSE OF IGSF FILTER

### I to V Convertor

The circuit in Figure 13 is an input current (I) to output voltage (V) convertor. The feedback portion of the circuit is a tee network of resistive elements consisting of a digitally controlled potentiometer and a fixed resistor  $R_1 (=R)$ . The input-output relationship for the I to V convertor is

$$\frac{V_0}{I_s} = -R \frac{(1+k-k^2)}{k}$$

where  $k$  is a number that varies from 0 to 1 and reflects the proportionate position of the wiper from one end (0) of the potentiometer to the other end (1). The programming of the location of the wiper changes the scale factor between the input current and output voltage without changing the values of any of the resistances and avoids the use of high value resistors in measuring low values of current. As  $k$  goes from 1 to 0, the scale factor goes from  $-R$  (1) to a theoretical  $-R(\infty)$ . The high impedance output of many transducers, like photodiodes and photovoltaic cells, is modeled as a current source.

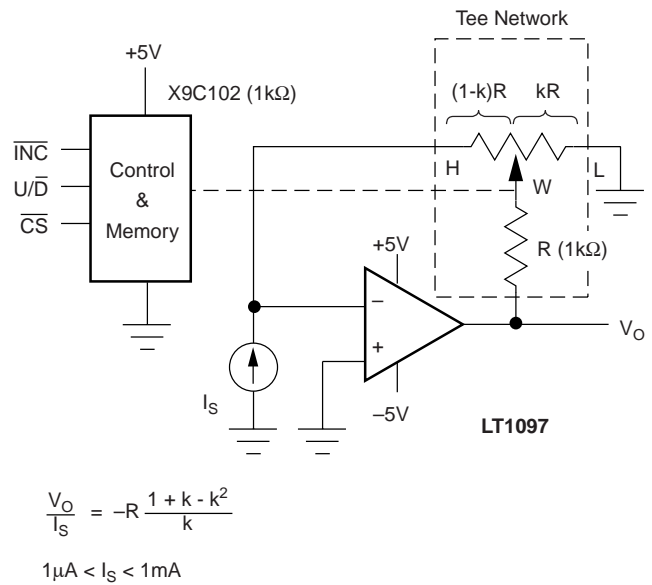


FIGURE 13. I TO V CONVERTOR




## Application Note 134

The programming of the 100 tap potentiometer provides for a two-decade change in effective resistance thus allowing the circuit to measure at least three decades of current. For the values shown, the circuit can measure current from 1μA to 1mA.

If we connect the tee network as shown in Figure 14, the expression for the scale factor changes to a parabolic-like expression given as  $-R(1+k-k^2)$ . This network can also be used in the traditional inverting amplifier circuit, Figure 15, to provide a variable gain described by


$$\frac{V_o}{V_s} = -\frac{R(1+k-k^2)}{R_1}$$

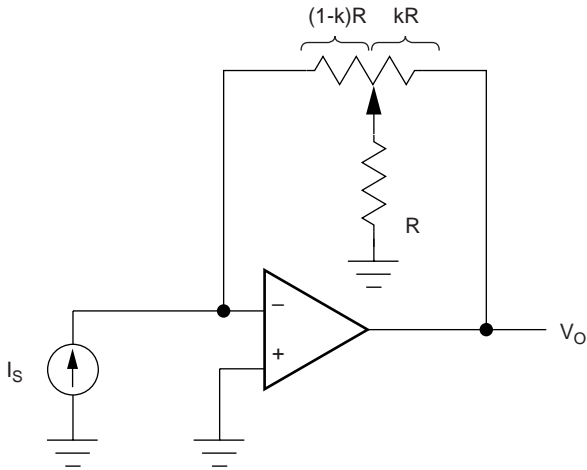As  $k$  goes from 1 to 0, the magnitude of the gain goes from  $R/R_1$  to 1.25 ( $R/R_1$ ) to  $R/R_1$  thus providing for a 25% variation in the circuit's voltage gain. Tee-like Network:



$$\frac{V_o}{I_s} = -R(1+k-k^2)$$

**FIGURE 14. I TO V CONVERTOR (VERSION 2)**

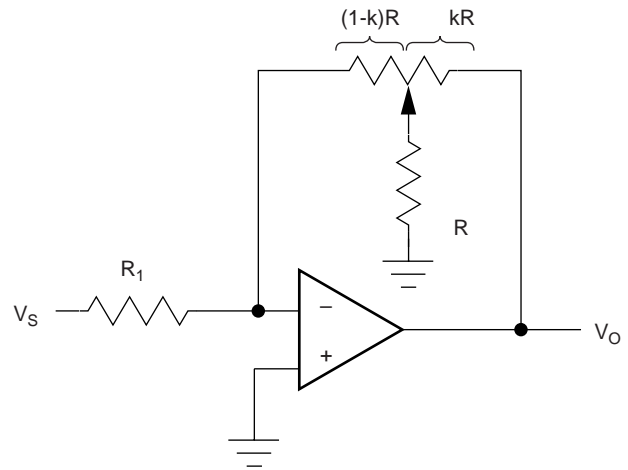

$$\frac{V_o}{V_s} = -\frac{R(1+k-k^2)}{R_1}$$

**FIGURE 15. AMPLIFIER WITH VARIABLE GAIN**

*Intersil Corporation reserves the right to make changes in circuit design, software and/or specifications at any time without notice. Accordingly, the reader is cautioned to verify that the Application Note or Technical Brief is current before proceeding.*

For information regarding Intersil Corporation and its products, see [www.intersil.com](http://www.intersil.com)