

Design Ideas for Intersil Digital Power Monitors

Abstract

The Intersil's Digital Power Monitor family is a highly versatile and flexible product. This Application Note will briefly describe the digital power monitor and present a variety of design ideas in which you can use a digital power monitor in assortment of different applications.

Table of Contents

Introduction	3
ISL28022 Key Features	3
ISL28023 Key Features	3
ISL28025 Key Features	3
Ideas Using ISL28022	4
Point of Load Power Monitor	4
Adjustable Point of Load Monitor	4
Power Monitor Boost Regulation	4
Floating Supply DPM (>60V or <0V Operation)	5
Force Voltage Measure Current and Voltage	5
A Lossless Current Sense Circuit	7
Improved Hall Effect Sensing	7
Combustible Gas Sensor Circuit	7
An Efficiency Measurement Using the DPM Broadcast Feature	8
Monitoring MultiCell Battery Levels Using the DPM Broadcast Command	9
Precision Current Sense	10
Ideas Using ISL28023	11
Generic Buck Regulator POL Circuit	11
Generic LDO Regulator POL Circuit	12
Generic Boost Regulator POL Circuit	13
High Side Voltage and Current Circuit	14
Using a Switch as a Sense Resistor	15
4 Gas Sensing Circuit	16
Ideas Using ISL28025	17
Generic Buck/Boost Regulator POL Circuit	17
Measure AC Currents	18
Sensor Monitor	18
Real Time Power Monitor System for Real Time Operating Systems, RTOS	19
DPM Used as a Control and Alert for a Multicell Balancing Circuit	22
PMBus Compatible Products Simplifies System Designs and Programming Them	23

List of Figures

FIGURE 1. Point of Load Monitoring Design Idea	4
FIGURE 2. Adjustable Point of Load Monitoring Design Idea	4
FIGURE 3. Power Monitor Boost Regulator Design Idea	5
FIGURE 4. Floating Supply Design Idea	5
FIGURE 5. A Simplified Schematic of a Force Voltage Measure Voltage and Current Circuit with Low Current Drive Capability	5
FIGURE 6. A Simplified Schematic of a Force Voltage Measure Voltage and Current Circuit with a Push-pull Output Stage	6
FIGURE 7. A Simplified Circuit Diagram of Remotely Measuring Current Through a Trace	7
FIGURE 8. An Illustration of Current Flow with Respect to the Magnetic Field Direction	7
FIGURE 9. A Simplified Circuit Diagram of a Hall Effect Sensor that Integrates the Current Conduction Path	7
FIGURE 10. A Simplified Diagram of a Combustible Gas Sensor Circuit Using the ISL28022	8
FIGURE 11. A Simplified Circuit that Uses Two ISL28022 to Measure a System Efficiency	9
FIGURE 12. A Simplified Multicell Monitoring Circuit	10
FIGURE 13. A Simplified Circuit Diagram that Measures Current and Temperature	11
FIGURE 14. Generic POL Circuit Using a Buck Converter and the ISL28023	11
FIGURE 15. Generic POL Circuit Using a LDO Converter and the ISL28023	12

Application Note 1955

FIGURE 16.	Generic POL Circuit Using a Boost Converter and the ISL28023	13
FIGURE 17.	A Simplified Circuit Illustration Showing Multiple ISL28023s Connected to One Smbus and One SMBALERT1 Line	14
FIGURE 18.	Generic POL Circuit Using an LDO Converter and the ISL28023	15
FIGURE 19.	Low Side Voltage and Current Monitoring Circuit that Uses SMBALERT1 as a Control	15
FIGURE 20.	A Simplified Schematic of a Switch Used as a Sense Resistor	15
FIGURE 21.	CMRR vs Frequency	16
FIGURE 22.	A Simplified Schematic for Gas Sensing	16
FIGURE 23.	Generic POL Circuit Using a Buck/Boost Converter and the ISL28025	17
FIGURE 24.	VSHUNT Bandwidth vs ADC Timing	18
FIGURE 25.	Simplified Circuit Using the ISL28025 to Measure AC Currents	18
FIGURE 26.	Primary VSHUNT AC Common Mode Voltage Range	18
FIGURE 27.	Simplified Schematic of a Pressure Monitor with a Safety Feature	19
FIGURE 28.	Simplified Example of Two ISL28025 Configured to Measure Real Time to a RTO System	20
FIGURE 29.	Group Command (A) without PEC (B) with PEC	20
FIGURE 30.	Measurement Bandwidth vs External CLK Frequency	21
FIGURE 31.	Simplified Circuit that Measures Power Delivered to the RTO System at a Slower Rate	21
FIGURE 32.	Simplified Circuit for Multicell Balancing	22
FIGURE 33.	An Example of a Power Distribution System Using the ISL28025 and Intersil ZLXXX Series	23

Introduction

The digital power monitor (DPM) is a digital current, voltage and power monitoring device for high and low-side power monitoring in positive and negative voltage applications. DPMs require an external shunt resistor to enable current measurements and translate the bus current to a voltage. The DPM measures the voltage across the shunt resistors and reports the measured value out digitally via an I²C interface. A register within the DPM is reserved to store the value of the shunt resistor, which allows the DPM to output a current value to an external digital device.

The DPM measures bus voltage and current sequentially. It has a power measurement functionality that multiplies the measured current and voltage values which is then stored in a unique register. This measurement allows the user to monitor power to or from the load in addition to current and voltage. The DPM can monitor supplies from 0V to 60V while operating on a chip supply ranging from 3V to 5.5V. The internal ADC sample rate can be configured to an internal oscillator (500kHz) or a user can provide a synchronized clock.

The ISL28022 is a basic digital power monitor with a single/primary channel that can measure voltage from 0V to 60V.

The ISL28023 has two channels which allow the user to monitor the voltage, current and power on two power supply rails. The two channels for the DPM consist of a primary channel and an auxiliary channel. The primary channel will allow and measure voltages from 0V to 60V or from 0V to 16.384V, depending on the option of the ISL28023. The auxiliary channel can tolerate and measure voltage from 0V to V_{CC}.

The ISL28025 has an additional low voltage read to measure a voltage after the rail has been regulated. The primary channel will allow and measure voltages from 0V to 60V or from 0V to 16.384V, depending on the option of the ISL28025. The auxiliary channel can tolerate and measure voltage from 0V to V_{CC}.

The ISL28023/5 have continuous fault detection for the primary channel only. It can be configured to set an alert for an overvoltage, undervoltage and/or overcurrent event with a response time of 500ns from the event. The ISL28023/5 have a temperature sensor with fault detection. An 8-bit margin DAC, controllable through I²C communication, is incorporated into the DPM. A voltage margining feature allows for the adjustment of the regulated voltage to the load. The margin DAC can help in proving the load robustness versus the applied supply voltage. The ISL28023/5 offer a 3.3V voltage regulator that can be used to power the chip in addition to low power peripheral circuitry. The DPM has an I²C power pin that allows the I²C master to set the digital communication supply voltage to the chip, an operating supply voltage range of 3V to 5.5V, and can accept I²C supply voltages between 1.2V and 5.5V. The DPM accepts SMBus protocols up to 3.4MHz. The ISL28023/5 is PMBus compliant up to 400MHz. The device has packet error code (PEC) functionality which uses an 8-bit cyclic redundancy check (CRC-8) represented by the polynomial x^8+x^2+x+1 . The ISL28023/5 can be configured for up to 55 unique slave addresses using 3 address select bits allowing 55 parts to communicate on a single I²C bus. This gives the designer the flexibility to select a unique address when another slave address conflicts with the DPM on the same I²C bus.

ISL28022 Key Features

- Integrated analog front end with digital output
 - Analog switch/MUX, ADC, voltage reference
 - Digital processing/serial communication circuitry (I²C/SMBus)
- Voltage, current, power monitoring and current direction
 - Current Sense: high-side, low-side, bidirectional
 - Wide common-mode input voltage range: 0V to 60V
 - Digital output
- Precision/accuracy
 - 16-bit $\Sigma\Delta$ ADC
 - Voltage/current measurement error: <0.3%

ISL28023 Key Features

- Integrated analog front end with digital output
 - Analog switch/MUX, ADC, voltage reference
 - Digital processing/serial communication circuitry (I²C/SMBus/PMBus)
- Voltage, current, power monitoring and current direction
 - Current sense: high-side, low-side, bidirectional
 - Wide common-mode input voltage range: 0V to 60V
 - Digital output
 - Internal 3.3V regulator
 - Internal temperature sense
 - 8-bit voltage output DAC
 - Auxiliary channel available
- Precision/accuracy
 - 16-bit $\Sigma\Delta$ ADC
 - Voltage/Current Measurement Error: <0.05%

ISL28025 Key Features

- Integrated analog front end with digital output
 - Analog switch/MUX, ADC, voltage reference
 - Digital processing/serial communication circuitry (I²C/SMBus/PMBus)
- Voltage, current, power monitoring and current direction
 - Current sense: high-side, low-side, bidirectional
 - Wide common-mode input voltage range: 0V to 60V
 - Digital output
 - Internal 3.3V regulator
 - Internal temperature sense
 - Auxiliary low voltage input channel
- Precision/accuracy
 - 16-bit $\Sigma\Delta$ ADC
 - Voltage/current measurement error: <0.05%

Ideas Using ISL28022

Point of Load Power Monitor

The circuit illustrated in [Figure 1](#) is a solution that can be used to monitor a load's performance. The voltage regulator regulates to a Point Of Load (POL) voltage. 5V, 3.3V, 2.5V and 1.8V are examples of POL voltages.

The main bus voltage applied to the voltage regulator regulates the voltage to the load at the VINM, VBUS and Sense node for the configuration shown in [Figure 1](#). The shunt resistor in the circuit allows the current to be monitored while regulating the voltage to the load. For example, the maximum shunt voltage the ISL28022 is able to measure is $\pm 320\text{mV}$. The shunt resistor value is determined by [Equation 1](#):

$$R_{\text{shunt}} = R_{\text{SH}} = \frac{0.32}{\text{Current}_{\text{FS}}} \quad (\text{EQ. 1})$$

Current_{FS} is the maximum current to be measured through the load. This is chosen by the user.

The DPM has over/undervoltage (OV/UV) sensing circuitry for the Bus and Shunt inputs. The levels of the error detection circuitry are controlled digitally via an I²C/SMBus interface. The status of each inputs' error detection can be read digitally via a register. The DPM allows for the summation of error detection bits to be routed to an interrupt pin. For the Point of Load Monitoring circuit shown in [Figure 1](#), the interrupt pin is connected to the enable pin of the regulator. In a fault condition, the DPM will trigger an interrupt causing the voltage regulator to shut down. When a fault exists, the DPM interrupt pin output state can be digitally programmed.

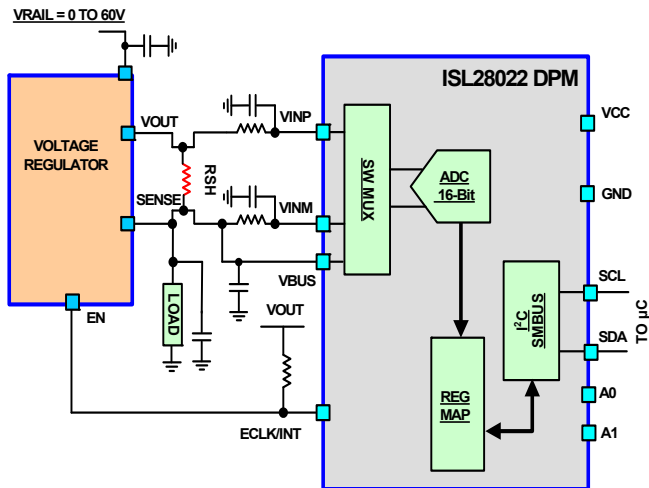


FIGURE 1. POINT OF LOAD MONITORING DESIGN IDEA

The DPM calculates the power and current internally and stores the results in an internal register. The V_{BUS} connected directly to the load, enables a measurement system that monitors power to the load.

Adjustable Point of Load Monitor

Many applications require unique voltages to optimize a circuit's potential. [Figure 2](#) is a microcontroller selectable point of load (POL) circuit. The circuit is very similar to the POL monitor discussed previously. The general purpose input output bits (GPIO) of the

microcontroller controls a multiplexer which connects a gain setting resistor to the adjust (ADJ) pin of the regulator. The feedback resistance (R_F), the multiplexer switch resistance and the value of the gain setting resistor (R₁ to R₈) determine the regulated output voltage (POL_V) to the load. [Equation 2](#) is a generic formula to determine the regulated POL_V.

$$\text{POL_V} = \alpha \cdot \left(\frac{R_F}{R_x + R_{\text{mux}}} + 1 \right) \quad (\text{EQ. 2})$$

The coefficient alpha, α , is dependent on the designed in regulator. For the ISL80101-ADJ, α equals 0.5. R_x is the value of the gain resistor (R₁ to R₈) selected by the microcontroller. R_{mux} is the multiplexer switch resistor value. The multiplexer switch resistance is a function of the current flowing through the switch. A general practice is to choose resistor values such that current flowing through the multiplexer is small. The ISL84781 has an On-resistance of 0.4 Ω .

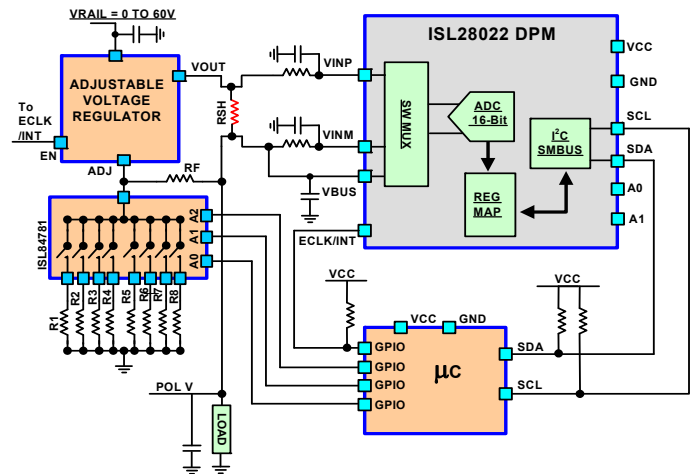


FIGURE 2. ADJUSTABLE POINT OF LOAD MONITORING DESIGN IDEA

Power Monitor Boost Regulation

The Power Monitor Boost Regulator application is an example of the DPM used as a digital helper ([Figure 3](#)). With minimal circuitry, the DPM enables smart designs that digitally monitor the electrical parameters to a load. Alternative designs require a current amplifier paired with an ADC. The ADC chosen is often not compliant to common communication standards, such as I²C. The DPM solves this problem and allows for 16 devices on a single I²C bus.

The ISL97516 chip is a high efficiency step-up voltage regulator. The maximum peak inductor current the regulator can deliver is 2.0A. If more output current is needed, the ISL97656 is rated for 4.0A maximum peak inductor current. For this particular application, the ISL97516 is configured to step up the voltage at the VDD pin to 12V. The voltage at VDD can range from 2.3V to 5.5V for normal 12V regulated operation. A USB power pin could be used to drive the ISL97516.

The regulation node of the circuit, shown in [Figure 3](#) is at V_{OUT}. The ISL97516 has feedback circuitry that removes the current sense resistor, R_{SH}, from impacting the regulation voltage. The current sense resistor is calculated using [Equation 1](#). [Equation 1](#) on [page 4](#) shows the formula used to calculate R_{shunt}.

Application Note 1955

The DPM interrupt pin is connected to the Enable pin of the regulator. The DPM has OV/UV alerts for both the Bus and Shunt channels. A fault condition from either channel powers down the voltage regulator.

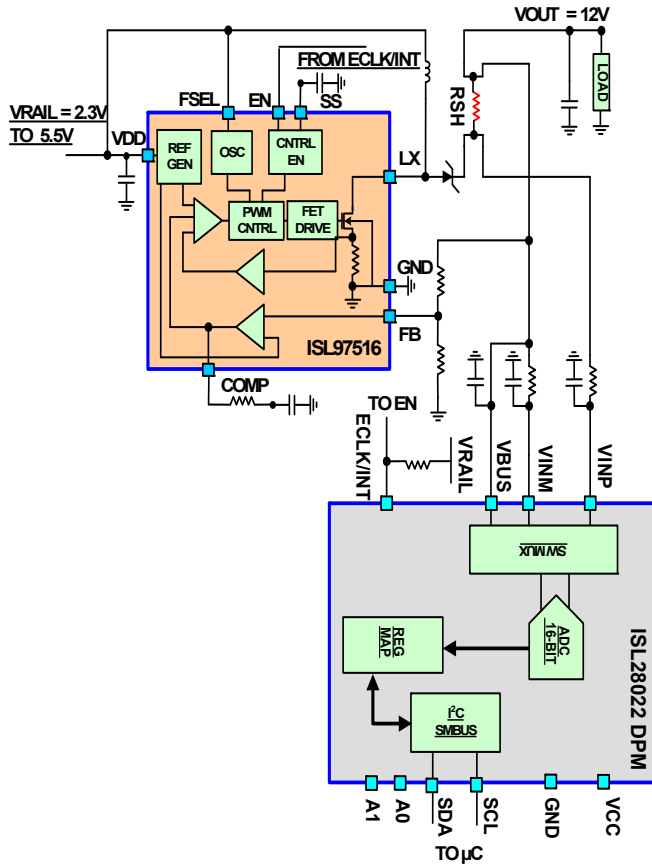


FIGURE 3. POWER MONITOR BOOST REGULATOR DESIGN IDEA

Floating Supply DPM (>60V or <0V Operation)

The DPM is operational when the potential of the measured circuitry is greater than the potential at the ground pin. In most applications the ground pin potential equals 0V. A zero potential ground reference limits the operating range of the DPM to 0V to 60V. This application illustrates the connectivity of the DPM to measure and operate at potentials greater than 60V or less than 0V.

Assume the application measures a -48V supply. The ground reference voltage of the system, V_{low} , equals -48V. V_{high} equals 0V for the example. The power supply voltage to the system is -48V. The load supply voltage is set by the voltage regulator, $V_{LOAD Reg}$. The regulator can be either a shunt or a linear regulator.

The voltage levels for I²C communication lines are determined by V_{low} and the DPM shunt regulator. A low voltage equals the V_{low} potential. A high level equals the summation of V_{low} and the Shunt Regulator voltage. For a -48V system with a 3.3V shunt regulator, a low voltage equals -48V and a high voltage level equals -44.7V. The voltage from the I²C communication pins can not be directly connected to a ground referenced microcontroller. The optocouplers are used to translate the voltage level from the -48V referenced system to the ground referenced microcontroller system.

The DPM measures voltage between two nodes. For the shunt input, the DPM measures the voltage between VINP and VINM nodes. For the Bus input, the DPM measures the difference between V_{BUS} and GND nodes. The V_{BUS} voltage for a floating system is calculated using Equation 3:

$$V_{bus} = V_{low} + (V_{bus_LSB} \cdot V_{bus_Reg}) \quad (EQ. 3)$$

V_{LOW} is the ground reference voltage of the system. In this instance, the value is -48V. V_{BUS_LSB} is the step size of the V_{BUS} measurement, which equals 4mV. V_{BUS_REG} is the integer value of the V_{BUS} measurement reported by the DPM.

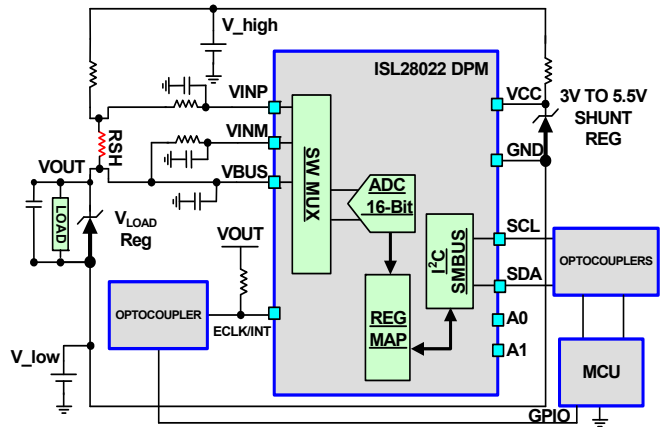


FIGURE 4. FLOATING SUPPLY DESIGN IDEA

Force Voltage Measure Current and Voltage

Many applications require testing of components or validating a system's performance by utilizing circuits that force voltage and measure current and voltage to a specific connection point. The circuit in Figure 5 is a force voltage measure current and voltage circuit.

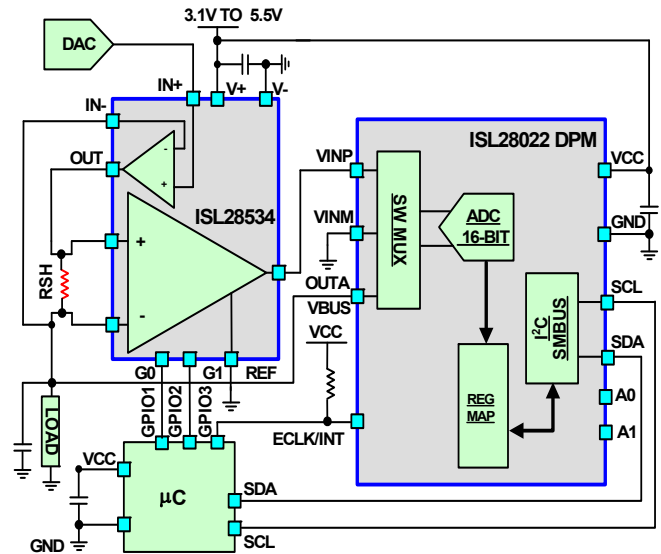


FIGURE 5. A SIMPLIFIED SCHEMATIC OF A FORCE VOLTAGE MEASURE VOLTAGE AND CURRENT CIRCUIT WITH LOW CURRENT DRIVE CAPABILITY

Application Note 1955

The digital-to-analog converter, DAC, is configured by the microcontroller. The DAC is either integrated into the microcontroller or a standalone discrete device depending on the level of precision needed. The output of the DAC is fed into the noninverting input of the ISL28534. The ISL28534 is a chopper-stabilized single output instrumentation amplifier with an additional operational amplifier (op amp) integrated into the die. The allowable voltages that can be fed to the op amp are 0.1V to V+ - 0.1V. The allowable supply voltages to the circuit ranges from 3.1V to 5.5V. The integrated op amp regulates the voltage to the load while delivering current. The op amp can successfully regulate the programmed voltage up to 1mA. For greater than 1mA drive currents, an external operational amplifier with higher current may be needed. Another approach is to add a push-pull output stage between the output of the integrated op amp and the sense resistor. The push-pull output stage that enables higher drive capability for the circuit is shown in [Figure 6](#).

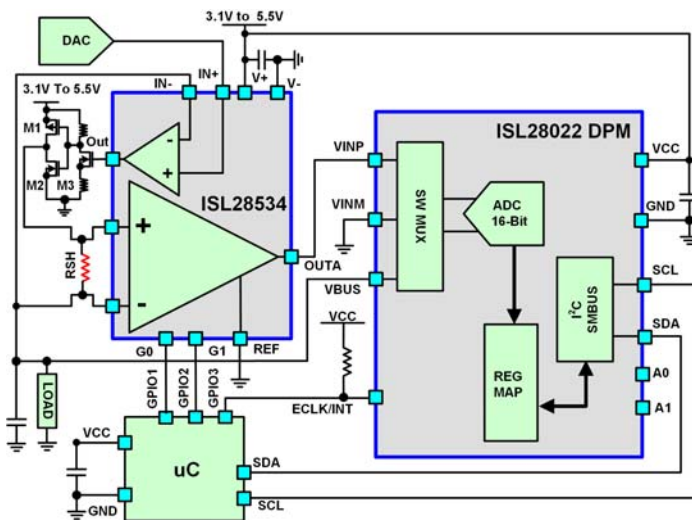


FIGURE 6. A SIMPLIFIED SCHEMATIC OF A FORCE VOLTAGE MEASURE VOLTAGE AND CURRENT CIRCUIT WITH A PUSH-PULL OUTPUT STAGE

The addition of the power MOSFETs between the shunt resistor, RSH, and the load increases the drive current to the load. The MOSFETs are labeled M1 and M2 in [Figure 6](#).

The feedback loop of the shunt resistor, RSH, and the power MOSFETs, M1 and M2, between the IN- terminal and Out terminal of the op amp, enhances the drive capability to the load. The IN-terminal regulates the voltage to the load, while the current is steered from 3.1V to 5V supply through the MOSFET, M1, to the load. The additional power stage limits the voltage delivered to the load.

Integrated into the ISL28534 is an instrumentation amplifier, IA, that can be configured to 1 of 9 gain ranges. The ISL28534 is one product of a family of six products. The products are differentiated by gain values and the number of outputs. The purpose of the instrumentation amplifier, IA, is to extend the measurable current range by using one sense resistor.

The ISL28534 gain selection spans from 1 to 1000. The voltage noise floor of the IA is 0.5µV at a high gain. The lowest voltage the IA can resolve is 1µV as a conservative value. The ISL28534 has an input offset current of 300pA at room temperature. The lowest current that can be measured is 500pA. The current value is dependent on the operational temperature range of the circuit.

The output of the IA connects to the shunt input (VINP, VINM) of the DPM. The full scale measurable range of the shunt input is ±320mV. Voltage readings that exceed 320mV in magnitude, require a reduction of gain in the IA setting. The DPM digital comparators can be set to fire an interrupt for readings above 320mV. The interrupt can be routed to either the interrupt or a GPIO pin of the microcontroller. The connection allows the DPM to notify the microcontroller to decrement the gain of the IA when the output reading of the IA exceeds 320mV.

If the minimum current to be measured is 500pA, what is the shunt resistor value, RSH, and the full scale current that the circuit can measure? The lowest measured current reading should occur at the IA's highest gain while the voltage drop across the shunt resistor equals the IA resolution voltage. The bounded criterion discussed determines the shunt resistor value. The shunt resistor value can be calculated using [Equation 4](#):

$$R_{\text{sense}} = R_{\text{SH}} = \frac{V_{\text{IA_Res}}}{I_{\text{min}}} \quad (\text{EQ. 4})$$

$V_{\text{IA_Res}}$ is the resolution value of the IA, which equals 1µV for the application. I_{min} is the minimum current to be measured. The example shows I_{min} equals 500pA. The shunt resistor is calculated to be 2kΩ.

The full scale current of any IA gain setting can be calculated using [Equation 5](#):

$$\text{Current}_{\text{FS}} = \frac{V_{\text{shunt_range}}}{G_{\text{IA}} \cdot R_{\text{sense}}} \quad (\text{EQ. 5})$$

G_{IA} is the IA gain setting. R_{sense} is the shunt resistor value, which equals 2kΩ for the giving example. $V_{\text{shunt_range}}$ is the PGA range setting for the DPM. For example, the shunt range setting value is 320mV. The full scale current range for the circuit occurs at an IA gain setting of 1. Using [Equation 5](#), the measurable full scale current equals 150µA.

The least significant bit, LSB, for the shunt input equals 10µV for the DPM. The current_{LSB} can be calculated using [Equation 6](#):

$$\text{Current}_{\text{LSB}} = \frac{\text{Current}_{\text{FS}}}{G_{\text{IA}} \cdot \text{ADC}_{\text{res}}} \quad (\text{EQ. 6})$$

The ADC_{res} equals 2^{15} or 32768 for the example. The $\text{Current}_{\text{FS}}$ is calculated using [Equation 5](#). The G_{IA} is the gain of the IA. The V_{BUS} input of the DPM is connected to the load allowing for power measurements. The V_{BUS} can also be connected as an independent node. The power measurement value returned from the DPM would be meaningless.

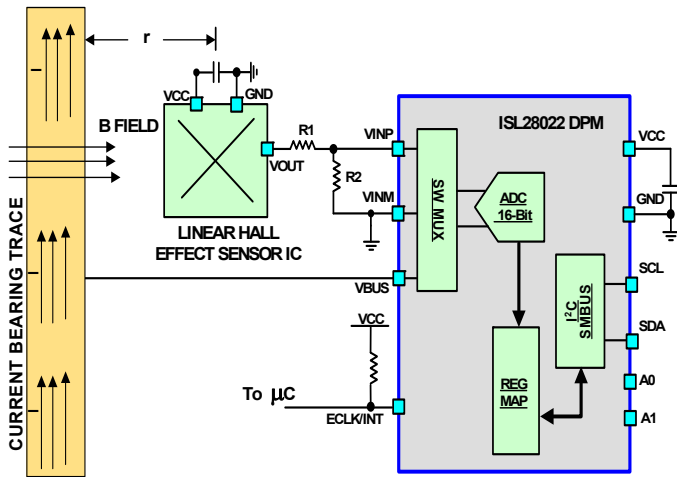


FIGURE 7. A SIMPLIFIED CIRCUIT DIAGRAM OF REMOTELY MEASURING CURRENT THROUGH A TRACE

A Lossless Current Sense Circuit

In measuring power to and from a system or load, the minimum voltage loss due to a sensing element and trace resistance is desired. The low voltage loss improves the efficiency of a system. The circuit in [Figure 7](#) measures current through a trace by measuring the magnetic field, B, emitted from the current flowing through the trace. The B field is directly proportional to the magnitude and direction of the current flowing through the trace. The B field is perpendicular to the current flow. The direction of the B field with respect to current flow is illustrated in [Figure 8](#).

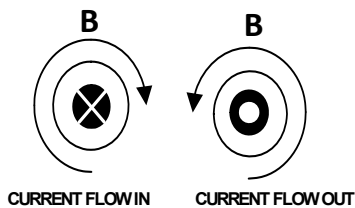


FIGURE 8. AN ILLUSTRATION OF CURRENT FLOW WITH RESPECT TO THE MAGNETIC FIELD DIRECTION

The mathematical relation between the magnitude of the current and the magnetic field is represented in [Equation 7](#):

$$B = \frac{\mu_0 \cdot I}{2 \cdot \pi \cdot r} \quad I = \frac{2 \cdot \pi \cdot r \cdot B}{\mu_0} \quad (\text{EQ. 7})$$

μ_0 is the permeability of the magnetic field flow. The permeability value, μ_0 , of free space equals $4\pi \cdot 10^{-7}$ H/m. The value r is the distance in meters between the conductor and the linear hall effect sensor. The I is the current flowing in amps through the conductor. B is the magnetic field in Gauss.

CAUTION:

Every technology has drawbacks. The lossless current sense is no exception. Hall effect sensors measure the total available magnetic field at the set location. Current bearing traces routed near the sensor will change the magnetic field at the sensor and

ultimately change the accuracy of the measurement. The sensor will also measure changes in the environmental magnetic field. This could be due to a switching motor or any device that radiates energy. A magnetic shield can encapsulate the current bearing trace of interest and the hall effect sensor to reduce the environmental interference the sensor is subjected to. The magnetic shield will change the gain between the current flowing in the trace and the output voltage of the sensor.

The resistor divider, R_1 and R_2 , in [Figure 7](#) attenuates the voltage from the linear hall effect sensor to the maximum voltage range, 320mV, of the ISL28022 V_{SHUNT} input (VINP, VINM). The V_{BUS} input of the ISL28022 is connected to the current bearing trace allowing the ISL28022 to calculate power to the load.

Improved Hall Effect Sensing

Recently, linear hall effect sensors that integrate the current conduction path, and provide environmental shielding and temperature compensation circuitry in a single package, have improved the drawbacks associated with the linear hall effect sensor. The integrated solution simplifies the gain calculation between the current flowing through the conductor and the output voltage. The single chip solution also simplifies the layout because the current bearing wire is a set distance from the hall effect sensor.

The integrated conduction path (IP+, IP-) has resistance ranging from 0.1m Ω to 2m Ω . The current sense in [Figure 9](#) is not a lossless system.

The resistor divider, R_1 and R_2 , in [Figure 9](#) attenuates the voltage from the linear hall effect sensor to the maximum voltage range, 320mV for example, of the ISL28022 V_{SHUNT} input (VINP, VINM). The V_{BUS} input of the ISL28022 is connected to the current bearing trace allowing the ISL28022 to calculate power to the load.

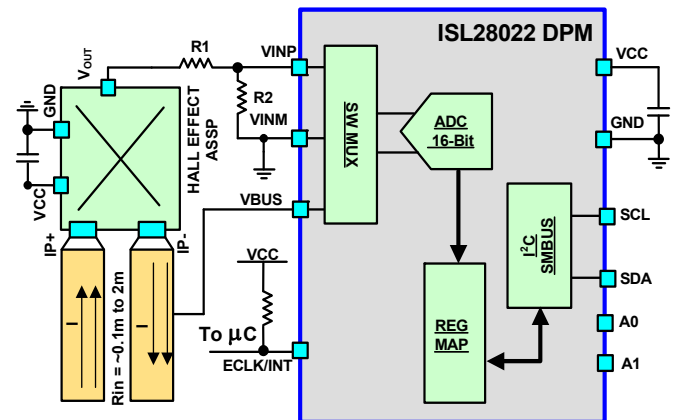


FIGURE 9. A SIMPLIFIED CIRCUIT DIAGRAM OF A HALL EFFECT SENSOR THAT INTEGRATES THE CURRENT CONDUCTION PATH

Combustible Gas Sensor Circuit

The DPM measures current by measuring a voltage across the shunt inputs (VINM, VINP). A 15-bit digital number representing the sense resistor value is stored in the calibration register. The DPM divides the voltage measured across the shunt inputs by the calibration register value and stores the results in the current register.

Application Note 1955

In the combustible gas sensor application ([Figure 10](#)), the current measurement reading from the DPM is not used. The voltage reading across the Wheatstone bridge determines the concentration of gas in the environment. The resistive network on the left leg of the Wheatstone bridge is a coarse null to the combustible gas sensor. The ISL95810 is a digitally controlled potentiometer (DCP). The DCP is used to fine tune the null potential to 0V across the shunt inputs for a known concentration of gas. In the event of a power interruption to the circuit, the ISL95810 has nonvolatile memory integrated with the DCP. The DCP will default to the save memory position once power is resumed to the circuit.

The gain between the change in concentration and the change in volts varies between sensors and sensing gas. The DPM has a digital comparator that can trigger an interrupt line when a voltage exceeds a set level. A set voltage threshold for the shunt input corresponds to a set gas level. When the concentration of gas exceeds a set level, the DPM triggers an alarm causing the ECLK/INT pin to transition from V_{CC} voltage level to ground. The ground potential activates the relay and disable power to the sensor circuit. See also [See “4 Gas Sensing Circuit” on page 16](#).

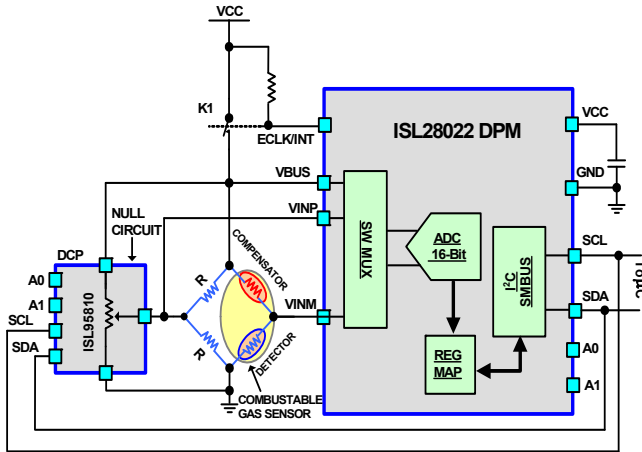


FIGURE 10. A SIMPLIFIED DIAGRAM OF A COMBUSTIBLE GAS SENSOR CIRCUIT USING THE ISL28022

An Efficiency Measurement Using the DPM Broadcast Feature

As energy costs rise and the world focuses on clean energy, there is a need for electronics to efficiently convert power delivered to a circuit into work performed. Power efficiency, η , is an electronic

parameter used to quantify the efficiency of a system. [Equation 8](#) defines the formula for power efficiency.

$$\eta = \left(\frac{P_{\text{load}}}{P_{\text{total}}} \right) \cdot 100 \quad (\text{EQ. 8})$$

P_{total} is the power delivered to current leg prior to being converted.

In the electronics field, efficiency ratings are mostly associated with converting power from one form to another. Examples of power conversion circuitry are DC/DC converters, AC/DC converters, buck/boost regulators and digital regulators. P_{load} is the power delivered to the load.

The simplified circuit in [Figure 11](#) is an example of using two ISL28022s to measure the efficiency of a DC/DC converter (ISL95870). The first ISL28022, DPM1, measures the total power, P_{total} , for the circuit. DPM2 measures power to the load, P_{load} . DPM1 and DPM2 are connected to the same I²C bus. The two ISL28022s can synchronously measure their respective signals by sending a broadcast trigger command sent to each device. A broadcast trigger command that instructs each ISL28022 device to measure both current and voltage is achieved by writing to the command register, register 0, using the slave address of 0x7F. The slave address 0x7F will write to all ISL28022s independent of address setting.

The command register, register 0, configures the range setting for both bus (BRNG) and shunt (PG) inputs and the sampling mode for the chip. The command register also configures the ADC sampling rate for both channels of the ISL28022. To successfully synchronize the ISL28022s to sample simultaneously, each ISL28022 has to have the same bus and shunt range and ADC acquisition settings.

Assume a bus range of 16V, a shunt range of 40mV and an ADC acquisition rate of 508 μ s for both channels. A single power acquisition will be made and the chip will sit idle. The command that is sent simultaneously to both chips is 0x7F, 0x00, 0x019B. The ranges for each input are for the lowest settings. PGA = BRNG = 0. The ADC acquisition rate is the same for both channels. SADC = BADC = 3 or 508 μ s. The setting for the mode bits is 3. Once the write command has been received and executed by the ISL28022, the ADC will begin converting the signal. The two ISL28022s should be synchronized as long the distance between master (microcontroller) and ISL28022 are roughly the same between the two ISL28022s.

Once the ADC has completed the conversion for both bus and shunt channels, the master should read register 3 of each ISL28022 serially.

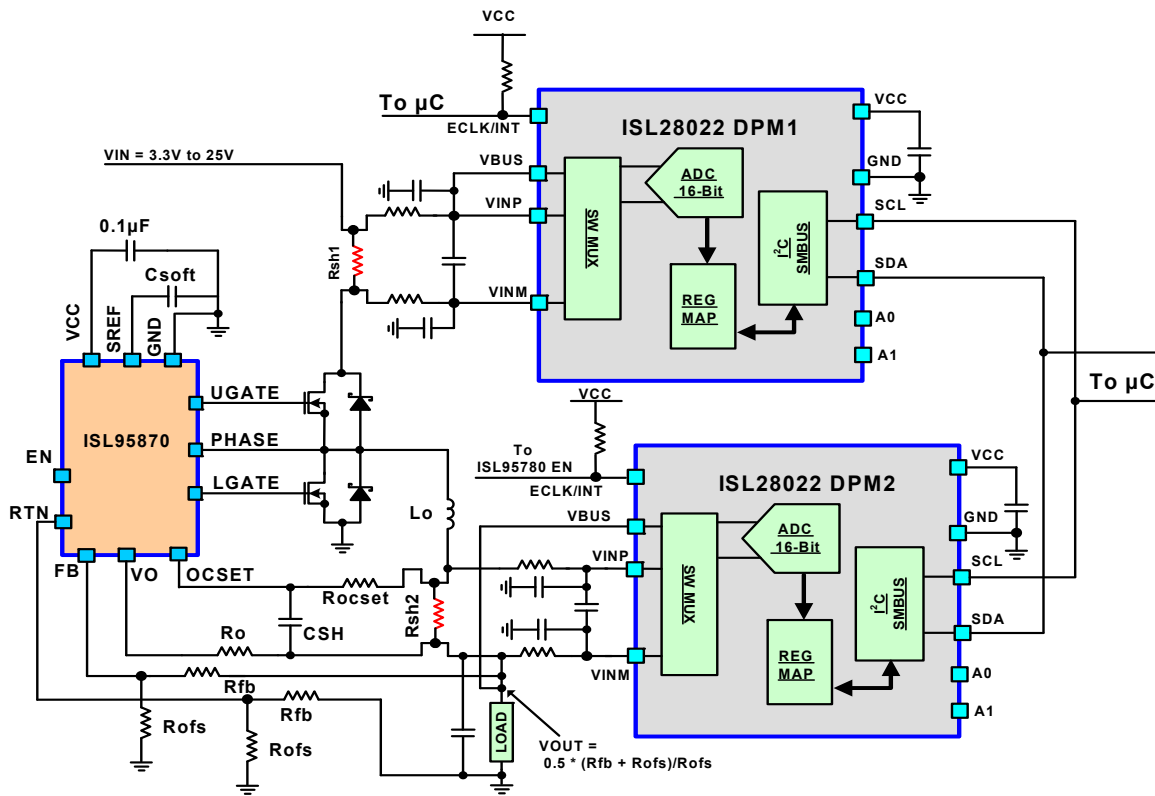


FIGURE 11. A SIMPLIFIED CIRCUIT THAT USES TWO ISL28022 TO MEASURE A SYSTEM EFFICIENCY

Monitoring MultiCell Battery Levels Using the DPM Broadcast Command

There are many battery chemistries in today's marketplace. Each battery chemistry has its own unique benefits and drawbacks. For example, lithium ion batteries can deliver a lot of power to a load for an extended period of time but the technology comes with a cost due to the exotic materials used to construct the battery. Lithium ion cells degrade uniquely with each charge and discharge cycle. Lithium ion batteries often are paired with multicell balancing circuits to maximize battery life and discharge time.

Lead acid batteries are cheap and a mature technology. Lead acid batteries have a predictable and uniform degradation versus discharge and charging cycles. The batteries have more loss with respect to delivering power to a load. Many customers that use lead acid battery technology do not require multicell balancing but desire cell monitoring to determine the charge on the battery. It is similar to fuel gauge measurement.

Figure 12 is a simplified circuit that monitors each cell of a 48V battery pack. The ISL28022 can measure voltages up to 60V. The ground of each ISL28022 is referenced to the ground of the battery pack. The negative terminal of the V_{BUS} input is the ground pin of the ISL28022. The ISL28022 has a unique feature that allows a master, microcontroller, to talk to all ISL28022s with one command. The use of the 0x7E slave address allows the master to write to all registers at once. The reading of the registers still has to be performed sequentially. The broadcast command allows the synchronization of measurements between two or more ISL28022.

Once a measurement has been retrieved by the master, each cell voltage is calculated by a series of subtractions.

$$V_{cell1} = V_{BUS}(DPM1)$$

$$V_{cell2} = V_{BUS}(DPM2) - V_{BUS}(DPM1)$$

$$V_{cell3} = V_{BUS}(DPM3) - V_{BUS}(DPM2)$$

$$V_{cell4} = V_{BUS}(DPM4) - V_{BUS}(DPM3)$$

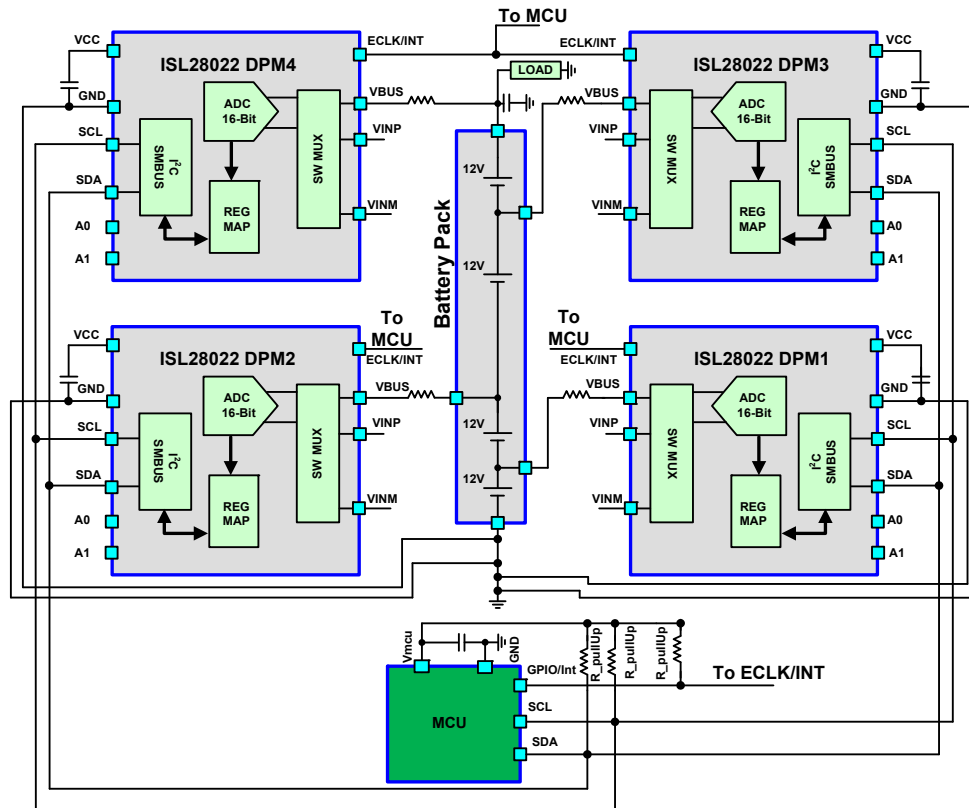


FIGURE 12. A SIMPLIFIED MULTICELL MONITORING CIRCUIT

Precision Current Sense

The inaccuracies in most current sensing applications reside with either the sense resistor or the measurement system. The ISL28022 has a measurement accuracy of $\pm 0.2\%$ typically. Depending on the magnitude of the current to be sensed, the current sense resistor, R_{SH} , is the least accurate device of the system. Applications that require large current measurements use small valued shunt resistors. The material composition of small resistors are often constructed with metal. Metal has a high temperature coefficient. Copper's temperature coefficient is 3862ppm/K. For a 50A current measurement system, the sense resistor value equals 0.8m Ω . Equation 9 is the relationship between Kelvin (K), Celsius (C) and Fahrenheit (F) temperatures.

$$C = \frac{5}{9} \cdot (F - 32) \quad C = K - 273 \quad (\text{EQ. 9})$$

Suppose a sense resistor, consisting of mostly metal, changes by 10°C. Assume the temperature coefficient of the sense resistor is 600ppm/C. The change in shunt resistance for a 10°C rise is calculated using Equation 10:

$$R = R_0 \cdot (1 + TC \cdot \Delta T) \quad (\text{EQ. 10})$$

R_0 is the original value of the resistor at T which equals T_0 (0.8 Ω). TC is the temperature coefficient of the shunt resistor (600ppm/C). ΔT is the change in temperature (10°C). The new resistance value of the shunt resistor is 0.8048m Ω . or a 0.6% change in resistance. The change in resistor value directly affects the measurement accuracy of the system.

Measuring the temperature change of the sense resistor with a known TC stabilizes the system accuracy measurement versus temperature. The simplified circuit in Figure 13 measures current and temperature. The ISL71590 or the commercial version of the part is a temperature sensor that outputs a current with respect to temperature. The output current changes 1 μ A/K.

Equation 11 is the temperature calculation with respect to a chosen r_{load} (R_1) value.

$$T_C = \frac{V_{BUS}}{1\mu \cdot R_1} - 273 \quad (\text{EQ. 11})$$

T_C is the temperature in centigrade. V_{BUS} is the bus voltage measured across the R_1 resistor. The V_{BUS} connects to the ISL28022. R_1 is the load resistor for the circuit. The temperature sensor needs at least 4V to operate. Equation 12 calculates the R_1 value that yields the largest temperature to voltage gain ratio.

$$R_1 = \frac{V - 4}{(T_{max} + 273) \cdot 1 \cdot \mu} \quad (\text{EQ. 12})$$

V is the voltage applied to the temperature sensor and the resistor. The temperature sensor requires a 4V drop across the sensor to be operational. T_{max} is the maximum temperature to be measured in centigrade.

Application Note 1955

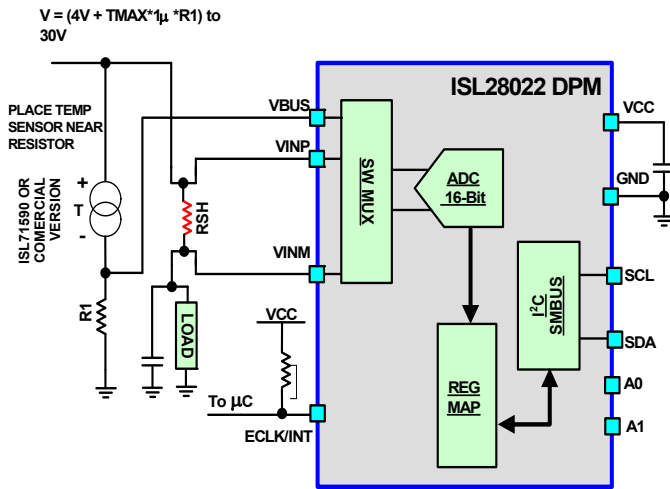


FIGURE 13. A SIMPLIFIED CIRCUIT DIAGRAM THAT MEASURES CURRENT AND TEMPERATURE

Ideas Using ISL28023

Generic Buck Regulator POL Circuit

The circuit in [Figure 14](#) is a generic step-down voltage circuit that converts a high voltage between 4.5V and 36V to a lower voltage that is at least 3V lower than the voltage applied to ISL85415. The output voltage to the load is programmed via the 8-bit margin DAC within the ISL28023, plus external resistors R_2 and R_1 . R_3 is used to more precisely tune the output voltage. For most applications, R_3 is not installed or optional. The 8-bit margin DAC within the ISL28023 has many voltage ranges allowing for more precision than 8-bits. V_{OUT} to the load can be calculated using [Equation 13](#).

$$V_{out} = 0.6 + (0.6 - DAC_OUT) \cdot \frac{R_2}{R_1} \quad (\text{EQ. 13})$$

The ISL85415 can deliver up to 500mA to a load. The buck regulator's ripple noise to the load is a function of the inductor value (L_o). Large value inductors result in low magnitude ripple currents, while sacrificing responsiveness to fast transient loads. The inductor (L_o) value for the circuit in [Figure 14](#) can be calculated using [Equation 14](#).

$$L_o = \frac{(V_{in} - V_{out}) \cdot V_{out}}{FS \cdot \Delta I} \cdot \frac{V_{out}}{V_{in}} \quad (\text{EQ. 14})$$

- V_{IN} is the input voltage to the ISL85415. The voltage can range from 4.5V to 36V.
- V_{OUT} is the regulated voltage value to the load.
- FS is the switching frequency of the buck regulator. For the ISL85415, the frequency can be programmed between 300kHz to 2MHz.
- ΔI is the desired ripple current. A common ripple current value is 30% of the full-scale current delivered to the load.

A bypass capacitor at the load is used to minimize the voltage noise to the load. The voltage ripple to the load is a function of

the type of bypass capacitor. The voltage ripple to the load can be calculated using either [Equation 15](#) or [16](#).

$$V_{out\text{ripple}} = \frac{\Delta I}{8 \cdot FS \cdot C_{\text{bypass}}} \quad (\text{EQ. 15})$$

$$V_{out\text{ripple}} = \Delta I \cdot C_{\text{bypass}} \quad (\text{EQ. 16})$$

Ceramic capacitors have lower series equivalent resistance than other electrolytic capacitors. [Equation 15](#) represents the $V_{out\text{ripple}}$ calculation with a ceramic capacitor as a bypass, and [Equation 16](#) represents the $V_{out\text{ripple}}$ when an electrolytic bypass capacitor is used.

- ΔI is the ripple current magnitude
- FS is the switching frequency of the buck regulator

RSH in [Figure 14](#) is the shunt resistor that converts the current delivered to the load to a voltage. The voltage is measured by the ISL28023. The full-scale voltage of the shunt inputs (V_{INP} - V_{INM}) is $\pm 80\text{mV}$. The value of the shunt resistor is digitized internally by the ISL28023 allowing the device to report current measurements.

The ISL28023 has analog comparators with user defined programmable digital thresholds allowing for the inputs of the primary shunt (V_{INP} , V_{INM}) and BUS (V_{BUS}) pins to be tested versus acceptable levels. The ISL28023 has two SMB alert pins. In [Figure 14](#), $SMBALERT1$ is an open drain connected to the enable pin of the ISL85415. In the alert event, the $SMBALERT1$ pin changes state causing the ISL85415 to become disabled. The $SMBALERT2$ has a push/pull output with logic levels tied to I^2C_{VCC} voltage. The $SMBALERT2$ is tied to the interrupt pin of the microcontroller. An unacceptable event on the primary channel alerts the microcontroller.

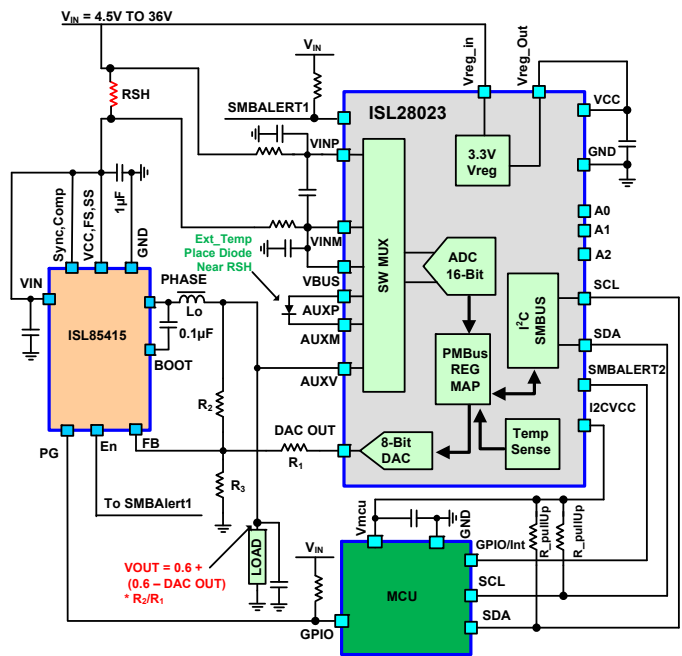


FIGURE 14. GENERIC POL CIRCUIT USING A BUCK CONVERTER AND THE ISL28023

Application Note 1955

The I²CVCC can either be tied to the VCC pin of the ISL28023 or to the power supply pin of the microcontroller. The I²CVCC pin controls the operation voltage of the ISL28023 digital core. Therefore, the I²C/SMBus/PMBus inputs and SMB alert pins logic levels are a slave to the I²CVCC voltage.

The ISL28023 has an internal 3.3V voltage regulator that accepts input voltages ranging from 4.5V to 60V. The regulator is used to power the ISL28023 and some light external peripheral circuitry. The maximum drive current of the voltage regulator is 6mA.

The ISL28023's auxiliary shunt channel (Aux_N,Aux_P) can be programmed to change functionality from measuring a voltage between ±80mV to measuring a temperature through a diode. The auxiliary channel's external temperature mode injects two currents (20µA/ 100µA) into the diode and measures the change in diode voltage between the two currents. The change in diode voltage translates to a temperature. Diodes are useful to accurately measure temperature change. A user may want to measure the temperature change of a resistor for accurate current measurements. The external temperature sense is useful for high current applications where the resistor material consists of mostly metal.

The AUXV pin can be used to measure the regulated voltage to the load. The AUXV pin can only measure voltages up to the VCC voltage of the ISL28023 chip. For the circuit in Figure 14, the maximum measurable voltage by the AuxV channel would be 3.3V.

Generic LDO Regulator POL Circuit

Low Drop Out (LDO) voltage regulators are mostly used in applications that require a regulated supply while a minimum voltage difference exists between the applied voltage to the regulator and the regulated voltage. A battery application is an example where an LDO may be used. LDO's may also be used in noise sensitive applications. There is no internal clock or switching signals within an LDO. Because of the lack of switching circuitry, the output regulated signal does not have noise compared to a buck regulator. Applications that are sensitive to EMI susceptibility may use an LDO.

The circuit in Figure 15 converts the bus voltage which is between 3V and 6V to a lower regulated voltage that can be as high as 400mV from the bus voltage applied to the ISL80101ADJ. The output voltage to the load is set via the 8-bit DAC, R₂ and R₁. R₃ is used to more precisely tune the output voltage. For most applications, R₃ is not installed. The 8-bit DAC within the ISL28023 has many voltage ranges allowing for more precision. V_{OUT} to a load can be calculated using:

$$V_{out} = 0.5 + (0.5 - DAC_OUT) \cdot \frac{R_2}{R_1} \quad (EQ. 17)$$

RSH in Figure 15 is a shunt resistor that converts the current delivered to the load to a voltage. The voltage is measured by the ISL28023. The full-scale voltage of the shunt inputs (VINP-VINM) is ±80mV. The value of the shunt resistor is digitized internally to the ISL28023 enabling the device to report current measurements.

The ISL28023 has analog comparators with user defined programmable digital thresholds. The comparator circuitry allows for inputs of the primary channel (VINP, VINM, VBUS) to be

tested versus programmable levels. The ISL28023 has two SMBALERT pins. In Figure 15, SMBALERT1 is an open-drain pin connected to the enable pin of the ISL80101ADJ. In the event of an alert, the SMBALERT1 pin changes state causing the ISL80101ADJ to become disabled. The SMBALERT2 has a push/pull output with logic levels tied to the I²CVCC voltage. The SMBALERT2 is tied to the interrupt pin of the microcontroller. An unacceptable event on the primary channel will alert the microcontroller.

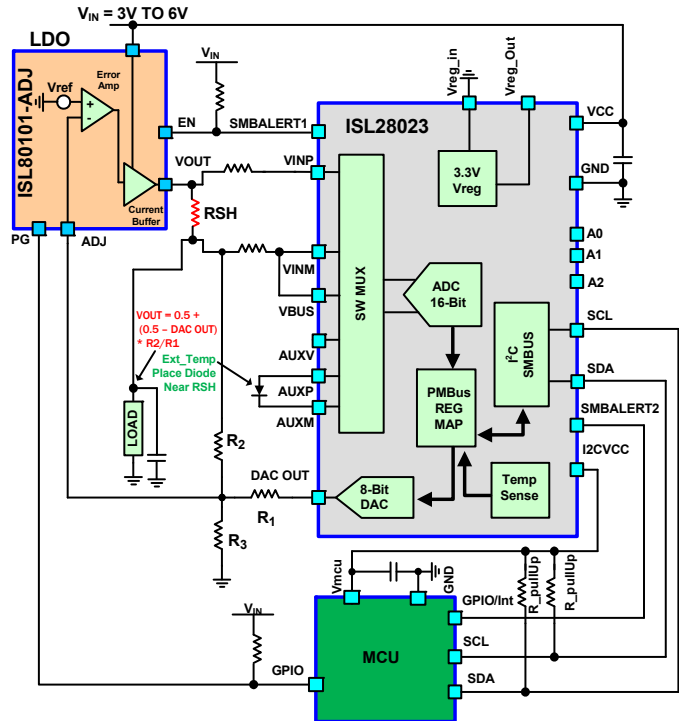


FIGURE 15. GENERIC POL CIRCUIT USING A LDO CONVERTER AND THE ISL28023

The I²CVCC can either be tied to the VCC pin of the ISL28023 or to the power supply pin of the microcontroller. The I²CVCC pin controls the operating voltage of the ISL28023 digital core. The I²C/SMBus/PMBus inputs and SMBALERT pins logic levels are a slave to the I²CVCC voltage.

The ISL28023's auxiliary shunt channel (Aux_N,Aux_P) can be programmed to change functionality from measuring a voltage between ±80mV to measuring a temperature through a diode. In the external temperature mode, a current source injects two currents (20µA/ 100µA) into an external diode measuring the change in diode voltage between the two currents. The change in diode voltage translates to a temperature. Diodes are good at accurately measuring temperature change. A user may want to measure the temperature change of a resistor for accurate current measurements. In high current applications, the material of a resistor consists mostly of metal. Metal has a high temperature coefficient. Monitoring the temperature change of a resistor allows for compensation of resistance change due to temperature.

The AUXV pin measures the regulated voltage to load. The AUXV pin measures voltages up to the VCC voltage of the ISL28023 chip. For the circuit in Figure 15, the maximum measurable voltage for the AuxV channel is the bus voltage to the circuit, V_{IN}.

Application Note 1955

Generic Boost Regulator POL Circuit

The circuit in [Figure 16](#) is a generic circuit that boosts the input voltage to a set output voltage that is dependent on the 8-bit DAC inside the ISL28023. The ISL97516 can boost input voltages from as low as 2.3V to 25V. The circuit in [Figure 16](#) is able to boost input voltages from 3V to 25V. This is due to ISL28023 minimum supply voltage.

The circuit in [Figure 16](#) is designed with two shunt resistors (R_{SH} , R_{SH2}) to measure the efficiency, η , of the regulator. R_{SH2} resistor measures the total current to the regulator and the load. R_{SH2} is connected to the auxiliary channel of the ISL28023. The auxiliary channel can accept voltages from 0 to V_{CC} of the ISL28023. A basic filter is designed between the R_{SH2} and the auxiliary input. The filter may not be required depending on the desired accuracy of the measurement, and the signal purity from the input source, V_{rail} .

R_{SH} measures the high voltage current to the load. The supply voltage to the load, V_{OUT} , is greater than V_{CC} . The R_{SH} resistor is connected to the primary channel (VINP, VINM, V_{BUS}) because the inputs accept voltages up to 60V. The primary channel

connects to a series of analog alert comparators. The alerts can be conditioned for polarity, duration, and threshold levels. The alerts can be masked and uniquely configured for each alert pin. The alert pins are labeled as SMBALERT1 and SMBALERT2. SMBALERT1 is an open drain that requires a pull-up resistor up to 20V to operate properly. SMBALERT2 has a push/pull output stage with logic levels tied to the I^2C voltage. SMBALERT2 is tied to the enable pin of the ISL97516. If an overcurrent or over/undervoltage event occurs, SMBALERT2 will change state causing the ISL97516 to become disabled. SMBALERT1 is tied to the microcontroller.

Assume a circuit diagram has the many ISL28023 modules connected to the same I^2C bus. All modules have SMBALERT1 tied to the interrupt/GPIO pin of the microcontroller as shown in [Figure 17](#). In the event of an alert from any or multiple modules SMBALERT1 will change logic state resulting in an interrupt to the microcontroller. The ISL28023 has a unique broadcast command that returns the lowest valued slave address that has a SMBALERT1 error. The command feature prevents the microcontroller from having to find the ISL28023(s) with a SMBALERT1 error.

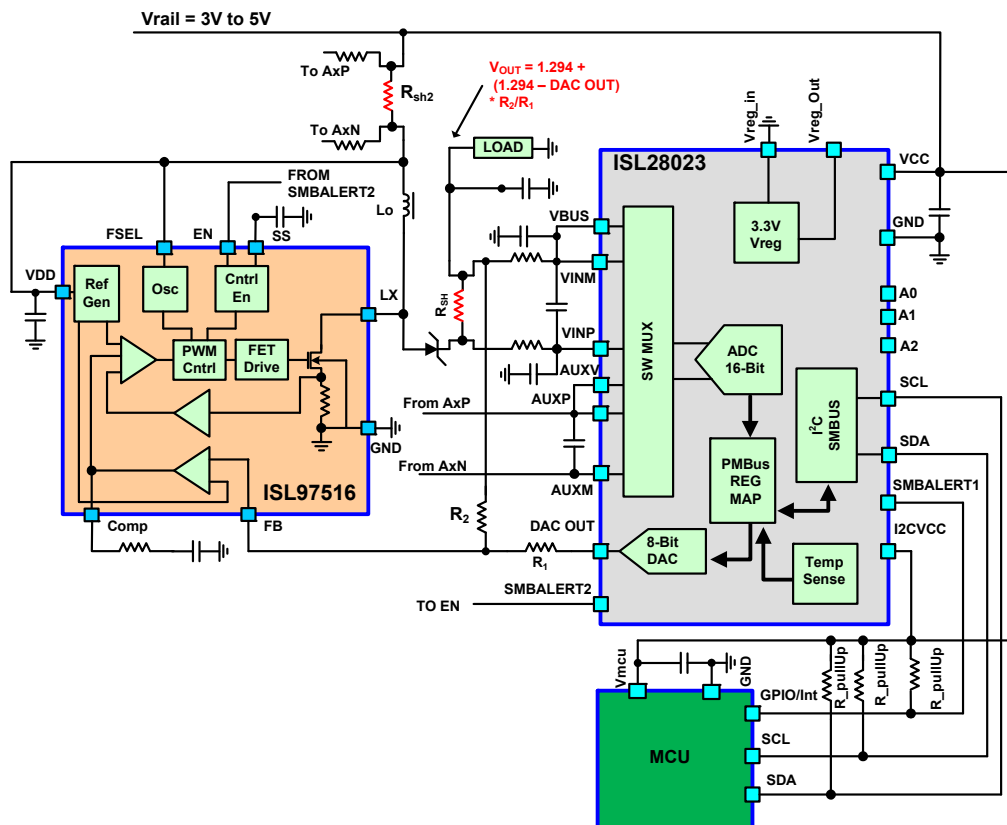


FIGURE 16. GENERIC POL CIRCUIT USING A BOOST CONVERTER AND THE ISL28023

Application Note 1955

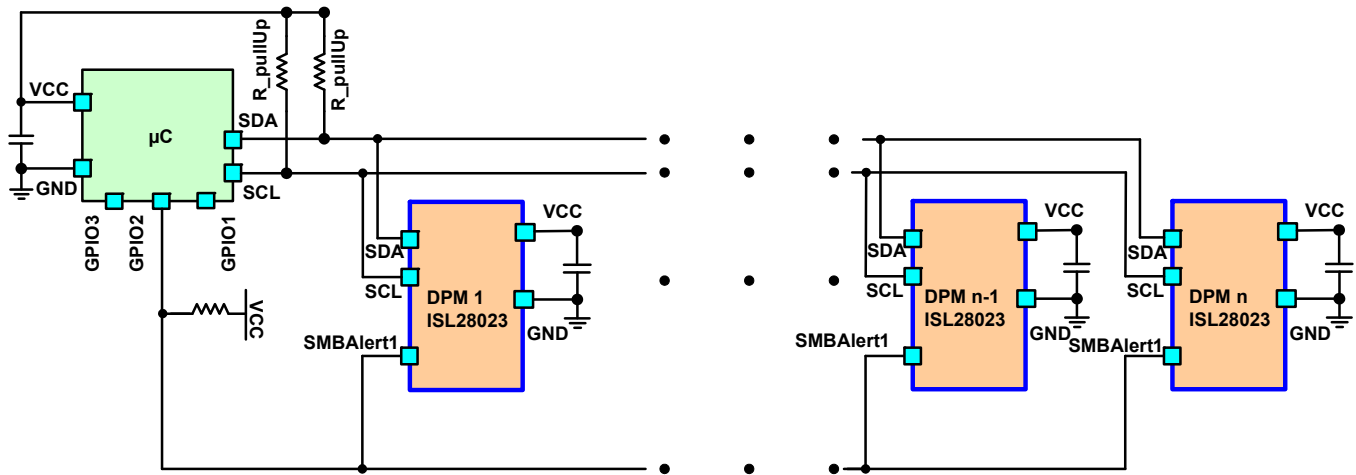


FIGURE 17. A SIMPLIFIED CIRCUIT ILLUSTRATION SHOWING MULTIPLE ISL28023s CONNECTED TO ONE SMBUS AND ONE SMBALERT1 LINE

The voltage to the load is set by configuring the 8-bit DAC inside the ISL28023 and the ratio of R_2 to R_1 . The 8-bit DAC has 8 voltage ranges allowing the user to fine tune the output voltage. The output voltage can be set using Equation 18.

$$V_{out} = 1.294 + (1.294 - DAC_OUT) \cdot \frac{R_2}{R_1} \quad (EQ. 18)$$

The performance of the ISL97516 is dependent on the chosen inductor, L_o . The chosen inductor should be able to handle the peak current delivered to load. The inductor value can be calculated using Equation 19.

$$L = \frac{V_{in}^2 \cdot (V_{in} - V_{out})}{2 \cdot V_{out} \cdot F_{sw} \cdot (I_{out} \cdot V_{out} - I_{peak} \cdot V_{in})} \quad (EQ. 19)$$

- V_{IN} is the bus voltage supplied to the boost regulator.
 - For Figure 16, the input voltage is between 3V and 25V.
- V_{OUT} is the desired regulated voltage.
 - The output voltage is between 3V and 25V. The output voltage is always greater than the input voltage.
- I_{OUT} is the average current delivered to the load.
- I_{PEAK} is the peak inductor current.
- F_{SW} is the switching rate of the regulator.
 - The switching frequency of the regulator can be programmed to either 620kHz or 1.25MHz.

Inductor values between 2µH to 33µH are common.

A bypass capacitor at the load is used to minimize the voltage noise to the load. The voltage ripple to the load is a function of the type of bypass capacitor. The voltage ripple can be calculated using Equation 20.

$$V_{out_ripple} = \frac{I_{out} \cdot \left(1 - \frac{V_{in}}{V_{out} + V_{diode}} \right)}{F_{sw} \cdot C} + I_{out} \cdot ESR \quad (EQ. 20)$$

- I_{OUT} is the current delivered to the load
- V_{IN} is the bus voltage supplied to the boost regulator
- V_{OUT} is the regulated voltage
- V_{diode} is the activation voltage of the diode
 - This is nominally equaled to 0.6V
- F_{sw} is the switching voltage of the ISL97516
- C is the chosen bypass capacitor value
- ESR is the equivalent series resistance of the capacitor
 - For X5R and X7R ceramic capacitors, the value is low
 - Tantalum and other electrolytic capacitors have a higher ESR value

High Side Voltage and Current Circuit

There are many applications today that require voltage and current protection to a load. The circuit in Figure 18 monitors the current and voltage to the load. In the event of an overcurrent or voltage, an alert will be triggered causing the SMBALERT2 pin to change logic state from a high to a low. Q1 will turn off causing M1 to turn off. The event results in power to the load being severed.

The circuitry drawn in Figure 18 accepts voltage values from 4.5V to 60V. The minimum voltage the internal 3.3V regulator can regulate is 4.5V. The 3.3V regulator powers the ISL28023 and the MCU. The regulator sources 6mA of current. The MCU connected to the power supply should draw less than 5mA.

AN ALTERNATIVE CONNECTION

If the monitored voltage is between 4.5V and 20V, Q1 and RS can be eliminated from Figure 18 by using the SMBALERT1 pin to control the M1 MOSFET. Another alternative connection is to monitor the current on the low side of the load as shown in Figure 19.

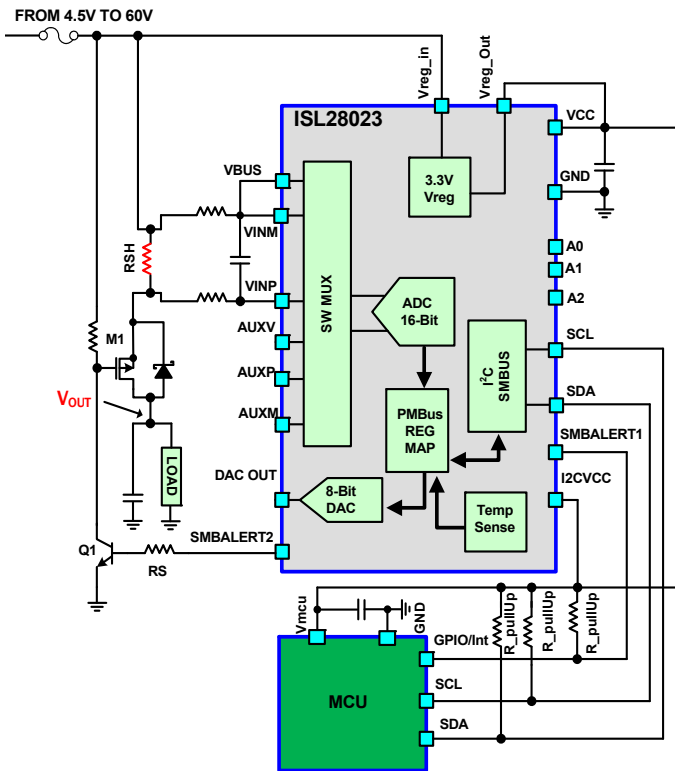


FIGURE 18. GENERIC POL CIRCUIT USING AN LDO CONVERTER AND THE ISL28023

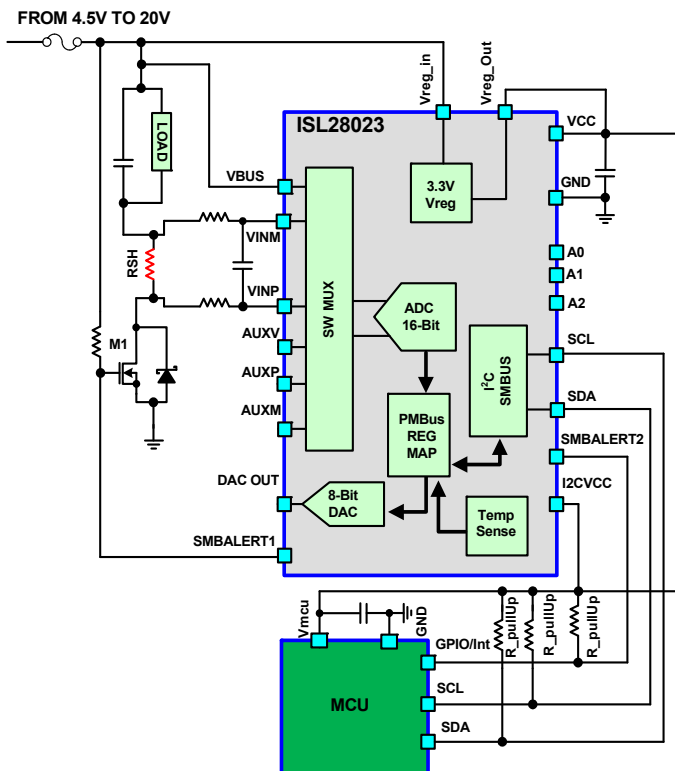


FIGURE 19. LOW SIDE VOLTAGE AND CURRENT MONITORING CIRCUIT THAT USES SMBALERT1 AS A CONTROL

Using a Switch as a Sense Resistor

In low voltage applications, the voltage drop resulting in measuring a current through a sense resistor is significant with respect to the load voltage. The shunt channels of the ISL28023 (VINP, VINM and AUX_P, AUX_N) have a full-scale voltage range of $\pm 80\text{mV}$. A full-scale voltage drop across a sense resistor from a 0.85V supply is roughly 10%. Many applications have a switch or FET in series to the load in the event that power to the load can be severed when too much current is sourced to the load. The simplified schematic in Figure 20 is an example of a switch used as sense resistor and to cut power to the load.

The ISL8366 is a low r_{ON} quad switch used as circuit breaker and sense resistor to load. One switch within the ISL8366 can pass up to $\pm 300\text{mA}$ of current. Four switches in parallel can handle 1.2A of current. The average ON-resistance for a single switch is 0.266Ω across the current range. The graph in Figure 21 illustrates the ON-resistance of the ISL8366 versus the current passing through the switch. The ON-resistance is flat from 1mA to 300mA. At lower currents the ON-resistance varies by approximately $5\text{m}\Omega$.

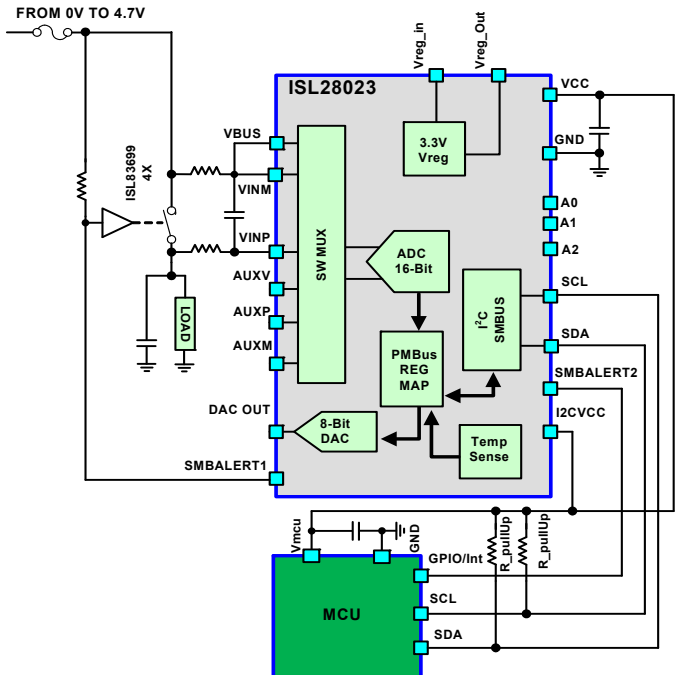


FIGURE 20. A SIMPLIFIED SCHEMATIC OF A SWITCH USED AS A SENSE RESISTOR

Application Note 1955

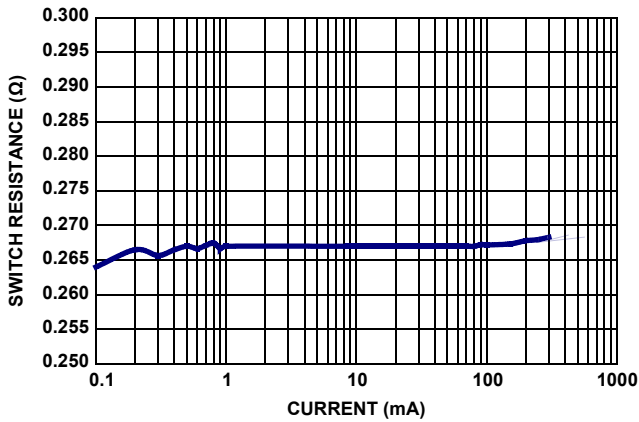


FIGURE 21. CMRR VS FREQUENCY

Connecting four switches in parallel divides the r_{ON} resistance by four as well as the variance across current. The sense resistor becomes 66.5mΩ.

The full-scale range of the primary shunt input is $\pm 80\text{mV}$. From Ohms law, the maximum current that is measured for 67mΩ sensing element is 1.2A. The application may require the highest resolution for measurable currents to 750mA. The V_{SHUNT} reading for 750mA of current with a 67mΩ sensing element is 49.88mV. The ISL28023 has configurable current range. The LSB (least significant bit) is calculated by using Equation 21.

$$\text{Current}_{\text{LSB}} = \frac{\text{Current}_{\text{FS}}}{\text{ADC}_{\text{res}}} = \frac{0.75}{32768} = 2.289\mu\text{A} \quad (\text{EQ. 21})$$

$\text{Current}_{\text{FS}}$ is the full-scale measurable current or 750mA for this application. ADC_{res} is 15 bits in one current direction (0mA to 750mA). The ISL28023 calculates the current for each reading if the CalReg is programmed properly. The CalReg is calculated using Equation 22.

$$\text{CalReg}_{\text{val}} = \text{integer} \left[\frac{0.00512}{(\text{Current}_{\text{LSB}} \cdot R_{\text{shunt}})} \right]$$

$$\text{CalReg}_{\text{val}} = \text{integer} \left[\frac{0.00512}{(2.2289 \cdot 10^{-6} \cdot 0.0665)} \right] = 34543 \quad (\text{EQ. 22})$$

The current measurement for the primary shunt can be read from register 0x8C. The decimal current is calculated using Equation 23.

$$\text{Current} = \text{Reg}_{0x8C_{\text{value}}} \cdot \text{Current}_{\text{LSB}} \quad (\text{EQ. 23})$$

$\text{Reg}_{0x8C_{\text{value}}}$ is the value returned from reading register 0x8C of the ISL28023. $\text{Current}_{\text{LSB}}$ is the value from Equation 21.

4 Gas Sensing Circuit

Gas monitoring is prevalent in safety and manufacturing applications. Gas Sensing, more specifically electrochemical gas sensing, keeps miners safe from such toxins as hydrogen sulfide (H_2S) and carbon monoxide (CO). Households in the US are required to have CO detectors along with fire detectors for air quality protection. The food industry is using gas sensors to

determine the freshness of food at fisheries and at the supermarket. In the manufacturing process, gas sensors are used to monitor the amount of gas element transferred from one medium to another.

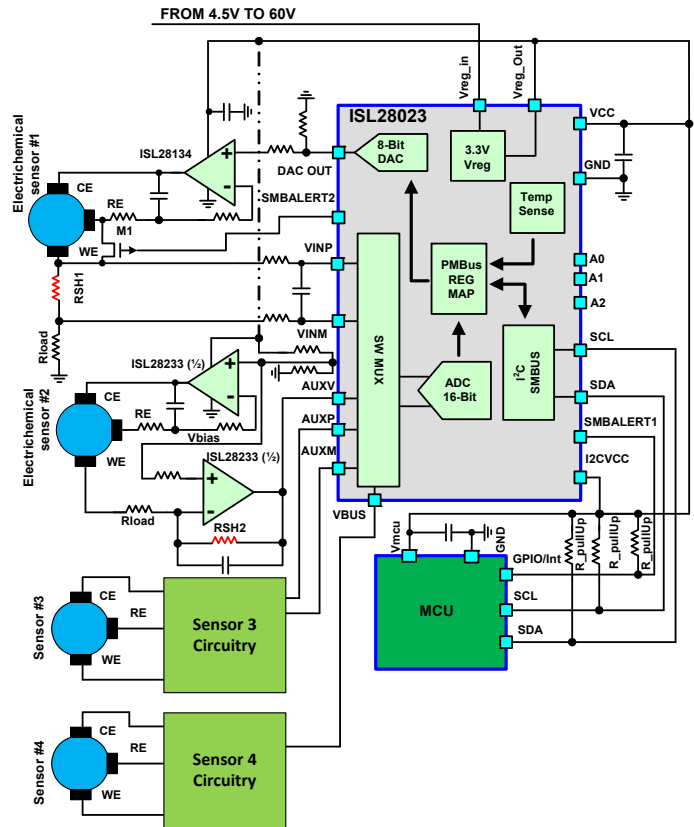


FIGURE 22. A SIMPLIFIED SCHEMATIC FOR GAS SENSING

The ISL28023 is a full featured digital power monitor that has a DAC, ADC and alert comparators. The ISL28023 reduces to an I²C ADC/DAC with alerts. The simplified circuit in Figure 22 is a four element gas sensor.

The ISL28023 has an internal 3.3V regulator that regulates voltages from 4.5V to 60V. The regulator is used to power the ISL28023 and low power peripheral sensor circuitry.

Most electrochemical sensors are nonbiased (do not require an activation voltage). In the case of measuring a gas concentration using a biased sensor, the ISL28023 has an internal 8-bit DAC with many voltage ranges to bias the sensor. The electrochemical sensor1 in Figure 22 is a biased sensor. The sensor is biased via the internal DAC and the ISL28134. The ISL28134 is a low noise, zero offset chopper stabilized amplifier. The amplifier is used to ensure the solution potential is equal to the DAC output voltage versus current change. The electrochemical solution (electrolyte) between the counter electrode (CE) and the working electrode (WE) has an impedance. As the concentration of the selective gas increases, more current flows. The increased current flow with electrolyte resistance changes the potential between the WE and CE electrodes. The resultant is a less than predictable conversion of gas concentration to current flow. The reference electrode (RE) is an electrode that monitors the solution potential.

Application Note 1955

In [Equation 13](#), R_{SHUNT} is equal to the shunt resistor, R_{SH} , value. $V_{shuntFS}$ is the full scale voltage value of the shunt channel (V_{INP} , V_{INM}). In most applications the value is equal to 80mV. For applications that require a full scale range less than 80mV, the defined value should be used as the $V_{shuntFS}$ value.

Utilizing the result of the $Current_{FS}$ equation, the $Current_{LSB}$ is calculated using [Equation 14](#).

$$Current_{LSB} = \frac{Current_{FS}}{ADC_{res}} \quad (EQ. 26)$$

The ADC_{res} variable is the resolution of the ADC in one sign direction. The ADC_{res} equals 2^{15} or 32768.

The integer value from the resultant of [Equation 27](#) is the value programmed into the $IOUT_CAL_GAIN$, reg 0x38, register to enable current calculations.

$$CalReg_{val} = \text{integer} \left[\frac{0.00512}{(Current_{LSB} \cdot R_{shunt})} \right] = \text{integer} \left(\frac{167.77216}{V_{shuntFS}} \right) \quad (EQ. 27)$$

The overcurrent, OC, comparator can be configured to trigger an alert for a user defined overcurrent condition. Any alert conditions from the V_{BUS} or V_{SHUNT} (V_{INP} and V_{INM}) inputs can trigger the $SMBALERT$ pin causing the regulator to turn off.

Measure AC Currents

There are many applications that utilize the use of alternating current (AC) signal sources to either control or activate a load. Motors and power distribution circuits are some examples of AC loads.

The ISL28025 is able to measure lower frequency signals. The ISL28025 can be programmed to uniquely configure the acquisition time of each input. The ADC acquisition time directly determines the measurable bandwidth of an input. [Figure 24](#) is the bandwidth response of the ISL28025 vs ADC timing.

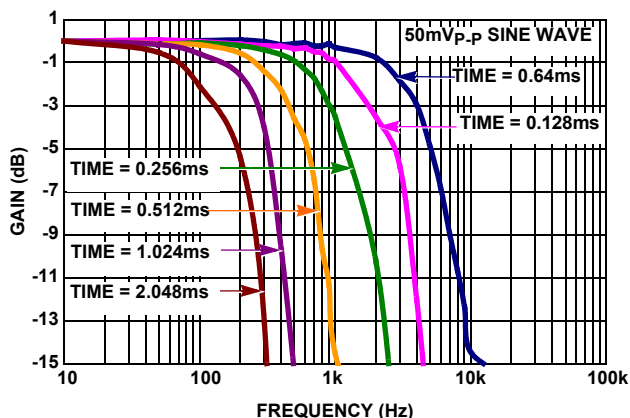


FIGURE 24. V_{SHUNT} BANDWIDTH vs ADC TIMING

The circuit in [Figure 25](#) configures the ISL28025 V_{SHUNT} input (V_{INP} , V_{INM}) as a low side current sense. The primary inputs (V_{INP} , V_{INM} and V_{BUS}) of the ISL28025 are able to accept input voltages ranging from 0V to 60V. The primary V_{SHUNT} input has a measurable range of $\pm 80mV$. The low side current sensing

architecture with the dynamic inputs of the ISL28025 allows for high voltage current measurements. Programming the digitized shunt resistor, R_{SH} , value into the ISL28025 enables current measurements from the device.

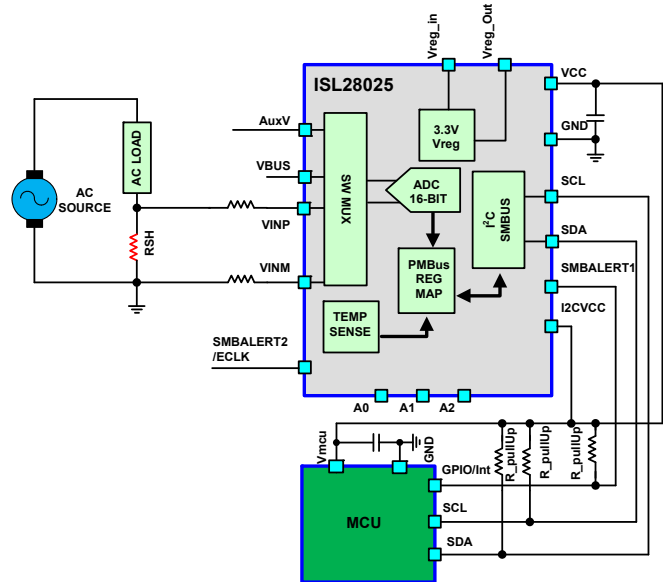


FIGURE 25. SIMPLIFIED CIRCUIT USING THE ISL28025 TO MEASURE AC CURRENTS

The ISL28025 measures current accurately from a common mode of -30mV to 60V. The graph in [Figure 26](#) illustrates the current measurement capabilities versus the common mode shunt voltage of the ISL28025.

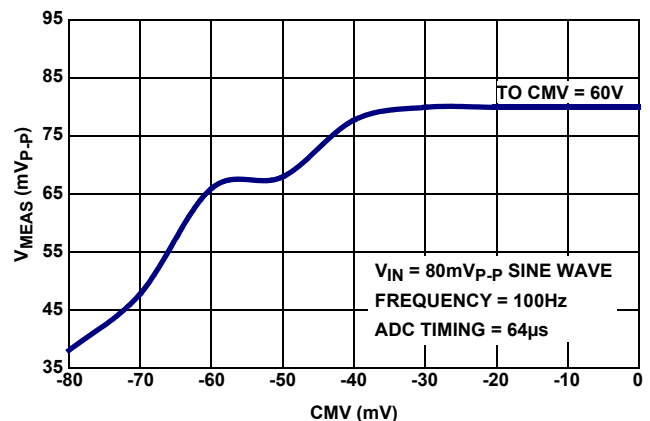


FIGURE 26. PRIMARY V_{SHUNT} AC COMMON MODE VOLTAGE RANGE

Sensor Monitor

There are many applications that quantify the analog world. Applications range from safety to controlling a manufacturing process. The root of each application requires a sensor, which translates the desired analog parameter to a fundamental electronic parameter of voltage, current, resistance or frequency.

[Figure 27](#) is a simplified electronic circuit that translates pressure to a digital signal. Suppose a 24V battery is connected to the pressure monitor powering the electronic circuitry as well as the safety valve for the pressurized container. The ISL28025

Application Note 1955

has an integrated 3.3V voltage regulator that regulates input voltages between 4.5V to 60V. The voltage regulator can be used to power up the ISL28025 and some light powered peripheral circuitry. The voltage regulator powers the pressure sensor, the ISL28025 and the MCU.

The pressure sensor in [Figure 27](#) translates pressure into current. The ISL28025 uses VINP and VINM to monitor the current from the sensor. The ISL28025 has analog comparators that detects overvoltage, undervoltage and overcurrent conditions on the V_{BUS} and V_{SHUNT} (VINM and VINP) inputs. The response time of each comparator is approximately 0.5µs. The response of the comparator can be configured for glitch response, masking and alert polarity.

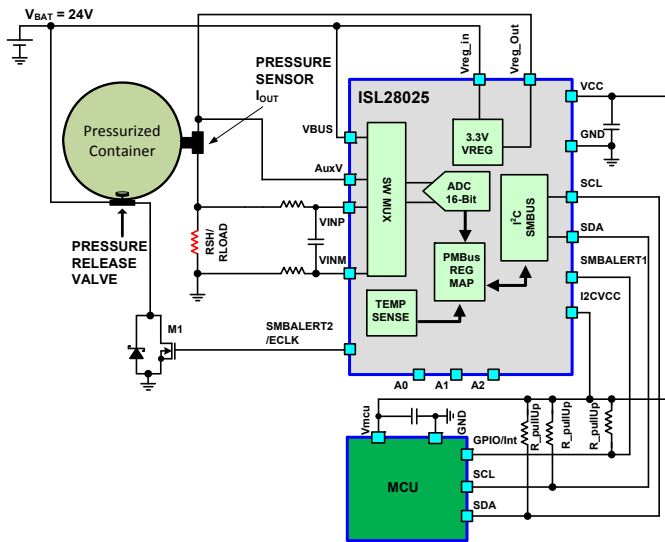


FIGURE 27. SIMPLIFIED SCHEMATIC OF A PRESSURE MONITOR WITH A SAFETY FEATURE

The pressure circuit is connected to the SMBALERT2, which is a push/pull output stage that has logic levels agreeable to the voltage applied to the I2CVCC pin. The SMBALERT2 pin controls a valve by way of a transistor. If the pressure in the chamber exceeds a threshold pressure, the ISL28025 will signal an alert to the SMBALERT2 pin, which energizes a pressure relieving valve resulting in the pressure in the container to reduce.

The V_{BUS} input is used to monitor the battery voltage and the AuxV input monitors the 3.3V voltage.

The ISL28025 is offered in a WLCSP16 package. The package is frugal on space and perhaps can be mounted on the back of the pressure sensor.

Real Time Power Monitor System for Real Time Operating Systems, RTOS

For many real time monitoring systems (RTOS), the use of real time power measurements for determining the efficiency of software to monitoring the security of the real time system (RTS).

The circuit in [Figure 28](#) is a simplified circuit that uses two ISL28025s to measured real time power. The Group Command from the PMBus command set synchronizes both ISL28025s to the same acquisition starting time.

The Group Command is a concatenation of two or more instructions sent from the master. Each instruction is separated by a repeat start command. The execution of the instructions begins when the start bit is received by the slave. An illustration of the Group Command protocol is shown in [Figure 29](#).

Application Note 1955

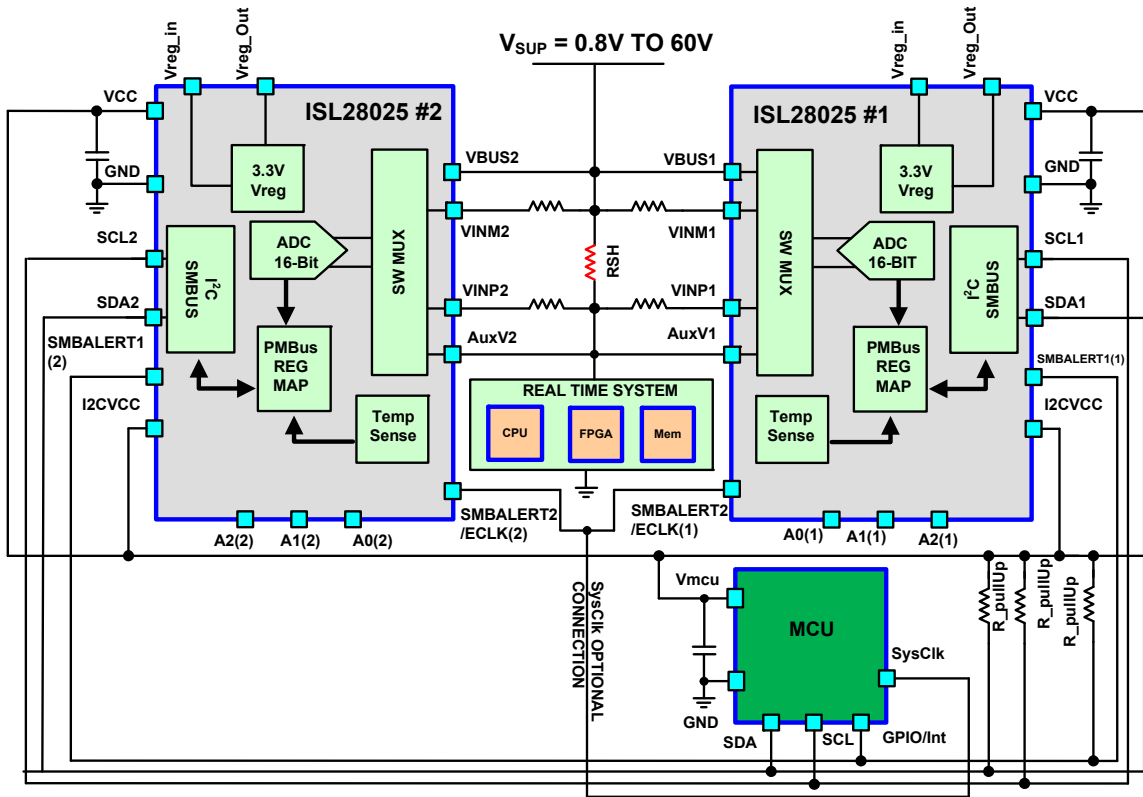


FIGURE 28. SIMPLIFIED EXAMPLE OF TWO ISL28025 CONFIGURED TO MEASURE REAL TIME TO A RTO SYSTEM

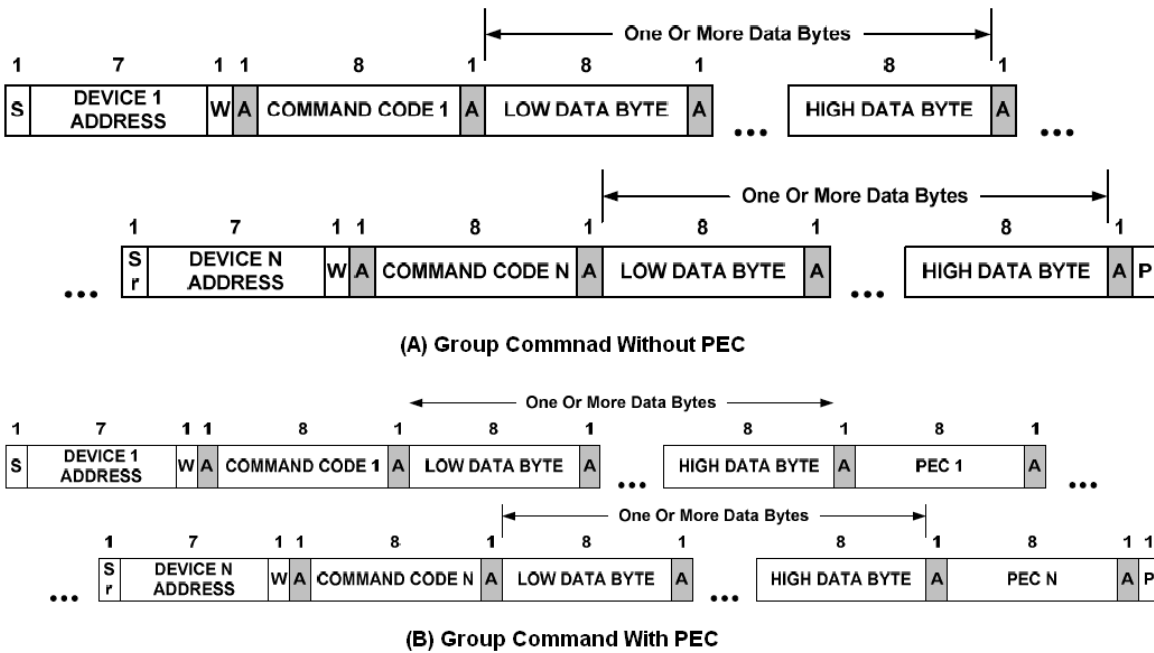


FIGURE 29. GROUP COMMAND (A) WITHOUT PEC (B) WITH PEC

Application Note 1955

All measurements between the two ISL28025 chips will remain synchronized as well as each ISL28025 system clock is matched or another Group Command is received. To guarantee synchronized acquisitions, the microcontroller can supply a system clock to each ISL28025 EXTCLK pin. The system clock will control the internal clock of each ISL28025. The acquisition times set by the Configure IChannel (Reg 0xD4) and Configure VChannel (Reg 0xD5) channels are based on an internal system clock of 500kHz. Apply an internal system clock either high or lower will adjust the acquisition times inversely to the ratio of the applied internal system clock frequency to the default system clock frequency of 500kHz. The effects of varying the system clock frequency is displayed in [Figure 30](#).

To measure real time power, one of the ISL28025s should read current constantly while the other measures the voltage delivered to the RTS. The microcontroller (MCU) will read each device individually and multiply the current and voltage values to yield the power consumption at the instant of time.

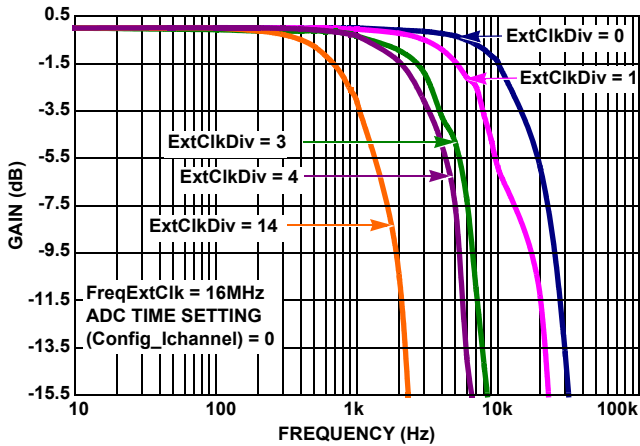


FIGURE 30. MEASUREMENT BANDWIDTH vs EXTERNAL CLK FREQUENCY

A SLOWER MEASUREMENT OF POWER

One ISL28025 can measure power but does so in a ping pong manner. The ISL28025 will measure voltage and then current followed by a calculation of power. [Figure 31](#) illustrates a slower version of monitoring power to the RTS.

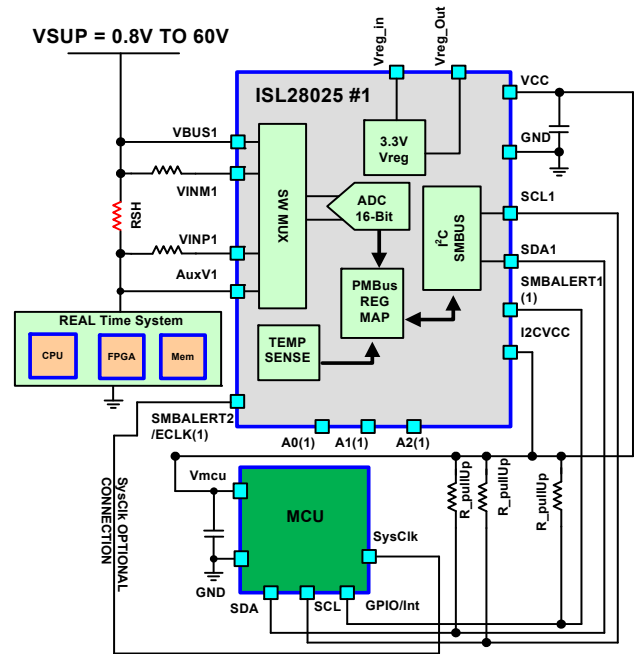


FIGURE 31. SIMPLIFIED CIRCUIT THAT MEASURES POWER DELIVERED TO THE RTS SYSTEM AT A SLOWER RATE

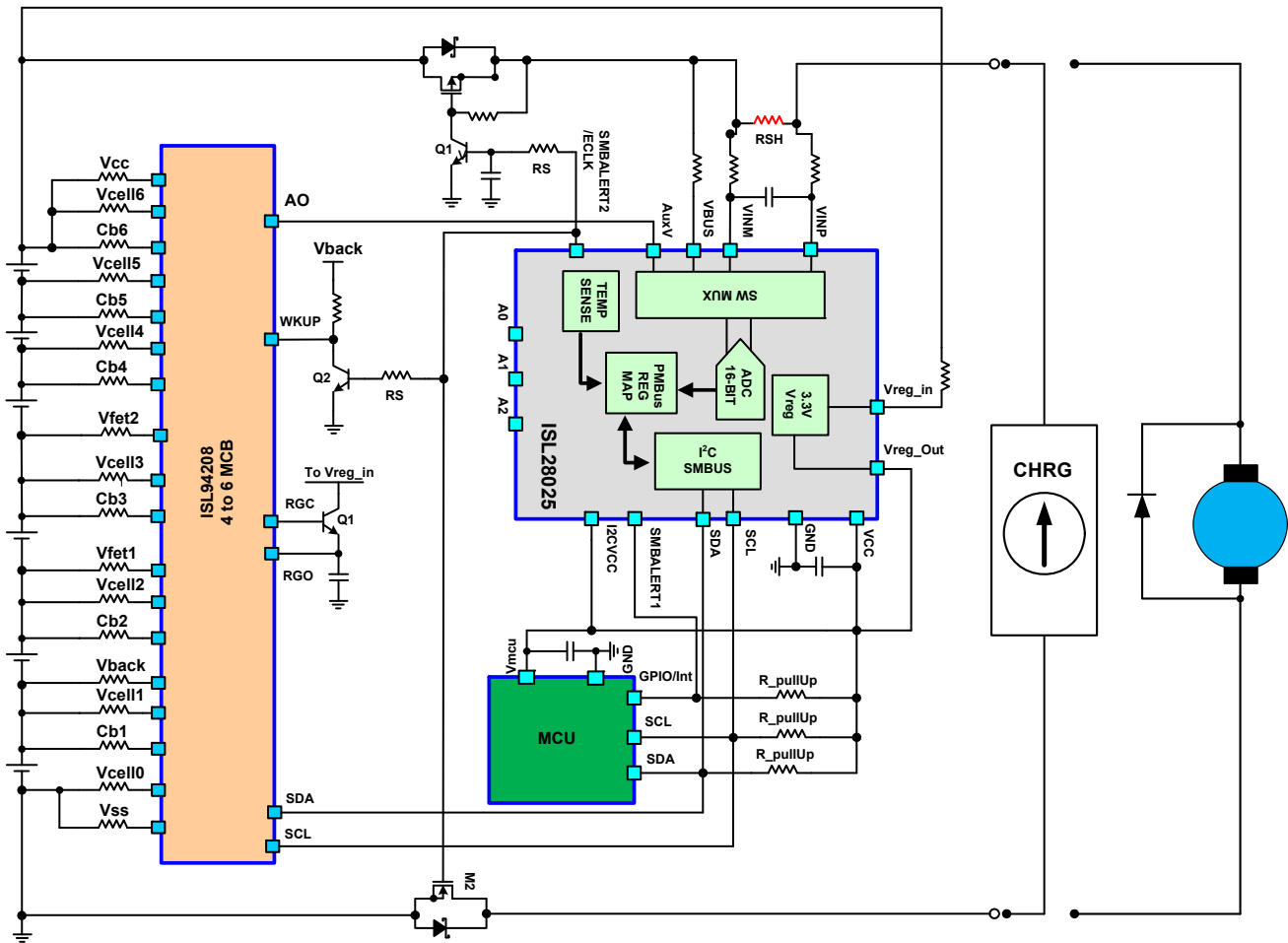


FIGURE 32. SIMPLIFIED CIRCUIT FOR MULTICELL BALANCING

DPM Used as a Control and Alert for a Multicell Balancing Circuit

Batteries are used in many applications such as electric vehicles, power tools, medical electronics, battery backup systems and other portable electronics. The development of battery technologies to utilize unique chemical offerings have improved the lifetime and the source current of a battery. The elements used to improve battery technology are not as plentiful as older technologies. The use of these elements increase battery cost. Designs that utilize newer battery technologies require monitoring each battery cell as well as balancing the cells evenly. In balancing the cells, the overall battery life improves, the usage times improve and the health of the battery is always known.

Figure 32 is a simplified circuit for a 6-cell battery pack. The ISL94208 is ideal for Li-ion batteries. The ISL94208 is a multicell balancing controller that routes the battery voltage of each cell through a multiplexer to pin AO, where the voltage can be read. AO is connected to the AUXV pin of the ISL28025.

The ISL28025 is powered by the battery pack through a 3.3V regulator. The input of the 3.3V regulator accepts input voltages from 4.5V to 60V. The voltage regulator is capable of powering some low powered circuitry along with the ISL28025.

The primary shunt input (VINP, VINM) operates in the presence of common mode voltages ranging from 0V to 60V. The ISL28025 can calculate the current by digitizing the shunt resistor value, RSH. The VBUS input is able to measure voltages up to 60V. The VBUS pin is connected to the top of the battery pack. The measurement node is known as the pack voltage.

SMBALERT2 is a push/pull output pin that drives a NMOS (M2) and a PMOS (M1) via a transistor (Q1). The ISL28025 has analog comparators that monitor the primary bus and shunt inputs for overvoltage, undervoltage and overcurrent conditions. In the event that a comparator is tripped, the SMBALERT2 can disconnect the charger circuit or load from the battery pack. The reaction time of the analog comparators are roughly 500ns. The SMBALERT pins active polarity and force state can be set through I²C commands.

The Q1 transistor is connected to the RGO and RGC pins of the ISL94208 which activates the 3.3V regulator inside the ISL94208. The Q1 transistor should be able to accept VCE equal to 60V.

The ISL94208 is a battery management analog front end IC has internal controlling FETs to bypass a cell from charging in the instance of an unequal charge distribution within a battery pack. The integrated balancing FETs have the ability to reroute a maximum of 200mA charging current.

Application Note 1955

The ISL94208 has a deep sleep feature that shuts down all essential circuitry. The device consumes up to 10 μ A of supply current in deep sleep mode. The ISL28025 has a low power mode. The ISL28025 consumes less than 1 μ A in this mode. The wake-up mode is activated when a low to high logic state transition is received from the SMBALERT2 pin of ISL28025. Q2 is activated causing the WKUP pin logic state to transition from high to low. The transition of WKUP pin logic state results in the ISL94208 waking up.

All functionality of the chip is controlled through an I²C interface.

PMBus Compatible Products Simplifies System Designs and Programming Them

PMBus is an industry standard that standardizes the register maps across products. The PMBus capability simplifies the coding required to communicate to each chip. If several unique PMBus products have an analog-to-digital converter, ADC, integrated into the chips and are connected to the same I²C bus, the programmer needs to command a read from one register to receive the results from each integrated circuit. Controlling each IC works the same way.

Figure 33 illustrates a system that includes both digital power monitors and Intersil's power modules. The ISL28025 versatile input range (0V to 60V) makes the integrated circuit easy to design in. The ISL28025 is an easy solution to monitoring system power in evolved power applications. DPM1 in Figure 33 is connected to monitor the overall system power delivered to the localized subsystems. The SMBALERT2 of DPM1 controls a FET switch, M1, to act like a circuit breaker to the subsystems. DPM1 allows the user to quickly monitor the health of a system.

The drain of M1 feeds into a power subsystem. An example of a power subsystem is representative in DPM2 through 4 and Intersil 1 to 3. Intersil has a portfolio of the power products, ZLxxx series, which regulate set voltages for high current point of loads applications. The Intersil products use a DC/DC architecture to regulate a supply. The architecture is good for delivering large currents to a load in an efficient manner at the cost of a noisier supply voltage. Some power subcircuits may require a more precise load with less current. In such cases, a LDO regulator can be employed with a DPM.

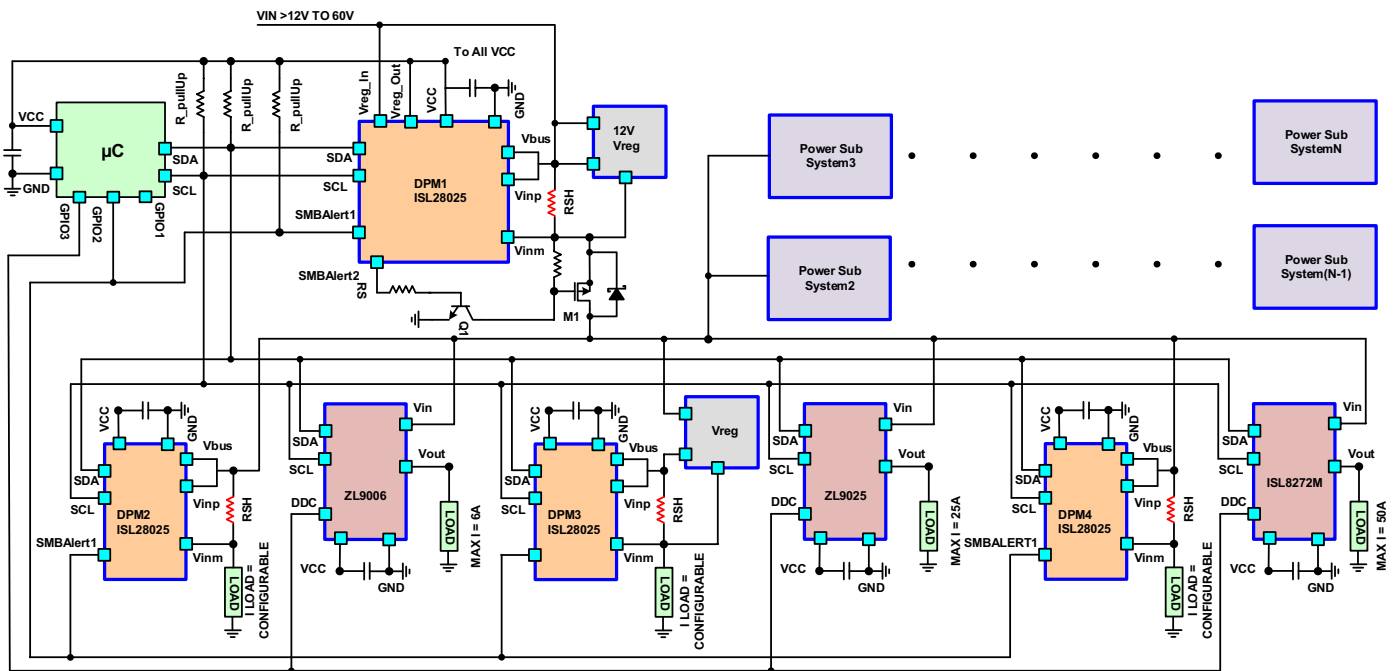


FIGURE 33. AN EXAMPLE OF A POWER DISTRIBUTION SYSTEM USING THE ISL28025 AND INTERSIL ZLXXXX SERIES

Intersil Corporation reserves the right to make changes in circuit design, software and/or specifications at any time without notice. Accordingly, the reader is cautioned to verify that the document is current before proceeding.

For information regarding Intersil Corporation and its products, see www.intersil.com