

Optimum AC performance of current feedback amplifiers in general and of the HA-5020 in particular depends upon careful selection of the feedback resistor, R_F . The benefit of higher usable bandwidth (compared with conventional voltage feedback amplifiers) and the ability to control the frequency response (by choosing the value of R_F) carries an expense in that the design process becomes more complicated. This is particularly true if an intuitive knowledge of how the device will behave in the end application is lacking. The purpose of this App Note is to provide a conceptual foundation on which this intuitive knowledge can be built.

The choice of the optimum resistor value depends upon design goals for the application subject to conditions of closed loop gain, source impedance, and load. As a point of reference, typical curves are provided in the data sheet that show how the frequency response is affected by closed loop gain, feedback resistor value, and load resistance. Source impedance, if it is large, becomes a factor only in conjunction with capacitance at the inputs. The data sheet curves are all generated with a 50Ω source impedance.

To illustrate how one might approach the problem of selecting a feedback resistor based on closed loop gain, consider the simple model of Figure 1. Between the inputs is a unity gain voltage buffer with non-zero output impedance indicated by R_I . The transimpedance gain, R_Z , is a function of frequency having a high DC value that forces I_E to zero. The model's behavior is influenced by external elements consisting of a feedback network (R_F and R_G), source and load impedances (R_S and R_L), and stray capacitance at the amplifier's inputs (C_S).

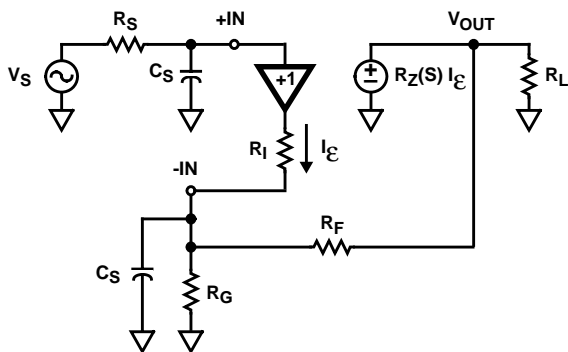


FIGURE 1. SIMPLE CURRENT FEEDBACK AMPLIFIER MODEL
Derivation of the transfer function will confirm that the non-zero inverting input impedance, R_I , causes the circuit's bandwidth to degrade as the closed loop gain increases, while stray capacitance at the negative input gives rise to

gain peaking particularly at low gains (intuitively, C_S is in parallel with R_G causing the gain as determined by the feedback network to increase with frequency).

Gain peaking due to capacitance at the inverting input is most easily dealt with by placing a resistor in series with the positive input. If we assume that the stray capacitance at the positive input equals the stray at the negative input, we can choose R_S equal to the parallel combination of R_F and R_G . This introduces a pole at the positive input which cancels the zero at the negative input, thereby eliminating the gain peak. Note that any remaining gain peaking is a result of excessive phase shift around the loop. Excess phase shift around the loop can be reduced by increasing R_F .

Bandwidth degradation due to non-zero inverting input resistance is also easy to deal with as long as the product of the closed loop gain and the inverting input resistance does not exceed the optimum value for R_F in unity gain. By solving the transfer function for constant bandwidth, we arrive at the following equations for R_F and R_G :

$$R_F = R_{FO} - A_{CL} * R_I \tag{EQ. 1}$$

$$R_I = R_F / (A_{CL} - 1) \tag{EQ. 2}$$

Where,

R_{FO} is the optimum value for unity gain (1000Ω),

R_I is the inverting input impedance (75Ω), and

A_{CL} is the desired closed loop gain.

A comparison between actual measured results in Figures 2 and 3 provides graphic reinforcement for the utility of these equations. Figure 2 illustrates the failure to consider stray input capacitance and inverting input resistance, while Figure 3 incorporates the lessons learned from analyzing our simple model.

In Figure 2, a family of closed loop gain curves was obtained on a representative unit using $R_S = 50\Omega$ and constant R_F ($R_F = R_{FO} = 1000\Omega$). The measured stray capacitance at either input was $2pF$. The results in Figure 3 were obtained from the same unit, except that (within the constraints of available standard resistor values) R_F and R_G were chosen according to the equations above and R_S was chosen to be equal to the parallel combination of R_F and R_G .

One limitation of the above model is that it does not include the effects of the load. In general if R_L is 400Ω or above, the response is independent of the load. If R_L is less than 400Ω , the response becomes more damped and the bandwidth degrades. Here again the bandwidth degradation can be compensated for by lowering the value of R_F .

 


FIGURE 2. FREQUENCY RESPONSE vs CLOSED LOOP GAIN USING FIXED $R_F = 1k\Omega$, $R_S = 50\Omega$, $R_L = 402\Omega$

TABLE 1. RESISTOR VALUES FOR FIGURE 2

A_V	R_F (Ω)	R_G (Ω)	R_S (Ω)	BW (MHz)	PEAKING (dB)
+1	1K	-	50	97	1
+2	1K	1K	50	84	<0
+6	1K	200	50	22	<0
+10	1K	110	50	16	<0

 


FIGURE 3. FREQUENCY RESPONSE vs CLOSED LOOP GAIN $R_F = 1000-A_V(75\Omega)$, $R_S = R_F \parallel R_G$, $R_L = 402\Omega$

TABLE 2. RESISTOR VALUES FOR FIGURE 3

A_V	R_F (Ω)	R_G (Ω)	R_S (Ω)	BW (MHz)	PEAKING (dB)
+1	909	-	909	87	2
+2	825	825	422	87	2
+6	562	110	90.9	74	0.5
+10	237	26.1	23.7	62	0.5

NOTE: $R_F = 1000-A_V(75\Omega)$, $R_S = R_F \parallel R_G$, $R_L = 402\Omega$

All Intersil semiconductor products are manufactured, assembled and tested under **ISO9000** quality systems certification.

Intersil semiconductor products are sold by description only. Intersil Corporation reserves the right to make changes in circuit design and/or specifications at any time without notice. Accordingly, the reader is cautioned to verify that data sheets are current before placing orders. Information furnished by Intersil is believed to be accurate and reliable. However, no responsibility is assumed by Intersil or its subsidiaries for its use; nor for any infringements of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of Intersil or its subsidiaries.

For information regarding Intersil Corporation and its products, see web site www.intersil.com

Sales Office Headquarters

NORTH AMERICA

Intersil Corporation
P. O. Box 883, Mail Stop 53-204
Melbourne, FL 32902
TEL: (321) 724-7000
FAX: (321) 724-7240

EUROPE

Intersil SA
Mercure Center
100, Rue de la Fusee
1130 Brussels, Belgium
TEL: (32) 2.724.2111
FAX: (32) 2.724.22.05

ASIA

Intersil (Taiwan) Ltd.
7F-6, No. 101 Fu Hsing North Road
Taipei, Taiwan
Republic of China
TEL: (886) 2 2716 9310
FAX: (886) 2 2715 3029