intersi

# Micropower Clock Oscillator Provides Control for Battery Operated Circuits (HA7210, ICL7642)

Application Note

November 1996

AN9317.1

The HA7210 low power oscillator is ideal for battery powered circuits that require a precision clock. It operates well from a single 3V to 5V supply, uses extremely low current, and produces a clock output that is very stable over temperature and supply voltage. In addition, it requires only an external crystal and can operate from under 32kHz to over 10MHz.

This application note shows how the HA7210 can be used with a quad CMOS op amp to make a control circuit that will automatically switch a battery-powered digital system into micropower "sleep mode" when not in use and trigger the system on again when an external event (sound, pressure, etc.) is detected. This function is extremely useful for applications like remote metering, where a battery-powered system may need to record occasional events yet remain in a power down state most of the time.

This control circuit can be configured to turn on with an AC or DC coupled event sensor and turn off using either a preset time delay or an external digital system command. When triggered into the power-up mode, it supplies a precision system clock, a buffered analog ground reference and a scaling signal amplifier for an A/D converter. In the power-down mode, it draws less than  $50\mu$ A of standby current.

# **Circuit Operation**

As shown in Figure 1, the control circuit operates from a single 3V to 5V battery and uses only a quad CMOS op amp (ICL7642) and a HA7210 low power oscillator chip. Two Power-Down Reset options are available: one for a preset time delay after turn-on, and another for external digital command as explained in the following text.

 ${\sf R}_1$  and  ${\sf R}_2$  create an analog signal ground reference voltage,  ${\sf V}_{\sf REF}$ , at 1/2 of the battery voltage.  ${\sf C}_2$  is used to filter noise from this high impedance point. The analog reference voltage is then buffered by IC1A and output to the other three amplifiers.

Amplifier B is used as a high-pass filter and amplifier such that a fast edge (like a sudden noise into a microphone) will produce a large positive swing at the output. Diode  $D_1$  prevents the output from moving very much below the analog reference voltage.  $C_1$  can be determined experimentally depending on the application, sensor type, and sensitivity required.

Amplifier C is used as a comparator and latch. The inverting terminal is nominally at the analog reference,  $V_{REF}$ , but the non-inverting terminal is lower than  $V_{REF}$  due to the hysteresis of R<sub>5</sub>. In the absence of a microphone/sensor signal, the output of amplifier B is also at  $V_{REF}$ , so that  $V_{REF}(R_5/(R_4 + R_5))$  appears at the non-inverting input of amplifier C.


When the output of amplifier B produces a voltage at the non-inverting terminal of amplifier C higher than  $V_{REF}$ , the output of C latches into the high state. This state cannot be changed by any condition at the input of IC1B due to the hysteresis provided by  $R_5$ . Because the output stage of amplifier C is CMOS, it can drive a light load nearly to the positive supply rail.

Voltage from the output of amplifier C is provided to the supply and ENable pins of the HA7210 low power oscillator. When this happens, the oscillator turns on and provides a clock output to the rest of the system.  $C_3$  is used as a bypass capacitor for the supply pin. If faster oscillator turn-on is required, the HA7210 supply pin (pin 1) may be tied directly to the battery and the output of amplifier C used to enable the HA7210. In this case, the oscillator will draw some quiescent current when not in use, but significantly lower than when enabled. Capacitance at the output of the HA7210 should be minimized to keep the active supply current as low as possible.

As shown, amplifier D can be used as a scaling amplifier for a system A/D converter.  $R_7$  and  $R_8$  are used to scale the gain of the amplifier (G = 1 +  $R_8/R_7$ ). The input of the amplifier is extremely high impedance, so that any type of high impedance sensor may be used.
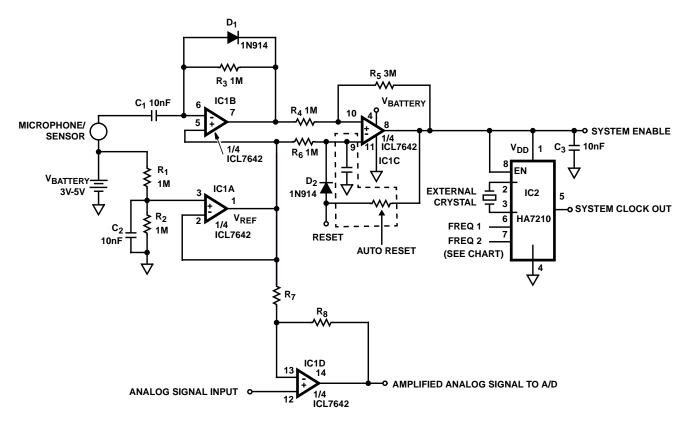
### Resetting the System

To put the system back into "sleep mode", two options are available. The digital system can send a logic high state to the Reset input, forcing the IC1C comparator/latch to reset to the low state. Alternatively, if desired, an auto-reset RC timer (shown in the dotted lines) will cause the circuit to automatically reset after a preset time interval. This time is determined by the time it takes for the capacitor at the inverting terminal to charge higher than the voltage at the noninverting terminal of IC1C.



NOTE: Provides Sleep Mode, Power-up Trigger, Optional Auto-reset, Scaling Amp for A/D, Precision System Clock Oscillator, and Analog Ground Reference

#### FIGURE 1. 2-CHIP MICROPOWER CONTROL CIRCUIT OPERATES FROM 3V BATTERY

ENABLE	FREQ 1	FREQ 2	OUTPUT RANGE
1	1	1	10kHz to 100kHz
1	1	0	100kHz to 1MHz
1	0	1	1MHz to 5MHz
1	0	0	5MHz to 10MHz+
0	Х	Х	High Impedance

TABLE 1. HA7210 OSCILLATOR CONTROL INPUTS

All Intersil semiconductor products are manufactured, assembled and tested under ISO9000 quality systems certification.

Intersil semiconductor products are sold by description only. Intersil Corporation reserves the right to make changes in circuit design and/or specifications at any time without notice. Accordingly, the reader is cautioned to verify that data sheets are current before placing orders. Information furnished by Intersil is believed to be accurate and reliable. However, no responsibility is assumed by Intersil or its subsidiaries for its use; nor for any infringements of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of Intersil or its subsidiaries.

For information regarding Intersil Corporation and its products, see web site www.intersil.com

# Sales Office Headquarters

NORTH AMERICA Intersil Corporation P. O. Box 883, Mail Stop 53-204 Melbourne, FL 32902 TEL: (321) 724-7000 FAX: (321) 724-7240 EUROPE Intersil SA Mercure Center 100, Rue de la Fusee 1130 Brussels, Belgium TEL: (32) 2.724.2111 FAX: (32) 2.724.22.05 ASIA Intersil (Taiwan) Ltd. 7F-6, No. 101 Fu Hsing North Road Taipei, Taiwan Republic of China TEL: (886) 2 2716 9310 FAX: (886) 2 2715 3029

2