



# DESIGN NOTES

## Ultralow Quiescent Current DC/DC Converters for Light Load Applications – Design Note 142

Sam Nork

In lightly loaded battery applications that require regulated power supplies, the quiescent current drawn by the DC/DC converter can represent a substantial portion of the average battery current drain. In such applications, minimizing the quiescent current of the DC/DC converter becomes a primary objective because this results in longer battery life and/or an increased power budget for the rest of the circuitry. The following two circuits provide regulated step-up and step-down DC/DC conversion and consume extremely low quiescent current.

### 2-Cell to 5V Conversion with $I_Q = 12\mu\text{A}$

The circuit in Figure 1 produces a regulated 5V output from a 2V to 5V input and consumes only  $12\mu\text{A}$  (typical) of supply current. The LTC<sup>®</sup>1516 is a charge pump DC/DC converter that uses Burst Mode<sup>™</sup> operation to provide a regulated 5V output.

This circuit achieves ultralow quiescent current by disabling the internal charge pump when the output is in regulation. The charge pump is enabled only when the output load forces the voltage on  $C_{OUT}$  to droop by approximately 80mV. External capacitors C1 and C2 are then used to transfer charge from  $V_{IN}$  to  $V_{OUT}$  until the output climbs back into regulation. This regulation method results in approximately 100mV of voltage ripple at the output.

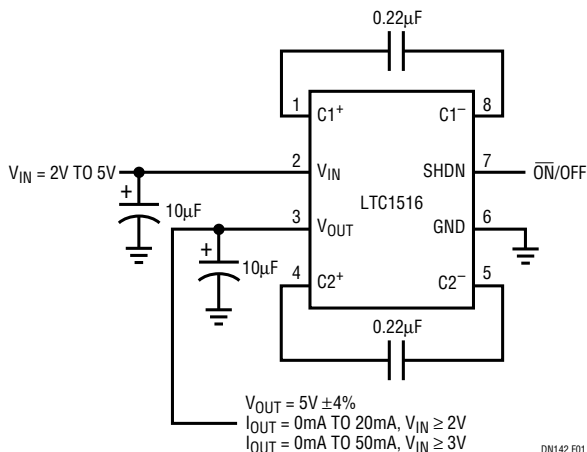


Figure 1. Regulated 5V Output from a 2V to 5V Input

The circuit is capable of providing up to 50mA of output current (for  $V_{IN} \geq 3\text{V}$ ). As shown in Figure 2, typical efficiency exceeds 70% with load currents as low as  $50\mu\text{A}$ .

The low quiescent current of the LTC1516 may render shutdown of the 5V supply unnecessary because the  $12\mu\text{A}$  quiescent current is lower than the self-discharge rate of many batteries. However, the part is also equipped with a  $1\mu\text{A}$  shutdown mode for additional power savings.

### Ultralow Quiescent Current ( $I_Q < 5\mu\text{A}$ ) Regulated Supply

The LTC1516 contains an internal resistor divider that draws only  $1.5\mu\text{A}$  (typ) from  $V_{OUT}$ . During no-load conditions, the internal load causes a droop rate of only 150mV per second on  $V_{OUT}$  with  $C_{OUT} = 10\mu\text{F}$ . Applying a 5Hz to

LTC and LT are registered trademarks of Linear Technology Corporation. Burst Mode is a trademark of Linear Technology Corporation.

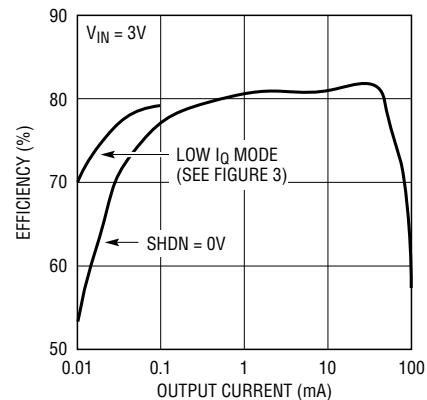


Figure 2. Efficiency vs Output Current

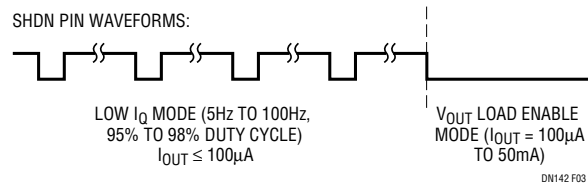


Figure 3. SHDN Pin Waveforms for Ultralow Quiescent Current Supply

100Hz, 95% to 98% duty cycle signal to the SHDN pin ensures that the circuit of Figure 1 comes out of shutdown frequently enough to maintain regulation during no-load or low-load conditions. Since the part spends nearly all of its time in shutdown, the no-load quiescent current (see Figure 4) is approximately equal to  $(V_{OUT})(1.5\mu A)/(V_{IN})(\text{Efficiency})$ .

The LTC1516 must be out of shutdown for a minimum duration of 200 $\mu$ s to allow enough time to sense the output and keep it in regulation. As the  $V_{OUT}$  load current increases, the frequency with which the part is taken out of shutdown must also be increased to prevent  $V_{OUT}$  from drooping below 4.8V during the OFF phase. A 100Hz 98% duty cycle signal on the SHDN pin ensures proper regulation with load currents as high as 100 $\mu$ A. When load current greater than 100 $\mu$ A is needed, the SHDN pin must be forced low, as in normal operation. The typical no-load supply current for this circuit with  $V_{IN} = 3V$  is only 3.2 $\mu$ A.

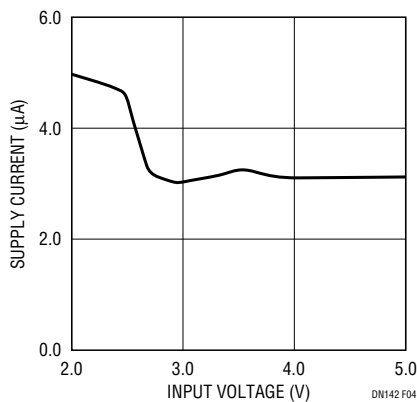


Figure 4. No-Load  $I_{CC}$  vs Input Voltage for Low  $I_q$  Mode

### Micropower LDO Regulator Consumes <5 $\mu$ A

The micropower linear regulator shown in Figure 5 delivers a regulated 3.3V output using less than 5 $\mu$ A quiescent current. With such low operating current, a standard 9V alkaline battery can power this regulator for 10 years.

Circuit operation is very straightforward. The LTC1440's internal reference connects to one input of the feedback comparator. A feedback voltage divider formed by R2 and R3 establishes the output voltage. The output of the comparator enables the current source formed by Q1, Q2, R1 and R4. When LTC1440's output is low, Q1 is turned on, allowing current to charge output capacitor C4. Local feedback formed by R4, Q1 and Q2 creates a constant current source from  $V_{IN}$  to C4. Peak charging current is set by R4 and the  $V_{BE}$  of Q2, which also provides current limiting in case of an output short to ground. With the values shown in Figure 5, the regulator is guaranteed to

deliver at least 10mA output current with inputs as low as 4.8V (that is, from a fully discharged 9V battery).

Because the regulator implements a hysteretic feedback loop in place of the traditional linear feedback loop, no compensation is needed for loop stability. Furthermore, the extremely high gain of the comparator provides excellent load regulation and transient response. However, as with the LTC1516, the comparator hysteresis necessarily produces a small amount of output ripple. Output ripple can be reduced to 10mV–20mV peak-to-peak with feedforward capacitor C3 (see Figure 6), but no-load quiescent current increases by approximately 1.5 $\mu$ A. Without C3 the quiescent current is about 4.5 $\mu$ A, but output ripple is 50mV to 100mV peak-to-peak.

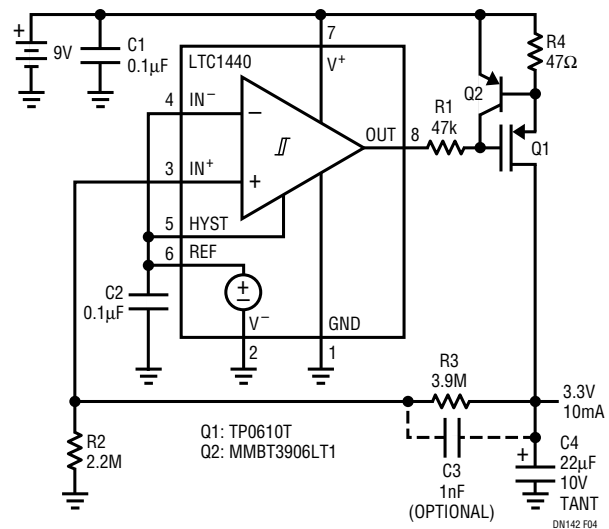


Figure 5. Micropower LDO Regulator

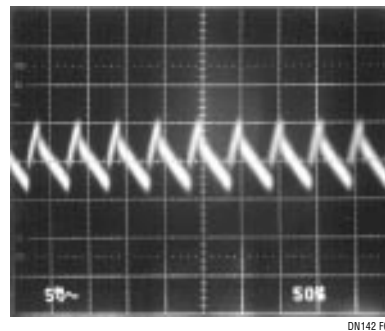


Figure 6. Typical Output Ripple Using 1nF Feedforward Capacitor

For literature on our DC/DC Converters, call **1-800-4-LINEAR**. For applications help, call (408) 432-1900, Ext. 2361