

comprised of T1, C4 and Q1. The Royer converter produces a 90% efficient, zero DC component, 60kHz sinusoidal waveform based on the average current in L1. Sinusoidal currents from both CCFLs are returned to the LT1768 through the DIO1/DIO2 pins. A fraction of the CCFL current pulls against the V_C pin closing the loop. A single capacitor on the V_C pin provides loop compensation and CCFL current averaging, which results in constant CCFL current regardless of line and load conditions. Varying the value of the V_C current source via the Multimode Dimming block varies the CCFL current and resultant light intensity.

Multimode Dimming

Previous solutions used intensity control schemes that were limited to either linear or PWM control. Linear control schemes provide the highest efficiency circuits but either limit dimming range or violate lamp specifications to achieve wide dimming ratios. PWM control schemes offer wide dimming range but produce high crest-factor waveforms detrimental to CCFL life and waste power at higher currents. The LT1768's patented Multimode Dimming combines the best of both control schemes to extend CCFL life while providing the widest possible dimming range.

The circuit in Figure 1 accepts either a 0V to 5V DC voltage, or a 0V to 5V, 1kHz PWM waveform and converts to a DC voltage. The filtered input voltage is sent to the LT1768 PROG pin, which controls lamp intensity by placing the LT1768 into one of five distinct modes of operation. Referring to Figure 2, which mode is in use is determined by the voltages on the PROG and PWM pins and by the currents that flow out of the R_{MAX} and R_{MIN} pins.

Off mode ($V_{PROG} < 0.5V$) sets the CCFL current to zero.

Minimum current mode ($0.5V < V_{PROG} < 1.0V$) sets the CCFL current to a precise minimum level set by the R_{MIN} resistor. This mode determines the minimum lamp current and intensity.

Maximum current mode ($V_{PROG} > 4V$) sets the CCFL current to a precise maximum level set by the R_{MAX} resistor. Setting the CCFL current in this mode to the manufacturers maximum rating achieves maximum intensity and ensures no degradation in the lamp lifetime.

In linear mode ($V_{PWM} < V_{PROG} < 4V$), CCFL current is controlled linearly with the voltage on the PROG pin.

Data Sheet Download

<http://www.linear-tech.com/go/dnLT1768>

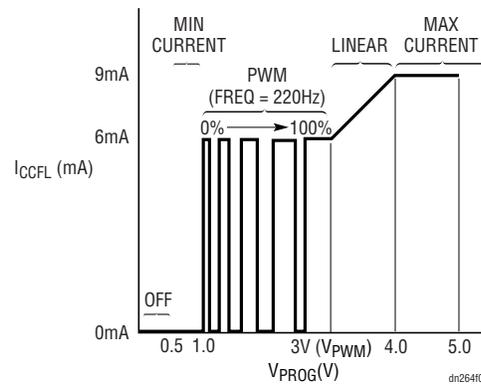


Figure 2. Lamp Current vs PROG Voltage

Linear mode provides the best current-to-light conversion and highest efficiency.

In PWM mode ($1V < V_{PROG} < V_{PWM}$), the CCFL current is modulated between the minimum CCFL current and the value for CCFL current in linear mode with $V_{PROG} = V_{PWM}$. The PWM frequency is set by a single capacitor on the C_T pin. The PWM duty cycle is set by the voltage on the PROG pin with 1V equal to 0%, and 100% (linear mode) equal to V_{PWM} . The LT1768's PWM mode enables wide dimming ratios while reducing the high crest factor found in PWM-only dimming solutions.

When combined, these five modes of operation allow the creation of a DC-controlled CCFL current profile that can be tailored to enable the widest possible dimming ratio while maximizing CCFL lifetime.

LT1768 Fault Modes

The LT1768 also has fault detection to ensure that lamp current and Royer transformer ratings are not exceeded under fault conditions. If one CCFL lamp is open, the LT1768 activates a fault flag and adjusts the current in the remaining so that it never exceeds the maximum current set by the R_{MAX} resistor. If both lamps are open circuit, the LT1768 shuts down the Royer section to avoid any hazardous high voltage conditions.

Additional Features

The LT1768 also provides a temperature-compensated 5V reference, an undervoltage lockout feature, thermal shutdown and a logic-compatible shutdown pin that reduces supply current when activated. The LT1768 is available in a 16-pin SSOP package.

For literature on our CCFL Controllers, call **1-800-4-LINEAR**. For applications help, call (408) 432-1900, Ext. 2593