

DESIGN NOTES

100MHz Op Amp Features Low Noise Rail-to-Rail Performance While Consuming Only 2.5mA – Design Note 308

Glen Brisebois

The new LT[®]6202 op amp combines 100MHz gain-bandwidth, 1.9nV/ $\sqrt{\text{Hz}}$ voltage noise and rail-to-rail inputs and outputs, while consuming only 2.5mA. It also features a low 0.75pA/ $\sqrt{\text{Hz}}$ current noise, and it contributes exceptionally low total noise and distortion power in small-signal applications. The device is fully specified on 3V, 5V and $\pm 5\text{V}$ supplies and is available in commercial and industrial temperature grades in both the SOT and SO packages. Dual and quad versions are also available as the LT6203 and LT6204, respectively.

Low Power, 2.4nV/ $\sqrt{\text{Hz}}$, Photodiode AC Transimpedance Amplifier Outperforms Monolithic Solutions

You can't optimize for everything. Op amp designs that try to squeeze good JFETs into their high speed monolithic processes inevitably compromise other parameters, usually resulting in high supply currents. Figure 1 shows a simple way to get the best of both worlds using the LT6202 and a low noise discrete JFET. The JFET acts as a source follower, buffering the inverting input of the LT6202 and making it suitable for the high impedance feedback elements R1 and R2. The LT6202 forces the JFET source to 0V, with R3 ensuring that the JFET runs an I_{DRAIN} of 1mA. Because the JFET is run well below its minimum

I_{DSS} and has a narrow range of pinchoff voltages, the circuit is guaranteed to self bias just below ground, typically at about -0.5V . Without a photocurrent signal in the photodiode, the LT6202 output sits at the same voltage and tracks it. When the photodiode is illuminated, the current must come from the LT6202 output through R1 and R2 so the output goes up as it would with a normal transimpedance amplifier.

Amplifier input noise density and gain-bandwidth product were measured to be 2.4nV/ $\sqrt{\text{Hz}}$ and 100MHz, respectively, with only 3.8mA supply current. This is unparalleled in the monolithic world where 5 to 6 times the supply current would be expected for similar performance. The 100MHz gain-bandwidth product of the LT6202 is maintained in this circuit because the JFET has a high g_m , approximately $1/80\Omega$, which looks into 4.99k Ω so its loop attenuation is less than 2%. Total circuit input capacitance including board parasitics is measured at 3.5pF. This is less than the specified C_{GS} of the JFET because the JFET source is not grounded but rather looks into R3 and the high impedance op amp input. This fact combined with the low input voltage noise makes the circuit well suited to both large and small photodetectors. Using a small photodiode with 2.5pF junction capacitance and adjusting parasitic feedback capacitance for 4% overshoot in the transient response, closed loop bandwidth is 1.6MHz.

Figure 2 shows the LT6202 applied in a manner very similar to that shown in Figure 1. In this case however, the JFET is not allowed to dictate the DC bias conditions. Instead of simply grounding the LT6202 noninverting input, an LTC2050 drives it (and therefore the source) exactly to where it needs to be for zero JFET gate voltage. The addition of the LTC2050 increases the total supply current by about 1mA. AC performance is nearly identical to the uncorrected circuit of Figure 1, with the additional benefit of excellent DC performance. Output offset is 200 μV and output noise is 2mV_{p-p} measured in a 20MHz bandwidth.

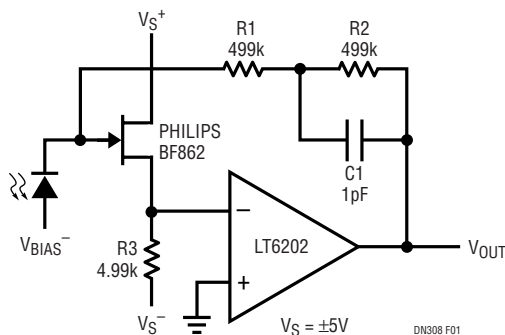


Figure 1. Low Noise, Low Power Photodiode Amplifier is Better than Monolithics. Low Bias Current, Low Current Noise and Unity Gain Stability Keep the Circuit Operational from 0 Ω to several G Ω

LTC and LT are registered trademarks of Linear Technology Corporation.

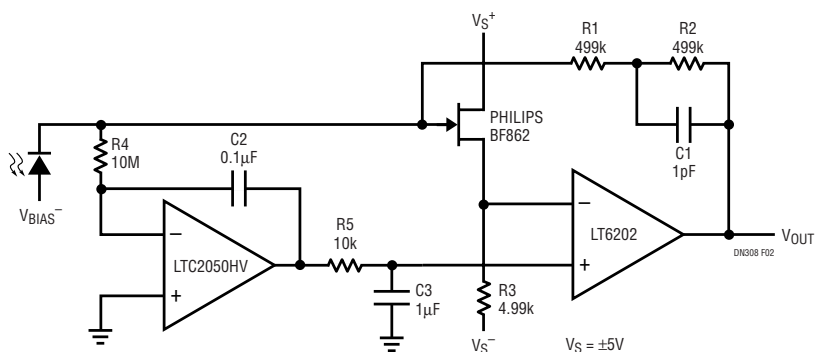


Figure 2. Modified Circuit Provides Similar Noise and AC Performance, with DC Precision Restored by the LTC2050

Single Supply 16-Bit ADC Driver

Figure 3 shows the LT6203 driving an LTC1864 unipolar 16-bit, 250ksps A/D converter. The bottom half of the LT6203 is in a gain of 1 and buffers the 0V negative full-scale signal V_{LOW} into the negative input of the LTC1864. The upper half of the LT6203 is in a gain of 10, referenced to the buffered voltage V_{LOW} and drives the positive input of the LTC1864. The input range of the LTC1864 is 0V to 5V so for best results the input range of V_{IN} is from V_{LOW} , about 0.4V to about 0.82V. Figure 4 shows an FFT obtained with a 10.1318kHz (coherent) input waveform, with no windowing or averaging. Spurious free dynamic range is seen to be 100dB.

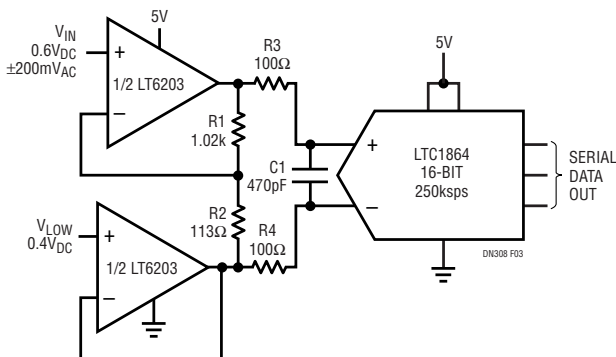


Figure 3. Single Supply 16-Bit ADC Driver

Although the LTC1864 has a sample rate far below the gain bandwidth of the LT6203, using this amplifier is not necessarily a case of overkill. A/D converters have sample apertures that are extremely narrow (infinitesimal as far as mathematicians are concerned) and make demands on upstream circuitry far in excess of what the innocent looking sample rate would imply. In addition, when an A/D converter takes a sample, it applies a small capacitor to its inputs causing a fair amount of glitch energy and expects the voltage on the capacitor to settle to the true value very quickly. Finally, the LTC1864 has a 20MHz analog input bandwidth and can be used in undersampling applications, again requiring a source bandwidth and settling speed higher than the Nyquist criterion would imply.

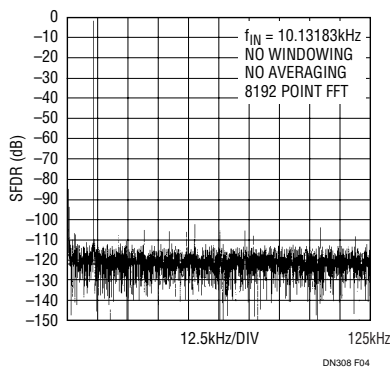


Figure 4. FFT of 10kHz Sine Wave Showing 100dB SFDR

Conclusion

The LT6202, LT6203 and LT6204 are fast, low noise amplifiers which have been optimized for low power consumption. Their rail-to-rail inputs and outputs provide flexibility and ease of use and maximize dynamic range.

Data Sheet Download

<http://www.linear.com/go/dnLT6202>

For literature on our Op Amps, call **1-800-4-LINEAR**. For applications help, call (408) 432-1900, Ext. 2759