

# **PAL PROGRAMMABLE ARRAY LOGIC Handbook**




**Monolithic  
Memories**  
Bipolar is our business.

**\$5.00**



# PAL PROGRAMMABLE ARRAY LOGIC Handbook

Patent Allowed

 

First Edition


<b>Introduction</b>	<b>1</b>
<b>Reliability</b>	<b>2</b>
<b>PAL Family Data Sheet</b>	<b>3</b>
<b>Design Concept</b>	<b>4</b>
<b>Applications</b>	<b>5</b>
<b>Representatives/Distributors</b>	<b>6</b>

*author John Birkner*

*contributors, { Bill Black  
Paul Franklin  
Shlomo Waser*



 **Monolithic Memories**  
Bipolar is our business.



## The PAL Concept

*Monolithic Memories' family of PAL devices gives designers a powerful tool with unique capabilities for use in new and existing logic designs. The PAL saves time and money by solving many of the system partitioning and interface problems brought about by increases in semiconductor device technology.*

*Rapid advances in large scale integration technology have led to larger and larger standard logic functions; single I.C.s now perform functions that formerly required complete circuit cards. While LSI offers many advantages, advances have been made at the expense of device flexibility. Most LSI devices still require large numbers of SSI/MSI devices for interfacing with user systems. Designers are still forced to turn to random logic for many applications.*

*The "complexity gap" between TTL and LSI devices has led to ineffective use of both. The TTL provides the speed and flexibility, but it is ineffective in terms of package count, power consumption, and P.C. board space. LSI offers high functional density and low power consumption, but it is slow and rigidly partitioned. Even the microprocessor, widely acclaimed for its flexibility, is slow and expensive when the costs of programming and support interfaces are considered.*

*The designer is confronted with another problem when a low to medium complexity product is designed. Often the*

*function is well defined and could derive significant benefits from fabrication as an integrated circuit. However, the design cycle for a custom circuit is long and the costs can be very high. This makes the risk significant enough to deter most users. The technology to support maximum flexibility combined with fast turn around on custom logic has simply not been available.*

*Attempts to solve these problems have led to increasing interest in fuse programmable logic devices. These devices can all be user configured to provide custom functions. PROMs, FPLAs, FPGAs, and PMUXs have all been used in this way. These approaches have met with some success, but all are deficient in one or more areas. PROMs require careful design to avoid undesirable data transitions; FPLAs are expensive, difficult to program and complex to understand; FPGAs and PMUXs are not widely available and lack flexibility. All of these devices still require extensive interface logic for use in systems.*

*The PAL family offers a fresh approach to using fuse programmable logic. PALs are a conceptually unified group of devices which combine programmable flexibility with high speed and an extensive selection of interface options. PALs can lower inventory, cut design cycles and provide high complexity with maximum flexibility. These features, combined with lower package count and high reliability, truly make the PAL a circuit designer's best friend.*



## The PAL—Teaching Old PROMs New Tricks



MMI developed the modern PROM and introduced many of the architectures and techniques now regarded as industry standards. As the world's largest PROM manufacturer, MMI has the proven technology and high volume production capability required to manufacture and support the PAL.

The PAL is an extension of the fusible link technology pioneered by Monolithic Memories for use in bi-polar PROMs. The fusible link PROM first gave the digital systems designer the power to "write on silicon." In a few seconds he was able to transform a blank PROM from a general purpose device into one containing a custom algorithm, microprogram, or Boolean transfer function. This opened up new horizons for the use of PROMs in computer control stores, character generators, data storage tables and many other applications. The wide acceptance of this technology is clearly demonstrated by today's multi-million dollar PROM market.

The key to the PROM's success is that it allows the designer to quickly and easily customize the chip to fit his unique requirements. The PAL extends this programmable flexibility by utilizing proven fusible link technology to implement logic functions. Using PALs the designer can quickly and effectively implement custom logic varying in complexity from random gates to complex arithmetic functions.

### ANDs and ORs

The PAL implements the familiar sum of products logic by using a programmable AND array whose output terms feed a fixed OR

array. Since the sum of products form can express any Boolean transfer function, the PAL's uses are only limited by the number of terms available in the AND - OR arrays. PAL's come in different sizes to allow for effective logic optimization.

Figure 1 shows the basic PAL structure for a two input, one output logic segment. The general logic equation for this segment is

$$\text{Output} = (I_1f_1 + \bar{f}_1)(\bar{I}_1f_2 + \bar{f}_2)(I_2f_3 + \bar{f}_3)(\bar{I}_2f_4 + \bar{f}_4) + (I_1f_5 + \bar{f}_5)(\bar{I}_1f_6 + \bar{f}_6)(I_2f_7 + \bar{f}_7)(\bar{I}_2f_8 + \bar{f}_8)$$

where the "f" terms represent the state of the fusible links in the PAL's AND array. An unblown link represents a logic 1. Thus,

fuse blown,  $f = 0$

fuse intact,  $f = 1$

An unprogrammed PAL has all fuses intact.

 


Figure 1

### New Device, New Notation

Logic equations, while convenient for small functions, rapidly become cumbersome in large systems. To reduce possible confusion, complex logic networks are generally defined by logic diagrams and truth tables. Figure 2 shows the logic convention adopted to keep PAL logic easy to understand and use. In the figure, an "x" represents an intact fuse used to perform the logic AND function. (Note: the input terms on the common line with the x's are not connected together.) The logic symbology shown in Figure 2 has been informally adopted by integrated circuit manufacturers because it clearly establishes a one-to-one correspondence between the chip layout and the logic diagram. It also allows the logic diagram and truth table to be combined into a compact and easy to read form, thereby serving as a convenient shorthand for PALs. The two input - one output example from Figure 1 redrawn using the new logic convention is shown in Figure 3.

 


Figure 2

 


Figure 3

As a simple PAL example, consider the implementation of the transfer function:

$$\text{Output} = I_1 \bar{I}_2 + \bar{I}_1 I_2$$

The normal combinatorial logic diagram for this function is shown in figure 4, with the PAL logic equivalent shown in figure 5.

 


Figure 4

 


Figure 5

Using this logic convention it is now possible to compare the PAL structure to the structure of the more familiar PROM and PLA. The basic logic structure of a PROM consists of a fixed AND array whose outputs feed a programmable OR array (figure 6). PROMs are low-cost, easy to program, and available in a variety of sizes and organizations. They are most commonly

used to store computer programs and data. In these applications the fixed input is a computer memory address; the output is the contents of that memory location.

 


Figure 6

The basic logic structure of the PLA consists of a programmable AND array whose outputs feed a programmable OR array (Figure 7). Since the designer has complete control over all inputs and outputs, the PLA provides the ultimate flexibility for implementing logic functions. They are used in a wide variety of applications. However, this generality makes PLA's expensive, quite formidable to understand, and are costly to program (they require special programmers).

The basic logic structure of the PAL, as mentioned earlier, consists of a programmable AND array whose outputs feed a fixed OR array (Figure 8). The PAL combines much of the flexibility of the PLA with the low cost and easy programmability of the PROM. Table 1 summarizes the characteristics of the PROM, PLA, and PAL logic families.

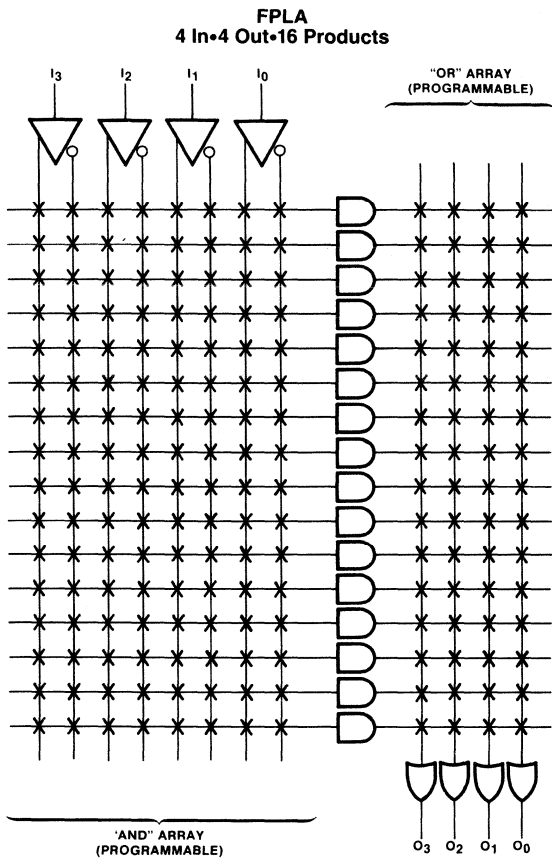


Figure 7

 


Figure 8

1

	AND	OR	OUTPUT OPTIONS
PROM	Fixed	Prog	TS, OC
FPLA	Prog	Prog	TS, OC, Fusible Polarity
FPGA	Prog	None	TS, OC, Fusible Polarity
PMUX	Fix/Prog	Fixed	TS
PAL	Prog	Fixed	TS, Registered, Feedback, I/O

Table 1

### PALs For Every Task

The members of the PAL family and their characteristics are summarized in Table 2. They are designed to cover the spectrum of logic functions at reduced cost and lower package count. This allows the designer to select the PAL that best fits his application. PALs come in the following basic configurations:

### Gate Arrays

PAL gate arrays are available in sizes from 10 x 8 (10 input terms, 8 output terms) to 16 x 2, with both active high and active low output configurations available. This wide variety of input/output formats allows the PAL to replace many different sized blocks of combinatorial logic with single packages.

### Registered Outputs with Feedback

High end members of the PAL family feature registered data outputs with register feedback. Each product term is stored into a D-type output flip-flop on the rising edge of the system clock (Figure 9). The Q output of the flip-flop can then be gated to the output pin by enabling the active low three-state buffer.

In addition to being available for transmission, the Q output is fed back into the PAL array as an input term. This feedback

**PAL input/output/function chart**

PART NUMBER	INPUT	OUTPUT	PROGRAMMABLE I/O's	FEEDBACK register	OUTPUT polarity	FUNCTIONS	TPD ns, TYP	IOL mA	ICC mA, TYP
PAL10H8	10	8			AND-OR	AND-OR GATE ARRAY	25	8	55
PAL12H6	12	6			AND-OR	AND-OR GATE ARRAY	25	8	55
PAL14H4	14	4			AND-OR	AND-OR GATE ARRAY	25	8	55
PAL16H2	16	2			AND-OR	AND-OR GATE ARRAY	25	8	55
PAL10L8	10	8			AND-NOR	AND-OR INVERT GATE ARRAY	25	8	55
PAL12L6	12	6			AND-NOR	AND-OR INVERT GATE ARRAY	25	8	55
PAL14L4	14	4			AND-NOR	AND-OR INVERT GATE ARRAY	25	8	55
PAL16L2	16	2			AND-NOR	AND-OR INVERT GATE ARRAY	25	8	55
PAL16C1	16	2			BOTH <sup>1</sup>	AND-OR GATE ARRAY	25	8	55
PAL16L8	10	8	6		AND-NOR	AND-OR INVERT GATE ARRAY	25	24	140
PAL16R8	8	8		8	AND-NOR	AND-OR INVERT ARRAY W/REG'S	25	24	150
PAL16R6	8	8	2	6	AND-NOR	AND-OR INVERT ARRAY W/REG'S	25	24	150
PAL16R4	8	8	4	4	AND-NOR	AND-OR INVERT ARRAY W/REG'S	25	24	150
PAL16X4	8	8	4	4	AND-NOR	AND-OR-XOR INVERT W/REG'S	25	24	160
PAL16A4	8	8	4	4	AND-NOR	AND-CARRY-OR-XOR INVERT W/REG'S	25	24	160

<sup>1</sup>Simultaneous AND-OR and AND-NOR outputs

Table 2

 


Figure 9

allows the PAL to "remember" the previous state, and it can alter its function based upon that state. This allows the designer to configure the PAL as a state sequencer which can be programmed to execute such elementary functions as count up, count down, skip, shift, and branch. These functions can be executed by the registered PAL at rates of up to 20 MHz.

**Programmable I/O**

Another feature of the high-end members of the PAL family is

programmable input/output. This allows the product terms to directly control the outputs of the PAL (Figure 10). One product term is used to enable the three-state buffer, which in turn gates the summation term to the output pin. The output is also fed back into the PAL array as an input. Thus the PAL drives the I/O pin when the three-state gate is enabled; the I/O pin is an input to the PAL array when the three-state gate is disabled. This feature can be used to allocate available pins for I/O functions or to provide bi-directional output pins for operations such as shifting and rotating serial data.

 


Figure 10

## Arithmetic Functions

The arithmetic functions add, subtract, greater than, and less than are implemented by two additional features of the registered PAL (Figure 11). First, the sum of products is segmented into two sums exclusive OR ed (XOR) at the input of the D-type flip-flop. This allows carries from previous operations to be XOR ed with the two variable sums generated by the PAL array. Second, the flip-flop's Q output is combined with input terms to form  $I+Q$ ,  $I+\bar{Q}$ ,  $\bar{T}+Q$ , and  $\bar{T}+\bar{Q}$  terms which are then fed back into the PAL array as inputs. This option provides for

versatile operations on two variables and facilitates the parallel generation of carries necessary for fast arithmetic operations.

Figure 12 shows how the PAL array can be programmed to combine the available terms to form sixteen logical products in an ALU or controller application.

It should now be clear that the PAL family can replace most Small-Scale Integrated Logic (SSI) logic in use today, thereby lowering product cost and giving the designer even greater flexibility in implementing logic functions.

 


Figure 11

 


Figure 12

## PAL Technology

PALs are manufactured using the proven TTL Schottky bipolar process used to make fusible-link PROMs. An NPN emitter follower array forms the programmable AND array. PNP inputs provide high-impedance inputs (.25 mA max.) to the array. All outputs are standard TTL drivers with internal active pull-up transistors. Typical PAL propagation delay time is 25 ns, and all PALs are packaged in space saving 20-pin "skinny-dips".

## PAL Programming

PALs can be programmed in any standard PROM programmer with the addition of a PAL personality card. The PAL appears to the programmer as a 512 x 4 PROM. During programming four of the PAL outputs are selected for programming while the other four outputs and the eight inputs are used for addressing. The outputs are then switched to program the other locations. Verification uses the same procedure with the programming lines held in a low state.

## PAL Data Security

The circuitry used for programming and logic verification can be used at any time to determine the logic pattern stored in the PAL array. For security, the PAL has a "last fuse" which can be blown to disable the verification logic. This provides a significant deterrent to potential copiers, and it can be used to effectively protect proprietary designs.

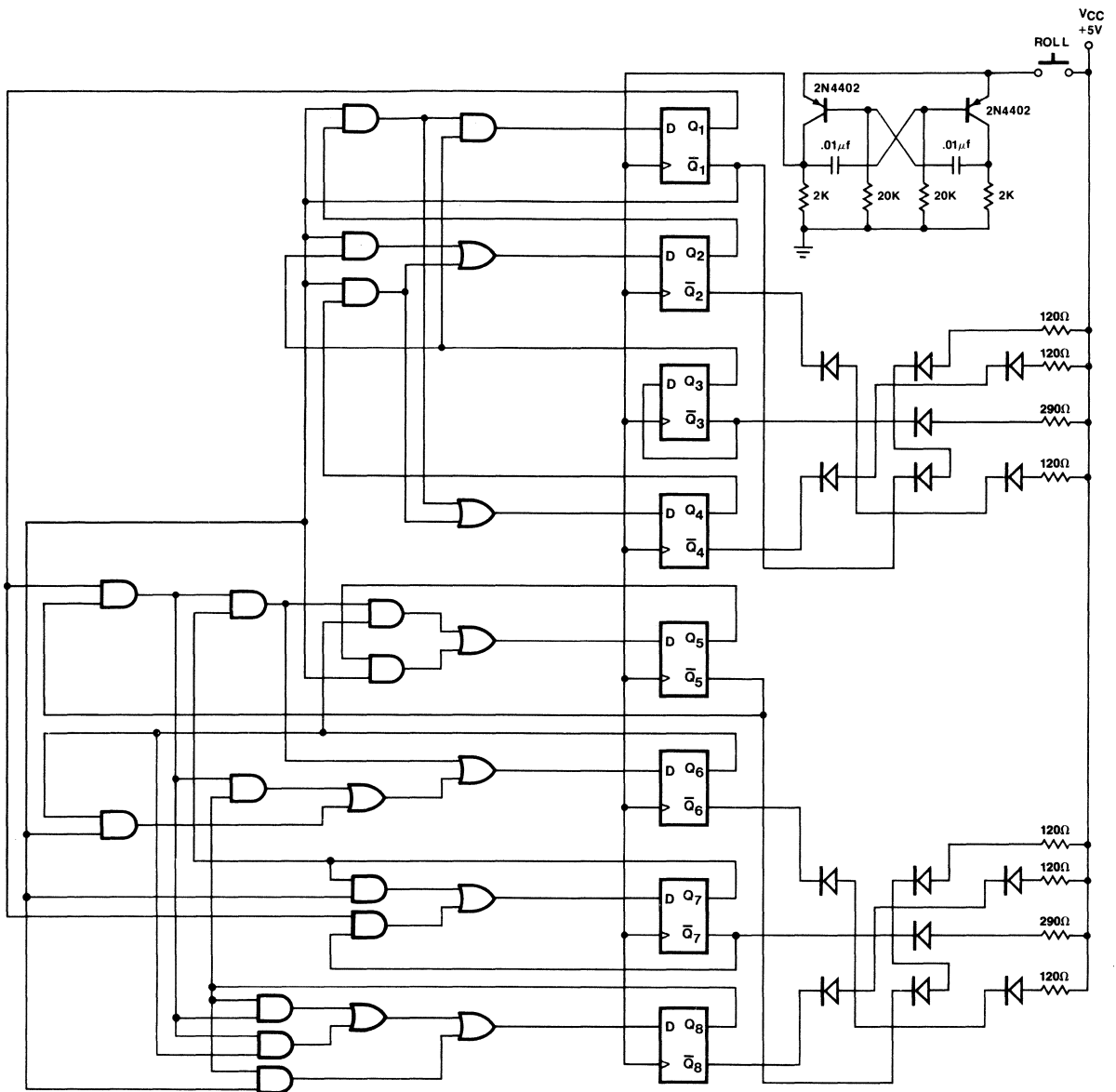


Figure 13

## PAL Part Numbers

The PAL part number is unique in that the part number code also defines the part's logic operation. The PAL parts code system is shown in Figure 14. For example, a PAL14L4CN would be a 14 input term, 4 output term, active-low PAL with a commercial temperature range packaged in a 20-pin plastic dip.

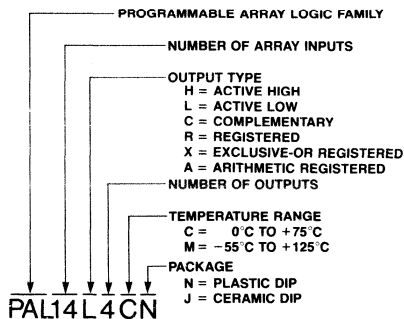


Figure 14

## PAL Logic Symbols

The logic symbols for each of the individual PAL devices gives a concise functional description of that PAL's logic function. This symbol makes a convenient reference when selecting the PAL that best fits a specific application. Figure 15 shows the logic symbol for a PAL10H8 gate array.

 


Figure 15

## A PAL Example

As an example of how the PAL enables the designer to reduce costs and simplify logic design, consider the design of a simple,

high-volume consumer product: an electronic dice game. This type of product will be produced in extremely high volume, so it is essential that every possible production cost be minimized.

The electronic dice game is simply constructed using a free running oscillator whose output is used to drive two asynchronous modulo six counters. When the user "rolls" the dice (presses a button), the current state of the counters is decoded and latched into a display resembling the pattern seen on an ordinary pair of dice.

A conventional logic diagram for the dice game is shown in Figure 13. (A detailed logic derivation is shown in the PAL applications section of this manual.) It is implemented using standard TTL, SSI and MSI parts, with a total I.C. count of eight: six quad gate packages and two quad D-latches. Looks like a nice, clean logic design, right? Wrong!!

## PAL Goes to the Casino

A brief examination of Figure 13 reveals two basic facts: first, the circuit contains mostly simple, combinatorial logic, and second, it uses a clocked state transition sequence. Remembering that the PAL family contains ample provision for these features, the PAL catalog is consulted. The PAL16R8 has all the required functions, and the entire logic content of the circuit can be programmed into a single PAL shown in Figure 16.

In this example, the PAL effected an eight to one package count reduction and a significant cost savings. This is typical of the power and cost-effective performance that the PAL family brings to logic design.

1


 


Figure 16

## Advantages of Using PALs

 

The PAL has a unique place in the world of logic design. Not only does it offer many advantages over conventional logic, it also provides many features not found anywhere else. The PAL family:

- Programmable replacement for conventional TTL logic.
- Reduces IC inventories substantially and simplifies their control.
- Reduces chip count by 4 to 1.
- Expedites and simplifies prototyping and board layout.
- Saves space with 20-pin Skinny DIP packages.
- High speed: 25ns typical propagation delay.
- Programmed on standard PROM programmers.
- Programmable three-state outputs.
- Special feature eliminates possibility of copying by competitors.

All of these features combine together to lower product development costs and increase product cost effectiveness. The bottom line is that PALs save money.

## Direct Logic Replacement




In both new and existing designs the PAL can be used to replace various logic functions. This allows the designer to optimize a circuit in many ways never before possible. The PAL is particularly effective when used to provide interfaces required by many LSI functions. PAL flexibility combined with LSI function density makes a powerful team.

## Design Flexibility

The PAL offers the systems logic designer a whole new world of options. Until now, the decision on logic system implementation was usually between SSI/MSI logic functions on one hand and microprocessors on the other. In many cases the function required is too awkward to implement the first way and too simple to justify the second. Now the PAL offers the designer high functional density, high speed, and low cost. Even better, PALs come in a variety of sizes and functions, thereby further increasing the designer's options.


## Space Efficiency

 

By allowing designers to replace many simple logic functions with single packages, the PAL allows more compact P.C. board layouts. The PAL's space saving 20-pin "skinny dip" helps to further reduce board area while simplifying board layout and fabrication. This means that many multi-card systems can now be reduced to one or two cards, and that can make the difference between a profitable success or an expensive disaster.

 
## Smaller Inventory

The PAL family can be used to replace up to 90% of the conventional TTL family with just 15 parts. This considerably lowers both shelving and inventory cataloging requirements. Even better, small custom modifications to the standard functions are easy for PAL users, not so easy for standard TTL users.





## High Speed

 


The PAL family runs faster or equal to the best of bipolar logic circuits. This makes the PAL the ideal choice for most logical operations or control sequence which requires a medium complexity and high speed. Also, in many microcomputer systems, the PAL can be used to handle high speed data interfaces that are not feasible for the microprocessor alone. This can be used to significantly extend the capabilities of the low-cost, low-speed NMOS microprocessor into areas formerly requiring high-cost bipolar microprocessors.

## Easy Programming

The members of the PAL family can be quickly and easily programmed using standard PROM programmers. This allows designers to use PALs with a minimum investment in special

## Secure Data

 


equipment. Many types of programmable logic, such as the FPLA, require an expensive, dedicated programmer.

The PAL verification logic can be completely disabled by blowing out a special "last link." This prevents the unauthorized copying of valuable data, and makes the PAL perfect for use in any application where data integrity must be carefully guarded.


## Summary

The 15 member PAL family of logic devices offers logic designers new options in the implementation of sequential and combinatorial logic designs. The family is fast, compact, flexible, and easy to use in both new and existing designs. It promises to reduce costs in most areas of design and production with a corresponding increase in product profitability.

1

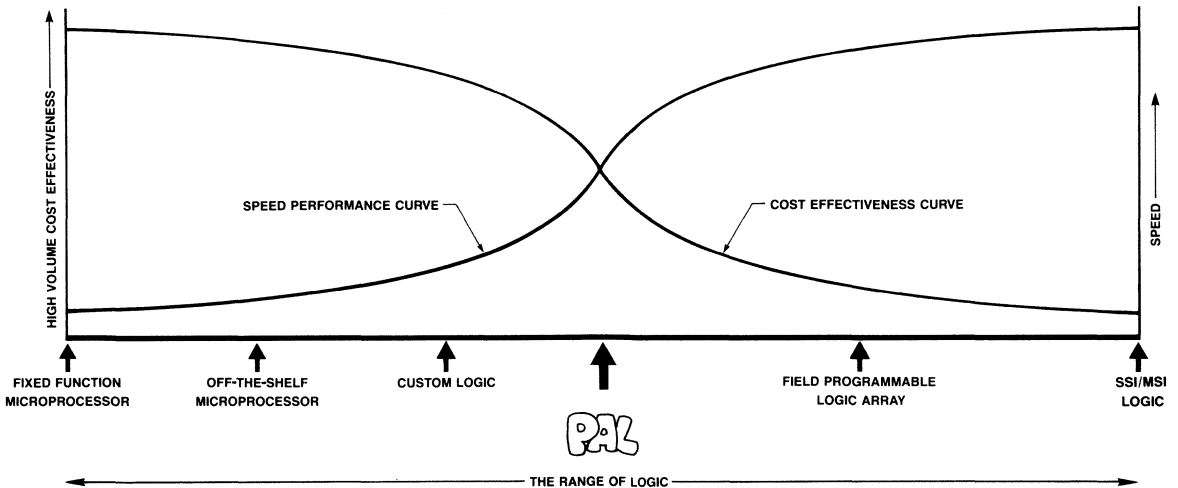



 

**Introduction 1**


**Reliability 2**

**PAL Family Data Sheet 3**



**Design Concept 4**

**Applications 5**


**Representatives/Distributors 6**

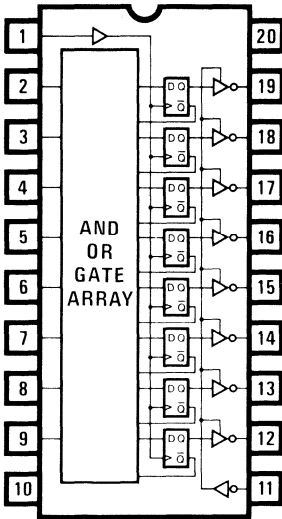

PAL16R8 Logic Symbols

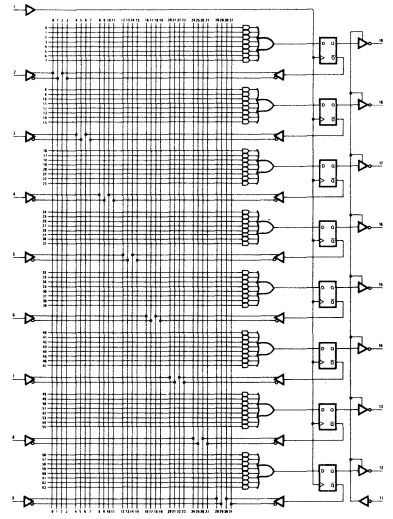 

PAL16R8 Logic Diagram

 

PAL16R8 Metalization

Figure 1

Reliability

Large-scale integrated circuits have always appealed to the system designer for the obvious reasons of lower cost and improved reliability. With a host of PROMs, RAMs and Microprocessors available today, you might expect most systems to reflect simple, small printed circuit boards populated mainly with LSI circuits. However, that is not the case. We still find a myriad of SSI and MSI packages surrounding a relatively few LSI circuits because the latter must be supported by a large number of gates, i.e., random logic, to efficiently meet a given hardware design goal. In the past many approaches have evolved from the R & D laboratory to circumvent the problem. Discretionary wiring techniques using metal mask options to delineate the interconnect pattern were the most actively pursued. Texas Instruments used this process and employed two or more levels of metalization interconnecting many die on a whole wafer to yield a custom device. Other notable attempts have Fairchild's "Micro-matrix" and most recently Hughes' "SCAT", Schottky cell array technology. All suffer from the same problems: 1. Complex two-or three-level metalization processing, 2. Custom design of new circuits and masks, 3. Small production runs with little meaningful accumulation of process and design history to optimize yield and reliability.

The latter point is the underlying factor for the failure of most custom LSI devices to live up to the reliability improvement factor expected of them over the equivalent SSI circuitry.

PALs present an equitable LSI solution to this random logic problem. Instead of metal mask options and small production runs we have a family of fifteen devices using conventional Schottky TTL processing and the fusible link technology that has made bipolar PROMs so widely accepted for over six years. On the average, the PAL accomplishes a fourfold reduction in overall pin/package count. The immediate benefits to system reliability are clear:

1. A reduction in board level complexity translates to fewer solder joints and plated through holes which are significant board-level failure points. In fact, multilayer PCB designs may be able to be implemented using the more reliable and less costly two-sided configuration.

2. Less devices on a board simplifies diagnostics resulting in a reduction of the overall handling, probing, etc. of the components. This reduces the probability of overstress through inadvertent shorting of traces or pins.

3. A reduction of packages means less wire bonds to fail. In fact, most semiconductor failures are related to packaging, i.e., hermeticity, die attach, etc. The less packages per system, the higher the system reliability.

PALs are simply programmable AND arrays feeding a fixed OR structure. See Figure 1. At the die level, the PAL circuit complexity does not exceed the 512-bit PROM on the smaller die and the 2048-bit PROM on the two larger die. Reference Table 1. In fact, in real applications, parts of the circuit are inactive or passive. On closer inspection one finds that as a maximum, only 70% of the circuitry is actually optioned at one time on a specific PAL, since the same die is used to produce PAL pinout options. The programming circuitry is only active during the fusing process. After programming it ceases to operate. Thus, the total active circuitry after programming is not more than 50% of what is on the die.

Another important aspect of the PAL that positively impacts reliability is the very low READ current in an unblown fuse, less than 0.5 mA as compared to a typical programming current of 50 mA. Since power dissipation in the fuse is a function of  $I^2$ , there are more than four orders of magnitude safety margin in actual operation. The programmable "AND" array is implemented using an emitter follower circuit with each NPN transistor in series with a fusible link. See Figure 2. The fusible link, with a typical resistance of  $40\Omega$  in the unprogrammed state, Figure 3,

2

DEVICE NUMBER	AND ARRAY ORGANIZATION					NUMBER OF TEST FUSES	DIE SIZE	POWER DISSIPATION (TYP)	
	INPUT LINES	X	T/C <sup>1</sup>	X	PRODUCT LINES = NUMBER OF FUSES				
PAL10H8	10		2		16	320	42	13K Mil <sup>2</sup>	275 mW
PAL10L8	10		2		16	320	42	13K Mil <sup>2</sup>	275 mW
PAL12H6	12		2		16	384	44	13K Mil <sup>2</sup>	275 mW
PAL12L6	12		2		16	384	44	13K Mil <sup>2</sup>	275 mW
PAL14H4	14		2		16	448	46	13K Mil <sup>2</sup>	275 mW
PAL14L4	14		2		16	448	46	13K Mil <sup>2</sup>	275 mW
PAL16H2	16		2		16	512	48	13K Mil <sup>2</sup>	275 mW
PAL16L2	16		2		16	512	48	13K Mil <sup>2</sup>	275 mW
PAL16C1	16		2		16	512	48	13K Mil <sup>2</sup>	275 mW
PAL16L8	16		2		64	2048	98	18K Mil <sup>2</sup>	700 mW
PAL16R8	16		2		64	2048	98	18K Mil <sup>2</sup>	750 mW
PAL16R6	16		2		64	2048	98	18K Mil <sup>2</sup>	750 mW
PAL16R4	16		2		64	2048	98	18K Mil <sup>2</sup>	750 mW
PAL16X4	16		2		64	2048	98	19K Mil <sup>2</sup>	800 mW
PAL16A4	16		2		74 <sup>(2)</sup>	2048	98	19K Mil <sup>2</sup>	800 mW

Note 1: True and Complement  
 Note 2: 10 Product Lines are Fixed

Table 1

Two AND Array Cells

 


Figure 2

 


Figure 3, Unprogrammed Fuse




Figure 4, Programmed Fuse

becomes an open circuit after programming, Figure 4. To assure programmability, test fuses are provided along both the input line and the product line axis in the AND array (see Table 1). These are factory programmed to provide assurance that the devices will easily program in the field. Additionally, the test lines serve to check the decoding circuitry and provide a mechanism for AC testing the unprogrammed PAL.

MMI produces these devices using the same reliable Schottky TTL technology and design rules as used in our PROM/ROM product line. Assembly is accomplished either in a standard 20-pin hermetic cerdip using a low temperature vitreous seal or a new plastic epoxy dip with thermal dissipation comparable to the ceramic, i.e.,  $\Theta_{ja} = 60^\circ\text{C/Watt}$ . The cerdip package is specially processed to guarantee low residual moisture levels, < 500 PPM. Ultrasonic bonding using aluminum wire for cerdip and ultrasonic gold bonding for plastic both use a thicker, 1.25

mil diameter wire for increased reliability. Screening and testing follow MIL-STD-883.

Empirical data being collected on 1024 and 2048 bit PROMs that were manufactured two or more years ago, and representing actual field use in rugged operating environments support a .01% per thousand hour failure rate. Assuming progress on the design/process learning curve, it is fair to say that some improvements can be expected on present generation PROMs. Since PALs actually are smaller than these PROMs, we expect even better results. Extensive life testing of PALs is an integral part of Monolithic Memories' continuing program of product reliability evaluation. All MMI's circuits, including PALs, are manufactured in the same plant that has received DESC facility certification to MIL-M-38510. Projected failure rate data for PALs are described in Figure 5.

 


1. Curves based on 1eV activation energy
2. Prom data based on 1.2 million Device hours @ 125°C T<sub>A</sub> (T<sub>J</sub> = 160°) and 5.62 million device hours field data @ 115°C T<sub>C</sub> (T<sub>J</sub> = 145°C)
3. PAL curves estimated based on circuit and fuse count equivalency; refer to Table 1.

**Figure 5. PAL Projected Failure Rate Data**

2






 

<b>Introduction</b>	<b>1</b>
<b>Reliability</b>	<b>2</b>
<b>PAL Family Data Sheet</b>	<b>3</b>
<b>Design Concept</b>	<b>4</b>
<b>Applications</b>	<b>5</b>
<b>Representatives/Distributors</b>	<b>6</b>

# Programmable Array Logic Family

## PAL Series 20 Data Sheet

 

Patent Allowed

### Features/Benefits

- Programmable replacement for conventional TTL logic.
- Reduces IC inventories substantially and simplifies their control.
- Reduces chip count by 4 to 1.
- Expedites and simplifies prototyping and board layout.
- Saves space with 20-pin Skinny DIP packages.
- High speed: 25ns typical propagation delay.
- Programmed on standard PROM programmers.
- Programmable three-state outputs.
- Special feature reduces possibility of copying by competitors.

### Description

The PAL family utilizes an advanced Schottky TTL process and the Bipolar PROM fusible link technology to provide user programmable logic for replacing conventional SSI/MSI gates and flip-flops at reduced chip count.

The family lets the systems engineer "design his own chip" by blowing fusible links to configure AND and OR gates to perform his desired logic function. Complex interconnections which previously required time-consuming layout are thus "lifted" from PC board etch and placed on silicon where they can be easily modified during prototype check-out or production.

The PAL transfer function is the familiar sum of products. Like the PROM, the PAL has a single array of fusible links. Unlike the PROM, the PAL is a programmable AND array driving a fixed OR array (the PROM is a fixed AND array driving a programmable OR array). In addition the PAL provides these options:


- Variable input/output pin ratio
- Programmable three-state outputs
- Registers with feedback
- Arithmetic capability

Unused inputs are tied directly to  $V_{CC}$  or GND. Product terms with all fuses blown assume the logical high state, and product terms connected to both true and complement of any single input assume the logical low state. Registers consist of D type flip-flops which are loaded on the low to high transition of the clock. All registers are designed to power up to logical high state at the output pin. PAL Logic Diagrams are shown with all fuses blown, enabling the designer use of the diagrams as coding sheets. 8½ x 11 Logic Diagrams are available on request.


The entire PAL family is programmed on inexpensive conventional PROM programmers with appropriate personality and socket adapter cards. Once the PAL is programmed and verified, two additional fuses may be blown to defeat verification. This feature gives the user a proprietary circuit which is very difficult to copy.

PART NUMBER	DESCRIPTION
PAL10H8	OCTAL 10 INPUT AND-OR GATE ARRAY
PAL12H6	HEX 12 INPUT AND-OR GATE ARRAY
PAL14H4	QUAD 14 INPUT AND-OR GATE ARRAY
PAL16H2	DUAL 16 INPUT AND-OR GATE ARRAY
PAL16C1	16 INPUT AND-OR/AND-OR-INVERT GATE ARRAY
PAL10L8	OCTAL 10 INPUT AND-OR-INVERT GATE ARRAY
PAL12L6	HEX 12 INPUT AND-OR-INVERT GATE ARRAY
PAL14L4	QUAD 14 INPUT AND-OR-INVERT GATE ARRAY
PAL16L2	DUAL 16 INPUT AND-OR-INVERT GATE ARRAY
PAL16L8	OCTAL 16 INPUT AND-OR-INVERT GATE ARRAY
PAL16R8	OCTAL 16 INPUT REGISTERED AND-OR GATE ARRAY
PAL16R6	HEX 16 INPUT REGISTERED AND-OR GATE ARRAY
PAL16R4	QUAD 16 INPUT REGISTERED AND-OR GATE ARRAY
PAL16X4	QUAD 16 INPUT REGISTERED AND-OR-XOR GATE ARRAY
PAL16A4	QUAD 16 INPUT REGISTERED AND-CARRY-OR-XOR GATE ARRAY

### Ordering Information

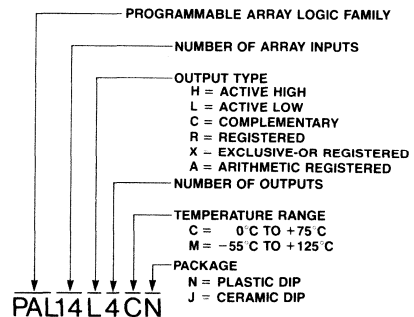

PAL Logic Symbols

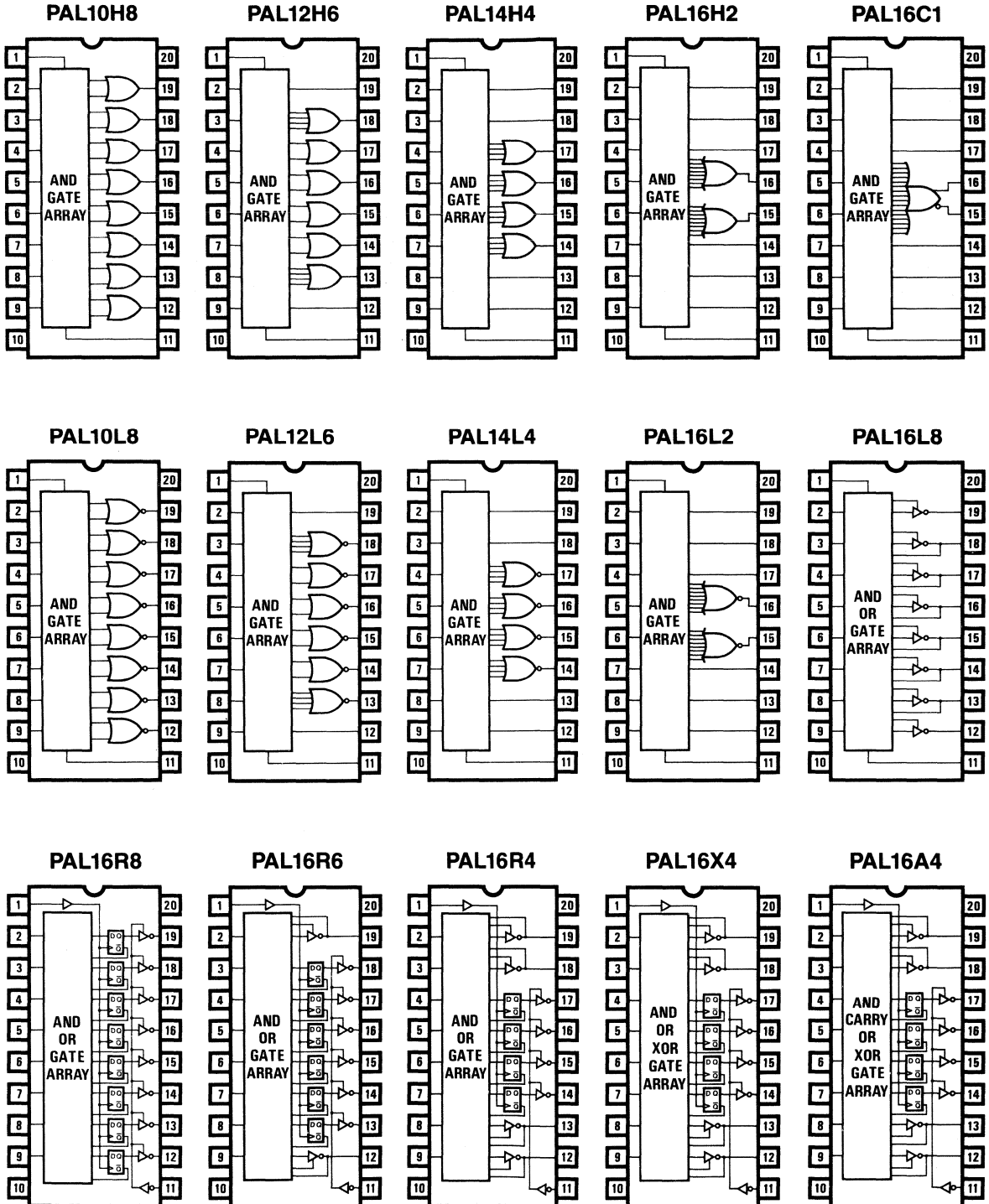

3

**Absolute Maximum Ratings**

Supply voltage $V_{CC}$ .....	Operating	Programming
Input voltage .....	7V	12V
Off-state output voltage .....	5.5V	12V
Storage temperature range .....	-65°C to 150°C	

**10H8, 12H6, 14H4, 16H2, 16C1, 10L8, 12L6, 14L4, 16L2**

**Recommended Operating Conditions**

SYMBOL	PARAMETER	MILITARY			COMMERCIAL			UNIT
		MIN	NOM	MAX	MIN	NOM	MAX	
$V_{CC}$	Supply voltage	4.5	5.0	5.5	4.75	5.00	5.25	V
$I_{OH}$	High-level output current			-2.0			-3.2	mA
$I_{OL}$	Low-level output current			8			8	mA
$T_A$	Operating free air temperature	-55		125 *	0		75	°C

**Electrical Characteristics**

Over Recommended Operating Temperature Range

SYMBOL	PARAMETER	TEST CONDITIONS	MIN	TYP	MAX	UNIT
			$V_{IH}$	High-level input voltage		
$V_{IL}$	Low-level input voltage				0.8	V
$V_{IC}$	Input clamp voltage	$V_{CC} = \text{MIN}, I_I = -18 \text{ mA}$			-1.5	V
$V_{OH}$	High-level output voltage	$V_{CC} = \text{MIN}, V_{IH} = 2V, V_{IL} = 0.8V, I_{OH} = \text{MAX}$	2.4			V
$V_{OL}$	Low-level output voltage	$V_{CC} = \text{MIN}, V_{IH} = 2V, V_{IL} = 0.8V, I_{OL} = \text{MAX}$			0.5	V
$I_I$	Input current at maximum input voltage	$V_{CC} = \text{MAX}, V_I = 5.5V$			1.0	mA
$I_{IH}$	High-level input current	$V_{CC} = \text{MAX}, V_I = 2.4V$			25	$\mu\text{A}$
$I_{IL}$	Low-level input current	$V_{CC} = \text{MAX}, V_I = 0.4V$			-250	$\mu\text{A}$
$I_{OS}$	Short-circuit output current	$V_{CC} = \text{MAX}$	-30		-130	mA
$I_{CC}$	Supply current	$V_{CC} = \text{MAX}$		55		mA

**Switching Characteristics**

Over Recommended Ranges of Temperature and  $V_{CC}$

SYMBOL	PARAMETER	TEST CONDITIONS†† $R_L = 2.0 \text{ K}\Omega$	MILITARY * $T_A = -55^\circ \text{ to } +125^\circ \text{C}$ $V_{CC} = 5.0V \pm 10\%$			COMMERCIAL $T_A = 0^\circ \text{ to } 75^\circ \text{C}$ $V_{CC} = 5.0V \pm 5\%$			UNIT
			MIN	TYP	MAX	MIN	TYP	MAX	
$t_{PD}$	From any input to any output	$C_L = 15\text{pF}$		25			25		ns

\* Operating Case Temperature only.  $T_C = 125^\circ \text{C}$

†† See Standard Test Load and Definition of Waveforms, page 3-24

# PAL Family

## 16L8, 16R8, 16R6, 16R4, 16X4, 16A4<sup>†</sup>

### Recommended Operating Conditions

SYMBOL	PARAMETER	MILITARY			COMMERCIAL			UNIT
		MIN	NOM	MAX	MIN	NOM	MAX	
V <sub>CC</sub>	Supply voltage	4.5	5.0	5.5	4.75	5.00	5.25	V
I <sub>OH</sub>	High-level output current			-2.0			-3.2	mA
I <sub>OL</sub>	Low-level output current			12			24	mA
T <sub>A</sub>	Operating free air temperature	-55		125*	0		75	°C

### Electrical Characteristics

#### Over Recommended Operating Temperature Range

SYMBOL	PARAMETER	TEST CONDITIONS	MIN	TYP	MAX	UNIT
V <sub>IH</sub>	High-level input voltage		2			V
V <sub>IL</sub>	Low-level input voltage				0.8	V
V <sub>IC</sub>	Input clamp voltage	V <sub>CC</sub> = MIN, I <sub>I</sub> = -18mA			-1.5	V
V <sub>OH</sub>	High-level output voltage	V <sub>CC</sub> = MIN, V <sub>IH</sub> = 2V, V <sub>IL</sub> = 0.8V, I <sub>OH</sub> = MAX	2.4			V
V <sub>OL</sub>	Low-level output voltage	V <sub>CC</sub> = MIN, V <sub>IH</sub> = 2V, V <sub>IL</sub> = 0.8V, I <sub>OL</sub> = MAX			0.5	V
I <sub>OZH</sub>	Off-state output current high-level voltage applied	V <sub>CC</sub> = MAX, V <sub>IH</sub> = 2V, V <sub>O</sub> = 2.4V, V <sub>IL</sub> = 0.8V			100	μA
I <sub>OZL</sub>	Off-state output current low-level voltage applied	V <sub>CC</sub> = MAX, V <sub>IH</sub> = 2V, V <sub>O</sub> = 0.4V, V <sub>IL</sub> = 0.8V			-100	μA
I <sub>I</sub>	Input current at maximum input voltage	V <sub>CC</sub> = MAX, V <sub>I</sub> = 5.5V			1.0	mA
I <sub>IH</sub>	High-level input current	V <sub>CC</sub> = MAX, V <sub>I</sub> = 2.4V			25	μA
I <sub>IL</sub>	Low-level input current	V <sub>CC</sub> = MAX, V <sub>I</sub> = 0.4V			-250	μA
I <sub>OS</sub>	Short-circuit output current	V <sub>CC</sub> = MAX,	-30		-130	mA
I <sub>CC</sub>	Supply Current	16L8		140	210 <sup>†</sup>	mA
		16R4, 16R6, 16R8	V <sub>CC</sub> = MAX	150	225 <sup>†</sup>	
		16X4, 16A4		160		

3

### Switching Characteristics

#### Over Recommended Ranges of Temperature and V<sub>CC</sub>

SYMBOL	PARAMETER	TEST CONDITIONS <sup>††</sup> R <sub>L</sub> = 667 Ω	MILITARY T <sub>A</sub> = -55° to +125°C V <sub>CC</sub> = 5.0V ± 10%			COMMERCIAL T <sub>A</sub> = -0° to +75°C V <sub>CC</sub> = 5.0V ± 5%			UNIT
			MIN	TYP	MAX	MIN	TYP	MAX	
t <sub>PD</sub>	Input to output	C <sub>L</sub> = 45pF		25	45		25	40	ns
t <sub>PD</sub>	Clock to output			15	25		15	25	ns
t <sub>PZX</sub>	Pin 11 to output enable			15	25		15	25	ns
t <sub>PXZ</sub>	Pin 11 to output disable	C <sub>L</sub> = 5pF		15	25		15	25	ns
t <sub>PZX</sub>	Input to output enable	C <sub>L</sub> = 45pF		25	45		25	40	ns
t <sub>PXZ</sub>	Input to output disable	C <sub>L</sub> = 5pF		25	45		25	40	ns
t <sub>w</sub>	Width of clock	High		25			25		ns
		Low		25			25		
t <sub>su</sub>	Setup time	16R8, 16R6, 16R4		45			40		ns
		16X4, 16A4							
t <sub>h</sub>	Hold time		0	-15		0	-15	ns	

\*Operating Case Temperature only, T<sub>C</sub> = 125°C

<sup>†</sup>I<sub>CC</sub> = MAX at minimum temperature

<sup>††</sup> See Standard Test Load and Definition of Waveforms, page 3-24

† PRELIMINARY

## Programming

PAL fuses are programmed using a low-voltage linear-select procedure which is common to all 15 PAL types. The array is divided into two groups, products 0 thru 31 and products 32 thru 63, for which pin identifications are shown in Figure 1. To program a particular fuse, both an input line and a product line are selected according to the following procedure:

- Step 1 Raise Output Disable, OD, to  $V_{IH}$
- Step 2 Select an input line by specifying  $I_0, I_1, I_2, I_3, I_4, I_5, I_6, I_7$  and L/R as shown in Table 1
- Step 3 Select a product line by specifying  $A_0, A_1$  and  $A_2$  one-of-eight select as shown in Table 2
- Step 4 Raise  $V_{CC}$  (pin 20) to  $V_{IH}$
- Step 5 Program the fuse by pulsing the output pins, O, of the selected product group to  $V_{IH}$  as shown in Table 2.
- Step 6 Lower  $V_{CC}$  (pin 20) to 6.0 V
- Step 7 Pulse the CLOCK pin and verify the output pin, O, to be Low for active Low PAL types or High for active High PAL types.
- Step 8 Lower  $V_{CC}$  (pin 20) to 4.2 V and repeat step 7
- Step 9 Should the output not verify, repeat steps 1 thru 8 up to five (5) times.

This procedure is repeated for all fuses to be blown (see programming waveforms).

To prevent further verification, two last fuses may be blown by raising pin I and pin II to  $V_p$ .  $V_{CC}$  is not required during this operation.

## Programming Parameters

$T_A = 25^\circ\text{C}$

SYMBOL	PARAMETER	LIMITS			UNIT
		MIN	TYP	MAX	
$V_{IH}$	Program-level input voltage	10.5	11	11.5	V
$I_{IH}$	Program-level input current	Output Program Pulse		50	mA
		Output Disable, OD		25	
		All Other Inputs		5	
$I_{CCH}$	Program Supply Current			400	mA
$T_P$	Program Pulse Width	10		50	$\mu\text{s}$
$t_d$	Delay time	100			ns
	Program Pulse duty cycle			25	%
$V_p$	Program/Verify-Protect-input voltage		20		V
$I_p$	Program/Verify-Protect-input current			400	mA


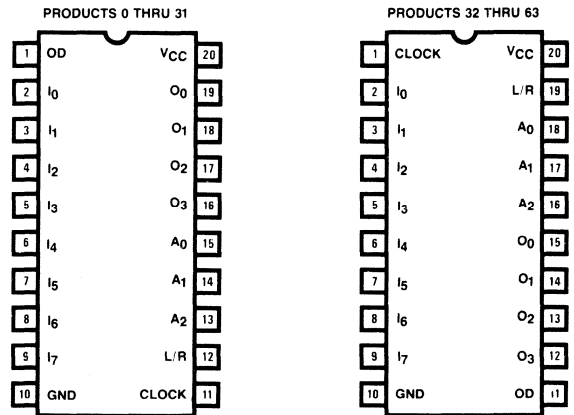


Figure 1 Pin Identification

## Programming Waveforms

 

**Voltage Legend**

L = Low-level input voltage,  $V_{iL}$   
 H = High-level input voltage,  $V_{iH}$   
 HH = High-level program voltage,  $V_{iHH}$

INPUT LINE NUMBER	PIN IDENTIFICATION								L/R
	I7	I6	I5	I4	I3	I2	I1	I0	
0	HH	HH	HH	HH	HH	HH	HH	L	L
1	HH	HH	HH	HH	HH	HH	HH	H	L
2	HH	HH	HH	HH	HH	HH	HH	L	HH
3	HH	HH	HH	HH	HH	HH	HH	H	HH
4	HH	HH	HH	HH	HH	HH	L	HH	L
5	HH	HH	HH	HH	HH	HH	H	HH	L
6	HH	HH	HH	HH	HH	HH	L	HH	HH
7	HH	HH	HH	HH	HH	HH	H	HH	HH
8	HH	HH	HH	HH	HH	L	HH	HH	L
9	HH	HH	HH	HH	HH	H	HH	HH	L
10	HH	HH	HH	HH	HH	L	HH	HH	HH
11	HH	HH	HH	HH	HH	H	HH	HH	HH
12	HH	HH	HH	HH	L	HH	HH	HH	L
13	HH	HH	HH	HH	H	HH	HH	HH	L
14	HH	HH	HH	HH	L	HH	HH	HH	HH
15	HH	HH	HH	HH	H	HH	HH	HH	HH
16	HH	HH	HH	L	HH	HH	HH	HH	L
17	HH	HH	HH	H	HH	HH	HH	HH	L
18	HH	HH	HH	L	HH	HH	HH	HH	HH
19	HH	HH	HH	H	HH	HH	HH	HH	HH
20	HH	HH	L	HH	HH	HH	HH	HH	L
21	HH	HH	H	HH	HH	HH	HH	HH	L
22	HH	HH	L	HH	HH	HH	HH	HH	HH
23	HH	HH	H	HH	HH	HH	HH	HH	HH
24	HH	L	HH	HH	HH	HH	HH	HH	L
25	HH	H	HH	HH	HH	HH	HH	HH	L
26	HH	L	HH	HH	HH	HH	HH	HH	HH
27	HH	H	HH	HH	HH	HH	HH	HH	HH
28	L	HH	HH	HH	HH	HH	HH	HH	L
29	H	HH	HH	HH	HH	HH	HH	HH	L
30	L	HH	HH	HH	HH	HH	HH	HH	HH
31	H	HH	HH	HH	HH	HH	HH	HH	HH

Table 1 Input Line Select


PRODUCT LINE NUMBER	PIN IDENTIFICATION						
	O3	O2	O1	O0	A2	A1	A0
0, 32	L	L	L	HH	L	L	L
1, 33	L	L	L	HH	L	L	HH
2, 34	L	L	L	HH	L	HH	L
3, 35	L	L	L	HH	L	HH	HH
4, 36	L	L	L	HH	HH	L	L
5, 37	L	L	L	HH	HH	L	HH
6, 38	L	L	L	HH	HH	HH	L
7, 39	L	L	L	HH	HH	HH	HH
8, 40	L	L	HH	L	L	L	L
9, 41	L	L	HH	L	L	L	HH
10, 42	L	L	HH	L	L	HH	L
11, 43	L	L	HH	L	L	HH	HH
12, 44	L	L	HH	L	HH	L	L
13, 45	L	L	HH	L	HH	L	HH
14, 46	L	L	HH	L	HH	HH	L
15, 47	L	L	HH	L	HH	HH	HH
16, 48	L	HH	L	L	L	L	L
17, 49	L	HH	L	L	L	L	HH
18, 50	L	HH	L	L	L	HH	L
19, 51	L	HH	L	L	L	HH	HH
20, 52	L	HH	L	L	HH	L	L
21, 53	L	HH	L	L	HH	L	HH
22, 54	L	HH	L	L	HH	HH	L
23, 55	L	HH	L	L	HH	HH	HH
24, 56	HH	L	L	L	L	L	L
25, 57	HH	L	L	L	L	L	HH
26, 58	HH	L	L	L	L	HH	L
27, 59	HH	L	L	L	L	HH	HH
28, 60	HH	L	L	L	HH	L	L
29, 61	HH	L	L	L	HH	L	HH
30, 62	HH	L	L	L	HH	HH	L
31, 63	HH	L	L	L	HH	HH	HH

Table 2 Product Line Select


Package Drawings

UNLESS OTHERWISE SPECIFIED:  
 ALL DIMENSIONS MIN.-MAX. IN INCHES.  
 ALL DIMENSIONS MIN.-MAX. IN MILLIMETERS.

N20 Plastic Dip

 


J20 Ceramic Dip

 





Logic Diagram PAL10H8

 


3

 


Logic Diagram PAL14H4

 


3

 


Logic Diagram PAL16C1

 

3

 


Logic Diagram PAL12L6

 


3

Logic Diagram PAL14L4

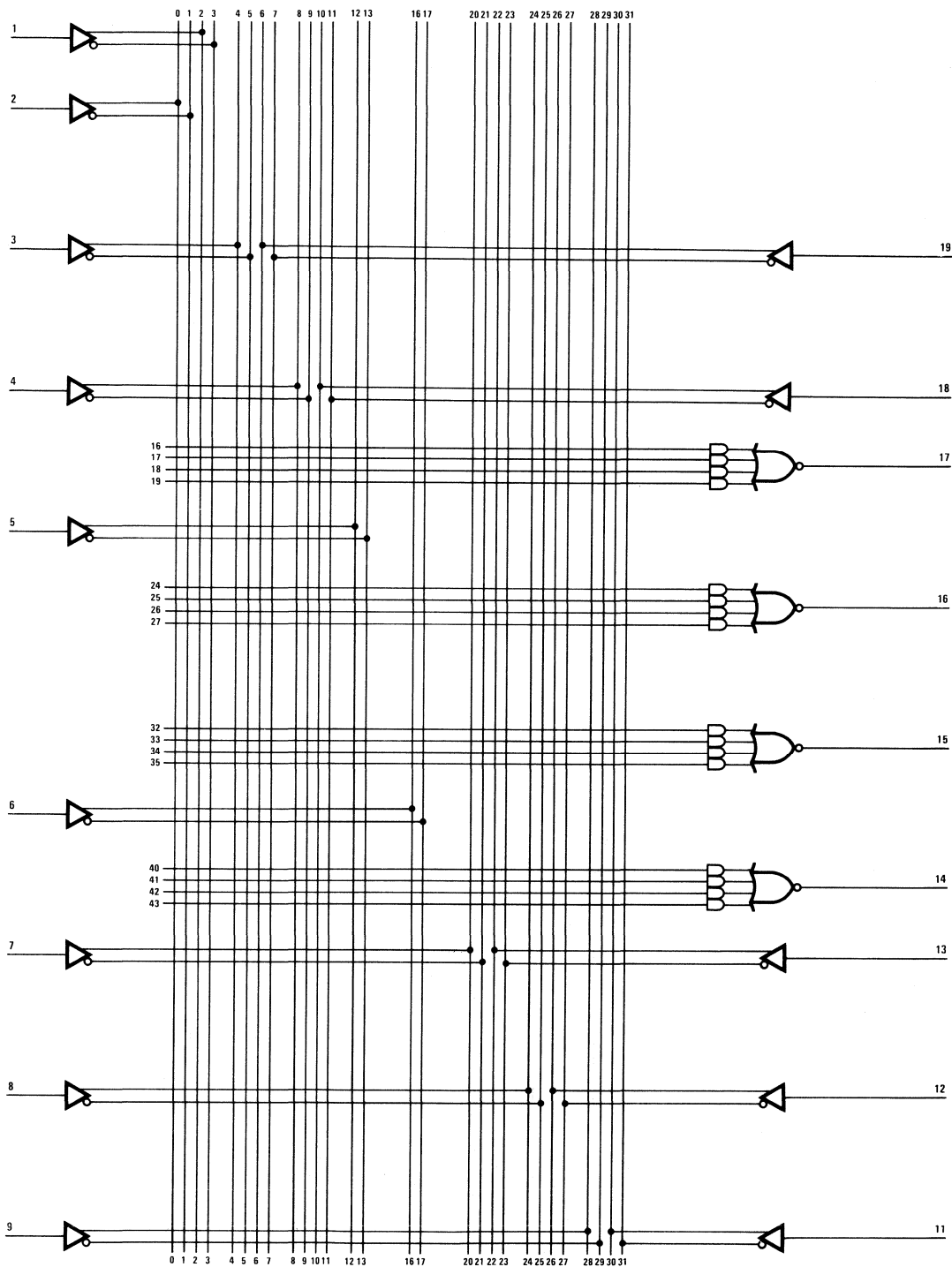







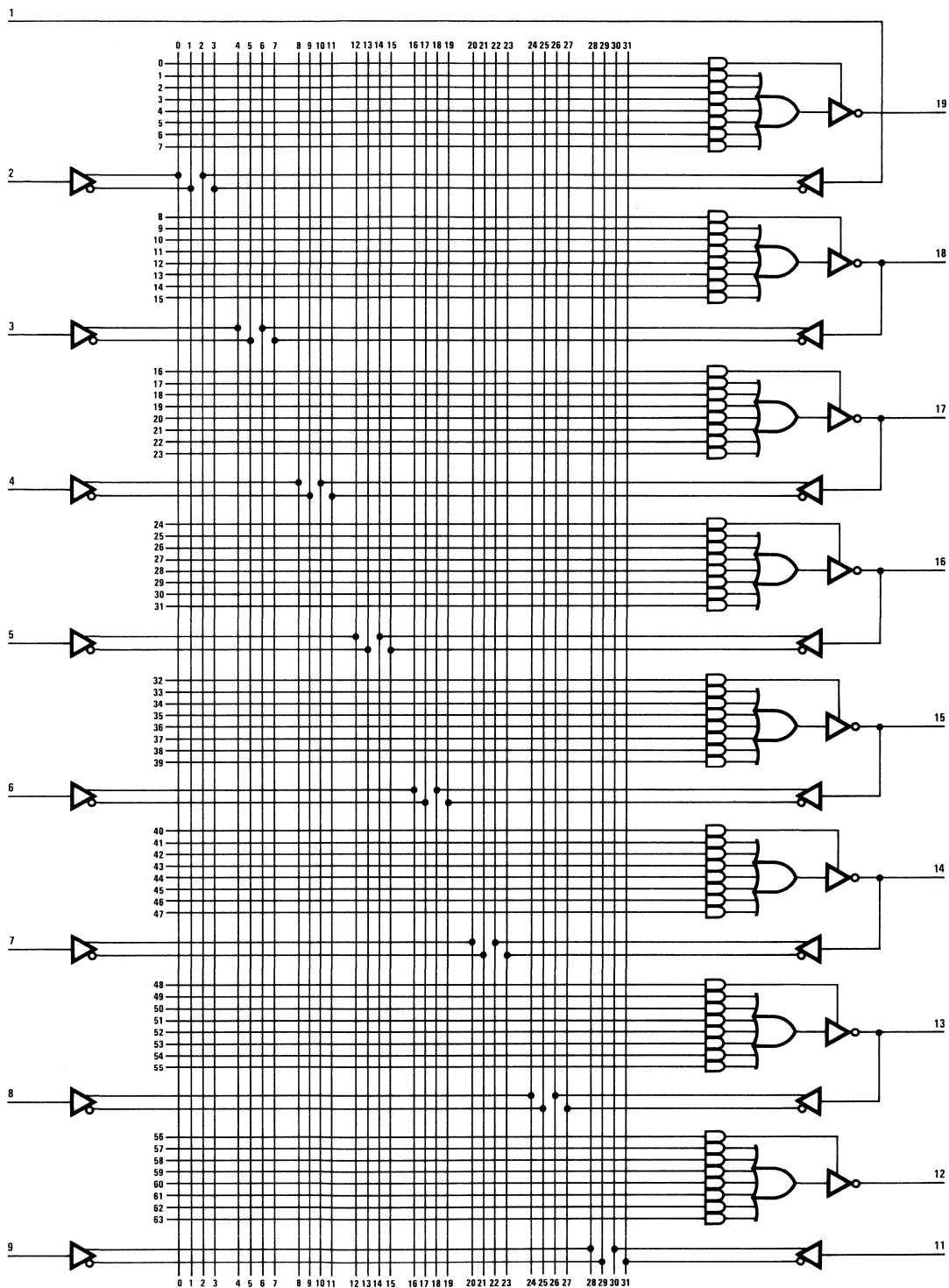


Logic Diagram PAL16R8

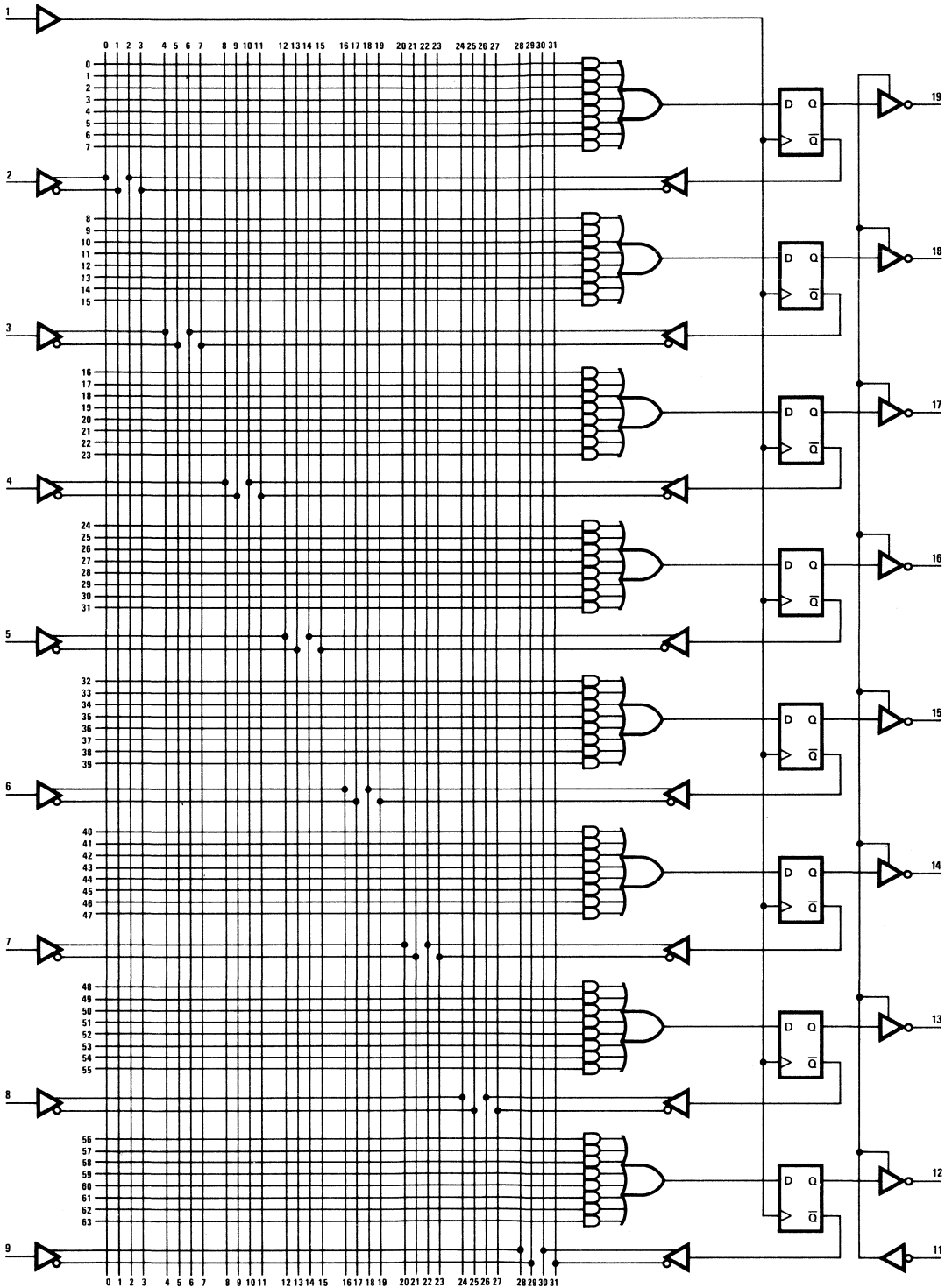

3

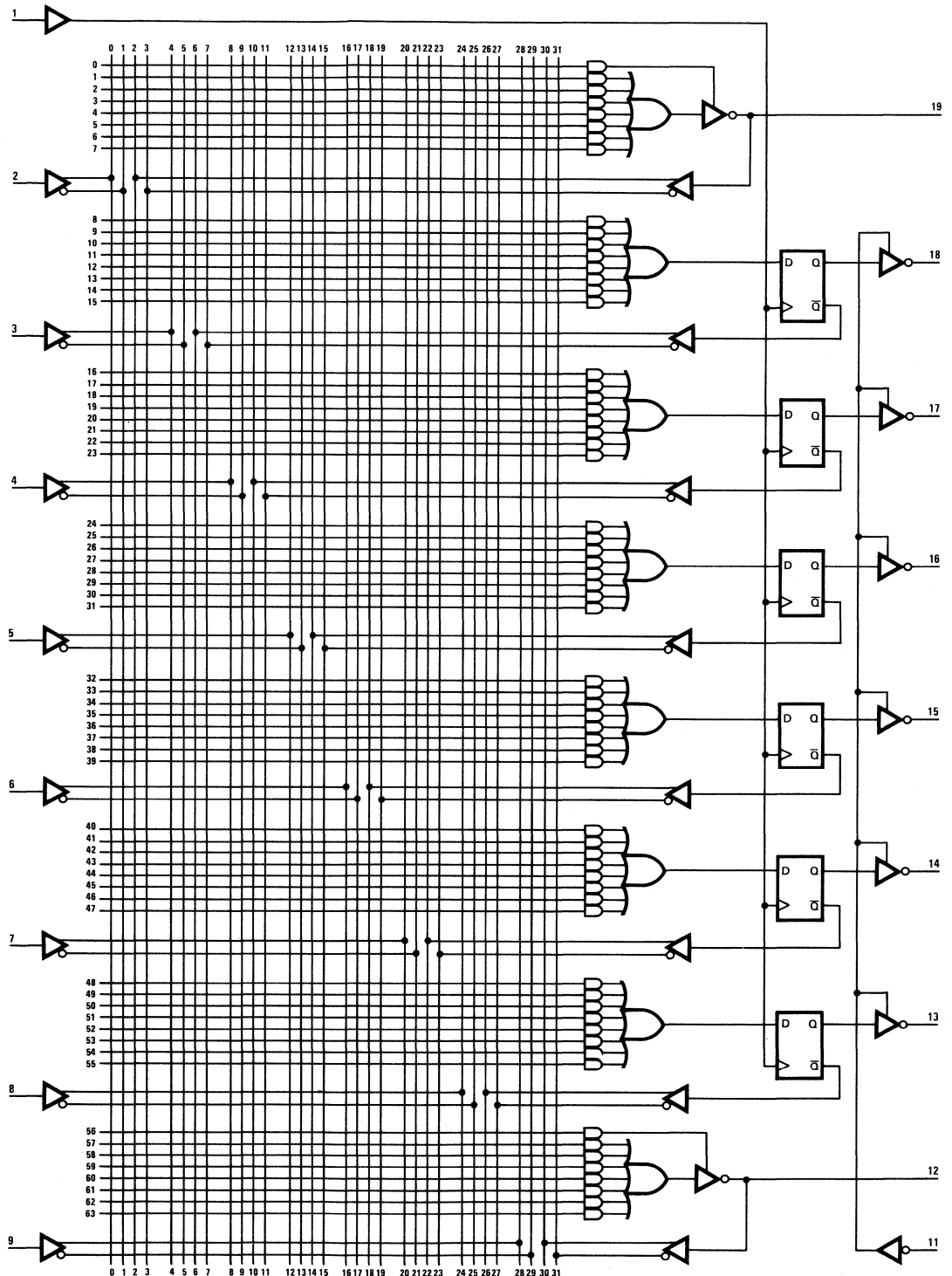


Logic Diagram PAL16R4

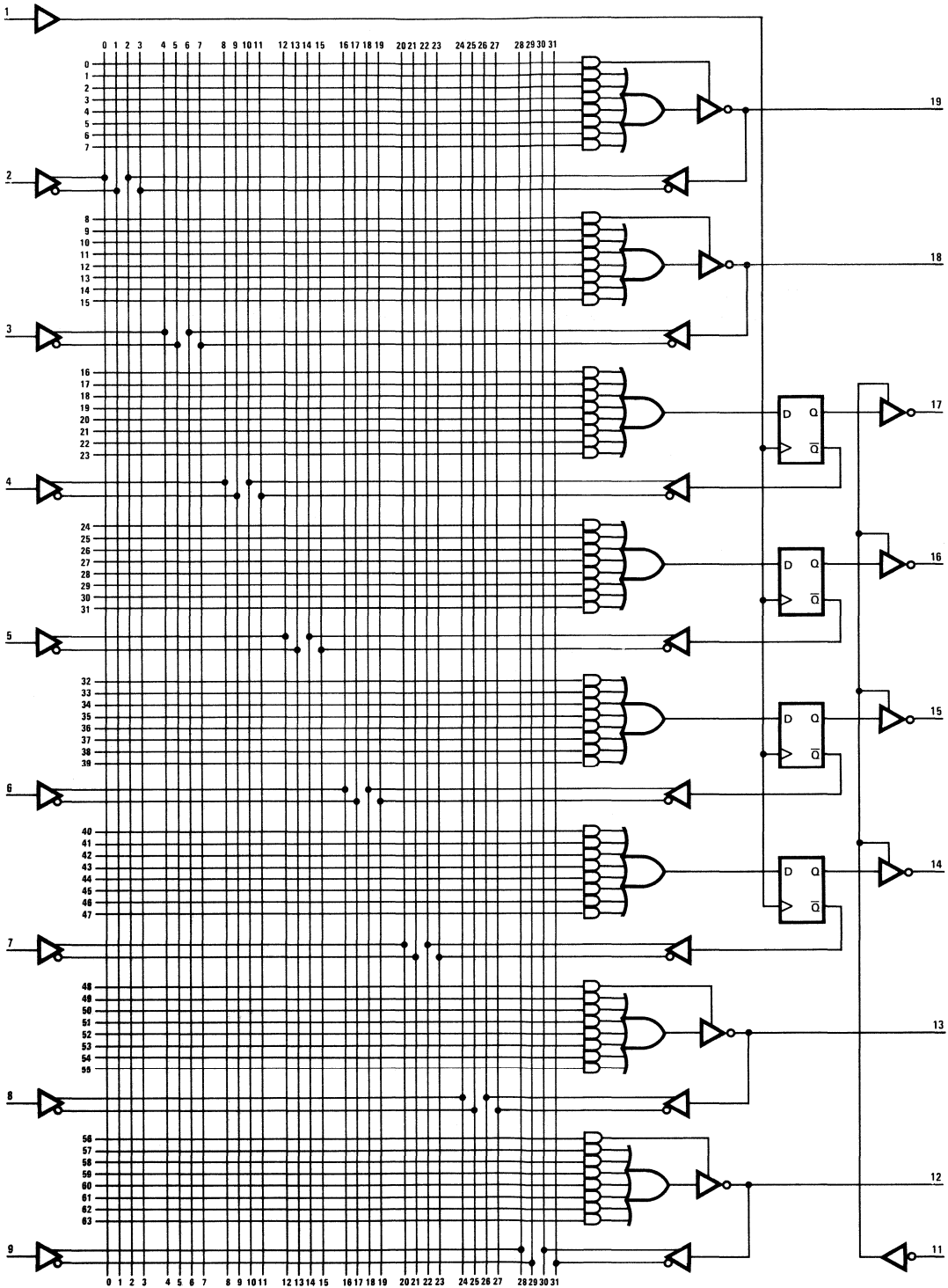


3

Logic Diagram PAL16X4

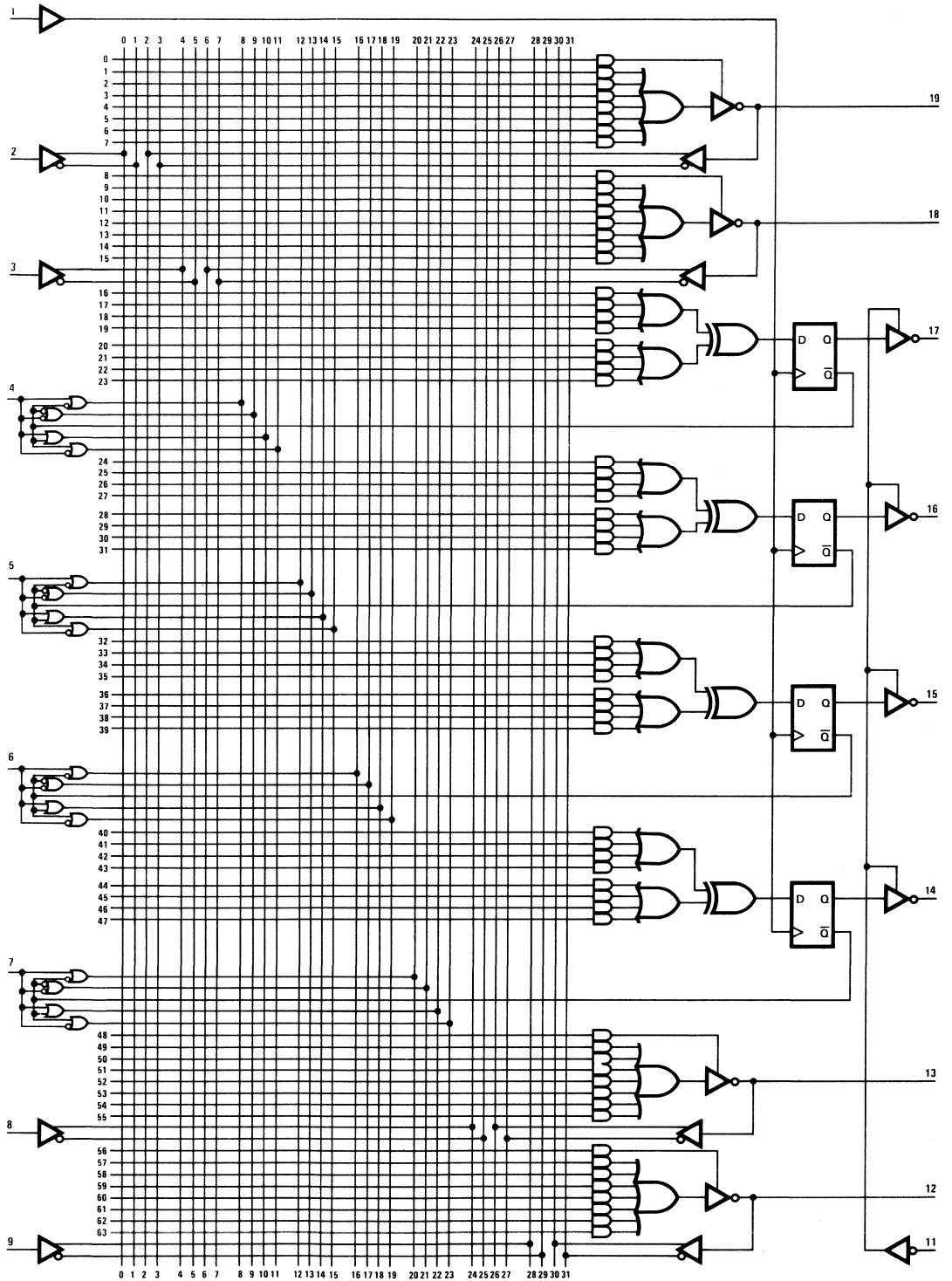


Logic Diagram PAL16A4

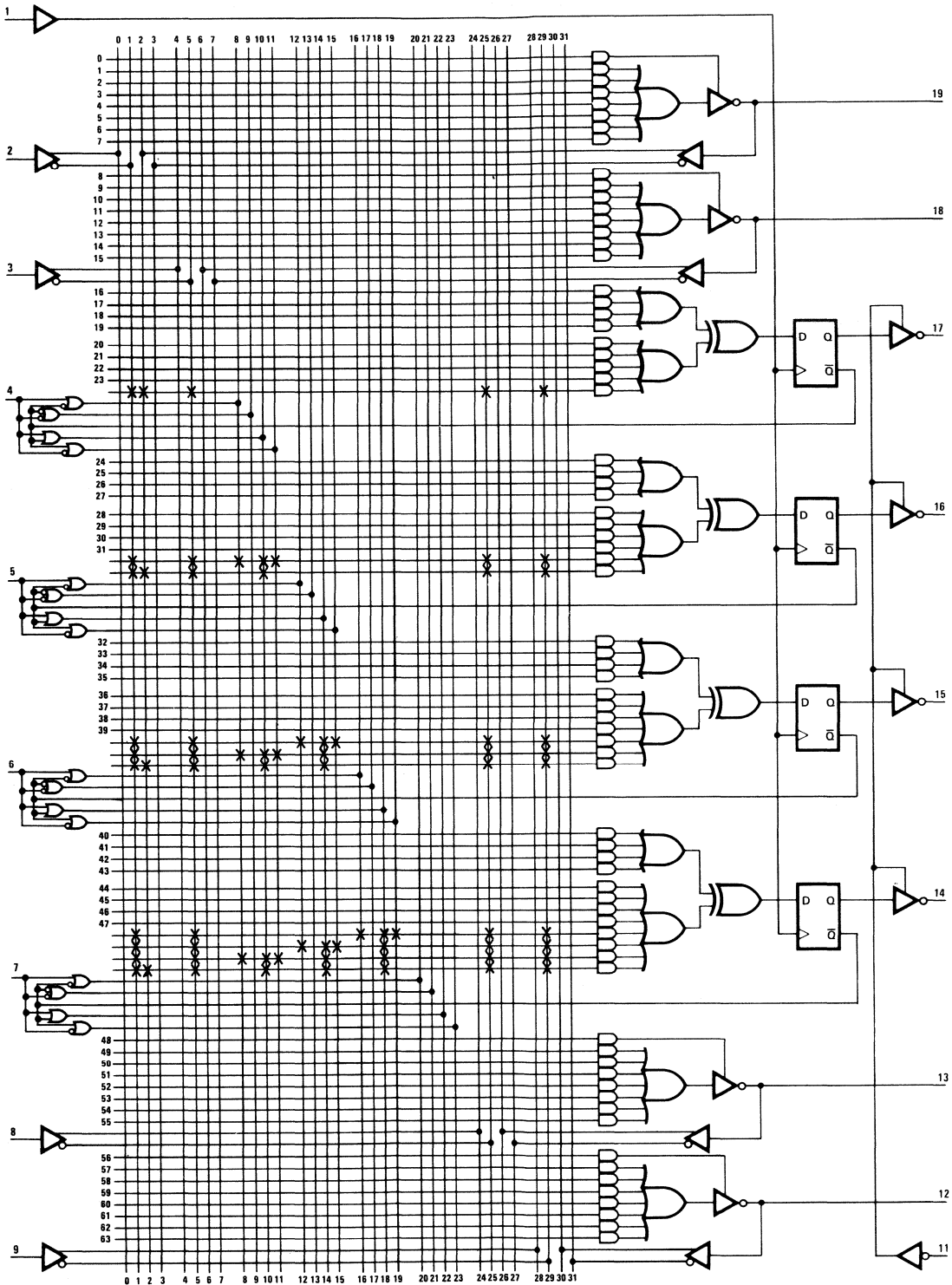


3

## Standard Test Load and Definitions of Waveforms


### Standard Test Load

 


### Test Waveforms

 


Setup and Hold

 

Pulse Width

 

Propagation Delay

 

Enable and Disable

NOTES: A.  $C_L$  includes probe and jig capacitance.

B. All diodes are 1N916 or 1N3064.

C.  $R_O = 1K$ ,  $V_T = 1.5V$

D. Waveform 1 is for an output with internal conditions such that the output is low except when disabled by the output control. Waveform 2 is for an output with internal conditions such that the output is high except when disabled by the output control.

E. In the examples above, the phase relationships between inputs and outputs have been chosen arbitrarily.

F. All input pulses are supplied by generators having the following characteristics:  $PRR \leq 1$  MHz,  $Z_{Out} = 50\Omega$  and:  $t_r \leq 15$  ns  $t_f \leq 6$  ns

G. When measuring propagation delay times of 3-state outputs, switches S1 and S2 are closed.



## Clock Frequency

### Maximum clock frequency, $f_{max}$

The highest rate at which the clock input of a bistable circuit can be driven through its required sequence while maintaining stable transitions of logic level at the output with input conditions established that should cause changes of output logic level in accordance with the specification.

## Current

### High-level input current, $I_{IH}$

The current into \* an input when a high-level voltage is applied to that input.

### High-level output current, $I_{OH}$

The current into \* an output with input conditions applied that according to the product specification will establish a high level at the output.

### Low-level input current, $I_{IL}$

The current into \* an input when a low-level voltage is applied to that input.

### Low-level output current, $I_{OL}$

The current into \* an output with input conditions applied that according to the product specification will establish a low level at the output.

### Off-state (high-impedance-state) output current (of a three-state output), $I_{OZ}$

The current into \* an output having three-state capability with input conditions applied that according to the product specification will establish the high-impedance state at the output.

### Short-circuit output current, $I_{OS}$

The current into \* an output when that output is short-circuited to ground (or other specified potential) with input conditions applied to establish the output logic level farthest from ground potential (or other specified potential).

### Supply current, $I_{CC}$

The current into \* the  $V_{CC}$  supply terminal of an integrated circuit.

\*Current out of a terminal is given as a negative value.

## Hold Time

### Hold time, $t_h$

The interval during which a signal is retained at a specified input terminal after an active transition occurs at another specified input terminal.

- NOTES: 1. The hold time is the actual time between two events and may be insufficient to accomplish the intended result. A minimum value is specified that is the shortest interval for which correct operation of the logic element is guaranteed.
2. The hold time may have a negative value in which case the minimum limit defines the longest interval (between the release of data and the active transition) for which correct operation of the logic element is guaranteed.

## Output Enable and Disable Time

### Output enable time (of a three-state output) to high level, $tpZH$ (or low level, $tpZL$ )

The propagation delay time between the specified reference points on the input and output voltage waveforms with the

three-state output changing from a high-impedance (off) state to the defined high (or low) level.

### Output enable time (of a three-state output) to high or low level, $tpZX$

The propagation delay time between the specified reference points on the input and output voltage waveforms with the three-state output changing from a high-impedance (off) state to either of the defined active levels (high or low).

### Output disable time (of a three-state output) from high level, $trpHZ$ (or low level, $trpLZ$ )

The propagation delay time between the specified reference points on the input and output voltage waveforms with the three-state output changing from the defined high (or low) level to a high-impedance (off) state.

### Output disable time (of a three-state output) from high or low level, $trpXZ$

The propagation delay time between the specified reference points on the input and output voltage waveforms with the three-state output changing from either of the defined active levels (high or low) to a high-impedance (off) state.

## Propagation Time

### Propagation delay time, $tpd$

The time between the specified reference points on the input and output voltage waveforms with the output changing from one defined level (high or low) to the other defined level.

### Propagation delay time, low-to-high-level output, $tpLH$

The time between the specified reference points on the input and output voltage waveforms with the output changing from the defined low level to the defined high level.

### Propagation delay time, high-to-low-level output, $tpHL$

The time between the specified reference points on the input and output voltage waveforms with the output changing from the defined high level to the defined low level.

3

## Pulse Width

### Pulse width, $t_w$

The time interval between specified reference points on the leading and trailing edges of the pulse waveform.

## Setup Time

### Setup time, $t_{SU}$

The time interval between the application of a signal that is maintained at a specified input terminal and a consecutive active transition at another specified input terminal.

- NOTES: 1. The setup time is the actual time between two events and may be insufficient to accomplish the setup. A minimum value is specified that is the shortest interval for which correct operation of the logic element is guaranteed.
2. The setup time may have a negative value in which case the minimum limit defines the longest interval (between the active transition and the application of the other signal) for which correct operation of the logic element is guaranteed.

## Voltage

### High-level input voltage, $V_{IH}$

An input voltage within the more positive (less negative) of the two ranges of values used to represent the binary variables.

NOTE: A minimum is specified that is the least positive value of high-level voltage for which operation of the logic element within specification limits is guaranteed.

### High-level output voltage, $V_{OH}$

The voltage at an output terminal with input conditions applied that according to the product specification will establish a high level at the output.

### Input clamp voltage, $V_{IC}$

An input voltage in a region of relatively low differential resistance that serves to limit the input voltage swing.

### Low-level input voltage, $V_{IL}$

An input voltage level within the less positive (more negative) of the two ranges of values used to represent the binary variables.

NOTE: A maximum is specified that is the most positive value of low-level input voltage for which operation of the logic element within specification limits is guaranteed.

### Low-level output voltage, $V_{OL}$

The voltage at an output terminal with input conditions applied that according to the product specification will establish a low level at the output.

### Negative-going threshold voltage, $V_T^-$

The voltage level at a transition-operated input that causes operation of the logic element according to specification as the input voltage falls from a level above the positive-going threshold voltage,  $V_{T+}$ .

### Positive-going threshold voltage, $V_{T+}$


The voltage level at a transition-operated input that causes operation of the logic element according to specification as the input voltage rises from a level below the negative-going threshold voltage,  $V_{T-}$ .

## Truth Table Explanations

H	= high level (steady-state)
L	= low level (steady-state)
↑	= transition from low to high level
↓	= transition from high to low level
X	= irrelevant (any input, including transitions)
Z	= off (high-impedance) state of a 3-state output
a..h	= the level of steady-state inputs at inputs A through H respectively
$Q_0$	= level of Q before the indicated steady-state input conditions were established
$\bar{Q}_0$	= complement of $Q_0$ or level of $\bar{Q}$ before the indicated steady-state input conditions were established
$Q_n$	= level of Q before the most recent active transition indicated by ↓ or ↑

If, in the input columns, a row contains only the symbols H, L, and/or X, this means the indicated output is valid whenever the input configuration is achieved and regardless of the sequence in which it is achieved. The output persists so long as the input configuration is maintained.

If, in the input columns, a row contains H, L, and/or X together with ↑ and/or ↓, this means the output is valid whenever the input configuration is achieved but the transition(s) must occur following the achievement of the steady-state levels. If the output is shown as a level (H, L,  $Q_0$ , or  $\bar{Q}_0$ ), it persists so long as the steady-state input levels and the levels that terminate indicated transitions are maintained. Unless otherwise indicated, input transitions in the opposite direction to those shown have no effect at the output.

 

<b>Introduction</b>	<b>1</b>
<b>Reliability</b>	<b>2</b>
<b>PAL Family Data Sheet</b>	<b>3</b>
<b>Design Concept</b>	<b>4</b>
<b>Applications</b>	<b>5</b>
<b>Representatives/Distributors</b>	<b>6</b>

## Selecting the Right PAL

The 15 PAL part types offer a wide range of complexity to choose from. Starting with the PAL10H8 (10 inputs, 8 active high outputs), the first 9 PAL types can replace random SSI gate functions at about a 4 to 1 chip count reduction. With a variety of input/output pin ratios and Active High or Active Low outputs, this group, described as combinatorial, is designed to provide the Low Power Schottky (LS) fan-out and fan-in characteristics of 8 mA output sink ( $I_{OL}$ ) for totem-pole outputs and 250  $\mu A$  input loading ( $I_{IL}$ ).

The next 6 PALs provide the additional features of three-state outputs, state sequencing, arithmetic, and programmable input/output pin ratios. The three-state outputs drive the standard LS output sink of 24 mA ( $I_{OL}$ ), providing bus driving capability. These sequential PALs are ideal for replacing existing MSI and/or defining new LSI functions not presently available.

Unused inputs should be tied to either  $V_{CC}$  or GND. The series resistor required for unused inputs on standard TTL is NOT required for PALs, thus using less parts.

## Defining the Pinout

The first step in designing a PAL is selecting the Pinout. The example shown below shows a method for circling a section of conventionally drawn logic to define a boundary for a PAL function. This boundary will dictate a specific number of input

pins and output pins. For the example, 8 inputs and 6 outputs are required, well within the capability of the PAL10L8. Assignment of inputs and outputs to specific pins can be done using the PAL Logic Symbol as shown below.



Note: This pinout selection can later be changed to suit printed circuit board layout as will be shown in the Dice Game example.

## Specifying the Design

Once a pinout is selected, the fuse pattern is specified by one of several methods. The Applications section of this handbook shows a variety of examples and design techniques. The basic method is simply to mark the PAL Logic Diagram with appropriate fuse interconnections for the desired logic transfer function. This can be accomplished by translating conventional logic diagrams to PAL Logic Diagrams. Next, the PAL Logic Diagram is translated to the PAL Programming Format, which is compatible with standard PROM programmer format for 512 x 4 (2048-bit) PROMs. The most common PROM programmer input medium is paper tape, with BHLF, BPNF or Hexadecimal Formats.

Fuses left intact are indicated on the logic diagram by an "X" at the intersection of the input line and the AND gate product line. A blown fuse is not marked. The PAL Logic Diagrams are provided with no fuses marked, allowing the designer to use the diagram as a coding format. Actually, the unprogrammed PAL is shipped with all X's (all fuses) intact. Each fuse node is identified by a Product Line Number and an Input Line Number which are used to locate the corresponding square in the PAL Programming Format. An "X" on the logic diagram corresponds to an "L" or an "N" in the programming format. A blank on the logic diagram corresponds to an "H" or a "P" on the programming format.

 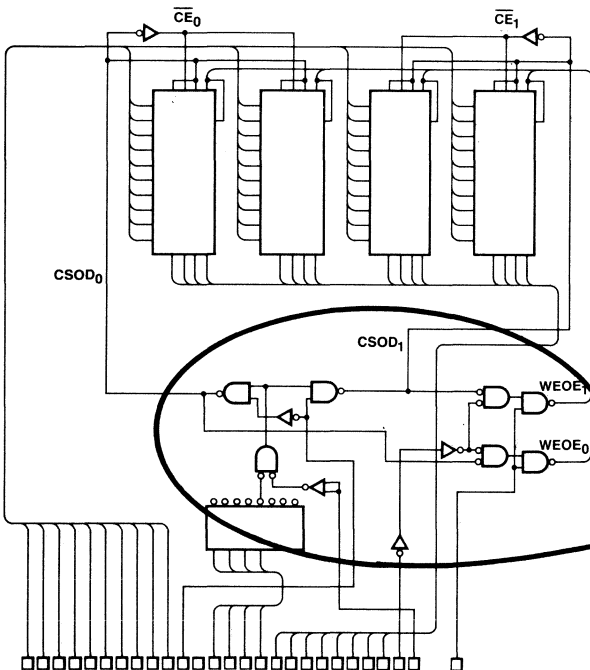Note: The first nine PALs appear to the PROM programmer as a depopulated 512 x 4 PROM. As the programmer will expect to verify all 2048 locations, the PAL Programming Format must provide the expected pattern for verifying non-existent fuse nodes. The expected patterns for non-existent fuse nodes are shown at the end of this section.



## PAL Legend

### Constants

LOW (L)	NEGATIVE (N)	ZERO (0)	GND	FALSE	×		FUSE NOT BLOWN
HIGH (H)	POSITIVE (P)	ONE (1)	V <sub>CC</sub>	TRUE	-		FUSE BLOWN

### Operators


- = Equal, .EQ.
- := Replaced by Following ↑
- ∕ Complement
- ◆ AND, Product
- + OR, Sum
- :+ XOR, .NE.
- Conditional Three State, Arithmetic

### Equations



Standard  $Q_1 = I_1 \bar{I}_2 + \bar{I}_1 I_2$

PALASM  $Q1 = I1 \diamond I2 + \bar{I}1 \diamond I2$

### Conventional Symbology

 


### PAL Symbology

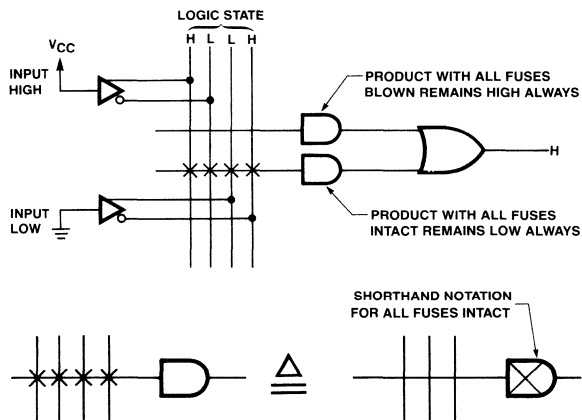 

4

### PAL Logic Diagram

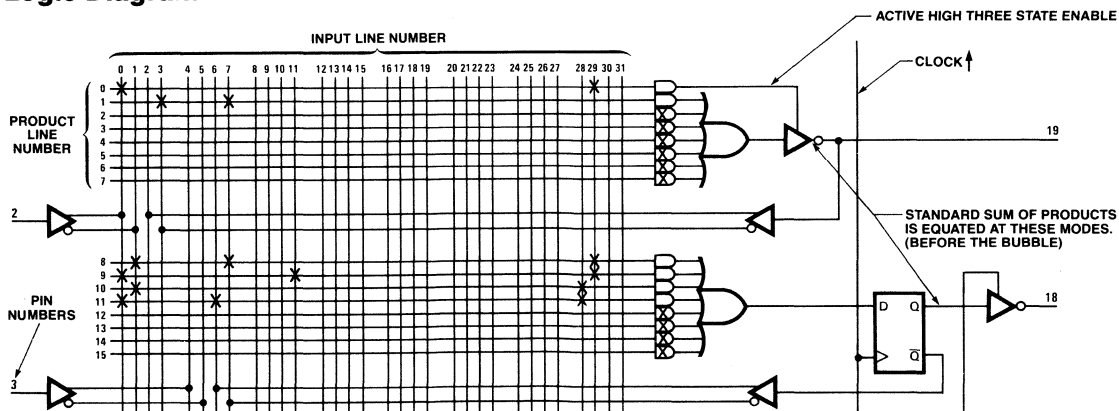

# Design Concepts

## PAL Programming Format

Pal \_\_\_\_\_

Pattern \_\_\_\_\_

Name \_\_\_\_\_

### For Products 0 thru 31

		O <sub>4</sub> O <sub>3</sub> O <sub>2</sub> O <sub>1</sub>																															
		24	16	8	0	25	17	9	1	26	18	10	2	27	19	11	3	28	20	12	4	29	21	13	5	30	22	14	6	31	23	15	7
↑ INPUTS 0 TO 31 ↓	0	0				32				64				96				128				160				192				224			
	1	1				33				65				97				129				161				193				225			
	2	2				34				66				98				130				162				194				226			
	3	3				35				67				99				131				163				195				227			
	4	4				36				68				100				132				164				196				228			
	5	5				37				69				101				133				165				197				229			
	6	6				38				70				102				134				166				198				230			
	7	7				39				71				103				135				167				199				231			
	8	8				40				72				104				136				168				200				232			
	9	9				41				73				105				137				169				201				233			
	10	10				42				74				106				138				170				202				234			
	11	11				43				75				107				139				171				203				235			
	12	12				44				76				108				140				172				204				236			
	13	13				45				77				109				141				173				205				237			
	14	14				46				78				110				142				174				206				238			
	15	15				47				79				111				143				175				207				239			
	16	16				48				80				112				144				176				208				240			
	17	17				49				81				113				145				177				209				241			
	18	18				50				82				114				146				178				210				242			
	19	19				51				83				115				147				179				211				243			
	20	20				52				84				116				148				180				212				244			
	21	21				53				85				117				149				181				213				245			
	22	22				54				86				118				150				182				214				246			
	23	23				55				87				119				151				183				215				247			
	24	24				56				88				120				152				184				216				248			
	25	25				57				89				121				153				185				217				249			
	26	26				58				90				122				154				186				218				250			
	27	27				59				91				123				155				187				219				251			
	28	28				60				92				124				156				188				220				252			
	29	29				61				93				125				157				189				221				253			
	30	30				62				94				126				158				190				222				254			
	31	31				63				95				127				159				191				223				255			


### For Products 32 thru 63

		56 48 40 32				57 49 41 33				58 50 42 34				59 51 43 35				60 52 44 36				61 53 45 37				62 54 46 38				63 55 47 39			
↑ INPUTS 0 TO 31 ↓	0	256				288				320				352				384				416				448				480			
	1	257				289				321				353				385				417				449				481			
	2	258				290				322				354				386				418				450				482			
	3	259				291				323				355				387				419				451				483			
	4	260				292				324				356				388				420				452				484			
	5	261				293				325				357				389				421				453				485			
	6	262				294				326				358				390				422				454				486			
	7	263				295				327				359				391				423				455				487			
	8	264				296				328				360				392				424				456				488			
	9	265				297				329				361				393				425				457				489			
	10	266				298				330				362				394				426				458				490			
	11	267				299				331				363				395				427				459				491			
	12	268				300				332				364				396				428				460				492			
	13	269				301				333				365				397				429				461				493			
	14	270				302				334				366				398				430				462				494			
	15	271				303				335				367				399				431				463				495			
	16	272				304				336				368				400				432				464				496			
	17	273				305				337				369				401				433				465				497			
	18	274				306				338				370				402				434				466				498			
	19	275				307				339				371				403				435				467				499			
	20	276				308				340				372				404				436				468				500			
	21	277				309				341				373				405				437				469				501			
	22	278				310				342				374				406				438				470				502			
	23	279				311				343				375				407				439				471				503			
	24	280				312				344				376				408				440				472				504			
	25	281				313				345				377				409				441				473				505			
	26	282				314				346				378				410				442				474				506			
	27	283				315				347				379				411				443				475				507			
	28	284				316				348				380				412				444				476				508			
	29	285				317				349				381				413				445				477				509			
	30	286				318				350				382				414				446				478				510			
	31	287				319				351				383				415				447				479				511			


## Paper Tape Inputs

Truth tables can be sent to MMI in an ASCII tape format. Information can be sent by mail or TWX. (MMI's TWX number is 910-339-9229.) Although MMI can program PALs with the tape in any format, the following formats have been the most popular.

## 8 Level TWX

 

## BHLF Format

 

The required heading information at the beginning of the tape is as follows:

CUSTOMER'S NAME AND PHONE _____	CUSTOMER SYMBOLIZED PART NUMBER _____
CUSTOMER'S TWX NUMBER (IF ANY) _____	TRUTH TABLE NUMBER (IF ANY) _____
PURCHASE ORDER NUMBER _____	TYPE OF FORMAT (IF ASCII, HEX, BHLF, ETC.) _____
MMI PART NUMBER _____	25 BELL OR RUBOUT CHARACTERS _____

An example is shown below:

```

BLARNEY ELECTRONICS 408-735-8104
TWX911-338-9225
PD142
PAL16R8
0431
PAT0001
BHLF
    
```

4

(25 Bell or Rubout Characters)

```

S
BLLLFH BLLLLF BLHLHF BLHHHF BLLHHF BHHHHF BLLLHF BLHLHF
:
:
:
:
:
:
:
:
BLLLLF BLHLHF BLHHHF BLLHHF BHHHHF BLLLHF BLHLHF BLLLLF
E
    
```

## BPNF Format

This format is identical to the BHLF format with the exception that a "P" designates a positive bit, and hence a "high" level, and an "N" represents a negative bit, and hence a "low" level.

## Hexadecimal Format

In this format the heading required is identical to the BHLF format but the data is different. Instead of an "S," the hexadecimal

data begins with the SOH or STX character (control A). The data is then represented by the hexadecimal character (0-9 and A-F) which represents the output data of address 0, followed by a space.

Next comes the output data of address 1 followed by a space, etc. The character ETX (control C) is used to end the data. Carriage return and line feed may be included to format the data when the tape is printed.

### Documenting the Design

Along with the opportunity to "design your own chip" comes the responsibility of documenting the device in a way that others can understand it. The reader who has been puzzled by logic diagrams showing PROMs to implement random logic can identify with this problem. The documentation for that PROM was a truth table containing no more than ones and zeros, hardly enough information to quickly figure out the function being performed. Using PALs without proper documentation can cause similar confusion.

Consider the technician on the production floor who is tracing logic faults when he observes a PAL16R8, PAT2719 on his logic schematic. "I wonder what this part does," he says to himself. Adjacent to the 16R8 is a 74LS240 which the technician recalls is a 20 pin octal buffer. He knows this because he looked it up in his TTL Databook, where the *data sheet* told all about the function of an octal buffer. "How can I figure out what a PAT2719 does?" he says. At this point the technician would like to reach for a PAL Databook containing a *data sheet* on the PAL16R8, PAT2719.

### PAL Design Specification

The PAL Design Specification is a recommended *data sheet* format for describing the function of a PAL once it has acquired the unique personality of a particular fuse pattern. A sample PAL Design Specification is shown on the next page. It contains the essential features of a data sheet including 1) Device Name, 2) Pin List, 3) Description, 4) Function Table and 5) Logic Dia-


gram (on additional page). Two additional features not found in conventional data sheets are also included. First, is the author's name and the date. This information is standard on most engineering documents. Second, are the equations which define the PAL transfer function. The equations specify the precise operation of the PAL and, accordingly, are useful in understanding the function. Of higher importance, however, the equations are the key to automating the process of "designing your own chip."

### PALASM

The equations in the PAL Design Specification, along with the PIN List and part number, contain the exact information necessary to generate PAL fuse patterns. Any friendly computer can transform the spec into programming instructions in the form of paper tape or, preferably, RS232C voltage waveforms for no-nonsense direct input to PROM programmers. With a little help from your computer, your PALs can be designed, documented and programmed within minutes.

PALASM, for PAL Assembler, is a Fortran IV program which translates a PAL Design Specification into a PAL Fuse Pattern and PAL Programming Format (BHLF or HEX). PALASM source code is available to users on the following pages. Other source code media is available on request.

 Examples of PALASM output are shown in the Applications section. The flow chart outlines the PALASM operation.





## Sample PAL Design Specification

PAL PART NO. (MUST START AT LINE 1, COLUMN 1)  
 PATTERN NO.  
 NAME OF DEVICE (MUST START ON LINE 3)

```

PALXXXX
PATXXXX
NAME OF DEVICE (EG. CLOCK GENERATOR, PORT ADDRESS DECODER, ETC)
    
```

PAL DESIGN SPECIFICATION  
AUTHOR'S NAME, DATE .....

```

PIN1 PIN2 3 /4 5 6 7 8 9 GND 11 12 13 /14 15 16 /17
18 19 VCC
    
```

PIN LIST (MUST START ON LINE 5)  
CONSISTS OF 20 SYMBOLIC NAMES WHICH  
ARE CONSECUTIVELY ASSIGNED TO  
PINS 1 THRU 20.

```

19 = PIN1*4 + /PIN2
18 = 5 + 6 + 7 + /8 + 9*11
/17 := 8*9
16 = 9*8
IF (PIN1*PIN2) 15 = 3 + 6
/14 = 3+6
IF ( VCC ) 13 = 8*7+PIN2
    
```

} EQUATIONS

### DESCRIPTION:

THIS PARAGRAPH DESCRIBES THE OPERATION OF THE DEVICE. APPLICATIONS INFORMATION MAY ALSO BE PROVIDED.

4


### FUNCTION TABLE

INPUTS		OUTPUTS								OPERATION			
PIN1	PIN2	7	8	9	12	13	14	15	16	17	18	19	
H	L	X	L	L	H	H	L	H	L	H	H	L	CLEAR
.	.	.	.	.	.	.	.	.	.	.	.	.	.
.	.	.	.	.	.	.	.	.	.	.	.	.	.
.	.	.	.	.	.	.	.	.	.	.	.	.	.

SEE DEFINITION OF TERMS FOR FUNCTION TABLE DEFINITIONS

# Design Concepts

## PALASM Flow Chart

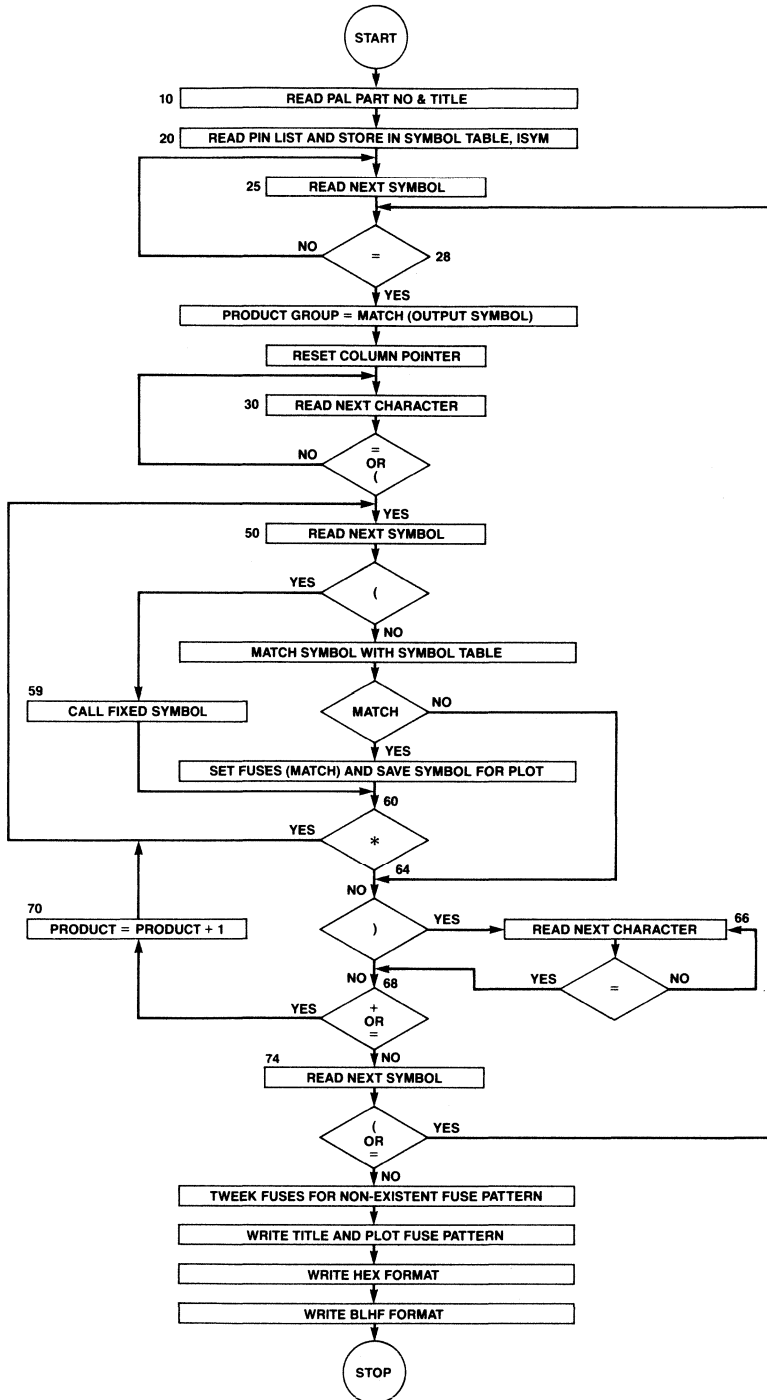

## PALASM Source Code

```

C      P A L A S M - TRANSLATES SYMBOLIC EQUATIONS INTO PAL OBJECT
C      CODE FORMATTED FOR DIRECT INPUT TO STANDARD
C      FROM PROGRAMMERS.
C
C      INPUT:      PAL DESIGN SPECIFICATION ASSIGNED
C                  TO DATA SET REFERENCE NUMBER 1
C                  AND TERMINAL INPUT ASSIGNED TO
C                  DATA SET REFERENCE NUMBER 5
C
C      OUTPUT:     FUSE PATTERN, HEX FORMAT, BHLF
C                  FORMAT, OR BPNF FORMAT ON DATA SET
C                  REFERENCE NUMBER 6
C
C      PART NUMBER: THE PAL PART NUMBER MUST
C                  APPEAR IN COLUMN ONE OF LINE ONE
C
C      PIN LIST:   20 SYMBOLIC PIN NAMES MUST APPEAR
C                  STARTING ON LINE 5
C
C      EQUATIONS:  STARTING FIRST LINE AFTER THE
C                  PIN LIST IN THE FOLLOWING FORMS:
C
C                  A = B♦C + D
C
C                  A := B♦C + D
C
C                  IF( A♦B ) C = D + E
C
C                  A2 := (A1.E0.B1) + /C
C
C                  BLANKS AND COLONS ARE IGNORED
C
C      OPERATORS:  =      EQUALITY
C                  :=     REPLACED BY (AFTER CLOCK)
C                  /      COMPLEMENT
C                  ♦      AND, PRODUCT
C                  +      OR, SUM
C                  :=:    IMPLIED EXCLUSIVE OR
C                  ○      CONDITIONAL THREE-STATE
C                       OR FIXED SYMBOL
C
C      FIXED SYMBOLS
C      FOR PAL16X4
C      AND PAL16A4
C      ONLY:      (AN+/BN)      WHERE N = 0,1,2,3
C                  (AN+BN)      FOR OUTPUT PINS
C                  (AN)         17,16,15,14, RESP
C                  (/AN+/BN)    A IS OUTPUT
C                  (/BN)        B IS INPUT
C                  (AN.NE.BN)
C                  (AN♦/BN)
C                  (/AN+BN)
C                  (AN.E0.BN)
C                  (BN)
C                  (AN♦BN)
C                  (/AN)
C                  (/AN♦/BN)
C                  (/AN♦BN)
C
C      SUBROUTINES: INITLZ,GETSYM,INCR,MATCH,FIXSYM,
C                  TWEEK,PLOT,HEX,BHLF
C
C      FUNCTIONS:  IXLATE
C
C      REV LEVEL:  D 5/7/78 JB
C
C      NOTES:      THE SOURCE CODE AS PRINTED HERE
C                  PRODUCED THE OBJECT CODE OF THE
C                  EXAMPLES IN THE APPLICATIONS
C                  SECTION ON A NATIONAL CSS IBM
C                  SYSTEM/370 FORTRAN IV(G).

```

**PALASM Source Code**

```

C     MAIN PROGRAM
C
COMMON  LBLANK,LLEFT,LAND,LDR,LSLASH,LEQUAL,LRIGHT
LOGICAL LBLANK,LLEFT,LAND,LDR,LSLASH,LEQUAL,LRIGHT,LFIRST,LFIX
LOGICAL LFUSES(32,64),LPHASE(20),LBUF(20),LMATCH
INTEGER  TITLE(80),ILINE(80),ICOLUM,ISYM(8,20),IBUF(8,20),L,H,N,P
DATA  LFUSES/2048*.FALSE./,ICOLUM/0/,L/L//,R/R//,X/X//,A/A//
C
READ(1,10) INDAI,IOT,INOD,TITLE,ILINE
10  FORMAT(3X,I2,A1,I1,/,/,80A1,/,/,80A1)
CALL INITLZ(INDAI,IOT,INOD,ITYPE,LFUSES,ILINE,ICOLUM)
DO 20 J=1,20
20  CALL GETSYM(LPHASE,ISYM,J,ILINE,ICOLUM,LFIX)
25  CALL GETSYM(LBUF,IBUF,1,ILINE,ICOLUM,LFIX)
28  IF(.NOT.LEQUAL) GO TO 25
    CALL MATCH(IMATCH,IBUF,ISYM)
    IF( (IMATCH.LT.12) .OR. (IMATCH.GT.19) ) GO TO 100
    I88PRD=(19-IMATCH)*8 + 1
    ICOLUM=0
30  CALL INCR(ILINE,ICOLUM)
    IF(.NOT. ( LEQUAL.OR.LLEFT ) ) GO TO 30
DO 70 I88PRD=1,16
    IPRD = I88PRD + I88PRD - 1
    LFIRST=.TRUE.
50  CALL GETSYM(LBUF,IBUF,1,ILINE,ICOLUM,LFIX)
    IF(LFIX) GO TO 59
    CALL MATCH(IMATCH,IBUF,ISYM)
    IF( (IMATCH.EQ.0) .OR. (IMATCH.EQ.10) ) GO TO 64
    IF(.NOT.LFIRST) GO TO 58
        LFIRST=.FALSE.
        DO 56 I=1,32
56         LFUSES(I,IPRD)=.TRUE.
58     IBUBL=0
        IF((( LPHASE(IMATCH)).AND.(.NOT.LBUF(1))) .OR.
C         ((.NOT.LPHASE(IMATCH)).AND.( LBUF(1)))) IBUBL=1
        IINPUT=IXLATE(IMATCH,ITYPE)+IBUBL
        IF(IINPUT.LE.0) GO TO 60
        LFUSES(IINPUT,IPRD)=.FALSE.
        CALL PLOT(LBUF,IBUF,LFUSES,IPRD,TITLE,.FALSE.)
        GO TO 60
59     CALL FIXSYM(LBUF,IBUF,ILINE,ICOLUM,LFIRST,LFUSES,IPRD)
60     IF(LAND) GO TO 50
64     IF(.NOT.LRIGHT) GO TO 68
66     CALL INCR(ILINE,ICOLUM)
        IF(.NOT.LEQUAL) GO TO 66
68     IF(.NOT. (LDR.OR.LEQUAL) ) GO TO 74
70     CONTINUE
74     CALL GETSYM(LBUF,IBUF,1,ILINE,ICOLUM,LFIX)
        IF(LLEFT.OR.LEQUAL) GO TO 28
100 IF(ITYPE.LE.4) CALL TWEED(ITYPE,IOT,LFUSES)
105 WRITE(6,110)
110 FORMAT(' OUTPUT ? PLOT=P HEX=H BHALF=L BPNF=N QUIT=Q')
READ(5,120) I
120 FORMAT(1A1)
    IF(I.EQ.P) CALL PLOT(LBUF,IBUF,LFUSES,IPRD,TITLE,.TRUE.)
    IF(I.EQ.H) CALL HEX(LFUSES)
    IF(I.EQ.L) CALL BHALF(LFUSES,H,L)
    IF(I.EQ.N) CALL BHALF(LFUSES,P,N)
    IF( (I.EQ.P).OR.(I.EQ.H).OR.(I.EQ.L).OR.(I.EQ.N) ) GO TO 105
STOP
END
C
C.....
C
SUBROUTINE INITLZ(INDAI,IOT,INOD,ITYPE,LFUSES,ILINE,ICOLUM)
INTEGER L,R,X,A
DATA L/L//,R/R//,X/X//,A/A//
IF( INDAI .LT. 16 ) ITYPE = (INDAI/2) - 4
IF( (INDAI .EQ. 16) .AND. (INOD .EQ. 2) ) ITYPE = 4
IF( (INDAI .EQ. 16) .AND. (INOD .EQ. 1) ) ITYPE = 4
IF( (INDAI .EQ. 16) .AND. (IOT .EQ. L) ) ITYPE = 5
IF( (IOT .EQ. R) .OR. (IOT .EQ. A) .OR. (IOT .EQ. X) ) ITYPE = 6
CALL INCR(ILINE,ICOLUM)
RETURN
END

```

**PALASM Source Code**

```

SUBROUTINE GETSYM(LPHASE, ISYM, J, ILINE, ICOLUM, LFIX)
COMMON  LBLANK, LLEFT, LAND, LOR, LSLASH, LEQUAL, LRIGHT
LOGICAL LBLANK, LLEFT, LAND, LOR, LSLASH, LEQUAL, LRIGHT
INTEGER ILINE(80), ISYM(8,20), IBLANK
DATA IBLANK// //
LFIX=.FALSE.
IF( (.NOT. (LLEFT.OR.LAND.OR.LOR.OR.LEQUAL.OR.LRIGHT) ) ) GO TO 10
CALL INCR(ILINE, ICOLUM)
IF(LLEFT) GO TO 60
10 LPHASE(J)=(.NOT. LSLASH )
IF(LPHASE(J)) GO TO 15
CALL INCR(ILINE, ICOLUM)
15 DO 20 I=1,8
20   ISYM(I, J)=IBLANK
25 DO 30 I=1,7
30   ISYM(I, J)=ISYM(I+1, J)
   ISYM(8, J)=ILINE(ICOLUM)
   CALL INCR(ILINE, ICOLUM)
   IF( LLEFT.OR.LBLANK.OR.LAND.OR.LOR.OR.LRIGHT.OR.LEQUAL ) GO TO 40
   GO TO 25
40 CONTINUE
C   WRITE(6,50) (ISYM(I, J), I=1,8)
C 50 FORMAT(' ',8A1)
RETURN
60 LFIX=.TRUE.
RETURN
END

C
C*****
C
SUBROUTINE INCR(ICOLM)
COMMON  LBLANK, LLEFT, LAND, LOR, LSLASH, LEQUAL, LRIGHT
LOGICAL LBLANK, LLEFT, LAND, LOR, LSLASH, LEQUAL, LRIGHT
INTEGER ILINE(80), IBLANK, ILEFT, IAND, IOR, ISLASH, IEQUAL, IRIGHT,
C   ICOLM
DATA IBLANK// //, ILEFT// //, IAND// //, IOR// //,
C   ISLASH// //, IEQUAL// //, IRIGHT// //, ICOLM// //
LBLANK=.FALSE.
10 ICOLM=ICOLM+1
IF(ICOLM.LE.79) GO TO 30
READ(1,20,ERR=60,END=60) ILINE
ICOLM=1
20 FORMAT(80A1)
30 IF( ILINE(ICOLM) .EQ. IBLANK ) LBLANK=.TRUE.
IF( ( ILINE(ICOLM) .EQ. IBLANK ) .OR. ( ILINE(ICOLM) .EQ. ICOLM ) )
C GO TO 10
LLEFT =( ILINE(ICOLM) .EQ. ILEFT )
LAND  =( ILINE(ICOLM) .EQ. IAND )
LOR   =( ILINE(ICOLM) .EQ. IOR )
LSLASH=( ILINE(ICOLM) .EQ. ISLASH)
LEQUAL=( ILINE(ICOLM) .EQ. IEQUAL)
LRIGHT=( ILINE(ICOLM) .EQ. IRIGHT)
C   WRITE(6,50) ILINE(ICOLM)
C 50 FORMAT(' ',1A1)
60 RETURN
END

C
C*****
C
SUBROUTINE MATCH(IMATCH, IBUF, ISYM)
INTEGER IBUF(8,20), ISYM(8,20)
LOGICAL LMATCH
IMATCH=0
DO 20 J=1,20
LMATCH=.TRUE.
DO 10 I=1,8
10 LMATCH=LMATCH.AND. (IBUF(I,1) .EQ. ISYM(I, J))
IF(LMATCH) IMATCH=J
20 CONTINUE
RETURN
END

```



## PALASM Source Code

```

SUBROUTINE PLOT(LBUF,IBUF,LFUSES,IPROD,TITLE,LDUMP)
INTEGER IBUF(8,20),IOUT(64),IBLANK,IAND,IOR,ISLASH,IDASH,X
C   ISAVE(64,32),TITLE(80)
DATA IBLANK////,IAND//◆//,ISAVE/2048◆//,
C   IOR//+//,ISLASH////,X//X//,IDASH//--//
LOGICAL LBUF(20),LFUSES(32,64),LDUMP
IF(LDUMP) GO TO 60
IF(ISAVE(IPROD,1).NE.IBLANK) RETURN
IF(LBUF(1) ) GO TO 5
DO 30 J=1,31
20   ISAVE(IPROD,J)=ISAVE(IPROD,J+1)
   ISAVE(IPROD,32)=ISLASH
5   DO 20 I=1,8
   IF( ISAVE(IPROD,I).NE.IBLANK ) RETURN
   IF( IBUF(I,1) .EQ. IBLANK ) GO TO 20
   DO 10 J=1,31
10    ISAVE(IPROD,J)=ISAVE(IPROD,J+1)
   ISAVE(IPROD,32)=IBUF(I,1)
20    CONTINUE
IF(ISAVE(IPROD,1).NE.IBLANK) RETURN
40 DO 50 J=1,31
50    ISAVE(IPROD,J)=ISAVE(IPROD,J+1)
   ISAVE(IPROD,32)=IAND
   RETURN
60 WRITE(6,62) TITLE
62 FORMAT(////,80A1,/)
DO 100 I88PRO=1,57,8
   DO 94 I8PRO=1,8
   IPROD=I88PRO+I8PRO-1
   ISAVE(IPROD,32)=IBLANK
   DO 70 I=1,32
   IF( ISAVE(IPROD,I) .NE. IBLANK ) GO TO 70
   DO 65 J=1,31
   ISAVE(IPROD,J)=ISAVE(IPROD,J+1)
   ISAVE(IPROD,32)=IBLANK
70    CONTINUE
   DO 80 I=1,32
   IOUT(I)=X
   IF( LFUSES(I,IPROD) ) IOUT(I)=IDASH
   IOUT(I+32)=ISAVE(IPROD,I)
80    CONTINUE
   WRITE(6,90) IOUT
90    FORMAT(8(//,4A1),//,32A1)
94    CONTINUE
   WRITE(6,96)
96    FORMAT(1X)
100   CONTINUE
RETURN
END
C
C.....
C
SUBROUTINE HEX(LFUSES)
LOGICAL LFUSES(32,64)
INTEGER ITEMP(32)
DATA BYP/224000000//,STX/240000000//,BELL/2E0E0E0E0/
WRITE(6,10)
10 FORMAT(//,/)
C***** NOTE: SOME FROM PROGRAMMERS NEED A START CHARACTER.
C***** THIS PROGRAM OUTPUTS AN STX FOR THE DATA I/O MODEL 9
C***** VIA A BYPASS CODE (BYP). (USE SOH FOR MODEL 5)
WRITE(6,5) BYP,BELL,BELL,BELL,BELL,BELL,BELL,BELL,BELL,BELL,STX
5 FORMAT(11A1)
DO 40 I=1,32,32
INC=I-1
DO 40 IPROD=1,8
DO 20 IINPUT=1,32
IHEX=0
IF(LFUSES(IINPUT,IPROD+ 0+INC)) IHEX=IHEX+1
IF(LFUSES(IINPUT,IPROD+ 8+INC)) IHEX=IHEX+2
IF(LFUSES(IINPUT,IPROD+16+INC)) IHEX=IHEX+4
IF(LFUSES(IINPUT,IPROD+24+INC)) IHEX=IHEX+8
20   ITEMP(IINPUT)=IHEX
40   WRITE(6,60) ITEMP
60   FORMAT(//,32(Z1,/,),/,)
WRITE(6,10)
RETURN
END

```

**PALASM Source Code**

```

SUBROUTINE TWEAK(ITYPE,IOT,LFUSES)
  INTEGER L,C
  LOGICAL LFUSES(32,64)
  DATA L//L//,C//C//
  IF(ITYPE.GE.4) GO TO 20
  DO 10 IPRD=1,64
    LFUSES(15,IPRD)=.TRUE.
    LFUSES(16,IPRD)=.TRUE.
    LFUSES(19,IPRD)=.TRUE.
    LFUSES(20,IPRD)=.TRUE.
    IF(ITYPE.GE.3) GO TO 10
    LFUSES(11,IPRD)=.TRUE.
    LFUSES(12,IPRD)=.TRUE.
    LFUSES(23,IPRD)=.TRUE.
    LFUSES(24,IPRD)=.TRUE.
    IF(ITYPE.GE.2) GO TO 10
    LFUSES( 7,IPRD)=.TRUE.
    LFUSES( 8,IPRD)=.TRUE.
    LFUSES(27,IPRD)=.TRUE.
    LFUSES(28,IPRD)=.TRUE.
  10  CONTINUE
  20  IF( ITYPE.EQ.1 ) GO TO 100
    DO 99 IINPUT=1,32
      DO 30 IPRD=1,8
        LFUSES(IINPUT,IPRD+ 0)= (IOT.NE.L)
        IF(IOT.NE.C) LFUSES(IINPUT,IPRD+56)= (IOT.NE.L)
      30  IF(ITYPE.LE.2) GO TO 99
        DO 40 IPRD=1,8
          LFUSES(IINPUT,IPRD+ 8)= (IOT.NE.L)
          IF(IOT.NE.C) LFUSES(IINPUT,IPRD+48)= (IOT.NE.L)
        40  IF(ITYPE.LE.3) GO TO 99
        DO 50 IPRD=1,8
          LFUSES(IINPUT,IPRD+16)= (IOT.NE.L)
          IF(IOT.NE.C) LFUSES(IINPUT,IPRD+40)= (IOT.NE.L)
        50  CONTINUE
      99  CONTINUE
  100  RETURN
      END
C
C*****
C
SUBROUTINE BHLF(LFUSES,H,L)
  LOGICAL LFUSES(32,64)
  INTEGER ITEMP(4,8),L,H
  WRITE(6,10)
  10  FORMAT(//,/,/,/)
  DO 20 I=1,32,32
    INC=I-1
    DO 20 IPRD=1,8
      DO 20 J=1,25,8
        DO 15 K=1,8
          IINPUT=J+K-1
          ITEMP(1,K)=L
          ITEMP(2,K)=L
          ITEMP(3,K)=L
          ITEMP(4,K)=L
          IF(LFUSES(IINPUT,IPRD+ 0+INC)) ITEMP(4,K)=H
          IF(LFUSES(IINPUT,IPRD+ 8+INC)) ITEMP(3,K)=H
          IF(LFUSES(IINPUT,IPRD+16+INC)) ITEMP(2,K)=H
          IF(LFUSES(IINPUT,IPRD+24+INC)) ITEMP(1,K)=H
        15  CONTINUE
      20  WRITE(6,30) ITEMP
    30  FORMAT(//,8('B',4A1,'F '))
  WRITE(6,10)
  RETURN
  END

```












 

<b>Introduction</b>	<b>1</b>
<b>Reliability</b>	<b>2</b>
<b>PAL Family Data Sheet</b>	<b>3</b>
<b>Design Concept</b>	<b>4</b>
<b>Applications</b>	<b>5</b>
<b>Representatives/Distributors</b>	<b>6</b>

# Applications Contents

Basic Gate Examples .....	PAL10H8 .....	5-3
Control Store Sequencer .....	PAL16R4,16R6 .....	5-9
Memory Interface Logic for 6800 .....	PAL10L8 .....	5-18
Dual I/O Port Decoder for S100 Bus .....	PAL12L6 .....	5-24
Memory Mapped I/O .....	PAL16L2 .....	5-30
8080 Control Logic For CPU Board .....	PAL16L8,12H6 ..	5-35
Hexadecimal Decoder Lamp Driver .....	PAL16L8 .....	5-42
Hex Keyboard Scanner .....	PAL16R4 .....	5-49
Micro Floppy Control Logic .....	PAL14H4 .....	5-55
Between Limits Comparator .....	PAL16X4,16C1 ..	5-59
Binary to BCD Converter .....	PAL16R8 .....	5-67
Electronic Dice Game .....	PAL16R8 .....	5-73
Three Phase Micro Engine .....	PAL16R8 .....	5-90
Priority Encoder with Register .....	PAL16R4 .....	5-92
Quadruple 3-Line-1-Line Data Selector .....	PAL14H4 .....	5-94
4-Bit Counter with Mux .....	PAL16R4 .....	5-96
6-Bit Shift Register .....	PAL16R6 .....	5-98
8-Bit Counter .....	PAL16R8 .....	5-100
Programmer Output Driver .....	PAL16L8 .....	5-102
24-Bit Fast Look-Ahead Carry Generator .....	PAL16L8 .....	5-104
4-Bit Up/Down Counter With Shift .....	PAL16X4 .....	5-106
ALU Accumulator .....	PAL16A4 .....	5-108

## Introduction to PAL Applications

The PAL family brings a unique flexibility to the field of logic design. Using PALs, designers can both replace conventional logic in existing products and optimize the design of new products. Previous sections discussed the PAL concept and provided information on the advantages gained and the techniques used when designing with PALs. This section shows PALs at work in applications ranging from simple logic gate replacement to complex control sequencers.

Each example is presented as a complete PAL design. The required logic function is described, the PAL that best solves the problem is selected, and the actual PAL logic implementation is shown. The PAL logic is shown as both the PAL design specification and the actual PALASM output for the PAL programmer. This makes the examples complete enough to serve as guides for designers using PALs in their own systems.

The PAL is a versatile device whose applications are practically unlimited. These applications examples, combined with the PAL design information contained in the rest of this book, will help designers to get the feel of PAL design procedures. With a little practice and study, PAL design will become a natural extension of the normal logic design process.

# Applications

## Basic Gate Examples



5

*The members of the PAL family are ideal for direct replacement of much combinatorial logic in many conventional designs. The ease with which PAL inputs and outputs can be programmed makes them a natural for use in applications where a small number of SSI/MSI logic functions are required. This section presents simple gate-for-gate logic function replacements using PALs. Later sections show how entire logic functions can be replaced using single PALs.*

**Example Gates No. 1**

PAL10H8  
 PAT0025  
 EXAMPLE GATES NO. 1

**Design Specification PAL10H8**


PAL DESIGN SPECIFICATION  
 JOHN DOE 12/10/77

A C E F H I K L N GND O NOTUSED NOTUSED P M J G D B VCC

$B = A$



$D = \neg C$

 

$G = E \cdot F$



$J = H + I$



$M = \neg K + \neg L$




$P = \neg N \cdot \neg O$



 **DESCRIPTION:**

THE EXAMPLE GATES DEMONSTRATE HOW FUSABLE LOGIC CAN IMPLEMENT THE BASIC BUFFER, INVERTER, AND, OR, NAND, NOR, FUNCTIONS. NOTE THE ONE FOR ONE CORRESPONDENCE BETWEEN CONVENTIONAL LOGIC SYMBOLY AND PAL LOGIC SYMBOLY




**Logic Symbol**



Example Gates No. 1

Logic Diagram PAL10H8

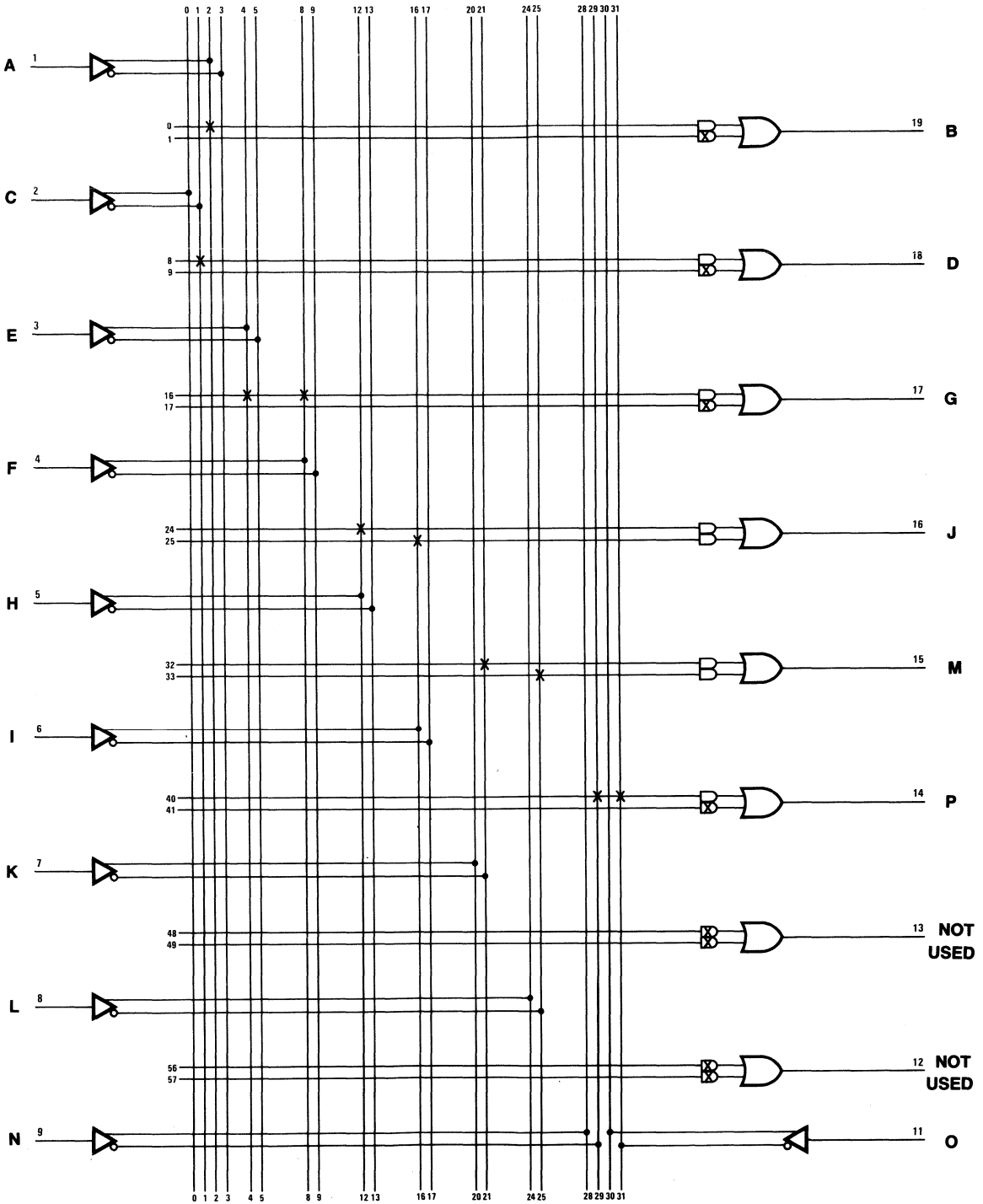

5

**Example Gates No. 2**

**Design Specification PAL10H8**

PAL10H8  
 PAT0025  
 EXAMPLE GATES NO. 2

PAL DESIGN SPECIFICATION  
 JOHN DOE 12/10/77

A B D E G H J K NC GND NC NC L NC I NC F NC C VCC

$C = A \cdot \overline{B}$



$F = D + \overline{E}$



$I = G \cdot \overline{H} + \overline{G} \cdot H$




$L = J \cdot K + \overline{J} \cdot \overline{K}$



 **DESCRIPTION:**


THE EXAMPLE GATES DEMONSTRATE HOW FUSABLE LOGIC CAN IMPLEMENT NON-STANDARD GATE FUNCTIONS AND ALSO THE EXCLUSIVE OR/NOR FUNCTIONS. NOTE THE ONE FOR ONE CORRESPONDENCE BETWEEN CONVENTIONAL LOGIC SYMBOLY AND PAL LOGIC SYMBOLY.



**Logic Symbol**

Example Gates No. 2

Logic Diagram PAL10H8

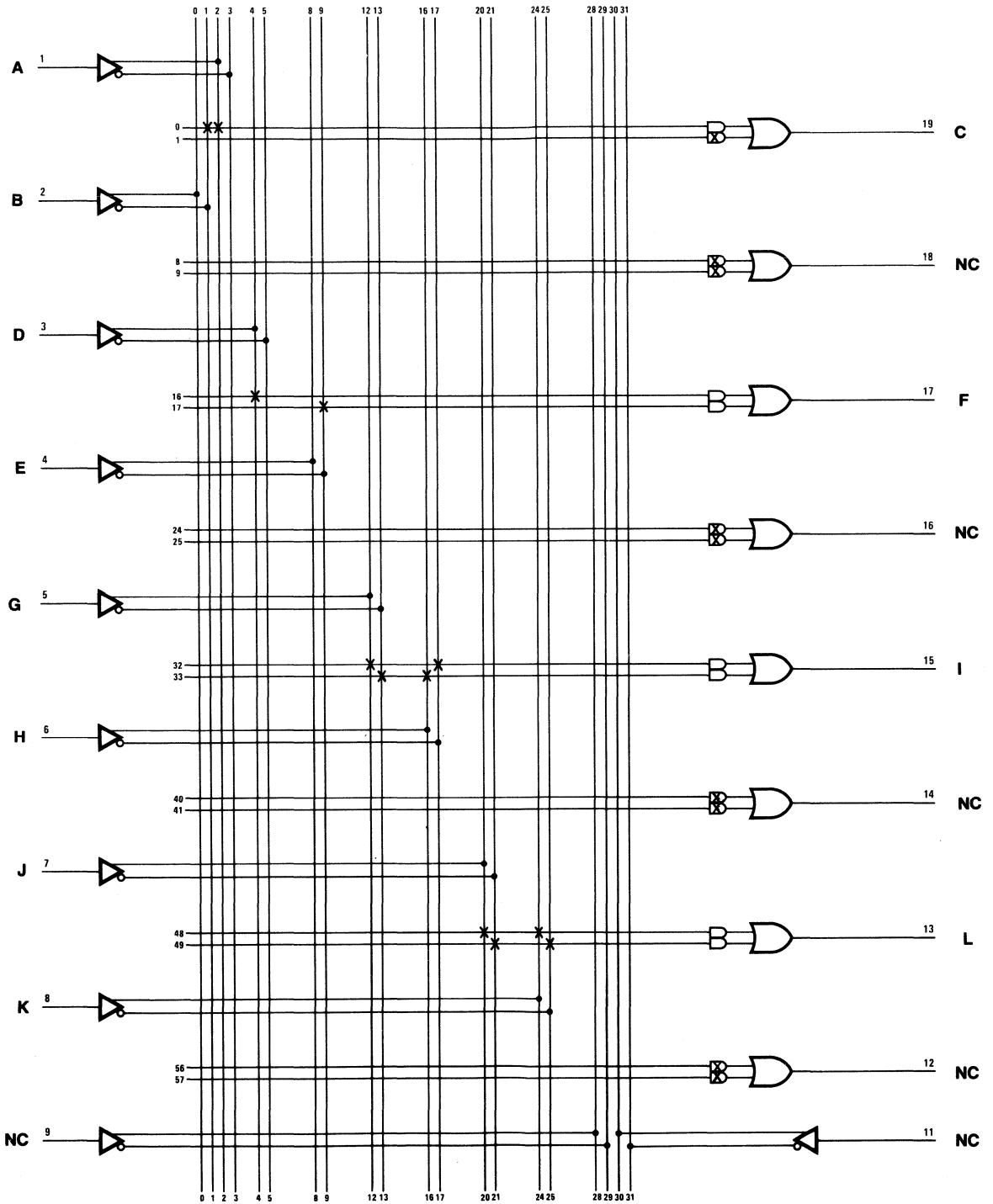


5



# Applications

## Control Store Sequencer

 

5

*Solutions to Control Store Sequencing are as varied as the problems that are solved by micro-programmed hardware. Where an engineer goes to his "ALU Book" to choose the appropriate device for his design, he is much less likely to use his "Sequencer Book" to select that function. Rather, he builds the function from standard MSI and SSI devices. Devices from the "Sequencer Book" tend to require very horizontal control store structures, however they lack the speed which a designer is usually trying to achieve with a horizontal control store.*

*The sequencer described in this application is designed for use with a vertical control store structure. The vertical control store has narrow control fields and may share field functions to increase field use efficiency. Designs that are built around vertical control stores are useful in applications where events occur at intervals in the microsecond range.*

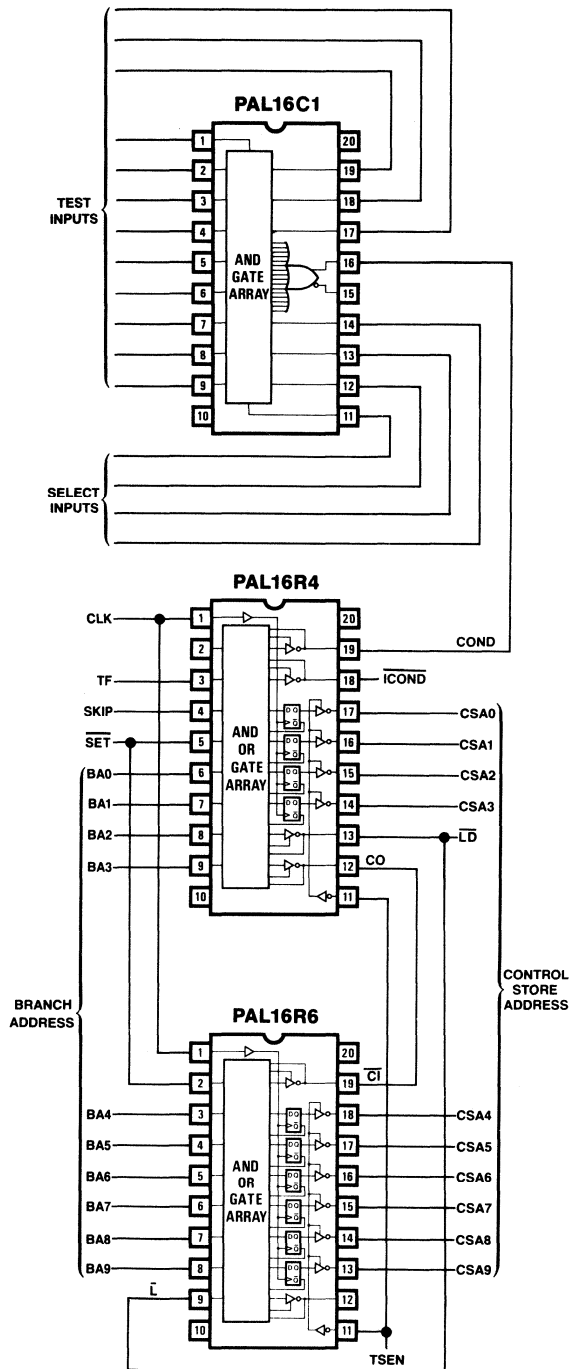


Figure 1

## Functional Description

This Control Store Sequencer is designed to use a minimum of control bits while providing sufficient sequencing flexibility. Only three bits are required for the basic sequencer control. The three bits combine to perform the following operations:

- CSA = CSA + 1    Increment the control store address;
- CSA = CSA + 2    Skip the next control store address; this is a simple form of branch capability; or
- CSA = BA        Load a branch address.

The three control bits are SKIP, COND, and TF. SKIP defines whether the sequencer will skip or load. COND is the condition which is tested to determine if the sequencer executes the operation defined by SKIP; and TF defines whether COND is tested true or false. Table 1 defines the sequencer operation.

SKIP	COND	TF	OPERATION
0	0	0	Load
0	0	1	Increment
0	1	0	Increment
0	1	1	Load
1	0	0	Skip
1	0	1	Increment
1	1	0	Increment
1	1	1	Skip

**Table 1.**

There are two additional control bits which are left to the user's discretion. They are  $\overline{SET}$  and  $\overline{TSEN}$ .  $\overline{SET}$  is a synchronous preset which is typically used as a power-on set; however it may also be used as a one-bit vector to the last addressable location during normal operation.  $\overline{TSEN}$  is the enable for the three-state outputs. This has several possible uses, such as a method of testing the hardware. The sequencer outputs are disabled and a test address is supplied from an external source.

The ten-bit sequencer is divided into two parts. The least significant four bits is constructed from a PAL16R4 and is the heart of the skip operation. During the skip operation the state of the least significant bit is maintained and the next three bits function as a three-bit binary counter, while during the increment operation the least significant four bits function as a four-bit binary counter. Carry out ( $\overline{CO}$ ) is generated during skip when CSA1 thru CSA3 equal 1, and during increment when CSA0 thru CSA3 equal 1.  $\overline{LD}$  is also generated by the least significant part and is a function of SKIP, TF, and COND. If SKIP equal one,  $\overline{LD}$  equal one; if SKIP equal zero, see Table 2.

The most significant six-bits is constructed from a PAL16R6 and is merely a six-bit binary counter with carry in (CI), synchronous load (LD) and synchronous set ( $\overline{SET}$ ). There is also an extra pin which may be used to generate carryout if it is desirable to expand beyond ten-bits.


TF	COND	$\overline{LD}$
0	0	0
0	1	1
1	0	1
1	1	0

**Table 2.**

## System Integration

One of the first features that is desirable from a system standpoint is the expansion of the COND input, so that more than one condition is available for testing. This is accomplished nicely by using a PAL16C1 as a multiplexer. Four terms are used as input selects. This leaves twelve terms which are used for condition inputs. At first this may seem wasteful as the four select terms can decode sixteen inputs. This is only superficial as the PAL allows the designer a degree of flexibility not found in a standard mux. One COND output should be either TRUE or FALSE in order to generate unconditional increments, skips, and branches. TRUE or FALSE needs only to be a function of the four select terms and does not require a condition input to be grounded or pulled up to  $V_{CC}$ . Other functions which the PAL multiplexer performs nicely is the AND, OR, or EXCLUSIVE OR of the condition inputs; functions which must be done externally with a standard multiplexer.

A function which at first glance appears to be missing is subroutine capability. The figure shows how the sequencer can be integrated into a system to provide subroutine capability.

 

**Figure 2**

In Figure 2 the same control store field is used to generate literals and branch addresses. Subroutining is accomplished by loading the return address in the register file before the subroutine jump is taken and then reading the return address out of the file when the subroutine return is executed.

## Conclusion

The PAL SEQUENCER is an example of the flexibility which previously was achieved only by the design of custom devices. In the design shown here, SKIP is just as easily defined as CSA = CSA + 4. The SKIP function can also be redefined to be a short branch; retain the state of the upper six bits and load the least significant four bits. The challenge of the PAL Family is not the integration of standard MSI and SSI functions but the direct implementation of system functions.

Control Store Sequencer, Least Significant Stage

Design Specification PAL16R4

PAL16R4

PAL DESIGN SPECIFICATION

PAT0028

BILL BLACK 12/14/77

CONTROL STORE SEQUENCER, LEAST SIGNIFICANT STAGE

CLK NC TF SKIP /SET BA0 BA1 BA2 BA3 GND /TSEN /CO /LD

CSA3 CSA2 CSA1 CSA0 /ICOND COND VCC

$$\overline{\text{CSA0}} := \overline{\text{SET}} \cdot \overline{\text{ICOND}} \cdot \text{CSA0} + \overline{\text{SET}} \cdot \overline{\text{ICOND}} \cdot \text{SKIP} \cdot \overline{\text{CSA0}} + \overline{\text{SET}} \cdot \overline{\text{ICOND}} \cdot \overline{\text{SKIP}} \cdot \overline{\text{BA0}}$$

$$\overline{\text{CSA1}} := \overline{\text{SET}} \cdot \text{CSA0} \cdot \text{CSA1} \cdot \overline{\text{ICOND}} + \overline{\text{SET}} \cdot \overline{\text{ICOND}} \cdot \overline{\text{CSA0}} \cdot \overline{\text{CSA1}} + \overline{\text{SET}} \cdot \overline{\text{ICOND}} \cdot \text{SKIP} \cdot \text{CSA1} + \overline{\text{SET}} \cdot \overline{\text{ICOND}} \cdot \overline{\text{SKIP}} \cdot \overline{\text{BA2}}$$

$$\overline{\text{CSA2}} := \overline{\text{SET}} \cdot \overline{\text{ICOND}} \cdot \text{CSA0} \cdot \text{CSA1} \cdot \text{CSA2} + \overline{\text{SET}} \cdot \overline{\text{ICOND}} \cdot \overline{\text{CSA0}} \cdot \overline{\text{CSA2}} + \overline{\text{SET}} \cdot \overline{\text{LD}} \cdot \overline{\text{CSA1}} \cdot \overline{\text{CSA2}} + \overline{\text{SET}} \cdot \overline{\text{ICOND}} \cdot \text{SKIP} \cdot \text{CSA1} \cdot \text{CSA2} + \overline{\text{SET}} \cdot \overline{\text{ICOND}} \cdot \overline{\text{SKIP}} \cdot \overline{\text{BA2}}$$


$$\overline{\text{CSA3}} := \overline{\text{SET}} \cdot \overline{\text{ICOND}} \cdot \text{CSA0} \cdot \text{CSA1} \cdot \text{CSA2} \cdot \text{CSA3} + \overline{\text{SET}} \cdot \overline{\text{ICOND}} \cdot \overline{\text{CSA0}} \cdot \overline{\text{CSA3}} + \overline{\text{SET}} \cdot \overline{\text{LD}} \cdot \overline{\text{CSA1}} \cdot \overline{\text{CSA3}} + \overline{\text{SET}} \cdot \overline{\text{LD}} \cdot \overline{\text{CSA2}} \cdot \overline{\text{CSA3}} + \overline{\text{SET}} \cdot \overline{\text{ICOND}} \cdot \text{SKIP} \cdot \text{CSA1} \cdot \text{CSA2} \cdot \text{CSA3} + \overline{\text{SET}} \cdot \overline{\text{ICOND}} \cdot \overline{\text{SKIP}} \cdot \overline{\text{BA3}}$$

$$\text{IF (VCC) } \text{CO} = \text{CSA0} \cdot \text{CSA1} \cdot \text{CSA2} \cdot \text{CSA3} + \text{TF} \cdot \overline{\text{COND}} \cdot \text{SKIP} \cdot \text{CSA1} \cdot \text{CSA2} \cdot \text{CSA3} + \overline{\text{TF}} \cdot \overline{\text{COND}} \cdot \text{SKIP} \cdot \text{CSA1} \cdot \text{CSA2} \cdot \text{CSA3}$$

$$\text{IF (VCC) } \text{ICOND} = \text{TF} \cdot \overline{\text{COND}} + \overline{\text{TF}} \cdot \overline{\text{COND}}$$

$$\text{IF (VCC) } \text{LD} = \text{TF} \cdot \overline{\text{COND}} \cdot \overline{\text{SKIP}} + \overline{\text{TF}} \cdot \overline{\text{COND}} \cdot \overline{\text{SKIP}}$$

DESCRIPTION: SEE TEXT

 


Logic Symbol





Control Store Sequencer, Least Significant Stage

Logic Diagram PAL16R4

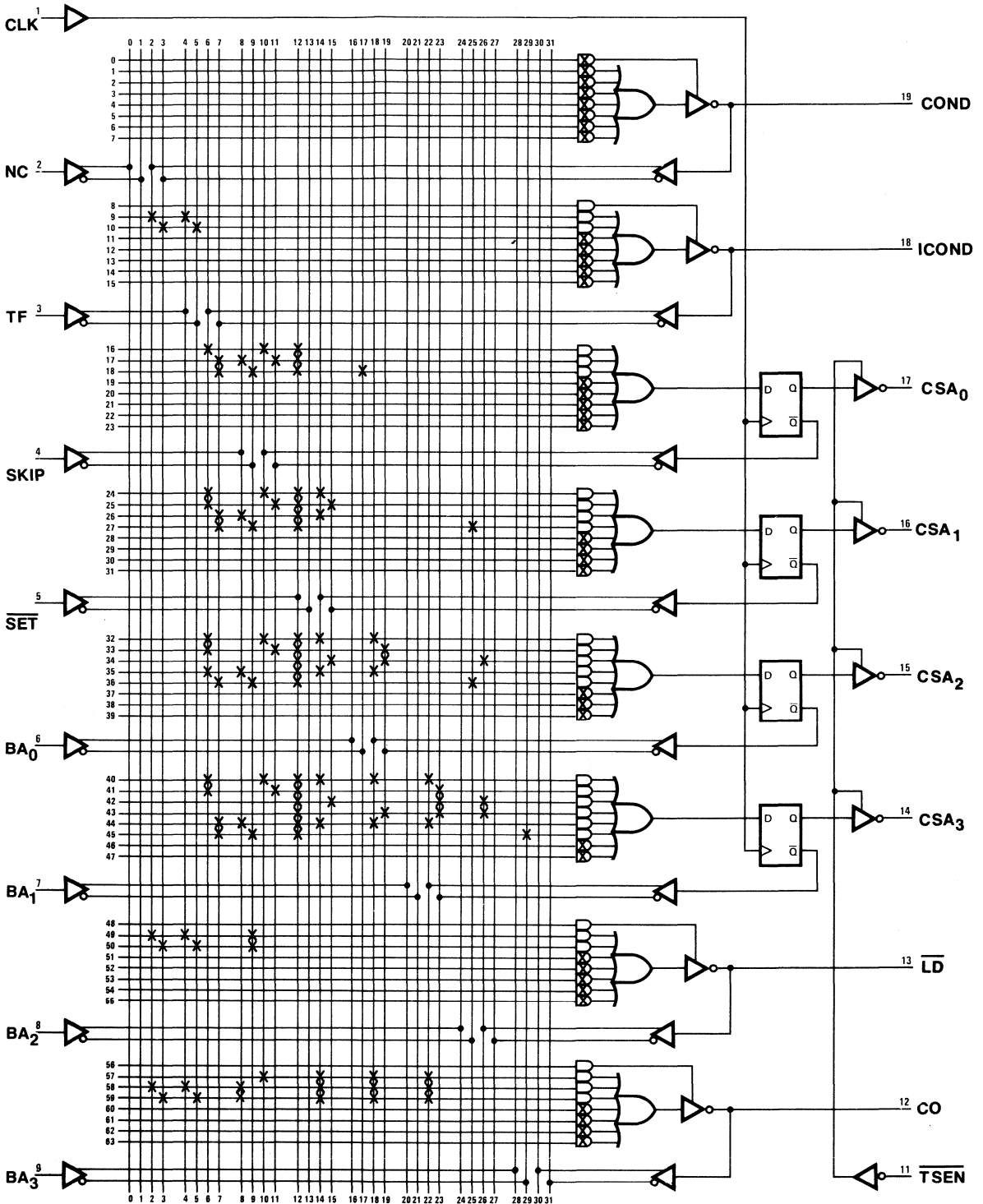

**Control Store Sequencer, Most Significant Stage**

**Design Specification PAL16R6**

PAL16R6

PAL DESIGN SPECIFICATION

PAT0029

BILL BLACK 12/14/77

CONTROL STORE SEQUENCER, MOST SIGNIFICANT STAGE

CLK /SET BA4 BA5 BA6 BA7 BA8 BA9 /LD GND /TSEN NC CSA9 CSA8 CSA7 CSA6  
CSA5 CSA4 /CI VCC

$\overline{\text{CSA4}} := \overline{\text{SET}} \cdot \overline{\text{CSA4}} \cdot \overline{\text{CI}} \cdot \overline{\text{LD}} + \overline{\text{CSA4}} \cdot \overline{\text{CI}} \cdot \overline{\text{LD}} \cdot \overline{\text{SET}} + \overline{\text{SET}} \cdot \overline{\text{LD}} \cdot \overline{\text{BA4}}$

$\overline{\text{CSA5}} := \overline{\text{SET}} \cdot \overline{\text{CSA4}} \cdot \overline{\text{CSA5}} \cdot \overline{\text{CI}} \cdot \overline{\text{LD}} + \overline{\text{SET}} \cdot \overline{\text{CSA5}} \cdot \overline{\text{CI}} \cdot \overline{\text{LD}}$   
 $+ \overline{\text{SET}} \cdot \overline{\text{CSA4}} \cdot \overline{\text{CSA5}} \cdot \overline{\text{LD}} + \overline{\text{SET}} \cdot \overline{\text{LD}} \cdot \overline{\text{BA5}}$

$\overline{\text{CSA6}} := \overline{\text{SET}} \cdot \overline{\text{CSA4}} \cdot \overline{\text{CSA5}} \cdot \overline{\text{CSA6}} \cdot \overline{\text{CI}} \cdot \overline{\text{LD}} + \overline{\text{SET}} \cdot \overline{\text{CSA6}} \cdot \overline{\text{CI}} \cdot \overline{\text{LD}}$   
 $+ \overline{\text{CSA4}} \cdot \overline{\text{CSA6}} \cdot \overline{\text{LD}} \cdot \overline{\text{SET}} + \overline{\text{SET}} \cdot \overline{\text{CSA5}} \cdot \overline{\text{CSA6}} \cdot \overline{\text{LD}}$   
 $+ \overline{\text{SET}} \cdot \overline{\text{LD}} \cdot \overline{\text{BA6}}$

$\overline{\text{CSA7}} := \overline{\text{SET}} \cdot \overline{\text{CSA4}} \cdot \overline{\text{CSA5}} \cdot \overline{\text{CSA6}} \cdot \overline{\text{CSA7}} \cdot \overline{\text{CI}} \cdot \overline{\text{LD}}$   
 $+ \overline{\text{SET}} \cdot \overline{\text{CSA7}} \cdot \overline{\text{CI}} \cdot \overline{\text{LD}} + \overline{\text{SET}} \cdot \overline{\text{CSA4}} \cdot \overline{\text{CSA7}} \cdot \overline{\text{LD}}$   
 $+ \overline{\text{SET}} \cdot \overline{\text{CSA5}} \cdot \overline{\text{CSA7}} \cdot \overline{\text{LD}} + \overline{\text{SET}} \cdot \overline{\text{CSA6}} \cdot \overline{\text{CSA7}} \cdot \overline{\text{LD}}$   
 $+ \overline{\text{LD}} \cdot \overline{\text{BA7}} \cdot \overline{\text{SET}}$

$\overline{\text{CSA8}} := \overline{\text{SET}} \cdot \overline{\text{CSA4}} \cdot \overline{\text{CSA5}} \cdot \overline{\text{CSA6}} \cdot \overline{\text{CSA7}} \cdot \overline{\text{CSA8}} \cdot \overline{\text{CI}} \cdot \overline{\text{LD}}$   
 $+ \overline{\text{SET}} \cdot \overline{\text{CSA8}} \cdot \overline{\text{CI}} \cdot \overline{\text{LD}} + \overline{\text{SET}} \cdot \overline{\text{CSA4}} \cdot \overline{\text{CSA8}} \cdot \overline{\text{LD}}$   
 $+ \overline{\text{SET}} \cdot \overline{\text{CSA5}} \cdot \overline{\text{CSA8}} \cdot \overline{\text{LD}} + \overline{\text{SET}} \cdot \overline{\text{CSA6}} \cdot \overline{\text{CSA8}} \cdot \overline{\text{LD}}$   
 $+ \overline{\text{SET}} \cdot \overline{\text{CSA7}} \cdot \overline{\text{CSA8}} \cdot \overline{\text{LD}} + \overline{\text{SET}} \cdot \overline{\text{LD}} \cdot \overline{\text{BA8}}$

$\overline{\text{CSA9}} := \overline{\text{SET}} \cdot \overline{\text{CSA4}} \cdot \overline{\text{CSA5}} \cdot \overline{\text{CSA6}} \cdot \overline{\text{CSA7}} \cdot \overline{\text{CSA8}} \cdot \overline{\text{CSA9}} \cdot \overline{\text{CI}} \cdot \overline{\text{LD}}$   
 $+ \overline{\text{SET}} \cdot \overline{\text{CSA9}} \cdot \overline{\text{CI}} \cdot \overline{\text{LD}} + \overline{\text{SET}} \cdot \overline{\text{CSA4}} \cdot \overline{\text{CSA9}} \cdot \overline{\text{LD}}$   
 $+ \overline{\text{SET}} \cdot \overline{\text{CSA5}} \cdot \overline{\text{CSA9}} \cdot \overline{\text{LD}} + \overline{\text{SET}} \cdot \overline{\text{CSA6}} \cdot \overline{\text{CSA9}} \cdot \overline{\text{LD}}$   
 $+ \overline{\text{SET}} \cdot \overline{\text{CSA7}} \cdot \overline{\text{CSA9}} \cdot \overline{\text{LD}} + \overline{\text{SET}} \cdot \overline{\text{CSA8}} \cdot \overline{\text{CSA9}} \cdot \overline{\text{LD}}$   
 $+ \overline{\text{SET}} \cdot \overline{\text{LD}} \cdot \overline{\text{BA9}}$

**5**

**DESCRIPTION:**

THE 6-BIT COUNTER INCREMENTS WHEN THE /LD LINE IS HIGH IF CARRY AND /SET. THE OUTPUTS ARE ENABLED WHEN /TSEN IS LOW.


**FUNCTION TABLE:**

/SET	CI	/LD	CLK	CSA	OPERATION
L	X	X	L-H	ALL HIGH	SET
H	X	L	L-H	BA	LD
H	H	H	L-H	CSA	NDP
H	L	H	L-H	CSA PLUS 1	INCR



Control Store Sequencer, Most Significant Stage

Logic Diagram PAL16R6

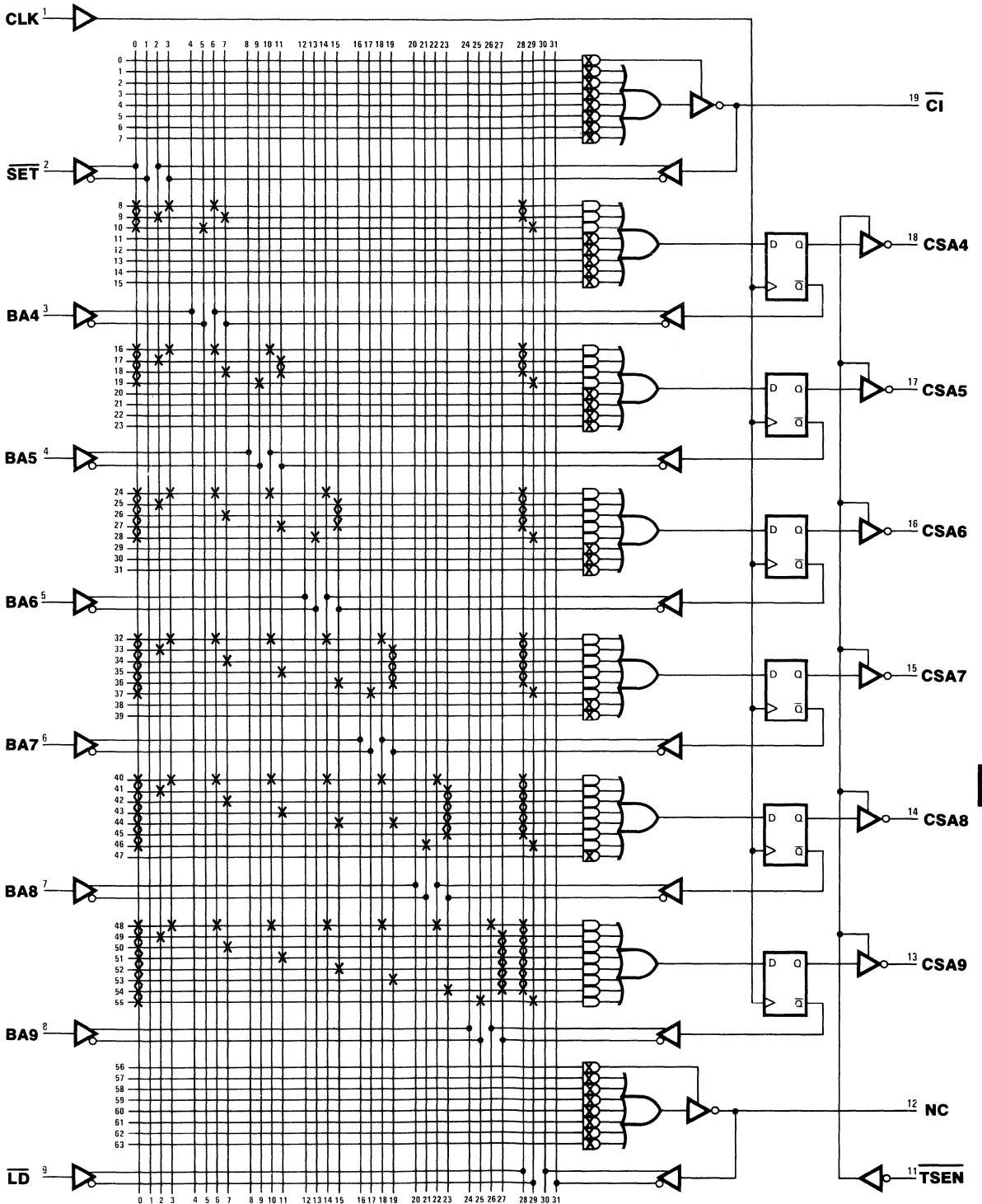

5

# Applications

## Memory Interface Logic for 6800 microprocessor Bus



*Most microcomputer system designs require the use of read/write and read only memory. The logic required to decode the microprocessor control signals into those signals required by the memory can be easily generated using a single PAL. This example shows how this logic is implemented for a read/write memory for the M6800 microcomputer. With minor modifications this logic can be easily extended to most other available microprocessors.*

## M6800 Memory Interface

### Functional Description

The M6800 microprocessor is interfaced to memories by decoding the system memory address bus and several system control lines to generate the required memory control signals. This function is normally performed by combinatorial logic. In many applications, however, the PAL provides a more effective solution.

### Circuit Operation

The logic schematic shown in Figure 1 is typical of most M6800 memory interfaces. The circuit shown is a 2048 x 8 bit static memory organized as four 1k x 4 bit RAM chips. The inputs to the RAM are the 10 memory address lines to select the individual memory location, the read/write line to determine whether data is to be read from or written into the memory, and the chip enable line to allow the device to perform the requested data transfer. Data to be written into the memory must be stable on the system data bus when the write signal is given. Data read from the memory will be placed on the data bus within one memory access time after the address has been decoded and the read signal given.

The circled area of combinatorial logic in Figure 1 is used to decode the 6800 address and control signals. Address bits 0-9 are routed directly to all four memory chips. Bit 10 is used to select whether chips 0 and 1 or chips 2 and 3 are to be selected. Bits 12-15 are connected to the A inputs of a digital comparator whose B inputs are jumpered to select the memory page address. If the memory is to be located from 0-800H (the first 2k page in the memory), all four comparator B inputs would be grounded. Then, whenever an address with bits 12-15 low appeared on the bus, a match would occur and the memory would be selected. Changing the jumpers allows the memory to be used anywhere in the 6800's address space or allows the use of multiple cards to construct a larger memory.

The read/write control logic for the memory is generated by decoding the read/write (R/W), phase 2 clock (Phase2), and valid memory address (Vphase2) system control lines. A logic high on the R/W line indicates a memory read; a logic high indicates a memory write.

The valid memory address line (Vphase2) is used to enable the address decoder output. When this enable occurs, the state of the address select and read/write logic is established. Then, when the phase 2 clock goes high, the memory transfer is performed. The relationship between the signals for both read and write operations is shown in Figure 2. (Consult 6800 data book for detailed design information.)

## PAL Implementation

All of the combinatorial logic in the circled area of figure 1 can be replaced by a single PAL. This will lower system cost by reducing the device package count and lowering P.C. board area. The logic section has eight input terms and six output terms. Referring to the PAL family table it is seen that the PAL 10L8 fits the task nicely. The only tricky part of the transition from combinatorial logic to a PAL is encountered in the address decoding section. In the original circuit the decoder is jumpered with a match address for use during the address comparison. With the PAL, the address is programmed directly into the gate array.

The general logic equations for the decoder are as follows:

$$\begin{aligned} \overline{WE00} &= \overline{VPHASE2} \cdot \overline{A10} \cdot \overline{A12} \cdot \overline{A13} \cdot \overline{A14} \cdot \overline{A15} \cdot \overline{PHASE2} \cdot \overline{RW} \\ \overline{WE01} &= \overline{VPHASE2} \cdot \overline{A10} \cdot \overline{A12} \cdot \overline{A13} \cdot \overline{A14} \cdot \overline{A15} \cdot \overline{PHASE2} \cdot RW \\ CSOD0 &= \overline{A10} \cdot \overline{A12} \cdot \overline{A13} \cdot \overline{A14} \cdot \overline{A15} \cdot PHASE2 \\ CSOD1 &= A10 \cdot A12 \cdot A13 \cdot A14 \cdot A15 \cdot PHASE2 \\ CE0 &= \overline{CSOD0} \\ CE1 &= \overline{CSOD1} \end{aligned}$$

The above equations show the decoder set for page 0 (0-800H), but this could be easily changed by modifying the address terms. Note that the CE0 and CE1 terms can either be derived directly or by feeding the CSOD0 and CSOD1 terms back into the PAL as inputs.

 


Figure 2

## Conclusion

The PAL makes an effective direct logic replacement in many combinatorial logic applications. This can make both new and old designs more cost effective. In this example, the PAL both lowers package count and increases circuit reliability in a typical microcomputer memory application. These advantages can be easily extended to similar designs.

Memory Interface Logic for 6800 Microprocessor Bus

Logic Schematic

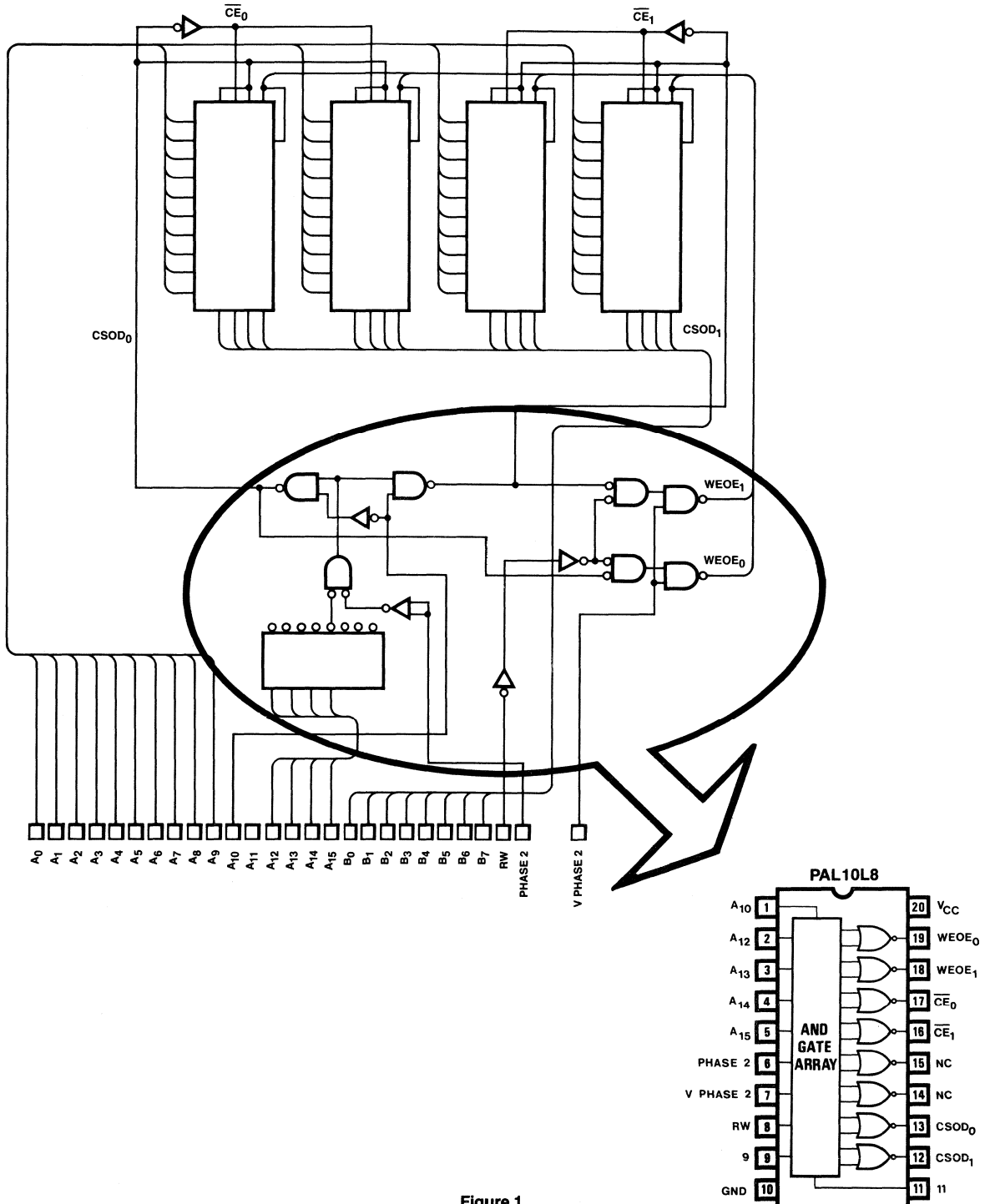


Figure 1



Memory Interface Logic for 6800 Microprocessor Bus

Design Specification PAL10L8

PAL10L8  
 PAT0011  
 MEMORY INTERFACE LOGIC FOR 6800 MICROPROCESSOR BUS

PAL DESIGN SPECIFICATION  
 JOHN BIRKNER 12/7/77

A10 A12 A13 A14 A15 PHASE2 VPHASE2 RW 9 GND  
 11 CSOD1 CSOD0 NC NC /CE1 /CE0 WEDE1 WEDE0 VCC

$$\overline{\text{WEDE0}} = \text{VPHASE2} \cdot \text{A10} \cdot \text{A12} \cdot \text{A13} \cdot \text{A14} \cdot \text{A15} \cdot \text{PHASE2} \cdot \text{RW}$$

$$\overline{\text{WEDE1}} = \text{VPHASE2} \cdot \text{A10} \cdot \text{A12} \cdot \text{A13} \cdot \text{A14} \cdot \text{A15} \cdot \text{PHASE2} \cdot \text{RW}$$

$$\text{CE0} = 9$$


$$\text{CE1} = 11$$

$$\text{CSOD0} = \overline{\text{A10}} \cdot \overline{\text{A12}} \cdot \overline{\text{A13}} \cdot \overline{\text{A14}} \cdot \overline{\text{A15}} \cdot \text{PHASE2}$$

$$\text{CSOD1} = \text{A10} \cdot \overline{\text{A12}} \cdot \overline{\text{A13}} \cdot \text{A14} \cdot \overline{\text{A15}} \cdot \text{PHASE2}$$

DESCRIPTION:

 THIS DEVICE PROVIDES THE INTERFACE LOGIC BETWEEN A 6800 MICROPROCESSOR BUS AND FOUR STATIC 4K MEMORY CHIPS. ADDRESS BUS, RW, PHASE2 AND VPHASE2 ARE DECODED TO PRODUCE THE PROPER WRITE ENABLE, CHIP ENABLE AND OUTPUT DISABLE SIGNALS FOR MEMORY DATA TRANSFERS. /CE0 AND /CE1 ARE THE COMPLEMENTS OF CSOD0 AND CSOD1, RESPECTIVELY BY EXTERNAL CONNECTIONS CSOD0 - PIN 9 AND CSOD1 - PIN 11.



Logic Symbol

Memory Interface Logic for 6800 Microprocessor Bus

Fuse Pattern PAL10L8

MEMORY INTERFACE LOGIC FOR 6800 MICROPROCESSOR BUS

```

-X-X- -X-- X--- -X-- X--- X--- X--- ---- VPHASE2♦/A10♦/A12♦/A13♦A14♦/A15
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX

```

```

---X- -X-- X--- X--- X--- X--- X--- ---- VPHASE2♦A10♦/A12♦/A13♦A14♦A15♦P
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX

```

```

----- ----- ----- ----- ----- ----- X--- 9
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX

```

```

----- ----- ----- ----- ----- --X- 11
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX

```

```

XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX

```

```

XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX

```

```

-X-X- -X-- -X-- -X-- X--- X--- X--- ---- /A10♦/A12♦/A13♦/A14♦/A15♦PHASE2
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX

```


```

---X- -X-- X--- -X-- X--- ----- ----- ---- A10♦/A12♦/A13♦A14♦/A15♦PHASE2
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX
XXXX XX-- XX-- XX-- XX-- XX-- XX-- XX-- XXXX

```

Memory Interface Logic for 6800 Microprocessor Bus


Logic Diagram PAL10L8

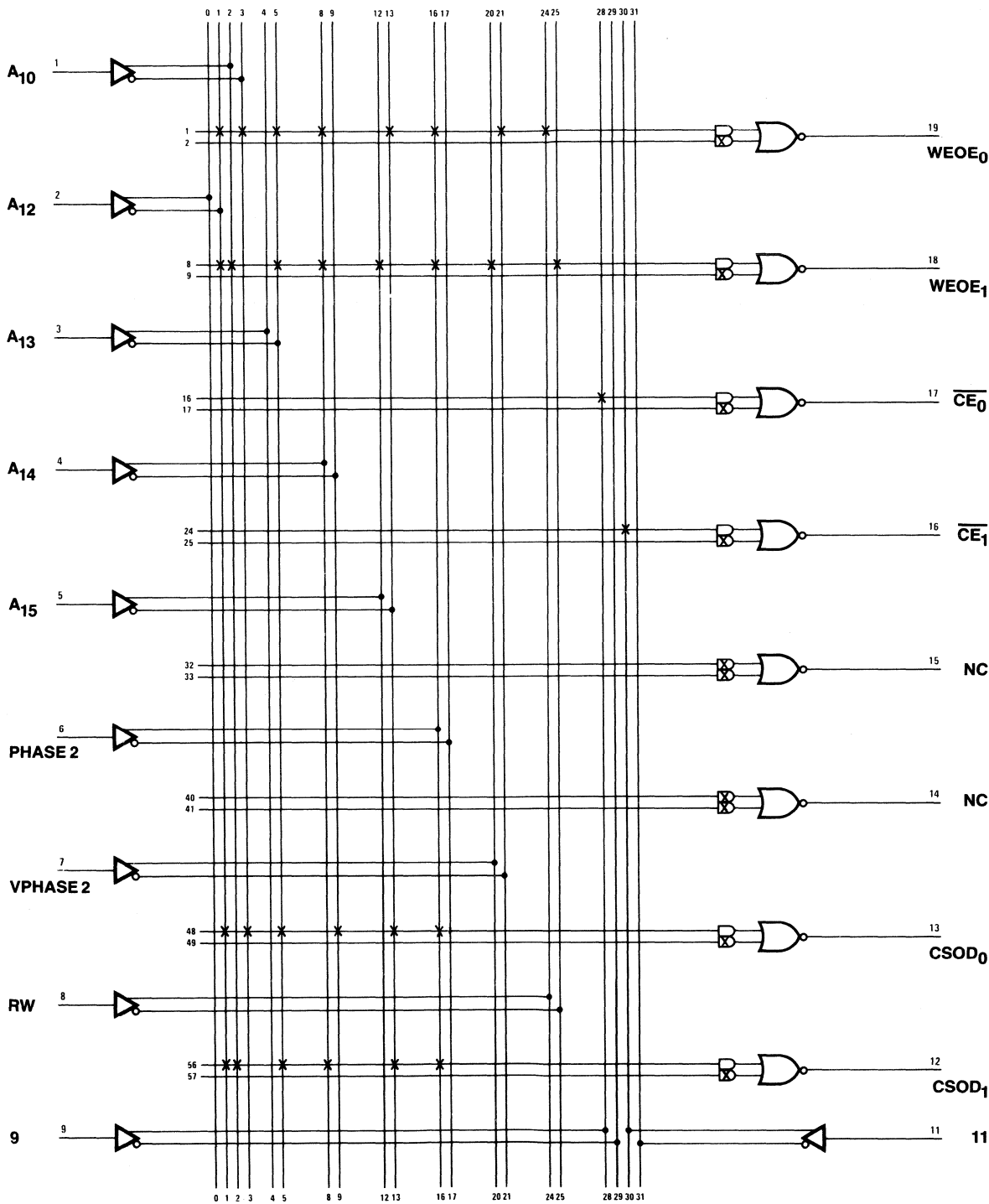

5

# Applications

## Dual I/O Port Decoder for S-100 Bus

 

*The S-100 bus is an informal standard bus structure used in many hobbyist computers. It has, however, proved useful and cost effective enough to find its way into many commercial applications. S-100 bus computers are based in the 8080/Z-80 family microcomputers, and this example shows how the S-100 bus signals can be decoded and used to control two bi-directional I/O ports in one of these systems.*

## Dual I/O Port Decoder for the S100 Bus

### Functional Description

The S-100 bus compatible family of computers are based on the 8080/Z-80 family of microcomputers. For I/O operations these computers place an 8 bit I/O address on the high and low order 8 bits of the 16 bit wide system memory address bus. This system allows up to 256 direct I/O devices in any system. The I/O addresses and the system control signals are decoded by I/O devices to initiate and control data transfer operations. The PAL provides an effective means of managing this type of data transfer.

### Circuit Description

The circuit shown in Figure 1 is a complete bi-directional two input, two output port interface for an S-100 bus computer. The PAL is used to decode the I/O addresses and the I/O control signals.

For input operations data is gated from the selected input port (A or B) onto the system data bus. For output operations data is gated from the system data bus to the selected output port.

The data I/O circuitry consists of four octal registers and two three state octal buffers connected together by an internal eight bit bi-directional data bus. For input operations the data is latched into the octal register when the device strobes the latch clock. When a read option addresses that input port, the register three state enable is clocked and the data is gated from the register, through the octal buffer and onto the S-100 data bus. For output operations an output address match causes the data to be gated off the S-100 data bus, through the octal buffer and latched into the octal output register. It will remain latched and available for reading until new data is written to that address. I/O devices can read the data by enabling the octal register's three state enable line.

### PAL Implementation

The PAL is used to monitor the bus I/O address and control signals. Address lines A0-A7 provide the address of the I/O port being accessed. The PDBIN signal is used to select the direction of data transfer: a logic high indicates an input operation, while a logic low indicates an output operation. The SINP signal indicates the bus is ready for an input data transfer; SOUT indicates that the data on the data bus is a valid output. The PWR signal indicates that the system bus is correctly powered up; PWR must be low for any data transfers to take place.

The control signals are decoded to produce six signals which operate the I/O logic. AIN and BIN are generated when the logic decode indicates an input from port A or B is to be performed. This will occur when the address programmed for A or B matches the address on the bus and PDBIN and SINP indicate an input operation. Similarly, AOUT and BOUT are generated when the address on the bus matches and PDBIN and SOUT indicate an output operation is being performed.

DIN is generated whenever an address match occurs and an input operation is to be performed. It is used to gate data from the selected input port through the octal buffer and onto the system data bus. DOUT is generated whenever an address match occurs and an output operation is being performed. It is used to gate data from the system data bus to the destination output register.

The logic equations for the control signals are as follows:

$$\begin{aligned} \overline{\text{AIN}} &= \overline{\text{A0}} \cdot \text{A1} \cdot \overline{\text{A2}} \cdot \text{A3} \cdot \overline{\text{A4}} \cdot \text{A5} \cdot \text{A6} \cdot \overline{\text{A7}} \cdot \overline{\text{PWR}} \cdot \text{SINP} \\ \overline{\text{AOUT}} &= \overline{\text{A0}} \cdot \text{A1} \cdot \overline{\text{A2}} \cdot \text{A3} \cdot \overline{\text{A4}} \cdot \text{A5} \cdot \text{A6} \cdot \overline{\text{A7}} \cdot \overline{\text{PWR}} \cdot \text{SOUT} \\ \overline{\text{BIN}} &= \text{A0} \cdot \overline{\text{A1}} \cdot \text{A2} \cdot \overline{\text{A3}} \cdot \text{A4} \cdot \text{A5} \cdot \overline{\text{A6}} \cdot \text{A7} \cdot \overline{\text{PWR}} \cdot \text{SINP} \\ \overline{\text{BOUT}} &= \text{A0} \cdot \overline{\text{A1}} \cdot \text{A2} \cdot \overline{\text{A3}} \cdot \text{A4} \cdot \text{A5} \cdot \overline{\text{A6}} \cdot \text{A7} \cdot \overline{\text{PWR}} \cdot \text{SOUT} \\ \text{DIN} &= \overline{\text{AIN}} + \overline{\text{BIN}} \\ \text{DOUT} &= \overline{\text{AOUT}} + \overline{\text{BOUT}} \end{aligned}$$

The above equations are for an A port address of 6A hex and a B port address of B5 hex. By changing terms any desired port address can be obtained.

This application has a total of 12 inputs (A0-A7, PWR, PDBIN, SINP, and SOUT) and six outputs (AIN, AOUT, BIN, BOUT, DIN, and DOUT). The entire function can be performed using a single PAL 12L6.

One advantage of using a PAL in this type of application is that it allows the address of the A and B I/O port pairs to be any eight bit address. As mentioned, in this example the A address is 6A hex and the B address is B5 hex. In a normal combinatorial design of this type the addresses must usually be made contiguous (i.e. A = 80 hex, B = 81 hex) to save decoding logic. The PAL approach offers more flexibility and uses fewer packages.

### Conclusion

The PAL combines together with latches and data buffers to make an efficient I/O port decoder and controller. This example has been for the S-100 bus, but the concept can be easily extended to other microcomputers and bus structures.

5

Dual I/O Port Decoder for the S100 Bus

Logic Schematic PAL12L6

 


Figure 1

**Dual I/O Port Decoder for the S100 Bus**

**Design Specification PAL12L6**

PAL12L6  
 PAT0010  
 DUAL I/O PORT DECODER FOR THE S100 BUS.

PAL DESIGN SPECIFICATION  
 VIC NEWTON 12/14/77

$\overline{PWR}$  A0 A1 A2 A3 A4 A5 A6 A7 GND SOUT SINT BOUT BIN  
 AOUT AIN DOUT DIN PDBIN VCC

$$\overline{DIN} = \overline{A0 \cdot A1} \cdot \overline{A2 \cdot A3} \cdot \overline{A4 \cdot A5} \cdot \overline{A6} \cdot \overline{A7} \cdot \overline{PDBIN} \cdot \overline{PWR} \cdot SINT + A0 \cdot \overline{A1} \cdot \overline{A2} \cdot \overline{A3} \cdot \overline{A4} \cdot \overline{A5} \cdot \overline{A6} \cdot \overline{A7} \cdot \overline{PDBIN} \cdot \overline{PWR} \cdot SINT$$

$$\overline{DOUT} = \overline{A0 \cdot A1} \cdot \overline{A2 \cdot A3} \cdot \overline{A4 \cdot A5} \cdot \overline{A6} \cdot \overline{A7} \cdot \overline{PDBIN} \cdot \overline{PWR} \cdot SOUT + A0 \cdot \overline{A1} \cdot \overline{A2} \cdot \overline{A3} \cdot \overline{A4} \cdot \overline{A5} \cdot \overline{A6} \cdot \overline{A7} \cdot \overline{PDBIN} \cdot \overline{PWR} \cdot SOUT$$

$$\overline{AIN} = \overline{A0 \cdot A1} \cdot \overline{A2 \cdot A3} \cdot \overline{A4 \cdot A5} \cdot \overline{A6} \cdot \overline{A7} \cdot \overline{PDBIN} \cdot \overline{PWR} \cdot SINT$$

$$\overline{AOUT} = \overline{A0 \cdot A1} \cdot \overline{A2 \cdot A3} \cdot \overline{A4 \cdot A5} \cdot \overline{A6} \cdot \overline{A7} \cdot \overline{PDBIN} \cdot \overline{PWR} \cdot SOUT$$

$$\overline{BIN} = A0 \cdot \overline{A1} \cdot \overline{A2} \cdot \overline{A3} \cdot \overline{A4} \cdot \overline{A5} \cdot \overline{A6} \cdot \overline{A7} \cdot \overline{PDBIN} \cdot \overline{PWR} \cdot SINT$$

$$\overline{BOUT} = A0 \cdot \overline{A1} \cdot \overline{A2} \cdot \overline{A3} \cdot \overline{A4} \cdot \overline{A5} \cdot \overline{A6} \cdot \overline{A7} \cdot \overline{PDBIN} \cdot \overline{PWR} \cdot SOUT$$

**DESCRIPTION:**

THE DUAL I/O PORT DECODER PROVIDES THE SIGNALS FOR ENABLING THE BUS BUFFERS, CLOCKING THE OUTPUT REGISTERS, AND ENABLING THE INPUT REGISTERS. IN THIS EXAMPLE PORT A IS ADDRESS 6A HEX AND PORT B IS ADDRESS B5 HEX. ANY TWO ADDRESSES CAN BE USED.

**FUNCTION TABLE:**

! ADDRESS	! SINT	SOUT	! PDBIN	$\overline{PWR}$	! DIN	DOUT	AIN	AOUT	BIN	BOUT
! NO MATCH	! X	X	! X	X	! H	H	H	H	H	H
! MATCH	! L	H	! L	L	! H	L	H	L	H	H
! MATCH	! H	L	! H	H	! L	H	L	H	H	H
! MATCH	! L	H	! L	L	! H	L	H	H	H	L
! MATCH	! H	L	! H	H	! L	H	H	H	L	H

ONLY THE ABOVE FOUR CONDITIONS WILL CAUSE THE OUTPUTS TO BECOME ACTIVE.

Dual I/O Port Decoder for the S100 Bus

Fuse Pattern PAL12L6

DUAL I/O PORT DECODER FOR THE S100 BUS.

```

XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX

```

```

-X-X- X-X- -X-- X--- -X-- X--- X-X- -X-- /A0♦A1♦/A2♦A3♦/A4♦A5♦A6♦/A7♦PDB
X-X- -X-X- X--- -X-- -X-- X--- -X-X- X--- A0♦/A1♦A2♦/A3♦A4♦A5♦/A6♦A7♦PDBI
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX

```

```

-X-X X-X- -X-- X--- -X-- X--- X--- -X-X- /A0♦A1♦/A2♦A3♦/A4♦A5♦A6♦/A7♦/PD
X-X- -X-X X--- -X-- -X-- X--- -X-X- X-X- A0♦/A1♦A2♦/A3♦A4♦A5♦/A6♦A7♦/PDB
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX

```

```

-X-X- X-X- -X-- X--- -X-- X--- X-X- -X-- /A0♦A1♦/A2♦A3♦/A4♦A5♦A6♦/A7♦PDB
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX

```

```

-X-X X-X- -X-- X--- -X-- X--- X--- -X-X- /A0♦A1♦/A2♦A3♦/A4♦A5♦A6♦/A7♦/PD
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX

```

```

X-X- -X-X- X--- -X-- X--- X--- -X-X- X--- A0♦/A1♦A2♦/A3♦A4♦A5♦/A6♦A7♦PDBI
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX

```

```

X--X -X-X X--- -X-- X--- X--- -X-- X-X- A0♦/A1♦A2♦/A3♦A4♦A5♦/A6♦A7♦/PDB
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX
XXXX XXXX XX-- XX-- XX-- XX-- XXXX XXXX

```

```


XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX

```



Dual I/O Port Decoder for the S100 Bus


Logic Diagram PAL12L6

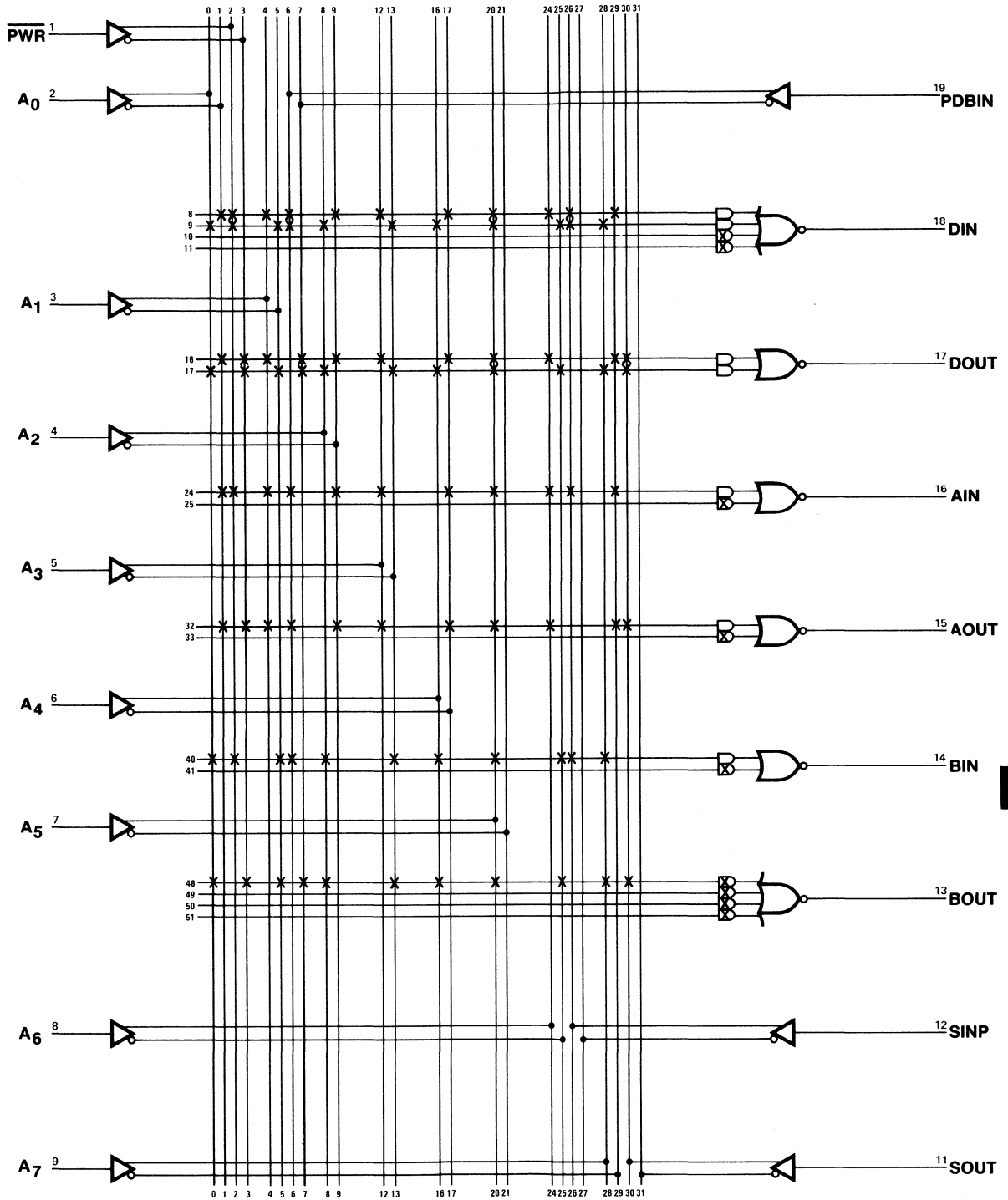

5

# Applications

## Memory Mapped I/O

 

*Memory mapped I/O is an interface technique which addresses I/O devices as a part of the computer's memory address space. Most computers (particularly microcomputers) provide many more instructions to manipulate memory contents than they have for direct I/O. Therefore, the use of memory mapping can make I/O control much more flexible. PALs can be used to make memory mapped I/O implementation easy and, if different memory addresses are required, the PAL can easily accommodate the changes.*

## Memory Mapped I/O

### Functional Description

Memory mapped I/O interfaces I/O devices to a computer by treating the device's physical address as a memory address. This removes the requirement for special I/O decoding and enhances the flexibility of the I/O system. The PAL provides a simple and direct method for implementing memory mapped I/O in mini and micro computer systems.

### Circuit Operation

The circuits shown in Figure 1 are typical of those found in memory mapped I/O applications. The inputs to the decode logic are the system memory address lines, A0-AF. The logic compares the address on the memory bus with the programmed comparison address. When an address on the bus matches, the I/O port enable signal is set. This enable signal can then be used in conjunction with other system control signals to transfer data to and from the system data bus. Other examples in this applications section cover this I/O control decoding in more detail.

### PAL Design

The PAL is used to monitor the system memory address bus. Typical microcomputers use a 16 bit address, so fully decoding the I/O addresses for two ports can be accomplished using the PAL 16L2. Partial decoding for a larger number of ports can be performed by other members of the PAL family.

The logic equations for the memory mapped I/O logic are as follows:

$$\text{PORT 0} = \overline{AB0} \cdot \overline{AB1} \cdot \overline{AB2} \cdot AB3 \cdot AB4 \cdot AB5 \cdot AB6 \cdot \overline{AB7} \cdot AB8 \cdot AB9 \cdot ABA \cdot ABB \cdot ABC \cdot \overline{ABD} \cdot ABE \cdot \overline{ABF}$$

$$\text{PORT 1} = AB0 \cdot \overline{AB1} \cdot \overline{AB2} \cdot AB3 \cdot AB4 \cdot AB5 \cdot AB6 \cdot \overline{AB7} \cdot AB8 \cdot AB9 \cdot ABA \cdot ABB \cdot ABC \cdot \overline{ABD} \cdot \overline{ABE} \cdot \overline{ABF}$$

The above example shows address decoding for memory locations 1f78 hex and 1f79 hex. Equation terms can be changed to accommodate any 16 bit address.

In operation, the PAL enable outputs will go high whenever one of the programmed addresses matches the address on the system memory address bus. Since the PAL fully decodes the address, any two I/O address may be used.

### Conclusion

The PAL provides a single chip decoder for use in memory mapped I/O operations. This technique lowers interface parts counts and allows users an effective way to interface I/O devices to the microcomputer system.

Memory Mapped I/O

Design Specification PAL16L2

PAL16L2  
 PAT0008  
 MEMORY MAPPED I/O

PAL DESIGN SPECIFICATION  
 JOHN BIRKNER 12/5/77

AB0 AB1 AB2 AB3 AB4 AB5 AB6 AB7 AB8 GND AB9 ABA ABB ABC  
 /PORT1 /PORT0 ABD ABE ABF VCC

PORT0 = /AB0♦/AB1♦/AB2♦AB3♦AB4♦AB5♦AB6♦/AB7♦AB8♦AB9♦ABA♦ABB♦ABC♦  
 /ABD♦/ABE♦/ABF

PORT1 = AB0♦/AB1♦/AB2♦AB3♦AB4♦AB5♦AB6♦/AB7♦AB8♦AB9♦ABA♦ABB♦ABC♦  
 /ABD♦/ABE♦/ABF

DESCRIPTION:

THE PAL DECODES THE SPECIFIED MEMORY ADDRESS WORD TO PRODUCE A PORT ENABLE FOR PORT0 AND PORT1 AS FOLLOWS:

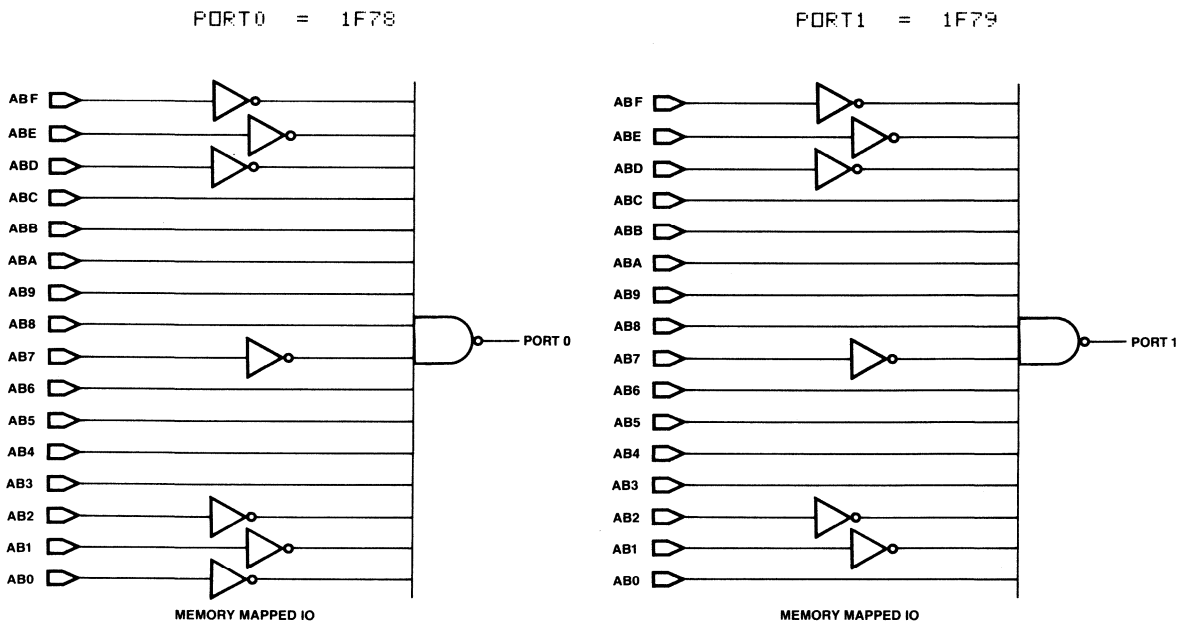


Figure 1

Memory Mapped I/O

Fuse Pattern PAL16L2

XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX

XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX

XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX

XX-X -X-X X--X X--- X--- X-X- -XX- X-X- /AB0♦/AB1♦/AB2♦AB3♦AB4♦AB5♦AB6♦\*
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX

XX-X -X-X X--X X--- X--- X-X- -XX- X-X- AB0♦/AB1♦/AB2♦AB3♦AB4♦AB5♦AB6♦\*
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX

XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX


XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX

XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX XXXX

\*PALASM Truncates beyond 31 characters

Memory Mapped I/O

Logic Diagram PAL16L2

 

# Applications

## 8080 Control Logic for CPU Board



5

*The 8080 is one of the most widely used of all current microprocessor designs. However, using the 8080 in a system requires that the designer decode and supply a fairly complex set of control signals. With the rapid decline in 8080 prices, the logic required to perform this control decoding has become more expensive than the 8080 itself. This example shows how a PAL can be used to eliminate much of this costly support logic in an 8080 based system CPU card.*

Portion of Random Control Logic for 8080 CPU Board

Design Specification PAL16L8

PAL16L8

PAL DESIGN SPECIFICATION

PAT0012

BOB BOSNYAK 12/16/77

PORTION OF RANDOM CONTROL LOGIC FOR 8080 CPU BOARD

PD EN EO EA S1 SA E1 DO DE GND SO NO C3 HA SS LA MW PW NC3 VCC

IF (VCC) /MW= SO♦/PW + SO♦/DE

IF (VCC) /LA= SA + DO

IF (VCC) /SS= /S1 + /PD + SA


IF (VCC) /HA= /S1 + /PD + SA + /EA + /E1

IF (VCC) /C3= /PD + /EO + /EA

IF (VCC) /NO= /PD + EN

DESCRIPTION:

PORTION OF LOGIC FROM 8080 CPU BOARD

 



Portion of Random Control Logic for 8080 CPU Board

Fuse Pattern PAL16L8

```

XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX

```

```

XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX

```

```

---- ---- ---- ---- ---- ---- ----
---- -X- - - - - - - - - - -X- /S1 /PM
---- - - - - - - - - - - -X- /S1 /DE
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX

```

```

---- ---- ---- ---- X---- ---- ----
---- - - - - - - - - - - -X- - - - /S1
XXXX XXXX XXXX XXXX XXXX XXXX XXXX /DO
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX

```

```

---- ---- ---- -X- ---- ---- ----
---X- - - - - - - - - - - - - - - /S1
---- - - - - - - - - - - -X- - - - /PD
XXXX XXXX XXXX XXXX XXXX XXXX XXXX /S1
XXXX XXXX XXXX XXXX XXXX XXXX XXXX /SA
XXXX XXXX XXXX XXXX XXXX XXXX XXXX

```

```

---- ---- ---- -X- ---- ---- ----
---X- - - - - - - - - - - - - - - /S1
---- - - - - - - - - - - -X- - - - /PD
---- - - - -X- - - - - - - - - - /SA
XXXX XXXX XXXX XXXX XXXX XXXX XXXX /EA
XXXX XXXX XXXX XXXX XXXX XXXX XXXX /E1

```

```

---- -X- ---- ---- ---- ---- ----
---X- -X- - - - - - - - - - - - - /PD
---- - - - -X- - - - - - - - - - /EO
XXXX XXXX XXXX XXXX XXXX XXXX XXXX /EA
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX

```


```

---- -X- ---- ---- ---- ---- ----
X---- - - - - - - - - - - - - - - /PD
XXXX XXXX XXXX XXXX XXXX XXXX XXXX /EN
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX

```

Portion of Random Control Logic for 8080 CPU Board

Logic Diagram PAL16L8

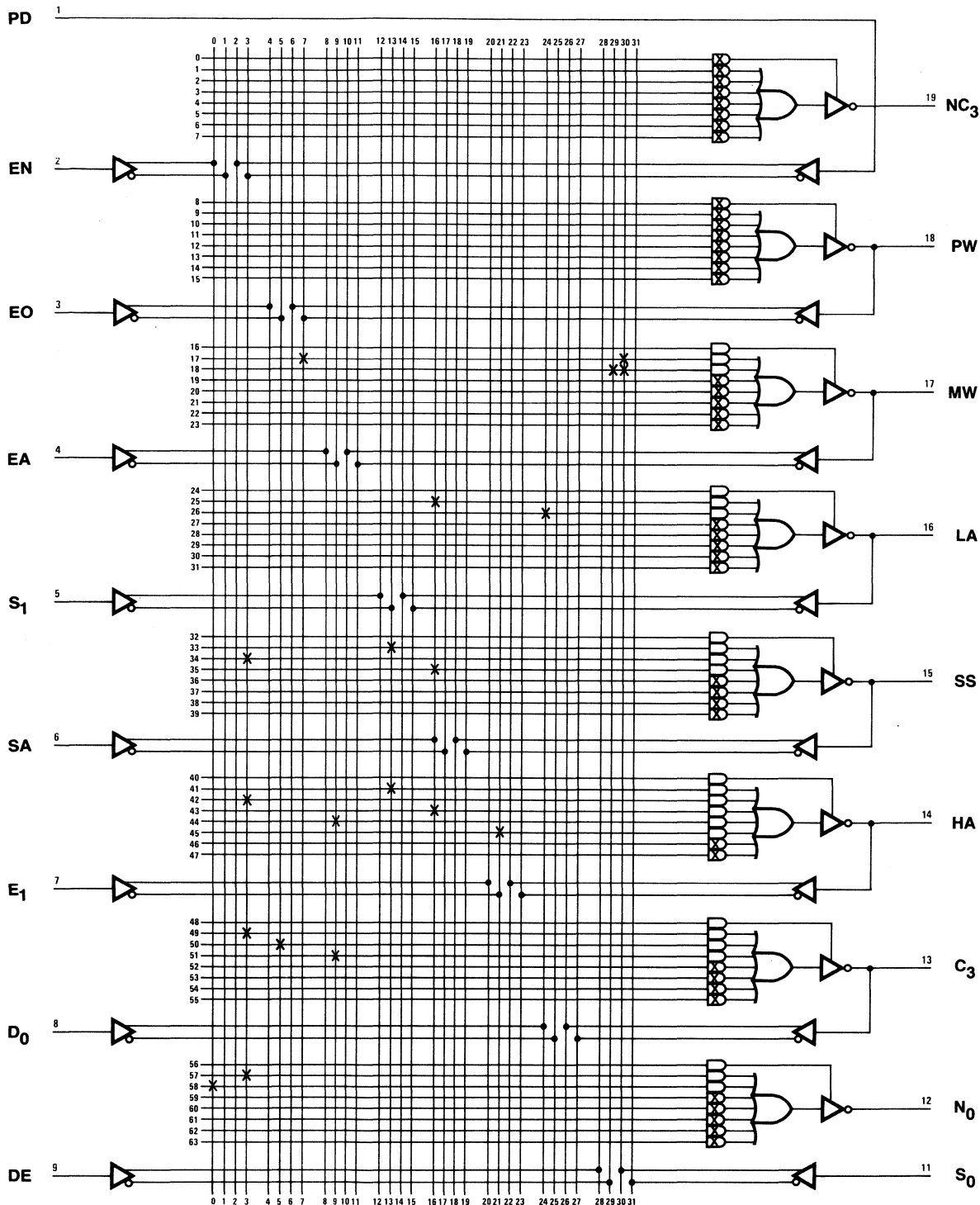

**Portion of Random Control Logic for 8080 CPU Board (Improved Design)**

**Design Specification PAL12H6**

PAL12H6  
PAT0013

PAL DESIGN SPECIFICATION  
JOHN BIRKNER 12/17/77

PORTION OF RANDOM CONTROL LOGIC FOR 8080 CPU BOARD (IMPROVED DESIGN)

PD EN EO EA S1 SA E1 DO DE GND SO NO3 NO C3 HA SS LA MW PW VCC

$MW = \neg SO + PW \cdot DE$

$LA = \neg SA \cdot \neg DO$

$SS = S1 \cdot PD \cdot \neg SA$

$HA = S1 \cdot PD \cdot \neg SA \cdot EA \cdot E1$


$C3 = PD \cdot EO \cdot EA$

$NO = PD \cdot \neg EN$

 **DESCRIPTION:**

PORTION OF LOGIC FROM 8080 CPU BOARD


NOTE: THIS DESIGN IS IMPROVED OVER THE PREVIOUS EXAMPLE AS WE WERE ABLE TO IMPLEMENT THE SAME EQUATIONS IN A SMALLER PAL. THIS WAS ACCOMPLISHED BY INVERTING THE EQUATIONS, THUS, REDUCING THE NUMBER OF PRODUCTS PER OUTPUT TO A MAXIMUM OF TWO.





Portion of Random Control Logic for 8080 CPU Board (Improved Design)

Logic Diagram PAL12H6

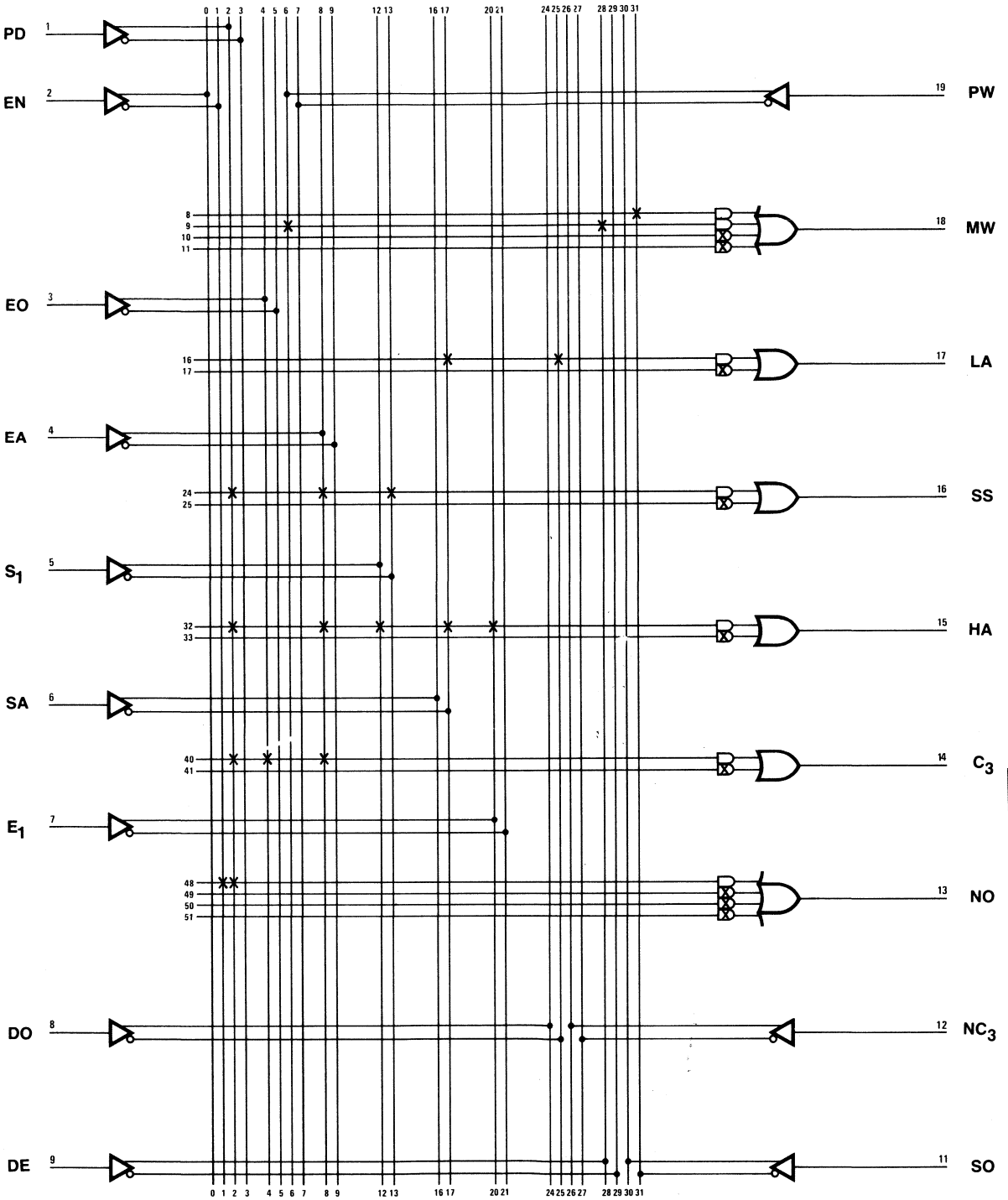

5

# Applications

## Hexadecimal Decoder Lamp Driver



*The increasing use of microcomputers has led to an increased need to display numbers in hexadecimal format (0 - 9, A - F). Standard drivers for this function are not available, so most applications are forced to use several packages to decode each digit of the display. Since six to twelve digits are often being displayed, this approach can become very expensive. This example demonstrates how the hexadecimal display format can be both decoded and the LED indicators driven using a single PAL for each digit of the display.*

## Hexadecimal Decoder Lamp Driver

### Functional Description

A hexadecimal decoder/lamp driver accepts a four bit hexadecimal digit, converts it to its corresponding seven segment display code, and activates the appropriate segments on the display. These drivers can be used in both direct drive and multiplexed display applications. A single PAL can provide both the basic decode/drive functions and additional useful features.

### Circuit Description

Figure 1 shows a three digit display system using three PALS to implement the complete decoding and display driving functions. The inputs to each section are a hexadecimal code on pins D0-D3, a ripple blanking signal, an intensity control signal, and a lamp test signal.

The hexadecimal codes will be decoded to form the seven segment code patterns shown in Figure 1. The input codes, digit represented, and output segments driven are as follows:

D3	D2	D1	D0	DIGIT	SEGMENTS
0	0	0	0	0	A,B,C,D,E,F
0	0	0	1	1	B,C
0	0	1	0	2	A,B,D,E,G
0	0	1	1	3	A,B,C,D,G
0	1	0	0	4	B,C,F,G
0	1	0	1	5	A,C,D,F
0	1	1	0	6	A,C,D,E,F
0	1	1	1	7	A,B,C
1	0	0	0	8	A,B,C,D,E,F,G
1	0	0	1	9	A,B,C,F,G
1	0	1	0	A	A,B,C,E,F,G
1	0	1	1	B	C,D,E,F,G
1	1	0	0	C	A,D,E,F
1	1	0	1	D	B,C,D,E,G
1	1	1	0	E	A,D,E,F,G
1	1	1	1	F	A,E,F,G

The ripple blanking input (RBI) is used to suppress leading zeroes in the display. The signal is propagated from the most significant digits down to the least significant digits. If the digit input is zero and the ripple blanking input is low (indicating that the previous digit is also a zero), all display segments are left blank and this digit position's ripple blanking output signal (RBO) is set low.

The intensity control signal (IC) is used to control the duty cycle of the display driver. When the signal is high, all segment outputs are turned off and the display is blank. Pulsing this pin with a duty cycled signal allows the adjustment of the display's perceived intensity.

The lamp test signal (LT) is used to verify that all segments in the display are working. When it is held high, all display segments are turned on.

### PAL Implementation

The display decoder driver requires an output section that can directly drive a seven segment display. Each display digit has seven inputs (D0-D3, RBI, IC, and LT) and eight output signals (segments A-G, and RBO). The PAL 16L8 has both the required number of I/O pins and the required drive capability.

The logic equations for the driver are shown on the PALASM input. They can be easily derived from the input codes and required blanking and test functions. One PAL is used for each digit, and the number of digits can be as large as required. With minor changes this basic logic could also be used with multiplexor logic to allow a single PAL to decode and drive a multi-digit display.

### Summary

The PAL provides a low cost and functionally flexible direct decoder/driver for use in a variety of display applications. This example demonstrated hexadecimal to seven segment code conversions, but many other display formats and code conversions can be implemented using similar techniques.



## Hex Decoder/7 Seg. Driver w/Ripple Blanking, Intensity Con., & Lamp Test
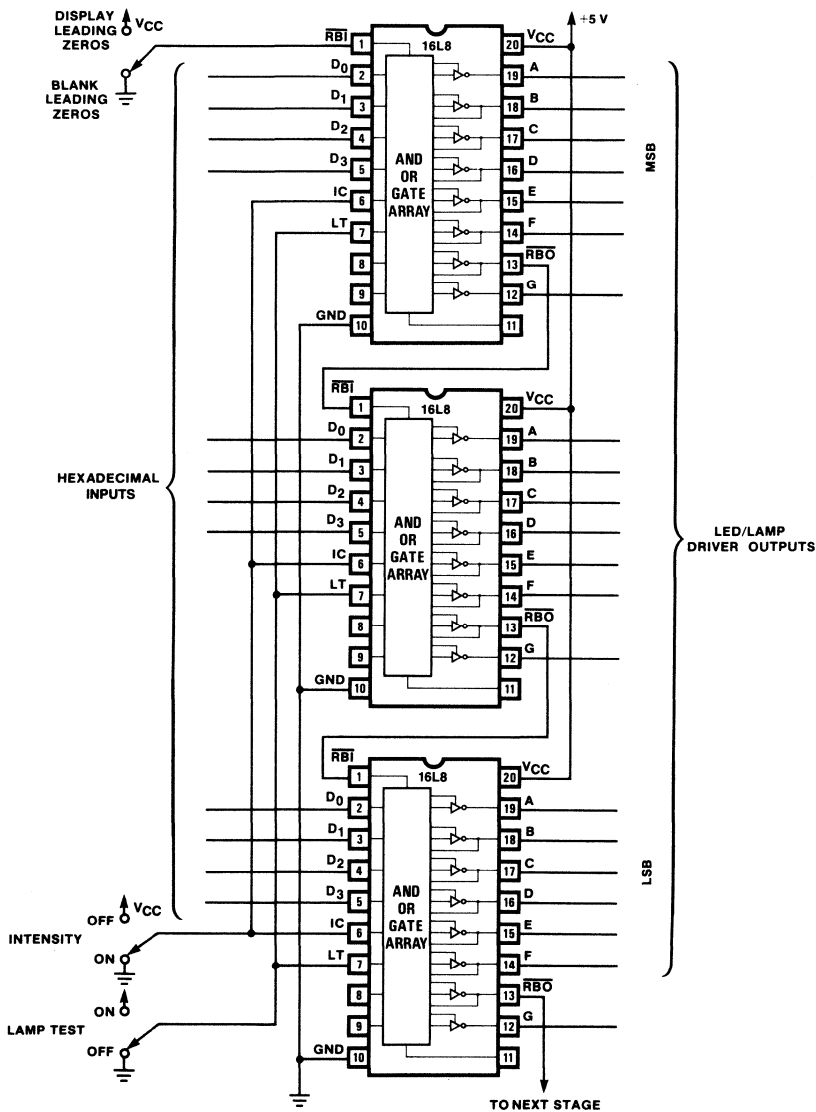 
## Logic Schematic

THREE STAGE HEXADECIMAL DECODER/DRIVER



PAL 16L8  
BCD TO HEXADECIMAL  
DECODER/7 SEGMENT  
DRIVER WITH RIPPLE BLANKING





Hex Decoder/7 Seg. Driver w/Ripple Blanking,  
Intensity Con., & Lamp Test

Design Specification PAL16L8

PAL16L8  
PAT0007

PAL DESIGN SPECIFICATION  
LES GARDINIER 12-14-77

HEX DECODER/7SEG. DRIVER W/RIPPLE BLANKING, INTENSITY CON., & LAMP TEST

/RBI D0 D1 D2 D3 IC LT NC NC GND NC G /RBD F E D C B A VCC

IF (/IC) /A = /RBD/D0/D2 + /RBD/D0/D3 + /RBD/D1/D2 +  
/RBD/D1/D2/D3 + /RBD/D0/D2/D3 + /RBD/D1/D2/D3 + LT

IF (/IC) /B = /RBD/D2/D3 + /RBD/D0/D2 + /RBD/D0/D1/D3 +  
/RBD/D0/D1/D3 + /RBD/D0/D1/D3 + LT

IF (/IC) /C = /RBD/D0/D1 + /RBD/D0/D2 + /RBD/D1/D2 +  
/RBD/D2/D3 + /RBD/D2/D3 + LT

IF (/IC) /D = /RBD/D1/D3 + /RBD/D0/D2/D3 +  
/RBD/D0/D1/D2 + /RBD/D0/D1/D2 + /RBD/D0/D1/D2 + LT

IF (/IC) /E = /RBD/D0/D2 + /RBD/D2/D3 + /RBD/D0/D1 +  
/RBD/D1/D3 + LT

IF (/IC) /F = /RBD/D0/D1 + /RBD/D2/D3 + /RBD/D1/D3 +  
/RBD/D0/D2 + /RBD/D1/D2/D3 + LT

IF (VCC) RBD = /D0/D1/D2/D3/RBI

IF (/IC) /G = /RBD/D1/D2 + /RBD/D0/D3 + /RBD/D2/D3 +  
/RBD/D0/D1 + /RBD/D1/D2/D3 + LT

DESCRIPTION:

THE HEXDECIMAL DECODER/7-SEGMENT DRIVER FEATURES ACTIVE LOW OUTPUTS FOR DRIVING DISPLAY DIRECTLY.

IF DATA INPUT IS ZERO AND RIPPLE BLANKING INPUT (/RBI) IS LOW THAT DIGIT WILL BE BLANKED AND RIPPLE BLANKING OUTPUT WILL BE LOW.

THE RIPPLE BLANKING OUTPUT (/RBD) PROVIDES BLANKING INFORMATION FOR THE NEXT LEAST SIGNIFICANT STAGE. IT PROVIDES A LOW IF /RBI IS LOW AND THE DATA IN IS ZERO.

WHEN HIGH THE INTENSITY CONTROL (IC) WILL TURN OFF THE ENTIRE DISPLAY. IC MAY BE PULSED TO VARY THE INTENSITY OF THE DISPLAY.

WHEN HIGH THE LAMP TEST INPUT (LT) WILL TURN ON THE DISPLAY.


FUNCTION TABLE:

INPUTS							OUTPUTS							
LT	IC	/RBI	D0	D1	D2	D3	A	B	C	D	E	F	G	/RBD
L	H	X	X	X	X	X	Z	Z	Z	Z	Z	Z	Z	X
L	L	H	L	L	L	L	L	L	L	L	L	L	H	L
L	L	L	L	L	L	L	H	H	H	H	H	H	H	L
H	L	X	X	X	X	X	L	L	L	L	L	L	L	X



Hex Decoder/7 Seg. Driver w/Ripple Blanking, Intensity Con., & Lamp Test

Logic Diagram PAL16L8

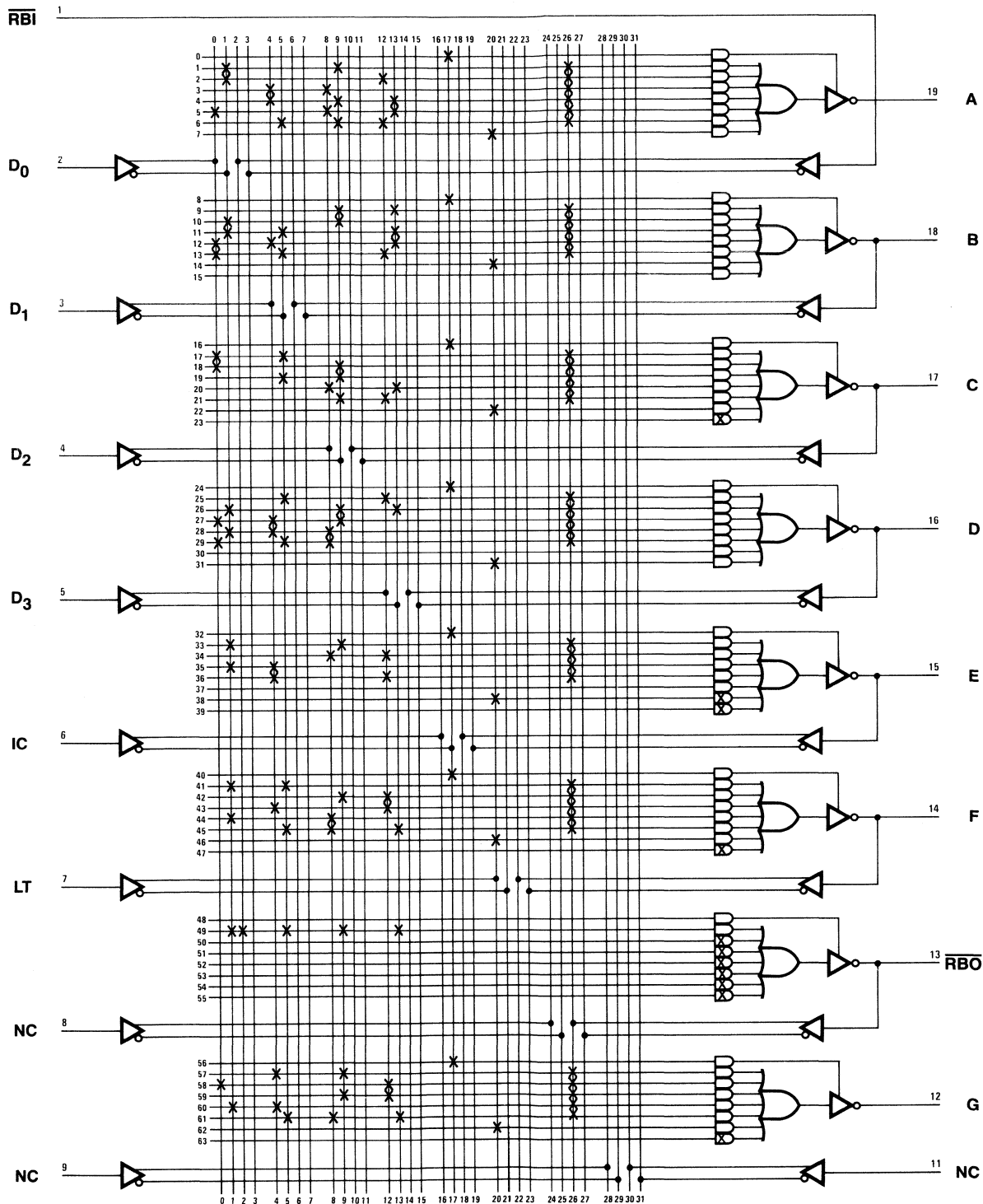


5



# Applications

## Hex Keyboard Scanner

 


5

*A problem similar to driving the hexadecimal display in the previous example is encountered in system input design. The popularity of consumer calculators has made the small keypad a widely available and low cost system input device. The logic required to scan these small keyboards is generated by using either SSI/MSI logic or a computer generated software scan. The logic may be quite expensive, and, if the microcomputer is in a functionally busy system, the software scan may be inadequate. A single PAL and a few other parts can now be used to implement this system function.*

Hex Keyboard Scanner

Logic Diagram PAL16L8

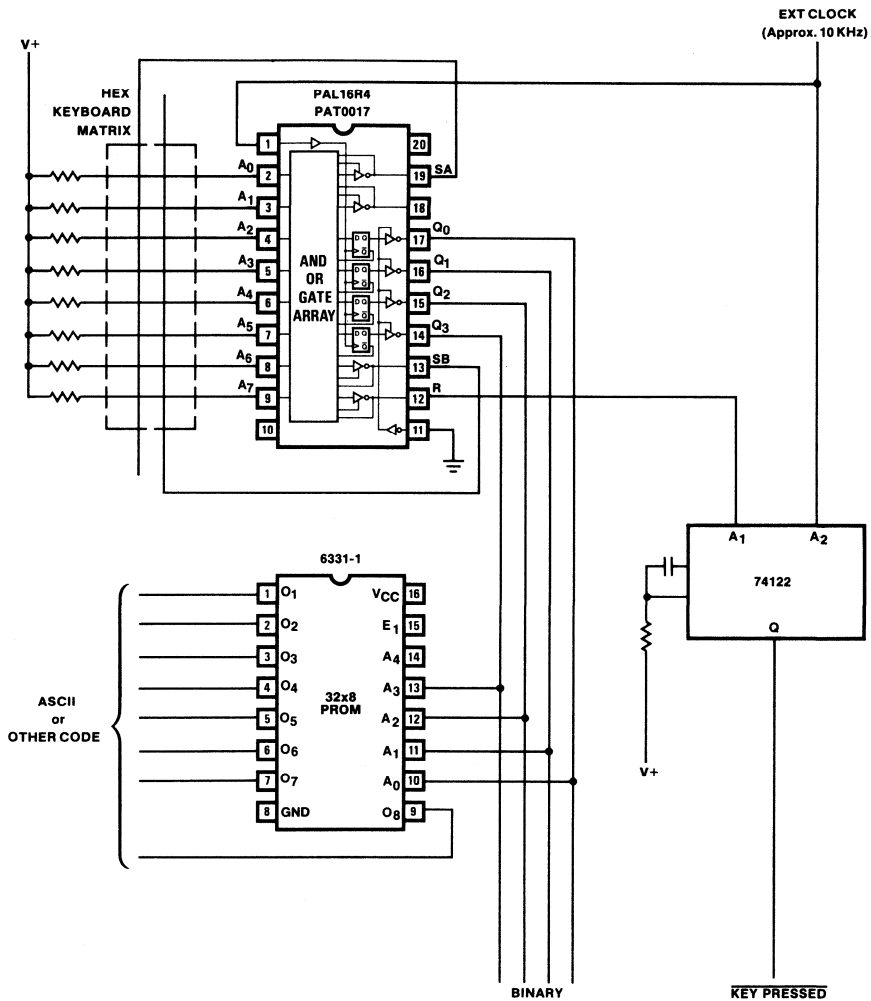

Hex Keyboard Scanner

Design Specification PAL16R4

PAL16R4  
 PAT0017  
 HEX KEYBOARD SCANNER

PAL DESIGN SPECIFICATION  
 VIC NEWTON 12/15/77

CLK A0 A1 A2 A3 A4 A5 A6 A7 GND /EN R SB Q3 Q2 Q1 Q0 NC SA VCC

$$\text{IF ( VCC ) } \text{/SA} = \text{/Q3}$$

$$\begin{aligned} \text{IF ( VCC ) } \text{/NC} = & \text{/A0}\cdot\text{/Q0}\cdot\text{/Q1}\cdot\text{/Q2} + \text{/A1}\cdot\text{Q0}\cdot\text{Q1}\cdot\text{/Q2} + \\ & \text{/A2}\cdot\text{Q0}\cdot\text{Q1}\cdot\text{/Q2} + \text{/A3}\cdot\text{Q0}\cdot\text{Q1}\cdot\text{Q2} + \\ & \text{/A4}\cdot\text{/Q0}\cdot\text{/Q1}\cdot\text{Q2} + \text{/A5}\cdot\text{Q0}\cdot\text{/Q1}\cdot\text{Q2} + \\ & \text{/A6}\cdot\text{/Q0}\cdot\text{Q1}\cdot\text{Q2} \end{aligned}$$

$$\text{/Q0} := \text{Q0}\cdot\text{R} + \text{/Q0}\cdot\text{/R}$$

$$\text{/Q1} := \text{Q0}\cdot\text{Q1}\cdot\text{R} + \text{/Q0}\cdot\text{/Q1}\cdot\text{R} + \text{/Q1}\cdot\text{/R}$$

$$\text{/Q2} := \text{Q0}\cdot\text{Q1}\cdot\text{Q2}\cdot\text{R} + \text{/Q0}\cdot\text{/Q2}\cdot\text{R} + \text{/Q1}\cdot\text{/Q2}\cdot\text{R} + \text{/Q2}\cdot\text{/R}$$


$$\text{/Q3} := \text{Q0}\cdot\text{Q1}\cdot\text{Q2}\cdot\text{Q3}\cdot\text{R} + \text{/Q0}\cdot\text{/Q3}\cdot\text{R} + \text{/Q1}\cdot\text{/Q3}\cdot\text{R} + \text{/Q2}\cdot\text{/Q3}\cdot\text{R} + \text{/Q3}\cdot\text{/R}$$

$$\text{IF ( VCC ) } \text{/SB} = \text{Q3}$$

$$\text{IF ( VCC ) } \text{/R} = \text{/NC} + \text{/A7}\cdot\text{Q0}\cdot\text{Q1}\cdot\text{Q2}$$

DESCRIPTION:

THE KEYBOARD SCANNER WILL SCAN A 16 KEY KEYBOARD ARRANGED IN A 2X8 MATRIX. THE SCANNER WORKS BY SELECTING ONE ROW OF 8 SWITCHES AND THEN SCANNING THE 8 INPUTS. A LOW ON ANY INPUT WILL DISABLE THE CLOCK GOING INTO THE ONE-SHOT. THE ONE-SHOT IS USED AS A DELAY TO ALLOW THE SWITCH BOUNCE TO SETTLE OUT. AT THE END OF THE TIME DELAY (10MS), KEYPRESSED WILL GO LOW. THE OUTPUTS WILL THEN GIVE THE BINARY CODE FOR THE SWITCH SELECTED. WHEN THE SWITCH IS RELEASED, KEYPRESSED WILL GO HIGH, AND SCANNING WILL CONTINUE. WHEN THE END OF THE ROW IS REACHED, THE SCANNER SWITCHES TO THE OTHER ROW AND CONTINUES SCANNING. THE EXTERNAL CLOCK SHOULD RUN IN THE RANGE OF 10 KHZ. IF ASCII OR OTHER CODED CHARACTERS ARE DESIRED, THE BINARY CAN BE CONVERTED USING A PROM.

 

Logic Symbol

Hex Keyboard Scanner

Fuse Pattern PAL16R4

```

-----X-----
XXXX XXXX XXXX XXXX XXXX XXXX XXXX /Q3
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX

-----X-----
-X-----X-----X----- /R0+Q0+Q1+Q2
-----X-----X----- /R1+Q0+Q1+Q2
-----X-----X----- /R2+Q0+Q1+Q2
-----X-----X----- /R3+Q0+Q1+Q2
-----X-----X----- /R4+Q0+Q1+Q2
-----X-----X----- /R5+Q0+Q1+Q2
-----X-----X----- /R6+Q0+Q1+Q2

-----X----- Q0+R
-----X----- /Q0+R
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX

-----X----- Q0+Q1+R
-----X----- /Q0+Q1+R
-----X----- /Q1+R
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX

-----X----- Q0+Q1+Q2+R
-----X----- /Q0+Q2+R
-----X----- /Q1+Q2+R
-----X----- /Q2+R
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX

-----X----- Q0+Q1+Q2+Q3+R
-----X----- /Q0+Q3+R
-----X----- /Q1+Q3+R
-----X----- /Q2+Q3+R
-----X----- /Q3+R
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX

-----X----- Q3
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX


-----X----- /NC
-----X----- /R7+Q0+Q1+Q2
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX

```



Hex Keyboard Scanner

Logic Diagram PAL16R4

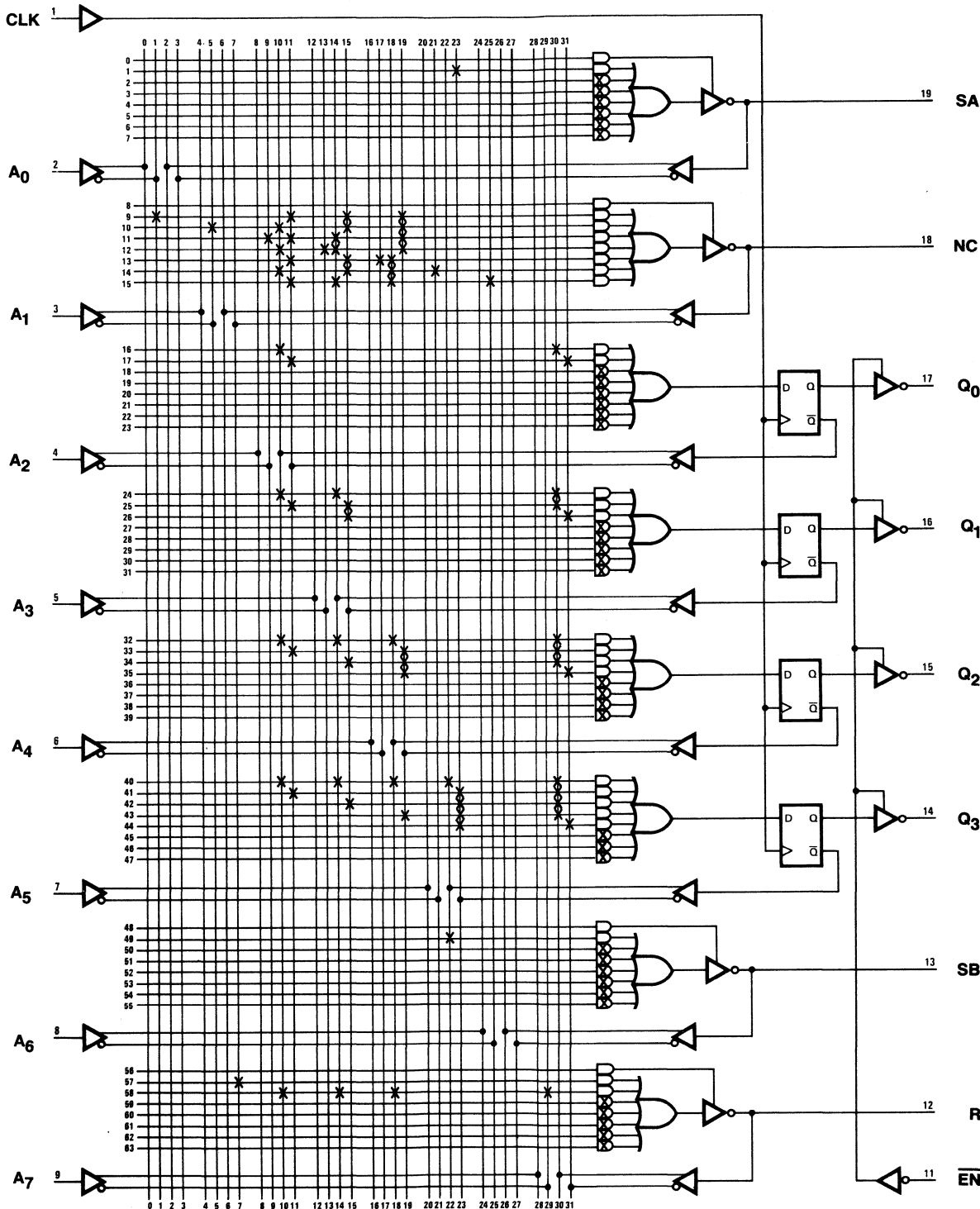

5



# Applications

## Micro Floppy Control Logic



5

*The floppy disk, and its smaller brother the micro-floppy, are becoming increasingly popular as mass storage devices on small systems. Most of these small systems are destined for high volume applications, so all possible production cost economies must be made. The disc controller is the most complicated (and expensive) portion of the disc sub-system, and this example shows how a PAL can be used to reduce the cost and size of the controller for a micro-floppy disc controller.*

Portion of Micro Floppy Control Logic

Design Specification PAL14H4

PAL14H4  
 PAT0024  
 PORTION OF MICRO FLOPPY CONTROL LOGIC

PAL DESIGN SPECIFICATION  
 BOB BOSNYAK 12/16/77

SCK T Q1 WCK Q2 /WE CRB WCRC /Q3 GND Q4 CD DD CRB DATABT SCREG SDREG N2 N1 VCC

$$SDREG = T \cdot Q1 \cdot \overline{WE} + SCK \cdot \overline{WE} + WE \cdot WCK$$


$$SCREG = Q2 \cdot Q1 \cdot WE + SCK \cdot \overline{WE} + WE \cdot WCK$$

$$DATABT = CRB \cdot WE \cdot WCRC + Q2 + T \cdot \overline{WE} \cdot \overline{Q3} + \overline{WCRC} \cdot WE \cdot DD$$

$$CKB = Q2 \cdot Q4 + T \cdot \overline{WE} + WE \cdot CD$$

DESCRIPTION:


PORTION OF FLOPPY DISC CONTROL LOGIC

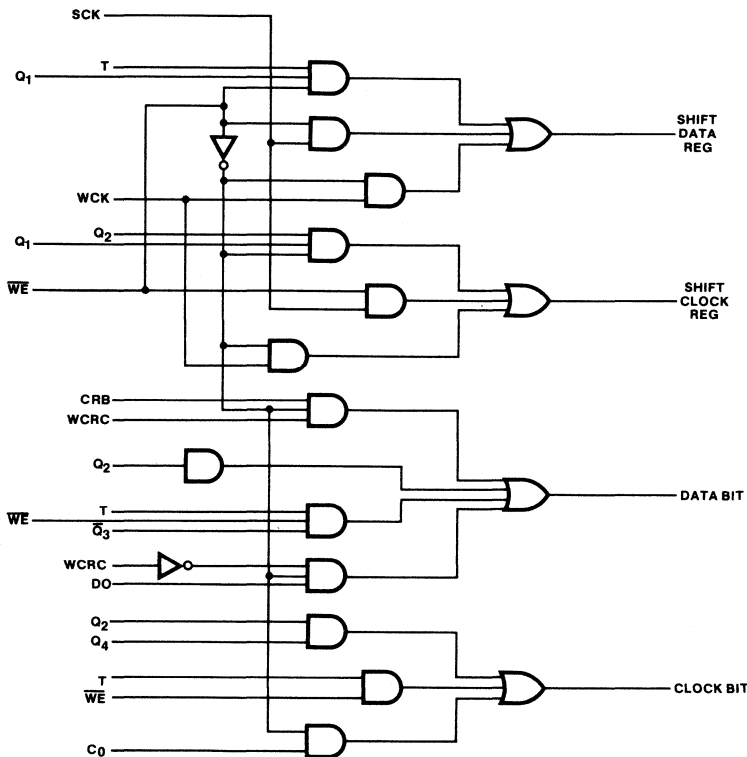



Portion of Micro Floppy Control Logic

Logic Diagram PAL14H4

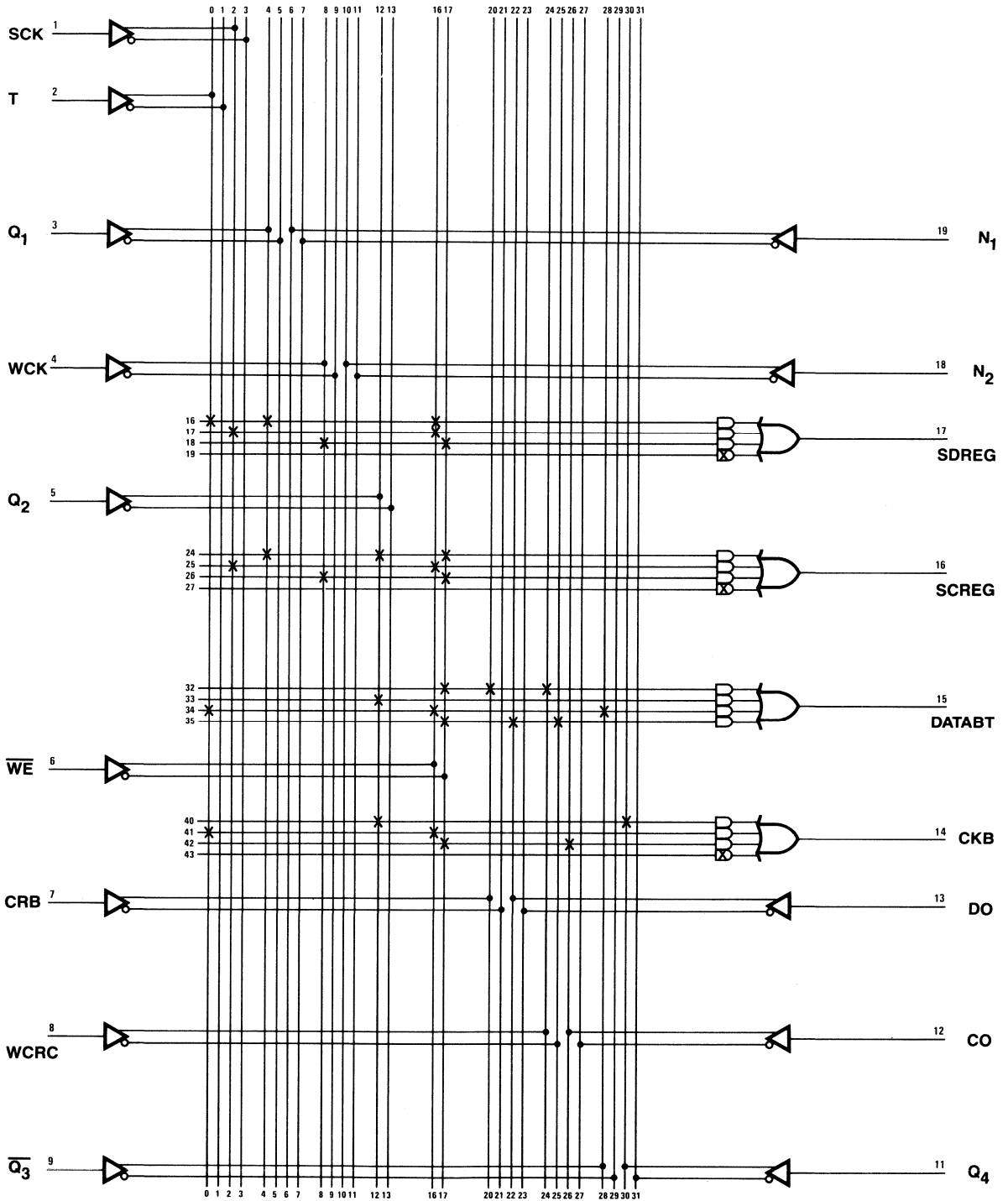

# Applications

## Between Limits Comparator



5

*In many systems applications it is desirable to keep a running check on the data passing by certain points in the system. This can be done for systems security or simply as a part of system diagnosis and self-checking. In various cases the limit checker may search for specific values, missing values, values in a specific range, or values out of a specific range. This example shows a PAL in a microcomputer bus watching application typical of many system limit checking requirements.*





## Between Limits Comparator/Register

## Design Specification PAL16X4

PAL16X4  
 PAT0020  
 BETWEEN LIMITS COMPARATOR / REGISTER

PAL DESIGN SPECIFICATION  
 JOHN BIRKNER 12/18/77

CLK LOAD CLEAR B0 B1 B2 B3 NC NC GND /E NC /EQ A3 A2 A1 A0 /LT /GT VCC

$$\text{IF (VCC) LT} = (\overline{A3} \cdot \overline{B3}) + (\overline{A2} \cdot \overline{B2}) + (\overline{A1} \cdot \overline{B1}) + (\overline{A0} \cdot \overline{B0}) + (A3 \cdot EQ \cdot B3) + (A2 \cdot EQ \cdot B2) + (A1 \cdot EQ \cdot B1) + (A0 \cdot EQ \cdot B0)$$

$$\text{IF (VCC) GT} = (\overline{A3} \cdot B3) + (\overline{A2} \cdot B2) + (\overline{A1} \cdot B1) + (\overline{A0} \cdot B0) + (A3 \cdot EQ \cdot B3) + (A2 \cdot EQ \cdot B2) + (A1 \cdot EQ \cdot B1) + (A0 \cdot EQ \cdot B0)$$

$$\overline{A0} := (\overline{A0}) \cdot \overline{\text{LOAD}} \cdot \overline{\text{CLEAR}} + (\overline{B0}) \cdot \overline{\text{LOAD}} \cdot \overline{\text{CLEAR}}$$

$$\overline{A1} := (\overline{A1}) \cdot \overline{\text{LOAD}} \cdot \overline{\text{CLEAR}} + (\overline{B1}) \cdot \overline{\text{LOAD}} \cdot \overline{\text{CLEAR}}$$

$$\overline{A2} := (\overline{A2}) \cdot \overline{\text{LOAD}} \cdot \overline{\text{CLEAR}} + (\overline{B2}) \cdot \overline{\text{LOAD}} \cdot \overline{\text{CLEAR}}$$

$$\overline{A3} := (\overline{A3}) \cdot \overline{\text{LOAD}} \cdot \overline{\text{CLEAR}} + (\overline{B3}) \cdot \overline{\text{LOAD}} \cdot \overline{\text{CLEAR}}$$

$$\text{IF (VCC) EQ} = (A3 \cdot EQ \cdot B3) + (A2 \cdot EQ \cdot B2) + (A1 \cdot EQ \cdot B1) + (A0 \cdot EQ \cdot B0)$$

## DESCRIPTION:

THE DEVICE CONTINUOUSLY COMPARES THE VALUE OF BUS, B, WITH THE VALUE OF REGISTER A AND REPORTS THE STATUS ON OUTPUTS GT, LT, AND EQ. GT INDICATES THAT B IS GREATER THAN A. LT INDICATES THAT B IS LESS THAN A. EQ INDICATES THAT A IS EQUAL TO B. THE VALUE OF REGISTER A MAY BE REWRITTEN BY LOWERING ENABLE LINE, /E. REGISTER A IS LOADED WITH THE VALUE ON BUS, B, WHEN THE LOAD LINE IS HIGH AND THE CLEAR LINE IS LOW ON THE LOW TO HIGH TRANSITION OF THE CLOCK.


## FUNCTION TABLE:

! LOAD !	CLEAR !	CLOCK !	REGISTER A !	OPERATION !
! L !	! L !	! L-H !	! A !	! NOP !
! X !	! H !	! L-H !	! ALL HIGH !	! CLEAR !
! H !	! L !	! L-H !	! B !	! LOAD B !



Between Limits Comparator/Register

Logic Diagram PAL16X4

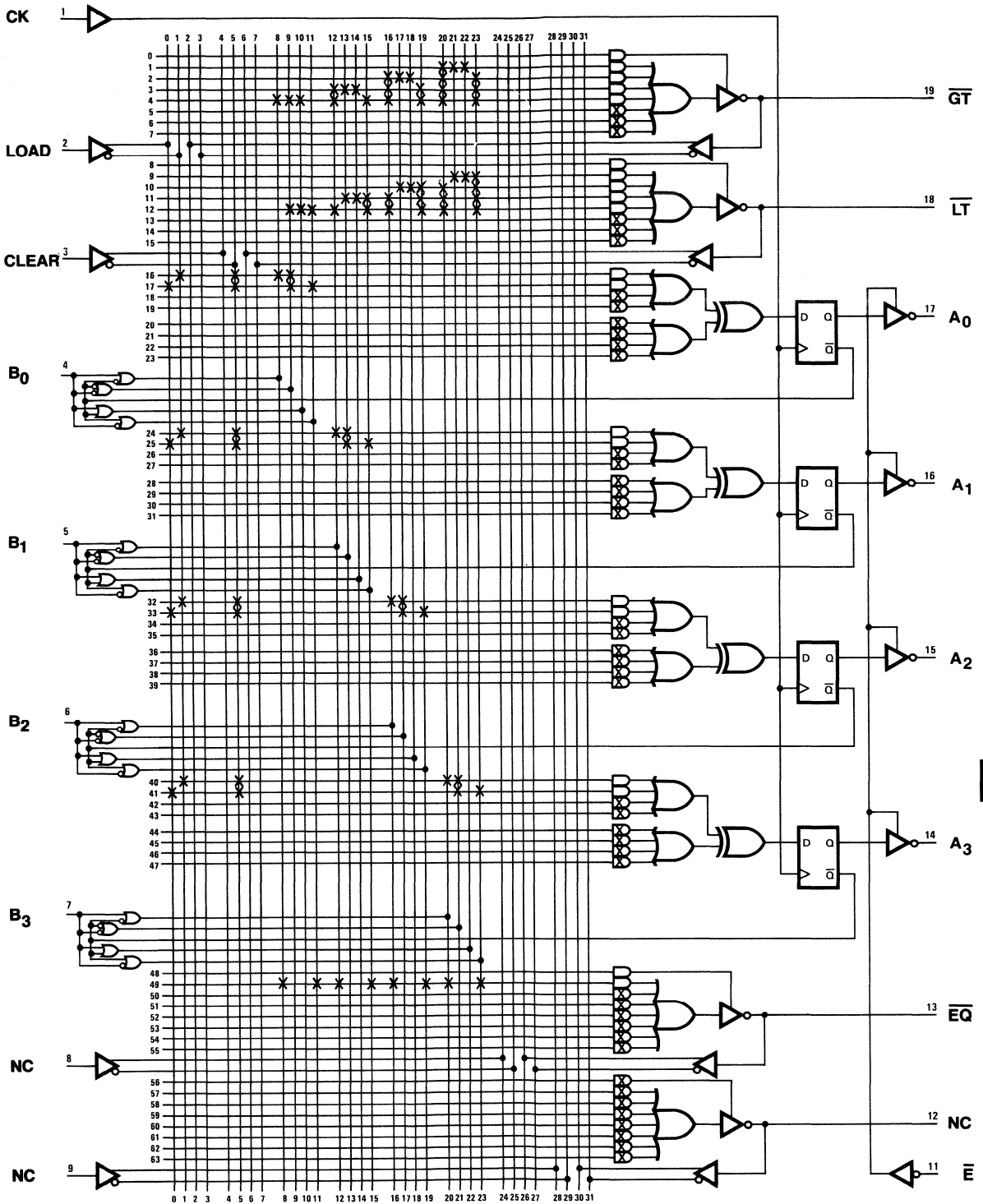

5

Between Limits Comparator/Logic

Design Specification PAL16C1

PAL16C1  
 PAT0021  
 BETWEEN LIMITS COMPARITOR / LOGIC


PAL DESIGN SPECIFICATION  
 JOHN BIRKNER 12/18/77

/EQ1U /LT1 /EQ1L /GT2 /EQ2U /LT2 /EQ2L /GT3 /EQ3U GND  
 /LT3 /EQ3L NC NC NC /BTWL /GT0 /LT0 /GT1 VCC

$$\begin{aligned} /BTWL = & GT3 + GT2 \cdot EQ3U + GT1 \cdot EQ3U \cdot EQ2U + GT0 \cdot EQ3U \cdot EQ2U \cdot EQ1U + \\ & LT3 + LT2 \cdot EQ3L + LT1 \cdot EQ3L \cdot EQ2L + LT0 \cdot EQ3L \cdot EQ2L \cdot EQ1L \end{aligned}$$

DESCRIPTION:

 THE BETWEEN LIMITS LOGIC DETERMINES THE BTWL STATUS AS A FUNCTION OF THE GT, LT AND EQ STATUS FROM THE COMPARITOR REGISTERS.




Logic Symbol




Between Limits/Comparator/Logic

Logic Diagram PAL16C1

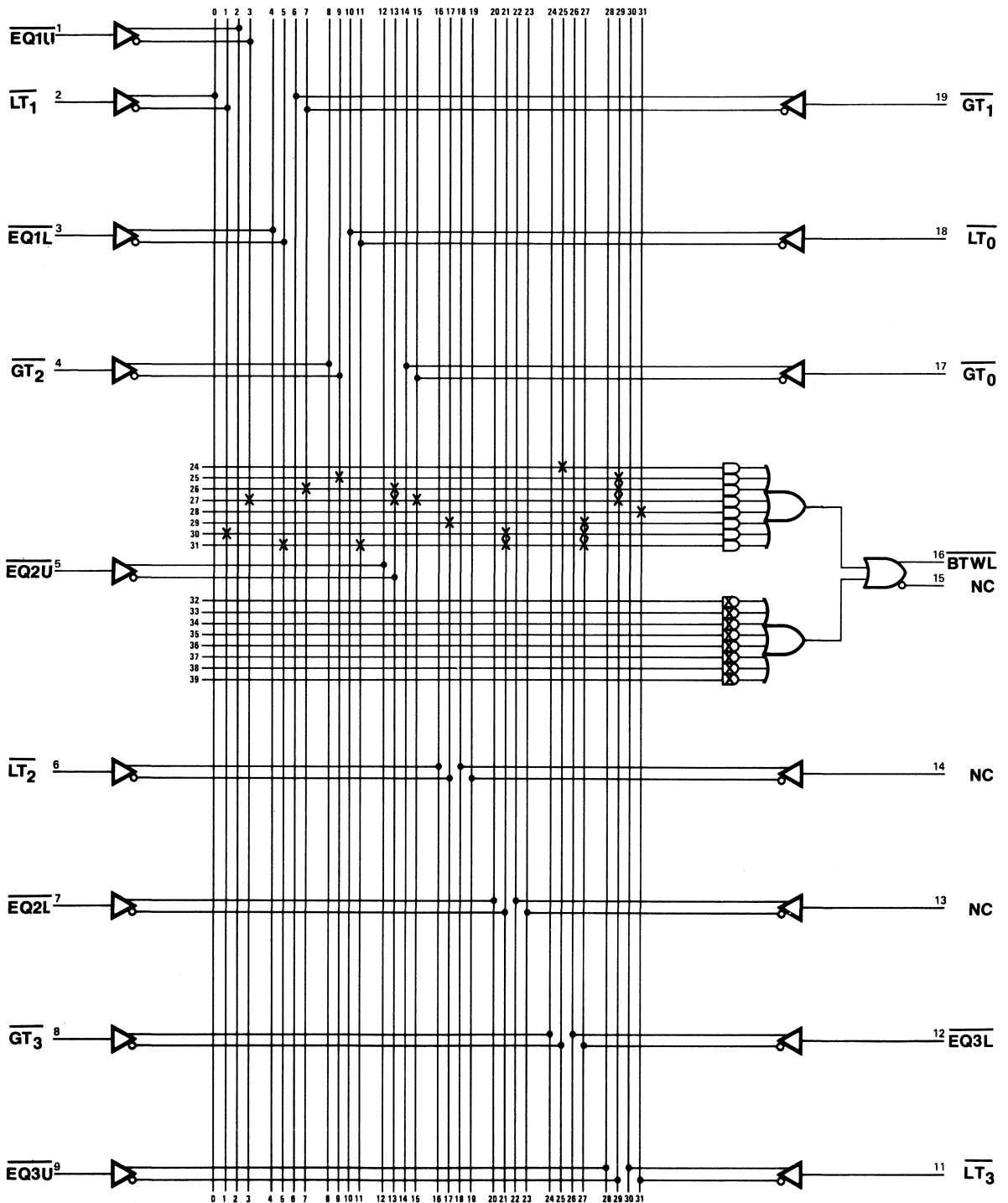

# Applications

## Binary to BCD

 

5

*One of the most common system requirements is the conversion between various code formats. In computer systems the normal codes used are binary, while most peripheral devices exchange data in codes based on BCD. (Both EBCDIC and ASCII codes can be considered in this class.) Whenever data is exchanged between these systems there is a high probability that some data will require code conversion. The PAL in this example performs binary to BCD conversion. In many applications this can be used to speed system operation by replacing slow software conversions with a low cost, fast hardware code converter.*





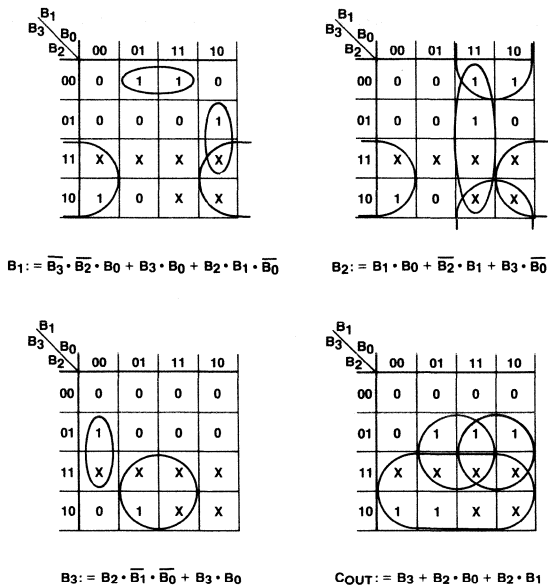


Figure 4, Karnaugh Maps

## Pal Implementation

The PAL16R8 implements two BCD digits. One of the pins is assigned to the clear (CLR) function. The BCD conversion register must be initialized to zero before shifting of the binary input data is started. The eight output registers are assigned to the two BCD digits.

At this point, it seems that we are short of one output pin for the C<sub>OUT</sub> in expanding to more BCD digits. However, the basic equations indicate that C<sub>OUT</sub> is a function of the four preceding BCD bits. Therefore, by inputting these four bits to the next stage, the C<sub>OUT</sub> is derived internally by the latter stage. A similar trick is used in each chip to cascade internally.

This expansion solution implies that in the least significant BCD stage the equation is:

$$(1) BO = C_{IN}$$

whereas in later stages the equation is:

$$(2) BO = C_{13} + C_{12} \cdot C_{10} + C_{12} \cdot C_{11}$$

where the C terms are driven by the corresponding B terms of a preceding stage. However, in order to have a universal solution, we OR the two equations. If the PAL is used as the least significant stage C<sub>10</sub>, C<sub>11</sub>, C<sub>12</sub> and C<sub>13</sub> are grounded and equation (1) holds. If the PAL is used as an intermediate stage, C<sub>IN</sub> is grounded and equation (2) holds.

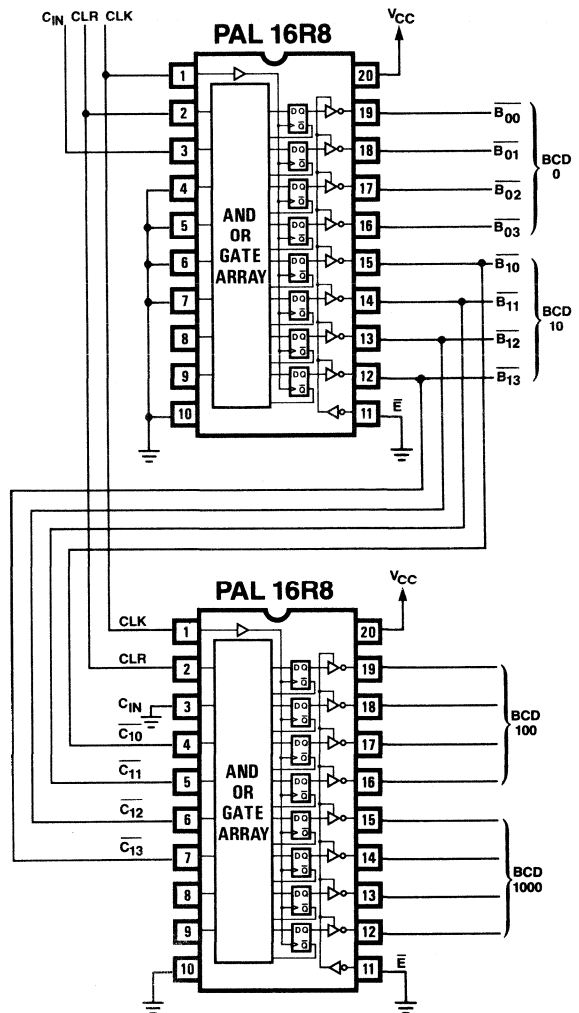


Figure 5, Logic Schematic

## Summary

A similar algorithm was described in Ref. 2, where the two BCD digits were implemented with four ICs and could be clocked at 80 ns. Here we described one chip implementation that can be clocked at 60 ns.

## References

1. "Binary to BCD Conversion Techniques" by B. MacDonald, EDN Dec. 1, 1969.
2. "Special PROM Mode Effects Binary to BCD Converter", by D.M. Brockman, Electronics.

**Binary to BCD Converter**

**Design Specification PAL16R8**

PAL16R8  
 PAT014  
 BINARY TO BCD CONVERTER

PAL DESIGN SPECIFICATION  
 SHLOMO WASER 1/6/78

CK /CLR CIN /C10 /C11 /C12 /C13 NC NC GND  
 /E /B13 /B12 /B11 /B10 /B03 /B02 /B01 /B00 VCC

$$B00 := \text{/CLR} \cdot \text{CIN} + \text{/CLR} \cdot \text{C13} + \text{/CLR} \cdot \text{C12} \cdot \text{C10} + \text{/CLR} \cdot \text{C12} \cdot \text{C11}$$

$$B01 := \text{/CLR} \cdot \text{/B03} \cdot \text{/B02} \cdot \text{B00} + \text{/CLR} \cdot \text{B03} \cdot \text{/B00} + \text{/CLR} \cdot \text{B02} \cdot \text{B01} \cdot \text{/B00}$$

$$B02 := \text{/CLR} \cdot \text{B01} \cdot \text{B00} + \text{/CLR} \cdot \text{/B02} \cdot \text{B01} + \text{/CLR} \cdot \text{B03} \cdot \text{/B00}$$

$$B03 := \text{/CLR} \cdot \text{B02} \cdot \text{/B01} \cdot \text{/B00} + \text{/CLR} \cdot \text{B03} \cdot \text{B00}$$


$$B10 := \text{/CLR} \cdot \text{B03} + \text{/CLR} \cdot \text{B02} \cdot \text{B00} + \text{/CLR} \cdot \text{B02} \cdot \text{B01}$$

$$B11 := \text{/CLR} \cdot \text{/B13} \cdot \text{/B12} \cdot \text{B10} + \text{/CLR} \cdot \text{B13} \cdot \text{/B10} + \text{/CLR} \cdot \text{B12} \cdot \text{B11} \cdot \text{/B10}$$

$$B12 := \text{/CLR} \cdot \text{B11} \cdot \text{B10} + \text{/CLR} \cdot \text{/B12} \cdot \text{B11} + \text{/CLR} \cdot \text{B13} \cdot \text{/B10}$$

$$B13 := \text{/CLR} \cdot \text{B12} \cdot \text{/B11} \cdot \text{/B10} + \text{/CLR} \cdot \text{B13} \cdot \text{B10}$$

DESCRIPTION: SEE TEXT

 

Binary to BCD Converter

Fuse Pattern PAL16R8

```

X--- X--- ---- ---- ---- ---- /CLR♦CIN
0--- ---- ---- ---- -X--- ---- /CLR♦C13
X--- ---- -X--- -X--- -X--- ---- /CLR♦C12♦C10
X--- ---- -X--- -X--- -X--- ---- /CLR♦C12♦C11
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX

X-X- ---- -X- -X- ---- ---- /CLR♦/B03♦/B02♦B00
X-X- ---- -X- -X- ---- ---- /CLR♦B03♦/B00
X-X- ---- -X- -X- ---- ---- /CLR♦B02♦B01♦/B00
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX

X-X- ---- -X- -X- ---- ---- /CLR♦B01♦B00
X-X- ---- -X- -X- ---- ---- /CLR♦/B02♦B01
X-X- ---- -X- -X- ---- ---- /CLR♦B03♦/B00
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX

X-X- -X- -X- ---- ---- /CLR♦B02♦/B01♦/B00
0-X- ---- -X- -X- ---- ---- /CLR♦B03♦B00
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX

X--- ---- -X- -X- ---- ---- /CLR♦B03
X-X- ---- -X- -X- ---- ---- /CLR♦B02♦B00
X-X- ---- -X- -X- ---- ---- /CLR♦B02♦B01
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX

X--- ---- ---- ---- -X- -X- -X- /CLR♦/B13♦/B12♦B10
X--- ---- ---- ---- -X- -X- -X- /CLR♦B13♦/B10
X--- ---- ---- ---- -X- -X- -X- /CLR♦B12♦B11♦/B10
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX


X--- ---- ---- ---- -X- -X- ---- /CLR♦B11♦B10
X--- ---- ---- ---- -X- -X- ---- /CLR♦/B12♦B11
X--- ---- ---- ---- -X- -X- ---- /CLR♦B13♦/B10
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX

X--- ---- ---- ---- -X- -X- -X- /CLR♦B12♦/B11♦/B10
X--- ---- ---- ---- -X- -X- -X- /CLR♦B13♦B10
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX

```


Binary to BCD Converter

Logic Diagram PAL16R8

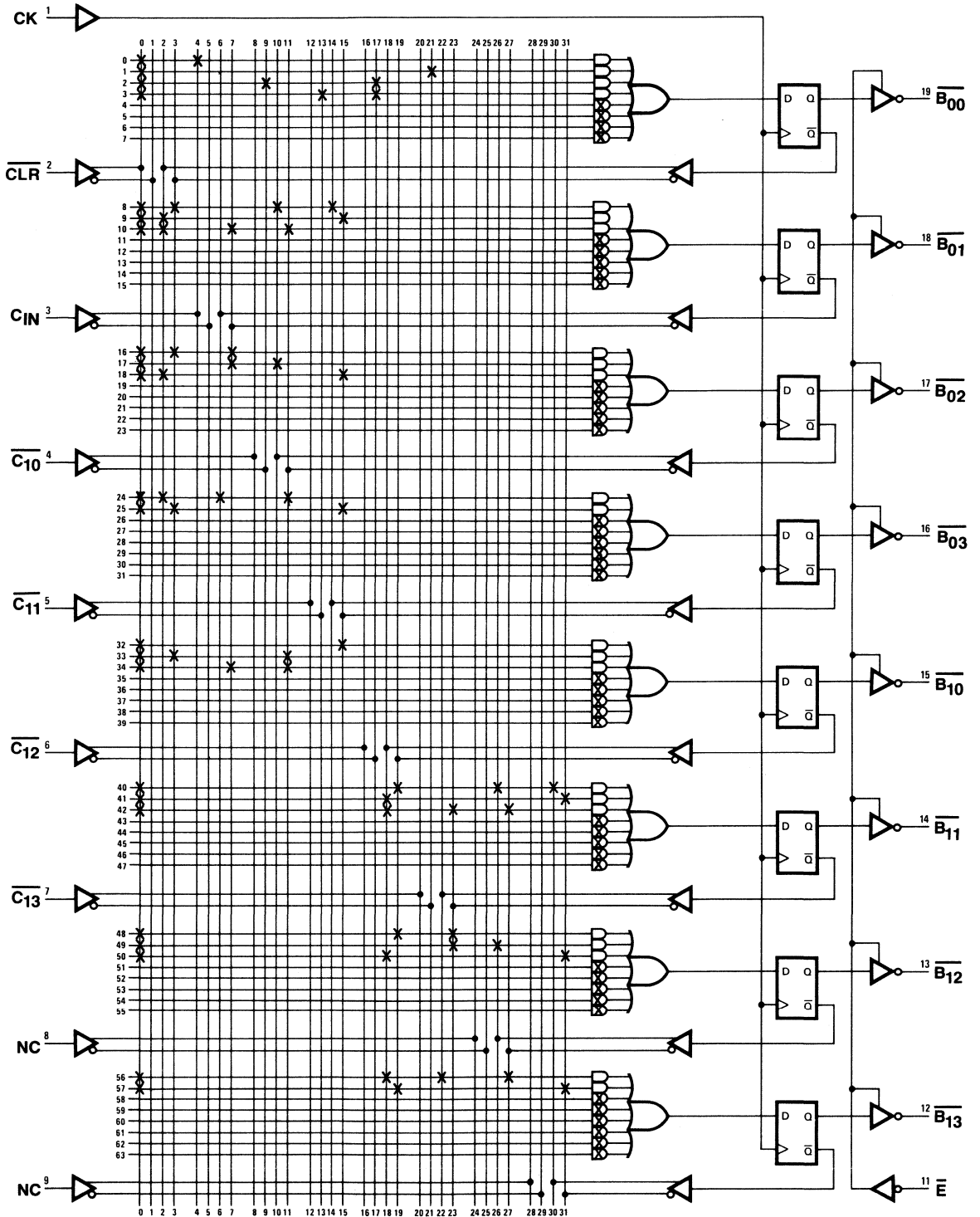

# Applications

## Electronic Dice Game

 

5

*A dice game can be implemented using a simple state sequencer and an oscillator. When the oscillator is running (ROLL), the dual modulo six counter increments through all possible states. When the free running oscillator is stopped, a random count will appear on the outputs.*

*In one die there are six states (1 through 6). In a set of dice there are six states on the one die for each of the six states of the other (36 states in all). Since the two dice are very similar it is possible to design one die and use the equations from it to design the second. Two designs will be shown. First, an eight chip SSI/MSI solution, then, a single chip PAL solution.*



Logic Design Using Standard TTL

In one die, seven LEDs make up the display (Figure 1). Notice they can be connected such that only four lines are required to drive them. The LEDs are turned on when the appropriate line is driven low. Since there are four lines to be driven it is necessary to use four D-type flip-flops for each die. For reference the outputs of the flip-flops are labeled Q<sub>1</sub>-Q<sub>4</sub> and the inputs are labeled D<sub>1</sub>-D<sub>4</sub> (Figure 2). By using the inverting output of the Flip-Flop we can use positive logic in the design. That is, a logical "1" at a Q output represents an LED being turned on.

 


Figure 1

Looking at the Karnaugh Maps (Figure 3), it may be noticed that the simplest logic equations were not generated. This was to insure a path to a valid state from all invalid states.

 


Figure 2

The present state of table 1 shows the preferred sequence in which the LEDs should turn on. The next state shows the conditions necessary to increment when clocked. From these two tables the Karnaugh Maps of Figure 3 were made. Using the Karnaugh Maps the following equations are obtained;

$$D_1 = \bar{Q}_1 Q_2 Q_3 \quad D_2 = \bar{Q}_1 Q_3 + \bar{Q}_1 Q_4$$

$$D_3 = \bar{Q}_3 \quad D_4 = \bar{Q}_1 Q_2 + \bar{Q}_1 Q_4$$

These equations satisfy the requirements for one die. By substituting Q<sub>5</sub>-Q<sub>8</sub> for Q<sub>1</sub>-Q<sub>4</sub> and D<sub>5</sub>-D<sub>8</sub> for D<sub>1</sub>-D<sub>4</sub> we have the following equations;

$$D_5 = \bar{Q}_5 Q_6 Q_7 \quad D_6 = \bar{Q}_5 Q_7 + \bar{Q}_5 Q_8$$

$$D_7 = \bar{Q}_7 \quad D_8 = \bar{Q}_5 \bar{Q}_7 + \bar{Q}_5 Q_8$$

STATE	PRESENT STATE				NEXT STATE			
	Q <sub>4</sub>	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	D <sub>4</sub>	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>
1	0	1	0	0	0	0	1	0
2	0	0	1	0	1	1	0	0
3	1	1	0	0	1	0	1	0
4	1	0	1	0	1	1	1	0
5	1	1	1	0	1	0	1	1
6	1	0	1	1	0	1	0	0

Table 1

# Applications

**D<sub>1</sub> KARNAUGH MAP**

$Q_3 \backslash Q_2$	$Q_1$ 00	01	11	10
00	X	0	X	X
01	X	0	0	X
11	0	1	X	X
10	0	X	X	X

**D<sub>2</sub> KARNAUGH MAP**

$Q_3 \backslash Q_2$	$Q_1$ 00	01	11	10
00	X	0	X	X
01	X	1	0	X
11	1	1	X	X
10	1	X	X	X

**D<sub>3</sub> KARNAUGH MAP**

$Q_3 \backslash Q_2$	$Q_1$ 00	01	11	10
00	X	1	X	X
01	X	1	1	X
11	0	0	X	X
10	0	X	X	X

**D<sub>4</sub> KARNAUGH MAP**

$Q_3 \backslash Q_2$	$Q_1$ 00	01	11	10
00	X	1	X	X
01	X	1	0	X
11	1	1	X	X
10	0	X	X	X

Note: X means Don't Care

Figure 3

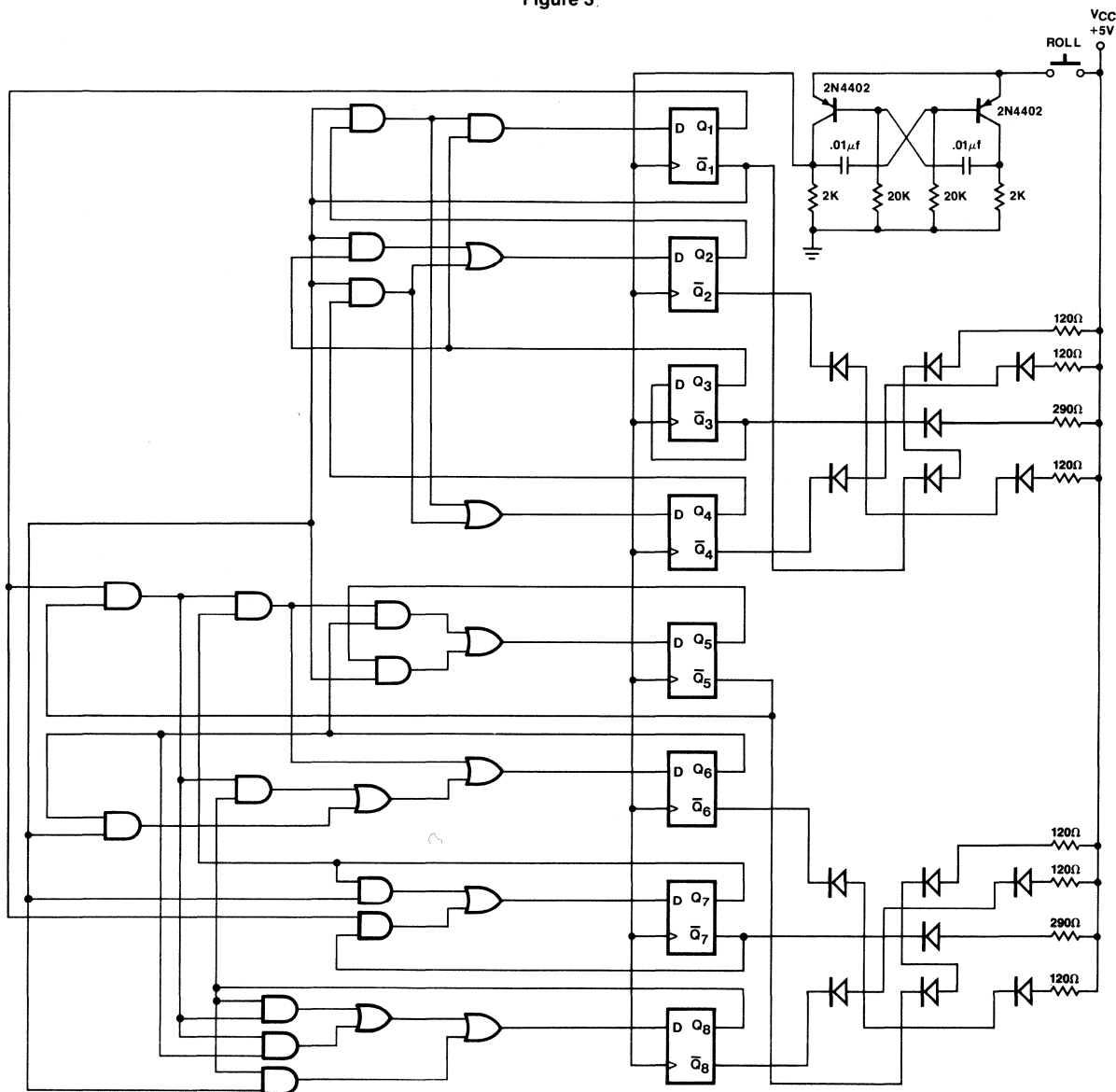


Figure 4



However, since this is a synchronous design the clocks of the two die are common. If the same equations are used for both die there will be only six different states. To get around this the first die is allowed to go through each of the six states incrementing with each clock. The second die is inhibited from incrementing except when the first die goes from the 6th state to the 1st state. At this time the second die is allowed to increment one time. Looking at the present state of table 1 it is noticed that whenever output  $Q_1$  is high, the next clock should increment the second die. Whenever  $Q_1$  is low the second die should remain the same. From this we now write all the equations.


$$\begin{aligned}
 D_1 &= \overline{Q_1} Q_2 Q_3 \\
 D_2 &= \overline{Q_1} Q_3 + \overline{Q_1} Q_4 \\
 D_3 &= \overline{Q_3} \\
 D_4 &= \overline{Q_1} Q_2 + \overline{Q_1} Q_4 \\
 D_5 &= \overline{Q_1} Q_5 + Q_1 \overline{Q_5} Q_6 Q_7 \\
 D_6 &= \overline{Q_1} Q_6 + Q_1 \overline{Q_5} Q_7 + Q_1 \overline{Q_5} Q_8 \\
 D_7 &= \overline{Q_1} Q_7 + Q_1 \overline{Q_7} \\
 D_8 &= \overline{Q_1} Q_8 + Q_1 \overline{Q_5} Q_6 + Q_1 \overline{Q_5} Q_8
 \end{aligned}$$

From these equations the logic diagram can be drawn. (Figure 4)
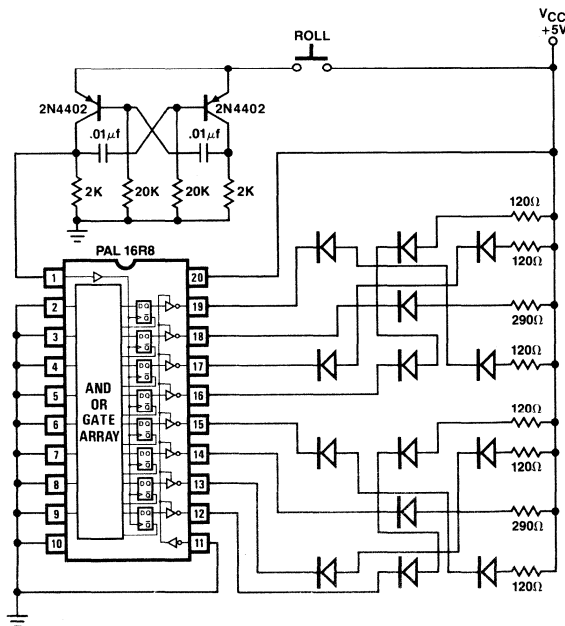
## Logic Design Using PALs

The design requires 8 registered outputs. Looking at the PAL Data Sheet we determine that a PAL16R8 best suits this application. The equations developed above can be used here without change. The PAL Design Specification shows the implementation of these equations.

Using this arbitrary pinout, however, makes the PC board layout awkward. Thus, another PAL Design Specification is shown with the pinouts chosen to convenience the PC board layout. This design is chosen for the circuit diagram of figure 5.



## Applications

### Rules for CRAPS

The following is a set of rules that apply whether you are playing in Las Vegas with dice or at home with a PAL.

The first roll is called the come-out and you win on a 7 or 11 or you "crap-out" on a 2 (snake eyes), 3 (ace caught a deuce) or 12 (box cars). If none of the above happens you will have rolled a number between 4 and 10. Mark this number well, you will need to roll it again to win. At this point no "crap" can hurt you, but unless you've programmed your PAL right, a seven can. Normal probabilities in 36 throws:

7 will appear	6 times
6	5
8	5
5	4
9	4
4	3
10	3
3	2
11	2
2	1
12	1



**Electronic Dice Game**

**Design Specification PAL16R8**

PAL16R8  
 PAT0001  
 ELECTRONIC DICE GAME

PAL DESIGN SPECIFICATION  
 ED VETTER 12/8/77

CK NC NC NC NC NC NC NC NC GND /E /08 /07 /06 /05 /04 /03 /02 /01 VCC

$$Q1 := /Q1 \oplus Q2 \oplus Q3$$

$$Q2 := /Q1 \oplus Q3 + /Q1 \oplus Q4$$

$$Q3 := /Q3$$

$$Q4 := /Q1 \oplus Q2 + /Q1 \oplus Q4$$

$$Q5 := Q1 \oplus /Q5 \oplus Q6 \oplus Q7 + /Q1 \oplus Q5$$


$$Q6 := Q1 \oplus /Q5 \oplus Q7 + Q1 \oplus /Q5 \oplus Q8 + /Q1 \oplus Q6$$

$$Q7 := Q1 \oplus /Q7 + /Q1 \oplus Q7$$

$$Q8 := Q1 \oplus /Q5 \oplus Q6 + Q1 \oplus /Q5 \oplus Q8 + /Q1 \oplus Q8$$

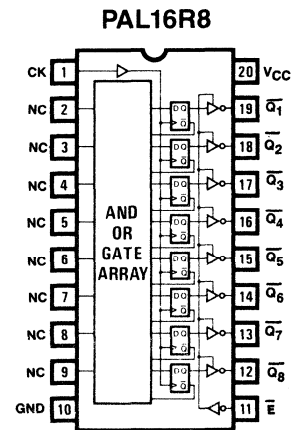**DESCRIPTION:**

THE DUAL MODULO-SIX COUNTER INCREMENTS ON THE RISING EDGE OF THE CLOCK INPUT (CK). THE THREE-STATE OUTPUTS ARE HIGH-Z WHEN THE ENABLE LINE (/E) IS HIGH AND ENABLED WHEN ENABLE LINE (/E) IS LOW. THERE ARE 36 DIFFERENT STATES TO THE COUNT SEQUENCE; EACH STATE CORRESPONDS TO ONE OF THE NUMBER COMBINATIONS TO BE DISPLAYED ON THE DICE. (SEE NEXT PAGE)



Electronic Dice Game

State Sequence Table PAL16R8

0	0	0	0	0	0	0	0	0	NUMBER	DISPLAYED
1	2	3	4	5	6	7	8		DIE 2	- DIE 1
H	H	L	H	H	H	L	H	1	-	1
H	L	H	H	H	H	L	H	2	-	1
H	H	L	L	H	H	L	H	3	-	1
H	L	L	L	H	H	L	H	4	-	1
H	L	L	L	H	H	L	H	5	-	1
L	L	H	L	H	H	L	H	6	-	1
H	H	L	H	H	L	H	H	1	-	2
H	L	H	L	H	L	H	H	2	-	2
H	H	L	L	H	L	H	H	3	-	2
H	L	H	L	H	L	H	H	4	-	2
H	L	L	L	H	L	H	H	5	-	2
L	L	H	L	H	L	H	H	6	-	2
H	H	L	H	H	H	L	L	1	-	3
H	L	H	H	H	H	L	L	2	-	3
H	H	L	L	H	H	L	L	3	-	3
H	L	H	L	H	H	L	L	4	-	3
H	L	L	L	H	H	L	L	5	-	3
L	L	H	L	H	H	L	L	6	-	3
H	H	L	H	H	L	H	L	1	-	4
H	L	H	H	H	L	H	L	2	-	4
H	H	L	L	H	L	H	L	3	-	4
H	L	H	L	H	L	H	L	4	-	4
H	L	L	L	H	L	H	L	5	-	4
L	L	H	L	H	L	H	L	6	-	4
H	H	L	H	H	L	L	L	1	-	5
H	L	H	H	H	L	L	L	2	-	5
H	H	L	L	H	L	L	L	3	-	5
H	L	H	L	H	L	L	L	4	-	5
H	L	L	L	H	L	L	L	5	-	5
L	L	H	L	H	L	L	L	6	-	5
H	H	L	H	L	L	H	L	1	-	6
H	L	H	H	L	L	H	L	2	-	6
H	H	L	L	L	L	H	L	3	-	6
H	L	H	L	L	L	H	L	4	-	6
H	L	L	L	L	L	H	L	5	-	6
L	L	H	L	L	L	H	L	6	-	6

Electronic Dice Game

Fuse Pattern PAL16R8

```

--X-  ---X  ---X  ----  ----  ----  ----  ----  /01+02+03
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX

```

```

--X-  ----  ---X  ----  ----  ----  ----  ----  /01+03
--X-  ----  ----  ----  ----  ----  ----  ----  /01+04
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX

```

```

----  ----  --X-  ----  ----  ----  ----  ----  /03
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX

```

```

--X-  ---X  ----  ----  ----  ----  ----  ----  /01+02
--X-  ----  ----  ----  ----  ----  ----  ----  /01+04
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX

```

```

---X  ----  ----  ----  ---X  ---X  ---X  ----  01+05+06+07
--X-  ----  ----  ----  ----  ---X  ----  ----  /01+05
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX

```

```

---X  ----  ----  ----  ---X  ----  ---X  ----  01+05+07
--X-  ----  ----  ----  ----  ---X  ----  ---X  01+05+08
--X-  ----  ----  ----  ----  ----  ---X  ----  /01+06
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX

```

```

---X  ----  ----  ----  ----  ----  ---X  ----  01+07
--X-  ----  ----  ----  ----  ----  ----  ---X  /01+07
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX

```


```

---X  ----  ----  ----  ---X  ---X  ----  ----  01+05+06
---X  ----  ----  ----  ---X  ----  ----  ---X  01+05+08
--X-  ----  ----  ----  ----  ----  ----  ---X  /01+08
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX
XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX  XXXX

```

Electronic Dice Game

Logic Diagram PAL16R8

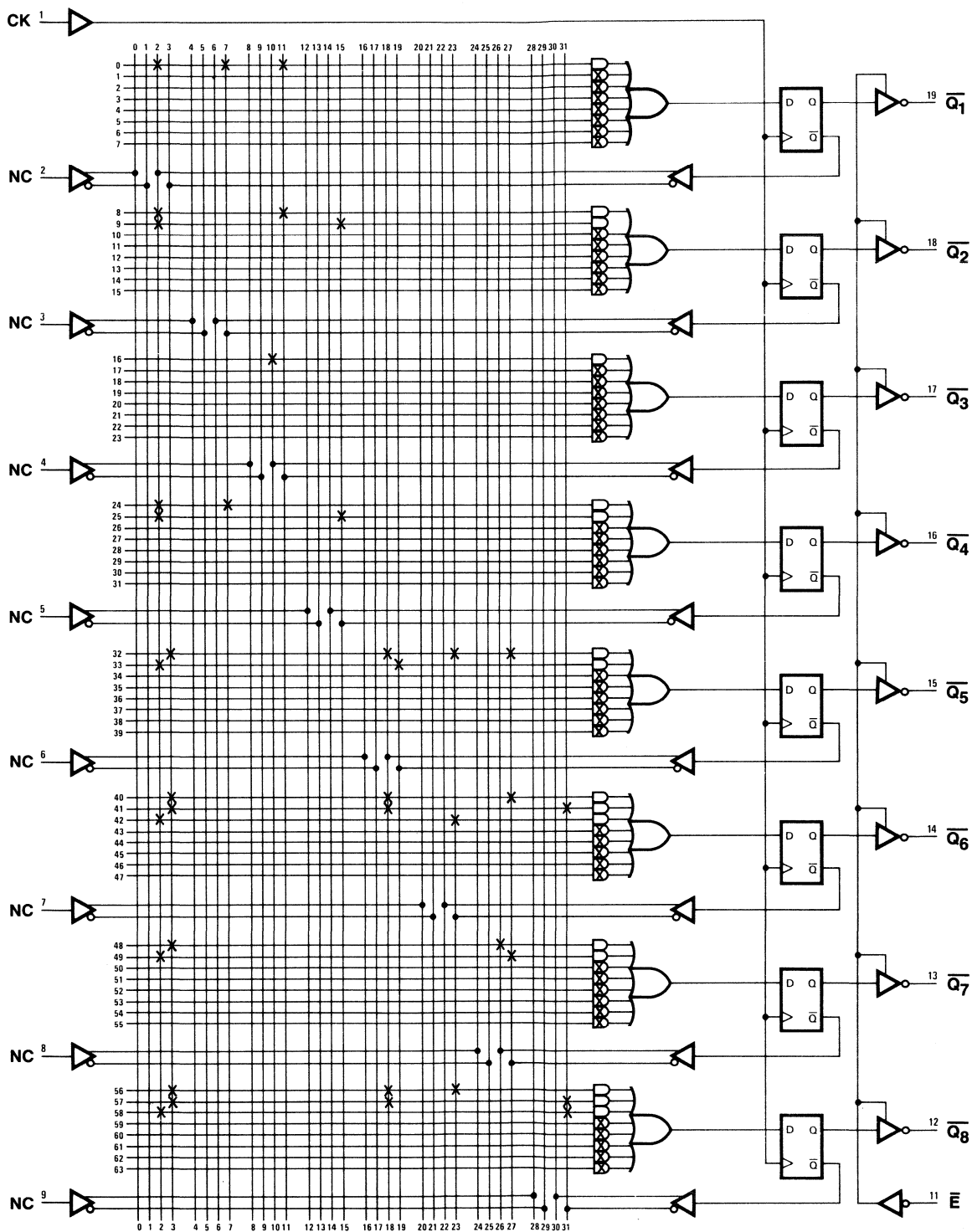

5

**Electronic Dice Game with Pinouts  
to Convenience PC Board Layout**

**Design Specification PAL16R8**

PAL16R8

PAT0002

ELECTRONIC DICE GAME WITH PINOUTS TO CONVENIENCE PC BOARD LAYOUT

PAL DESIGN SPECIFICATION  
ED VETTER 12/9/77

CK NC NC NC NC NC NC NC NC GND /E /05 /08 /07 /06 /01 /04 /03 /02 VCC

$Q_2 := /01 + 03 + /01 + 04$

$Q_3 := /03$

$Q_4 := /01 + 02 + /01 + 04$

$Q_1 := /01 + 02 + 03$

$Q_6 := Q_1 + /05 + 07 + Q_1 + /05 + 08 + /01 + 06$


$Q_7 := Q_1 + /07 + /01 + 07$

$Q_8 := Q_1 + /05 + 06 + Q_1 + /05 + 08 + /01 + 08$

$Q_5 := Q_1 + /05 + 06 + 07 + /01 + 05$

 **DESCRIPTION:**

THE DUAL MODULO-SIX COUNTER INCREMENTS ON THE RISING EDGE OF THE CLOCK INPUT (CK). THE THREE-STATE OUTPUTS ARE HIGH-Z WHEN THE ENABLE LINE (/E) IS HIGH AND ENABLED WHEN ENABLE LINE (/E) IS LOW. THERE ARE 36 DIFFERENT STATES TO THE COUNT SEQUENCE. EACH STATE CORRESPONDS TO ONE OF THE NUMBER COMBINATIONS TO BE DISPLAYED ON THE DICE.



**Logic Symbol**

Electronic Dice Game with Pinouts  
to Convenience PC Board Layout

State Sequence Table PAL16R8


: 0 0 0 0 0 0 0 0 :								NUMBER DISPLAYED			:	
: 2 3 4 1 6 7 8 5 :								DIE 2	-	DIE 1	:	
: H	L	H	H	H	L	H	H	:	1	-	1	:
: L	H	H	H	H	L	H	H	:	2	-	1	:
: H	L	L	H	H	L	H	H	:	3	-	1	:
: L	H	L	H	H	L	H	H	:	4	-	1	:
: L	L	L	H	H	L	H	H	:	5	-	1	:
: L	H	L	L	H	L	H	H	:	6	-	1	:
: H	L	H	H	L	H	H	H	:	1	-	2	:
: L	H	H	H	L	H	H	H	:	2	-	2	:
: H	L	L	H	L	H	H	H	:	3	-	2	:
: L	H	L	H	L	H	H	H	:	4	-	2	:
: L	L	L	H	L	H	H	H	:	5	-	2	:
: L	H	L	L	L	H	H	H	:	6	-	2	:
: H	L	H	H	H	L	L	H	:	1	-	3	:
: L	H	H	H	H	L	L	H	:	2	-	3	:
: H	L	L	H	H	L	L	H	:	3	-	3	:
: L	H	L	H	H	L	L	H	:	4	-	3	:
: L	L	L	H	H	L	L	H	:	5	-	3	:
: L	H	L	L	H	L	L	H	:	6	-	3	:
: H	L	H	H	L	H	L	H	:	1	-	4	:
: L	H	H	H	L	H	L	H	:	2	-	4	:
: H	L	L	H	L	H	L	H	:	3	-	4	:
: L	H	L	H	L	H	L	H	:	4	-	4	:
: L	L	L	H	L	H	L	H	:	5	-	4	:
: L	H	L	L	L	H	L	H	:	6	-	4	:
: H	L	H	H	L	L	L	H	:	1	-	5	:
: L	H	H	H	L	L	L	H	:	2	-	5	:
: H	L	L	H	L	L	L	H	:	3	-	5	:
: L	H	L	H	L	L	L	H	:	4	-	5	:
: L	L	L	H	L	L	L	H	:	5	-	5	:
: L	H	L	L	L	L	L	H	:	6	-	5	:
: H	L	H	H	L	H	L	L	:	1	-	6	:
: L	H	H	H	L	H	L	L	:	2	-	6	:
: H	L	L	H	L	H	L	L	:	3	-	6	:
: L	H	L	H	L	H	L	L	:	4	-	6	:
: L	L	L	H	L	H	L	L	:	5	-	6	:
: L	H	L	L	L	H	L	L	:	6	-	6	:





**Electronic Dice Game with Pinouts to Convenience PC Board Layout**

**Logic Diagram PAL16R8**

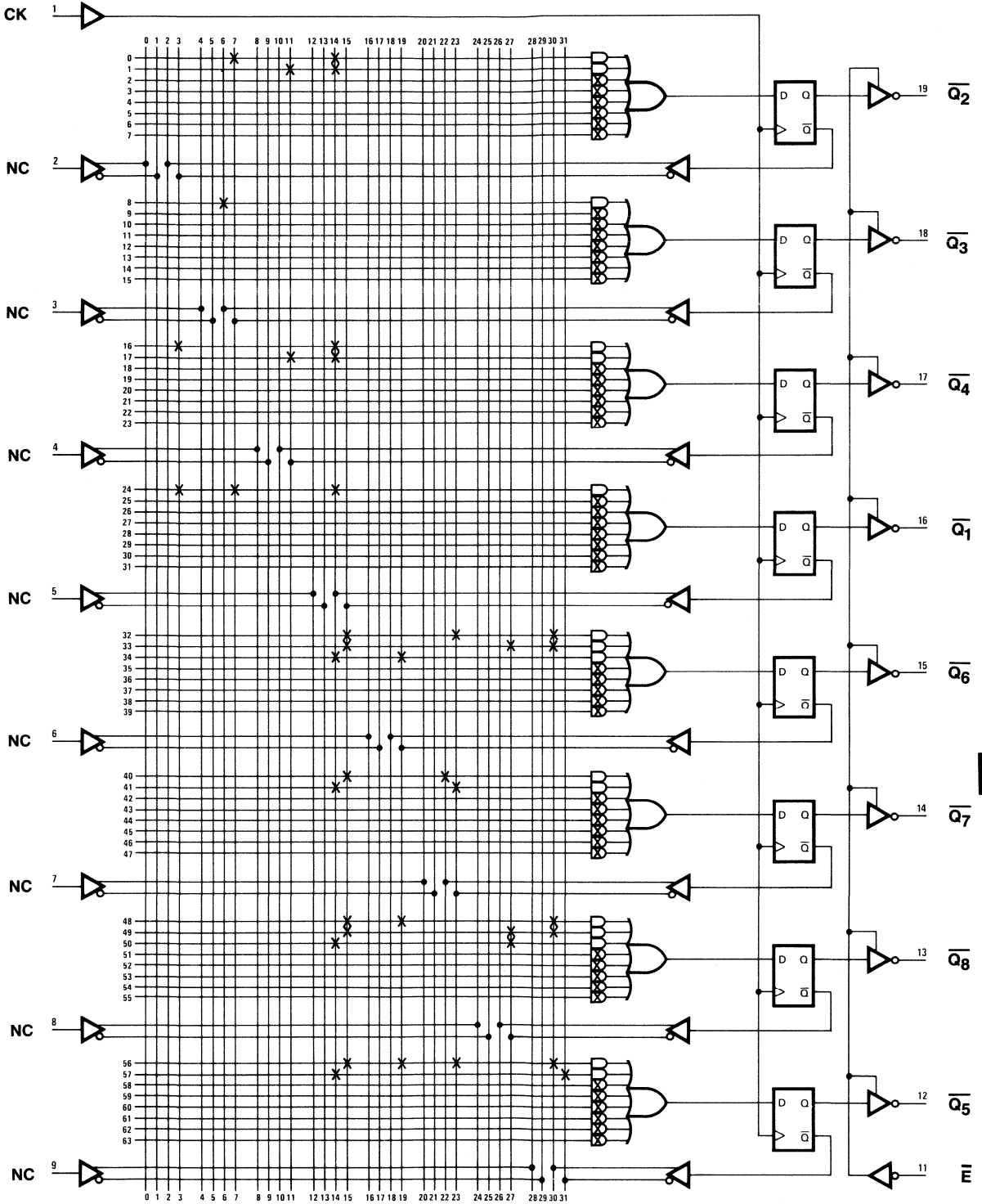



PAL Programming Format

Pal I6R8

Pattern PAT0002

Name ELECTRONIC DICE GAME

For Products 0 thru 31

	0	24 16 8 0	32	25 17 9 1	64	26 18 10 2	96	27 19 11 3	128	28 20 12 4	160	29 21 13 5	192	30 22 14 6	224	31 23 15 7
0	0		32		64		96		128		160		192		224	
1	1		33		65		97		129		161		193		225	
2	2		34		66		98		130		162		194		226	
3	3		35		67		99		131		163		195		227	
4	4		36		68		100		132		164		196		228	
5	5		37		69		101		133		165		197		229	
6	6		38		70		102		134		166		198		230	
7	7		39		71		103		135		167		199		231	
8	8		40		72		104		136		168		200		232	
9	9		41		73		105		137		169		201		233	
10	10		42		74		106		138		170		202		234	
11	11		43		75		107		139		171		203		235	
12	12		44		76		108		140		172		204		236	
13	13		45		77		109		141		173		205		237	
14	14		46		78		110		142		174		206		238	
15	15		47		79		111		143		175		207		239	
16	16		48		80		112		144		176		208		240	
17	17		49		81		113		145		177		209		241	
18	18		50		82		114		146		178		210		242	
19	19		51		83		115		147		179		211		243	
20	20		52		84		116		148		180		212		244	
21	21		53		85		117		149		181		213		245	
22	22		54		86		118		150		182		214		246	
23	23		55		87		119		151		183		215		247	
24	24		56		88		120		152		184		216		248	
25	25		57		89		121		153		185		217		249	
26	26		58		90		122		154		186		218		250	
27	27		59		91		123		155		187		219		251	
28	28		60		92		124		156		188		220		252	
29	29		61		93		125		157		189		221		253	
30	30		62		94		126		158		190		222		254	
31	31		63		95		127		159		191		223		255	

For Products 32 thru 63

	0	56 48 40 32	288	57 49 41 33	320	58 50 42 34	352	59 51 43 35	384	60 52 44 36	416	61 53 45 37	448	62 54 46 38	480	63 55 47 39
0	256		288		320		352		384		416		448		480	
1	257		289		321		353		385		417		449		481	
2	258		290		322		354		386		418		450		482	
3	259		291		323		355		387		419		451		483	
4	260		292		324		356		388		420		452		484	
5	261		293		325		357		389		421		453		485	
6	262		294		326		358		390		422		454		486	
7	263		295		327		359		391		423		455		487	
8	264		296		328		360		392		424		456		488	
9	265		297		329		361		393		425		457		489	
10	266		298		330		362		394		426		458		490	
11	267		299		331		363		395		427		459		491	
12	268		300		332		364		396		428		460		492	
13	269		301		333		365		397		429		461		493	
14	270		302		334		366		398		430		462		494	
15	271		303		335		367		399		431		463		495	
16	272		304		336		368		400		432		464		496	
17	273		305		337		369		401		433		465		497	
18	274		306		338		370		402		434		466		498	
19	275		307		339		371		403		435		467		499	
20	276		308		340		372		404		436		468		500	
21	277		309		341		373		405		437		469		501	
22	278		310		342		374		406		438		470		502	
23	279		311		343		375		407		439		471		503	
24	280		312		344		376		408		440		472		504	
25	281		313		345		377		409		441		473		505	
26	282		314		346		378		410		442		474		506	
27	283		315		347		379		411		443		475		507	
28	284		316		348		380		412		444		476		508	
29	285		317		349		381		413		445		477		509	
30	286		318		350		382		414		446		478		510	
31	287		319		351		383		415		447		479		511	

5



# Applications

**and ... HERE'S MORE!!**




**5**

*This section presents more PAL examples used in various systems. Some of the applications present PAL equivalents of standard logic functions. At first glance this may not seem useful. However, consider the case of the standard logic function that is "almost correct". If any special functions are required SSI/MSI logic must be added with an increase in cost. The PAL version of the same function can probably be modified internally to accommodate the change with no additional parts.*



Three Phase Micro Engine

Logic Diagram PAL16R8

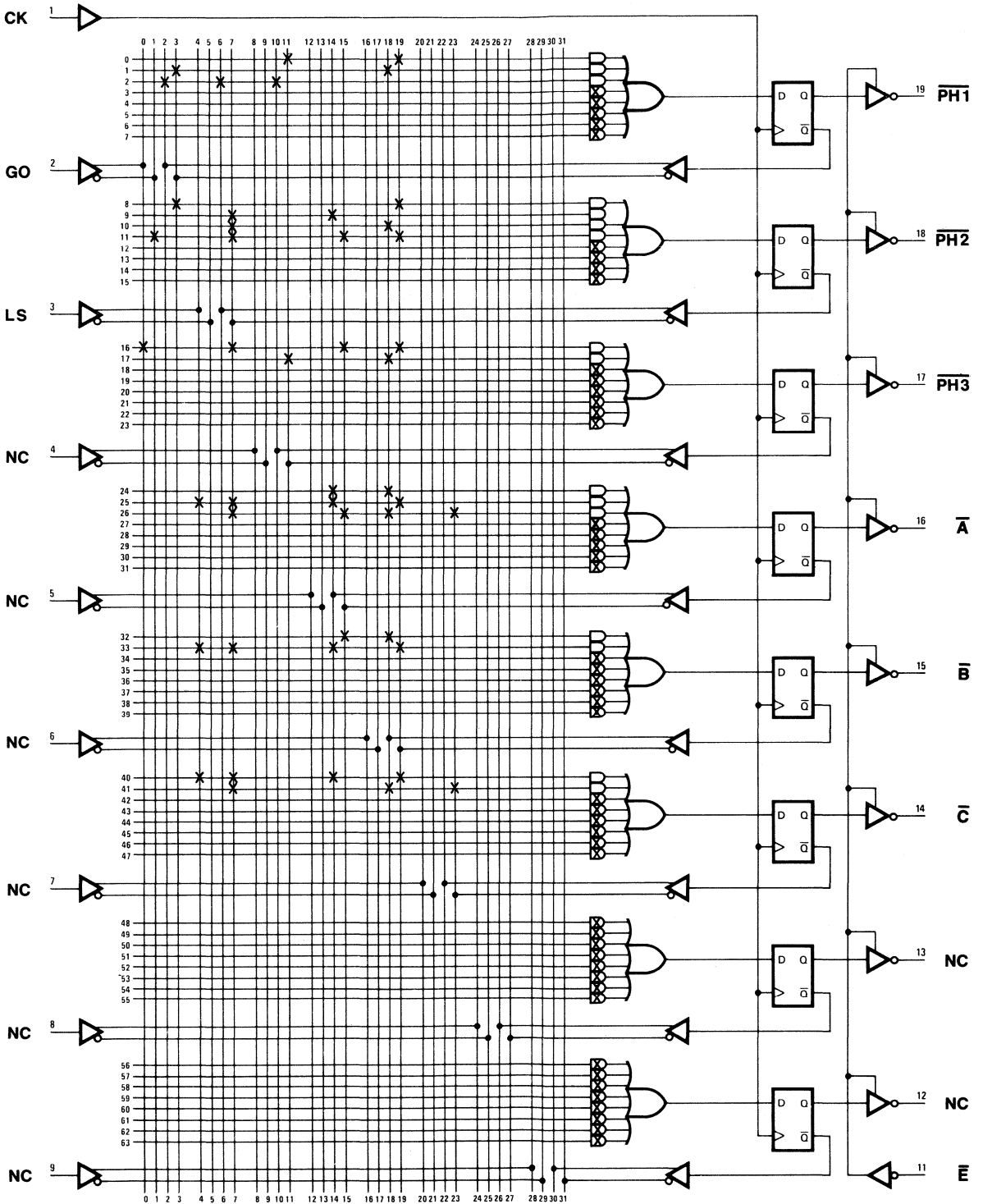

5

**8 Bit I/O Priority Interrupt Encoder with Registers**

**Design Specification PAL16R4**

PAL16R4

PAL DESIGN SPECIFICATION

PAT0005

PAUL ZAGAR 12/12/77

8 BIT I/O PRIORITY INTERRUPT ENCODER WITH REGISTERS

CK I1 I2 I3 I4 I5 I6 I7 I8 GND /E NC NC Q4 Q3 Q2 Q1 NC NC VCC

$$/Q1 := /I1+I2 + /I1+/I2+/I3+I4 + /I1+/I2+/I3+/I4+/I5+I6 + /I1+/I2+/I3+/I4+/I5+/I6+/I7+I8$$

$$/Q2 := /I1+/I2+I3 + /I1+/I2+/I3+I4 + /I1+/I2+/I3+/I4+/I5+/I6+I7 + /I1+/I2+/I3+/I4+/I5+/I6+/I7+I8$$

$$/Q3 := /I1+/I2+/I3+/I4+I5 + /I1+/I2+/I3+/I4+/I5+I6 + /I1+/I2+/I3+/I4+/I5+/I6+I7 + /I1+/I2+/I3+/I4+/I5+/I6+/I7+I8$$

$$/Q4 := I1+I2+I3+I4+I5+I6+I7+I8$$

**DESCRIPTION:**

THE I/O PRIORITY INTERRUPT ENCODER PRIORITIZES 8 I/O LINES (I1 THRU I8) OUTPUTTING I11 (Q3,Q2,&Q1 RESPECTIVELY) FOR THE HIGHEST PRIORITY I/O DEVICE (I1) AND 000 FOR AN INTERRUPT FROM THE LOWEST PRIORITY I/O DEVICE (I8). OUTPUT Q4 SERVES AS THE INTERRUPT FLAG AND GOES LOW WHEN ANY OF THE 8 I/O INPUTS GO HIGH. THE PRIORITY INTERRUPT ENCODER REGISTERS ARE UPDATED ON THE RISING EDGE OF THE CLOCK INPUT (CK). THE 3-STATE OUTPUTS ARE HIGH-Z WHEN THE ENABLE LINE (/E) IS HIGH AND ENABLED WHEN THE ENABLED LINE (/E) IS LOW.


**TRUTH TABLE**

/ I	I	I	I	I	I	I	I	I	0	0	0	0
E	8	7	6	5	4	3	2	1	4	3	2	1
H	X	X	X	X	X	X	X	X	Z	Z	Z	Z
L	X	X	X	X	X	X	X	H	L	H	H	H
L	X	X	X	X	X	X	H	L	L	H	H	L
L	X	X	X	X	X	H	L	L	L	H	L	H
L	X	X	X	X	H	L	L	L	L	H	L	L
L	X	X	X	H	L	L	L	L	L	L	H	H
L	X	X	H	L	L	L	L	L	L	L	H	L
L	X	H	L	L	L	L	L	L	L	L	L	H
L	H	L	L	L	L	L	L	L	L	L	L	L
L	L	L	L	L	L	L	L	L	H	H	H	H



8 Bit I/O Priority Interrupt Encoder with Registers

Logic Diagram PAL16R4

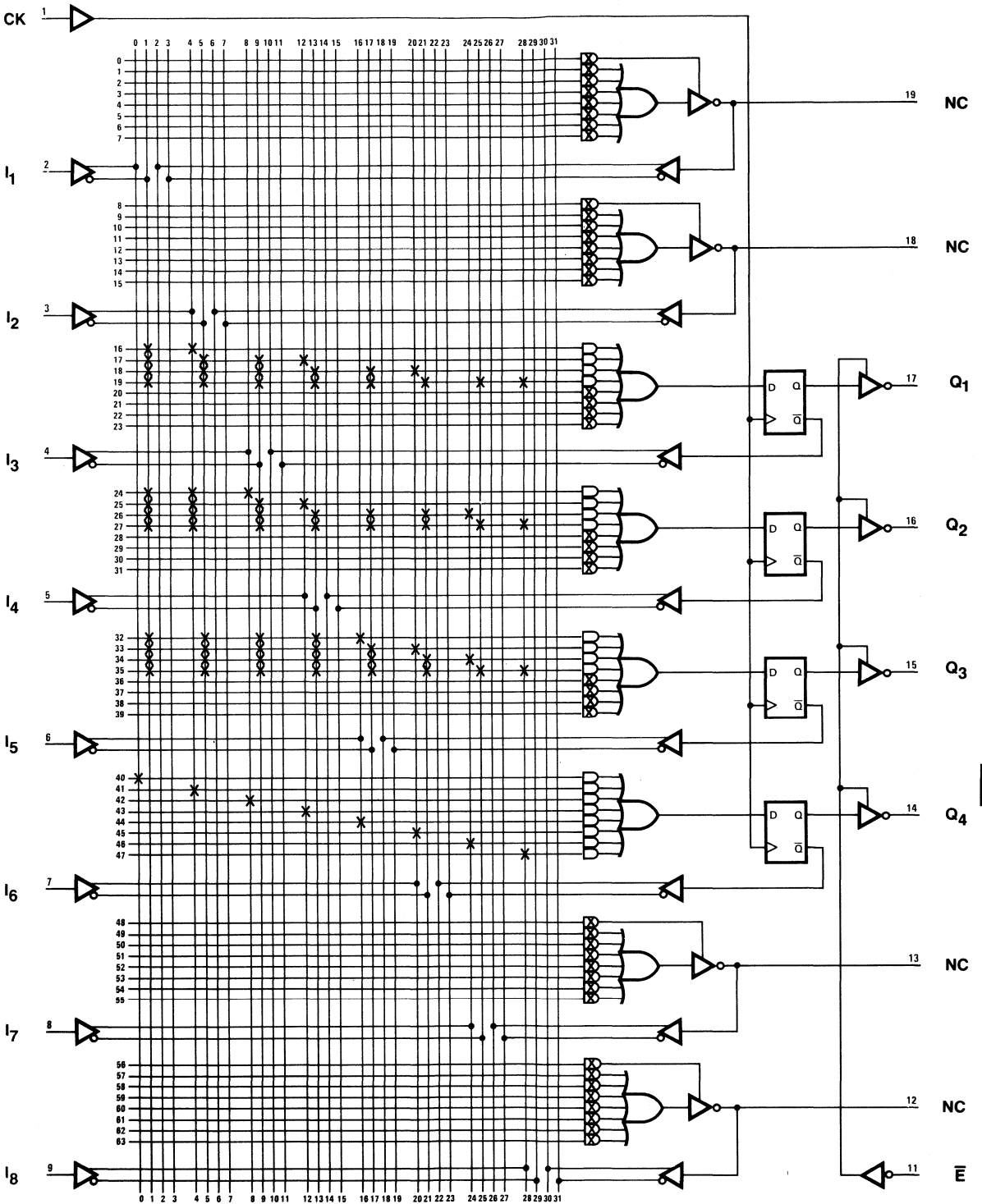

**Quadruple 3-Line-to-1-Line Data Selector Multiplexer**

**Design Specification PAL14H4**

PAL14H4

PAL DESIGN SPECIFICATION

PAT0016

VIC NEWTON 12/21/77

QUADRUPLE 3-LINE-TO-1-LINE DATA SELECTOR MULTIPLEXER

1A 2A 3A 4A 1B 2B 3B 4B 1C GND 2C 3C 4C 4Y 3Y 2Y 1Y S1 S0 VCC

$$1Y = 1A \cdot \overline{S0} \cdot \overline{S1} + 1B \cdot S0 \cdot \overline{S1} + 1C \cdot \overline{S0} \cdot S1$$

$$2Y = 2A \cdot \overline{S0} \cdot \overline{S1} + 2B \cdot S0 \cdot \overline{S1} + 2C \cdot \overline{S0} \cdot S1$$

$$3Y = 3A \cdot \overline{S0} \cdot \overline{S1} + 3B \cdot S0 \cdot \overline{S1} + 3C \cdot \overline{S0} \cdot S1$$

$$4Y = 4A \cdot \overline{S0} \cdot \overline{S1} + 4B \cdot S0 \cdot \overline{S1} + 4C \cdot \overline{S0} \cdot S1$$

**DESCRIPTION:**

A 4-BIT WORD IS SELECTED FROM ONE OF THREE SOURCES AND IS ROUTED TO THE FOUR OUTPUTS. TRUE DATA IS PRESENTED AT THE OUTPUTS. IF INVERTED DATA IS DESIRED, USE THE SAME EQUATIONS WITH THE PAL14L4.

**FUNCTION TABLE:**

S0	S1	OUTPUTS
L	L	A DATA
H	L	B DATA
L	H	C DATA
H	H	LOW

1A	1	+	+	20 VCC
2A	2	+	+	19 S0
3A	3	+	+	18 S1
4A	4	+	+	17 1Y
1B	5	+	+	16 2Y
2B	6	+	+	15 3Y
3B	7	+	+	14 4Y
4B	8	+	+	13 4C
1C	9	+	+	12 3C
GND	10	+	+	11 2C


PINOUT





4-Bit Counter with 2 Input Mux

Logic Diagram PAL16R4

 

5

6-Bit Shift Register with Three-State Outputs

Design Specification PAL16R6

PAL16R6

PAT0005

6-BIT SHIFT REGISTER WITH THREE-STATE OUTPUTS

PAL DESIGN SPECIFICATION  
JOHN BIRKNER 11/20/77

CK SR D0 D1 D2 D3 D4 D5 SL GND /E RILO Q5 Q4 Q3 Q2 Q1 Q0 LIRO VCC

IF ( SR+SL ) /LIRO = /Q0

/Q0 := /SR+SL+Q0 + SR+SL+Q1 + /SR+SL+LIRO + SR+SL+D0

/Q1 := /SR+SL+Q1 + SR+SL+Q2 + /SR+SL+Q0 + SR+SL+D1

/Q2 := /SR+SL+Q2 + SR+SL+Q3 + /SR+SL+Q1 + SR+SL+D2

/Q3 := /SR+SL+Q3 + SR+SL+Q4 + /SR+SL+Q2 + SR+SL+D3

/Q4 := /SR+SL+Q4 + SR+SL+Q5 + /SR+SL+Q3 + SR+SL+D4

/Q5 := /SR+SL+Q5 + SR+SL+RILO + /SR+SL+Q4 + SR+SL+D5


IF ( /SR+SL ) /RILO = /Q5

DESCRIPTION:

THE 6-BIT SHIFT REGISTER WILL HOLD, SHIFT RIGHT, SHIFT LEFT, OR LOAD ON THE RISING EDGE OF THE CLOCK (CK). THE THREE-STATE OUTPUTS ARE HIGH-Z WHEN THE ENABLE LINE (/E) IS HIGH AND ENABLED WHEN ENABLE LINE (/E) IS LOW.


FUNCTION TABLE

INPUTS				OUTPUTS									
SL	SR	RILO	LIRO	CLOCK	RILO	Q5	Q4	Q3	Q2	Q1	Q0	LIRO	OPERATION
L	L	X	X	L	Z	Q5	Q4	Q3	Q2	Q1	Q0	Z	NOP
L	H	X	X	L	Z	Q5	Q4	Q3	Q2	Q1	Q0	Z	NOP
L	L	X	X	H	Z	Q5	Q4	Q3	Q2	Q1	Q0	Z	NOP
H	H	X	X	H	Z	Q5	Q4	Q3	Q2	Q1	Q0	Z	NOP
L	H	X	X	L	Z	Q5	Q4	Q3	Q2	Q1	Q0	Q0	NOP
L	H	X	X	H	Z	Q5	Q4	Q3	Q2	Q1	Q0	Q0	NOP
H	L	X	X	L	Q5	Q5	Q4	Q3	Q2	Q1	Q0	Z	NOP
H	L	X	X	H	Q5	Q5	Q4	Q3	Q2	Q1	Q0	Z	NOP
L	L	X	X	L-H	Z	Q5	Q4	Q3	Q2	Q1	Q0	Z	HOLD
L	H	RI	X	L-H	Z	RI	Q5	Q4	Q3	Q2	Q1	Q1	RIGHT SHFT
H	L	X	LI	L-H	Q4	Q4	Q3	Q2	Q1	Q0	LI	Z	LEFT SHFT
H	H	X	X	L-H	Z	D5	D4	D3	D2	D1	D0	Z	LOAD D

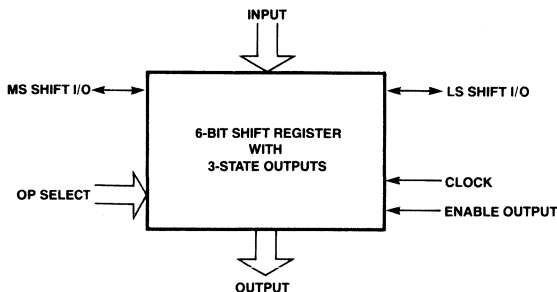

6-Bit Shift Register with Three-State Outputs

Logic Diagram PAL16R6

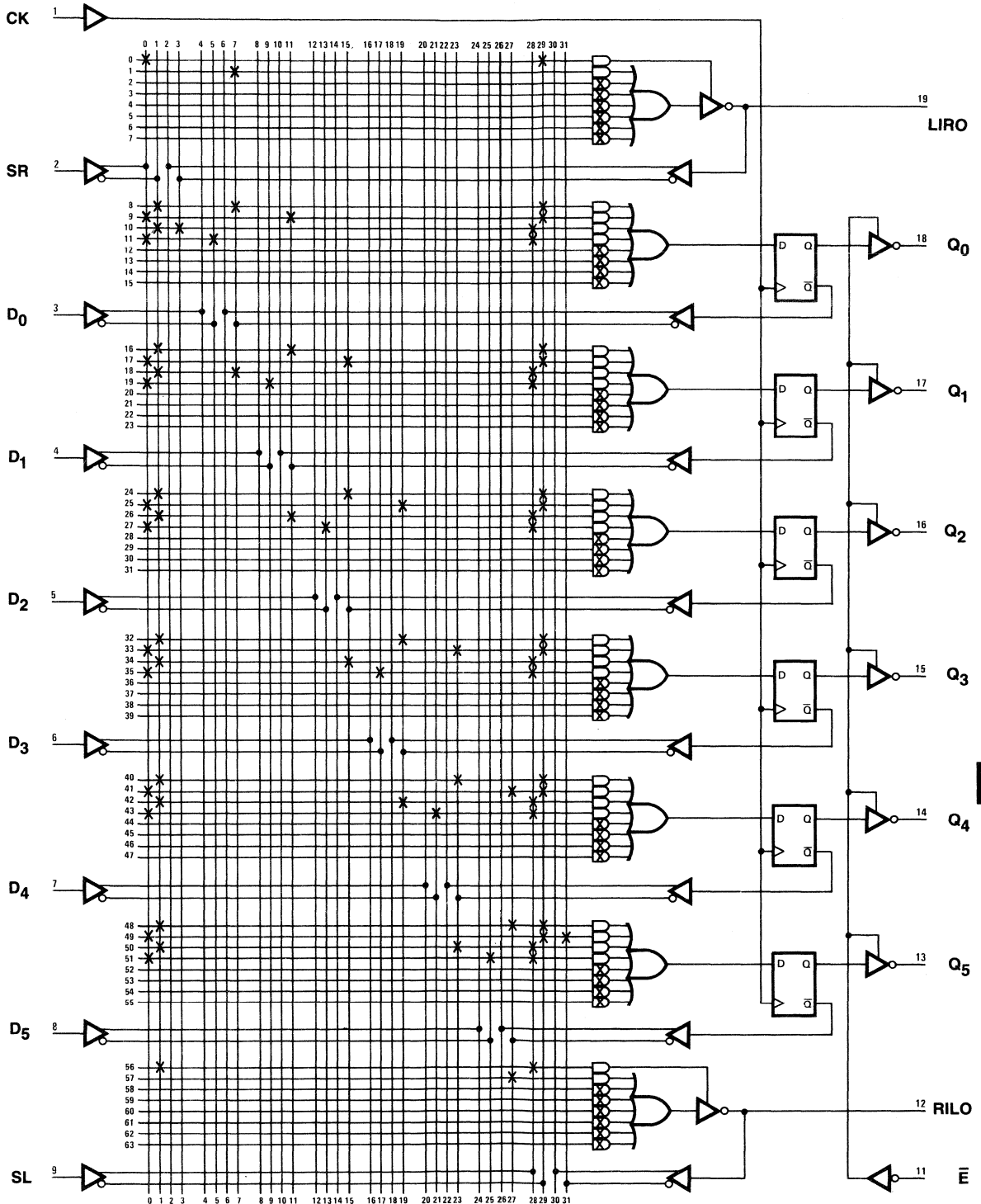

## 8-Bit Counter with Three-State Outputs

## Design Specification PAL16R8

PAL16R8  
 PAT0000  
 8-BIT COUNTER WITH THREE-STATE OUTPUTS

PAL DESIGN SPECIFICATION  
 J. BIRKNER 10/05/77

CK /PRESET NC NC NC NC NC NC NC NC GND /E Q7 Q6 Q5 Q4 Q3 Q2 Q1 Q0 VCC

$Q0 := \overline{\text{PRESET}} \cdot Q0$

$Q1 := \overline{\text{PRESET}} \cdot Q0 \cdot Q1 + \overline{\text{PRESET}} \cdot \overline{Q0} \cdot \overline{Q1}$

$Q2 := \overline{\text{PRESET}} \cdot Q0 \cdot Q1 \cdot Q2 + \overline{\text{PRESET}} \cdot \overline{Q0} \cdot \overline{Q2} + \overline{\text{PRESET}} \cdot \overline{Q1} \cdot \overline{Q2}$

$Q3 := \overline{\text{PRESET}} \cdot Q0 \cdot Q1 \cdot Q2 \cdot Q3 + \overline{\text{PRESET}} \cdot \overline{Q0} \cdot \overline{Q3} + \overline{\text{PRESET}} \cdot \overline{Q1} \cdot \overline{Q3} + \overline{\text{PRESET}} \cdot \overline{Q2} \cdot \overline{Q3}$

$Q4 := \overline{\text{PRESET}} \cdot Q0 \cdot Q1 \cdot Q2 \cdot Q3 \cdot Q4 + \overline{\text{PRESET}} \cdot \overline{Q0} \cdot \overline{Q4} + \overline{\text{PRESET}} \cdot \overline{Q1} \cdot \overline{Q4} + \overline{\text{PRESET}} \cdot \overline{Q2} \cdot \overline{Q4} + \overline{\text{PRESET}} \cdot \overline{Q3} \cdot \overline{Q4}$

$Q5 := \overline{\text{PRESET}} \cdot Q0 \cdot Q1 \cdot Q2 \cdot Q3 \cdot Q4 \cdot Q5 + \overline{\text{PRESET}} \cdot \overline{Q0} \cdot \overline{Q5} + \overline{\text{PRESET}} \cdot \overline{Q1} \cdot \overline{Q5} + \overline{\text{PRESET}} \cdot \overline{Q2} \cdot \overline{Q5} + \overline{\text{PRESET}} \cdot \overline{Q3} \cdot \overline{Q5} + \overline{\text{PRESET}} \cdot \overline{Q4} \cdot \overline{Q5}$

$Q6 := \overline{\text{PRESET}} \cdot Q0 \cdot Q1 \cdot Q2 \cdot Q3 \cdot Q4 \cdot Q5 \cdot Q6 + \overline{\text{PRESET}} \cdot \overline{Q0} \cdot \overline{Q6} + \overline{\text{PRESET}} \cdot \overline{Q1} \cdot \overline{Q6} + \overline{\text{PRESET}} \cdot \overline{Q2} \cdot \overline{Q6} + \overline{\text{PRESET}} \cdot \overline{Q3} \cdot \overline{Q6} + \overline{\text{PRESET}} \cdot \overline{Q4} \cdot \overline{Q6} + \overline{\text{PRESET}} \cdot \overline{Q5} \cdot \overline{Q6}$

$Q7 := \overline{\text{PRESET}} \cdot Q0 \cdot Q1 \cdot Q2 \cdot Q3 \cdot Q4 \cdot Q5 \cdot Q6 \cdot Q7 + \overline{\text{PRESET}} \cdot \overline{Q0} \cdot \overline{Q7} + \overline{\text{PRESET}} \cdot \overline{Q1} \cdot \overline{Q7} + \overline{\text{PRESET}} \cdot \overline{Q2} \cdot \overline{Q7} + \overline{\text{PRESET}} \cdot \overline{Q3} \cdot \overline{Q7} + \overline{\text{PRESET}} \cdot \overline{Q4} \cdot \overline{Q7} + \overline{\text{PRESET}} \cdot \overline{Q5} \cdot \overline{Q7} + \overline{\text{PRESET}} \cdot \overline{Q6} \cdot \overline{Q7}$


## DESCRIPTION:

THE 8-BIT COUNTER INCREMENTS ON THE RISING EDGE OF THE CLOCK INPUT (CK). THE THREE-STATE OUTPUTS ARE HIGH-Z WHEN THE ENABLE LINE (/E) IS HIGH AND ENABLED WHEN ENABLE LINE (/E) IS LOW. THE COUNTER IS SYNCHRONOUSLY PRESET (SET TO ALL HIGHS) WHEN THE PRESET LINE (/PRESET) IS LOW PRIOR TO THE CLOCK GOING HIGH.



8-Bit Counter with Three-State Outputs

Logic Diagram PAL16R8

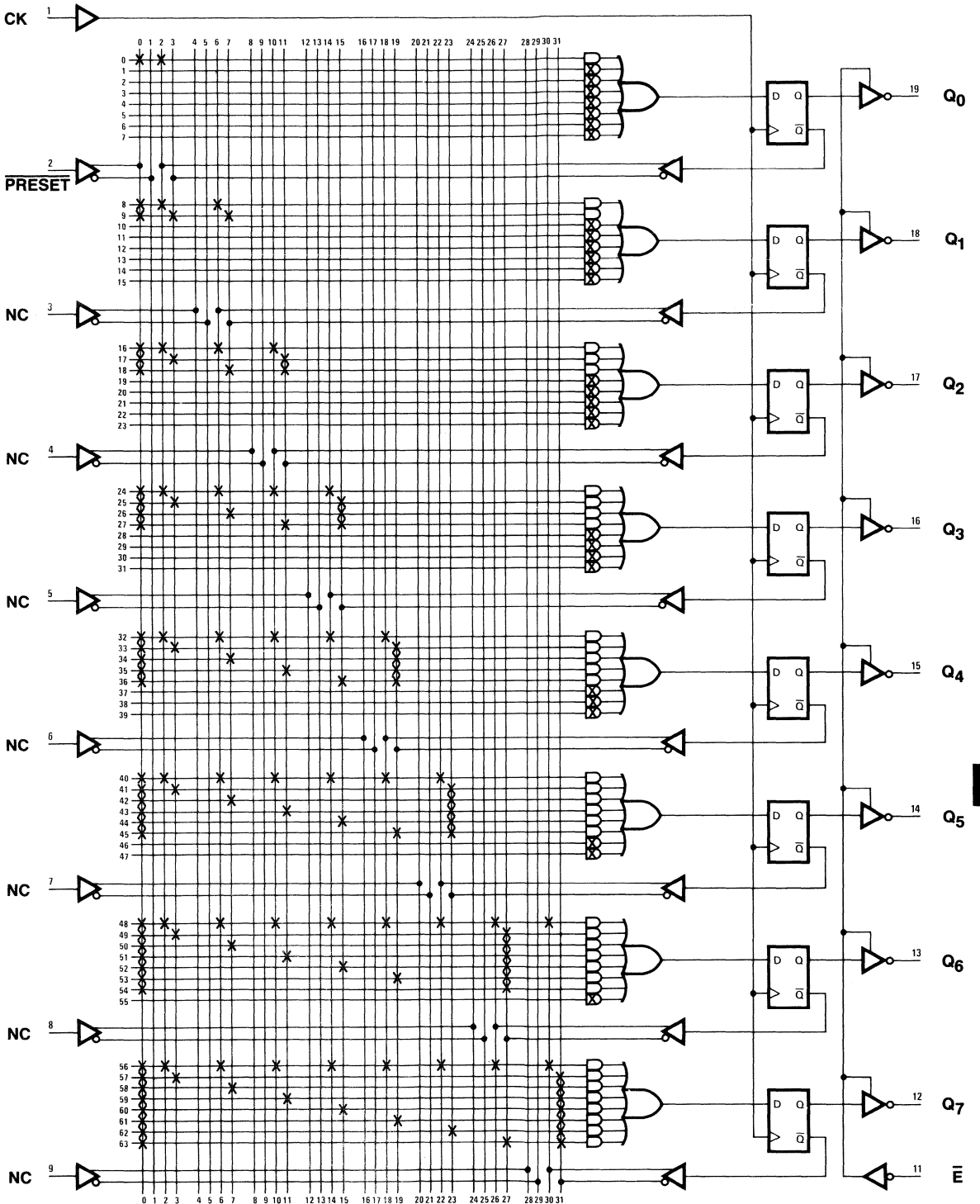

5

**Data I/O Programmer Analog Card Output Driver**

**Design Specification PAL16L8**

PAL16L8  
 PAT0009  
 DATA I/O PROGRAMMER ANALOG CARD OUTPUT DRIVER

PAL DESIGN SPECIFICATION  
 ANDY CHAN 12/14/77

1 2 3 4 5 6 7 8 9 GND 11 12 13 14 15 16 17 18 19 VCC

$$IF(11) \ /14 = \ /5+1+13+18 + 5+1+13+18 + \ /5+1+13+18 + \ /9+1+13+18 + 9+1+13+18$$

$$IF(11) \ /15 = \ /4+1+13+18 + 4+1+13+18 + \ /8+1+13+18 + 8+1+13+18$$

$$IF(11) \ /16 = \ /3+1+13+18 + 3+1+13+18 + \ /7+1+13+18 + 7+1+13+18$$

$$IF(11) \ /17 = \ /2+1+13+18 + 2+1+13+18 + \ /6+1+13+18 + 6+1+13+18$$

**DESCRIPTION:**


THE DEVICE MULTIPLEXES EIGHT OUTPUTS FROM THE SENSE AMPLIFIER ON THE ANALOG CARD TO FOUR THREE STATE OUTPUTS WHICH DRIVE THE DATA BUS, DO.

**FUNCTION TABLE:**

INPUTS				OUTPUTS				
11	1	18	13	14	15	16	17	OPERATIONS
H	L	L	L	9	8	7	6	UPPER OUTPUTS LOGIC LOW
H	L	L	H	/9	/8	/7	/6	UPPER OUTPUTS LOGIC HIGH
H	L	H	L	H	H	H	H	NOP
H	L	H	H	H	H	H	/6	UPPER OUTPUTS BOTH LOGIC
H	H	L	L	5	4	3	2	LOWER OUTPUTS LOGIC LOW
H	H	L	H	/5	/4	/3	/2	LOWER OUTPUTS LOGIC HIGH
H	H	H	L	H	H	H	H	NOP
H	H	H	H	5	H	H	H	LOWER OUTPUTS BOTH LOGIC
L	X	X	X	Z	Z	Z	Z	DISABLE

Data I/O Programmer Analog Card Output Driver

Logic Diagram PAL16L8

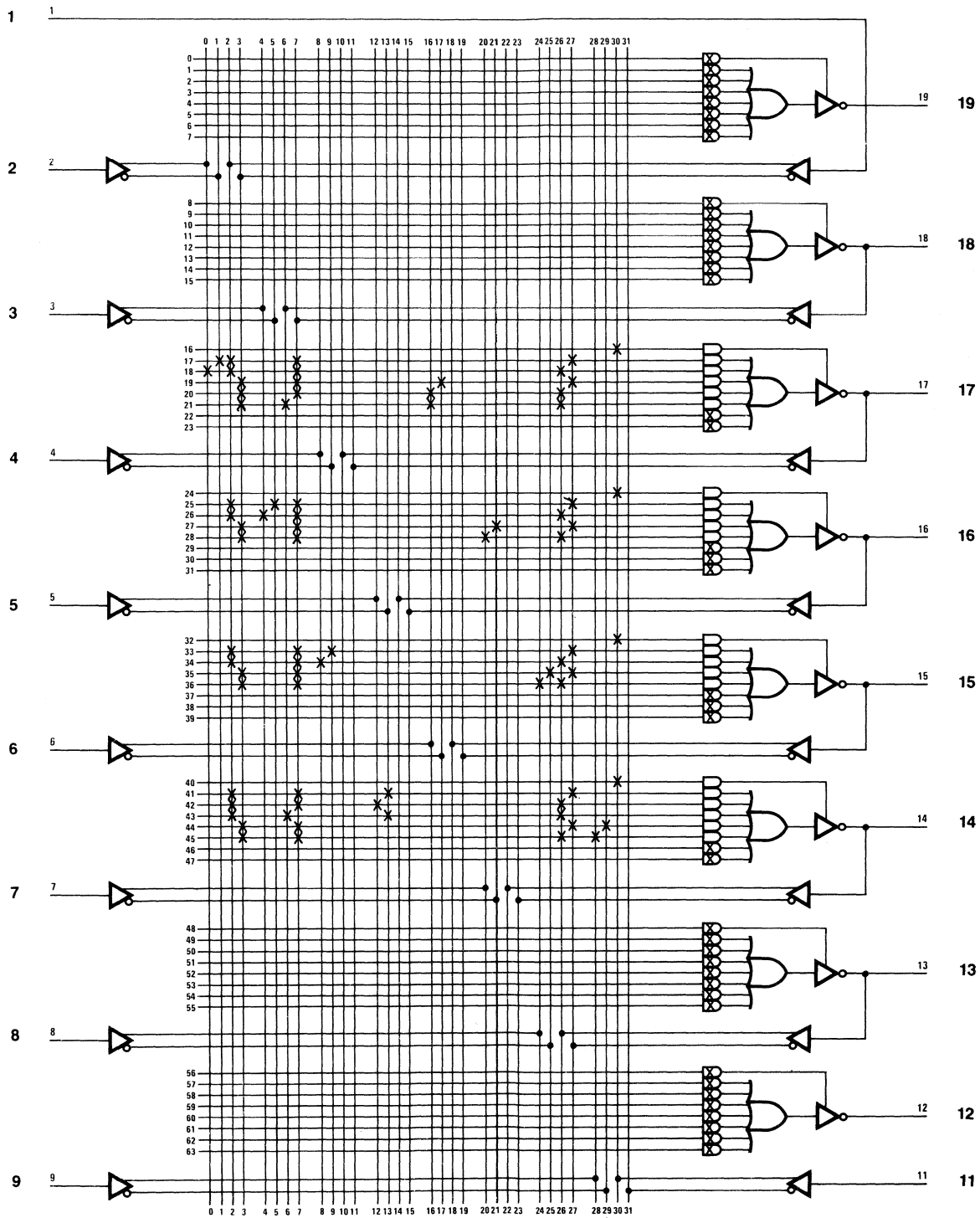

5

**24-Bit Fast Look-Ahead Carry Generator**

**Design Specification PAL16L8**

PAL16L8  
 PAT0018  
 24 BIT FAST LOOK-AHEAD CARRY GENERATOR

PAL DESIGN SPECIFICATION  
 VIC NEWTON 12/19/77

CN /G0 /P0 /G1 /P1 /G2 /P2 /G3 /P3 GND /G4 /P4 NC2  
 CN20 CN16 CN12 CN8 CN4 VCC

$$\text{IF (VCC) } /CN4 = /G0 \wedge /P0 + /G0 \wedge /CN$$

$$\text{IF (VCC) } /CN8 = /G1 \wedge /P1 + /G1 \wedge /G0 \wedge /P0 + /G1 \wedge /G0 \wedge /CN$$

$$\text{IF (VCC) } /CN12 = /G2 \wedge /P2 + /G2 \wedge /G1 \wedge /P1 + /G2 \wedge /G1 \wedge /G0 \wedge /P0 + /G2 \wedge /G1 \wedge /G0 \wedge /CN$$


$$\text{IF (VCC) } /CN16 = /G3 \wedge /P3 + /G3 \wedge /G2 \wedge /P2 + /G3 \wedge /G2 \wedge /G1 \wedge /P1 + /G3 \wedge /G2 \wedge /G1 \wedge /G0 \wedge /P0 + /G3 \wedge /G2 \wedge /G1 \wedge /G0 \wedge /CN$$

$$\text{IF (VCC) } /CN20 = /G4 \wedge /P4 + /G4 \wedge /G3 \wedge /P3 + /G4 \wedge /G3 \wedge /G2 \wedge /P2 + /G4 \wedge /G3 \wedge /G2 \wedge /G1 \wedge /P1 + /G4 \wedge /G3 \wedge /G2 \wedge /G1 \wedge /G0 \wedge /P0 + /G4 \wedge /G3 \wedge /G2 \wedge /G1 \wedge /G0 \wedge /CN$$

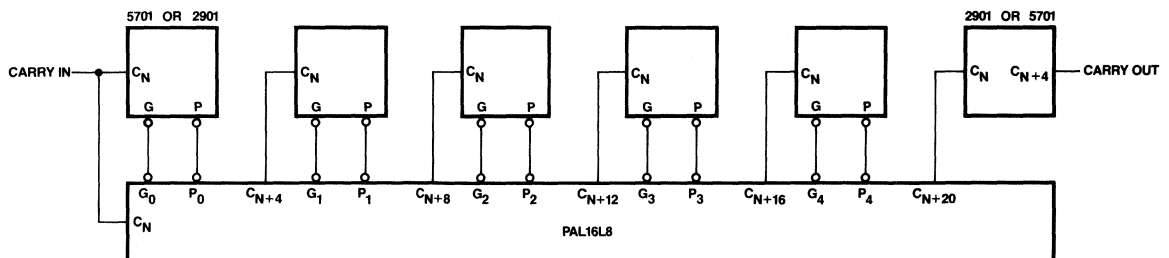**DESCRIPTION:**


THE LOOK-AHEAD CARRY GENERATOR ACCEPTS A CARRY INPUT AND UP TO FIVE PAIRS OF CARRY PROPAGATE AND CARRY GENERATE SIGNALS. IT PROVIDES ANTICIPATED CARRIES ACROSS SIX GROUPS OF BINARY ALU'S. THE LOOK-AHEAD CARRY GENERATOR CAN BE USED WITH BINARY ALU'S IN AN ACTIVE LOW OR ACTIVE HIGH INPUT OPERAND MODE BY REINTERPERTING THE CARRY FUNCTIONS. THE CONNECTIONS ARE IDENTICAL IN BOTH CASES.

24 BIT ALU'S CAN BE OBTAINED BY USING 4 BIT SLICES SUCH AS THE 5701 OR 2901.



24-Bit Fast Look-Ahead Carry Generator

Logic Diagram PAL16L8

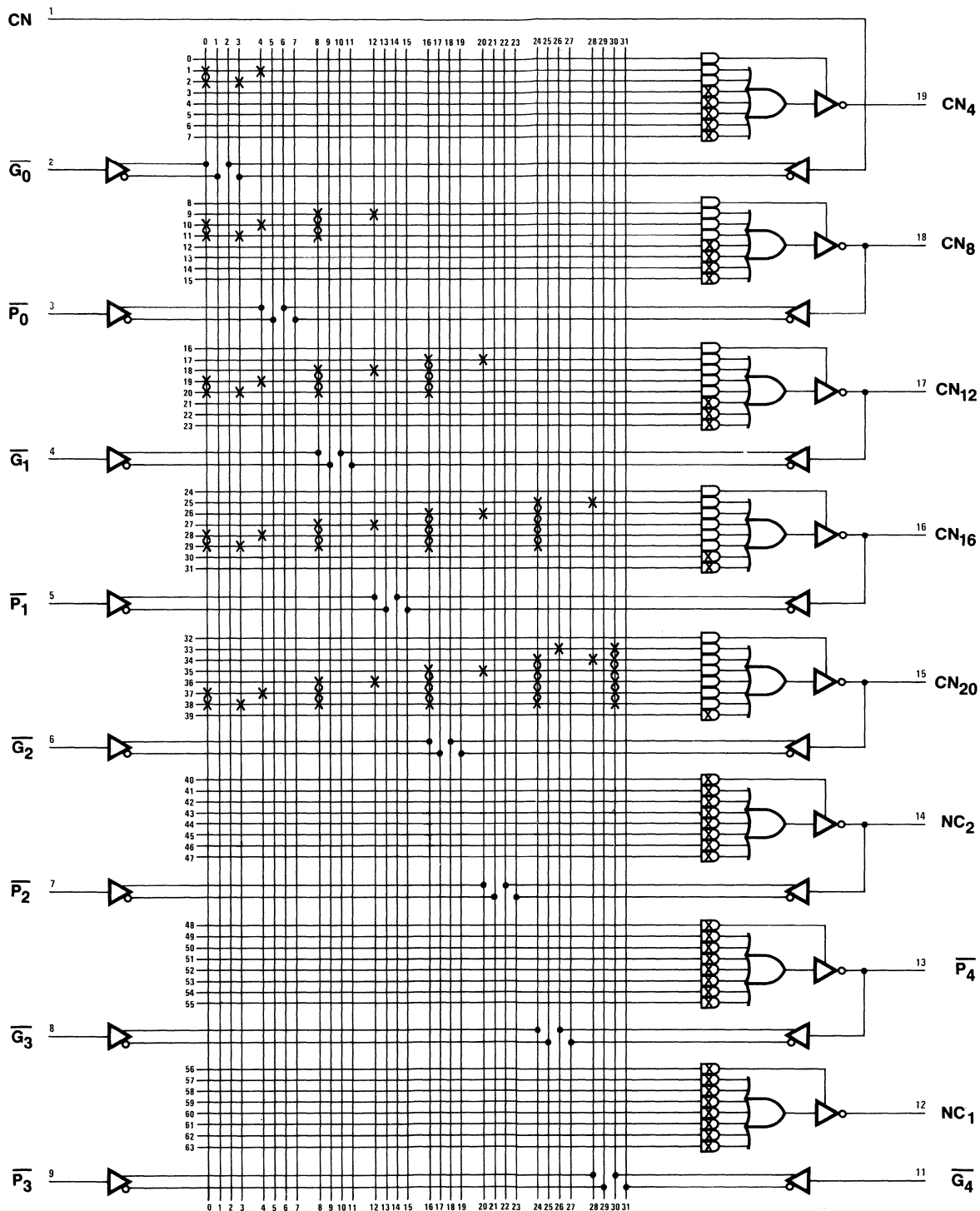

5

**4-Bit Up/Down Counter with Shift and Three-State Outputs**

**Design Specification PAL16X4**

PAL16X4 PAL DESIGN SPECIFICATION  
 PAT0026 JOHN BIRKNER 12/10/77  
 4 BIT UP/DOWN COUNTER WITH SHIFT AND THREE-STATE OUTPUTS

CLOCK I0 I1 B0 B1 B2 B3 I2 CLEAR GND /E /LIO NC A3 A2 A1 A0 NC /RIO VCC

IF( /I2+I1+I0 ) RIO = (A0)

/A0 := (/A0)+I2+I1+I0 + (/B0)+I2+I1+I0 + (/A1)+I2+I1+I0 + (/A0)+I2+I1  
 := (/RIO)+I2+I1+I0 +  
 RIO+I2+I1+I0 +  
 RIO+I2+I1+ I0 + CLEAR

/A1 := (/A1)+I2+I1+I0 + (/B1)+I2+I1+I0 + (/A2)+I2+I1+I0 + (/A1)+I2+I1  
 := (/A0)+I2+I1+I0 +  
 ( A0)+RIO+I2+I1+I0 +  
 (/A0)+RIO+I2+I1+ I0 + CLEAR

/A2 := (/A2)+I2+I1+I0 + (/B2)+I2+I1+I0 + (/A3)+I2+I1+I0 + (/A2)+I2+I1  
 := (/A1)+I2+I1+I0 +  
 ( A1)+( A0)+RIO+I2+I1+I0 +  
 (/A1)+(/A0)+RIO+I2+I1+ I0 + CLEAR

/A3 := (/A3)+I2+I1+I0 + (/B3)+I2+I1+I0 + /LIO+I2+I1+I0 + (/A3)+I2+I1  
 := (/A2)+I2+I1+I0 +  
 ( A2)+( A1)+( A0)+RIO+I2+I1+I0 +  
 (/A2)+(/A1)+(/A0)+RIO+I2+I1+ I0 + CLEAR

IF( I2 ) LIO = (A3)+I2+I1+I2 + ( A3)+( A2)+( A1)+( A0)+RIO+I2+I1+I0 +  
 (/A3)+(/A2)+(/A1)+(/A0)+RIO+I2+I1+ I0

**DESCRIPTION:**


THE UP/DOWN COUNTER WITH SHIFT WILL LOAD, SHIFT, COUNT UP, COUNT DOWN, CLEAR OR NOP ON THE RISING EDGE OF THE CLOCK AS SPECIFIED BY THE INSTRUCTION, I. SHIFT I/D, CARRY AND BORROW SHARE THE SAME I/D LINES (LIO AND RIO). ACTIVE HIGH OUTPUTS, A, ARE ENABLED WHEN /E IS LOW. NOTE: THE IMPLIED EXCLUSIVE OR, :=, MUST BE PLACED BETWEEN THE FOURTH AND FIFTH PRODUCT TERMS.

**FUNCTION TABLE:**

INPUTS				OUTPUTS									
CLEAR	I2	I1	I0	LIO	RIO	CLOCK	LIO	A3	A2	A1	A0	RIO	OPERATION
L	L	L	L	X	X	L-H	Z	A3	A2	A1	A0	Z	NOP
L	L	L	H	X	X	L-H	Z	B3	B2	B1	B0	Z	LOAD B
L	L	H	L	X	X	L-H	Z	R1	A3	A2	A1	A1	SHIFT RT
L	L	H	H	X	X	L-H	Z	ALL HIGH				Z	SET
L	H	L	L	Z	LI	L-H	A2	A2	A1	A0	LI	Z	SHIFT LT
L	H	L	H	Z	X	L-H	L	ALL HIGH				Z	SET
L	H	H	L	Z	CIN	L-H	COU	A PLUS ONE				Z	INC IF CIN
L	H	H	H	Z	BIN	L-H	BOU	A MINUS ONE				Z	DEC IF BIN
H	X	X	X	X	X	L-H	Z	ALL LOW				Z	CLEAR

4-Bit Up/Down Counter with Shift and Three-State Outputs

Logic Diagram PAL16X4

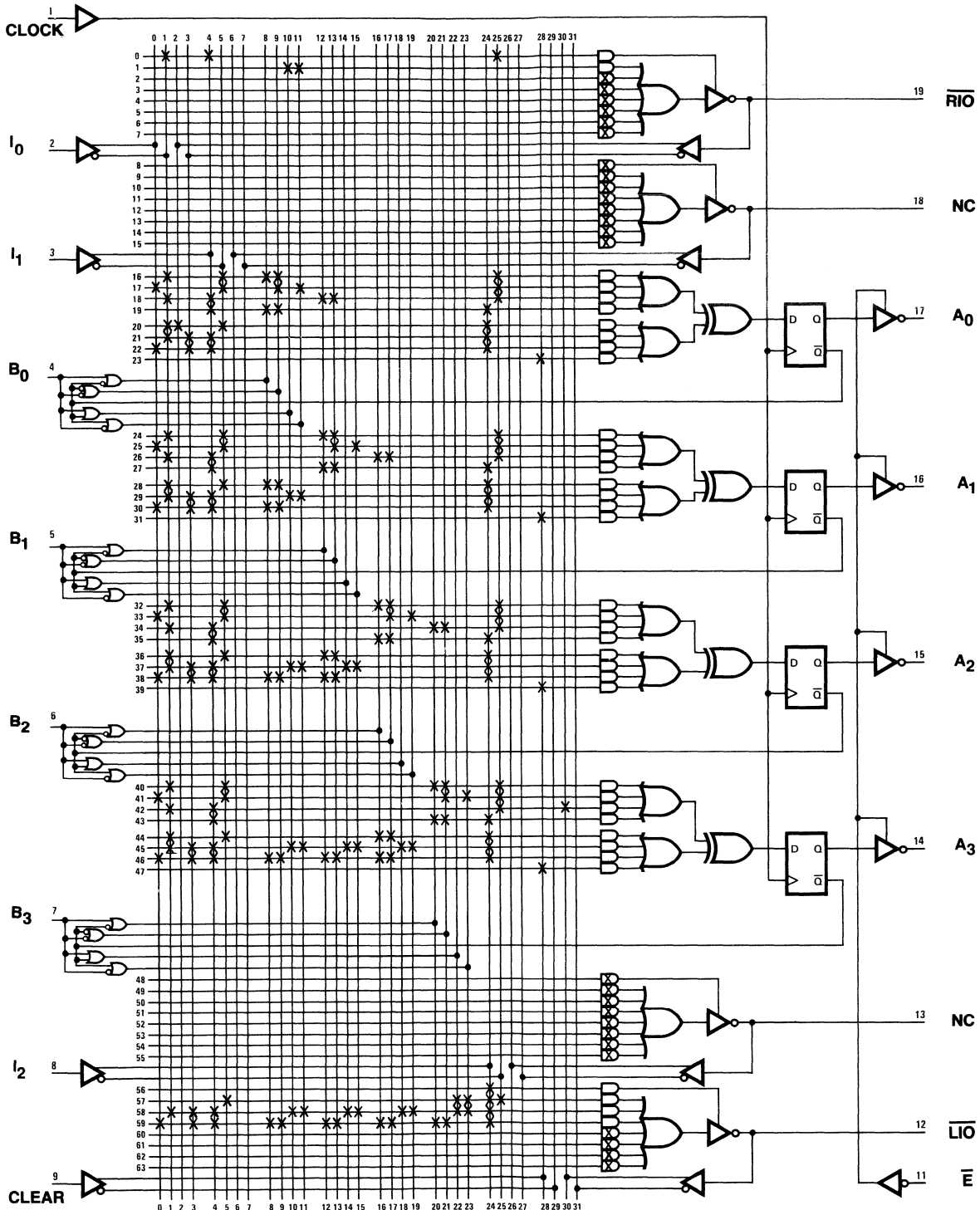

5

ALU Accumulator

Design Specification PAL16A4

PAL16A4  
PAT0026  
ALU/ACCUMULATOR

PAL DESIGN SPECIFICATION  
JOHN BIRKNER 12/15/77

CLOCK I0 I1 B0 B1 B2 B3 I2 I3 GND /E LID /P A3 A2 A1 A0 /G CIN VCC

$$\begin{aligned} /A0 := & /I3 \cdot /I2 \cdot /I1 \cdot /I0 \cdot (A0.EQ.B0) + /I3 \cdot /I2 \cdot /I1 \cdot I0 \cdot (/A0) + /I3 \cdot /I2 \cdot I1 \cdot /I0 \cdot (/B0) + \\ & /I3 \cdot I2 \cdot /I1 \cdot /I0 \cdot (B0) :+ : /I3 \cdot I2 \cdot /I1 \cdot I0 \cdot (/A0 \cdot /B0) + \\ & /I3 \cdot I2 \cdot I1 \cdot /I0 \cdot (/CIN) + /I3 \cdot I2 \cdot I1 \cdot I0 \cdot (/A1) + I3 \cdot (/A0) + CARRY0 \end{aligned}$$

$$\begin{aligned} /A1 := & /I3 \cdot /I2 \cdot /I1 \cdot /I0 \cdot (A1.EQ.B1) + /I3 \cdot /I2 \cdot /I1 \cdot I0 \cdot (/A1) + /I3 \cdot /I2 \cdot I1 \cdot /I0 \cdot (/B1) + \\ & /I3 \cdot I2 \cdot /I1 \cdot /I0 \cdot (B1) :+ : /I3 \cdot I2 \cdot /I1 \cdot I0 \cdot (/A1 \cdot /B1) + \\ & /I3 \cdot I2 \cdot I1 \cdot /I0 \cdot (/A0) + /I3 \cdot I2 \cdot I1 \cdot I0 \cdot (/A2) + I3 \cdot (/A1) + CARRY1 \end{aligned}$$

$$\begin{aligned} /A2 := & /I3 \cdot /I2 \cdot /I1 \cdot /I0 \cdot (A2.EQ.B2) + /I3 \cdot /I2 \cdot /I1 \cdot I0 \cdot (/A2) + /I3 \cdot /I2 \cdot I1 \cdot /I0 \cdot (/B2) + \\ & /I3 \cdot I2 \cdot /I1 \cdot /I0 \cdot (B2) :+ : /I3 \cdot I2 \cdot /I1 \cdot I0 \cdot (/A2 \cdot /B2) + \\ & /I3 \cdot I2 \cdot I1 \cdot /I0 \cdot (/A1) + /I3 \cdot I2 \cdot I1 \cdot I0 \cdot (/A3) + I3 \cdot (/A2) + CARRY2 \end{aligned}$$

$$\begin{aligned} /A3 := & /I3 \cdot /I2 \cdot /I1 \cdot /I0 \cdot (A3.EQ.B3) + /I3 \cdot /I2 \cdot /I1 \cdot I0 \cdot (/A3) + /I3 \cdot /I2 \cdot I1 \cdot /I0 \cdot (/B3) + \\ & /I3 \cdot I2 \cdot /I1 \cdot /I0 \cdot (B3) :+ : /I3 \cdot I2 \cdot /I1 \cdot I0 \cdot (/A3 \cdot /B3) + \\ & /I3 \cdot I2 \cdot I1 \cdot /I0 \cdot (/A2) + /I3 \cdot I2 \cdot I1 \cdot I0 \cdot /LID + I3 \cdot (/A3) + CARRY3 \end{aligned}$$

$$\begin{aligned} \text{IF (VCC) G} = & /I3 \cdot /I2 \cdot /I1 \cdot /I0 \cdot (A3 \cdot B3) + \\ & /I3 \cdot /I2 \cdot /I1 \cdot /I0 \cdot (A3 \cdot B3) \cdot (A2 \cdot B2) + \\ & /I3 \cdot /I2 \cdot /I1 \cdot /I0 \cdot (A3 \cdot B3) \cdot (A2 \cdot B2) \cdot (A1 \cdot B1) + \\ & /I3 \cdot /I2 \cdot /I1 \cdot /I0 \cdot (A3 \cdot B3) \cdot (A2 \cdot B2) \cdot (A1 \cdot B1) \cdot (A0 \cdot B0) \end{aligned}$$

$$\begin{aligned} \text{IF (VCC) P} = & /I3 \cdot /I2 \cdot /I1 \cdot /I0 \cdot (A3 \cdot B3) \cdot (A2 \cdot B2) \cdot (A1 \cdot B1) \cdot (A0 \cdot B0) + \\ & /I3 \cdot /I2 \cdot /I1 \cdot /I0 \cdot (/A3) \cdot (/A2) \cdot (/A1) \cdot (/A0) + \\ & /I3 \cdot /I2 \cdot I1 \cdot /I0 \cdot (/B3) \cdot (/B2) \cdot (/B1) \cdot (/B0) + \\ & /I3 \cdot /I2 \cdot I1 \cdot I0 \cdot (/A3 \cdot /B3) \cdot (/A2 \cdot /B2) \cdot (/A1 \cdot /B1) \cdot (/A0 \cdot /B0) + \\ & /I3 \cdot I2 \cdot /I1 \cdot /I0 \cdot (/A3 \cdot /B3) \cdot (/A2 \cdot /B2) \cdot (/A1 \cdot /B1) \cdot (/A0 \cdot /B0) + \\ & /I3 \cdot I2 \cdot I1 \cdot /I0 \cdot (/A2) \cdot (/A1) \cdot (/A0) \cdot /CIN + \\ & /I3 \cdot I2 \cdot I1 \cdot I0 \cdot (/LID \cdot /A3) \cdot (/A2) \cdot (/A1) \end{aligned}$$

$$\text{IF ( } /I3 \cdot I2 \cdot I1 \cdot /I0 \text{ ) } /LID = (/A3)$$

$$\text{IF ( } /I3 \cdot I2 \cdot I1 \cdot I0 \text{ ) } /CIN = (/A0)$$

NOTE: CARRY0 = /I3 · /I2 · /I1 · /I0 · CIN

$$\begin{aligned} \text{CARRY1} = & /I3 \cdot /I2 \cdot /I1 \cdot /I0 \cdot (A0 \cdot B0) + \\ & /I3 \cdot /I2 \cdot /I1 \cdot /I0 \cdot (A0 \cdot B0) \cdot CIN \end{aligned}$$

$$\begin{aligned} \text{CARRY2} = & /I3 \cdot /I2 \cdot /I1 \cdot /I0 \cdot (A1 \cdot B1) + \\ & /I3 \cdot /I2 \cdot /I1 \cdot /I0 \cdot (A1 \cdot B1) \cdot (A0 \cdot B0) + \\ & /I3 \cdot /I2 \cdot /I1 \cdot /I0 \cdot (A1 \cdot B1) \cdot (A0 \cdot B0) \cdot CIN \end{aligned}$$

$$\begin{aligned} \text{CARRY3} = & /I3 \cdot /I2 \cdot /I1 \cdot /I0 \cdot (A2 \cdot B2) + \\ & /I3 \cdot /I2 \cdot /I1 \cdot /I0 \cdot (A2 \cdot B2) \cdot (A1 \cdot B1) + \\ & /I3 \cdot /I2 \cdot /I1 \cdot /I0 \cdot (A2 \cdot B2) \cdot (A1 \cdot B1) \cdot (A0 \cdot B0) + \\ & /I3 \cdot /I2 \cdot /I1 \cdot /I0 \cdot (A2 \cdot B2) \cdot (A1 \cdot B1) \cdot (A0 \cdot B0) \cdot CIN \end{aligned}$$

DESCRIPTION:

THE ALU ACCUMULATOR LOADS THE A-REGISTER WITH ONE OF EIGHT OPERANDS ON THE RISING EDGE OF THE CLOCK. G AND P OUTPUT GENERATE AND PROPAGATE ON THE ADD INSTRUCTION. P OUTPUTS OP = ZERO ON INSTRUCTIONS 1,2,3,5,6,7.

! INPUTS										! OUTPUTS					! OPERATION	
! I3	! I2	! I1	! I0	! LID	! CIN	! LID	! A3	! A2	! A1	! A0	! CIN	!	!			
! L	! L	! L	! L	! X	! L	! Z	! A	! PLUS	! B	! Z	! Z	! ADD	! A=A PLUS B			
! L	! L	! L	! L	! X	! H	! Z	! A	! PL	! B	! PL	! 1	! Z	! ADD	! A=APLUSBPLUS1		
! L	! L	! L	! H	! X	! X	! Z	! A3	! A2	! A1	! A0	! Z	! NOP	! A=A			
! L	! L	! H	! L	! X	! X	! Z	! B3	! B2	! B1	! B0	! Z	! LOAD	! A=B			
! L	! L	! H	! H	! X	! X	! Z	!	!	!	!	!	!	! AND	! A=A·B		
! L	! H	! L	! L	! X	! X	! Z	! /B3	! /B2	! /B1	! /B0	! Z	!	! LOADCOMP	! A= /B		
! L	! H	! L	! H	! X	! X	! Z	!	!	!	!	!	!	! OR	! A=A+B		
! L	! H	! H	! L	! X	! LI	!	! A2	! A2	! A1	! A0	! LI	! Z	!	! SHIFT LEFT		
! L	! H	! H	! H	! RI	! X	!	! RI	! A3	! A2	! A1	!	! A1	! Z	!	! SHIFT RIGHT	
! H	! X	! X	! X	! X	! X	! Z	! A3	! A2	! A1	! A0	! Z	!	!	! NOP	! A=A	



```

X--- X--- ---- ---- ---- ---- X--- X--- /I3♦I2♦I1♦I0
----- XX-- ---- ---- ---- ---- /A0
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX

--- -- -- -- -- -- -- -- -- --
-X-- -X-- ---- ---- ---- X-XX -X-- -X-- /I3♦/I2♦/I1♦/I0♦A3♦B3
-X-- -X-- ---- ---- X-XX -X-- -X-- /I3♦/I2♦/I1♦/I0♦A3♦B3♦A2♦B2
-X-- -X-- ---- X-XX -X-- -X-- -X-- /I3♦/I2♦/I1♦/I0♦A3♦B3♦A2♦B2♦A1♦
-X-- -X-- X-XX -X-- -X-- -X-- -X-- /I3♦/I2♦/I1♦/I0♦A3♦B3♦A2♦B2♦A1♦
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX

-X-- -X-- X-X ---- ---- ---- -X-- -X-- /I3♦/I2♦/I1♦/I0♦A0.EQ.B0
X--- -X-- XX-- ---- ---- ---- -X-- -X-- /I3♦/I2♦/I1♦I0♦/A0
-X-- -X-- -X-X ---- ---- ---- -X-- -X-- /I3♦/I2♦I1♦/I0♦/B0
-X-- -X-- X-X ---- ---- ---- -X-- -X-- /I3♦I2♦/I1♦/I0♦B0
X--- -X-- XX-X ---- ---- ---- -X-- -X-- /I3♦I2♦/I1♦I0♦/A0♦/B0
-X-X -X-- ---- ---- ---- -X-- -X-- /I3♦I2♦I1♦/I0♦/CIN
X--- X--- ---- XX-- ---- ---- -X-- -X-- /I3♦I2♦I1♦I0♦/A1
----- XX-- ---- ---- ---- -X--- X--- I3♦/A0

-X-- -X-- ---- X-X ---- ---- ---- -X-- -X-- /I3♦/I2♦/I1♦/I0♦A1.EQ.B1
X--- -X-- ---- XX-- ---- ---- ---- -X-- -X-- /I3♦/I2♦/I1♦I0♦/A1
-X-- -X-- ---- -X-X ---- ---- ---- -X-- -X-- /I3♦/I2♦I1♦/I0♦/B1
-X-- -X-- ---- X-X ---- ---- ---- -X-- -X-- /I3♦I2♦/I1♦/I0♦B1
X--- -X-- ---- XX-X ---- ---- ---- -X-- -X-- /I3♦I2♦/I1♦I0♦/A1♦/B1
-X-- X--- XX-- ---- ---- ---- -X-- -X-- /I3♦I2♦I1♦/I0♦/A0
X--- X--- ---- XX-- ---- ---- ---- -X-- -X-- /I3♦I2♦I1♦I0♦/A2
----- XX-- ---- ---- ---- -X--- X--- I3♦/A1

-X-- -X-- ---- X-X ---- ---- ---- -X-- -X-- /I3♦/I2♦/I1♦/I0♦A2.EQ.B2
X--- -X-- ---- XX-- ---- ---- ---- -X-- -X-- /I3♦/I2♦/I1♦I0♦/A2
-X-- -X-- ---- -X-X ---- ---- ---- -X-- -X-- /I3♦/I2♦I1♦/I0♦/B2
-X-- -X-- ---- X-X ---- ---- ---- -X-- -X-- /I3♦I2♦/I1♦/I0♦B2
X--- -X-- ---- XX-X ---- ---- ---- -X-- -X-- /I3♦I2♦/I1♦I0♦/A2♦/B2
-X-- X--- XX-- ---- ---- ---- -X-- -X-- /I3♦I2♦I1♦/I0♦/A1
X--- X--- ---- XX-- ---- ---- ---- -X-- -X-- /I3♦I2♦I1♦I0♦/A3
----- XX-- ---- ---- ---- -X--- X--- I3♦/A2

-X-- -X-- ---- X-X ---- ---- ---- -X-- -X-- /I3♦/I2♦/I1♦/I0♦A3.EQ.B3
X--- -X-- ---- XX-- ---- ---- ---- -X-- -X-- /I3♦/I2♦/I1♦I0♦/A3
-X-- -X-- ---- -X-X ---- ---- ---- -X-- -X-- /I3♦/I2♦I1♦/I0♦/B3
-X-- -X-- ---- X-X ---- ---- ---- -X-- -X-- /I3♦I2♦/I1♦/I0♦B3
X--- -X-- ---- XX-X ---- ---- ---- -X-- -X-- /I3♦I2♦/I1♦I0♦/A3♦/B3
-X-- X--- XX-- ---- ---- ---- -X-- -X-- /I3♦I2♦I1♦/I0♦/A2
X--- X--- ---- XX-- ---- ---- ---- -X-- -X-X /I3♦I2♦I1♦I0♦/LID
----- XX-- ---- ---- ---- -X--- X--- I3♦/A3


--- -- -- -- -- -- -- -- -- --
-X-- -X-- -X- -X- -X- -X- -X-- /I3♦/I2♦/I1♦/I0♦A3♦B3♦A2♦B2♦A1♦
X--- -X-- XX-- XX-- XX-- XX-- -X-- /I3♦/I2♦/I1♦I0♦/A3♦/A2♦/A1♦/A0
-X-- -X-- -X-X -X-X -X-X -X-X -X-- /I3♦/I2♦I1♦/I0♦/B3♦/B2♦/B1♦/B0
X--- X--- -X- -X- -X- -X- -X-- /I3♦/I2♦I1♦I0♦/A3♦/B3♦/A2♦/B2♦/
X--- -X-- XX-X XX-X XX-X XX-X -X-- /I3♦I2♦/I1♦I0♦/A3♦/B3♦/A2♦/B2♦/
-X-X -X-- XX-- XX-- XX-- XX-- -X-- /I3♦I2♦I1♦/I0♦/A2♦/A1♦/A0♦/CIN
X--- X--- ---- XX-- XX-- XX-- X--- -X-X /I3♦I2♦I1♦I0♦/LID♦/A3♦/A2♦/A1

-X-- X--- ---- ---- ---- ---- -X--- -X-- /I3♦I2♦I1♦/I0
----- XX-- ---- ---- ---- ---- /A3
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX
XXXX XXXX XXXX XXXX XXXX XXXX XXXX

```

ALU Accumulator

Logic Diagram PAL16A4

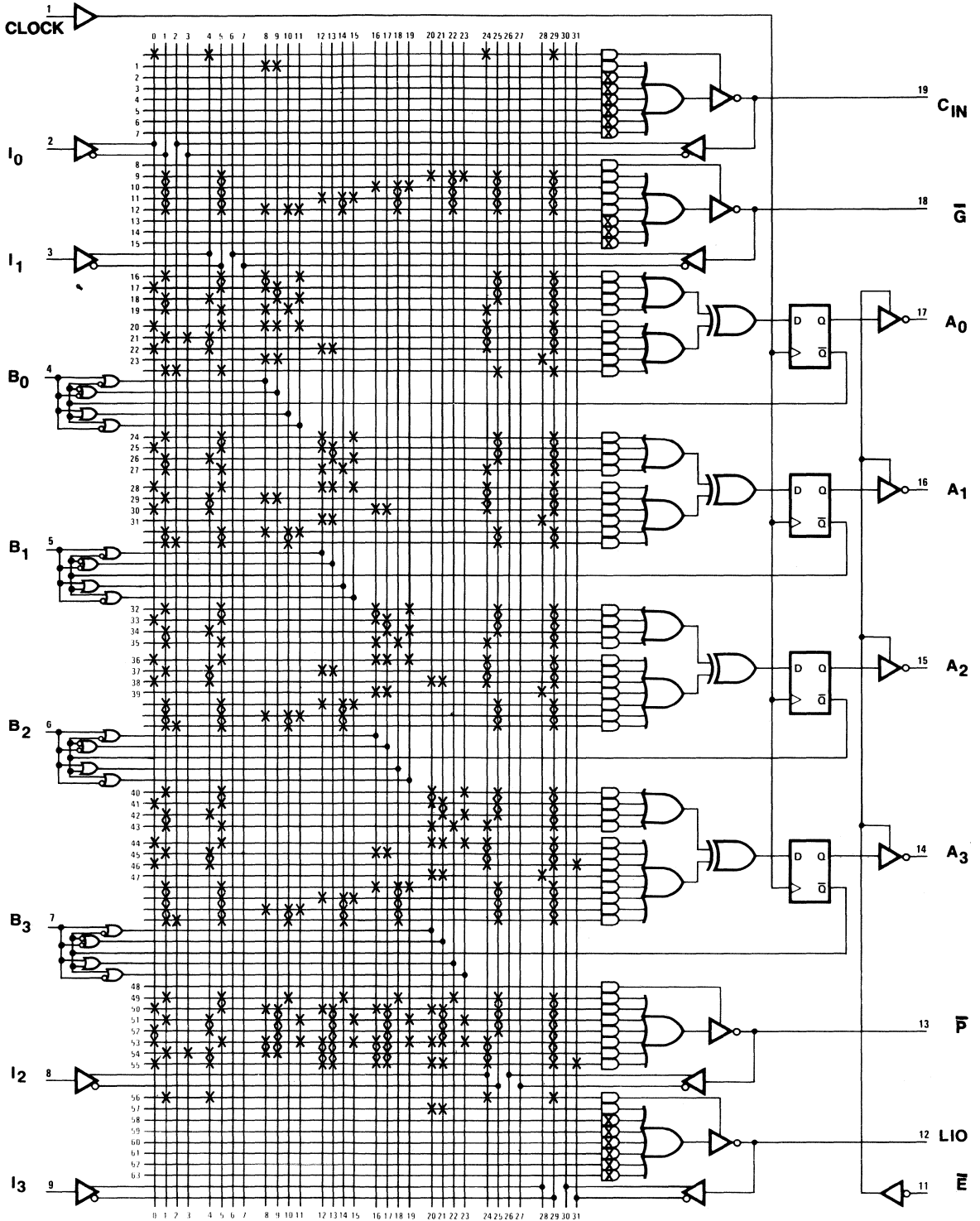



<b>Introduction</b>	<b>1</b>
<b>Reliability</b>	<b>2</b>
<b>PAL Family Data Sheet</b>	<b>3</b>
<b>Design Concept</b>	<b>4</b>
<b>Applications</b>	<b>5</b>
<b>Representatives/Distributors</b>	<b>6</b>

# Representatives

## U.S.A.

<b>Alabama</b> <b>Huntsville</b> REP, Inc. (205) 881-9270	<b>Iowa</b> <b>Cedar Rapids</b> S & O Sales (319) 393-1845	<b>Ohio</b> <b>Cincinnati</b> Makin Associates (513) 871-2424
<b>Arizona</b> <b>Scottsdale</b> Summit Sales (602) 994-4587	<b>Kansas</b> <b>Olathe</b> Rush and West (913) 764-2700	<b>Mentor</b> Makin Associates (216) 464-4330
<b>California</b> <b>Culver City</b> Bestronics (213) 870-9191	<b>Maryland</b> <b>Baltimore</b> Monolithic Sales (301) 296-2444	<b>Oregon</b> <b>Portland</b> N.W. Marketing (503) 297-2581
<b>Irvine</b> Bestronics (714) 979-9910	<b>Rockville</b> Monolithic Sales (301) 340-2130	<b>Pennsylvania</b> <b>Oreland</b> CMS Marketing (215) 885-5106
<b>Mountain View</b> Thresum Associates (415) 965-9180	<b>Massachusetts</b> <b>Needham Heights</b> Comp Rep Associates (617) 444-2484	<b>Tennessee</b> <b>Jefferson City</b> REP, Inc. (615) 475-4105
<b>San Diego</b> Littlefield & Smith (714) 455-0055	<b>Michigan</b> <b>Grosse Point</b> Greiner Associates (313) 499-0188	<b>Texas</b> <b>Dallas</b> West and Associates (214) 661-9400
<b>Colorado</b> <b>Wheatridge</b> Waugaman Associates (303) 423-1020	<b>Minnesota</b> <b>Minneapolis</b> Nortec Sales (612) 835-7414	<b>Utah</b> <b>Salt Lake City</b> Waugaman Associates (801) 363-0275
<b>Connecticut</b> <b>North Haven</b> Comp Rep Associates (203) 239-9762	<b>Missouri</b> <b>Ballwin</b> Rush and West (314) 394-7271	<b>Washington</b> <b>Bellevue</b> Northwest Marketing (206) 455-5846
<b>Florida</b> <b>Altamonte Springs</b> Dyne-A-Mark (305) 831-2097	<b>New Jersey</b> <b>Teaneck</b> R.T. Reid Associates (201) 692-0200	<b>Wisconsin</b> <b>Milwaukee</b> Sumer (414) 259-9060
<b>Clearwater</b> Dyne-A-Mark (813) 441-4702	<b>New York</b> <b>Rochester</b> L-Mar Associates (716) 328-5240	<b>CANADA</b>
<b>Fort Lauderdale</b> Dyne-A-Mark (305) 771-6501	<b>Syracuse</b> L-Mar Associates (315) 437-7779	<b>Ontario</b> <b>Milton</b> Cantec (416) 624-9696
<b>Georgia</b> <b>Tucker</b> REP, Inc. (404) 938-4358	<b>North Carolina</b> <b>Raleigh</b> REP, Inc. (919) 851-3007	<b>Ottawa</b> Cantec (613) 225-0363
<b>Illinois</b> <b>Rolling Meadows</b> Sumer (312) 394-4900		<b>Quebec</b> <b>Pierre Ponds</b> Cantec (514) 620-3121
<b>Indiana</b> <b>Indianapolis</b> Electro Reps (317) 255-4147		

# Distributors

## U.S.A.

### Alabama

**Huntsville**  
Hall-Mark Electronics (205) 837-8700

### Arizona

**Phoenix**  
Kierulff Electronics (602) 243-4101  
Sterling Electronics (602) 258-4531

### California

**Los Angeles**  
Kierulff Electronics (213) 685-5511

**Palo Alto**  
Kierulff Electronics (415) 968-6292

**San Diego**  
Intermark Electronics (714) 279-5200  
Kierulff Electronics (714) 278-2112

**Santa Ana**  
Intermark Electronics (714) 540-1322

**Sunnyvale**  
Diplomat/Westland (408) 734-1900  
Intermark Electronics (408) 738-1111

**Tustin**  
Kierulff Electronics (714) 731-5711

### Colorado

**Denver**  
Kierulff Electronics (303) 371-6500

**Wheatridge**  
Century Electronics (303) 424-1985

### Connecticut

**Hamden**  
Arrow Electronics (203) 248-3801

**Wilton**  
Components for Industries (203) 762-8691

### Florida

**Clearwater**  
Diplomat/Southland (813) 443-4514

**Fort Lauderdale**  
Arrow Electronics (305) 776-7790  
Hall-Mark Electronics (305) 971-9280

**Orlando**  
Hall-Mark Electronics (305) 855-4020

### Illinois

**Elk Grove Village**  
Hall-Mark Electronics (312) 437-8800  
Kierulff Electronics (312) 640-0200

### Indiana

**Indianapolis**  
Advent Electronics (317) 297-4910

### Kansas

**Shawnee Mission**  
Hall-Mark Electronics (913) 888-4747

### Maryland

**Baltimore**  
Arrow Electronics (202) 737-1700  
Pyttronics/Savage (301) 792-0780

**Gaithersburg**  
Pioneer Washington (301) 948-0710

**Savage**  
Pyttronics Industries (301) 792-0780

### Massachusetts

**Billerica**  
Kierulff Electronics (617) 935-5134

**Burlington**  
Lionex (617) 272-9400

**Woburn**  
Arrow Electronics (617) 933-8130

### Michigan

**Ann Arbor**  
Arrow Electronics (313) 971-8220

**Farmington**  
Diplomat/Northland (313) 477-3200

### Minnesota

**Bloomington**  
Arrow Electronics (612) 887-6400

Hall-Mark Electronics (612) 884-9056

### Missouri

**Earth City**  
Hall-Mark Electronics (314) 291-5350

### New Hampshire

**Manchester**  
Arrow Electronics (603) 668-6968

### New Jersey

**Fairfield**  
Kierulff Electronics (201) 575-6750

**Totowa**  
Diplomat/IPC (201) 785-1830

**Moorestown**  
Arrow Electronics (609) 235-1900

**Rutherford**  
Kierulff Electronics (201) 935-2120

**Saddlebrook**  
Arrow Electronics (201) 797-5800

### New Mexico

**Albuquerque**  
Century Electronics (505) 292-2700

### New York

**Buffalo**  
Summit Distributors (716) 884-3450

**Farmingdale**  
Arrow Electronics (516) 694-6800

**Rochester**  
Summit Distributors (716) 334-8110

**Smithtown**  
Current Components (516) 979-9030

**Woodbury**  
Diplomat Electronics (516) 921-9373

### North Carolina

**Raleigh**  
Hall-Mark Electronics (919) 832-4465

### Ohio

**Cleveland**  
Arrow Electronics (216) 464-2000

**Dayton**  
Arrow Electronics (513) 253-9176

### Oklahoma

**Tulsa**  
Hall-Mark Electronics (918) 835-8458

### Oregon

**Portland**  
Almac/Strom Electronics (503) 292-3534

### Pennsylvania

**Horsham**  
Pioneer/Delaware Valley (215) 674-4000

### Texas

**Austin**  
Hall-Mark Electronics (512) 837-2814  
Quality Components (512) 458-4181

**Dallas**  
Hall-Mark Electronics (214) 234-7400  
Quality Components (214) 387-4949

**Houston**  
Hall-Mark Electronics (713) 781-6100  
Quality Components (713) 772-7100  
Sterling Electronics (713) 627-9800

### Utah

**Salt Lake City**  
Calron Electric Supply (801) 487-7451  
Century Electronics (810) 972-6969

### Washington

**Seattle**  
Almac/Strom Electronics (206) 763-2300

**Tukwila**  
Kierulff Electronics (206) 575-4420

### Wisconsin

**West Allis**  
Hall-Mark Electronics (414) 476-1270

## CANADA

### Ontario

**Ottawa**  
Zentronics Limited (613) 238-6411

**Toronto**  
Future Electronics (416) 675-7820  
Zentronics Limited (613) 238-6411

### British Columbia

**Vancouver**  
Bowtek Electric (604) 736-1141

### Manitoba

**Winnipeg**  
Bowtek Electric (204) 633-9523

### Quebec

**Montreal**  
Future Electronics (514) 735-5775  
Zentronics Limited (514) 735-5361

### Alberta

**Edmonton**  
Bowtek Electric (403) 426-1072

6

## EUROPE

### Headquarters

**Monolithic Memories, GMBH**  
Mauerkircherstr. 4  
8000 München 80  
West Germany  
Phone: 89-982601  
Telex: 524385  
Fax: 89-983162

### AUSTRIA

**Ing. Ernst Steiner**  
Geylinggasse 16  
1130 Wien  
Phone: 222-822674  
Telex: 74013

### BELGIUM

**Ritro Electronics N.V.**  
Plantin & Moretuslei 172  
2000 Antwerpen  
Phone: 31-353272  
Telex: 33637

### DENMARK

**C-88**  
Uldvejen 10  
DK 2970 Hørsholm  
Phone: 2-570888  
Telex: 37578

### ENGLAND

**Memory Devices Ltd.**  
Central Avenue  
East Molesey  
KT8 OSN  
Phone: 1-9411066  
Telex: 929962

**Macro Marketing Ltd.**  
396 Bath Road  
Slough, Berkshire  
Phone: 6286-63011  
Telex: 847083

### FINLAND

**Telercas O.Y.**  
P.O. Box 2  
01511 Vantaa 51  
Phone: 0-821655  
Telex: 121111

### FRANCE

**Monolithic Memories France  
S.A.R.L.**  
Silic 463  
94613 Rungis Cedex  
Paris  
Phone: 1-6874500  
Telex: 202146F

**ALFATRONIC**  
La Tour d'Asnieres 4  
Avenue Laurent  
Cely 92606

Asnieres / Frankreich  
Phone: Asnieres 1-7914444  
Telex: 612790

### A2M

Assistance Microprocesseurs  
Microprogrammation  
40, Rue des Tilleuls  
92100 Boulogne  
Phone: 1-6036640  
Telex: 200491

### Radio Equipments-Antares S.A.

9, Rue Ernest Cognacq  
92301 Levallois Perret  
Phone: 1-7581111  
Telex: 620630

## GERMANY

### Monolithic Memories, GMBH

Mauerkircherstr. 4  
8000 München 80  
West Germany  
Phone: 89-982601  
Telex: 524385  
Fax: 89-983162

### ASTRONIC GMBH

Winzererstrasse 47 D  
8000 München 40  
Phone: 89-304011  
Telex: 5216187

### ELECTRONIC 2000

Vertriebs-GMBH  
Neumarkter Strasse 75  
8000 München 80  
Phone: 89-434061  
Telex: 522561

### PANEL Electronic Vertriebs GMBH

Hermann Oberth Str. 7  
8011 Putzbrunn  
Phone: 89-464024  
Telex: 529238

### POSITRON Bauelemente

Vertriebs GMBH  
Benzstrasse 1  
Postfach 1140  
7016 Gerlingen  
Phone: 7156-23051  
Telex: 7245266

## NETHERLANDS

### Ritro Electronics B.V.

Gelreweg 22  
Postbus 123  
2930 Barneveld  
Phone: 3420-5041  
Telex: 40553

### Famatra Benelux

P.O. Box 721  
4803 AS Breda  
Phone: 76-133457  
Telex: 54521

## ISRAEL

### TELSYS Ltd.

54, Jabotinsky Rd.  
Ramat-Gan  
Phone: 3-739865  
Telex: 032392

## ITALY

### Compres S.R.L.

20092 Cinisello Balsamo/Milano  
Viale Romagna 1  
Phone: 2-9280809  
Telex: 39484

## NORWAY

### Henaco A/S

P.O. Box 248  
Okern Torgveit 13  
Oslo 5  
Phone: 2-157550  
Telex: 16716

## SPAIN

### Comisa Ingenieros S.A.

Reina Mercedes, 20  
Madrid 20  
Spanien  
Phone: 1-2542901/04  
Telex: 237231

## SWEDEN

### NAXAB

Box 4115  
17104 Solna  
Phone: 8-985140  
Telex: 17912

## SWITZERLAND

### Baerlocher A.G.

Förrlibuckstrasse 110  
8005 Zürich  
Phone: 1-429900  
Telex: 53118

## FAR EAST

### Headquarters

### Monolithic Memories Japan KK

Parkside-Flat Bldg.  
4-2-2, Sendagaya  
Shibuya-Ku  
Tokyo 151  
Phone: 3-4039061  
Telex: 781-26364

## AUSTRALIA

### R & D Electronics Pty Ltd.

23 Burwood Rd.  
Burwood, Vic. 3125  
Phone: 288-8232  
Telex: AA33288

## INDIA

### Chawla Sales

3481, Netaji Subhash Marg.  
Daryaganj, New Delhi - 110002  
Phone: 277388

### Zenith Electronics

541 Panchratna  
Mama Parmanand Marg  
Bombay 4  
Phone: 384212  
Telex: 0113152



# **PAL PROGRAMMABLE ARRAY LOGIC Handbook**



**MONOLITHIC MEMORIES GMBH · EUROPEAN HEADQUARTERS  
MAUERKIRCHERSTR. 4 · D-8000 MÜNCHEN 80  
TELEFON (089) \*98 26 01 · TELEX 5 24385 mono d  
TELEKOPIERER INFOTEC 6000: 98 31 62**