

DESIGN SHOWCASE

Temperature Compensation Stabilizes LCD Contrast

The variation of LCD contrast with temperature can be a problem in some applications. Working in a meat-packing plant, for instance, you might go from scanning sides of beef in a refrigerated locker to downloading data from your LCD bar-code reader in a heated office. That temperature change would definitely require an LCD-bias adjustment.

Combining automatic bias adjustment with manual-adjust capability lets the user compensate for LCD viewing angles and manufacturing differences (Figure 1). This circuit provides a linear bias change with temperature, from -10V at 50°C to -15V at -20°C (Figure 2). (IC₁ is a power-supply chip for portable systems that includes two other switching-regulator controllers and four linear-regulator controllers, plus circuitry for backup-battery switchover, low-voltage warning, and power-fail reset.)

The automatic compensation is provided by a negative-temperature-coefficient resistor (R5) that affects the feedback for the V6 regulator in IC₁. Decreasing temperature, for instance, causes an increase in R5's resistance and a consequent increase in the LCD bias voltage (V6). R₄ linearizes the effect of R5, and R₃ adjusts the temperature coefficient of R5 to that of the LCD. (Other tempcos require different values for R₂ and R₃.)

To calculate R₂ and R₃, note that V₆ is a function of V_{D/A} and R_T. V_{D/A} is the output of the internal

5-bit D/A converter, which allows the user to digitally adjust the LCD bias voltage, and R_T is the sum of R₃ and the parallel combination of R₄ and R₅:

$$V_6 = V_{D/A} - \frac{(5V - V_{D/A})RT}{R_2}$$

$$\text{therefore } R_T = \frac{R_2(V_{D/A} - V_6)}{(5V - V_{D/A})}$$

Solve for R_T at the extremes of V₆ (-10V and -15V) using the midrange value for V_{D/A} (0.625V):

$$V_6 = -10V: R_T = 2.43R_2$$

$$V_6 = -15V: R_T = 3.57R_2$$

Equivalent expressions for R_T are based on its definition:

$$V_6 = -10V: R_T = R_3 + (R_5 @ 50^\circ\text{C}) \parallel R_4$$

$$V_6 = -15V: R_T = R_3 + (R_5 @ -20^\circ\text{C}) \parallel R_4$$

From the R5 data sheet, R₄ = 277kΩ (choose 280k, 1%), R₅ @ 50°C = 52.7kΩ, and R₅ @ -20°C = 250.1kΩ. Substitute these values above, equate corresponding expressions for R_T, and solve for R₂ and R₃:

$$R_2 = 172k\Omega \text{ (use } 169k\Omega, 1\%)$$

$$R_3 = 365k\Omega \text{ (use } 365k\Omega, 1\%)$$

(Circle 5)

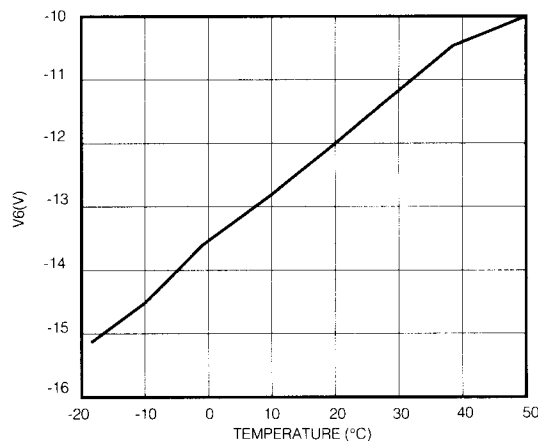


Figure 2. The regulator output in Figure 1 serves as a temperature-compensated bias voltage for LCDs.

DESIGN SHOWCASE

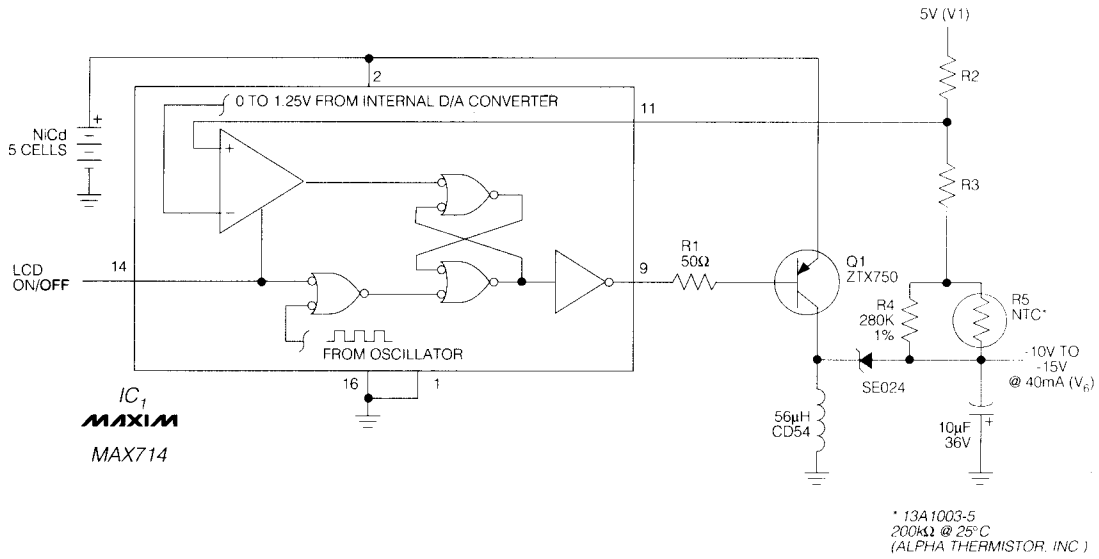


Figure 1. The negative-tempco resistor R5 modifies feedback in this switching regulator, resulting in a negative output voltage that varies with temperature. With properly chosen resistor values (see text) the circuit produces a temperature-compensated bias voltage that assures constant contrast in an LCD.