Mar 01, 2001



Understanding SAR ADCs

Successive-approximation-register (SAR) analog-to-digital converters (ADCs) represent the majority of the ADC market for medium to high resolution ADCs. SAR ADCs provide up to 5Msps sampling rates with resolutions from 8 to 18 bits. The SAR architecture allows for high performance, low power ADCs to be packaged in small form factors for today's demanding applications.

This paper will explain how the SAR ADC operates using a binary search algorithm to converge on the input signal. It also provides an explanation for the heart of the SAR ADC, the capacitive DAC and also the high-speed comparator. Finally, the article will contrast the SAR architecture against pipeline, flash ADCs.

Successive-approximation-register (SAR) analog-to-digital converters (ADCs) are frequently the architecture of choice for medium-to-high-resolution applications with sample rates under 5 megasamples per second (Msps). SAR ADCs most commonly range in resolution from 8 to 16 bits and provide low power consumption as well as a small form factor. This combination makes them ideal for a wide variety of applications, such as portable/battery-powered instruments, pen digitizers, industrial controls, and data/signal acquisition.

As the name implies, the SAR ADC basically implements a binary search algorithm. Therefore, while the internal circuitry may be running at several megahertz (MHz), the ADC sample rate is a fraction of that number due to the successive-approximation algorithm.

SAR ADC Architecture

Although there are many variations in the implementation of a SAR ADC, the basic architecture is quite simple (see Figure 1). The analog input voltage (V_{IN}) is held on a track/hold. To implement the binary search algorithm, the N-bit register is first set to midscale (that is, 100... .00, where the MSB is set to '1'). This forces the DAC output (V_{DAC}) to be $V_{REF}/2$, where V_{REF} is the reference voltage provided to the ADC. A comparison is then performed to determine if V_{IN} is less than or greater than V_{DAC} . If V_{IN} is greater than V_{DAC} , the comparator output is a logic high or '1' and the MSB of the N-bit register remains at '1'. Conversely, if V_{IN} is less than V_{DAC} , the comparator output is a logic low and the MSB of the register is cleared to logic '0'. The SAR control logic then moves to the next bit down, forces that bit high, and does another comparison.

The sequence continues all the way down to the LSB. Once this is done, the conversion is complete, and the N-bit digital word is available in the register.

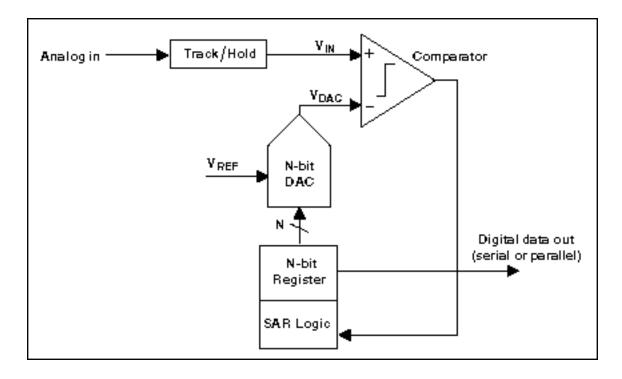


Figure 1. Simplified N-bit SAR ADC architecture

Figure 2 shows an example of a 4-bit conversion. The y-axis (and the bold line in the figure) represents the DAC output voltage. In the example, the first comparison shows that $V_{IN} < V_{DAC}$. Thus, bit 3 is set to '0'. The DAC is then set to 0100_2 and the second comparison is performed. As $V_{IN} > V_{DAC}$, bit 2 remains at '1'. The DAC is then set to 0110_2 , and the third comparison is performed. Bit 1 is set to '0', and the DAC is then set to 0101_2 for the final comparison. Finally, bit 0 remains at '1' because $V_{IN} > V_{DAC}$.

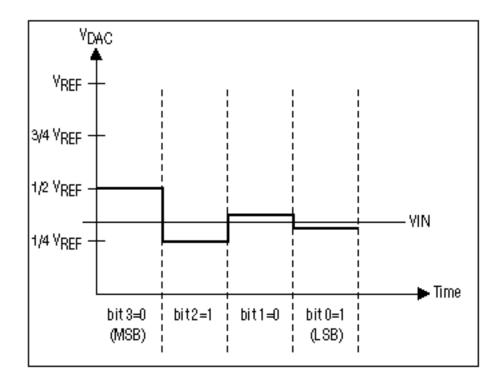


Figure 2. SAR operation (4-bit ADC example)

Notice that four comparison periods are required for a 4-bit ADC. Generally speaking, an N-bit SAR ADC will require N comparison periods and will not be ready for the next conversion until the current one is complete. This explains why these types of ADCs are power- and space-efficient, yet are rarely seen in speed-and-resolution combinations beyond a few Msps at 14 to 16 bits. Some of the smallest ADCs available on the market are based on the SAR architecture. The MAX1115-MAX1118 series of 8-bit ADCs as well as their higher-resolution counterparts, the MAX1086 and the MAX1286 (10 and 12 bits, respectively), fit in tiny SOT23 packages measuring 3mm by 3mm.

One other feature of SAR ADCs is that power dissipation scales with the sample rate, unlike flash or pipelined ADCs, which usually have constant power dissipation versus sample rate. This is especially useful in low-power applications or applications where the data acquisition is not continuous (for example, PDA digitizers).

In-Depth SAR Analysis

The two critical components are the comparator and the DAC. As we shall see later, the track/hold shown in Figure 1 can be embedded in the DAC and may not be an explicit circuit.

A SAR ADC's speed is limited by:

 The settling time of the DAC, which must settle to within the resolution of the overall converter, for example, 1/2LSB

- The comparator, which must resolve small differences in V_{IN} and V_{DAC} within the specified time
- The logic overhead

DAC

The maximum settling time of the DAC is usually determined by the MSB settling. This is simply because the MSB transition represents the largest excursion of the DAC output. In addition, the linearity of the overall ADC is limited by the linearity of the DAC. Therefore, SAR ADCs with more than 12 bits of resolution will often require some form of trimming or calibration to achieve the necessary linearity. This is due to the inherent component-matching limitations. Although it is somewhat process-and-design-dependent, component matching limits the linearity to about 12 bits in practical DAC designs. Many SAR ADCs use a capacitive DAC that provides an inherent track/hold function. Capacitive DACs employ the principle of charge redistribution to generate an analog output voltage. Because these types of DACs are prevalent in SAR ADCs, it is beneficial to discuss their operation.

A capacitive DAC consists of an array of N capacitors with binary weighted values plus one "dummy LSB " capacitor. Figure 3 shows an example of a 16-bit capacitive DAC connected to a comparator. During the acquisition phase, the array's common terminal (the terminal at which all the capacitors share a connection, see Figure 3) is connected to ground and all free terminals are connected to the input signal (Analog In or V_{IN}). After acquisition, the common terminal is disconnected from ground and the free terminals are disconnected from V_{IN}, effectively trapping a charge proportional to the input voltage on the capacitor array. The free terminals of all the capacitors are then connected to ground, driving the common terminal negative to a voltage equal to $-V_{IN}$.

As the first step in the binary search algorithm, the free terminal of the MSB capacitor is disconnected from ground and connected to V_{REF} , driving the common terminal in the positive direction by an amount equal to $1/2V_{REF}$. For example, if V_{IN} is equal to $3/4V_{REF}$, connecting the MSB capacitor to V_{REF} and the rest of the capacitors to ground will drive the common terminal to $(-3/4V_{REF} + 1/2V_{REF}) = -1/4V_{REF}$. When this voltage is compared to ground, the comparator output yields a logic '1', implying that the MSB is greater than $1/2V_{REF}$. Conversely, if V_{IN} is equal to $1/4V_{REF}$, the common terminal voltage is $(-1/4V_{REF} + 1/2V_{REF}) = +1/4V_{REF}$, and the comparator output is a logic '0'. Following this, the next-largest capacitor is disconnected from ground and connected to V_{REF} , and the comparator determines the next bit. This continues until all bits have been determined.

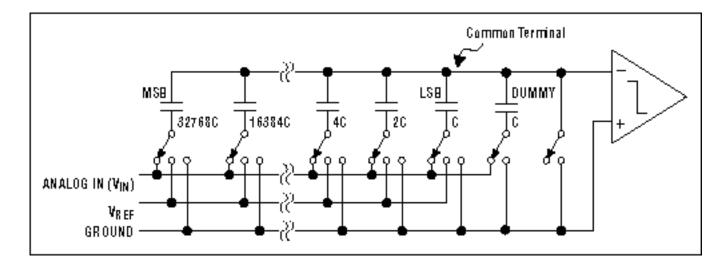


Figure 3. Capacitive DAC (16-bit example)

DAC Calibration

In an ideal DAC, each of the capacitors associated with the data bits would be exactly twice the value of the next-smaller capacitor. In high-resolution ADCs (for example, 16-bit), this results in a range of values too wide to be realized in an economically feasible size. The 16-bit SAR ADCs such as the MAX195 utilize a capacitor array that actually consists of two arrays that are capacitively coupled to reduce the LSB array's effective value. The capacitors in the MSB array are production-trimmed to reduce errors. Small variations in the LSB capacitors contribute insignificant errors to the 16-bit result. Unfortunately, trimming alone does not yield 16-bit performance or compensate for changes in performance due to changes in temperature, supply voltage, and other parameters. For this reason, the MAX195 includes a calibration DAC for each capacitor in the MSB array. These DACs are capacitively coupled to the main DAC output and offset the main DAC's output according to the value on their digital inputs.

During calibration, the correct digital code to compensate for the error in each MSB capacitor is determined and stored. Thereafter, the stored code is provided to the appropriate-calibration DAC whenever the corresponding bit in the main DAC is high, compensating for errors in the associated capacitor. Calibration is usually initiated by the user or done automatically on power-up. To reduce the effects of noise, each calibration experiment is performed many times (about 14,000 clock cycles in the MAX195), and the results are averaged. Calibration is best performed when the power-supply voltages are stable, and high-resolution ADCs should be recalibrated any time there is a significant change in supply voltages, temperature, reference voltage, or clock characteristics, because these parameters affect the DC offset. If linearity is the only concern, much larger changes in these parameters can be tolerated. Because the calibration data is stored digitally, there is no need to perform frequent conversions to maintain accuracy.

Comparator

The requirements of the comparator are speed and accuracy. Comparator offset does not affect

overall linearity as it appears as an offset in the overall transfer characteristic. In addition, offsetcancellation techniques are usually applied to reduce the comparator offset. Noise, however, is a concern, and the comparator is usually designed to have input-referred noise less than 1LSB. Additionally, the comparator needs to resolve voltages within the accuracy of the overall system; in other words, the comparator needs to be as accurate as the overall system.

SAR ADCs versus Other ADC Architectures

Versus Pipelined

A pipelined ADC employs a parallel structure in which each stage works on one to a few bits (of successive samples) concurrently. The inherent parallelism increases throughput, but at the expense of power consumption and latency. Latency in this case is defined as the difference between the time an analog sample is acquired by the ADC and the time when the digital data is available at the output. For instance, a five-stage pipelined ADC will have at least five clock cycles of latency, whereas a SAR has only one clock cycle of latency. Note that the latency definition applies only to the throughput of the ADC, not the internal clock of a SAR, which runs at many times the frequency of the throughput. Pipelined ADCs frequently have digital error correction logic to reduce the accuracy requirement of the flash ADCs (that is, comparators) in each pipeline stage. On the other hand, a SAR ADC requires the comparator to be as accurate as the overall system. A pipelined ADC generally takes up significantly more silicon area than an equivalent SAR. Like a SAR, a pipelined ADC with more than 12 bits of accuracy usually requires some form of trimming or calibration.

Versus Flash

A flash ADC is made up of a large bank of comparators, each consisting of wideband, low-gain preamp(s) followed by a latch. The preamps only have to provide gain but do not need to be linear or accurate; meaning, only the comparators' trip points have to be accurate. As a result, a flash ADC is the fastest architecture available. The primary trade-off for speed is the significantly lower power consumption and the smaller form factor. Although extremely fast 8-bit flash ADCs (or their folding/interpolation variants) exist with sampling rates as high as 1.5GS/s (for example, the MAX104/MAX106/MAX108), it is much harder to find a 10-bit flash, while 12-bit (and above) flash ADCs are not commercially viable products. This is simply because in a flash the number of comparators goes up by a factor of 2 for every extra bit of resolution, and, at the same time, each comparator has to be twice as accurate. In a SAR ADC, however, the increased resolution requires more accurate components, yet the complexity does not increase exponentially. Of course, SAR ADCs are not capable of speeds anywhere close to those of flash ADCs.

Versus Sigma-Delta Converter

Traditional oversampling/sigma-delta-type converters commonly used in digital audio applications have limited bandwidths of about 22kHz. Recently, some high-bandwidth sigma-

delta-type converters have reached bandwidths of 1MHz to 2MHz with 12 to 16 bits of resolution. These are usually very-high-order sigma-delta modulators (for example, 4th-order or higher) incorporating a multi-bit ADC and multi-bit feedback DAC. Sigma-delta converters have the innate advantage of requiring no special trimming or calibration, even to attain 16 to 18 bits of resolution. They also do not require anti-alias filters with steep roll-offs at the analog inputs, because the sampling rate is much higher than the effective bandwidth; the backend digital filters take care of this. The oversampling nature of the sigma-delta converter may also tend to "average out" any system noise at the analog inputs. However, sigma-delta converters trade speed for resolution. The need to sample many times (at least 16 times and often more) to produce one final sample dictates that the internal analog components in the sigma-delta modulator operate much faster than the final data rate. The digital decimation filter is also a challenge to design and consumes a lot of silicon area. The fastest high-resolution sigma-delta converters are not expected to have significantly higher bandwidth than a few MHz in the near future.

Conclusion

In summary, the primary advantages of SAR ADCs are low power consumption, high resolution and accuracy, and a small form factor. Because of these benefits, SAR ADCs can often be integrated with other larger functions. The main limitations of the SAR architecture are the lower sampling rates and the requirements for the building blocks (such as the DAC and the comparator) to be as accurate as the overall system.

References

1. Maxim Integrated Products; MAX195 data sheet, Rev 1, 12/1997.

2. Razavi, Behzad; Principles of Data Conversion System Design; IEEE Press, 1995.

3. Van De Plassche, Rudy; Integrated Analog-to-Digital and Digital-to-Analog Converters; Kluwer Academic Publishers, 1994.

4. Maxim Integrated Products; Understanding Pipelined ADCs.

More Information

MAX1065: QuickView Full (PDF) Data Sheet Free Samples
MAX1066: QuickView Full (PDF) Data Sheet Free Samples
MAX1111: QuickView Full (PDF) Data Sheet Free Samples
MAX1118: QuickView Full (PDF) Data Sheet
MAX1132: QuickView Full (PDF) Data Sheet Free Samples
MAX1133: QuickView Full (PDF) Data Sheet Free Samples
MAX1162: QuickView Full (PDF) Data Sheet Free Samples
MAX1165: QuickView Full (PDF) Data Sheet Free Samples
MAX1166: QuickView Full (PDF) Data Sheet Free Samples
MAX1280: QuickView Full (PDF) Data Sheet
MAX1290: QuickView Full (PDF) Data Sheet Free Samples
MAX195: QuickView Full (PDF) Data Sheet Free Samples