

Ultra Low Power Reset Generator

This application note describes an ultra-low power microprocessor reset generator that is capable of operating for decades from a single AA Lithium cell. Where continuous intermittent reset is desired, this relaxation-oscillator circuit can provide adjustable pulse width and reset period. Typical operation producing 100 μ s pulses each second requires only 1 μ A current from a 1.8-5.5V supply. Formulas are provided for calculation of component values for a wide range of pulse width and period.

When a processor-controlled device must be guaranteed to operate, designers often choose to reset the processor periodically rather than rely on a watchdog circuit. In low-power systems the periodic reset generator can consume a large part of the system current budget or may not be guaranteed to operate at low voltages.

This application note describes a low-power reset generator that generates a low going reset pulse of 100 μ S duration once per second, consumes less than 1 μ A and will operate from 1.8V to 5V with only slight variation of the output period.

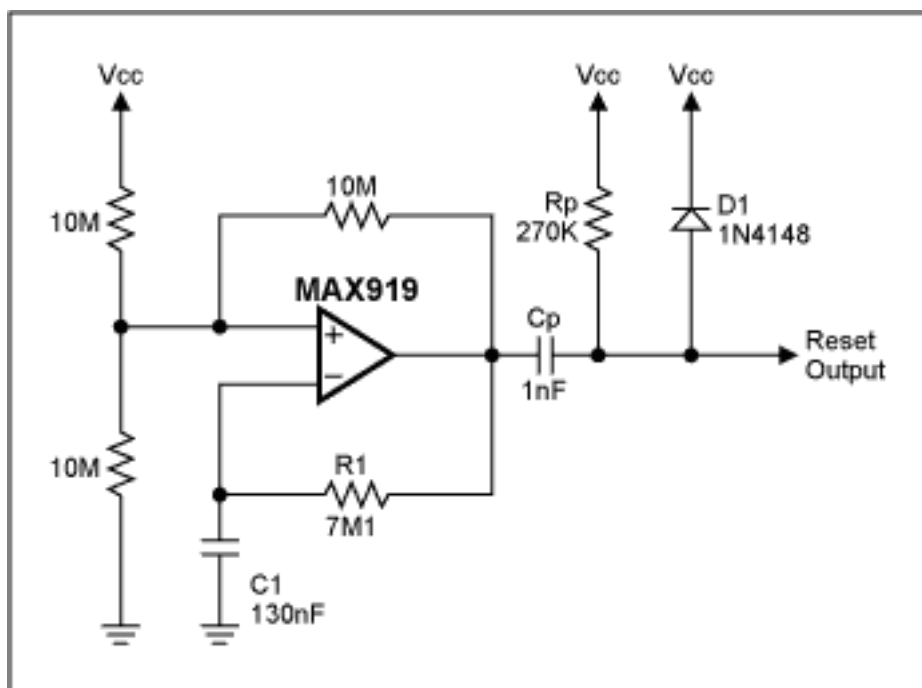


Figure 1. This reset circuit consumes less than 1 μ A and delivers a 100- μ sec-wide reset pulse every 1.3 sec.

The circuit is an adaptation of a normal relaxation oscillator with a differentiator and diode clamp on the output to generate the 100 μ S low going pulse. The pulse width can be adjusted by varying C_p or R_p and the polarity changed by repositioning D_1 . The period can be adjusted by varying R_1 or C_1 .

The 350nA supply current, 1.8V-5.5V supply voltage range and SOT23 package make the MAX919 ideal for this application. Measurements for the complete circuit give operating currents of less than 1 μ A at 25 $^\circ$ C, which would allow the circuit to operate from a single AA lithium cell for 250 years!

With careful component choice this circuit is able to generate periods from mS to minutes. To ensure good temperature stability R_1 and R_p should be metal film and C_1 and C_p should be NP0 type capacitors. Assuming a CMOS type input, high impedance and with a logic threshold of 30% of the supply rail, then the following formulas can be used to adjust the output pulse width and period:

$$\text{Pulse width} \cong 0.36 R_p C_p$$

$$\text{Period} \cong 1.4 R_1 C_1$$

Measured pulse width:

1.308 seconds @ 4.5V

1.306 seconds @ 1.8V

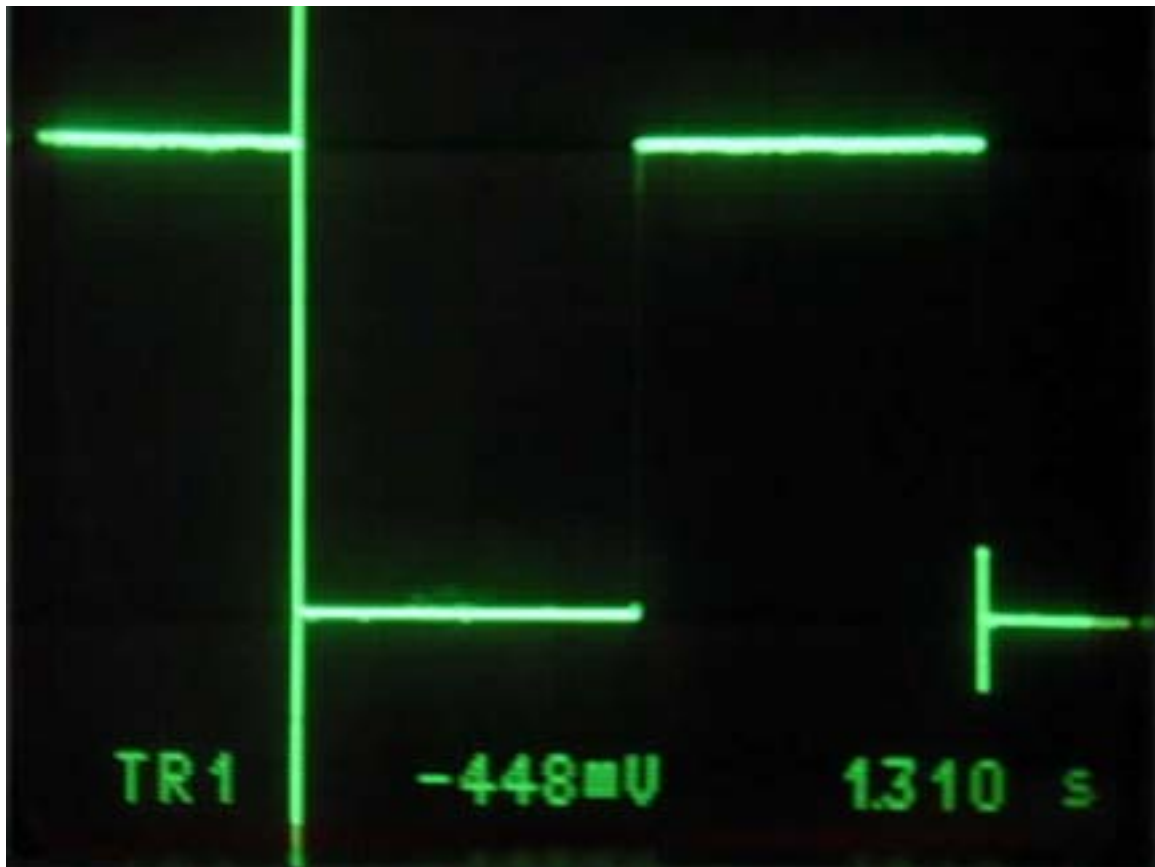


Figure 2. Comparator output; horizontal scale = 200mS/div, vertical scale = 1V/div, supply voltage = 4.5V, amplitude = 4.48Vp-p, period = 1.310 seconds.



Figure 3. Comparator output; horizontal scale = 200mS/div, vertical scale = 500mV/div, supply voltage = 1.7V, amplitude = 1.7Vp-p, period = 1.308 seconds.

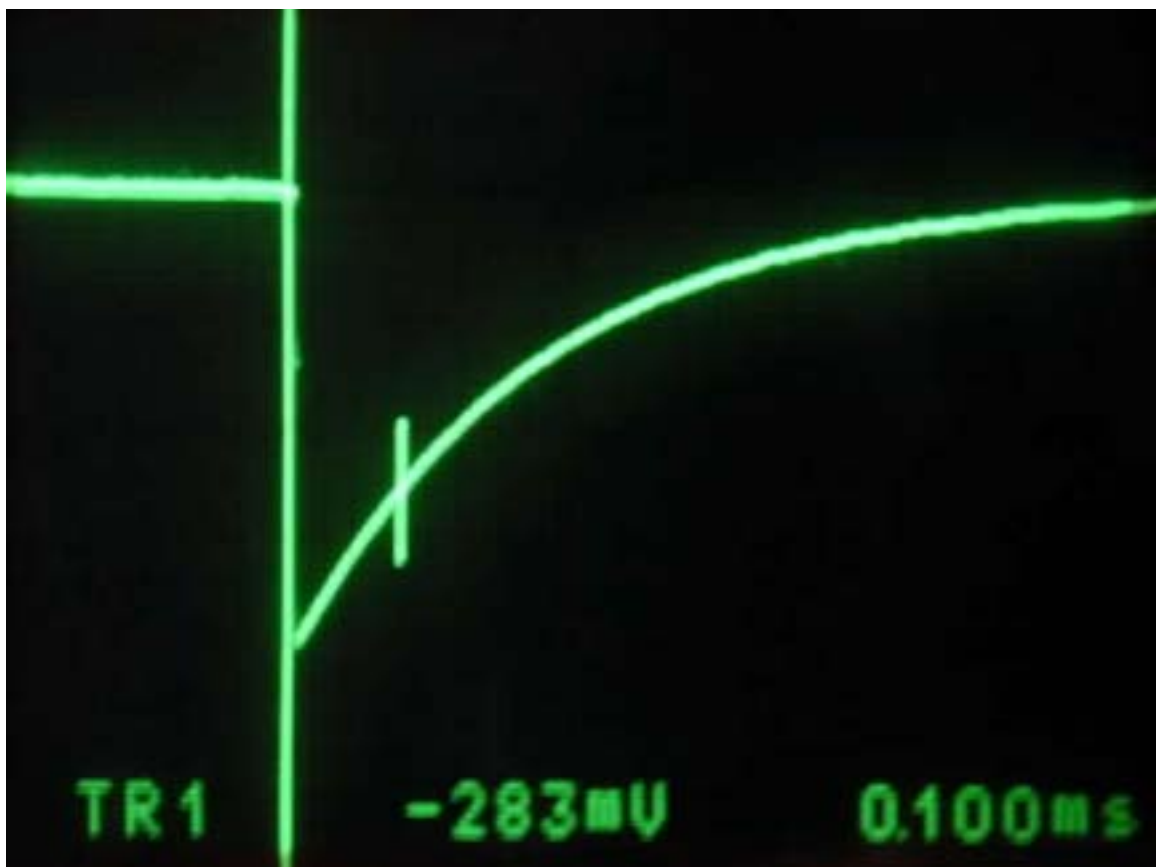


Figure 4. Pulse output; horizontal scale = $100\mu\text{S}/\text{div}$, vertical scale = $1\text{V}/\text{div}$, supply voltage = 4.5V , pulse width (30%) = $100\mu\text{S}$.

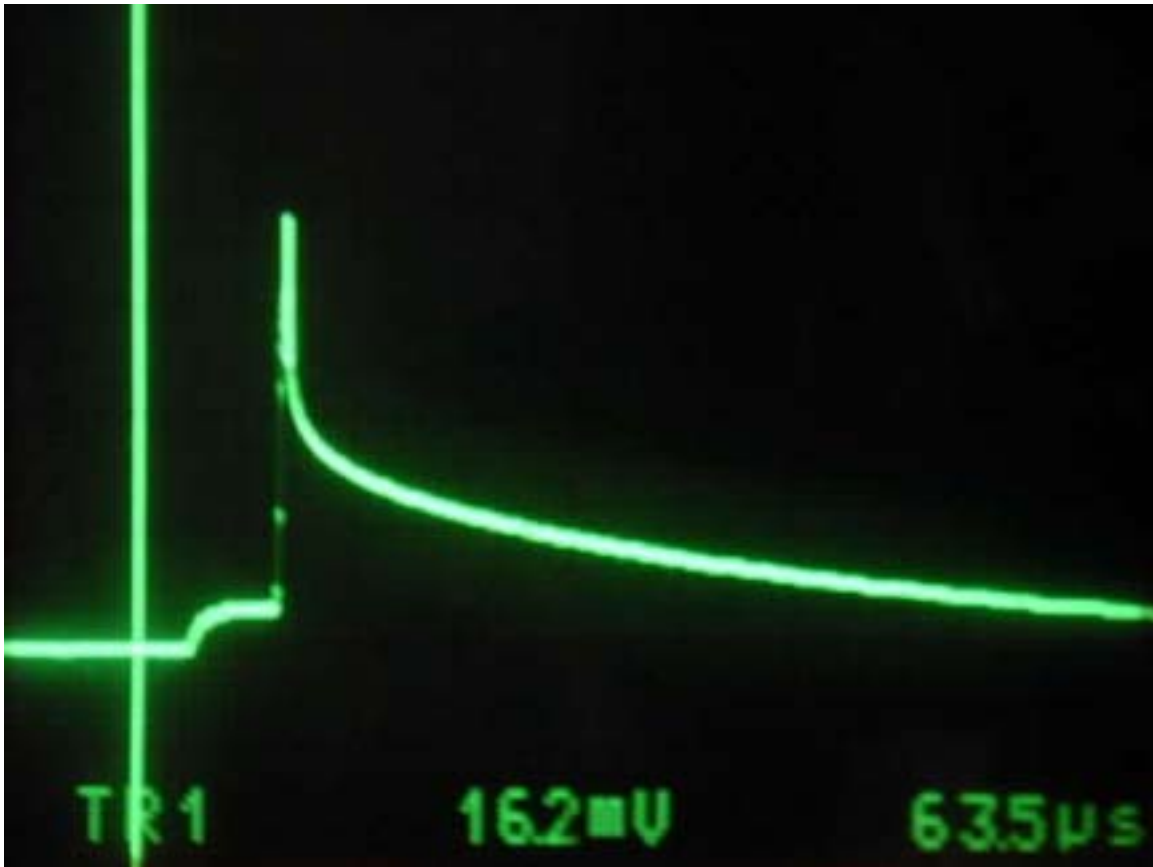


Figure 5. Clamp overshoot (at pulse output); horizontal scale = $50\mu\text{S}/\text{div}$, vertical scale = $50\text{mV}/\text{div}$, supply voltage = 4.5V , clamp overshoot = 162mV .

A similar version of this article appeared in the June 27, 2002 issue of *EDN* magazine.

DI456, September 2002

More Information

MAX919: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)