

APPLICATION NOTE 130

# Analog Switches Operate With 3V or 5V Supplies

*By adding a voltage doubler and voltage inverter, a single 3V or 5V power supply can produce the voltages necessary to improve the performance on a dual voltage analog switch. With the higher power supplies and wider range, the on resistance and timing performance are enhanced.*

By adding a single component to a 3V-only or 5V-only board, you can operate conventional CMOS analog switches with performance approaching that specified with  $\pm 15V$  supplies. This means fast switching, low on-resistance, CMOS/TTL compatibility, low power consumption, and a signal range ( $\pm V_{CC}$ ) that exceeds the input supply range ( $V_{CC}$  to ground).

Simply add a charge-pump voltage converter (IC1), which produces  $\pm 2V_{CC}$  outputs from a  $V_{CC}$  input. These unregulated voltages ensure reliable switch operation for  $V_{CC}$  levels as low as 3V. Logic thresholds for the switch remain unaffected.

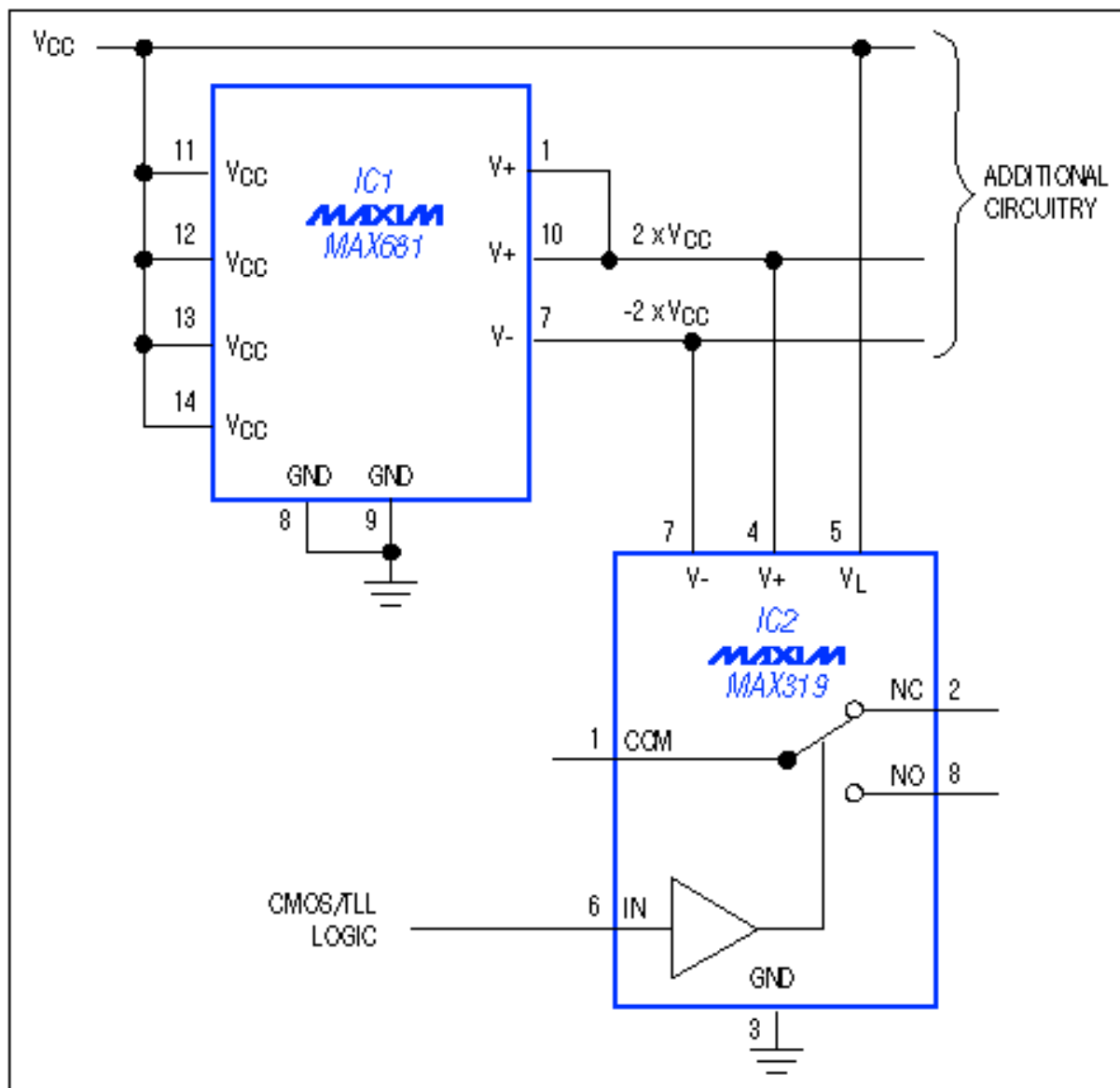




Figure 1. The charge pump (IC1) provides a local bipolar power supply for the CMOS analog switch (IC2).

A VCC of 3V (for instance) produces  $\pm 6V$  rails for the switch (IC2), resulting in on-resistance  $< 30\Omega$ , switching times  $< 200ns$ , leakage  $< 0.1nA$ , and ICC current  $< 0.5mA$ . Raising VCC to 5V produces  $\pm 10V$  rails, resulting in on-resistance  $< 20\Omega$ , switching times  $< 150ns$ , leakage  $< 0.4nA$ , and ICC current  $< 1.3mA$ .

IC1 can easily power additional switches and/or low-power op amps, but more than a few milliamps of load current degrades performance by lowering the unregulated supply rails.

### More Information

MAX319: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

MAX681: [QuickView](#) -- [Full \(PDF\) Data Sheet](#)