

## Low-Power 3V ADC is 0.05% Linear

*This application note describes using a microcontroller ( $\mu\text{C}$ ) with integrated digital-to-analog converter (DAC) and comparators to create a low cost ADC that is 0.05% linear.*

The simple 3V analog-to-digital converter (ADC) shown in Figure 1 is very small, requires no negative supply or expensive precision components, and draws minimal supply current ( $10\mu\text{A}$ ). A single conversion consists of 12,000 comparisons and takes about 300ms. The circuit operates as described below.

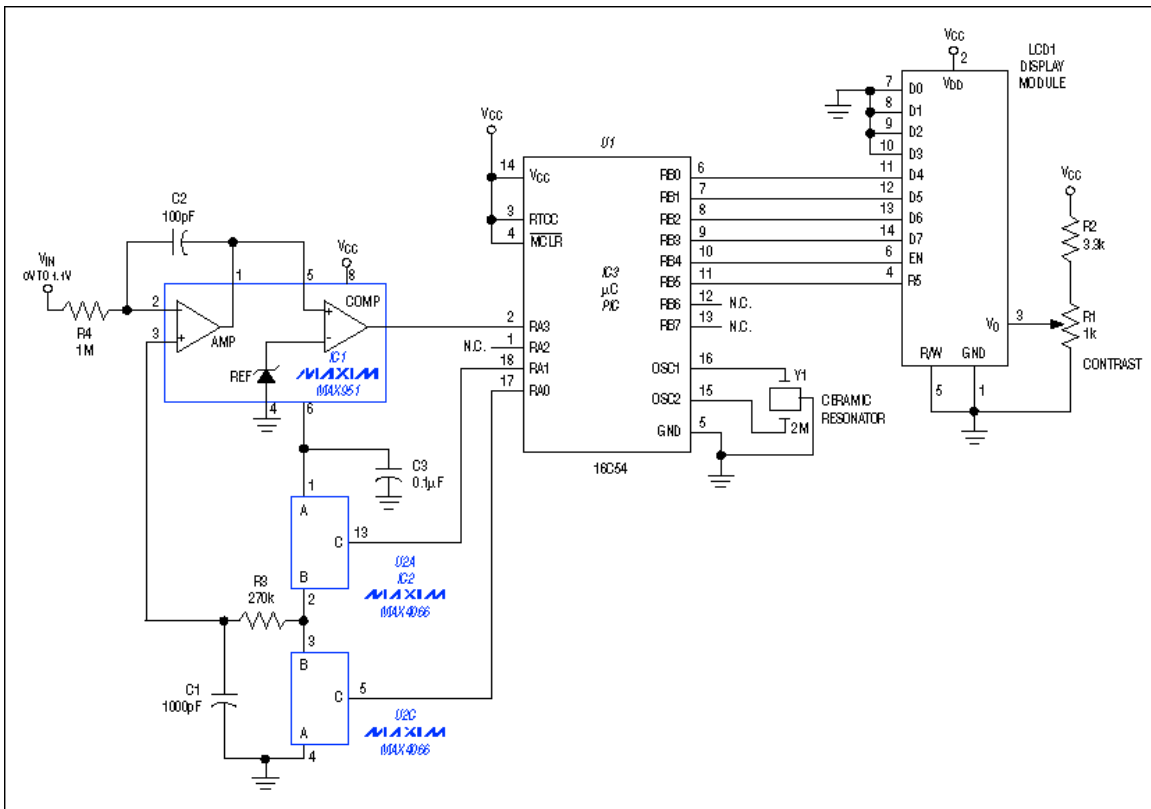


Figure 1. This inexpensive, 0.05%-linear ADC can be added to existing equipment or used to upgrade the converter included in certain  $\mu\text{C}$ s (such as the PIC 16C71).

Following each comparison, the microcontroller ( $\mu\text{C}$ ) closes one of two switches: IC2A (comparator high) or IC2B (comparator low). The switches connect either  $V_{\text{REF}}$  (1.2V) or ground to their "B" terminals, producing a pulse-width modulation (PWM) signal that is filtered by R3 and C1 and differentially integrated against  $V_{\text{IN}}$ . The result is compared against  $V_{\text{REF}}$ .

As this action integrates the error voltage up and down, the  $\mu\text{C}$  counts the number of comparisons for which the comparator output is high (IC2A switch closed). This count ( $N_{\text{H}}$ ) divided by 12,000 equals the PWM duty cycle. The system is fully ratiometric, so the duty cycle equals  $N_{\text{H}}/12000 = V_{\text{IN}}/V_{\text{REF}}$ . Rearranging and substituting  $V_{\text{REF}} = 1.2\text{V}$  yields  $V_{\text{IN}} = N_{\text{H}}/10,000$ .

Listing 1\* enables the the LCD module to display voltage values directly, like a digital panel meter. The subroutine "DVM" produces the actual A/D-conversion values required in an embedded application. Setting the span constant (number of comparisons) to 12,000 yields a 300ms conversion with 4-1/2 digits of resolution and produces a 1.1999 full-scale display. You can speed the conversion to 30ms by setting the span constant to 1200, which produces a 3-1/2 digit display that reads 1.199 at full scale.

IC2's near-ideal switching characteristics account for the low 0.05% nonlinearity. A high-performance, 3V-specified version of the industry-standard 4066, IC2 is a quad analog switch that features 35Ω on-resistances and 0.1nA (max) off leakages. You can save space by replacing IC2 with the MAX323 dual analog switch: a 3V single-pole/single-throw device with specifications similar to those of the MAX4066. The MAX323 resides in an 8-pin μMAX package (versus a 14-pin SO for the MAX4066).

V<sub>CC</sub> is limited to the maximum allowed by the μC (6V). IC1, which operates with V<sub>CC</sub> as low as 2.8V over temperature, draws only 7μA of supply current. The voltage reference in IC1 is stable for capacitive loads smaller than 100pF or larger than 0.05μF. To ensure stability, the reference's external bypass capacitor (C3) should be kept large.

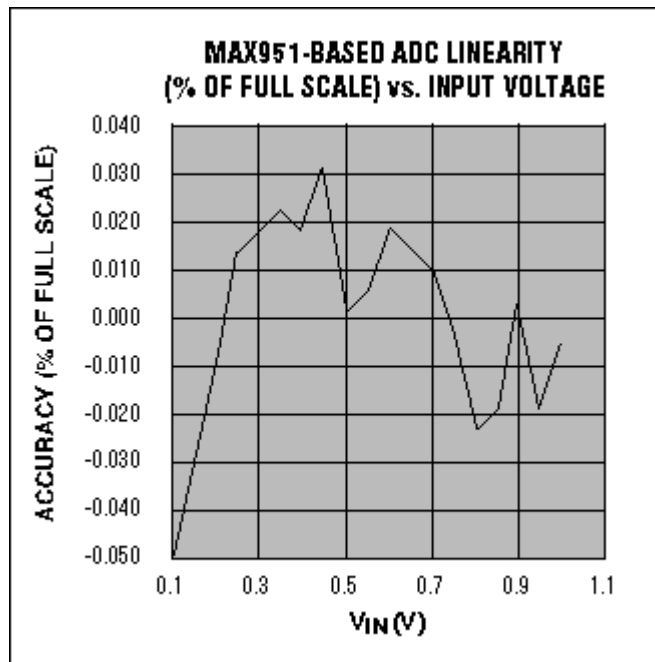


Figure 2. In Figure 1, the output nonlinearity (as a percentage of full scale) varies as shown.

\*See a similar version of this article in the June 19, 1997 issue of *EDN* magazine.

**MORE INFORMATION**

MAX4006: [QuickView](#)  
 MAX951: [QuickView](#)

-- [Full \(PDF\) Data Sheet \(256k\)](#)  
 -- [Full \(PDF\) Data Sheet \(368k\)](#)

-- [Free Sample](#)  
 -- [Free Sample](#)