

Pulse-Width Modulator Operates at Various Levels of Frequency and Power

Build a general-purpose pulse-width modulator using three op amps from a quad-op-amp device.

The many applications for pulse-width modulation (PWM) include voltage regulation, power-level control, and fan-speed control. A PWM circuit for such applications (Figure 1) can be implemented with three op amps from a single quad-op-amp chip. The use of op amps allows a wide variety of applications. Low-power op amps can be used in a low-power system, for example, and high-frequency op amps can be used for a high-frequency PWM. The Figure 1 circuit also generates a triangular wave.

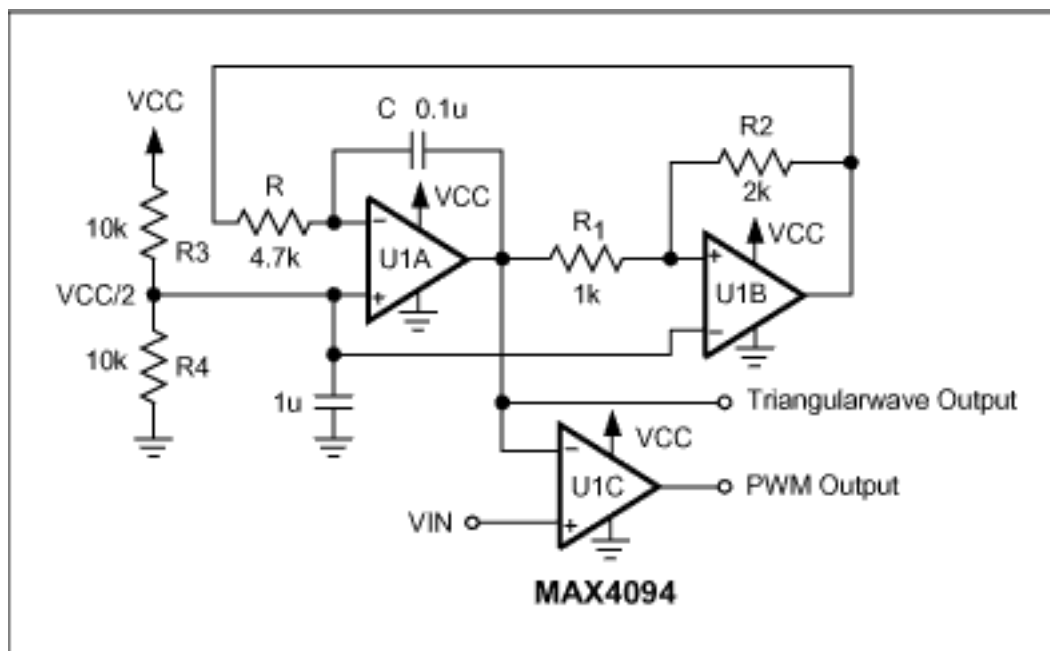


Figure 1. This 3-op-amp circuit produces a triangular wave and a variable-pulsewidth output.

The circuit consists of a triangle-wave generator (U1A and U1B) and a comparator (U1C). U1A is configured as an integrator (or de-integrator), and U1B as a comparator with hysteresis. At power-up, the comparator's output voltage is assumed to be zero.

U1A's non-inverting input is biased at $VCC/2$. A virtual connection between the inverting and non-inverting inputs allows a constant current through R equal to $I = VCC/2R$, which charges the capacitor C. Thus, the U1A integrator output increases linearly with time. When it reaches

0.75VCC, the comparator output (U1B) changes to its maximum output voltage (VCC). At that point the integrator begins to de-integrate, causing the output voltage to decrease linearly. When it reaches 0.25VCC the comparator output voltage changes to zero, and the cycle repeats. Thus, the integrator output is a triangular wave that swings between the levels of $\frac{1}{4}VCC$ and $\frac{3}{4}VCC$.

U1C compares the triangular wave against the dc level VIN. Its output is a square wave, with a duty cycle that varies from 0% to 100% as VIN varies from $\frac{1}{4}VCC$ to $\frac{3}{4}VCC$ (Figure 2). Frequency is determined by R, C, R₁, and R₂:

$$f = \frac{R_2}{4RCR_1}, \text{ where } R_2 > R_1.$$

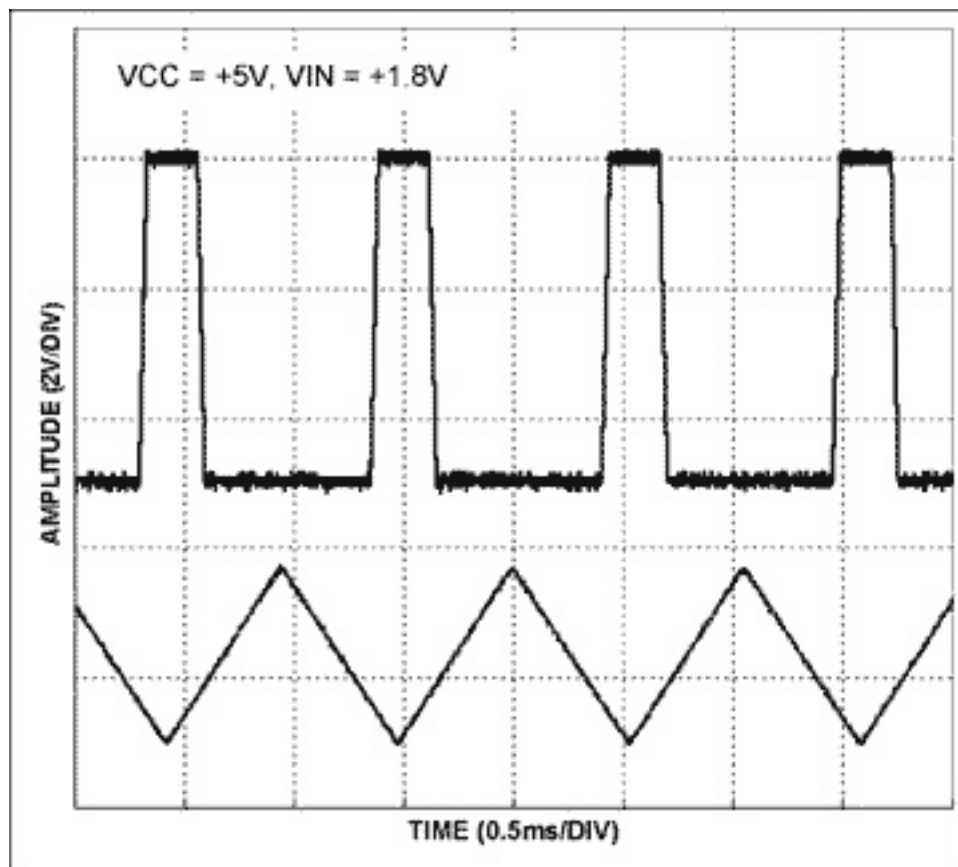


Figure 2. The Figure 1 circuit produces these PWM and triangular-wave outputs.

The ratio of R₂ and R₁ affects the operating frequency and the amplitude of the triangular wave. Given that V_{TH} is the triangular wave's maximum voltage and V_{TL} is its minimum voltage, the amplitude swing is:

$$V_{TH} = \frac{VCC(R_1 + R_2)}{2R_2} \text{ and } V_{TL} = \frac{VCC(R_2 - R_1)}{2R_2}, \text{ where } R_2 > R_1.$$

$$\text{Therefore, } V_{TH} - V_{TL} = \frac{R_1}{R_2} VCC \text{ (} R_2 > R_1 \text{)}.$$

The triangular wave's peak-to-peak voltage (the difference in its maximum and minimum voltages) is centered at the $VCC/2$ bias voltage generated by R_3 and R_4 . The circuit configuration shown allows the PWM to operate on a single supply. Use micropower op amps and larger resistors (R and $R_1 - R_4$) for low-power applications, and high-frequency op amps for higher-frequency applications. (The quad op amp shown comes in a single package.)

More Information

MAX4094: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)