

# App Note 3334: Interfacing a MAX6900 RTC with an 8051-Type Microcontroller

*This app note provides example hardware and software for interfacing the MAX6900 with an 8051-type microcontroller.*


## Description

This app note shows how to interface a MAX6900 I<sup>2</sup>C-Compatible RTC (real-time clock) to an 8051-type microcontroller ( $\mu$ C) and provides example code showing basic interface routines. The microcontroller used in this example is the DS2250, and the software is written in C.
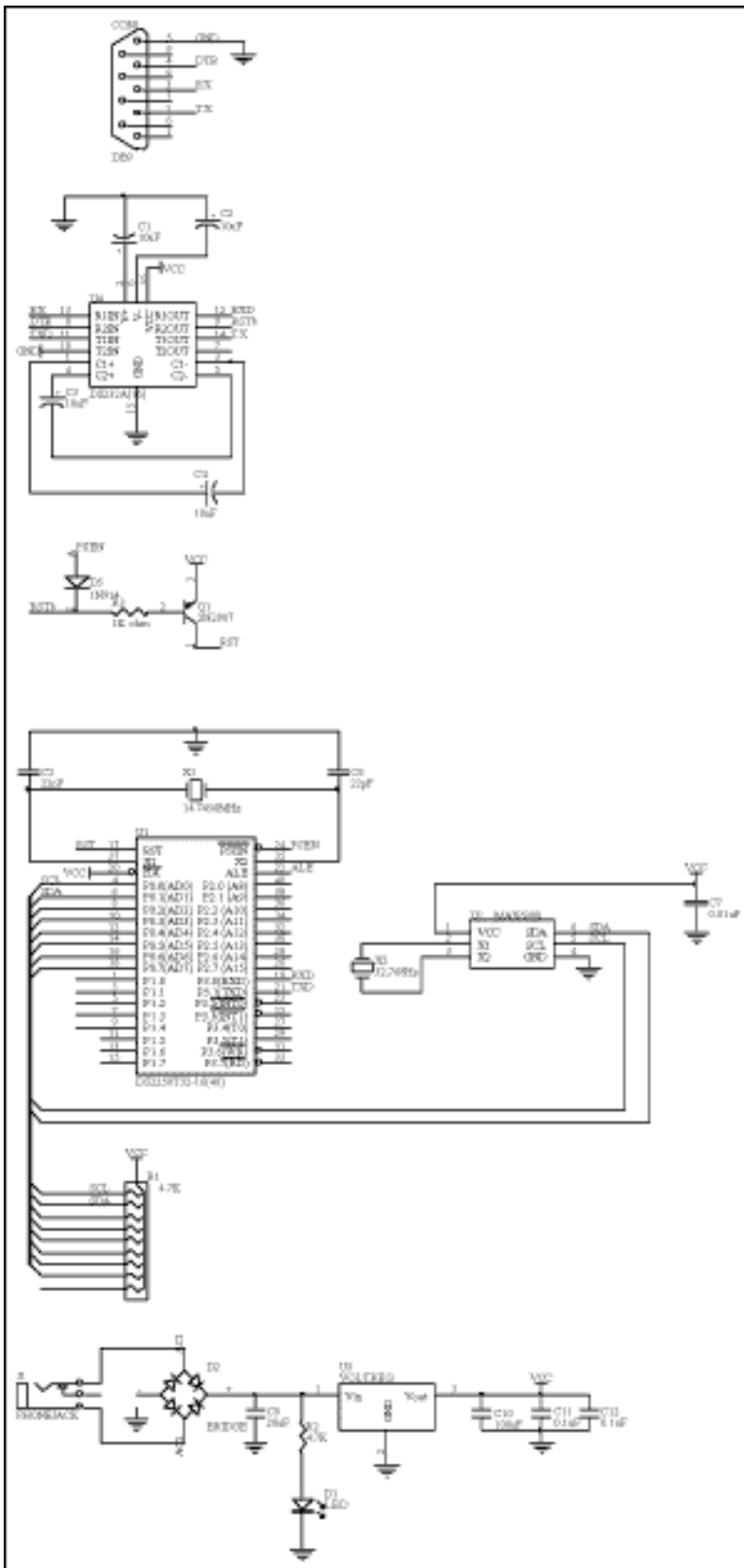
## Operation

The program uses two general-purpose port pins on the micro to operate as a master on the I<sup>2</sup>C bus. The MAX6900 operates as a slave device on the same bus.

A schematic of the circuit is shown in Figure 1. The software is shown in Figure 2.



[For Larger Image](#)

Figure 1. Schematic of Daughter Card

[Figure 2. Code Listing](#) (Download ZIP file)

## More Information

MAX6900: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)