

Reduced Termination Loss by Active Synthesis of Output Impedance

In high-speed transmission-line applications, it is important to match the output impedance of a line driver to the line. While this is achieved usually with a resistor, an active impedance synthesis has advantages. This application note describes how to use positive feedback around an op amp to create the desired output impedance. Equations and circuit examples are given for low-noise audio, and video op amps driving 50- to 600-ohm loads.

The Need for Termination

The output impedance of a circuit is important in transmission line-driving applications. The transmission line impedance, which is determined by the physical geometry of the conductors and insulation, must be matched at both the send and receive ends in order to minimize degrading signal reflections. When the characteristic impedance is not correctly matched at the drive and the receiver ends, not all of the signal energy is delivered to the load. Some energy is reflected back and will distort (or sometimes, almost cancel) the forward signal to the load.

RF engineers require accurate 50Ω terminations for their coaxial cables, video transmission engineers require accurate 75Ω terminations for their cables, and broadcast engineers require accurate 600Ω terminations for their audio circuits. Other standard termination values are 110Ω , 120Ω and 500Ω . The termination requirements are not confined to analog signals. Digital signals depend on correct line termination for accurate, high-speed transmission throughout a system.

Passive Resistive Termination

The usual method for achieving termination is to use a buffer amplifier with low output impedance, and add series resistance to the required value. This approach is simple, provided that the preceding buffer amplifier truly has a low output impedance across the band of interest.

A serious disadvantage of the simple resistor approach is, however, the 6dB loss of signal between the buffer output and the terminated load. This results in a serious loss of signal headroom, particularly in single supply systems.

Figure 1 shows a closed-loop buffer amplifier with a series resistance added outside the feedback loop to set the output impedance when measured looking back into the amplifier load terminal.

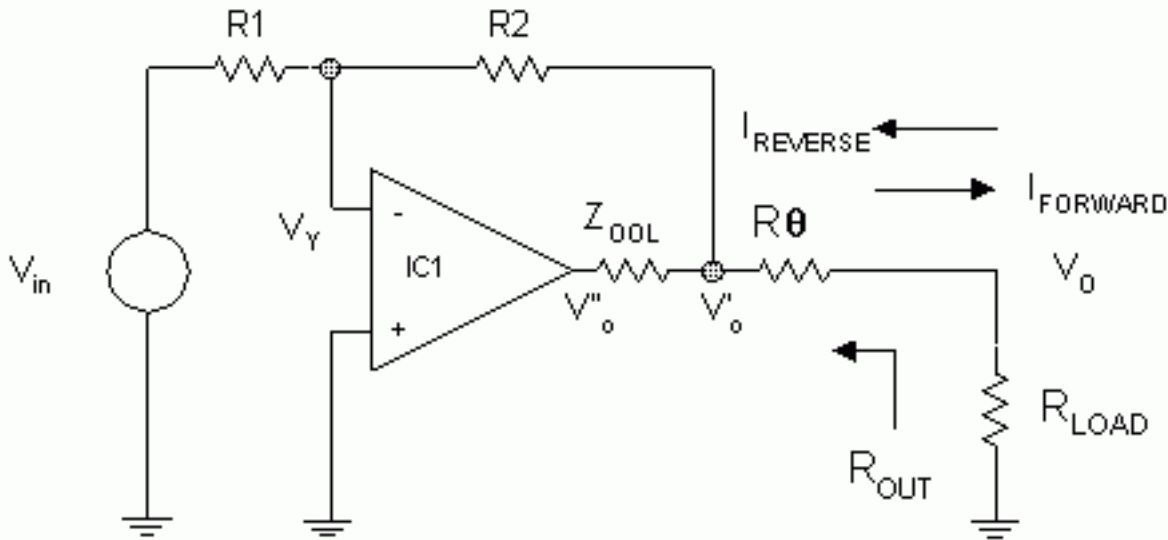


Figure 1. Simple Passive Termination.

Note in Figure 1 that forward current into the load, I_{FORWARD} , is determined by V_o/R_{LOAD} .

Synthesised output impedance, R_{OUT} , is determined by V_o/I_{REVERSE} , when V_{IN} is zero.

The understanding here is that the closed-loop output impedance of the op amp is low enough over a wide enough bandwidth to be ignored. Thus the chosen resistances set the output impedance. In Figure 1, R_{θ} is the series resistor that sets the impedance looking back into the output of IC1. $R_{\theta} = R_{\text{LOAD}} = R_{\text{OUT}}$ for correct back termination. The open-loop output resistance of the op amp is shown as R_{OOL} .

Voltage Gain is given by:

$$\frac{V_o}{V_{\text{IN}}} = -\frac{R2}{R1} \left(\frac{R_{\text{LOAD}}}{R_{\text{LOAD}} + R_{\theta}} \right) (1 + E_1)^{-1}$$

Error term is given by:

$$E_1 = \frac{1}{A_{\text{OP-AMP}}} \left(1 + \frac{R2}{R1} \right) \left(1 + \frac{R_{\text{OOL}}(R1 + R2 + R_{\theta} + R_{\text{LOAD}})}{(R1 + R2)(R_{\theta} + R_{\text{LOAD}})} \right)$$

Output Impedance is given by:

$$R_{\text{OUT}} = R_{\theta} + E_2$$

Error term is given by:

$$E_2 = \frac{R_{OOL}}{A_{OP-AMP}} \left(1 + \frac{R_2}{R_1}\right) \left(1 + \frac{1}{A_{OP-AMP}} \left(1 + \frac{R_2}{R_1} + \frac{R_{OOL}}{R_1}\right)\right)^{-1}$$

Errors due to finite open-loop gain (A_{OP-AMP}) of the op amp are shown.

Assuming infinite open-loop gain from an ideal op amp.

$$R_{OUT} = R\theta$$

Assuming infinite open-loop gain from an ideal op amp.

$$\frac{V_O}{V_{IN}} = -\frac{R_2}{R_1} \left(\frac{R_{LOAD}}{R_{LOAD} + R\theta}\right)$$

Figure 1 Advantage:

1. Simplicity. Select $R\theta$ to the required terminating value.
2. Modest short-circuit protection.
3. No interaction between R_1 - R_2 , and $R\theta$ to a first order.
4. Inverting and non-inverting gain operation allowed.

Fig 1 Disadvantages:

1. 6dB minimum loss between the amplifier output pin ($V'O$) and the load driving point (V_O) when $R\theta = R_{LOAD}$ (back terminated). Maximum output pk-pk voltage swing always less than half total power-supply voltage.
2. Doubled gain bandwidth required from the op amp.
3. Open-loop output resistance of the op amp affects results at high frequencies.

Active Synthesis of Output Impedance

Fortunately, a method exists to set output impedance and reduce the gain loss. The careful use of positive feedback around a voltage difference amplifier boosts a low-value output current-sensing resistor to the required final value.

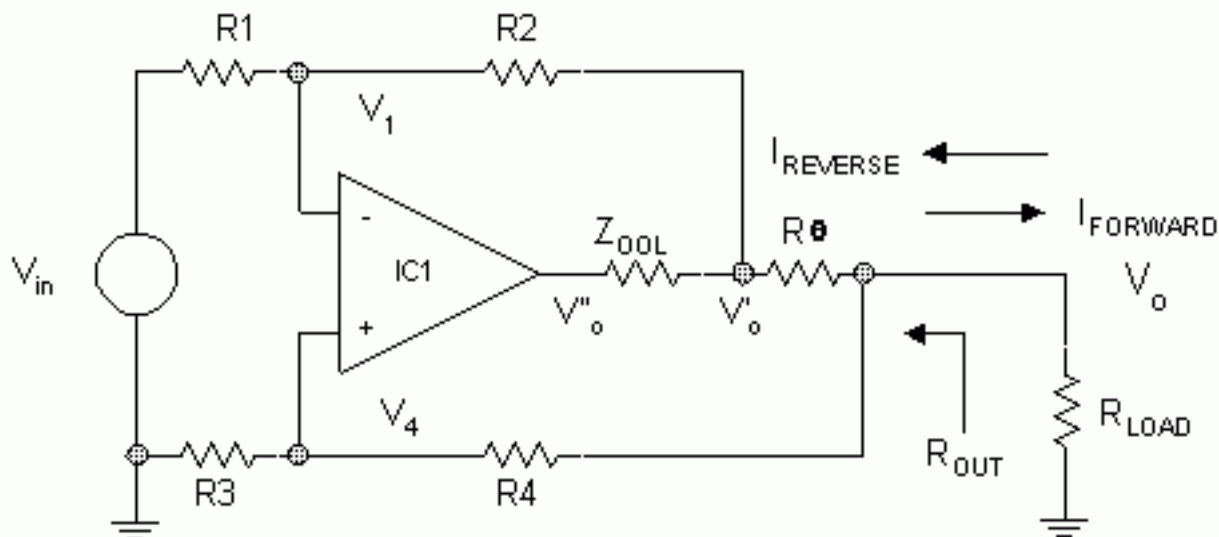


Figure 2. Single Op Amp Active Termination

Note in Figure 2 that forward current into the load, I_{FORWARD} , is determined by V_o / R_{LOAD} .

Synthesised output impedance R_{OUT} is determined by V_o / I_{REVERSE} , when V_{IN} is zero.

Figure 2 shows a single op amp with both negative and positive feedback loops setting gain and output impedance. R_{θ} is placed in series with the load, and is used to sample the current into the load. Positive feedback through R_3 and R_4 is used to boost the effect of R_{θ} . For circuit stability, negative feedback must dominate the proceedings, and this fact limits the amount of boost available.

The open-loop output resistance of the op amp is included to allow for the situation when R_{OOL} becomes close in value to R_{θ} at high frequencies as the loop gain rolls off.

Voltage Gain for Figure 2 is given by:

$$\frac{V_o}{V_{\text{IN}}} = - \frac{\frac{R_2}{R_1} (1 + E_3)^{-1}}{1 - \left(1 + \frac{R_2}{R_1}\right) \left(1 + \frac{R_4}{R_3}\right)^{-1} (1 + E_3)^{-1} + \frac{R_{\theta}}{R_3 + R_4} \left(1 + \frac{R_3 + R_4}{R_{\text{LOAD}}}\right)}$$

Error term is given by:

$$E_3 = \frac{1}{A_{OP-AMP}} \left(1 + \frac{R_2}{R_1} \right) \left(1 + \frac{R_{OOL}}{(R_1 + R_2)} \left(1 + \frac{(R_1 + R_2)}{R_{\theta} + \frac{R_{LOAD}(R_3 + R_4)}{R_{LOAD} + R_3 + R_4}} \right) \right)$$

Output Impedance for Figure 2 is given by:

$$R_{OUT} = \frac{R_{\theta}}{1 - \left(1 + \frac{R_2}{R_1} \right) \left(1 + \frac{R_4}{R_3} \right)^{-1} (1 + E_3)^{-1} + \left(\frac{R_{\theta}}{R_3 + R_4} \right)}$$

Errors due to finite open-loop gain of the op amp are shown.

Note that the overall input-to-output signal path in Figure 2 is inverting.

Assuming infinite open-loop gain from an ideal op amp, output impedance is:

$$R_{OUT} = \frac{R_{\theta}}{1 - \left(1 + \frac{R_2}{R_1} \right) \left(1 + \frac{R_4}{R_3} \right)^{-1} + \left(\frac{R_{\theta}}{R_3 + R_4} \right)}$$

Generally, the term $[R_{\theta} / [R_3 + R_4]]$ is $\ll [1 + R_2/R_1][1 + R_4/R_3]^{-1}$, so may be ignored.

$$R_{OUT} = \frac{R_{\theta}}{1 - \left(1 + \frac{R_2}{R_1} \right) \left(1 + \frac{R_4}{R_3} \right)^{-1}}$$

Assuming infinite open-loop gain from an ideal op amp, voltage gain is:

$$\frac{V_o}{V_{IN}} = - \frac{\frac{R_2}{R_1}}{1 - \left(1 + \frac{R_2}{R_1} \right) \left(1 + \frac{R_4}{R_3} \right)^{-1} + \frac{R_{\theta}}{R_3 + R_4} \left(1 + \frac{R_3 + R_4}{R_{LOAD}} \right)}$$

Rearranging the output impedance into the gain equation:

$$\frac{V_o}{V_{IN}} = - \frac{\frac{R2}{R1}}{\frac{R\theta}{R_{OUT}} + \frac{R\theta}{R3 + R4} + \frac{R\theta}{R_{LOAD}}}$$

In general, $R_{LOAD} = R_{OUT}$ for reverse-termination applications. Thus:

$$\frac{V_o}{V_{IN}} = - \frac{\frac{R2}{R1}}{\frac{2R\theta}{R_{LOAD}} + \frac{R\theta}{R3 + R4}}$$

Fig 2 Advantages:

1. Significantly reduced loss between the amplifier output pin ($V'O$) and the load driving point (V_O). If $R\theta = 0.1R_{LOAD}$, loss is only 0.83dB. In other words, a significantly increased pk-pk output voltage swing for a given power supply, compared to the passive termination case.
2. Modest, short-circuit protection at main output.
3. Easy to use.

Fig 2 Disadvantages:

1. Positive and negative feedback coexist. Negative feedback must dominate at all times for stability.
2. Interaction between R1-R4. Suitable for fixed-gain and termination conditions only.
3. Inverting only practical operation.
4. Positive feedback will tend to produce an increase in distortion performance over the purely negative feedback case.

Measurement of Output Impedance

There are some simple ways to measure the impedance modulus looking back into the output terminals of the circuit. The measurement of the output impedance of the circuit under test is shown in Figure 3. The input to the circuit under test is grounded.

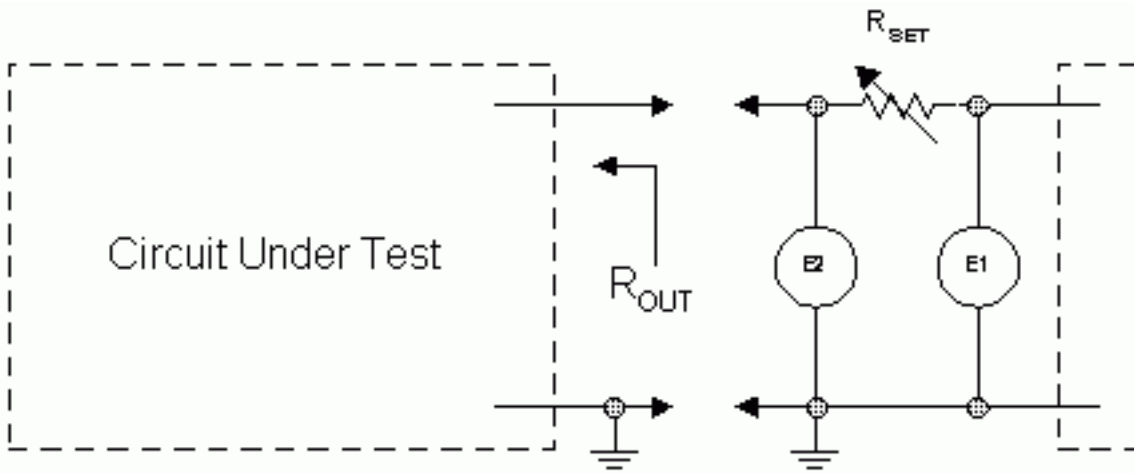


Figure 3. Measure Output Impedance

Perhaps the obvious approach in Figure 3a is to set the value of R_{SET} at a particular frequency, so that $|E2|$ is $\frac{1}{2}|E1|$. The value shown on R_{SET} is equal to Z_{OUT} of the circuit under test. This is only true if Z_{OUT} is purely resistive at the test frequency. Any reactive component will introduce large errors into this so called "6dB" method.

A more accurate approach is to adjust R_{SET} for $|E2|$ 20dB less than $|E1|$. Then:

$$|R_{OUT}| = R_{SET} / 9$$

Practically, R_{SET} may be fixed at a value 10x the nominal impedance to be measured. The ratio of $E1$ and $E2$ then leads to the value of " Z_{OUT} ."

If the ratio is made 40dB:

$$|R_{OUT}| \text{ is given by } R_{SET} / 99$$

Care needs to be exercised when using the 40dB ratio, as the source voltage could be greater than the breakdown of the circuit under test. This is relevant when low-voltage op amps are under consideration.

A second method is to use a suitable network analyser.

A third method, specific to active impedance boosting techniques, is to measure the voltage and phase directly across the current-sense resistor R_{Ω} . From the voltage difference, the synthesised output impedance is given by:

Referring to Figure 2.

$$R_{OUT(MEASURED)} = R_{\theta} \times \left(\frac{1}{1 - \frac{V_{O'}}{V_O}} \right)$$

Referring to Figure 2, and taking into account the effect of R3 and R4 in parallel with the output.

$$R_{OUT(MEASURED)} = R_{OUT} \times \left(\frac{R3 + R4}{R_{OUT} + R3 + R4} \right)$$

The incident or input drive voltage from the test source is V_O (in Figure 2), and the reflected voltage from the op amp output is $V_{O'}$ (in Figure 2). A vector voltmeter can be used to extract both amplitude and phase difference. The ratio $V_{O'} / V_O$ is further modified by $\cos \phi$. The big drawback of this method is the need to identify small voltage differences across R_{θ} in the presence of relatively large signal levels.

Design

The circuit shown in Figure 2 is chosen when a specified output resistance is required for a very low loss between amplifier and final output. R_{LOAD} and R_{OUT} are both known quantities. R_{θ} is chosen to be as small as possible, commensurate with overall circuit stability.

By how much should R_{θ} be "boosted"? A practical upper limit is x10 (ie $R_{\theta} = 0.1 R_{LOAD}$). This will produce a termination loss of 0.83dB. A thorough analysis of each situation should be performed, but some of the variables, such as open-loop output resistance, are difficult to confirm from data sheet specifications. The higher the boost, the more positive feedback is applied, giving rise to reduced phase margins and increased closed-loop distortion. The final choice of "boost" will be a delicate compromise between termination loss and other closed-loop parameters. The operational amplifiers should be chosen to have unity-gain stability.

Ensure that the time constant of the negative feedback loop dominates the overall loop control. This means that the positive feedback loop ideally should roll off before the negative feedback loop. Referring to Figure 2, the first-order time constant (TC) of the negative feedback loop is:

$$TC(-) = C_{COM} (R1 \parallel R2)$$

The time constant of the positive feedback loop is:

$$TC(+) = C_{COM} (R3 \parallel R4)$$

C_{COM} = Common mode capacitance at + and - inputs of the op-amp. Set $TC(-) < TC(+)$.

This assumes that the capacitance at the op-amp inputs is greater than the parasitic capacitance of the feedback loop resistors. In wideband situations it is appropriate to split each of R1-R4 into two equal value resistors to effectively halve the parasitic capacitance.

If the circuit does not actually oscillate, there may be in-band response peaking. This can be checked by sweeping the circuit with a small signal (50mV to 100mV) sine wave to identify and plot the closed-loop frequency response (with load), and by correcting any in-band peaking by adjusting the feedback time constants.

Example 1

600 Ω single ended audio cable active termination.

Power supply = +5V

Gain = 1 (0dB)

$R_{OUT} = R_{LOAD} = 600\Omega$.

Chose termination loss = 1dB.

The MAX4475 op-amp is chosen for its excellent distortion characteristics, bandwidth, and output drive capability. It is also unity-gain stable.

$$\left| \frac{R2}{R1} \right| = \frac{2R\theta}{R_{LOAD}} + \frac{R\theta}{R3 + R4}$$

$R_{OUT} = R_{LOAD}$, and Gain = 1.

$$R_{OUT} = \frac{R\theta}{1 - \left(1 + \frac{R2}{R1}\right) \left(1 + \frac{R4}{R3}\right)^{-1} + \left(\frac{R\theta}{R3 + R4}\right)}$$

$R_{LOAD} = 600R$ for test purposes, and $R\theta = 75R$ as nearest preferred value. $R\theta = 0.125 R_{LOAD}$.

$R2 = 0.25R1$

Let $R1 = 10k$, then $R2 = 2.5k$. Use $R2 = 2.4k + 100R$. Then:

$$\left(1 + \frac{R2}{R1}\right) \left(1 + \frac{R4}{R3}\right)^{-1} = 0.875$$

given that R_{θ} , and $R_{LOAD} = R_{OUT}$ as shown above.

This ratio provides the boost to R_{θ} .

$$R_4 = 0.428R_3.$$

Let $R_3 = 10k$. Then $R_4 = 4.28k$. Use $R_4 = 4.3k$.

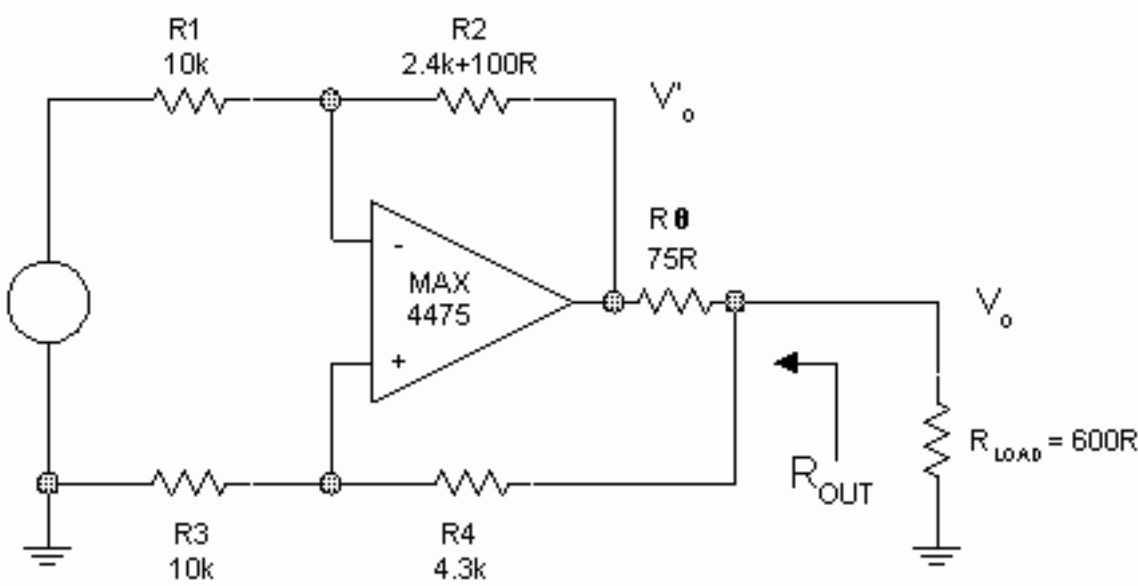


Figure 4. Example 1 (Power supply decoupling not shown for clarity.)

Table 1. Gain vs. Frequency [0dB = 137.5mV_{RMS}]

| Frequency (kHz) | Gain (dB) | Phase (Deg) |
|-----------------|-----------|-------------|
| 100 | -0.3 | 5.6 |
| 220 | -0.5 | 14 |
| 430 | -1.0 | 23 |
| 580 | -1.5 | 29 |
| 710 | -2.0 | 33 |
| 830 | -2.5 | 37 |
| 940 | -3.0 | 39 |
| 1050 | -3.5 | 47 |
| 1170 | -4.0 | 52 |
| 1370 | -5.0 | 62 |

Table 2. Voltage Difference Across $R_{SET}=6.2k\Omega$ (Fig3) 0dB = 486mV_{RMS}

| Frequency (kHz) | dB (across 6.2k Ω) | R _{OUT} (Ω) |
|-----------------|----------------------------|-------------------------------|
| 100 | -21.5 | 517 |
| 220 | -21.8 | 502 |
| 430 | -22.4 | 468 |
| 580 | -23.2 | 429 |
| 710 | -24 | 392 |
| 830 | -24.6 | 364 |
| 940 | -25.2 | 340 |
| 1050 | -26 | 313 |
| 1170 | -26.6 | 287 |
| 1370 | -28 | 249 |

Calculated gain = -0.18dB with values shown above.

Calculated output impedance = 572 Ω . This value is determined by R3+R4 || R_{OUT} reducing the calculated value.

Example 2

50 Ω single-ended active terminated broadband cable driver.

Power supply = +5V.

Gain = 1 (0dB).

R_{OUT} = R_{LOAD} = 50 Ω .

Chose termination loss = 1dB.

The MAX4265 op amp is chosen for its excellent distortion characteristics, bandwidth, and output drive capability. It is also unity-gain stable.

For 1dB termination loss.

$$R_{\theta} = 0.122 R_{LOAD}$$

R_{LOAD} = 50R for test purposes, and R θ = 6.8R as nearest preferred value. R θ = 0.136 R_{LOAD}.

$$R_2 = 0.272 R_1.$$

Let R1=1k. Then R2=272R. Use R2=270R as nearest preferred value. Then:

$$\left(1 + \frac{R_2}{R_1}\right) \left(1 + \frac{R_4}{R_3}\right)^{-1} = 0.864$$

when R_{θ} and $R_{LOAD} = R_{OUT}$ as shown above.

This ratio provides the boost to R_{θ} .

$$R_4 = 0.472R_3.$$

Let $R_3 = 1k$. Then $R_4 = 472R$. Use $R_4 = 470R$ as nearest preferred.

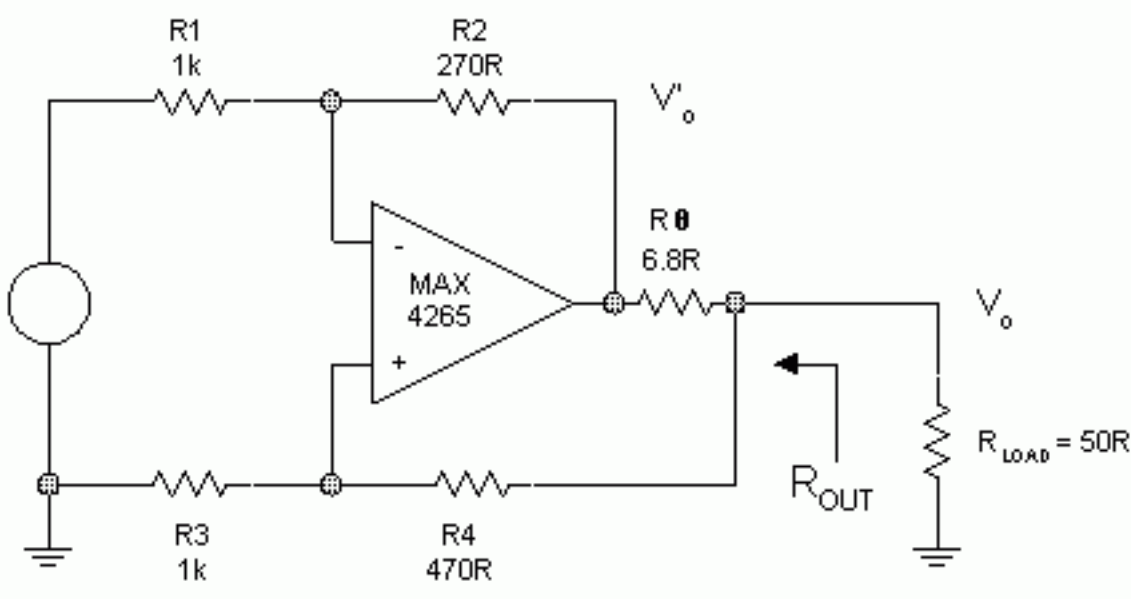


Figure 4. Example 2 (Power supply decoupling omitted for clarity.)

Table 3. Gain vs. Frequency 0dB = 70mV_{RMS}

| Frequency (MHz) | Gain (dB) | Phase (Deg) |
|-----------------|-----------|-------------|
| 1.0 | -0.3 | 0 |
| 2.0 | -0.3 | -3.5 |
| 4.0 | -0.4 | -10.25 |
| 6.0 | -0.7 | -16.5 |
| 8.0 | -1.0 | -23.5 |
| 10.0 | -1.3 | -30 |
| 15.0 | -2.3 | -44 |
| 20.0 | -3.5 | -58 |
| 30.0 | -7.0 | 87 |

Table 4. Voltage Difference Across $R_{SET} = 510R$ (Fig3) 0dB = 225mV_{RMS}

| Frequency (MHz) | dB Across 510 Ω | Phase (Deg) | R_{OUT} (Ω) |
|-----------------|------------------------|-------------|------------------------|
|-----------------|------------------------|-------------|------------------------|

| | | | |
|-----|-------|-------|-------|
| 1.0 | -21 | -3.2 | 45.4 |
| 2.0 | -21 | -4.4 | 45.4 |
| 4.0 | -21 | -7.25 | 45.4 |
| 8.0 | -21.8 | -14.5 | 41.45 |
| 10 | -22.1 | -15.5 | 40 |
| 20 | -23.7 | -21 | 33.3 |

Calculated Gain = -0.63dB with values shown above, and taking into account additional 50W source resistance not included in R1.

Calculated Output Impedance = 45.5Ω. This value is determined by $R3+R4 \parallel R_{OUT}$ reducing the calculated value.

Conclusion

The careful application of positive feedback around a conventional voltage difference operational amplifier may be used to synthesise an output impedance higher than the usual value obtained from the application of negative feedback. This is useful in single-supply amplifier applications where the driving amplifier must drive the load from a known source impedance. A termination "gain" of some 5dB may be achieved compared to normal passive termination.

Expressions have been developed to help gain an insight into the effects of open-loop gain and output impedance on the final closed-loop performance. Examples of the circuits have been built and demonstrate the ease of use of the circuits given.

More Information

MAX4265: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

MAX4475: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)