

APPLICATION NOTE 518: Boost Converter Yields Orderly Shutdown

Some microprocessor (μ P) systems require more time for shutdown than is provided by conventional circuits for power-fail detection. Between first warning and the actual loss of power, such systems have extensive "housekeeping" tasks to perform in addition to the memory-write operations that save critical data.

A backup battery and dc-dc regulator can buy extra time for the μ P by maintaining VCC at 5V following the initial warning of impending power loss (**Figure 1**). When VCC falls below 4.65V, μ P supervisor IC1 issues a logic-low signal at pin 7. This signal applies a non-maskable interrupt (NMI) to the μ P, and (via Q2) turns off Q1 and pulls IC2 out of shutdown.

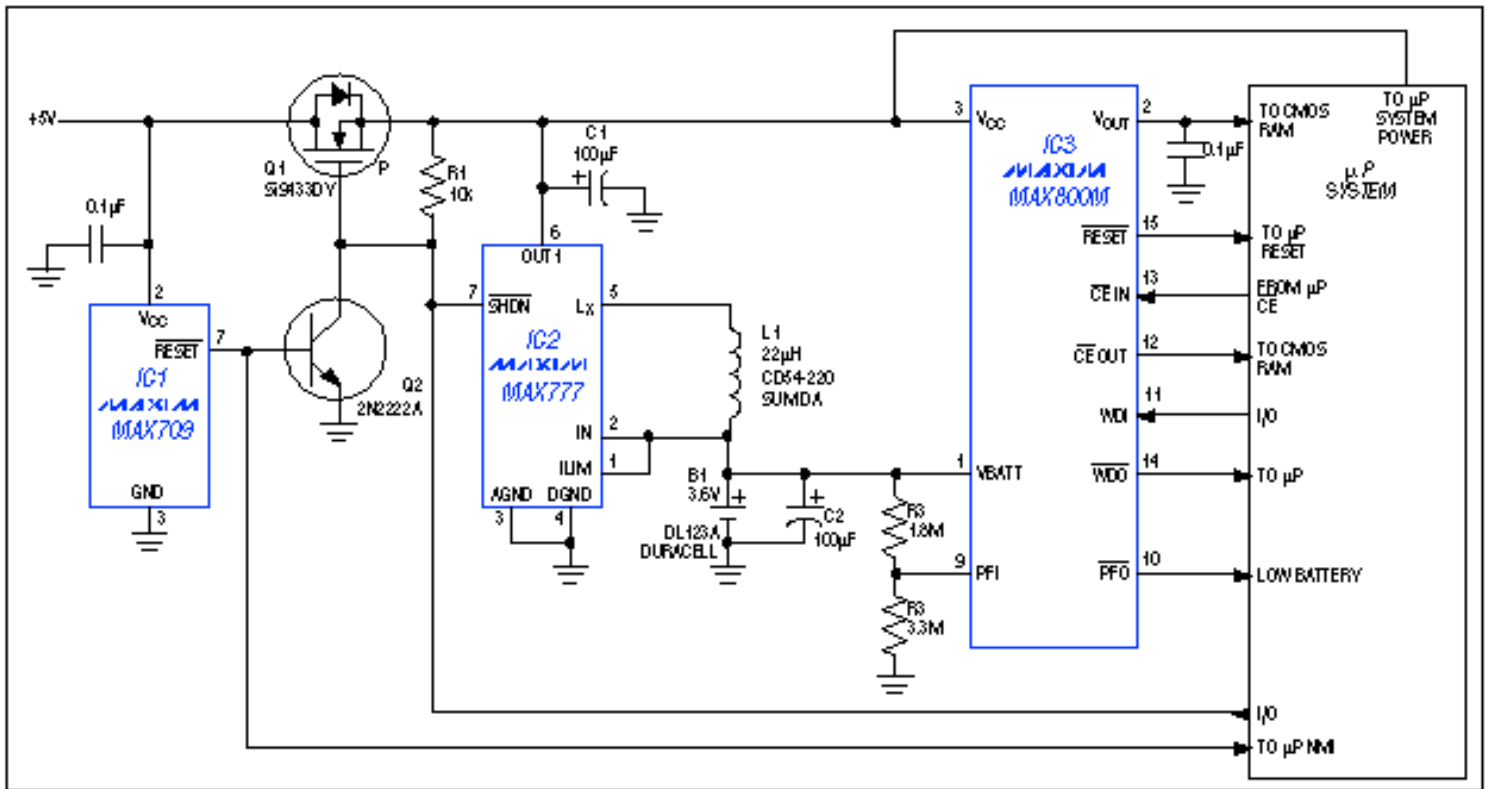


Figure 1. During the brief interval between a low-VCC warning and power fail, this system's boost converter (IC2) derives 5V from the backup battery, giving the μ P time to complete its shutdown routine.

As the μ P shutdown routine begins, IC2 quickly restores the VCC line to 5V, which supplies as much as 200mA from a 2.5V lithium cell. When the routine ends, the μ P shuts down IC2 via an I/O line, allowing a second decline in VCC. At 4.4V, the μ P supervisor IC3 enters its normal battery-backup mode. If desired, you can connect separate batteries for the boost converter and for RAM backup.

More Information

MAX800M: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)