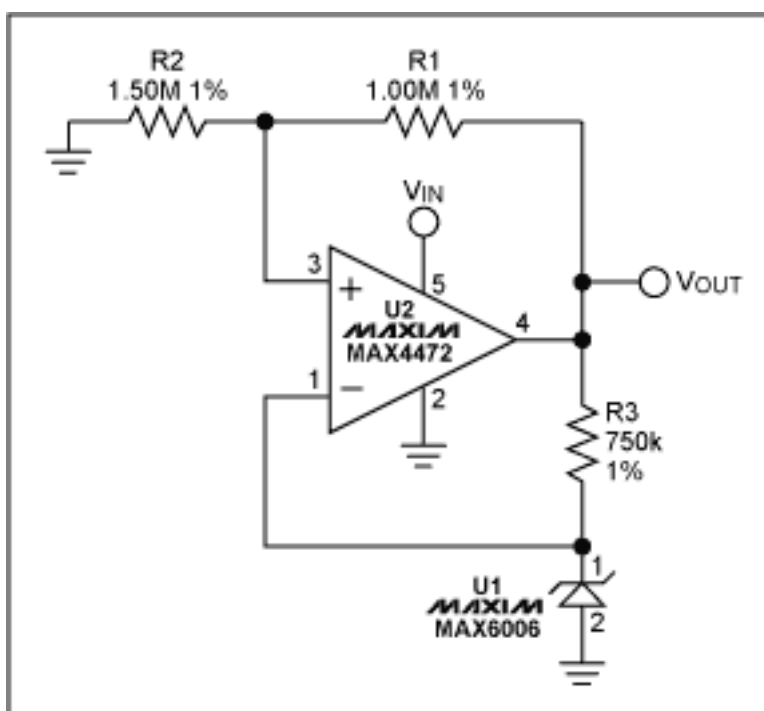


## Low-Voltage Series Reference Draws Only 2.4μA

*Using a shunt reference and op amp, a low power, low-voltage series reference can be designed. The circuit consumes very low power (2.4μA) and offers excellent line regulation (90dB) and load regulation (0.1V/A). This circuit provides excellent performance compared to many series references currently available.*

In systems with miniscule power budgets, implementing a low-power voltage reference involves many compromises. One option is the low-voltage shunt reference. Available since the birth of the bandgap cell, this device traditionally operates with less current than does a series reference. The shunt reference offers flexibility in its bias and application, but can sink or source only modest currents. The series reference improves the sink/source capability, but incurs a 10X increase in supply current.

Combining the low power consumption of a shunt reference with series-reference performance yields an ultra-low-power series reference with excellent line and load regulation (Figure 1). The heart of this circuit is the 1μA, +1.25V shunt reference U1. Bias current for this shunt reference comes directly from the amplified reference voltage, virtually eliminating line-regulation error. Because the op amp (U2) supplies the load current, load regulation is much better than that of resistively biased bandgap references.



*Figure 1. A shunt reference (U1) in this series-reference circuit yields a composite circuit with the advantages of both shunt and series references.*

The most important attribute of the op amp and the shunt reference is low supply current. Total supply current for the devices shown (U1 and U2) is 2.4 $\mu$ A, which includes the current in the feedback network. This network sets the output to +2.0V, but is easily adjusted for other voltages.

The circuit sinks and sources current quite well. Line regulation is 90dB from  $V_{IN} = 2.2V$  to 5.5V, and load regulation (with  $V_{IN} = 2.5V$ ) is 1 $\mu$ V per 10 $\mu$ A of output current. The total supply current is 2.4 $\mu$ A, independent of the supply voltage. This performance vastly exceeds that of series references currently available, whose minimum supply currents are 10 $\mu$ A and above.

A similar version of this article appeared in the August 20, 2001 issue of *Electronic Design* magazine.

DI398, November 2001

### **More Information**

MAX4472: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)