

Flyback Circuit Powers Broadband Phone Networks

With the advent of broadband access, many companies have developed high voltage SLICs (subscriber line interface card) which control the ringing and voice transmission on phone systems. The SLICs essentially perform two functions. One is ringing the phone at the customer's premises. Another is generating loop current for off-hook operation. Power supplies for SLICs have special requirements.

Multiple Line, Multiple Phone Applications Power Requirements

The equivalent circuit for a US ringer, at the ringer frequency of about 20Hz, essentially presents a resistive load of $8k\Omega$ per phone. The number of parallel phones on a line is called the ringer equivalent number (REN). The North American ringing load requirement of five REN is among the world's most stringent. Ringing a phone requires a minimum phone ring voltage of $45V_{RMS}$ ($40V_{RMS}$ at the handset). The phone ringing voltage can be either trapezoidal or sinusoidal. The sinusoidal waveform places more stringent demands on the power supply. A sine wave with a $45V_{RMS}$ requirement needs a peak voltage of $64V$ (negative). Peak power supply current for one phone is $64/8k = 8mA$. The power supply must put out a few additional volts above the $64V$ peak for protection resistors voltage drop and SLIC output amplifier overhead. However, line resistances can add to the total required voltage. The phone lines are generally longer for a central-office (CO) application as compared to a typical DSL or cable-modem customer. In the application considered here (for Legerity Inc. using AMD79R79 SLIC) this voltage requirement is $-90V$.

Many applications power multiple lines. Phones may ring sequentially to reduce peak power or some overlap may be allowed which then dictates the power requirements. Peak current requirements for a $REN=5$ application is $40mA$. The AMD79R79 SLIC, developed by Legerity Inc., sets this requirement to $56mA$ (to account for various tolerances in the SLIC circuit). In an application using four lines and allowing for overlap in two of four lines, peak current requirements are $112mA$. Any line-card ringing implementation requires the removal of the ring signal from the subscriber line within a specified time after the subscriber goes off-hook. This prevents the ring signal from causing discomfort to the subscriber. In order to detect this status a DC current path is established between ground and the supply for a specified time (150 msec. for the AMD79R79 SLIC). The SLIC device senses the DC current for ring trip, resulting in the removal of the ring signal. Applications using AMD79R79 typically set the value of this DC current at about 40% higher than the load presented by the phone (both values can be set independently in AMD79R79). This sets the DC ring trip current at $100mA$ for a $REN=5$ application. If the application also uses four lines with overlap of two out of four lines, then the ring trip current presents an additional load of $200mA$ for $150msec$. Therefore, the power supply should be designed for a maximum load of at least $312mA$ at $-90V$ output.

Besides ringing the phone, the power supply must power the voice transmission and reception. In many cases, once voice transmission begins the SLIC requires a lower input voltage of about -24V to establish a 20 to 25mA loop. In a single line, single phone application, designs combine the lower and higher supply voltage and operate the SLIC at a compromise voltage of about -53V. For a multiple line application the ringer and talk portions can be powered by the same supply. A typical load for the 20mA loop is 200Ω to 500Ω. This implies 4V to 12V drops across the load and the remainder across the SLIC. A more efficient way is to use two different supplies for the ringer and the voice transmission, as in the application being considered. For multi-line operation, if one line is off-hook in the talk-state, it is operating on the lower supply voltage and cannot be ringing. The power for the talk-state will then see a maximum load of about 100mA.

These applications use wall-mounted DC supplies that produce 10V to 25V, but generally supply the required 12V. Table 1 below summarizes this discussion about power requirements for an AMD79R79 application using four lines with overlap of two out of four lines.

Table 1: Power Supply Requirements for AMD79R79 Four-Line Application

Parameter	Requirement
Input Voltage	12V ±10%
Output Power	3 to 30W (12W typical)
Output Voltage	-90V/-30V
-30V requirements (Overlap for two of four lines)	Regulation ±4V (±13%) Maximum Output Current 150mA Ripple 50mV p-p
-90V requirements (Overlap for two of four lines)	Regulation ±6V (±6%) Maximum Output Current 320mA Ripple 50mV p-p

Flyback Power Supply with MAX1856

A multi-tapped inductor and a PFET can be used to generate the two required voltages from a positive input. The P-channel devices typically have higher on-resistance when compared to N-channel devices. The voltage stress on the PFET will be very high in the multi-tapped inductor topology. A multi-winding flyback topology using a NFET yields higher power and better efficiency. The stress on the NFET is also much less as the turns ration reduces the reflected output voltage as compared to the full output voltage appearing at the PFET in the tapped inductor topology.

For the multi-winding flyback topology the MAX1856 controller is used to regulate the output voltage (Figure 1). The MAX1856 operates in a current control mode. An internal op-amp inverts the sensed negative output voltage without needing any external active components. A resistor between the MAX1856 reference voltage and the feedback pin, which is internally

referenced to ground, sets the current in the resistive output voltage divider. An external resistor at the **FREQ** pin determines the switching frequency. The highest possible frequency of 500kHz is chosen to deliver the maximum output power of 30W specified for this application.

Continuous conduction mode needs a larger primary inductance and a larger size transformer. But, it improves efficiency and reduces peak current values, thereby reducing turn-off losses in the NFET. This, however, does not imply that either the primary or secondary current flows continuously. In flyback power supplies continuous mode refers to the magnetic field continuity in the transformer core over one complete switching cycle. The circuit in Figure 1 is designed to operate in the continuous conduction mode.

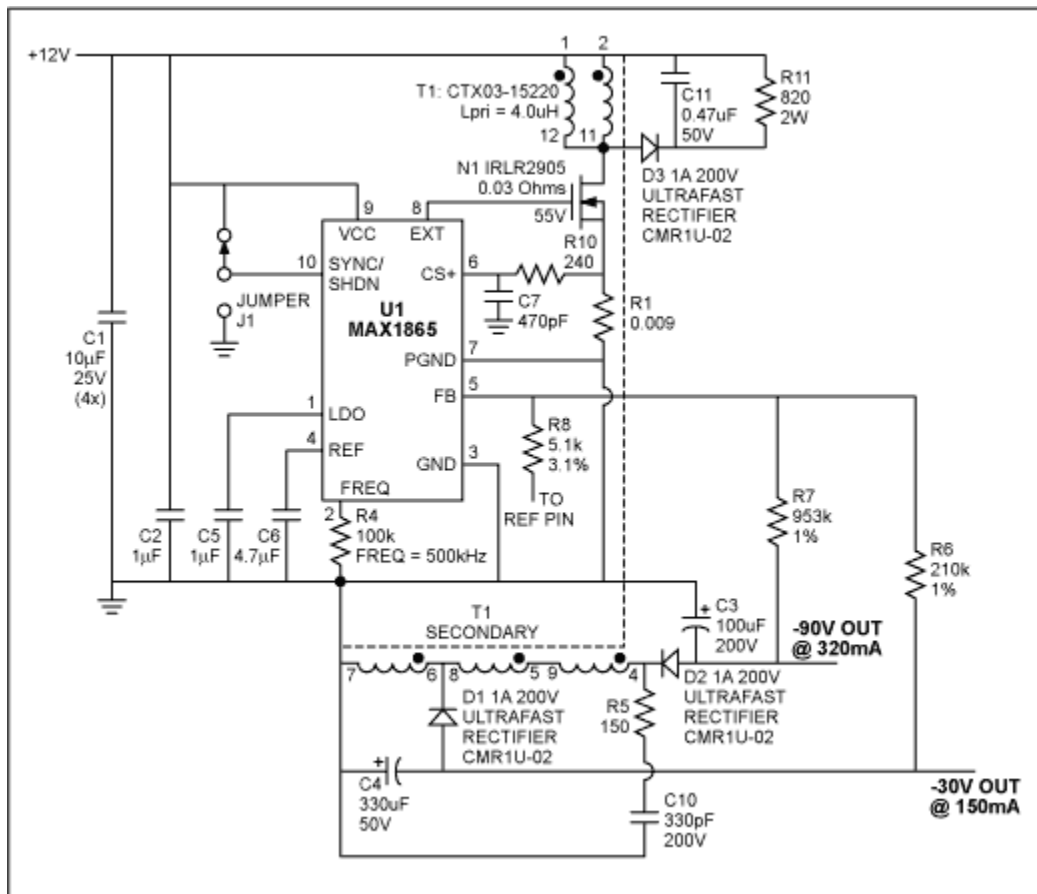


Figure 1. Power supply for AMD79R79 SLIC

The input voltage is applied to the primary of the transformer, T1. An external MOSFET switch drives the other side of the primary transformer. The MAX1856 turns on the MOSFET to effectively apply the input voltage across the primary of transformer T1. The "dot" end of the primary is more positive than the "no-dot" end. Primary current increases linearly with a rate of change directly proportional to the input voltage and inversely proportional to the primary inductance. The switch stays on for a time period determined by the duty cycle and switching

frequency. The duty cycle is determined by the transformer turns ratio, input voltage and output voltage. Peak primary current, I_P , is the final value of the primary current before the switch turns off. Energy proportional to the square of the peak current is stored by the magnetic field in the transformer.

The secondary winding carries a reflected voltage proportional to primary voltage by turns ratio with the same "dot" polarity. While the MOSFET switch is on the diodes D1 and D2 are reverse biased, which prevents secondary current flow. When the switch turns off, the decreasing magnetic field induces an abrupt voltage reversal in the transformer windings such that the "no-dot" side is now at higher potential than the "dot" side. Diodes D1 and D2 become forward biased and secondary current rises quickly to its peak value (proportional to peak primary current I_P by inverse turns ratio). Primary current immediately drops to zero. Secondary current now decreases linearly at a rate directly proportional to the output voltage and inversely proportional to the secondary inductance.

The MOSFET drain voltage quickly rises to the sum of the input voltage and the reflected output voltage. The selected MOSFET has a breakdown voltage greater than this. The primary leakage inductance, L_{LP} , of the transformer resonates with the output capacitance, C_{OSS} , of the MOSFET and the primary transformer capacitance, C_P , during MOSFET turn-off. This results in a voltage overshoot during turn-off proportional to the parasitic impedance of this resonant circuit. The voltage overshoot adds to the voltage seen across the MOSFET during turn-off. An RCD snubber is used to clamp the voltage to be less than the breakdown voltage of the MOSFET. The switch turns on at the beginning of the next cycle and the secondary current drops to zero abruptly. The stored energy is not completely delivered to the load. Energy remains in the core and causes an initial step in the primary current waveform when the switch turns on (Figure 2). The diodes D1 and D2 are reverse biased and turn off. The secondary leakage inductance of the transformer resonates with the self-capacitance of the secondary rectifiers during this turn off. An RC snubber is used at the cathode of rectifier D2 to damp the ringing. Only one snubber is required on the higher voltage output. The initial turn-off spike is still present and reflected in the primary as seen in the current waveform in Figure 2.

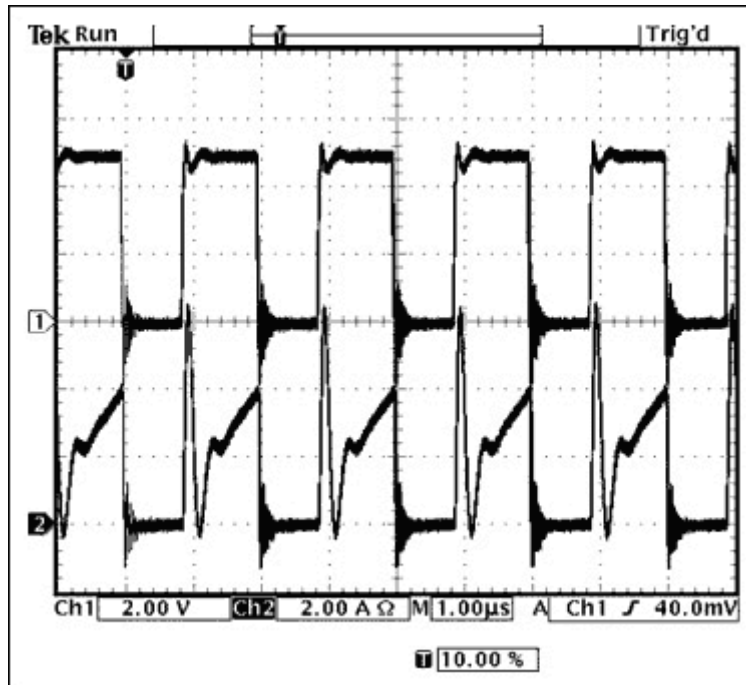


Figure 2. Primary current in flyback (CH1= Voltage @ EXT; CH2=Primary Current)

The MAX1856 can drive a wide variety of logic-level N-channel MOSFETs. Key parameters considered for MOSFET selection include the gate charge, reverse transfer capacitance, breakdown voltage, on-resistance and threshold voltage. The required values of these parameters are dictated by the gate drive capability of MAX1856 and efficiency requirements of the circuit. The general design procedure for selecting a MOSFET and other circuit components is explained in greater detail in the MAX1856 data sheet.

One of the most important factors in the flyback supply design is the transformer. The MAX1856 works with economical off-the-shelf transformers. The AMD79R79 SLIC power supply uses the transformer CTX03-15220 from Cooper Electronics with a primary inductance of 4 μ H. A split feed back technique (Figure 1) and tight coupling in the transformer windings improves cross-regulation. This feature is extremely important in this application due to the wide range of current loads possible on both outputs. The talk battery supply (-30V) can deliver 8mA (when all phones are idle) and as much as 150mA. The ringer supply (-90V) can deliver currents of 1 to 320mA. The typical output power required in this application is 12W (Table 1). However, during a ring trip condition the supply can safely deliver 30W required. Figure 3 shows the excellent cross-regulation achieved by this circuit for the ringer supply (-90V). The talk battery supply (-30V) changed by less than 100mV (for nominal input voltage of 12V) under all load conditions. The output ripple was 20mV on both outputs. This shows the circuit performs very well within the specifications of Table 1.

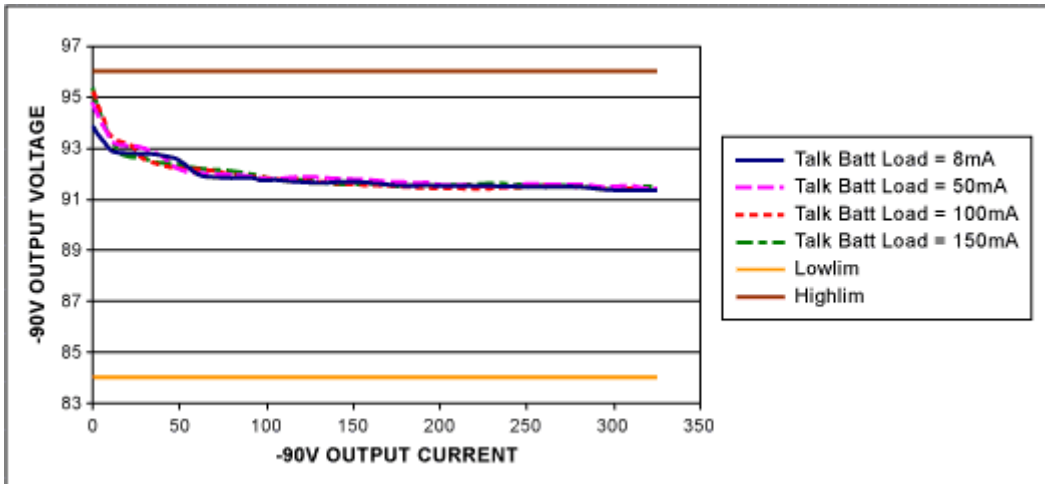


Figure 3. Flyback power supply meets regulation requirements

MORE INFORMATION

MAX1856: [QuickView](#) -- [Full \(PDF\) Data Sheet \(608k\)](#) -- [Free Sample](#)