

Interfacing the PDSP Family Application Brief

AB16 - 3.0 June 1996

INTRODUCTION

Mitel Semiconductor's PDSP family of DSP functional blocks are fabricated on a high speed CMOS process, and incorporate several design features to ease interfacing and board layout. However there are a few precautions which should be taken which will ensure trouble-free board design and operation.

All parts in the PDSP family are designed with the generic structure of Fig.1.

 


Fig.1 PDSP structure

The registered input is designed with a positive set-up time (ie data must be presented before the rising edge of the clock) and zero hold time (ie the data is allowed to change anytime after the rising edge of the clock). The input levels are designed for compatability with LSTTL outputs ($V_{IH} = 2.2V$, $V_{IL} = 0.8 V$), and the output, although conventional CMOS stages, are specified into a load of 2 standard LSTTL inputs + 20pF for track loading.

All PDSP devices have tri-state output buffers preceded by an output register, this ensures that the output data is valid for a whole clock cycle. To simplify timing requirements further, the clock to output valid delay is generally less than half a cycle at the maximum specified clock rate.

AB16

NOISE

The operating margins of all devices on a board of high-speed logic can best be maintained by providing a guiet environment free of noise spikes, undershoot, and ringing. The key elements in creating such an environment are good supply decoupling and termination of interconnections.

POWER DISTRIBUTION

To maintain wide operating margins across all devices on a board, the supply impedance at each device must be kept to a minimum. The internal design of PDSP devices is such that the input registers, main logic, and output buffers have separate supply pins. This arrangement is designed to ensure that current spikes generated in the output drivers do not modulate the supply to the input gates, hence altering the thresholds. Although these multiple supply pins are internally connected, the internal paths are not particularly low impedance, and therefore each individual Vcc pin should be separately decoupled.

The total supply impedance at a device is a function of the supply line impedance and the decoupling capacitors. In practice, the effect of local decoupling does not extend very far, because of the very fast edges of the current spikes generated by CMOS output stages and the inductive nature of the PCB tracks. In order to minimise the effects of these transients, the decoupling capacitors should be high quality, low inductance parts mounted as close as possible to the device pins, with as short a track length as is practical. Capacitor values should be in the 0.1 to 0.47µF region, too small and there will be insufficient decoupling, too large and the equivalent inductance will reduce decoupling efficiency. The quality of the ground connection is also important, this should be either a solid plane or a grid to minimise inductance and prevent loss of noise margin due to differential ground noise between devices.

Low frequency current transients can best be handled by tantalum capacitors mounted close to the edge connector where the panel tracks meet the backplane power distribution system. Such large capacitors provide bulk energy storage which prevents voltage drops due to the long inductive path between the logic board and the system power supply.

TRACK TERMINATION

On a large board PCB tracks look like shorted transmission lines to the signals they are carrying . This causes reflection of the signal resulting in undershoot, overshoot or ringing. Particular cases which can cause difficulty are large RAM arrays being addressed by the PDSP1601 - the long track lengths and heavy capacitative loading can store and reflect amounts of energy leading to severe ringing - and LSTTL to CMOS interface via long tracks which can suffer severe undershoot. In both cases track termination is best effected by a series resistor at the driving end (typically 10 or 18 ohms). Parallel termination is not recommended since it reduces the voltage swing at the input (making the noise margin even worse), consumes DC power (hardly desirable in a CMOS system) and doesn't work very well in any case.

VERIFICATION

When a board design is complete and the prototype built, it is good practice to check the power supplies to each device and the signals on the buses with a wideband 'scope to ensure that excessive noise, ringing or undershoot is not present. A board which works on the bench but which is marginal because of noise problems will almost certainly exhibit gremlins in the field.



HEADQUARTERS OPERATIONS

MITEL SEMICONDUCTOR

Cheney Manor, Swindon, Wiltshire SN2 2QW, United Kingdom. Tel: (01793) 518000

Fax: (01793) 518411

MITEL SEMICONDUCTOR

1500 Green Hills Road, Scotts Valley, California 95066-4922 United States of America. Tel (408) 438 2900 Fax: (408) 438 5576/6231

Internet: http://www.gpsemi.com

CUSTOMER SERVICE CENTRES

- FRANCE & BENELUX Les Ulis Cedex Tel: (1) 69 18 90 00 Fax: (1) 64 46 06 07
- GERMANY Munich Tel: (089) 419508-20 Fax: (089) 419508-55
- ITALY Milan Tel: (02) 6607151 Fax: (02) 66040993
- JAPAN Tokyo Tel: (03) 5276-5501 Fax: (03) 5276-5510
- KOREA Seoul Tel: (2) 5668141 Fax: (2) 5697933
- NORTH AMERICA Scotts Valley, USA Tel: (408) 438 2900 Fax: (408) 438 5576/6231
- SOUTH EAST ASIA Singapore Tel:(65) 3827708 Fax: (65) 3828872
- **SWEDEN** Stockholm Tel: 46 8 702 97 70 Fax: 46 8 640 47 36
- TAIWAN, ROC Taipei Tel: 886 2 25461260 Fax: 886 2 27190260
- UK, EIRE, DENMARK, FINLAND & NORWAY

Swindon Tel: (01793) 726666 Fax: (01793) 518582

These are supported by Agents and Distributors in major countries world-wide. © Mitel Corporation 1998 Publication No. AB16 Issue No. 3.0 June 1996

TECHNICAL DOCUMENTATION - NOT FOR RESALE. PRINTED IN UNITED KINGDOM

This publication is issued to provide information only which (unless agreed by the Company in writing) may not be used, applied or reproduced for any purpose nor form part of any order or contract nor to be regarded as a representation relating to the products or services concerned. No warranty or guarantee express or implied is made regarding the capability, performance or suitability of any product or service. The Company reserves the right to alter without prior notice the specification, design or price of any product or service. Information concerning possible methods of use is provided as a guide only and does not constitute any guarantee that such methods of use will be satisfactory in a specific piece of equipment. It is the user's responsibility to fully determine the performance and suitability of any equipment using such information and to ensure that any publication or data used is up to date and has not been superseded. These products are not suitable for use in any medical products whose failure to perform may result in significant injury or death to the user. All products and materials are sold and services provided subject to the Company's conditions of sale, which are available on request.