Application Note 40 Using the RC6333/RC6334 Video Amplifiers as Set-Top Box Buffers/Drivers

Introduction

The RC6333/RC6334 are ideal as general purpose amplifiers and specially suited for high speed and high performance requirements of buffers/drivers in set-top boxes. They can meet needs of the front end and the back-end part of the system where Analog to Digital or Digital To Analog convertion takes place.

Figure 1 shows the use of the RC6333/RC6334 at the output of a video encoder for buffering multiple outputs. Although newer encoders may directly drive single loads, the use of a buffer improves the return loss and offers ESD protection against signals from TV. The output of the encoder or DAC is usually a current signal that is converted into a voltage and filtered. Use of the buffer allows the DAC load to be dropped to 500Ω from the 150Ω usually used, thus reducing the power. This results in better signal quality and performance from the encoders in a cost-effective manner. High frequency applications require good grounding, power supply decouping, low parasitic capacitance and inductance, and good isolation between inputs to minimize their crosstalk. Avoid coupling from output to input to prevent positive feedback.

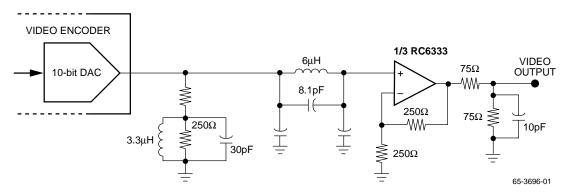


Figure 1. Output Buffer for Video Encoder/DACs

The information contained in this data book shall not by implication or otherwise become part of the terms and conditions of any sale. Raytheon's liability shall be determined solely by its terms and conditions of sale. No representation as to application or use or that the products are either licensed or free from patent infringement is intended or implied. Raytheon reserves the right to change the circuitry and other data at any time without notice and assumes no liability for errors.

LIFE SUPPORT POLICY:

Raytheon's products are not authorized for use in life support applications, wherein failures or malfunctions can reasonable be expected to result in personal injury, without the express written approval of the General Manager of Raytheon Semiconductor Division.

Raytheon Electronics Semiconductor Division 350 Ellis Street Mountain View CA 94043 415.968.9211 800.722.7074 FAX 415.966.7742