Application Note 45

Replacement of Cypress' CY7B922/CY7B932 or CY7B923/CY7B933 Transmitter & Receiver with RCC700A Transceiver


This application note is intended to provide a transparent method to convert the customer's design-in of Cypress' CY7B922/CY7B932 or CY7B923/CY7B933 transmitter and receiver with Raytheon Semiconductor's single chip CMOS solution, RCC700A. This assumes the following:

• Only the control codes K28.0 through K28.7 are being used in the design with Cypress chips.

Most likely, the customer is using an ASIC, programmable gate array or a programmable logic to interface to Cypress' chips. If this is the case, they can reprogram the chip to accommodate Raytheon Semiconductor's RCC700A quite easily as noted in the figure and PAL equations.

PAL Equations

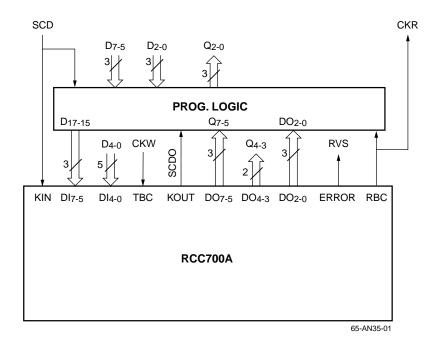DI7=D2*SCD+/SCD*D7 DI6=D1*SCD+/SCD*D6 DI5=D0*SCD+/SCD*D5 Q2=Q7*KOUT+/KOUT*DO2 Q1=Q6*KOUT+/KOUT*DO1 Q0=Q5*KOUT+/KOUT*DO0



AN45 APPLICATION NOTE

The information contained in this data sheet has been carefully compiled; however, it shall not by implication or otherwise become part of the terms and conditions of any subsequent sale. Raytheon's liability shall be determined solely by its standard terms and conditions of sale. No representation as to application or use or that the circuits are either licensed or free from patent infringement is intended or implied. Raytheon reserves the right to change the circuitry and any other data at any time without notice and assumes no liability for errors.

LIFE SUPPORT POLICY:

Raytheon's products are not designed for use in life support applications, wherein a failure or malfunction of the component can reasonably be expected to result in personal injury. The user of Raytheon components in life support applications assumes all risk of such use and indemnifies Raytheon Company against all damages

Raytheon Electronics Semiconductor Division 350 Ellis Street Mountain View CA 94043 415 968 9211 FAX 415 966 7742