

AN10894

Application aspects of the UBA3070 switch mode LED driver

Rev. 1 — 12 January 2011

Application note

Document information

Info	Content
Keywords	UBA3070 switch mode, current source, LED string driver applications, buck converter
Abstract	This document contains guidelines for the design and configuration of a UBA3070 IC switch mode LED driver application.



Revision history

Rev	Date	Description
v.1	20110112	first release

Contact information

For more information, please visit: <http://www.nxp.com>

For sales office addresses, please send an email to: salesaddresses@nxp.com

1. Introduction

This document provides guidelines for the design and configuration of a UBA3070 switch mode current source application. The circuit of the UBA3070 demo board version 1.20 (see *UM10400*) is used as a starting point for all explanation and illustrations.

The UBA3070 IC is a controller for switch mode LED driver applications e.g. LED backlighting units for LCD TV and general lighting applications. A typical application for a UBA3070 IC is as a boundary mode buck converter which due to its fundamental properties operates as a switch mode current source. Refer to *AN10876* for further information.

2. Scope

This document is organized as follows:

- [Section 3](#) provides detailed information on the principles of operation, an explanation of in-circuit current flow and current level detection. Also included is a list of typical application characteristics, a component table including typical component values.
- [Section 4](#) provides detailed information about the purpose of key non-IC components, including equations for calculating their optimal values and reference examples.
- [Section 5](#) provides detailed information about direct and indirect demagnetization (demag) detection.

3. Principles of operation

To fully understand the operation cycle and principles of in-circuit current flow refer to [Figure 1](#) and [Figure 2](#). [Figure 1](#) shows the in-circuit current flow, [Figure 2](#) shows the current waveform.

3.1 Operation cycle

1. When MOSFET Q1 is closed, the current in inductor L1 starts to rise linearly (red/outer line in [Figure 1](#)).
2. When I_{peak} is reached, Q1 is opened by the internal logic of the UBA3070 IC.
3. With L1 current continuing to flow through diode D3, the current now starts to decrease linearly.
4. When L1 current decreases to 0 A, Q1 is closed and the operation cycle repeats from [1](#).

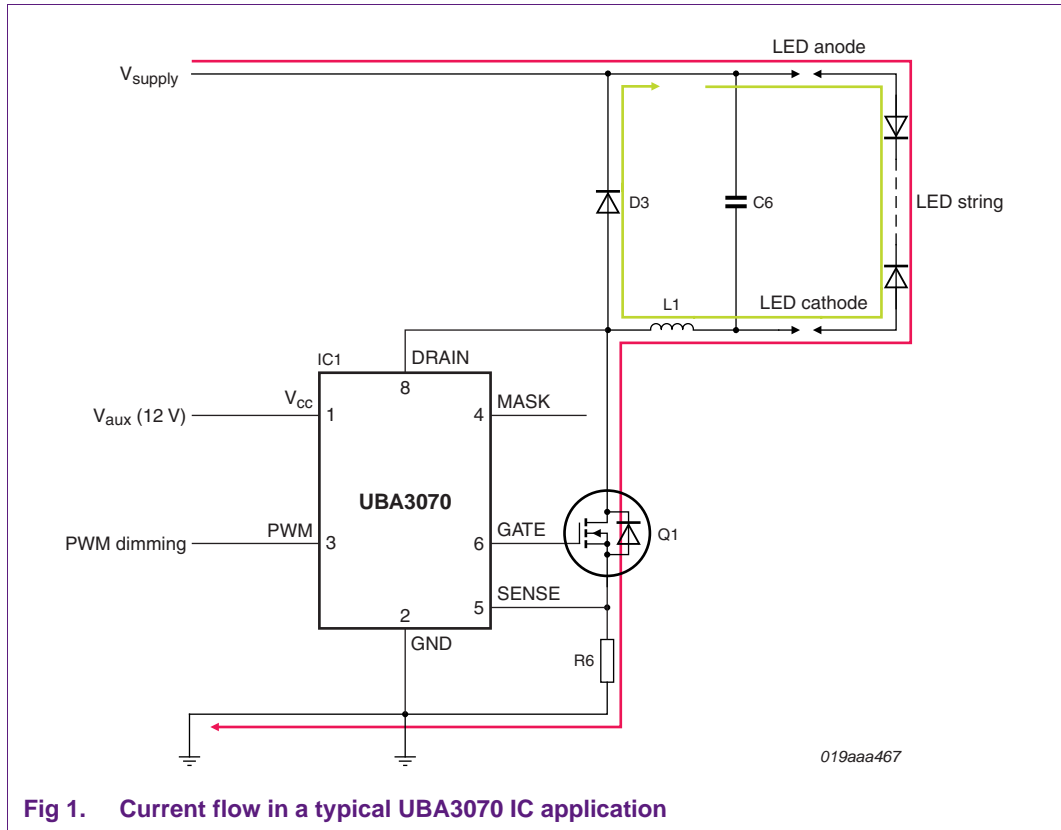


Fig 1. Current flow in a typical UBA3070 IC application

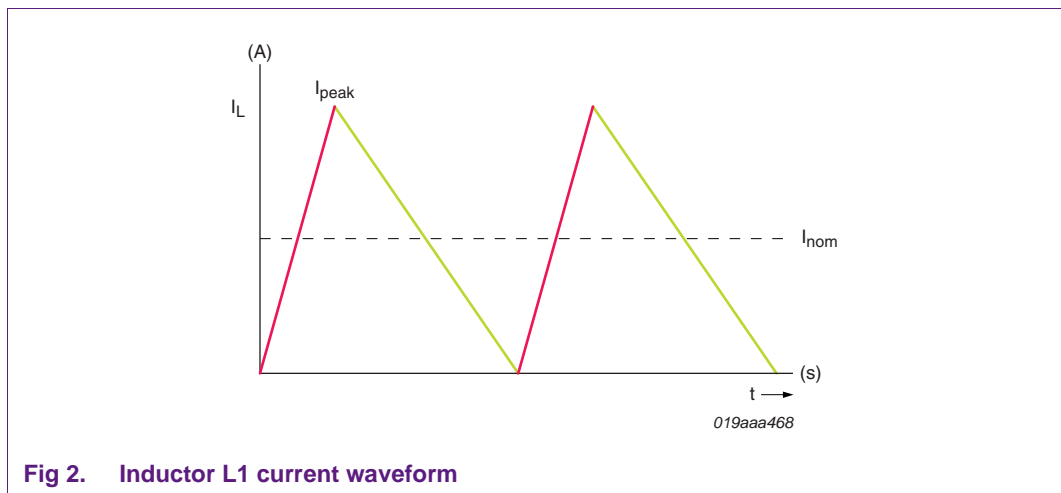


Fig 2. Inductor L1 current waveform

Figure 1 and Figure 2 show that the current rise and fall rates are constant due to the voltage drop across L1. They remain fixed during both the primary stroke (Q1 on-state) and the secondary stroke (Q1 off-state). Therefore, as there is no dead-time between cycles, the average current in L1 and in the LEDs is half of the value of I_{peak} .

Peak current level (I_{peak}) is detected during the primary stroke. As the current in sense resistor R6 is the same as the current in L1, the voltage drop across R6 is a measure for the inductor current. By feeding back the voltage drop across sense resistor R6 to the UBA3070 IC SENSE pin, the peak current level is detected. The default sense level on the SENSE pin is 0.52 V.

The zero current level (or L1 demagnetization) is detected at the end of the secondary stroke. The UBA3070 includes a design feature which allows the reporting of zero current when a voltage level of < 100 mV is present on the MASK pin. L1 is regarded to be demagnetized during such conditions.

Two options exist to transform the detection of L1 demagnetization into a precise signal for the MASK pin. The two options include:

- Direct demag detection. Explained in detail in [Section 5.1](#)
- Indirect demag detection. Explained in detail in [Section 5.2](#)

[Figure 3](#) shows the full diagram of a UBA3070 application that uses the direct demag detection option. The current in L1 is mirrored and scaled by the asymmetric current mirror (Q2, Q3, R4, R7). The scaled current causes a voltage drop across R5, which is applied to the MASK pin after filtering.

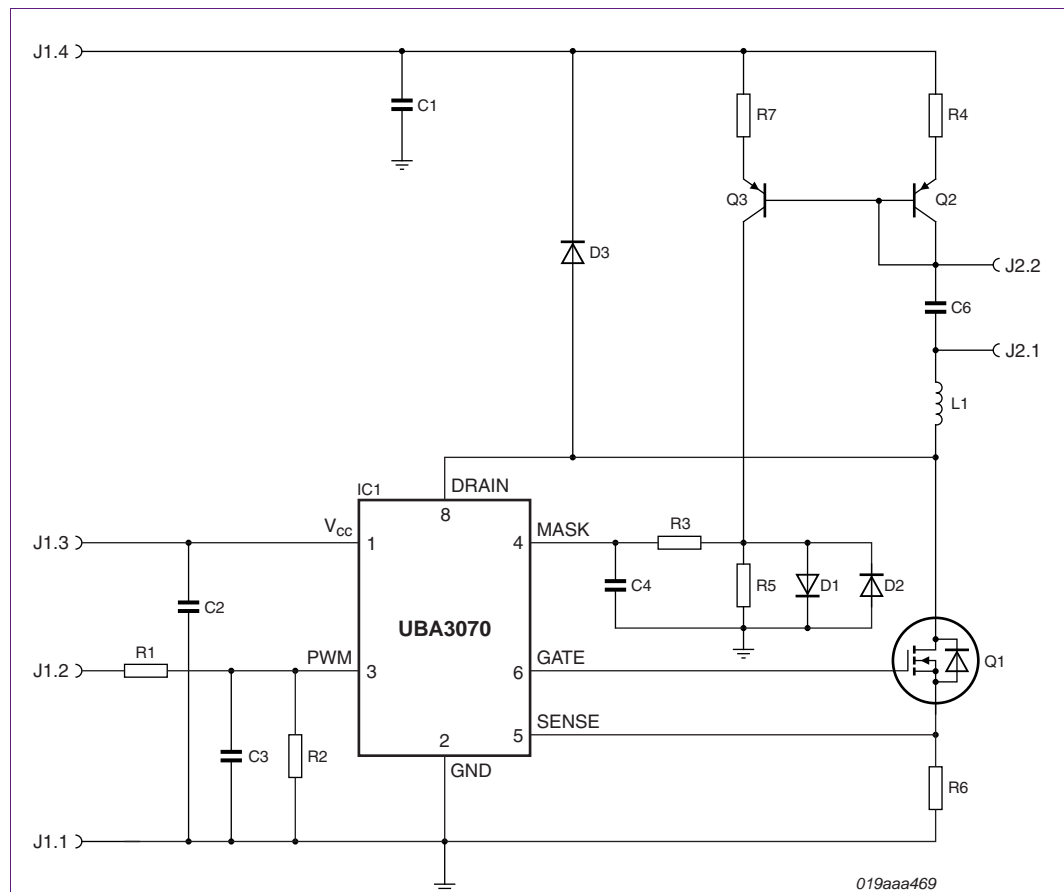


Fig 3. UBA3070 full circuit diagram (with direct demag detection)

Detailed below is a list of typical UBA3070 application characteristics.

- Output current: ~350 mA
- Maximum main supply voltage: 200 V (J1.1 = GND, J1.4 = V_{supply})
- Auxiliary voltage: 12 V (J1.1 = GND, J1.3 = V_{aux})

- LED string drive capability: maximum cumulative V_F voltage drop = 170 V (approximately 60 red LEDs or 45 green/blue/white series LEDs)

Detailed in [Table 1](#) is list of components and values used in a typical UBA3070 application. Refer to [Figure 3](#).

Table 1. Component list

Reference	Component	Remark
IC1	UBA3070	NXP Semiconductors
Q1	PHD9NQ20T	NXP Semiconductors; varies with implementation
Q2	BCP51	NXP Semiconductors
Q3	BF723	NXP Semiconductors; varies with implementation
D1	BAS316	NXP Semiconductors
D2	BAS316	NXP Semiconductors
D3	BYG20J	Vishay
C1	22 μ F, 200 V	varies with implementation
C2	100 μ F, 25 V	-
C3	180 pF	-
C4	22 pF	-
C6	100 nF, 250 V	varies with implementation
L1	560 μ H, 700 mA	varies with implementation
R1	1 k Ω , 0.125 W	-
R2	10 k Ω , 0.125 W	-
R3	22 k Ω , 0.125 W	-
R4	0.75 Ω , 0.25 W	varies with implementation
R5	10 k Ω , 0.125 W	-
R6	0.75 Ω , 0.25 W	varies with implementation (sense resistor)
R7	510 Ω , 0.125 W	-

4. Component selection

[Section 4.1](#) to [Section 4.3](#) states the purpose of key non-IC components used in typical UBA3070 applications. The equations and examples are provided to identify the relationship between circuit components, key circuit values and component selection. Refer to [Figure 3](#).

4.1 Selecting resistor R6

Sense resistor R6 determines the peak current that will flow through the LED string. The operating cycle was described in [Section 3.1](#).

The relationship between the average (or nominal) LED current and R6 can be calculated using equations [Equation 1](#) and [Equation 2](#):

$$I_{LED} = \frac{I_{peak}}{2} = \frac{V_{peak}}{2 \cdot R6} = \frac{0.26}{R6} \tag{1}$$

$$R6 = \frac{V_{peak}}{2 \cdot I_{LED}} = \frac{0.26}{I_{LED}} \quad (2)$$

Second order effects may require the adjustment of R6 by up to 10 % (up to 10 % lower than calculated using [Equation 2](#)). R6 must be selected with sufficient power handling capability.

Example: Under optimal design conditions the current through the LED string (of arbitrary length) must be 350 mA. The value of R6 can be calculated using [Equation 3](#):

$$R6 = \frac{0.26}{I_{LED}} = \frac{0.26}{0.35} \approx 0.75\Omega \quad (3)$$

The input voltage for the circuit (V_{supply} in [Figure 1](#)) must be at least 20 % higher (a factor of 1.20) than the cumulative nominal voltage drop across the LED string, e.g. a string of 30 white LEDs with a nominal voltage drop of 3.3 V at 350 mA must be supplied by V_{supply} of at least = 1.2 (30 × 3.3) = 120 V.

4.2 Selecting inductor L1

Inductor L1 determines the conversion frequency. The conversion frequency of the LED driver is intended to be in the 100 kHz range for the following reasons:

- In-chip technology requires the maximum switching frequency to be lower than 145 kHz
- The considerable current loop length (multiple LEDs in series) and the LED ripple current impose ElectroMagnetic Interference (EMI) restrictions. Regulations (legislation) require sufficient separation from the 150 kHz EMI mask frequency.

Charging time of L1 is given by [Equation 4](#):

$$t_c = L_1 \times \frac{2 \times I_{LED}}{V_{supply} - V_{LED}} \quad (4)$$

In the example shown in [Figure 3](#), let's assume that the supply voltage (V_{supply} , connected between J1.4 and J1.1) is 170 V. For 30 white LEDs (V_F for each element is approximately 3.3 V), the voltage drop across the LED string (V_{LED}) would be 100 V (at 350 mA LED current).

Discharging time of L1 is given by [Equation 5](#):

$$t_d = L_1 \times \frac{2 \times I_{LED}}{V_{LED}} \quad (5)$$

As a result the switching frequency is given by [Equation 6](#):

$$f_{sw} = \frac{1}{t_c + t_d} \quad (6)$$

If L1 has a value of 560 μH, the switching frequency would be approximately 105 kHz.

At a given main supply voltage and a given LED current, the maximum switching frequency is achieved when $t_c = t_d$. This condition occurs when the LED string voltage is half of the supply voltage, see [Equation 7](#):

$$V_{LED} = \frac{t_c}{t_c + t_d} \cdot V_{supply} = \frac{V_{supply}}{2} \tag{7}$$

In cases of variable load where the main supply voltage and LED current is fixed, L1 must be chosen so that the maximum allowable switching frequency of the UBA3070 IC can never be exceeded.

[Figure 4](#) shows a normalized graph of f_{sw} versus V_{LED} / V_{supply} .

If a maximum switching frequency $f_{sw} = 145$ kHz is required, then the smallest possible inductance value can be calculated using [Equation 8](#):

$$L_1 = \frac{V_{supply}}{8 \cdot f_{sw} \cdot I_{LED}} = \frac{1}{1160000} \cdot \frac{V_{supply}}{I_{LED}} \tag{8}$$

When $V_{supply} = 170$ V and $I_{LED} = 350$ mA, the smallest possible L1 would be 418 μ H.

Furthermore, L1 must be chosen with a suitable saturation current (i.e. $> 2 \times I_{LED}$), 145 kHz operation capability and with good power dissipation capabilities.

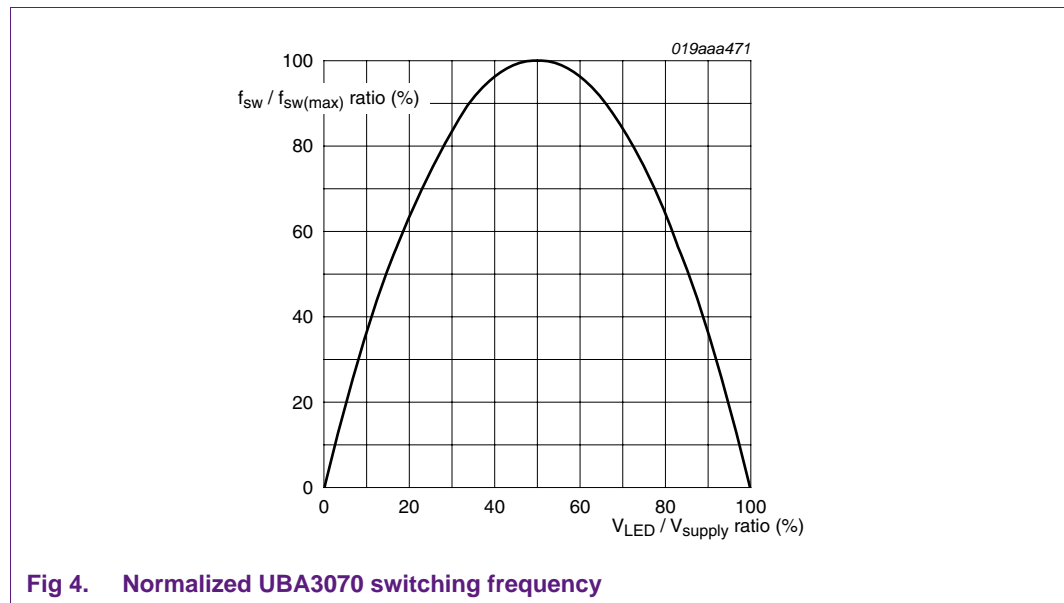


Fig 4. Normalized UBA3070 switching frequency

4.3 Selecting capacitor C6

Capacitor C6 determines the filtering of the coil current to reach acceptable ripple current through the LEDs. In addition, C6 also determines the rise and fall current tails during switch-on and switch-off of the converter. Turning the converter on and off, is the method used for Pulse-Width Modulation (PWM) dimming. Furthermore, C6 must be chosen carefully, trading-off ripple, tailing requirements and dimming range.

The dynamic resistance of the LED string needs to be used for making a first estimate:

$$Ripple_percentage = \frac{I}{\pi \times R_{dyn(LED)} \times C6 \times f_{sw}} \quad (9)$$

$$C6 = \frac{I}{\pi \times R_{dyn(LED)} \times Ripple_percentage \times f_{sw}} \quad (10)$$

with

$$R_{dyn(LED)} = \frac{\partial V_{LED}}{\partial I_{LED}} \text{ at nominal } I_{LED} \quad (11)$$

Ripple percentage (alternatively, ripple factor) is defined as the peak-to-peak value of the ripple current amplitude divided by the DC (nominal) current value.

Example: Consider an LED string of 30 white LEDs. The average target current through the LEDs is 350 mA. At 350 mA the voltage drop across one LED is 3.3 V and at 351 mA, the voltage drop is 3.31 V. The approximate $R_{dyn(LED)}$ is given in [Equation 12](#):

$$R_{dyn(LED)} = \frac{\partial V_{LED}}{\partial I_{LED}} = \frac{30 \times (3.31 - 3.3)}{0.351 - 0.350} = 300\Omega \quad (12)$$

Allowing a 10 % ripple (a factor of 0.10) on the current through the LEDs and a switching frequency of 105 kHz, then C6 can be calculated using [Equation 13](#):

$$C6 = \frac{I}{\pi \cdot 300 \cdot 0.10 \cdot 105000} \approx 101nF \quad (13)$$

5. Demagnetization (demag) detection circuits

Various demag detection options can be employed. Two options that are practically feasible are discussed: direct and indirect demag detection. Though the circuit design and the components used are slightly different, the purpose of both circuits is to provide/generate a precise signal about the magnetization status of L1 to the UBA3070 MASK pin. Each demag detection option is explained in [Section 5.1](#) and [Section 5.2](#).

5.1 Direct demag detection

Direct demag detection is the default mode and the most accurate detection option when a high level of LED current accuracy is required. [Figure 3](#) shows a typical direct demag detection circuit is built around an asymmetric current mirror comprising Q2, R4, Q3 and R7 which senses the current through L1 then translates the sensed current level into a voltage signal using R5. The voltage is limited to ± 0.7 V by the anti-parallel diodes D1 and D2. The current flow into the MASK pin is limited by resistor R3 with capacitor C4 managing some of the noise rejection.

In order to maintain high efficiency, the mirrored current (I_{MR}) must only be a fraction of the current through L1. However, the mirrored current must not be too small in order to obtain sufficient noise immunity. A few hundred μA in the mirrored branch is typically a good compromise. A mirrored current of approximately 500 μA is assumed for the remainder of this section.

$$I_{MR} = 500\mu A \quad (14)$$

The bipolar PNP transistors Q2 and Q3 should preferably both have high h_{FE} figures. In addition, Q2 must be capable of handling $2 \times I_{LED}$ collector current, while the maximum operating voltage of the transistor can be low e.g. < 20 V. Transistor Q3 must be capable of withstanding V_{supply} between collector and emitter, while the maximum operating current can be low (at least $2 \times I_{MR}$).

Table 2. Suggested Q2 bipolar transistors

I_{LED}	Q2 transistor type
≤ 250 mA	BCX17, BCX18
250 mA to 500 mA	BCX51, BCX52, BCX53
500 mA to 1 A	PBSS5320X
1 A to 2 A	PBSS5520X, PBSS301PZ

Table 3. Suggested Q3 bipolar transistors

V_{supply}	Q3 transistor type
≤ 50 V	BC856
50 V to 100 V	BSS63, PMBT5401
100 V to 200 V	BF623, BF723, BF823, PXTA92
200 V to 500 V	PBHV9040T

The operation of the current mirror Q2/Q3 is more accurate when the voltage drop across the mirror resistors R4/R7 is larger. However, a higher voltage drop leads to higher power loss and lower efficiency of the circuit. A workable compromise for V_{MR} in relation to I_{LED} is detailed in [Table 4](#).

Table 4. Suggested I_{LED} dependent V_{MR} values

Nominal LED current I_{LED}	Suggested V_{MR}	R4 power rating
≤ 350 mA	250 mV	0.25 W
350 mA to 700 mA	150 mV	0.5 W
700 mA to 1.5 A	100 mV	0.5 W

With V_{MR} , I_{MR} and I_{LED} known, the direct demag detection circuit component values can be calculated using [Equation 15](#) [Equation 16](#) and [Equation 17](#):

$$R4 = \frac{V_{MR}}{I_{LED}} \tag{15}$$

$$R7 = \frac{V_{MR}}{I_{MR}} \tag{16}$$

$$R5 = \frac{5.0}{I_{MR}} \tag{17}$$

In-circuit components of fixed value are detailed in [Table 5](#).

Table 5. Fixed components in the direct demag detection circuit

Component	Value
D1, D2	BAS316, 1N4148, BAV99 (dual diode) or equivalent
R3	22 k Ω
C4	22 pF

5.1.1 Calculating component values

Given that the nominal programmed LED current (I_{LED}) is 350 mA and that the operating voltage (V_{supply}) is 170 V. From [Table 2](#) and [Table 3](#), Q2 and Q3 are selected as BCX53 and PXTA92 respectively and a value for V_{MR} from [Table 4](#) as:

$$V_{MR} = 0.25V \quad (18)$$

The values for resistors R4, R7 and R5 can be calculated using [Equation 15](#), [Equation 16](#) and [Equation 17](#):

$$R_4 = \frac{V_{MR}}{I_{LED}} = \frac{0.5}{0.35} = 0.71\Omega \quad (19)$$

$$R_7 = \frac{V_{MR}}{I_{MR}} = \frac{0.25}{0.0005} = 500\Omega \quad (20)$$

$$R_5 = \frac{5.0}{I_{MR}} = \frac{5.0}{0.0005} = 10000\Omega \quad (21)$$

5.2 Indirect demag detection

Indirect demag detection is the least accurate detection option when high levels of LED current accuracy is required. [Figure 5](#) shows a typical indirect demag detection circuit that uses the ringing of the drain node of MOSFET Q1 as an indication of L1 losing it's energy. The ringing signal propagates through C9 and R10 and the first valley of the signal forces the voltage on the MASK pin to drop below 100 mV. For the UBA3070 this is the indication that a new cycle must start, refer to [Section 3.1](#).

The ringing signal contributes to the less accurate nature of this detection option. In addition, other switching signals can be misinterpreted by this circuit configuration (as an indication of the inductor becoming energy-less) causing inaccurate current control. For example, PWM dimming can cause additional signals appearing on the drain node of Q1 that interfere with accurate current control. Therefore, applications that require a high level of LED current accuracy and where PWM dimming is used, indirect demag detection may not be the optimal option.

The component configuration for this detection option can also be implemented on the UBA3070 V1.2 demo board. [Table 6](#) shows the component changes with respect to the Bill Of Materials (BOM) shown in ([Table 1](#)).

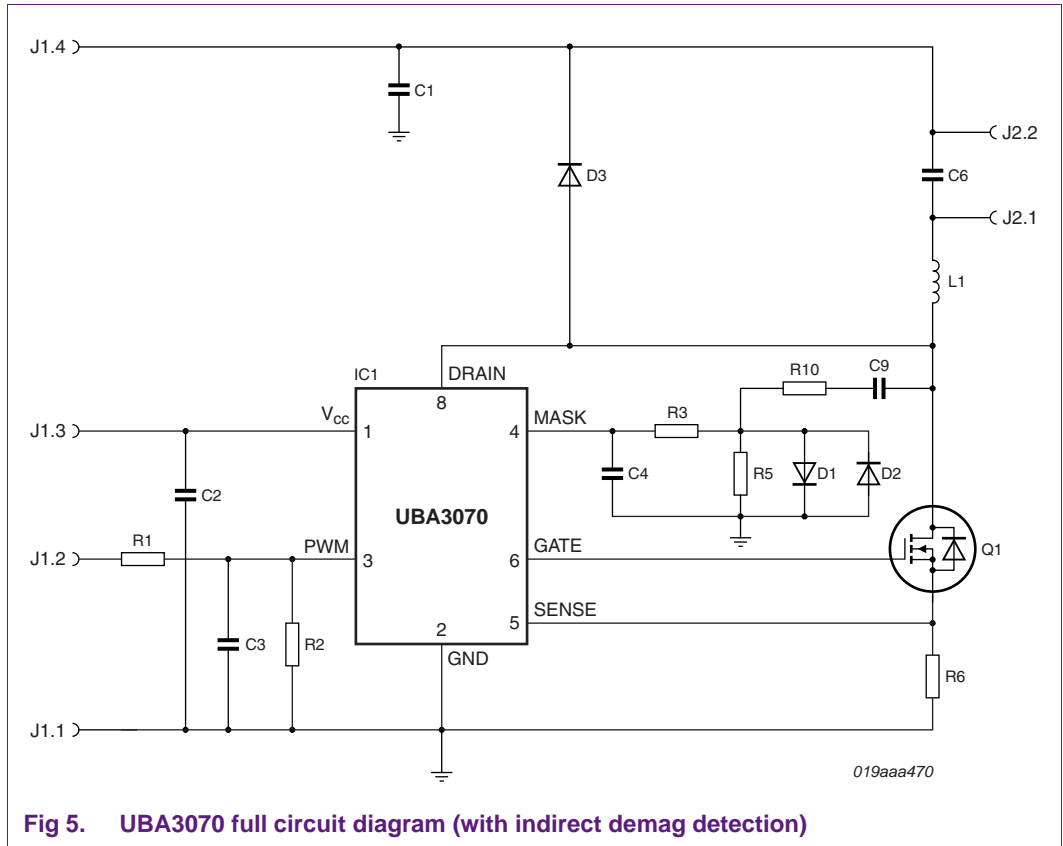


Fig 5. UBA3070 full circuit diagram (with indirect demag detection)

Table 6. List of component changes

Reference	Value (typical)	Remark
Q2	not mounted	-
Q3	not mounted	-
C9	330 pF, 200 V	-
R4	not mounted	-
R5	1 kΩ	-
R7	not mounted	-
R10	22 kΩ, 0.125 W	-

6. Abbreviations

Table 7. Abbreviations

Acronym	Description
BOM	Bill Of Materials
EMI	ElectroMagnetic Interference
IC	Integrated Circuit
LCD	Liquid Crystal Display
LED	Light Emitting Diode
PNP	Positive Negative Positive
MOSFET	Metal-Oxide Semiconductor Field Effect Transistor
PWM	Pulse-Width Modulation

7. References

- [1] **UBA3070** — Data sheet
- [2] **UM10436** — User manual
- [3] **AN10876** — Buck converters for SSL application note

8. Legal information

8.1 Definitions

Draft — The document is a draft version only. The content is still under internal review and subject to formal approval, which may result in modifications or additions. NXP Semiconductors does not give any representations or warranties as to the accuracy or completeness of information included herein and shall have no liability for the consequences of use of such information.

8.2 Disclaimers

Limited warranty and liability — Information in this document is believed to be accurate and reliable. However, NXP Semiconductors does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information.

In no event shall NXP Semiconductors be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, NXP Semiconductors' aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the *Terms and conditions of commercial sale* of NXP Semiconductors.

Right to make changes — NXP Semiconductors reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

Suitability for use — NXP Semiconductors products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an NXP Semiconductors product can reasonably be expected to result in personal injury, death or severe property or environmental damage. NXP Semiconductors accepts no liability for inclusion and/or use of NXP Semiconductors products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

Applications — Applications that are described herein for any of these products are for illustrative purposes only. NXP Semiconductors makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using NXP Semiconductors products, and NXP Semiconductors accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine whether the NXP Semiconductors product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

NXP Semiconductors does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using NXP Semiconductors products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). NXP does not accept any liability in this respect.

Export control — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from national authorities.

Evaluation products — This product is provided on an "as is" and "with all faults" basis for evaluation purposes only. NXP Semiconductors, its affiliates and their suppliers expressly disclaim all warranties, whether express, implied or statutory, including but not limited to the implied warranties of non-infringement, merchantability and fitness for a particular purpose. The entire risk as to the quality, or arising out of the use or performance, of this product remains with customer.

In no event shall NXP Semiconductors, its affiliates or their suppliers be liable to customer for any special, indirect, consequential, punitive or incidental damages (including without limitation damages for loss of business, business interruption, loss of use, loss of data or information, and the like) arising out of the use of or inability to use the product, whether or not based on tort (including negligence), strict liability, breach of contract, breach of warranty or any other theory, even if advised of the possibility of such damages.

Notwithstanding any damages that customer might incur for any reason whatsoever (including without limitation, all damages referenced above and all direct or general damages), the entire liability of NXP Semiconductors, its affiliates and their suppliers and customer's exclusive remedy for all of the foregoing shall be limited to actual damages incurred by customer based on reasonable reliance up to the greater of the amount actually paid by customer for the product or five dollars (US\$5.00). The foregoing limitations, exclusions and disclaimers shall apply to the maximum extent permitted by applicable law, even if any remedy fails of its essential purpose.

Non-automotive qualified products — Unless this data sheet expressly states that this specific NXP Semiconductors product is automotive qualified, the product is not suitable for automotive use. It is neither qualified nor tested in accordance with automotive testing or application requirements. NXP Semiconductors accepts no liability for inclusion and/or use of non-automotive qualified products in automotive equipment or applications.

In the event that customer uses the product for design-in and use in automotive applications to automotive specifications and standards, customer (a) shall use the product without NXP Semiconductors' warranty of the product for such automotive applications, use and specifications, and (b) whenever customer uses the product for automotive applications beyond NXP Semiconductors' specifications such use shall be solely at customer's own risk, and (c) customer fully indemnifies NXP Semiconductors for any liability, damages or failed product claims resulting from customer design and use of the product for automotive applications beyond NXP Semiconductors' standard warranty and NXP Semiconductors' product specifications.

8.3 Trademarks

Notice: All referenced brands, product names, service names and trademarks are the property of their respective owners.

9. Tables

Table 1.	Component list	6
Table 2.	Suggested Q2 bipolar transistors	10
Table 3.	Suggested Q3 bipolar transistors	10
Table 4.	Suggested I_{LED} dependent V_{MR} values	10
Table 5.	Fixed components in the direct demag detection circuit	10
Table 6.	List of component changes	12
Table 7.	Abbreviations	13

10. Figures

Fig 1.	Current flow in a typical UBA3070 IC application	.4
Fig 2.	Inductor L1 current waveform	.4
Fig 3.	UBA3070 full circuit diagram (with direct demag detection)	.5
Fig 4.	Normalized UBA3070 switching frequency	.8
Fig 5.	UBA3070 full circuit diagram (with indirect demag detection)	.12

11. Contents

1	Introduction	3
2	Scope	3
3	Principles of operation	3
3.1	Operation cycle.	3
4	Component selection	6
4.1	Selecting resistor R6	6
4.2	Selecting inductor L1	7
4.3	Selecting capacitor C6	8
5	Demagnetization (demag) detection circuits .	9
5.1	Direct demag detection.	9
5.1.1	Calculating component values	11
5.2	Indirect demag detection	11
6	Abbreviations	13
7	References	13
8	Legal information	14
8.1	Definitions.	14
8.2	Disclaimers	14
8.3	Trademarks	14
9	Tables	15
10	Figures	16
11	Contents	17

Please be aware that important notices concerning this document and the product(s) described herein, have been included in section 'Legal information'.

© NXP B.V. 2011.

All rights reserved.

For more information, please visit: <http://www.nxp.com>

For sales office addresses, please send an email to: salesaddresses@nxp.com

Date of release: 12 January 2011

Document identifier: AN10894