

AN10944

1930 MHz to 1990 MHz Doherty amplifier using the BLF7G20LS-200

Rev. 1 — 4 January 2011

Application note

Document information

Info	Content
Keywords	RF power transistors, Doherty architecture, LDMOS, power amplifier, RF performance, Digital PreDistortion (DPD), W-CDMA, BLF7G20LS-200
Abstract	This application note describes the design and performance of a Doherty power amplifier for base stations in the 1930 MHz to 1990 MHz band using the BLF7G20LS-200 LDMOS transistor



Revision history

Rev	Date	Description
v.1	20110104	initial version

Contact information

For more information, please visit: <http://www.nxp.com>

For sales office addresses, please send an email to: salesaddresses@nxp.com

1. Introduction

This application note describes the design characteristics and RF performance of a state-of-the-art Doherty power amplifier for base stations in the 1930 MHz to 1990 MHz band using the BLF7G20LS-200 LDMOS transistor.

The amplifier uses two BLF7G20LS-200 devices in a Doherty architecture on a Rogers 3006 PCB having a thickness of 0.64 mm (0.025"). The design ensures high-efficiency while maintaining a very similar peak power capability of two transistors combined. The input and output sections are internally matched, benefiting the amplifier design with high gain and good gain flatness and phase linearity over the frequency band of 1930 MHz to 1990 MHz.

The BLF7G20LS-200 is a seventh generation LDMOS device using NXP Semiconductor's advanced LDMOS process.

2. Test summary

The amplifier was characterized under the following conditions:

- Network analyzer measurements for power gain (G_p), delay time (t_d) and Input Return Loss (IRL):
 - output power (P_L) = 46 dBm
 - drain-source voltage (V_{DS}) = 30 V
 - main power amplifier quiescent drain current (I_{Dq}) (main amplifier) = 1600 mA
 - gate-source voltage of peak amplifier (V_{GS}) (peak amplifier) = 0.296 V
- Standard IS-95 ACPR, gain and efficiency measurements:
 - P_L = 49 dBm
 - I_{Dq} (main amplifier) = 1600 mA
 - V_{GS} (peak amplifier) = 0.296 V
 - V_{DS} = 30 V
 - IS-95 signal (pilot, paging, sync, 6 traffic channels with Walsh codes 8 to 13, PAR = 9.7 dB at 0.01 % probability)
- Power and efficiency measurements (peak output power):
 - using a pulsed signal and measuring the 3 dB compression points with a pulse width of 12 μ s, duty cycle of 10 % at V_{DS} = 30 V, I_{Dq} (main amplifier) = 1600 mA and V_{GS} (peak amplifier) = 0.296 V
- 2-carrier W-CDMA measurements demonstrating Digital PreDistortion (DPD) correction:
 - P_L = 49 dBm
 - 15 MHz spacing
 - V_{DS} = 30 V
 - I_{Dq} (main amplifier) = 1600 mA
 - V_{GS} (peak amplifier) = 0.3 V

Table 1. Performance summary

Frequency (GHz)	G _p at 49 dBm (dB)	IRL at 49 dBm (dB)	Peak output power (P _{L(M)}) (dBm)	Drain efficiency (η_D) at 49 dBm (%)	ACPR (IS-95) at 49 dBm (dBc)
1.93	17.11	-11.8	57.03	40.34	-39.6
1.96	17.38	-11.6	57.04	40.96	-40.6
1.99	17.32	-12.74	57.04	41.73	-41.2

3. Test circuit


The test circuit is designed on a Rogers 3006 PCB having a thickness of 0.64 mm (0.025"), shown in [Section 5 "BLF7G20LS-200 Doherty test circuit" on page 12](#). $V_{DS} = 30$ V. The gate biasing circuits are connected to the 30 V power supplies. There are 8 V regulators on the board. I_{Dq} (main amplifier) and V_{GS} (peak amplifier) can be adjusted using potentiometers.

4. RF performance

 4.1 Network analyzer measurements

Network analyzer measurements were performed under the following conditions:


- $P_L = 46 \text{ dBm}$
- $V_{DS} = 30 \text{ V}$
- $I_{Dq} \text{ (main amplifier)} = 1600 \text{ mA}$
- $V_{GS} \text{ (peak amplifier)} = 0.296 \text{ V}$



 4.2 IS-95 measurements


The IS-95 measurements were performed under the following conditions:

- Signal: IS-95 (pilot, paging, sync, 6 traffic channels with Walsh codes 8 to 13, PAR = 9.7 dB at 0.01% probability)
- Bias: $V_{DS} = 30\text{ V}$
- I_{Dq} (main amplifier) = 1600 mA
- V_{GS} (peak amplifier) = 0.296 V



- (1) $G_p = 1930\text{ MHz}$.
- (2) $G_p = 1960\text{ MHz}$.
- (3) $G_p = 1900\text{ MHz}$.
- (4) $\eta_D = 1930\text{ MHz}$.
- (5) $\eta_D = 1960\text{ MHz}$.
- (6) $\eta_D = 1990\text{ MHz}$.

Fig 2. Power gain and drain efficiency as a function of average output power, IS-95

 

- (1) 1930 MHz – 885 kHz.
- (2) 1960 MHz – 885 kHz.
- (3) 1990 MHz – 885 kHz.
- (4) 1930 MHz + 885 kHz.
- (5) 1960 MHz + 885 kHz.
- (6) 1990 MHz + 885 kHz.
- (7) 1930 MHz – 1.98 MHz.
- (8) 1930 MHz + 1.98 MHz.
- (9) 1960 MHz – 1.98 MHz.
- (10) 1960 MHz + 1.98 MHz.
- (11) 1990 MHz – 1.98 MHz.
- (12) 1990 MHz + 1.98 MHz.

Fig 3. Adjacent Channel Power Ratio (ACPR) as a function of output power

4.3 Peak output power measurements

Peak output power was measured using a pulsed signal with a pulse width of 12 μs and duty cycle of 10 %, and measuring the 1 dB and 3 dB compression points.

The peak power measurements were performed under the following conditions:

- Bias: $V_{DS} = 30\text{ V}$
- I_{Dq} (main amplifier) = 1600 mA
- V_{GS} (peak amplifier) = 0.296 V


 


Fig 4. Peak output power as a function of frequency

 

- (1) $f = 1930\text{ MHz}$.
- (2) $f = 1960\text{ MHz}$.
- (3) $f = 1990\text{ MHz}$.
- (4) $f = 1930\text{ MHz}$.
- (5) $f = 1960\text{ MHz}$.
- (6) $f = 1990\text{ MHz}$.


Fig 5. Power gain and efficiency as a function of output power


4.4 DPD measurements

The DPD measurements were performed using an in-house designed DPD system under the following conditions:

- $f_c = 1930$ MHz
- DPD system: 2-carrier W-CDMA signal, spacing: 15 MHz
- $V_{DS} = 30$ V, I_{Dq} (main amplifier) = 1600 mA, V_{GS} (peak amplifier) = 0.3 V

 In [Figure 6](#) to [Figure 11](#), adjacent lower channel values are the difference in power between the channel within the LH pair of green vertical lines and the channel within the LH pair of red vertical lines. Adjacent upper channel values are the difference in power between the channel within the RH pair of green vertical lines and the channel within the RH pair of red vertical lines.





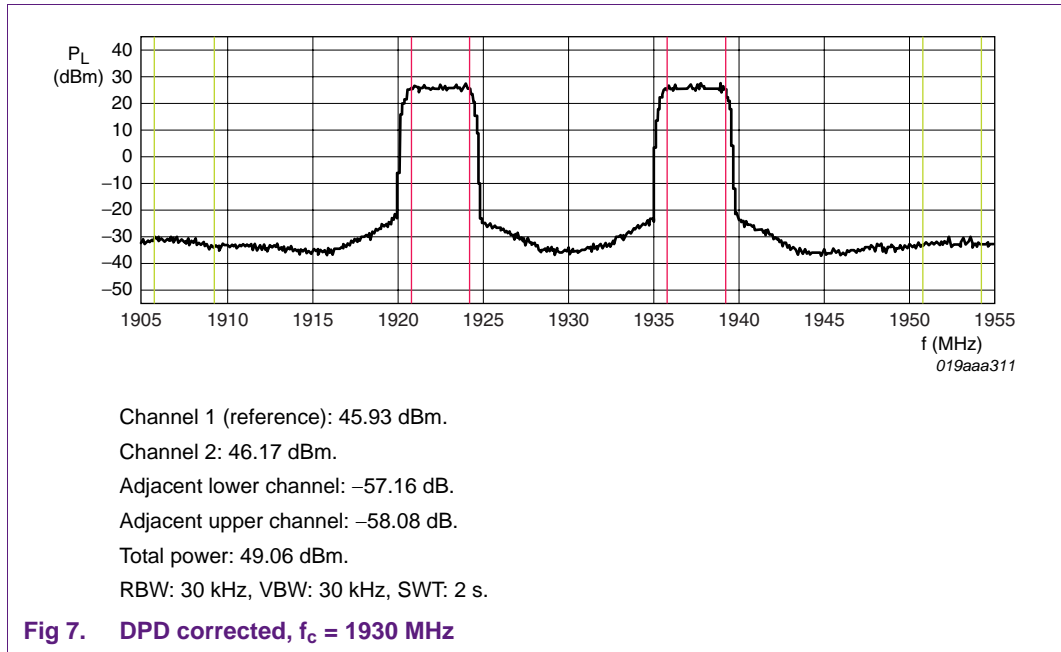

1930 MHz to 1990 MHz Doherty amplifier using the BLF7G20LS-200

The following DPD measurements were performed under the following conditions:

 
 
- $f_c = 1960$ MHz
- DPD system: 2-carrier W-CDMA signal, spacing: 15 MHz
- $V_{DS} = 30$ V, I_{Dq} (main amplifier) = 1600 mA, V_{GS} (peak amplifier) = 0.3 V



1930 MHz to 1990 MHz Doherty amplifier using the BLF7G20LS-200

The following DPD measurements were performed under the following conditions:

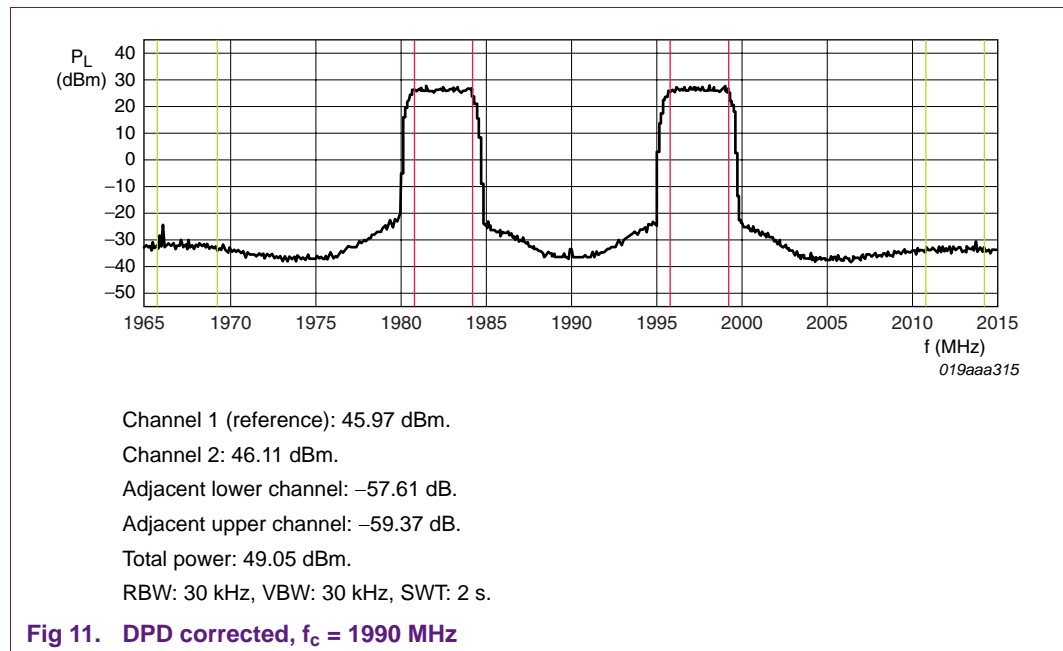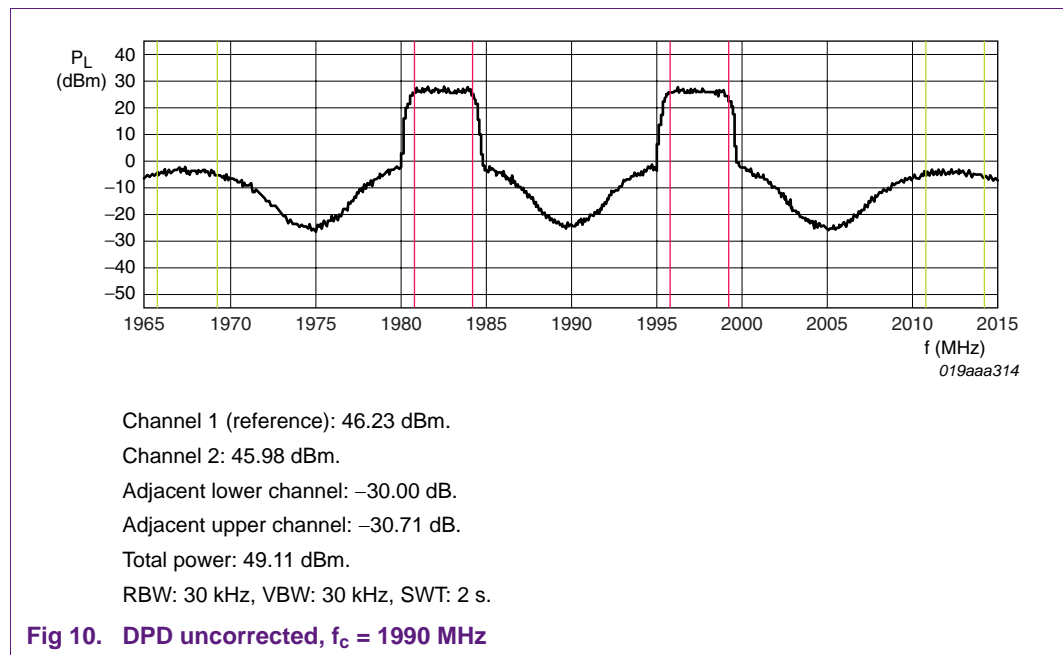- $f_c = 1990$ MHz
- DPD system: 2-carrier W-CDMA signal, spacing: 15 MHz
- $V_{DS} = 30$ V, I_{Dq} (main amplifier) = 1600 mA, V_{GS} (peak amplifier) = 0.3 V



5. BLF7G20LS-200 Doherty test circuit

The test circuit is designed on a Rogers 3006 PCB having a thickness of 0.64 mm (0.025”).


 


Fig 12. BLF7G20LS-200 Doherty test circuit

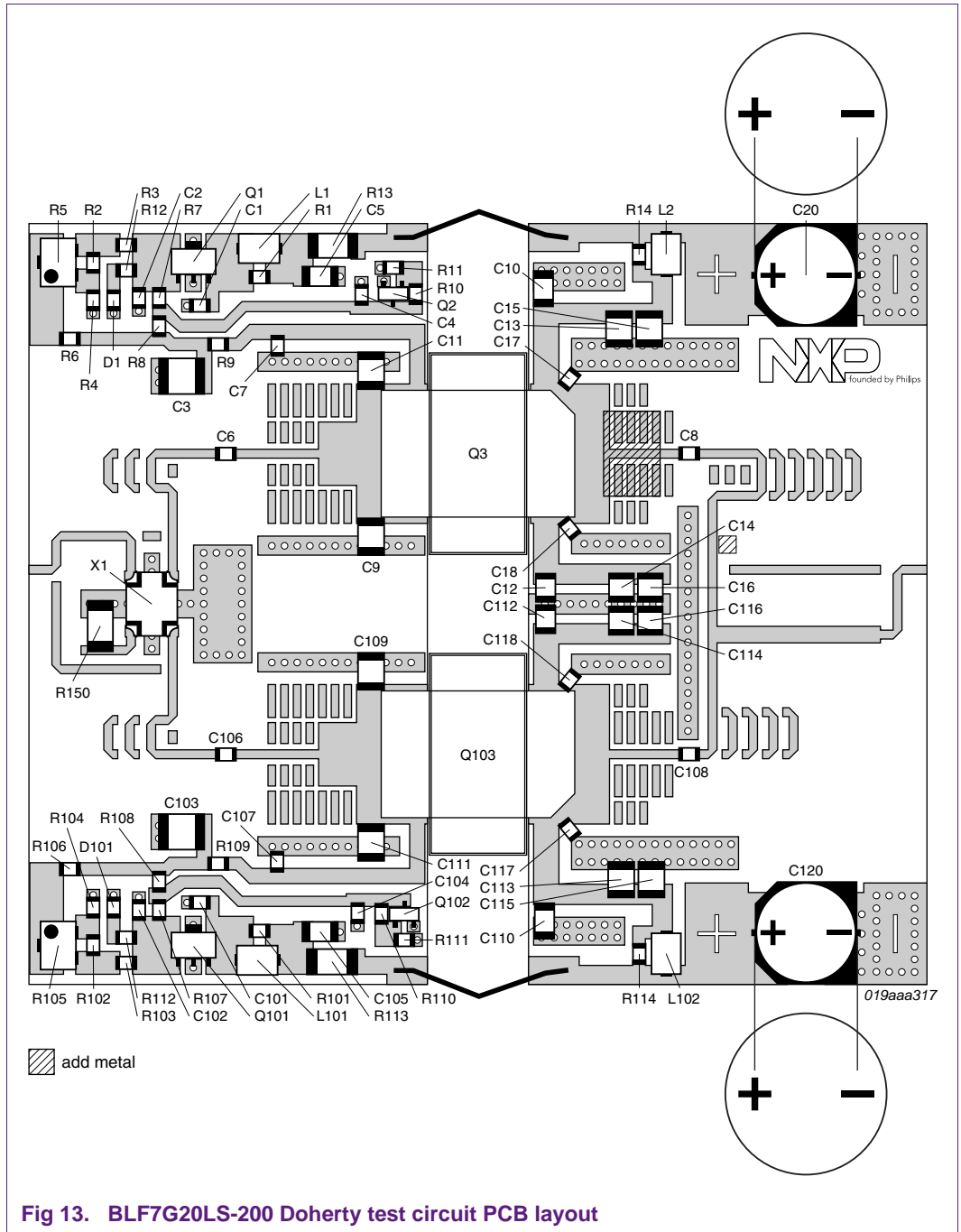

5.1 BLF7G20LS-200 Doherty test circuit components

Table 2. BLF7G20LS-200 Doherty test circuit components

Designator	Description	Part identifier	Manufacturer
Input PCB	BLF7G20LS-200 Doherty PA Input-Rev2 ^[1]	BLF7G20LS-200 Doherty PA Input 25Ro3006	Metro circuits
Output PCB	BLF7G20LS-200 Doherty PA Output-Rev2 ^[1]	BLF7G20LS-200 Doherty PA Output 25Ro3006	Metro circuits
Q1, Q101	78L08 voltage regulator	NJM#78L08UA-ND	NJR
Q2, Q102	2N2222 NPN transistor	MMBT2222	Fairchild
Q3, Q103	BLF7G20LS-200	BLF7G20LS-200	NXP Semiconductors
R1, R14, R101, R114	9.1 Ω	CRCW08059R09FKEA	Vishay Dale
R2, R3, R102, R103	430 Ω	CRCW0805432RFKEA	Vishay Dale
R4, R104	75 Ω	CRCW080575R0FKTA	Vishay Dale
R5, R105	200 Ω , potentiometer	3214-1-201E	Bourns
R6, R106	2 k Ω	CRCW08052K00FKTA	Vishay Dale
R7, R107	1.1 k Ω	CRCW08051K10FKEA	Vishay Dale
R8, R108	11 k Ω	CRCW080511K0FKEA	Vishay Dale
R9, R109	5.1 Ω	CRCW08055R11FKEA	Vishay Dale
R10, R110	5.1 k Ω	CRCW08055K10FKTA	Vishay Dale
R11, R111	910 Ω	CRCW0805909RFKTA	Vishay Dale
R12, R112	1.1 k Ω	CRCW08051K10FKEA	Vishay Dale
R13, R113	499 Ω , 0.5 W	CRCW2010499RFKEF	Vishay Dale
X1	3 dB, hybrid coupler, 30 W	1J503S	Anaren
L1, L2, L101, L102	ferroxcube bead	2743019447	Fair Rite
C1, C2, C4, C101, C102, C104	100 nF ceramic 0805	S0805W104K1HRN-P4	MultiComp
C3, C103	4.7 μ F	C4532X7R1H475M	TDK
C5, C105	1 μ F	C3216X7R1H105K	TDK
C6, C7, C8, C106, C107, C108	15 pF	600F	American Technical Ceramics
C9, C11, C109, C111	0.9 pF	100B	American Technical Ceramics
C13, C14, C113, C114	15 pF	ATC100B150JT500X	American Technical Ceramics
C15, C16, C115, C116	10 μ F	GRM32DF51H106ZA01L	MuRata
C10, C110	1 μ F	GRM31CR72A105KA01L	MuRata
C20, C120	220 μ F, 50 V electrolytic SMT	PCE3474CT-ND	Panasonic
C17, C117	2.0 pF	600F	American Technical Ceramics
C18, C118	2.4 pF	600F	American Technical Ceramics

[1] Rogers 3006; $\epsilon_r = 6.15 \pm 0.15$; thickness 0.64 mm (0.025"); 35 μ m (1 oz.) copper on each side.

6. Abbreviations

Table 3. Abbreviations

Acronym	Description
ACPR	Adjacent Channel Power Ratio
CCDF	Complementary Cumulative Distribution Function
DPD	Digital PreDistortion
LDMOS	Laterally Diffused Metal-Oxide Semiconductor
PAR	Peak-to-Average power Ratio
PCB	Printed-Circuit Board
RBW	Resolution BandWidth
SMT	Surface-Mount Technology
SWT	SWEEP Time
UMTS	Universal Mobile Telecommunications System
VBW	Video BandWidth
W-CDMA	Wideband Code Division Multiple Access

7. Legal information

7.1 Definitions

Draft — The document is a draft version only. The content is still under internal review and subject to formal approval, which may result in modifications or additions. NXP Semiconductors does not give any representations or warranties as to the accuracy or completeness of information included herein and shall have no liability for the consequences of use of such information.

7.2 Disclaimers

Limited warranty and liability — Information in this document is believed to be accurate and reliable. However, NXP Semiconductors does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information.

In no event shall NXP Semiconductors be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, NXP Semiconductors' aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the *Terms and conditions of commercial sale* of NXP Semiconductors.

Right to make changes — NXP Semiconductors reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

Suitability for use — NXP Semiconductors products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an NXP Semiconductors product can reasonably be expected to result in personal injury, death or severe property or environmental damage. NXP Semiconductors accepts no liability for inclusion and/or use of NXP Semiconductors products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

Applications — Applications that are described herein for any of these products are for illustrative purposes only. NXP Semiconductors makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using NXP Semiconductors products, and NXP Semiconductors accepts no liability for any assistance with applications or customer product

design. It is customer's sole responsibility to determine whether the NXP Semiconductors product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

NXP Semiconductors does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using NXP Semiconductors products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). NXP does not accept any liability in this respect.

Export control — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from national authorities.

Evaluation products — This product is provided on an "as is" and "with all faults" basis for evaluation purposes only. NXP Semiconductors, its affiliates and their suppliers expressly disclaim all warranties, whether express, implied or statutory, including but not limited to the implied warranties of non-infringement, merchantability and fitness for a particular purpose. The entire risk as to the quality, or arising out of the use or performance, of this product remains with customer.

In no event shall NXP Semiconductors, its affiliates or their suppliers be liable to customer for any special, indirect, consequential, punitive or incidental damages (including without limitation damages for loss of business, business interruption, loss of use, loss of data or information, and the like) arising out of the use of or inability to use the product, whether or not based on tort (including negligence), strict liability, breach of contract, breach of warranty or any other theory, even if advised of the possibility of such damages.

Notwithstanding any damages that customer might incur for any reason whatsoever (including without limitation, all damages referenced above and all direct or general damages), the entire liability of NXP Semiconductors, its affiliates and their suppliers and customer's exclusive remedy for all of the foregoing shall be limited to actual damages incurred by customer based on reasonable reliance up to the greater of the amount actually paid by customer for the product or five dollars (US\$5.00). The foregoing limitations, exclusions and disclaimers shall apply to the maximum extent permitted by applicable law, even if any remedy fails of its essential purpose.

7.3 Trademarks

Notice: All referenced brands, product names, service names and trademarks are the property of their respective owners.

8. Contents

1	Introduction	3
2	Test summary	3
3	Test circuit	4
4	RF performance	5
4.1	Network analyzer measurements	5
4.2	IS-95 measurements	6
4.3	Peak output power measurements	7
4.4	DPD measurements	8
5	BLF7G20LS-200 Doherty test circuit	12
5.1	BLF7G20LS-200 Doherty test circuit components	14
6	Abbreviations	15
7	Legal information	16
7.1	Definitions	16
7.2	Disclaimers	16
7.3	Trademarks	16
8	Contents	17

Please be aware that important notices concerning this document and the product(s) described herein, have been included in section 'Legal information'.

© NXP B.V. 2011.

All rights reserved.

For more information, please visit: <http://www.nxp.com>

For sales office addresses, please send an email to: salesaddresses@nxp.com

Date of release: 4 January 2011

Document identifier: AN10944