

AN10953

BLF645 10 MHz to 600 MHz 120 W amplifier

Rev. 1 — 3 March 2011

Application note

Document information

Info	Content
Keywords	BLF645, broadband
Abstract	The BLF645 is a 100 W, 32 V LDMOS RF power push-pull transistor for broadcast transmitter and industrial applications from HF to 1.4 GHz. This application note describes a broadband amplifier that delivers more than 100 W from 10 MHz to 600 MHz.



Revision history

Rev	Date	Description
v.1	20110303	initial version


Contact information

For more information, please visit: <http://www.nxp.com>

For sales office addresses, please send an email to: salesaddresses@nxp.com

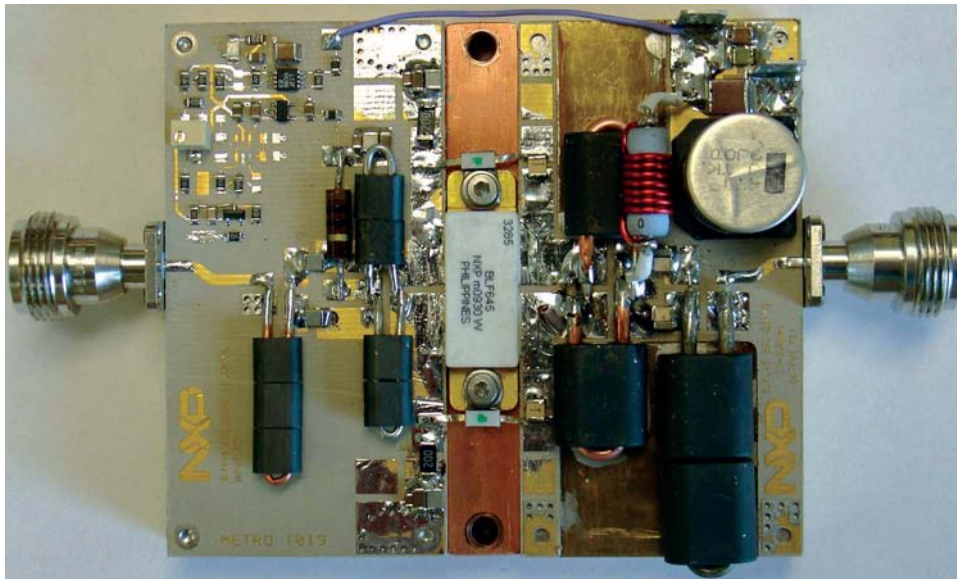1. Introduction

The BLF645 is a 100 W LDMOS RF power push-pull transistor for broadcast transmitter and industrial applications in the HF to 1.4 GHz frequency range. This application note describes a broadband amplifier which delivers more than 100 W from 10 MHz to 600 MHz.



019aaa994

Fig 1. BLF645 10 MHz to 600 MHz amplifier

2. Test summary



The RF performance described in [Section 3](#) may be summarized as follows:



Table 1. Summary of RF performance


Item	Performance
Specified frequency range	10 MHz to 512 MHz
Specified drain voltage	28 V
Quiescent drain current	1 A
Input return loss	≥ 5 dB; 15 dB typical
Peak CW power	≥ 100 W; 120 W typical
Gain	≥ 22.5 dB
Gain flatness	1.8 dB
Efficiency at 100 W	≥ 50 %
Efficiency flatness at 100 W	12 %
IMD3 at 100 W PEP	-30 dBc typical



3. RF Performance


3.1 1-Tone CW

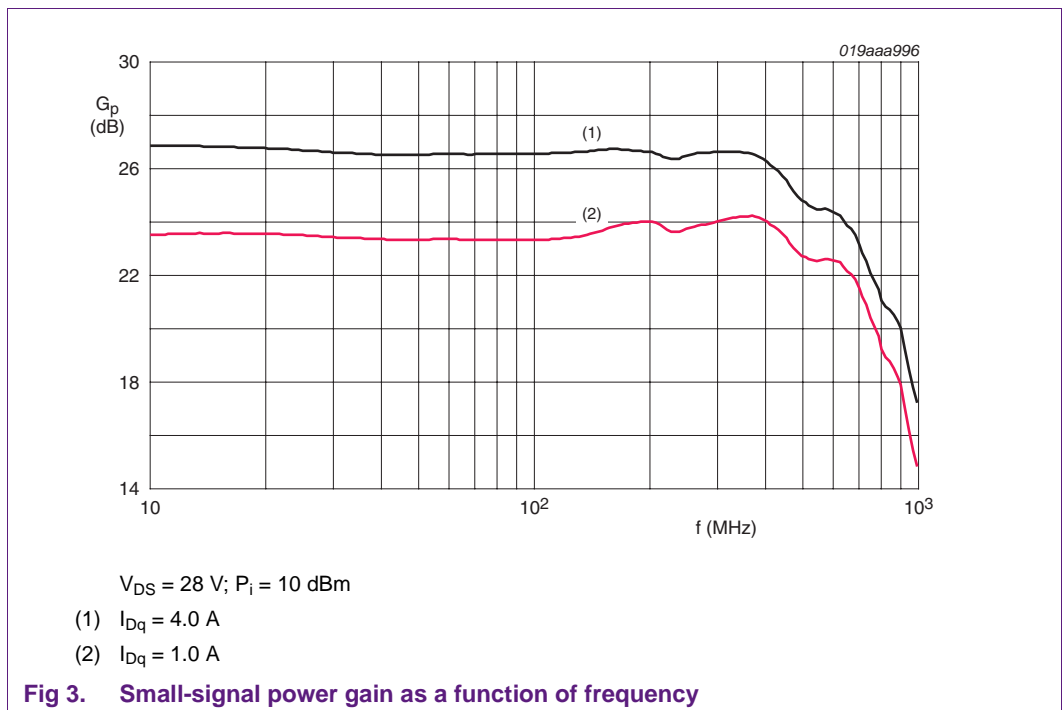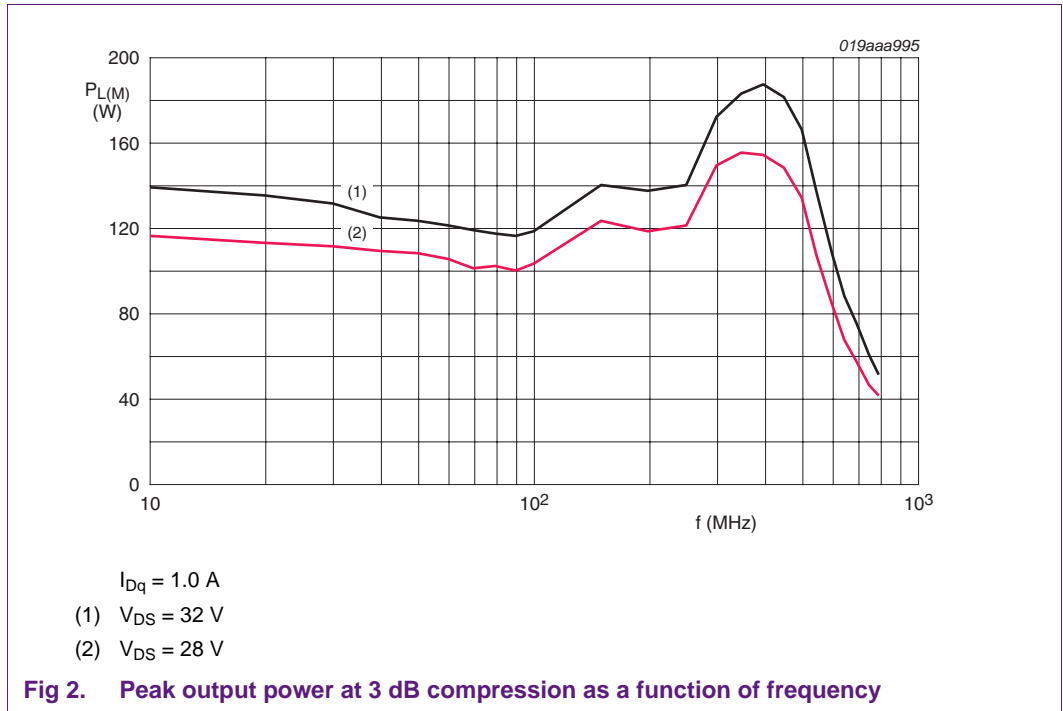

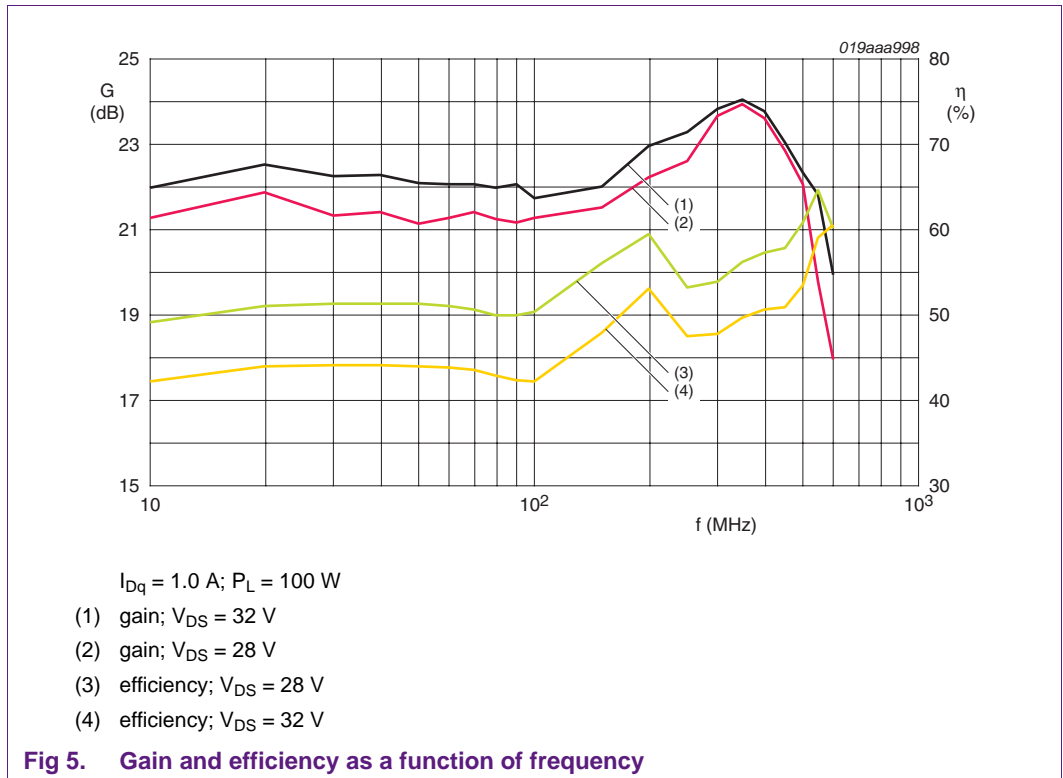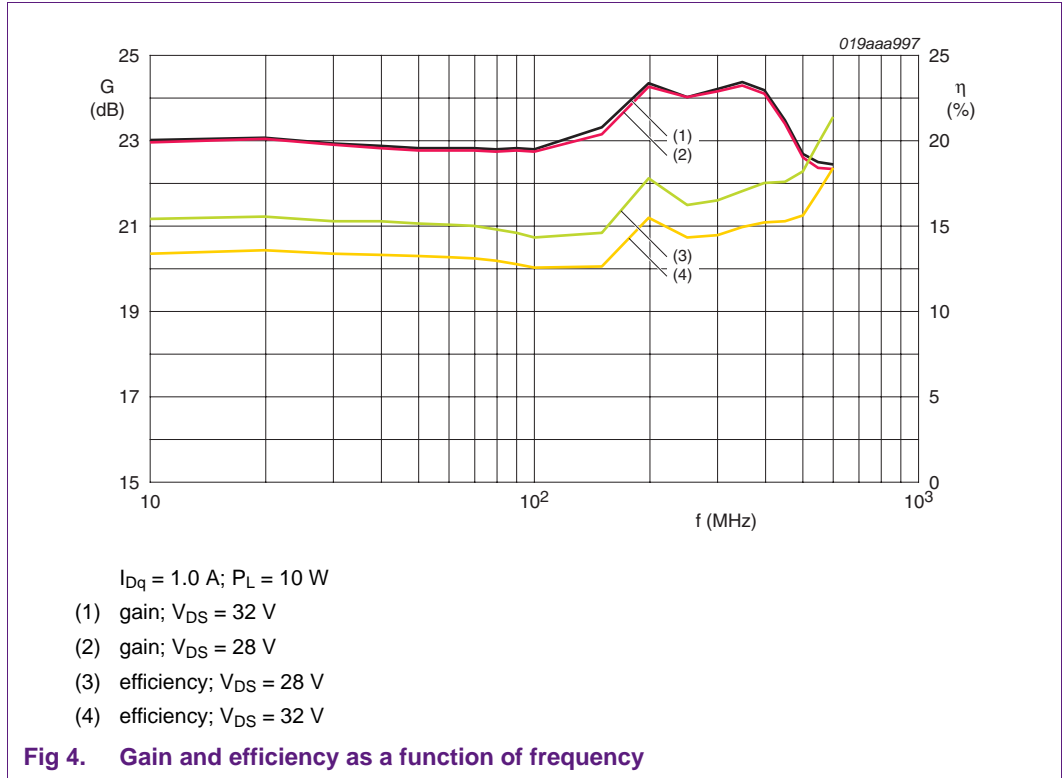

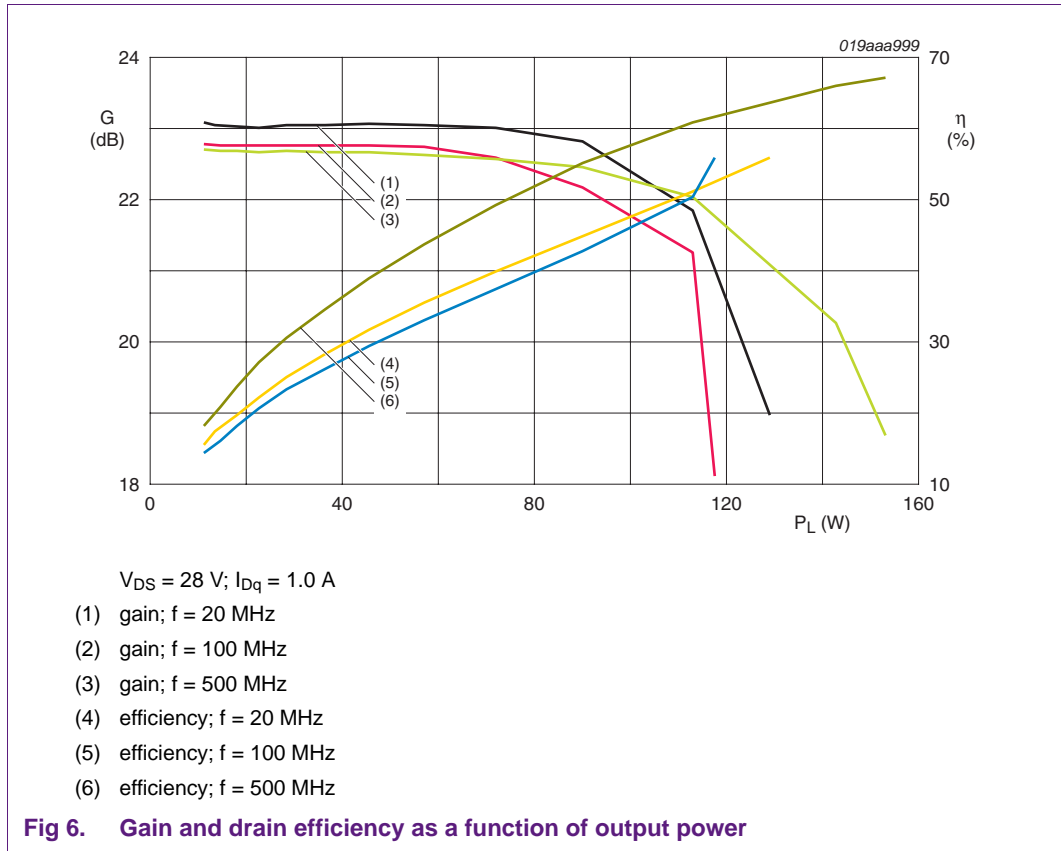


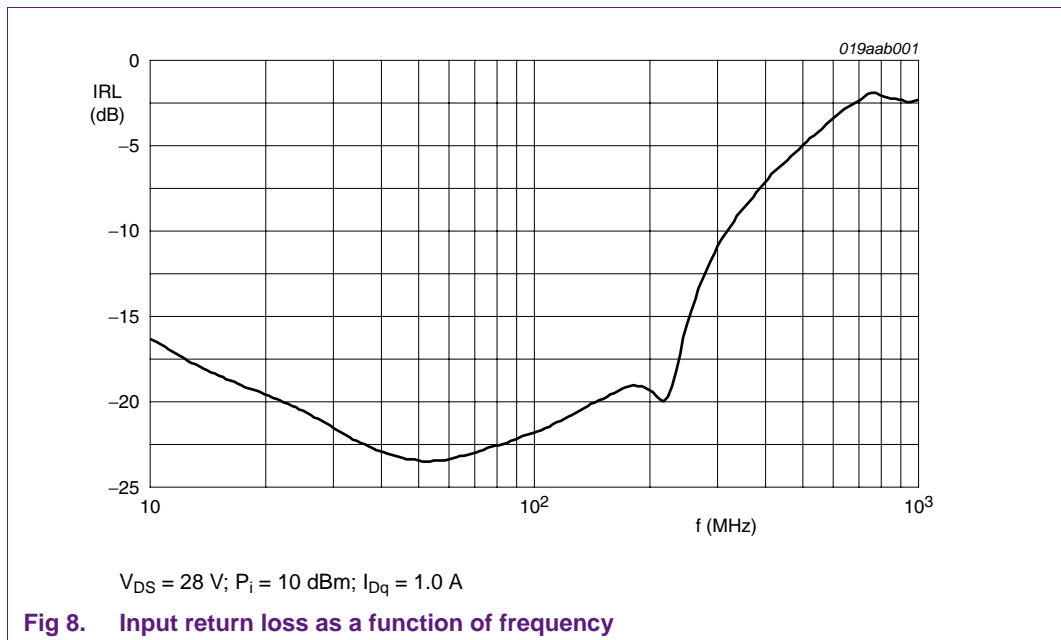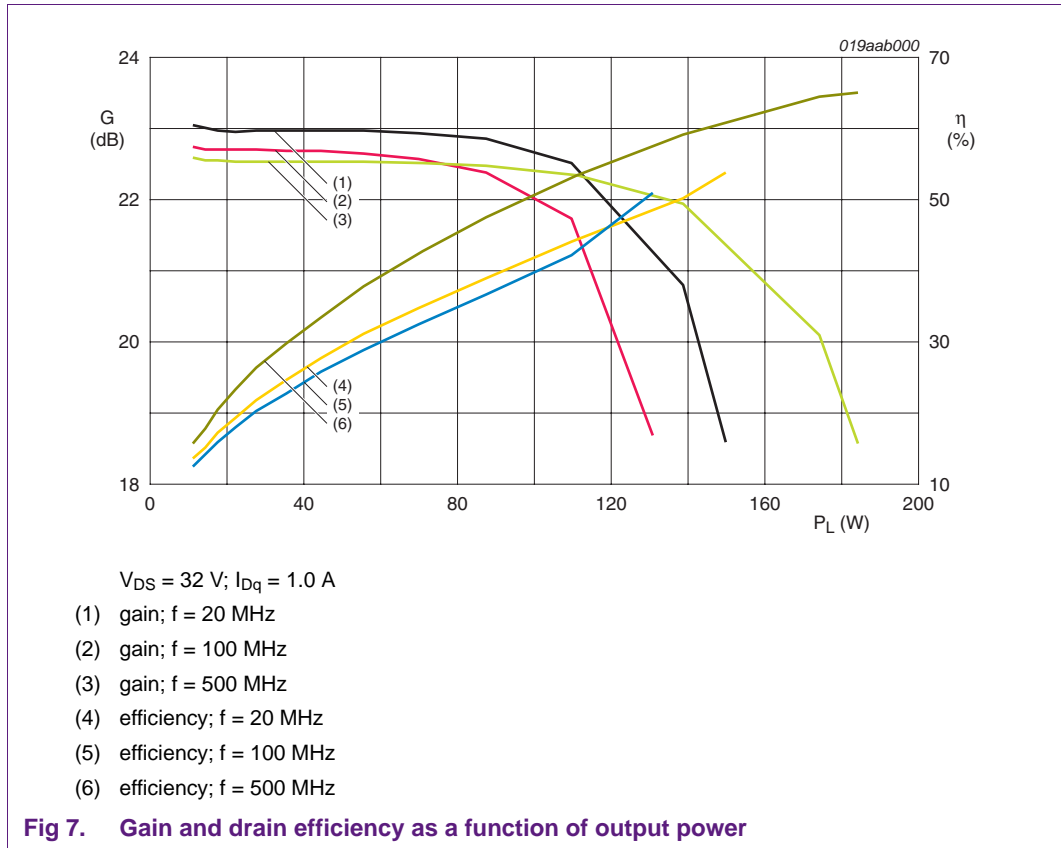


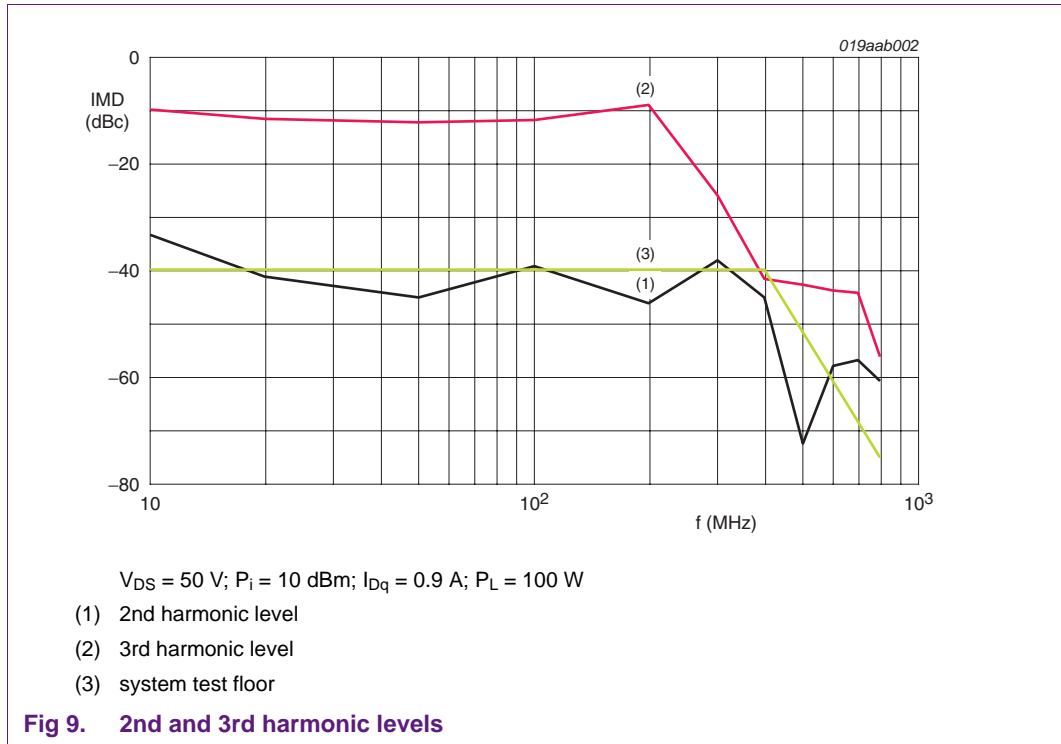

Note that the measured 2nd harmonic levels are at the system test limit, so the actual levels may be significantly lower.

3.2 2-Tone CW

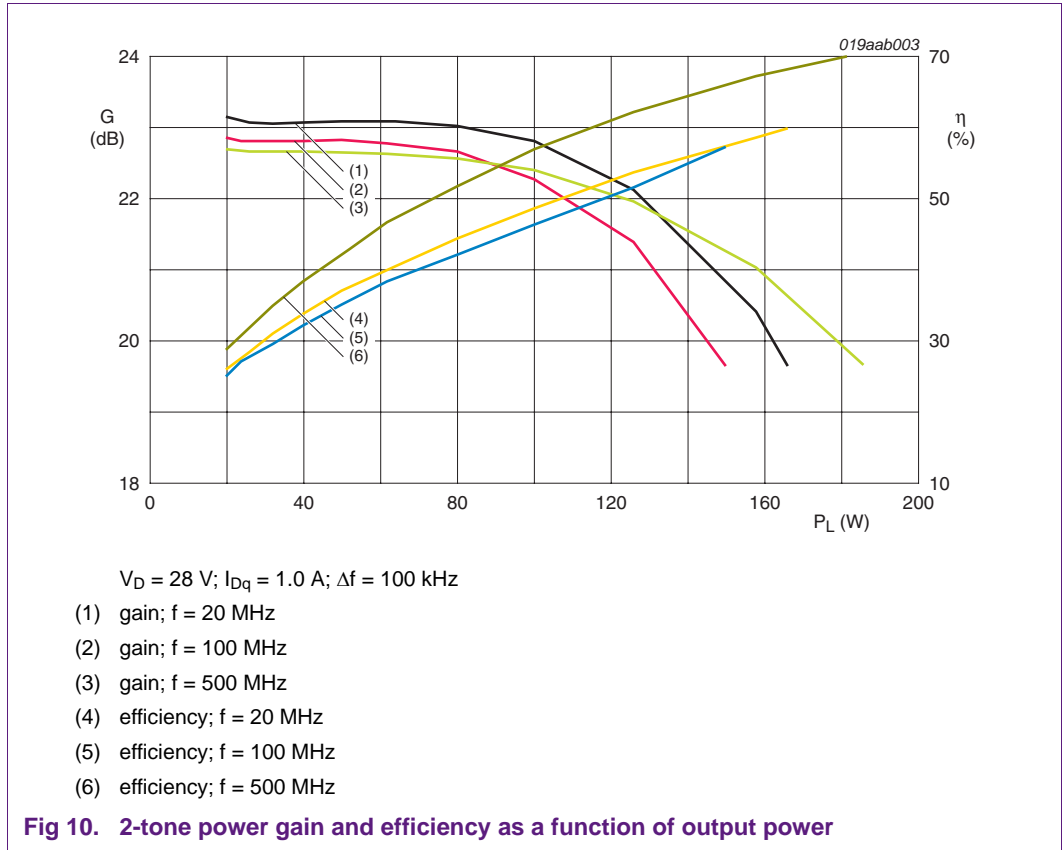

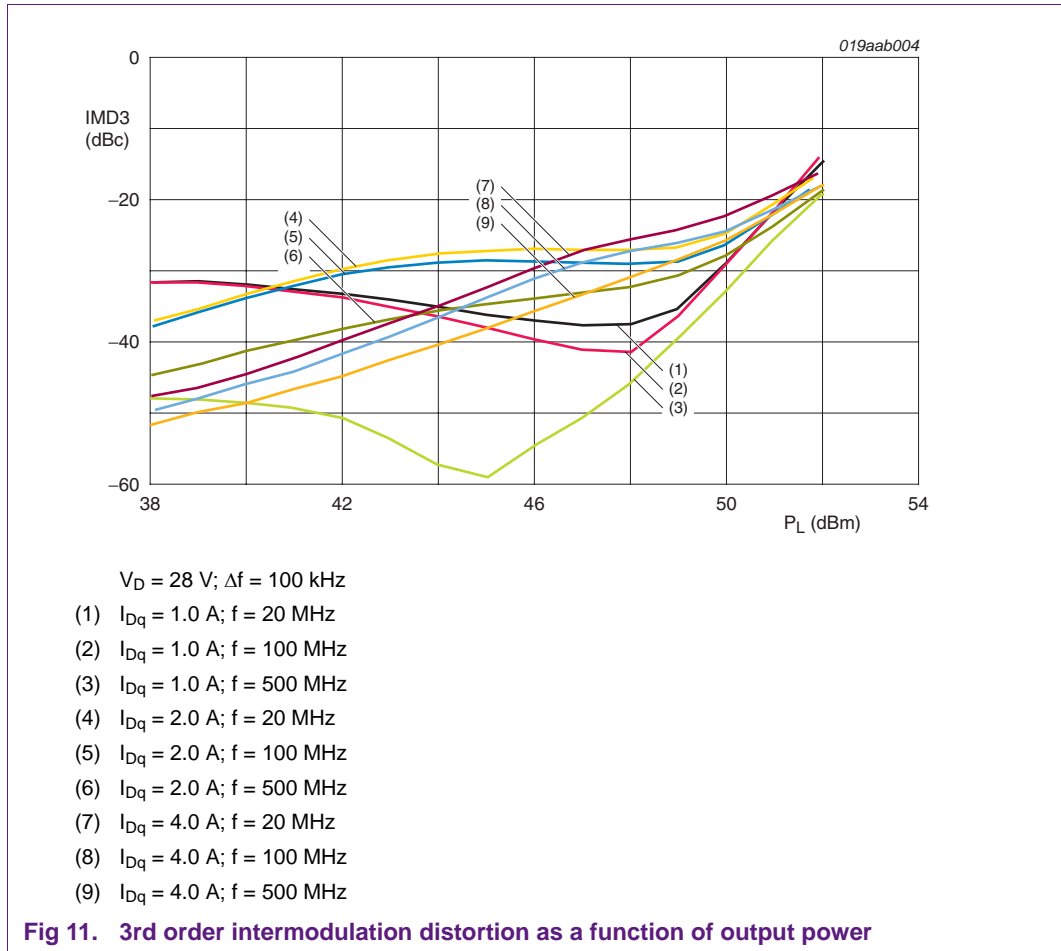

3.3 Alternative input matching

It is possible to improve input return loss at high frequencies by matching the input with a 9:1 transformer constructed with 18 Ω cable, as illustrated in [Figure 12](#). However, this has the undesired effect of reducing gain flatness and low-frequency gain, so it was not used in the design described in this application note.



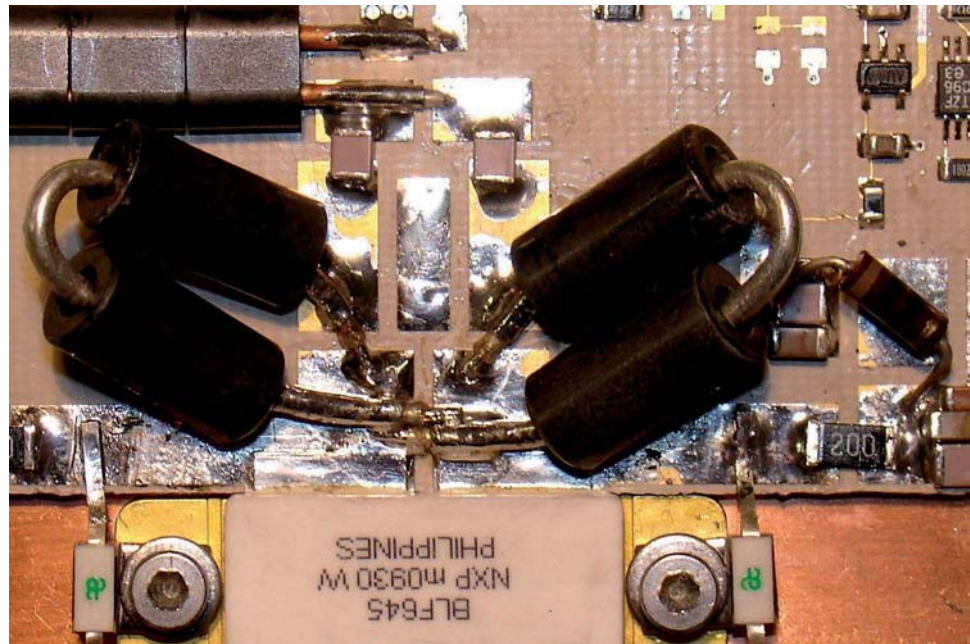
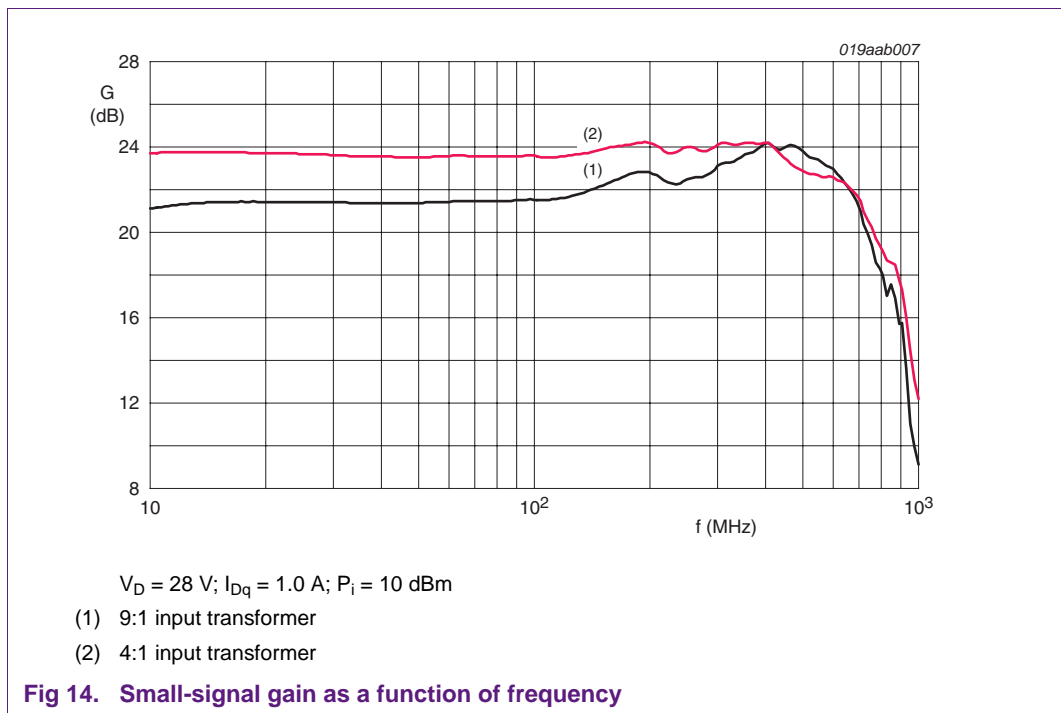


Fig 12. 9:1 input transformer

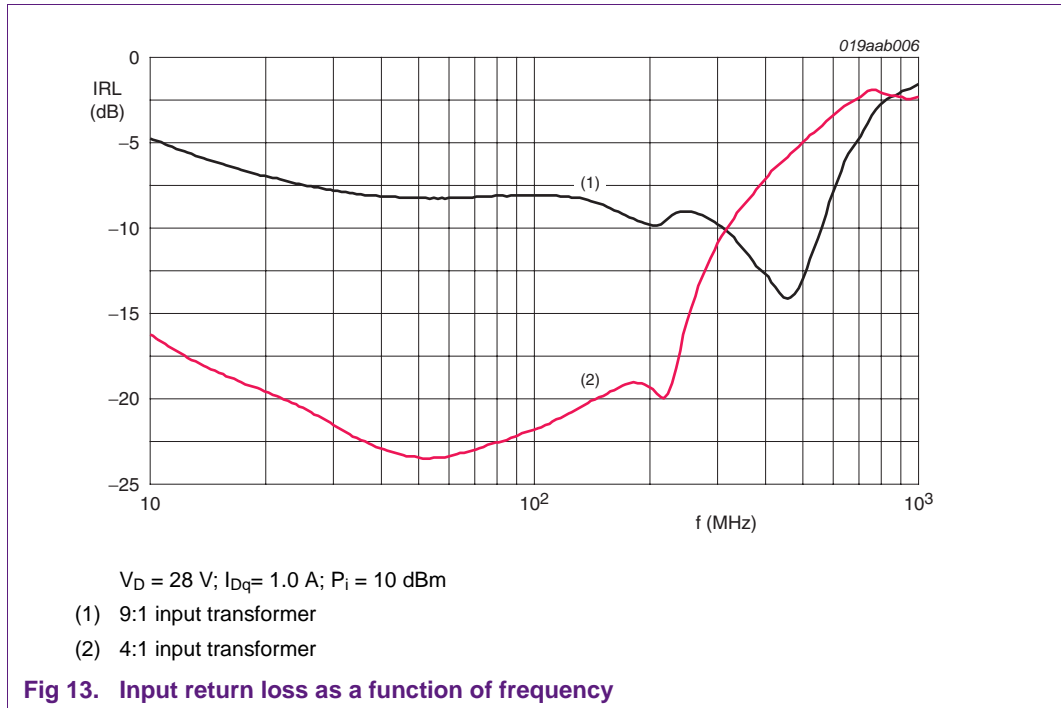

4. PCB information

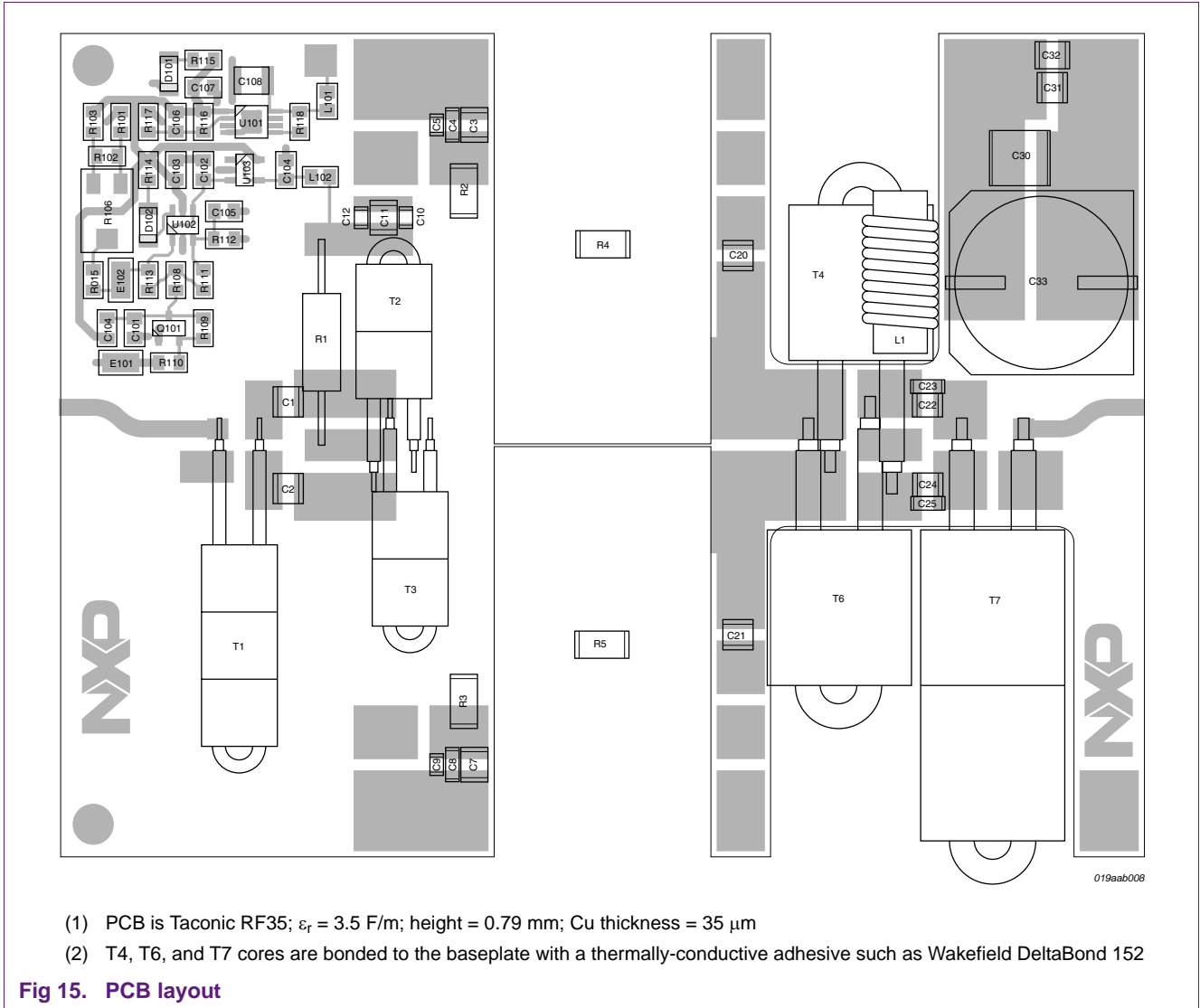

4.1 RF circuit

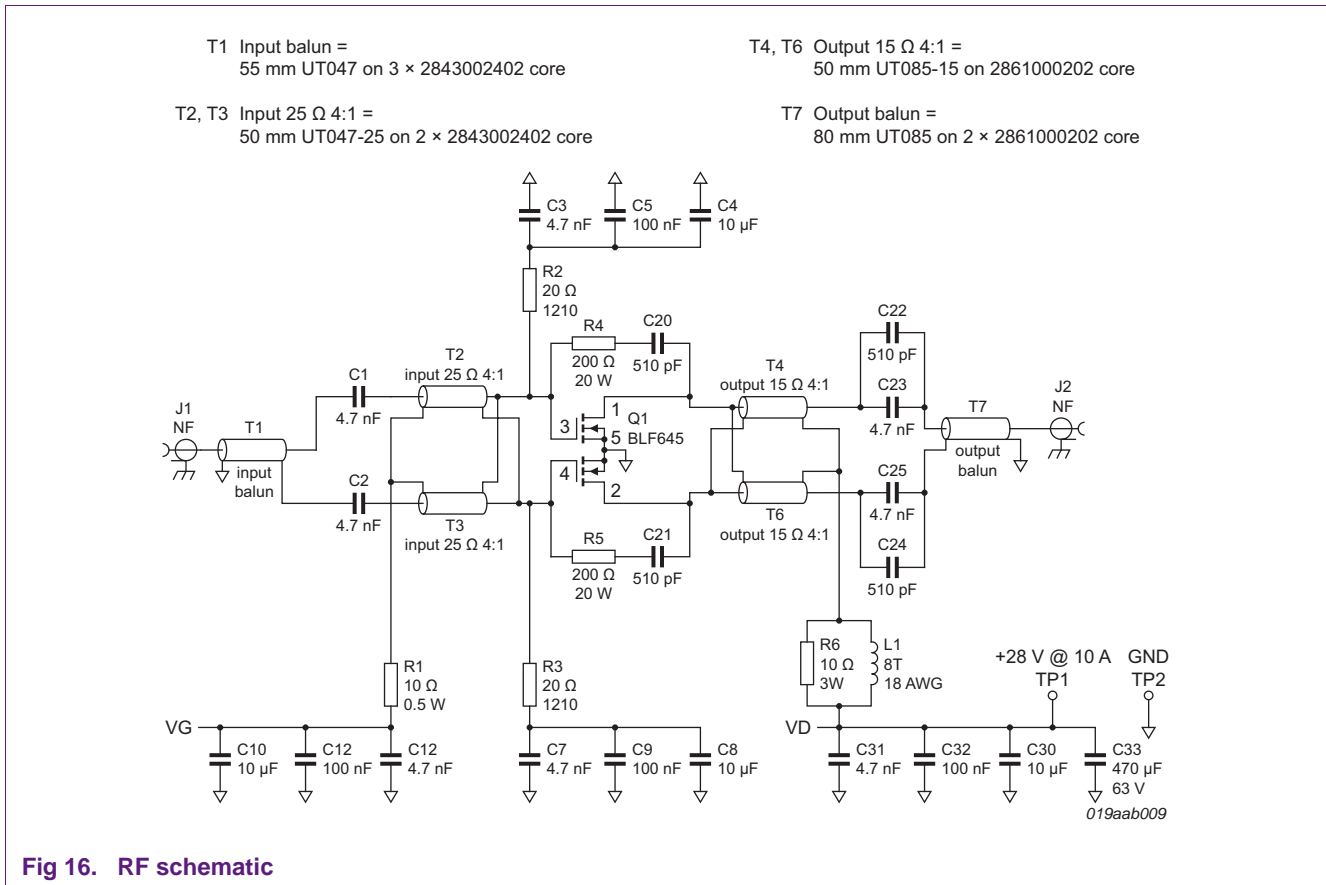


Fig 16. RF schematic

Table 2. RF circuit bill of materials

Component	Description	Value	Remarks
C1, C2, C3, C7, C11, C23, C25, C31	capacitor, 100 V 5 % NP0, 1210	4.7 nF	
C4, C8, C10	capacitor, 10 V 10 % X7R, 1206	10 μF	
C5, C9, C12	capacitor, 50 V 10 % X7R, 0805	100 nF	
C20, C21, C22, C24	capacitor, 500 V 5 % NP0	510 pF	ATC 100B
C30	capacitor, 100 V 10 % X7S, 2220	10 μF	TDK C5750X7S2A106M
C32	capacitor, 100 V 10 % X7R, 1210	100 nF	
C33	capacitor, 63 V, alum electrolytic	470 μF	
L1	8 turns 18AWG on R6		
T1	55 mm UT-047 50 Ω coax + (3) Fair-Rite 2861002402 core		input balun
T2, T3	50 mm UT-047 25 Ω coax + (2) Fair-Rite 2861002402 core		4:1 input transformer
T4, T6	50 mm UT-085C-15 15 Ω coax + Fair-Rite 2861000202 core		4:1 output transformer
T7	80 mm UT-085 50 Ω coax + (2) Fair-Rite 2861000202 core		1:1 output balun

Table 2. RF circuit bill of materials

Component	Description	Value	Remarks
R1	resistor, 5 % CC, 0.5 W	10 Ω	
R2, R3	resistor, 5 % 100 ppm CF, 2010	20 Ω	
R4, R5	resistor, 5 % 20 W flange-mount	200 Ω	ATC FR10300N0200J
R6	resistor, 5 % 3 W MF	10 Ω	

4.2 Bias circuit

Table 3. Bias circuit bill of materials

Component	Description	Value	Remarks
L101, L102	ferrite bead, 200 mA, 0805	1000 Ω	
C101, C102	capacitor, 50 V 10 % X7R, 0805	100 nF	
C105, C106, D102, U102, R111, R112, R114, E101, E102	not installed		
C103, C104, C107	capacitor, 50 V 10 % X7R, 0805	1 μ F	
C108	capacitor, 100 V 10 % X7R, 1210	2.2 μ F	
D101	LED, green, 1206		
U101	voltage regulator		Linear LT3010EMS8E
Q101	transistor NPN 45 V 100 mA GP		NXP Semiconductors BC847B
U103	rail-rail opamp		National LM7321MF
R106	potentiometer, 5 turns cermet	200 Ω	
R113, R117, R118	resistor, 1% 100 ppm CF, 0805	10.0 k Ω	
R104, R115	resistor, 1% 100 ppm CF, 0805	1.10 k Ω	
R105	resistor, 1% 100 ppm CF, 0805	2 k Ω	
R102, R103, R108	resistor, 1% 100 ppm CF, 0805	432 Ω	
R116	resistor, 1% 100 ppm CF, 0805	52.3 k Ω	
R109	resistor, 1% 100 ppm CF, 0805	5.11 k Ω	
R101	resistor, 1% 100 ppm CF, 0805	0.0 Ω	
R110	resistor, 1% 100 ppm CF, 0805	909 Ω	

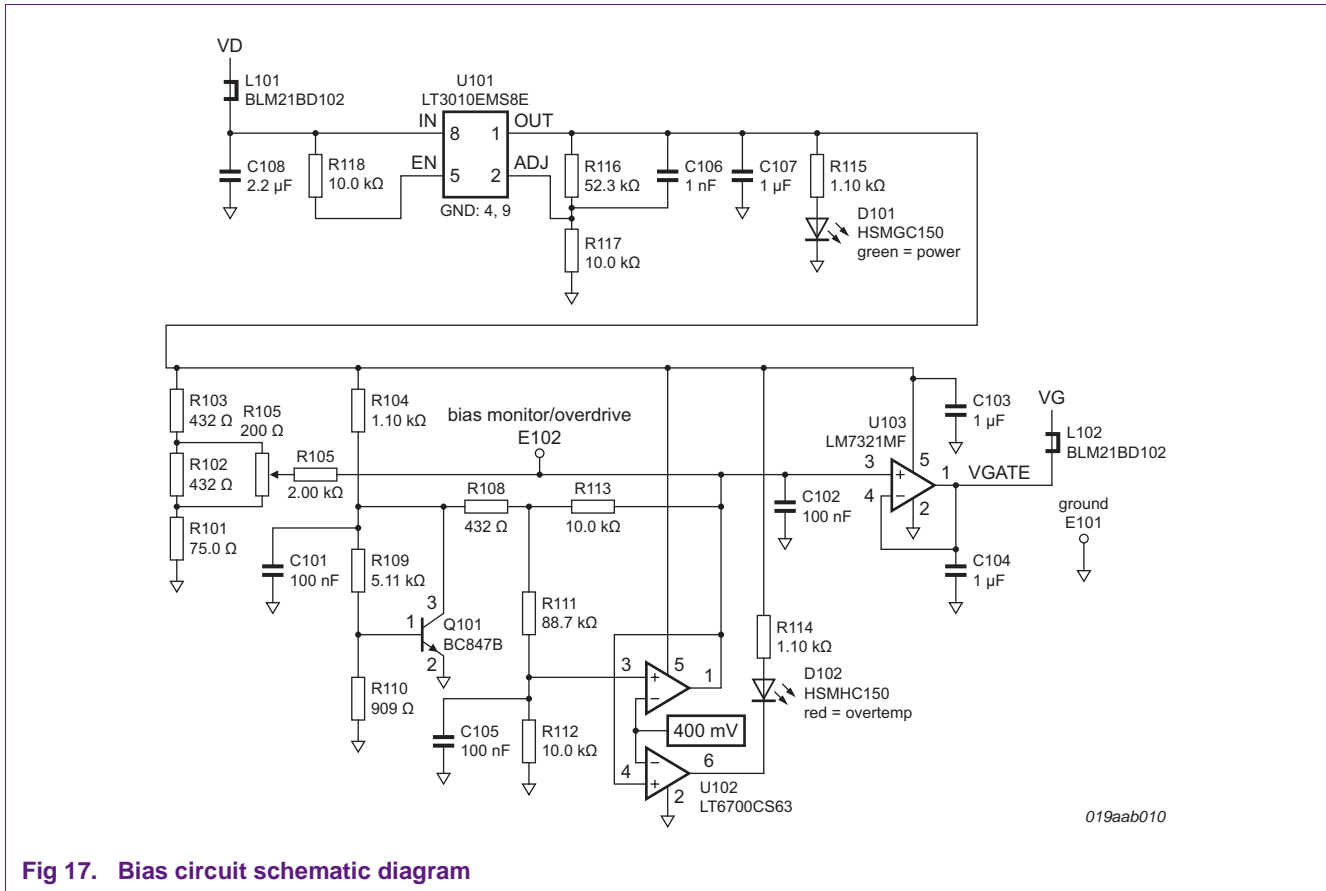


Fig 17. Bias circuit schematic diagram

5. Abbreviations

Table 4. Abbreviations

Acronym	Description
ACPR	Adjacent Channel Power Ratio
CCDF	Complementary Cumulative Distribution Function
DPD	Digital PreDistortion
IBW	Integration BandWidth
LDMOS	Laterally Diffused Metal-Oxide Semiconductor
MOSFET	Metal Oxide Silicon Field Effect Transistor
PAR	Peak-to-Average power Ratio
W-CDMA	Wideband Code Division Multiple Access

6. Legal information

6.1 Definitions

Draft — The document is a draft version only. The content is still under internal review and subject to formal approval, which may result in modifications or additions. NXP Semiconductors does not give any representations or warranties as to the accuracy or completeness of information included herein and shall have no liability for the consequences of use of such information.

6.2 Disclaimers

Limited warranty and liability — Information in this document is believed to be accurate and reliable. However, NXP Semiconductors does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information.

In no event shall NXP Semiconductors be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, NXP Semiconductors' aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the *Terms and conditions of commercial sale* of NXP Semiconductors.

Right to make changes — NXP Semiconductors reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

Suitability for use — NXP Semiconductors products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an NXP Semiconductors product can reasonably be expected to result in personal injury, death or severe property or environmental damage. NXP Semiconductors accepts no liability for inclusion and/or use of NXP Semiconductors products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

Applications — Applications that are described herein for any of these products are for illustrative purposes only. NXP Semiconductors makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using NXP Semiconductors products, and NXP Semiconductors accepts no liability for any assistance with applications or customer product

design. It is customer's sole responsibility to determine whether the NXP Semiconductors product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

NXP Semiconductors does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using NXP Semiconductors products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). NXP does not accept any liability in this respect.

Export control — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from national authorities.

Evaluation products — This product is provided on an "as is" and "with all faults" basis for evaluation purposes only. NXP Semiconductors, its affiliates and their suppliers expressly disclaim all warranties, whether express, implied or statutory, including but not limited to the implied warranties of non-infringement, merchantability and fitness for a particular purpose. The entire risk as to the quality, or arising out of the use or performance, of this product remains with customer.

In no event shall NXP Semiconductors, its affiliates or their suppliers be liable to customer for any special, indirect, consequential, punitive or incidental damages (including without limitation damages for loss of business, business interruption, loss of use, loss of data or information, and the like) arising out of the use of or inability to use the product, whether or not based on tort (including negligence), strict liability, breach of contract, breach of warranty or any other theory, even if advised of the possibility of such damages.

Notwithstanding any damages that customer might incur for any reason whatsoever (including without limitation, all damages referenced above and all direct or general damages), the entire liability of NXP Semiconductors, its affiliates and their suppliers and customer's exclusive remedy for all of the foregoing shall be limited to actual damages incurred by customer based on reasonable reliance up to the greater of the amount actually paid by customer for the product or five dollars (US\$5.00). The foregoing limitations, exclusions and disclaimers shall apply to the maximum extent permitted by applicable law, even if any remedy fails of its essential purpose.

6.3 Trademarks

Notice: All referenced brands, product names, service names and trademarks are the property of their respective owners.

7. Contents

1	Introduction	3
2	Test summary	4
3	RF Performance	5
3.1	1-Tone CW	5
3.2	2-Tone CW	10
3.3	Alternative input matching	12
4	PCB information	14
4.1	RF circuit	15
4.2	Bias circuit	16
5	Abbreviations	17
6	Legal information	18
6.1	Definitions	18
6.2	Disclaimers	18
6.3	Trademarks	18
7	Contents	19

Please be aware that important notices concerning this document and the product(s) described herein, have been included in section 'Legal information'.

© NXP B.V. 2011.

All rights reserved.

For more information, please visit: <http://www.nxp.com>

For sales office addresses, please send an email to: salesaddresses@nxp.com

Date of release: 3 March 2011

Document identifier: AN10953