



AN10954

GreenChip SR TEA1795T dual synchronous rectification driver IC

Rev. 1 — 14 December 2010

Application note

Document information

Info	Content
Keywords	TEA1795T, MOSFET, driver IC, synchronous, rectifier, resonant, converter
Abstract	The TEA1795T is a dual synchronous rectifier driver IC for a resonant converter, which can be used to control the gates of two separated MOSFETs configured as diodes on the secondary side of a resonant converter.



Revision history

Rev	Date	Description
v.1	20101214	First issue

Contact information

For more information, please visit: <http://www.nxp.com>

For sales office addresses, please send an email to: salesaddresses@nxp.com

1. Introduction

The TEA1795T is a dual synchronous rectifier driver IC for a resonant converter. Using this IC the gates of two separated MOSFETs, configured as diodes on the secondary side of a resonant converter, can be controlled. [Figure 1](#) shows the basic configuration of a resonant converter with two SR MOSFETs on the secondary side. The MOSFETs are placed in the ground path of the circuit, making the supply of the driver IC easier.

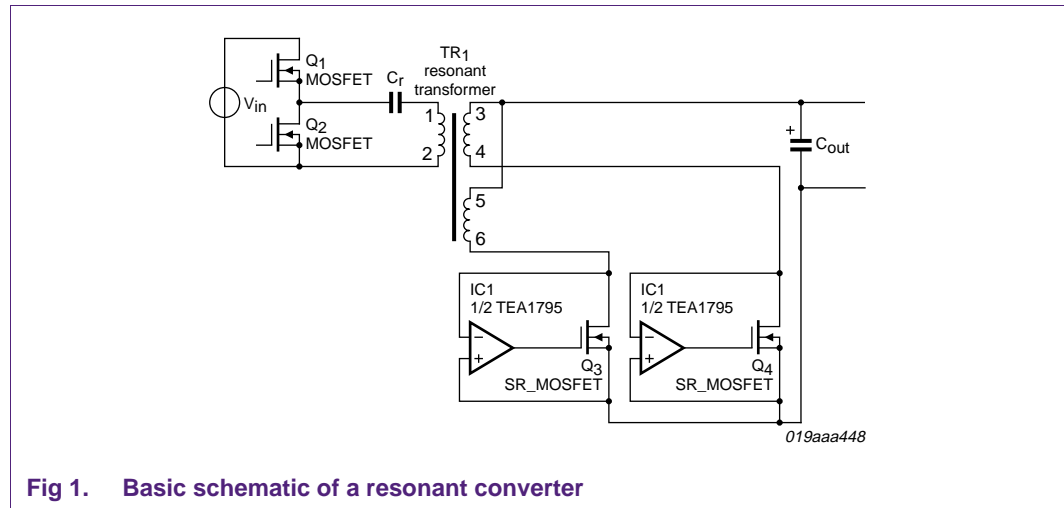


Fig 1. Basic schematic of a resonant converter

2. Quick start-up

This section describes how to start the device quickly. The IC is suitable in a resonant converter and can drive two SR MOSFETs on secondary side (see [Figure 1](#)). The MOSFETs have to be placed with their source at ground level. The IC can drive two MOSFETs independently because there are two drivers in the package.

The drain-source voltage (V_{DS}) is measured separately for each driver to determine what the status of the MOSFET should be (on or off). When a negative current is flowing through the MOSFET or, in other words, the anti-parallel diode is conducting, the MOSFET is turned on. The negative current is detected by a voltage drop over the MOSFET of at least -0.6 V. A comparator with a threshold level of -220 mV becomes HIGH and causes the MOSFET to turn on.

A timer is triggered, which stops the output from changing for a period of 520 ns in order to prevent any form of oscillation. After the blanking time the MOSFET can either be turned off or stay turned on, depending on the value of V_{DS} .

The drain-source voltage must be higher than -12 mV for the MOSFET to turn off. After the MOSFET has been turned off a second timer is triggered and the MOSFET status does not change for a period of 400 ns. Then the MOSFET can be turned on again.

In addition to the levels of -12 mV and -220 mV, a third level is used which regulates the drain-source voltage to -25 mV. This third level is active when V_{DS} is between -25 mV and -12 mV. It was added to speed up the turn-off of the MOSFET (see [Section 7.1.1](#)).

Figure 2 shows the pinning diagram of the TEA1795T. The DSA and SSA pins or the DSB and SSB pins must be connected to the drain and the source of the MOSFET to measure the drain-source voltage. The SSA and SSB pins must be connected as close as possible to the source pins. The DSA and DSB pins must be connected as close as possible to the drain pins. This prevents wrong measurement values being obtained because of the voltage drop over the tracks and the layout of the Printed-Circuit Board (PCB). The outputs of the drivers are pins GDA and GDB, which have to be connected to the gates of the MOSFETs.

The supply pin of the IC is V_{CC}. It can be connected to an output voltage of the resonant converter because of its wide supply voltage range (8.5 V to 38 V).

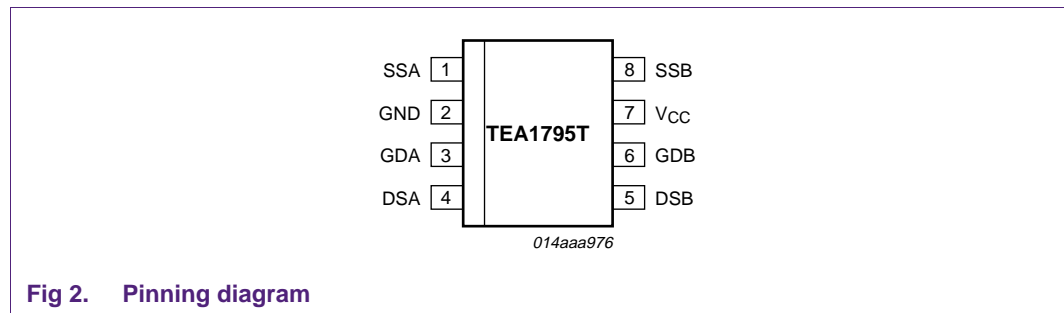


Fig 2. Pinning diagram

Table 1. Pin descriptions

Symbol	Pin	Description
SSA	1	source sense input MOSFET A
GND	2	ground
GDA	3	gate driver output MOSFET A
DSA	4	drain sense input for synchronous timing MOSFET A
DSB	5	drain sense input for synchronous timing MOSFET B
GDB	6	gate driver output MOSFET B
V _{CC}	7	supply voltage
SSB	8	source sense input MOSFET B

Careful attention must be paid to the layout of the PCB to get the best possible results. Tracks from drain to DSA (or DSB) and from source to SSA (or SSB) form a loop which must be as short as possible. This can be achieved by routing them as closely as possible and parallel to each other. Alternatively, they can be put above each other in a dual-layer PCB (see Figure 23). A filter can be added to the system to improve the design, depending on the MOSFET used and the mode of operation (CCM or DCM) (see Section 7.1.2 and Section 7.2.1).

3. Resonant converter versus flyback

The TEA1795T has been developed for a resonant converter supply. It is derived from the TEA1761, a MOSFET driver IC for flyback SR. The main difference is the blanking time after turn-on.

The differences between a resonant converter supply and a flyback supply are:

- The secondary current does not have to start at the beginning of a primary switching transition
- The current increases and decreases (sinusoidally)
- The switching frequency can be much higher
- The dI/dt of the current is much higher

In a flyback converter the secondary phase starts when the current through the switch (diode, MOSFET) is at its maximum. This is not the case in a resonant converter, where the current starts at 0 A and rises until it has reached its maximum. Then it decreases again. The overall shape of the current is more or less sinusoidal (see [Figure 3](#)).

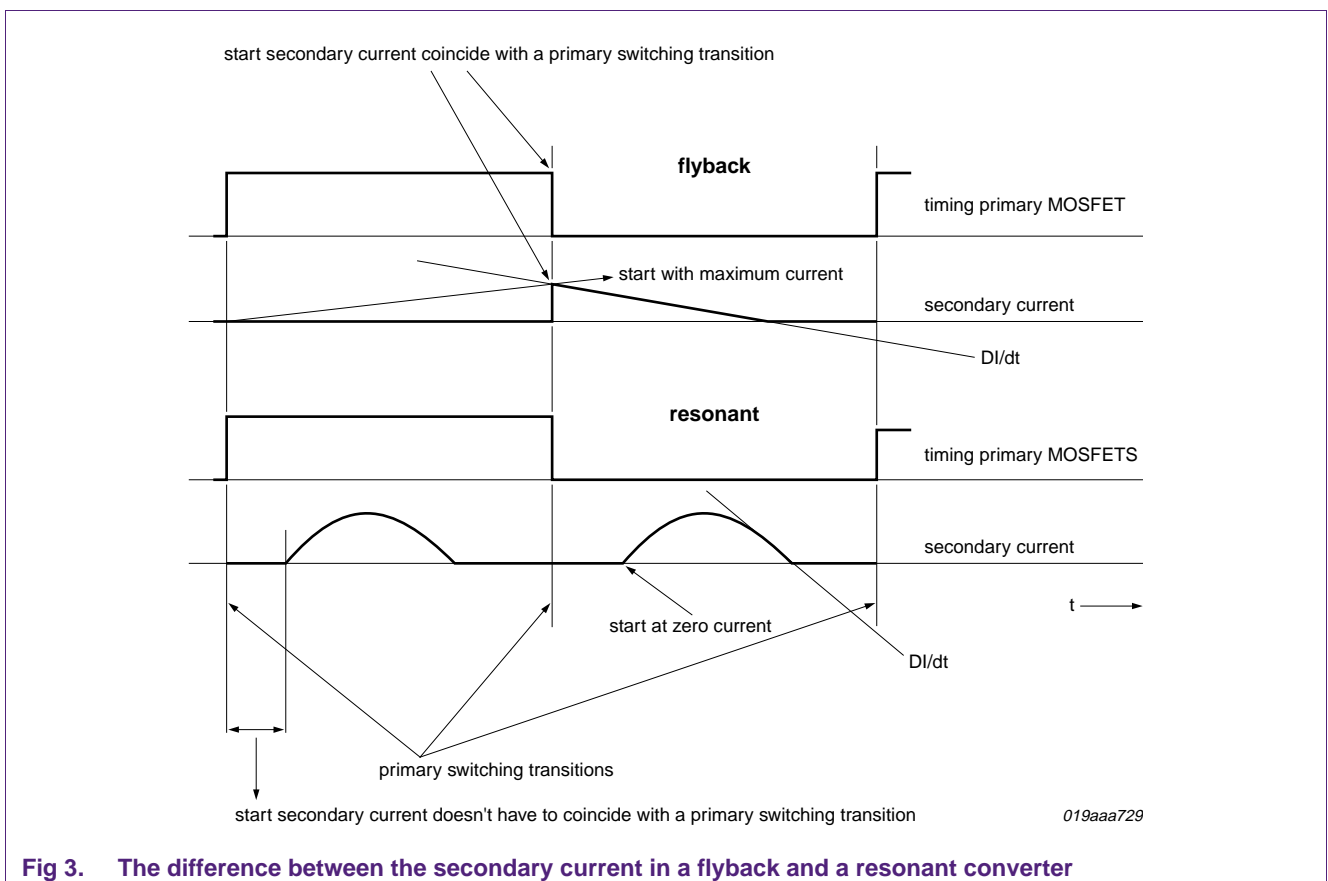


Fig 3. The difference between the secondary current in a flyback and a resonant converter

The current does not have to start at the beginning of a primary switching transition. This makes the timing more vulnerable to incorrect sensing, causing the SR-MOSFET to switch at the wrong moment.

4. Diodes as rectifiers

In older designs, Schottky diodes were used to rectify the current on the secondary side. The advantages of Schottky diodes compared to PN-diodes are:

- Lower voltage drop
- Less reverse recovery

The Schottky diodes also have a few disadvantages:

- Higher parasitic capacitance
- Reverse leakage current
- Not available for higher output voltages

Two modes can be distinguished in a resonant converter:

- Continuous Conduction Mode (CCM)
- Discontinuous Conduction Mode (DCM)

For DCM the secondary current can be modeled using [Equation 1](#):

$$\begin{cases} I_{sec} = I_{amp} \times \left| \sin(\omega_1 \times (t - t_{no})) \right| \wedge \frac{k \times \pi}{\omega_1} \leq t \leq \frac{(k+1) \times \pi}{\omega_1} \wedge k \in N \\ I_{sec} = 0 \wedge \frac{(k+1) \times \pi}{\omega_1} \leq t \leq \frac{(k+1) \times \pi}{\omega_1} + t_{no} \end{cases} \quad (1)$$

Where:

- I_{amp} is amplitude of the current
- ω_1 is the radial frequency
- I_{sec} is the secondary current
- t_{no} is the time that the secondary current is zero (see [Figure 4](#))

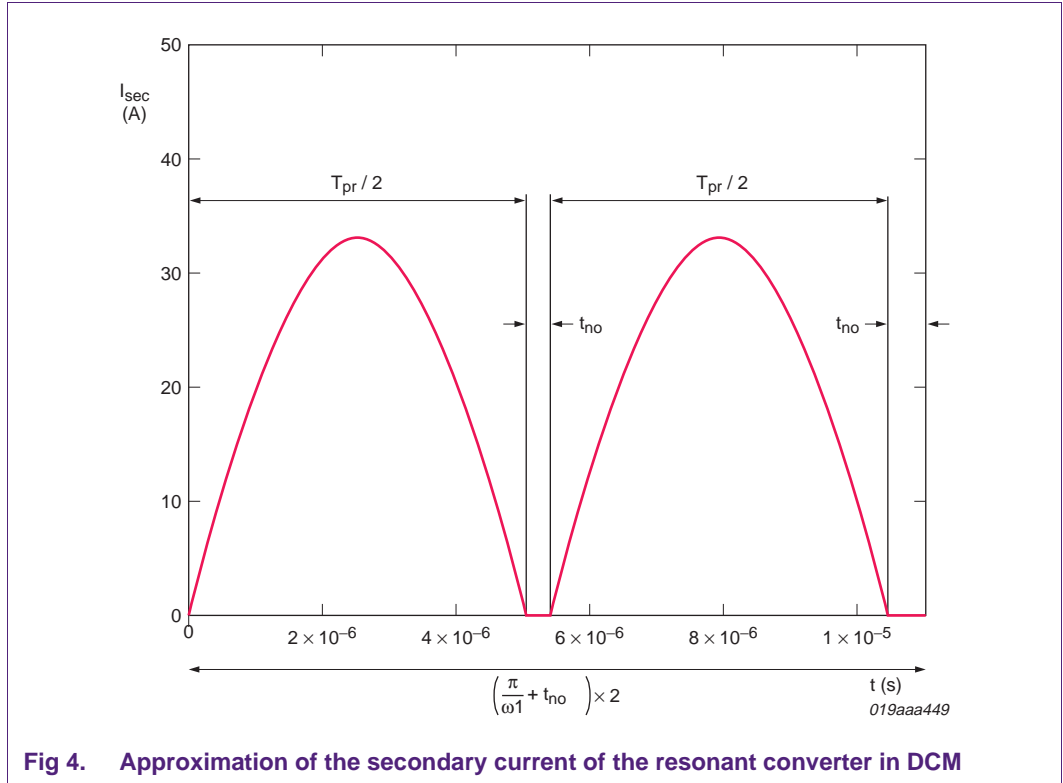


Fig 4. Approximation of the secondary current of the resonant converter in DCM

For I_{amp} [Equation 2](#) and [Equation 3](#) can also be written:

$$\begin{aligned}
 P_O &= V_O \times \frac{I}{\frac{t_{pr}}{2} + t_{no}} \times \int_0^{\frac{t_{pr}}{2}} I_{amp} \times \sin(\omega_1 \times t) \\
 &= \frac{2}{\pi} \times V_O \times I_{amp} \times \frac{I}{1 + 2 \times \frac{t_{no}}{t_{pr}}}
 \end{aligned}
 \tag{2}$$

or

$$I_{amp} = \left(1 + 2 \times \frac{t_{no}}{t_{pr}}\right) \times \frac{\pi}{2} \times \frac{P_O}{V_O}
 \tag{3}$$

Where:

- $t_{pr} = 2 \times \pi / \omega_1$
- P_O is the output power
- V_O is the output voltage

The voltage drop of a Schottky diode can be calculated with [Equation 4](#):

$$V_f(I_d) = V_{f0} + R_d \times I_d
 \tag{4}$$

Finally, the total dissipation in the secondary rectifiers taking the current as shown in [Figure 4](#) can be calculated with [Equation 5](#):

$$P_{tot} = \left(\frac{2}{\pi} \times V_F \times I_{amp} + \frac{1}{2} \times R_d \times I_{amp}^2 \right) \times \frac{I}{I + 2 \times \frac{t_{no}}{t_{pr}}} \quad (5)$$

By replacing I_{amp} with [Equation 3](#) the power dissipation changes to [Equation 6](#):

$$P_{tot} = \left(V_F \times \frac{P_O}{V_O} + \frac{\pi^2}{8} \times R_d \times \frac{P_O^2}{V_O^2} \times \left(I + 2 \times \frac{t_{no}}{t_{pr}} \right) \right) \quad (6)$$

Equations for the CCM case can be created as equivalents of the DCM case equations. In [Section 11.2](#) the CCM case is presented in detail. Here only the results are shown.

Example:

- $t_{no} = 500 \text{ ns}$
- $t_{th0} = 500 \text{ ns}$
- $P_O = 240 \text{ W}$
- $V_O = 12 \text{ V}$
- $R_d = 5 \text{ m}\Omega$
- $V_F = 280 \text{ mV}$

For CCM the dissipation in the diodes equals: 7.925 W. For DCM the dissipation equals: 8.314 W.

5. MOSFETs as rectifiers

Ideally if the diodes are replaced by SR-MOSFETs the dissipation in the DCM case is reduced to:

$$P_{tot} = \frac{1}{2} \times R_{DSon} \times I_{amp}^2 \times \frac{I}{I + 2 \times \frac{t_{no}}{t_{pr}}} = \frac{\pi^2}{8} \times R_{DSon} \times \frac{P_O^2}{V_O^2} \times \left(I + 2 \times \frac{t_{no}}{t_{pr}} \right) \quad (7)$$

Example for DCM mode:

- $V_F = 280 \text{ mV}$
- $R_d = 5 \text{ m}\Omega$
- $P_O = 240 \text{ W}$
- $t_{no} = 500 \text{ ns}$
- $t_{pr} = 10 \text{ }\mu\text{s}$ (keeping in mind that t_{pr} is not the period time but $t_{pr} + 2 \times t_{no}$ is)
- $V_O = 12 \text{ V}$
- $R_{DSon} = 4 \text{ m}\Omega$

With Schottky diodes, the dissipation will be 8.314 W and with MOSFETS 2.171 W. Compared to the 240 W output power this is an improvement of approximately 2.6 % (going from 3.5 % to 0.91 %). For CCM mode with $t_{\text{thllo}} = 500 \text{ ns}$ and $t_{\text{sw}} = 10 \text{ }\mu\text{s}$, the values are respectively 7.925 W (3.3 %) and 1.86 W (0.78 %). This is an improvement of 2.5 %.

Remark: An additional control IC is needed to turn on and turn off the MOSFET at the right time (see [Section 6](#)).

Remark: When the MOSFET is not conducting, it behaves like a diode, so losses are higher (see [Equation 28](#)).

6. Basic functionality of the TEA1795T

When using MOSFETs instead of diodes, the MOSFET has to be turned on when current is flowing through it. It has to be turned off when there is no current flowing through it. The TEA1795T IC has been developed to realize these functions. [Section 6.1](#) describes the turn-on function. [Section 6.2](#) describes the turn-off function.

6.1 The turn-on function

It is easy to detect if current is flowing through the MOSFET. A MOSFET that is not conducting (turned on) behaves like a diode. When current is flowing through the diode the voltage drop is above 0.5 V. A level of -220 mV has been built in in the IC to which this voltage can be compared. When this level is exceeded the TEA1795 charges the gate of the MOSFET and turns it on. Depending on the current flowing through the diode, the voltage drops to $V_{DS} = I_{DS} \times R_{DSon}$.

6.2 The turn-off function

A second level has been built in to turn the MOSFET off again. When the drain-source voltage drop is less than 12 mV, meaning that the current through the MOSFET is below a certain level (see [Equation 8](#), the MOSFET is turned off again.

$$I_{DS_off} \leq \frac{12 \text{ mV}}{R_{DSon}} \tag{8}$$

Example: if the current is behaving as described in [Equation 2](#) and $R_{DSon} = 4 \text{ m}\Omega$, then $I_{DS_off} = 3 \text{ A}$.

Summary: The MOSFET is turned on at $V_{DS} < -220 \text{ mV}$. The MOSFET is turned off at $V_{DS} > -12 \text{ mV}$.

The pin connections are shown in [Figure 2](#). The voltage drop over the MOSFET is measured differentially (driver A: DSA (pin 4) – SSA (pin 1); driver B DSB (pin 5) – SSB (pin 8)). The outputs of the drivers are GDA for driver A and GDB for driver B. Finally, two pins are left, the GND (pin 2) and the positive connection of the power supply (V_{CC} , pin 7). In [Table 1](#) the pinning information is listed.

7. Improving the system

The following improvements have to do with the turn-on and turn-off moments of the MOSFETs:

- Turn-on:
 - Immediate turn-off after turn-on
 - false turn-on
 - parasitic turn-on
- Turn-off:
 - premature turn-off
 - turn-off is too late
 - false turn-off


7.1 Turn-on

7.1.1 Immediate turn-off after turn-on

A blanking time has been built in to prevent the MOSFET from turning off immediately after it has been turned on, because the drain-source voltage is still above the turn-off level (-12 mV). This blanking time is typically 520 ns. If, after 520 ns the value is above the regulation level (-25 mV) or the turn-off level, the gate is discharged until the regulation level is reached or the MOSFET is turned off.


The disadvantage of the blanking time feature is that if the current becomes zero during this blanking time it reverses and causes additional losses. If, after the blanking time, the drain-source voltage is still below the regulation level, the gate voltage is lowered until the drain-source voltage equals regulation level.

The regulation level mentioned above is added to the IC. When the input voltage is higher than this regulation level but lower than the turn-off level the IC regulates the drain-source voltage to -25 mV by controlling the gate voltage of the MOSFET. The MOSFET is normally used in its linear region, but by lowering the gate voltage to just above the threshold level the MOSFET enters its saturation region. This prevents the MOSFET turning off too late when the turn-off level is reached. To turn off the MOSFET, the gate voltage only needs to decrease slightly, instead of requiring a discharge from a high gate voltage to the threshold voltage. [Figure 5](#) shows the decision levels of the TEA1795T.

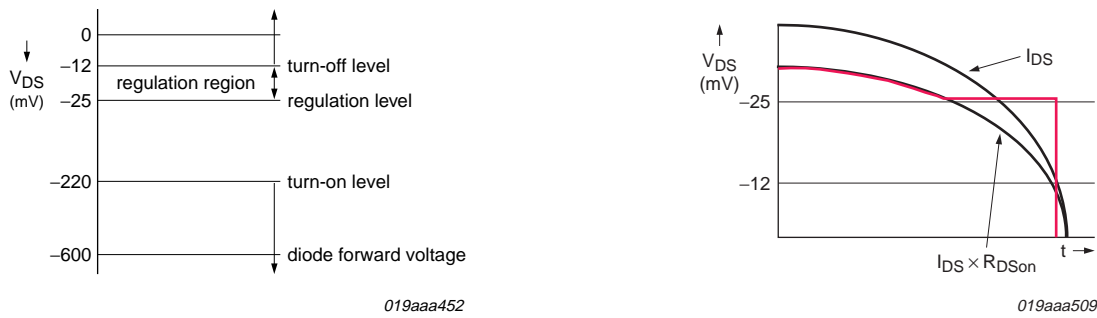

a. turn-off, regulation and turn-on levels[1]

b. Drain-source voltage[2]

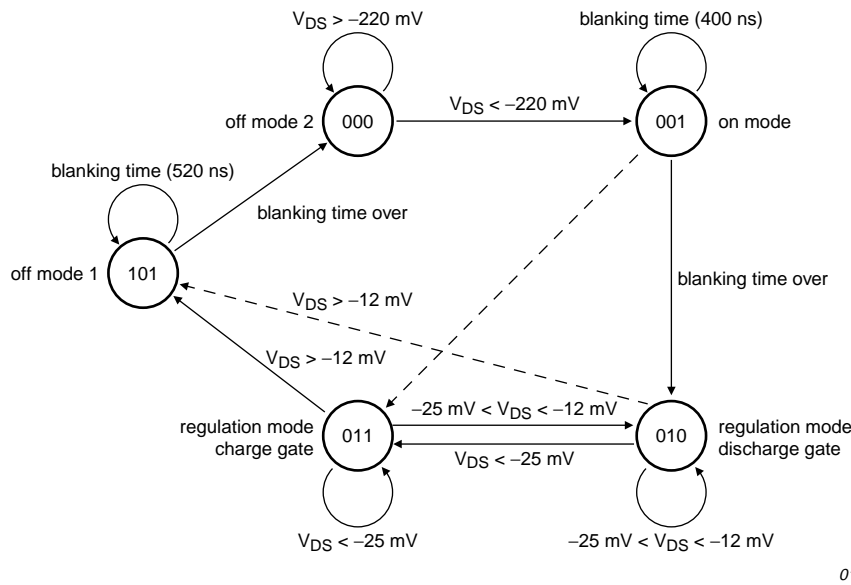

c. TEA1795T state diagram[3]

- (1) Three levels are built in: turn-on level (-220 mV), turn-off level (-12 mV) and regulation level (-25 mV).
- (2) If the drain-source voltage is lower than -25 mV the gate is totally charged (Linear mode). As soon as the drain-source voltage increases to above -25 mV the gate is discharged until the drain-source voltage is -25 mV again (Saturation mode). Above -12 mV the gate is fully discharged (off mode)
- (3) 000, 001, 010, 011, and 101 are the five states.

Fig 5. The decision matrix of the TEA1795

The regulation level means that between this level (-25 mV) and the turn-off level (-12 mV) the IC stabilizes V_{DS} to -25 mV by charging or discharging the gate. When the current becomes too low to keep V_{DS} at -25 mV the drain voltage exceeds -12 mV and the MOSFET is turned off very quickly. If current is still present, the MOSFET behaves like a diode again and the voltage decreases to below -0.5 V.

7.1.2 False turn-on

Ideally, the MOSFET is turned on and off at the zero crossing of the current. However, some parasitic components have a negative impact on the behavior of the synchronous rectifier. The secondary inductance and the drain-source capacitance form a resonant network which causes some oscillation of the drain-source voltage during the switching of one of the MOSFETs (primary or secondary). [Figure 6](#) shows the schematic.


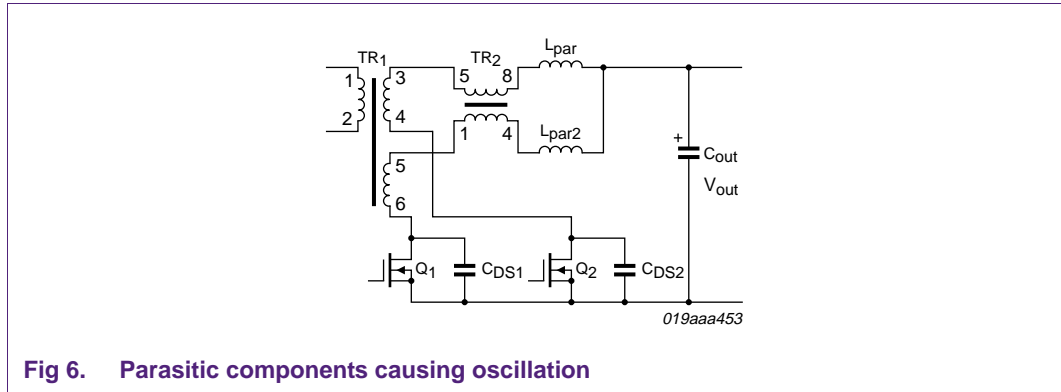


Fig 6. Parasitic components causing oscillation

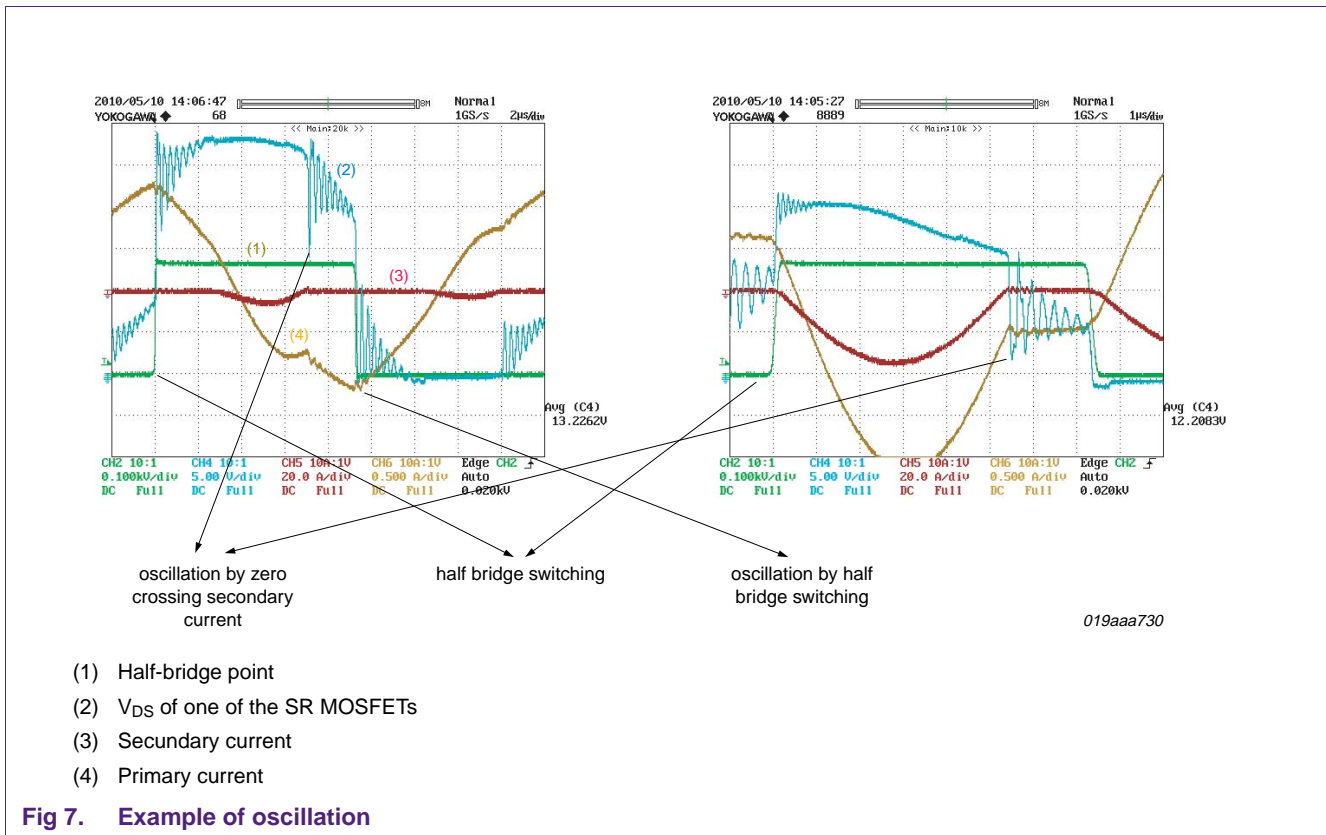[Figure 7](#) shows examples of oscillations. When the voltage of the drain-source decreases below -220 mV false triggering of the MOSFET occurs, causing unstable behavior.



- (1) Half-bridge point
- (2) V_{DS} of one of the SR MOSFETs
- (3) Secondary current
- (4) Primary current

Fig 7. Example of oscillation

An RC-filter is placed in front of the input of the driver IC to filter out the high frequency component in the drain-source voltage (see [Figure 11](#)). This prevents false triggering of the MOSFET.

The voltage difference between pin 1 and pin 4 (and also between pin 5 and pin 8) for a step from V_I to 0 V can be calculated with [Equation 9](#):

$$V_{C1}(t) = V_I \times \exp\left(-\frac{t}{R \times C}\right) \tag{9}$$


Where:

- $V_{C1}(t) = 0.1 V_I$ (= 10 % of the end value)
- $t = 100 \text{ ns}$
- $R = 3.9 \text{ k}\Omega$

The result is a capacitor value (C) of 10 pF.

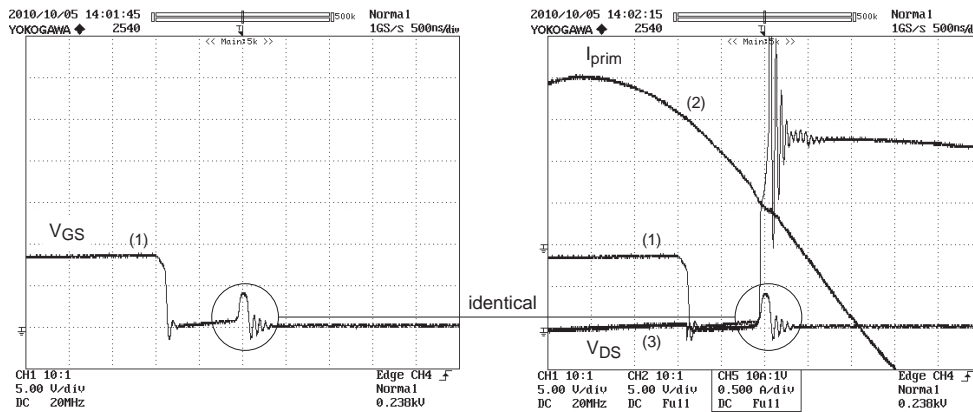7.1.3 Parasitic turn-on

When the drain-source voltage ([Figure 8](#), line 3) rapidly increases, the gate voltage ([Figure 8](#), line 1) is lifted to the threshold level of the MOSFET, causing it to turn on. This is caused by the weak sinking capability of the driver output during the transition from Regulation mode to the Off mode of the IC (see [Figure 5](#)). During the regulation mode the sinking capability is taken care by a 24Ω MOSFET. The 1Ω MOSFET is only available in the off-mode. It takes time to turn on this 1Ω MOSFET, because of the internal delay. When this MOSFET is conducting, the gate of the SR MOSFET is discharged again. Therefore a spike is visible on the gate during the transition.



019aaa885

The gate voltage of one of the SR MOSFETs (left). It shows a small pulse after the MOSFET is turned off. The small pulse is caused by fast rising of the drain-source voltage (right).

- (1) Gate source voltage.
- (2) Primary current.
- (3) Drain-source voltage over the primary MOSFET.

Fig 8. Parasitic turn-on

7.2 Turn-off

7.2.1 Premature turn-off

The drain-source voltage is measured between two points of the PCB. The impedance between these points incorporates the resistance of the track, the MOSFET and inductance L_{par} . L_{par2} is also part of the parasitic inductance, but it does not have any impact on the measurement (see [Figure 9](#)).

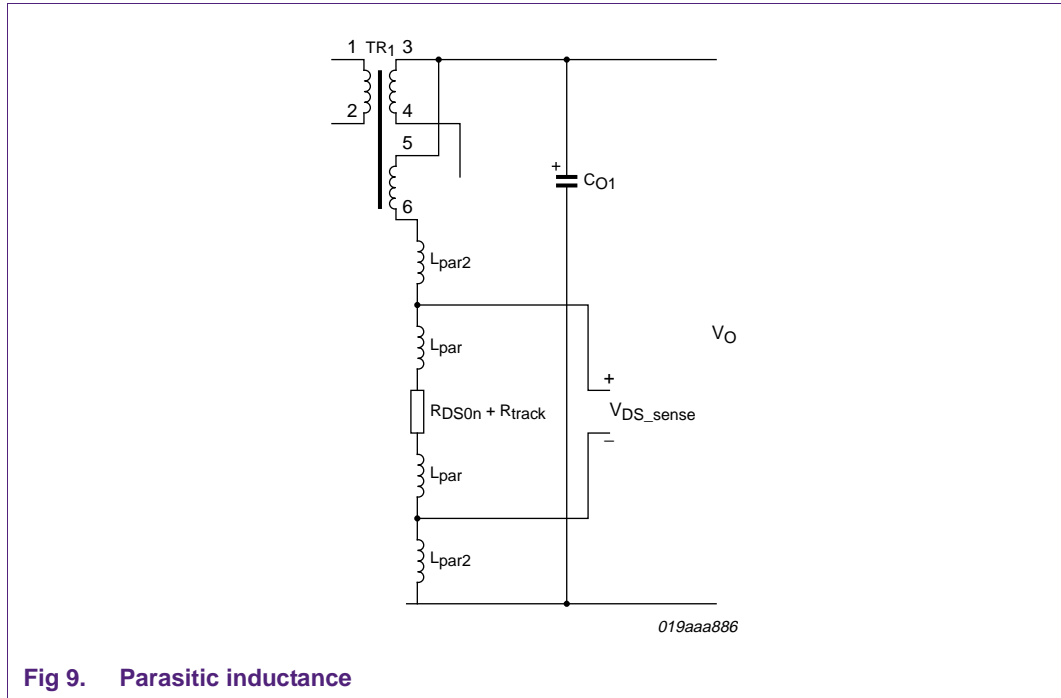


Fig 9. Parasitic inductance

[Equation 10](#) calculates the voltage over the inductance:

$$V_L(t) = L_{par} \times \frac{dI_{ds}}{dt} \tag{10}$$

If the secondary current can be modeled using [Equation 11](#):

$$I_{DS}(t) = |I_{amp} \times \sin(\omega_I \times t)| \tag{11}$$

Then the induced voltage equals:


$$V_L(t) = L_{par} \times \frac{d}{dt}(I_{amp} \times \sin(\omega_I \times t)) \tag{12}$$

Combined with the resistance between the measuring points the voltage drop equals:

$$\left[\begin{aligned} V_{DS}(t) &= I_{amp} \times L_{par} \times \omega_I \times \cos(\omega_I \times t) + R_{DSon} \times I_{amp} \times \sin(\omega_I \times t) \\ &= I_{amp} \times \sqrt{(L_{par}^2 \times \omega_I^2 + R_{DSon}^2)} \times \cos(\omega_I \times t - \varphi) \\ \varphi &= \text{atan}\left(\frac{R_{DSon}}{L_{par} \times \omega_I}\right) \end{aligned} \right. \tag{13}$$

Figure 10 shows an example, where:

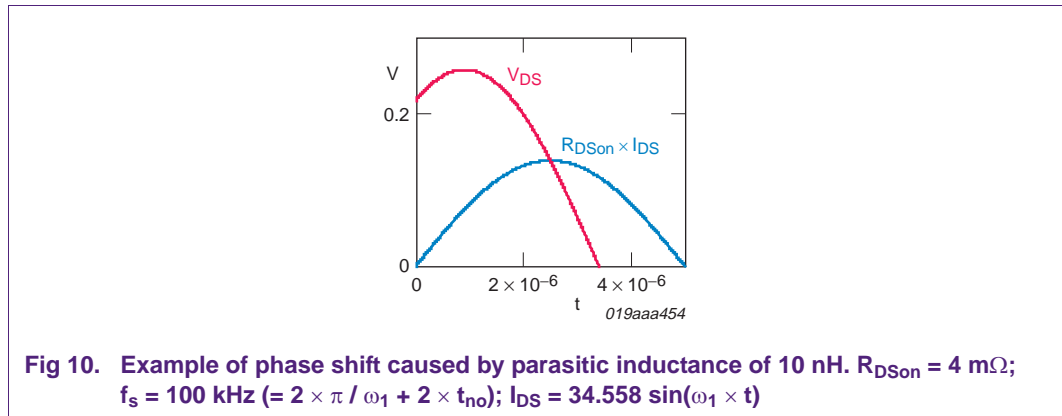
- $L_{par} = 10 \text{ nH}$
- $R_{DSon} = 4 \text{ m}\Omega$
- $I_{DS}(t) = 34.558 \times \sin(\omega_1 \times t)$



The time (t_1) of the early turn-off of the MOSFET can be calculated with Equation 14:

$$\frac{t_{pr}}{2} - t_1 = \text{acos}\left(\left(\frac{V_{th}}{I_{amp} \times \sqrt{L_{par}^2 \times \omega_1^2 + R_{DSon}^2}}\right) + \phi\right) \tag{14}$$

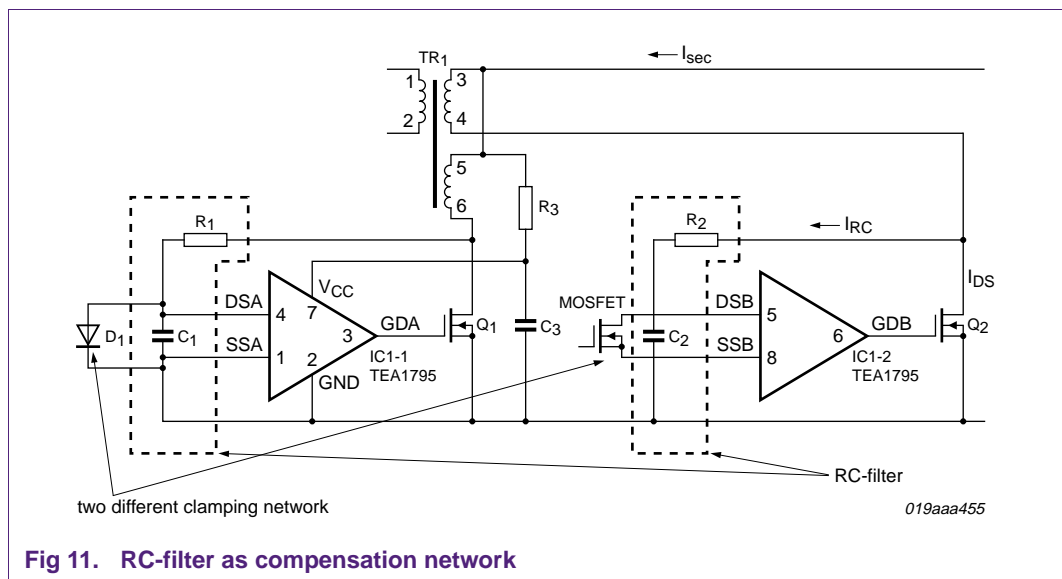In this case it is approximately $1.627 \mu\text{s}$, giving an additional loss of $3.686 \text{ W} - 2.171 \text{ W} = 1.515 \text{ W}$. The result of this inductance is that the losses are almost doubled. Therefore a solution to decrease these losses is required. One solution is to use an RC filter as a compensation network (see Figure 11).



The associated equations are:

$$\begin{cases} I_{sec}(s) = I_{DS}(s) + I_{RC}(s) \\ R_1 \times I_{RC} + V_{CI} = L_{par} \times \frac{dI_{ds}}{dt} + R_{DSon} \times I_{DS} \\ I_{RC} = C_1 \times \frac{dV_{CI}}{dt} \end{cases} \quad (15)$$

The solution for this system in the time domain is given in [Section 11](#). In the s-domain the system can be written as:

$$\begin{cases} I_{sec}(s) = I_{DS}(s) + I_{RC}(s) \approx I_{DS}(s) \\ \left(R_1 + \frac{I}{C_1 \times s}\right) \times I_{RC} = (s \times L_{par} \times R_{DSon} + I) \times I_{DS} \Rightarrow \begin{cases} I_{sec}(s) \approx I_{DS}(s) \\ V_{CI} = \frac{\left(\frac{L_{par} \times s}{R_{DSon}} + I\right)}{(R_1 \times C_1 \times s + I)} \times R_{DSon} \times I_{DS} \end{cases} \\ V_{CI} = \frac{I_{RC}}{C_1 \times s} \end{cases} \quad (16)$$

If:

$$\frac{L_{par}}{R_{DSon}} = R_1 \times C_1 \quad (17)$$

the last part of [Equation 16](#) changes to:


$$V_{CI} = R_{DSon} \times I_{DS} \quad (18)$$

Example:


- $L_{par} = 10 \text{ nH}$
- $R_{DSon} = 4 \text{ m}\Omega$
- $R_1 = 3.9 \text{ k}\Omega$

Results in: $C_1 = 641 \text{ pF}$.

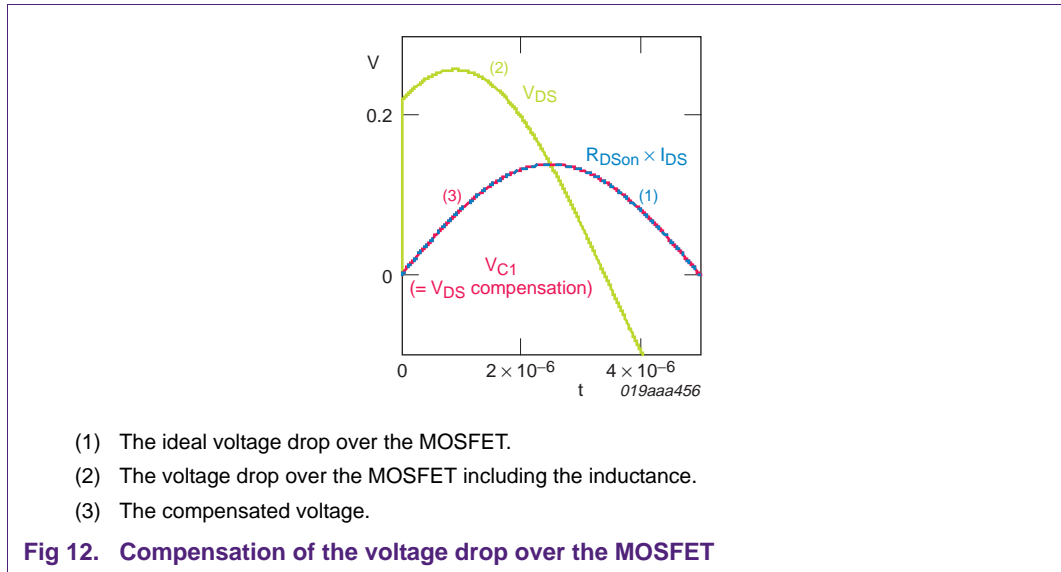[Figure 12](#) shows the result of the compensation. Ideally, the capacitor voltage follows the drain-source voltage very accurately. In reality, however, this is very often not the case.




When one of the secondary MOSFET is conducting, the other MOSFET has a voltage drop of approximately twice the output voltage. The compensation capacitor C_1 is also charged to this voltage. When the voltage drops to below zero because the voltage over the transformer reverses, the capacitor is also discharged to -220 mV. If the built-in diode of the MOSFET conducts this is approximately -0.6 V. [Figure 13](#) shows the voltage of the capacitor as a function of time. It takes $10.3 \mu\text{s}$ to discharge the capacitor.

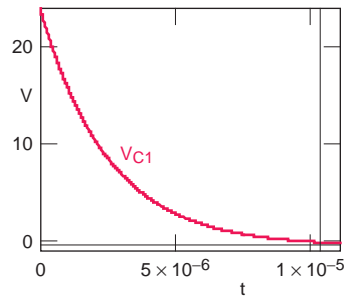

019aaa457

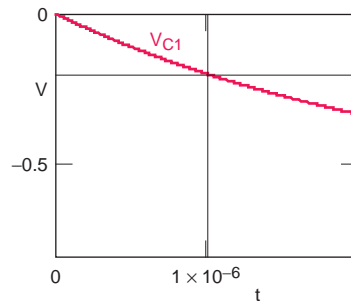a. The discharge time of the compensation capacitor equals 10.3 μs . This time can also be calculated with Equation 9 ($R_1 = 3.9 \text{ k}\Omega$; $C_1 = 641 \text{ pF}$; $V_{C1} = -0.2 \text{ V}$, $V_{in} = 24 \text{ V}$).



019aaa511

b. The capacitor voltage is clamped down to 0 V:
The discharge time compensation capacitor equals 1.02 μs

Fig 13. The discharge time of the compensation capacitor from 24 V to -0.22 V when the MOSFET is turned on

Without further adaptations this compensation circuit does not work. The first one is to clamp the voltage to 0 V (MOSFET) or 250 mV (RF Schottky diode). This reduces the discharge time (from 0 V to -220 mV) to 1.02 μs . The second one to compromise between the delay caused by capacitor C_1 and to what extent the induction (L_{par}) is compensated, expressed by the function "Early" (see Figure 14). A larger compensation capacitor results in a larger turn-on delay, which again results in a better compensation.


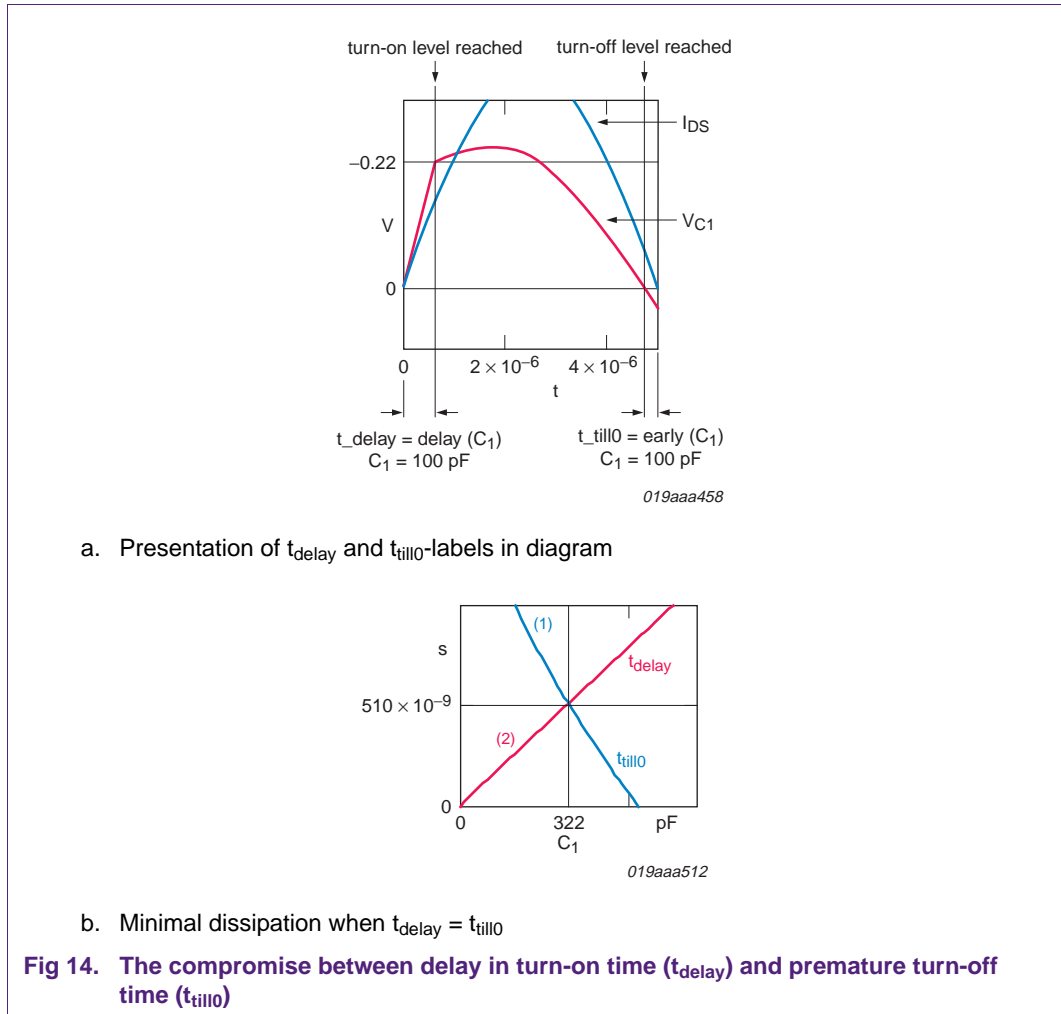


Fig 14. The compromise between delay in turn-on time (t_{delay}) and premature turn-off time (t_{till0})

The calculation of the function $t_{\text{till0}} = \text{Early}(C_1)$ is explained in [Section 11](#). Here only the result for an amplitude of a current of 34.6 A and a parasitic inductance of 10 nH is given. [Figure 15](#) shows how the total dissipation (P_{tot}) depends on the C_1 value of 322 pF. The minimum dissipation approximately coincides with a C_1 value of 322 pF, where $t_{\text{delay}} = t_{\text{till0}}$ is valid (see [Figure 14](#)). The delay time and the early time are around 510 ns.

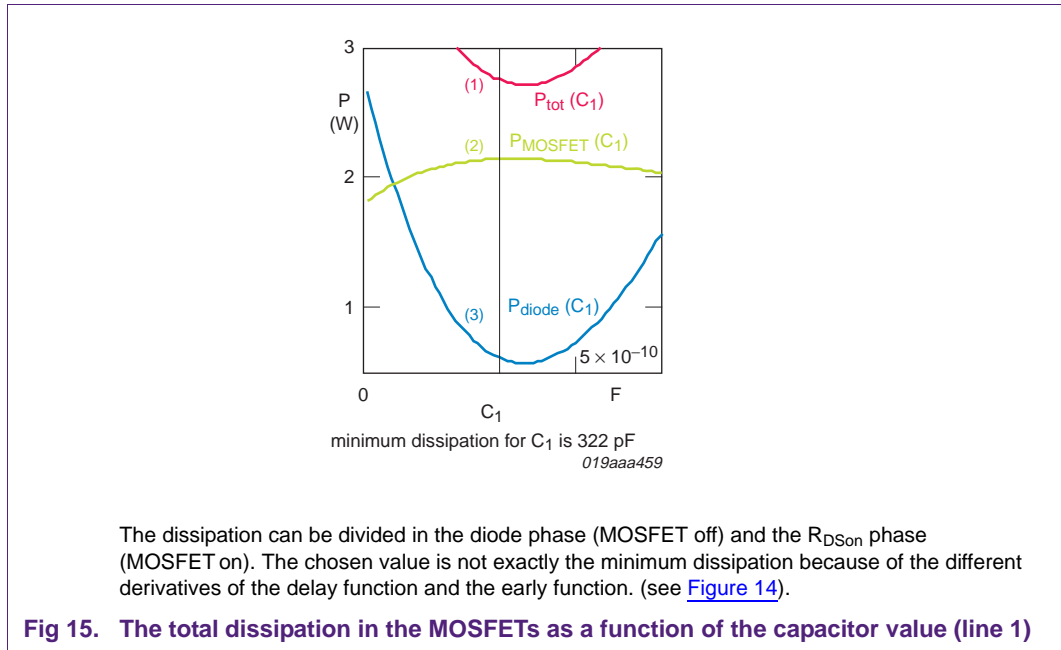

In [Figure 15](#) the minimum dissipation does not coincide with the chosen value. This is caused by different values with which the delay function increases and the early function decreases.


The dissipation is increased from 2.171 W (optimal switching) to 2.751 W (with compensation $R_1 = 3.9 \text{ k}\Omega$, and $C_1 = 322 \text{ pF}$). These values are calculated without taking into account the delay in the IC and with a MOSFET used to clamp the filter capacitor voltage to 0 V. If instead of a MOSFET a diode is used, the voltage is clamped to 250 mV.

The new optimal value of C_1 changes to 247.14 pF; $t_{\text{delay}} = t_{\text{fill0}} = 726.5 \text{ ns}$; $P_{\text{tot}} = 3.316 \text{ W}$.

R_1 is dimensioned as $R_1 = 3.9 \text{ k}\Omega$ because the maximum current coming out of the DSA and DSB pins is 1 μA , giving a voltage drop of approximately 4 mV. In the worst case the turn-off threshold level is lowered to -8 mV instead of -12 mV.

The dissipation in the resistor cannot be ignored, because of the relatively low value of R_1 (3.9 k Ω). E.g., when the output voltage is 12 V one of the two resistors will always have a 24 V voltage drop, while the other resistor is at approximately ground level. 24 V means a dissipation of around 150 mW. This can be a problem for very low load specifications. Two options are possible to improve the low load dissipation.

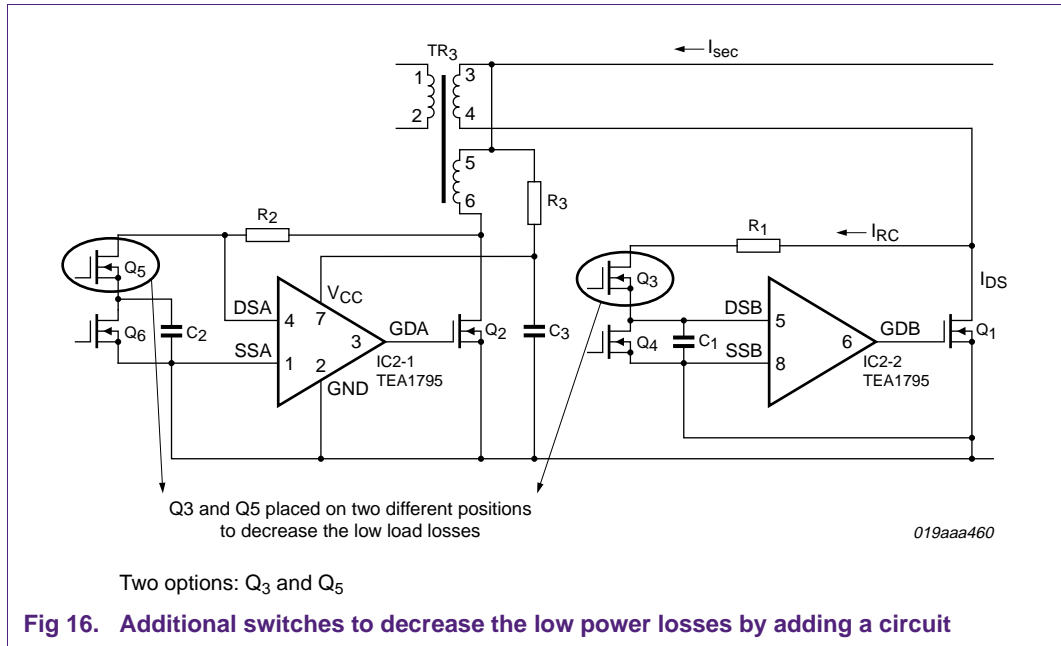- A switch Q_3 is added in series with R_1 (see [Figure 16](#)). The sense is connected to the source of Q_3
- In the second option the source (Q_3) is not connected to the sense input, but the drain (Q_5) is.



It is important to know how large the compensation capacitor has to be, so the correct MOSFET (Q₃ or Q₅) can be selected. The drain-source capacitance of Q₄ and Q₆ are placed parallel to the compensation capacitance.

Table 2. Compensation capacitance

	V _{DS}		
	100 mV (Typical)	10 V (Typical)	10 V (Maximum)
C_{iss}			
2N7002	41 pF	31 pF	50 pF
BSN20	21 pF	17 pF	27 pF
BSS123	110 pF	55 pF	-
C_{oss}			
2N7002	25 pF	6.8 pF	30 pF
BSN20	17 pF	7 pF	15 pF
BSS123	100 pF	12 pF	-

The timing of the switches (Q₃, Q₄, Q₅, and Q₆) is set in the following way: When the voltage of Q₁ is low, Q₅ has to be off and Q₆ has to be on. On the other hand when the voltage of Q₁ is high Q₅ has to be on and Q₆ has to be off. The same can be said about the state of Q₃ and Q₄ (see [Table 3](#)).

Table 3. The states of Q₃, Q₄, Q₅, and Q₆

State	Q ₃	Q ₄	Q ₅	Q ₆
Q ₁ = LOW; Q ₂ = HIGH	off	on	on	off
Q ₁ = HIGH; Q ₂ = LOW	on	off	off	on

The next step is to find the right driver signals to meet the states in [Table 3](#). There are two options:

- To derive the signal from the transformer winding (see [Figure 17](#), Q₃ – Q₄ configuration)
- To derive the signal from the driver output (see [Figure 17](#), Q₅ – Q₆ configuration)

If transformer winding is used the gate of Q₃ is connected via a resistance division to the drain of Q₂. Q₄ is connected to the drain of Q₁. The gate of Q₅ is connected to the drain of Q₁ (see [Figure 17](#)). The gate of Q₆ is connected to the drain of Q₂.


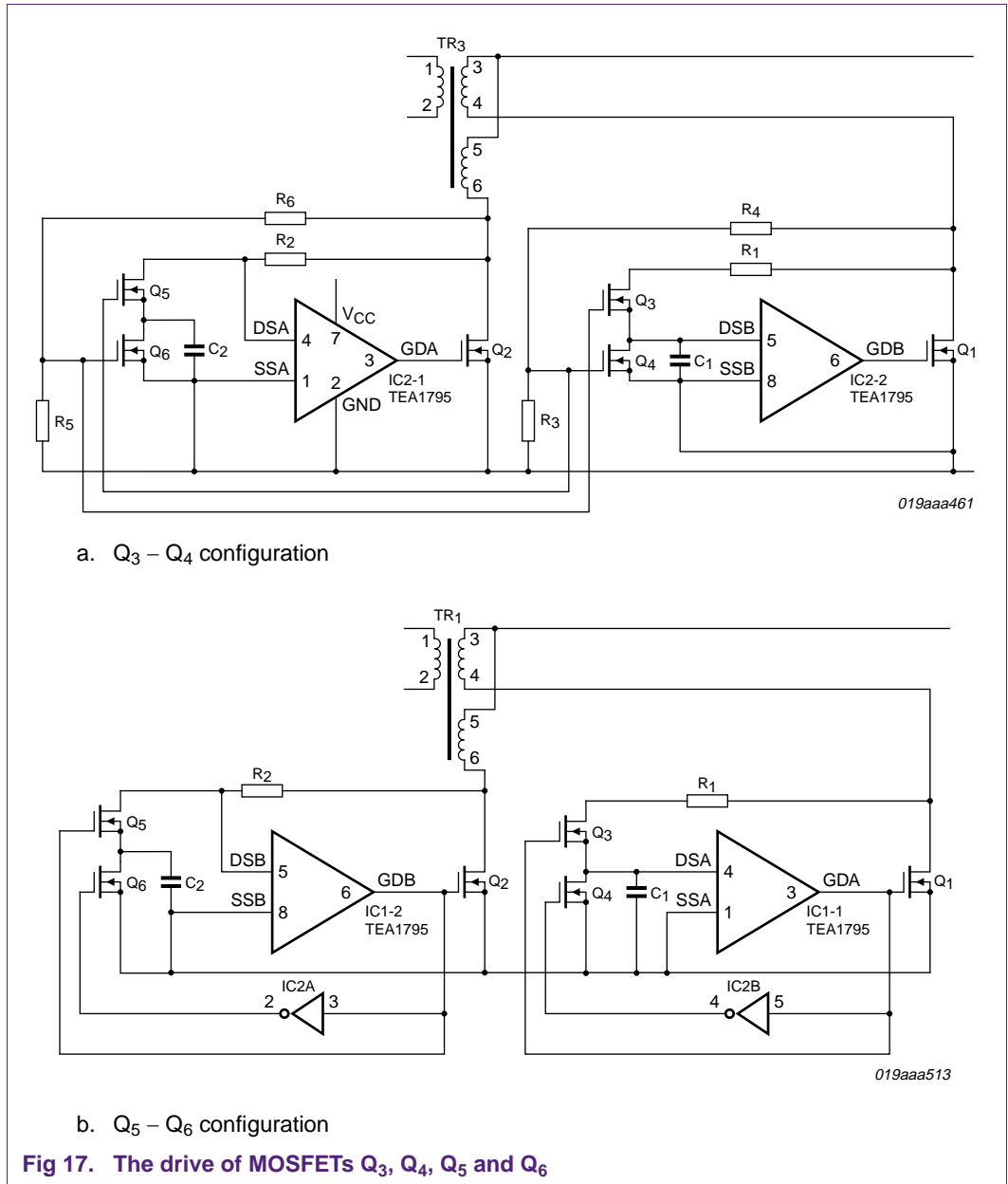


Fig 17. The drive of MOSFETs Q₃, Q₄, Q₅ and Q₆

Figure 18 to Figure 20 show the measurement results for the first schematic (Q₃ – Q₄ configuration).

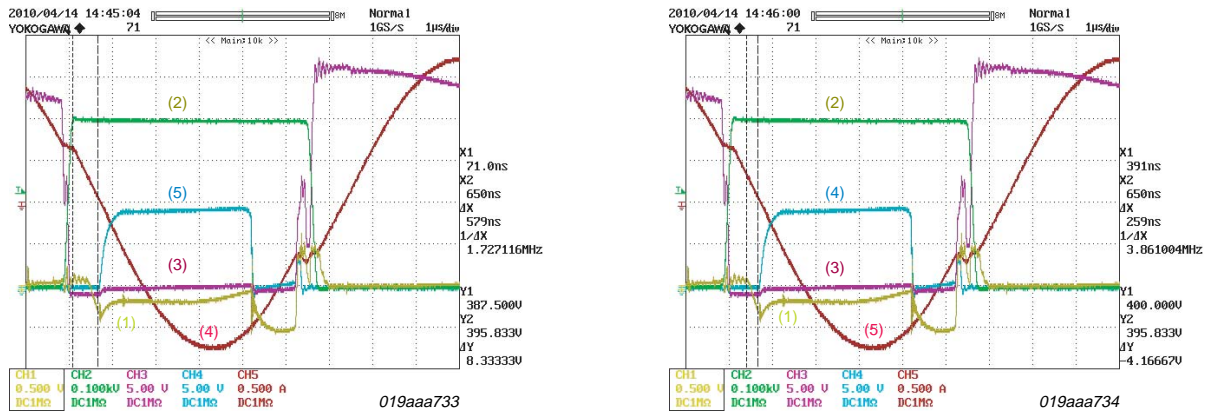


$C_1 = 33 \text{ pF}$; $R_1 = 3.9 \text{ k}\Omega$; $I_{\text{load}} = 15 \text{ A}$

- (1) Voltage on the DSA pin
- (2) Half-bridge point
- (3) Drain-source voltage on MOSFET
- (4) Gate source voltage
- (5) Primary transformer current
 - a. The total delay before MOSFET is turned on ($C_1 = 33 \text{ pF}$)
 - b. The delay caused by the charge of the compensation capacitor ($C_1 = 33 \text{ pF}$)

Fig 18. Measurement results of the TEA1795 with compensation network

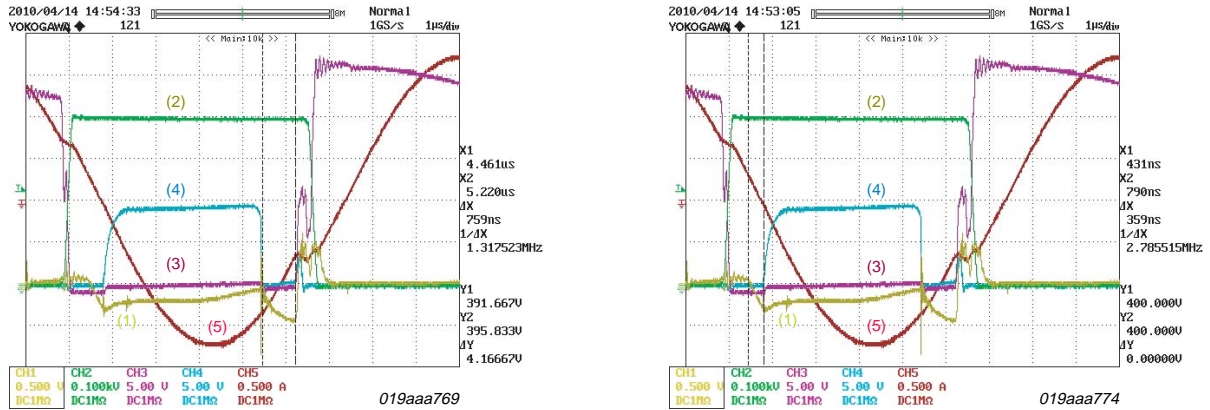The delay between the current starting to flow through the MOSFET and the turn-on of the MOSFET is 597 ns. 259 ns is caused by charging the capacitor and 338 ns by the delay of switching Q₃ and Q₄. The premature turn-off is approximately 1 μs .



$C_1 = 100 \text{ pF}$; $R_1 = 3.9 \text{ k}\Omega$; $I_{\text{load}} = 15 \text{ A}$


- (1) Voltage on the DSA pin
 - (2) Half-bridge point
 - (3) Drain-source voltage on MOSFET
 - (4) Gate source voltage
 - (5) Primary transformer current
- a. The capacitance is increased to 100 pF. The delay is increased with 100 ns (see [Figure 18](#))
- b. Increasing the compensation capacitor from 33 pF to 100 pF prematurely causes switching to decrease from 1 μs to 759 ns

Fig 19. Measurement results of the TEA1795 with compensation network

The delay between the current starting to flowing through MOSFET and the turn-on the MOSFET is 697 ns. 359 ns is caused by charging the capacitor and 338 ns is caused by the delay of switching Q_3 and Q_4 . The premature turn-off is approximately 759 ns.

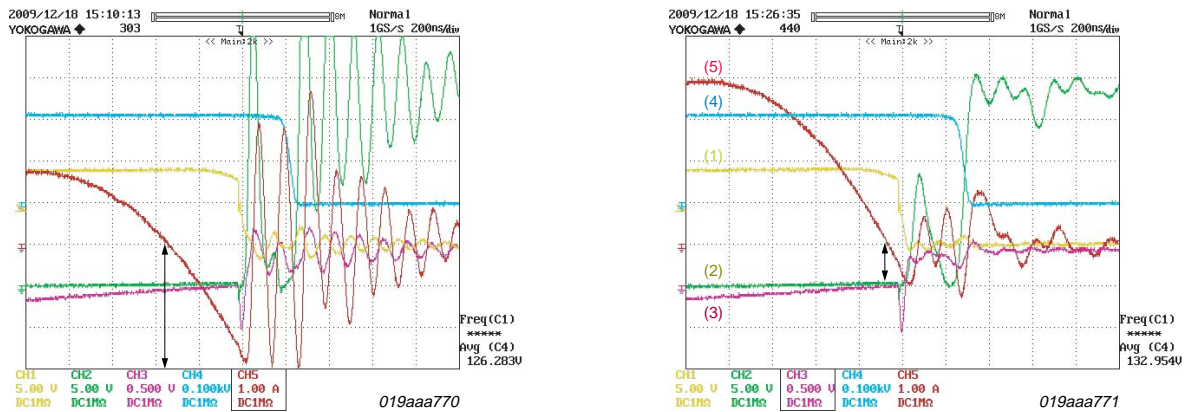8. DCM versus CCM

It does not matter whether the converter is working in CCM mode or DCM mode. There is, however, one exception: the dimensioning of the RC filter is different for DCM and CCM. The MOSFETs have to turn off at the right time to prevent current flowing in the wrong direction (see [Figure 20](#)). In Continuous Conduction Mode (CCM) the di/dt during commutation (going to zero) is much higher than the di/dt in Discontinuous Conduction Mode (DCM). Therefore, in CCM, the input filter of the IC has to be dimensioned in such a way that only the high frequency oscillation is filtered out and compensation for parasitic inductance is not necessary.



Capacitance = 100 pF; Resistance = 3.9 kΩ; $I_{load} = 15\text{ A}$

- (1) Voltage on the DSA pin
- (2) Half-bridge point
- (3) Drain-source voltage on MOSFET
- (4) Gate source voltage
- (5) Primary transformer current
 - a. High reverse current causes a lot of ringing
 - b. Low reverse current causes much less ringing

Fig 20. Measurement results of the TEA1795 with compensation network


9. Issues

9.1 Unstable behavior of the control voltage at low output power

The TEA1795 only turns on the MOSFET if the voltage drop over of the MOSFET is at least 220 mV (see [Section 6.1](#)). When the MOSFET is conducting the voltage drops to a few millivolts. This difference in voltage causes a high current dump which again causes a large power transfer per cycle. The transfer can only be changed by changing the control signal. When the voltage drop over of the MOSFET is less than 220 mV no power is delivered to the output. Therefore a small change in the control signal leads to a major difference in power transfer, which causes an oscillation.

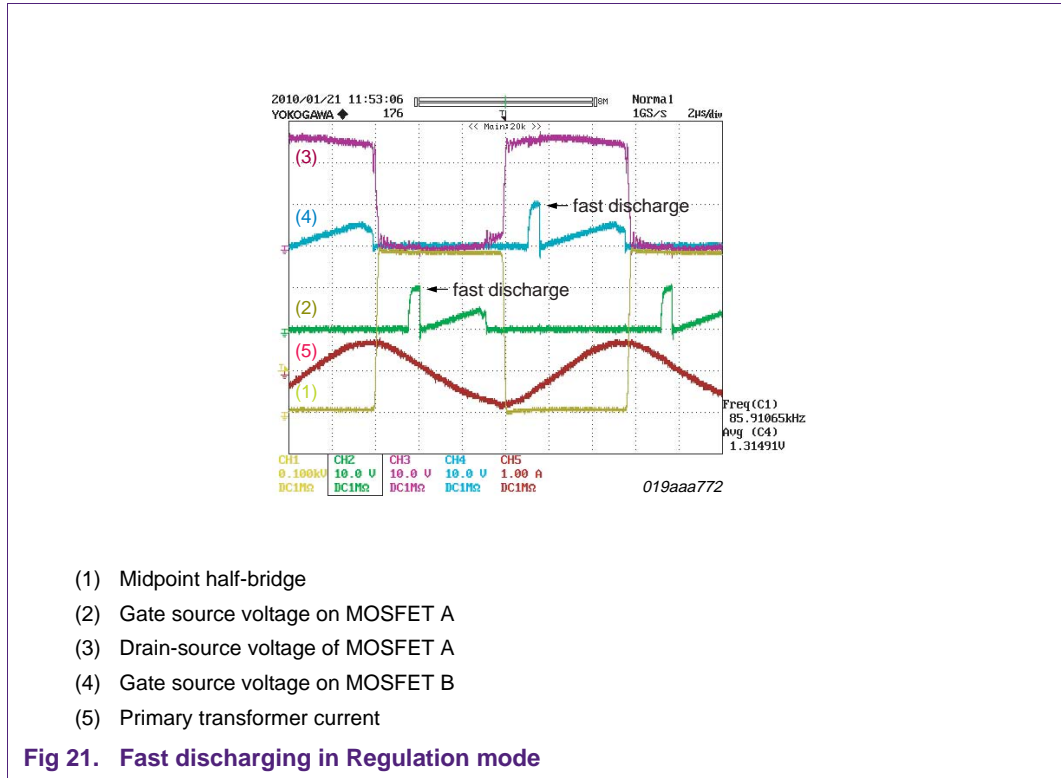9.2 Fast discharging of the gate in Regulation mode

When the blanking time following the turn-on of the SR-MOSFET is passed, the IC changes from On mode to Regulation mode. When the measured drain-source voltage is higher than -25 mV the IC regulates the drain-source voltage to -25 mV. The gate is fully discharged, because the turn-off circuit is also active at that moment. The IC compensates this behavior again by charging the gate voltage. This charge current is only 5 mA so that the charging is very slow. [Figure 21](#) shows the result of this behavior.



9.3 Power supply in Off mode

If the power supply is in the Off mode, the IC gets no supply. Despite the absence of power the output of the driver is low ohmic. This is caused by an internal charge on a gate of the output MOSFET of the driver. This charge cannot flow away and causes the output of the IC to stay low ohmic. This is important to know when testing the output of the driver.

9.4 Double pulses

It is possible that double pulses on the gate voltage occur, because of the way the SR MOSFETs are controlled (see [Figure 22](#)).

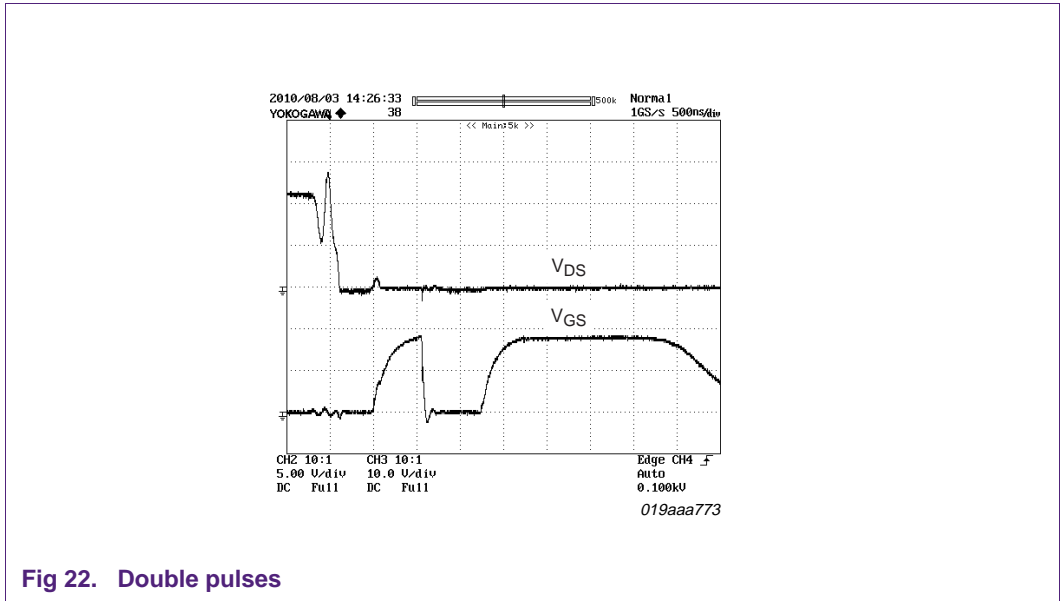


Fig 22. Double pulses

10. Layout of the IC

When designing the layout the following things are important for getting the lowest possible inductance:

- The sense connections must be as close as possible to the pins of the MOSFET
- The loop between the drain sense wire and the source sense wire must be as short as possible

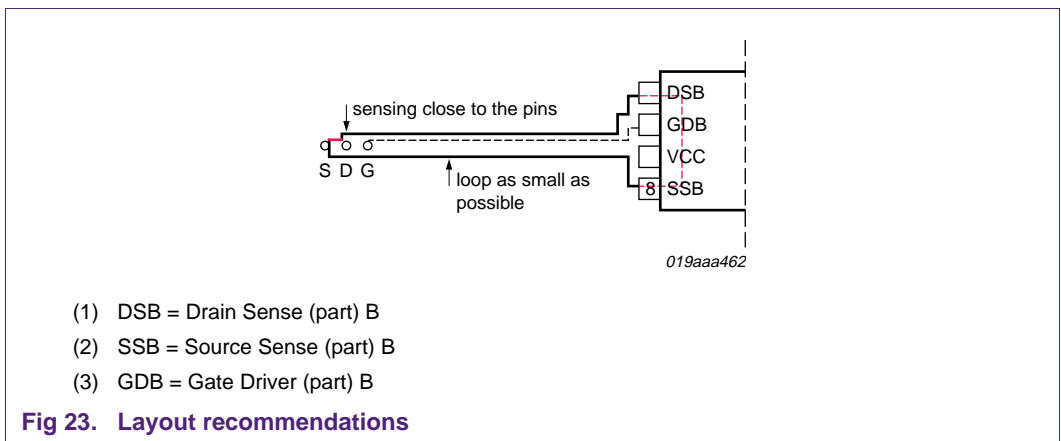


Fig 23. Layout recommendations

11. Overview calculations

11.1 DCM mode calculations

Simple presentation of the secondary current:

$$\begin{cases} I_{sec} = I_{amp} \times \left| \sin(\omega_1 \times (t - k \times t_{no})) \right| \wedge \frac{k \times \pi}{\omega_1} \leq t \leq \frac{(k+1) \times \pi}{\omega_1} \wedge k \in N \\ I_{sec} = 0 \wedge \frac{(k+1) \times \pi}{\omega_1} \leq t \leq \frac{(k+1) \times \pi}{\omega_1} + t_{no} \end{cases} \quad (19)$$

The switching period can be calculated with [Equation 20](#):

$$t_{sw} = t_{pr} + 2 \times t_{no} = \frac{2 \times \pi}{\omega_1} + 2 \times t_{no} \quad (20)$$

P_O the output power, V_O the output voltage, and I_O the output current are related in the following way:

$$P_O = V_O \times I_O \quad (21)$$

A combination of the all equations above results in:

$$\begin{aligned} P_O &= V_O \times \frac{I}{\frac{\pi}{\omega_1} + t_{no}} \int_0^{\frac{\pi}{\omega_1}} I_{amp} \times \sin(\omega_1 \times t) = \frac{2}{\pi} \times V_O \times I_{amp} \times \frac{\frac{2 \times \pi}{\omega_1}}{\frac{2 \times \pi}{\omega_1} + t_{no}} \\ &= \frac{2}{\pi} \times V_O \times I_{amp} \times \frac{I}{1 + \frac{\omega_1 \times t_{no}}{\pi}} \end{aligned} \quad (22)$$

The amplitude (I_{amp} in [Equation 22](#)) can be calculated with [Equation 23](#):

$$I_{amp} = \left(1 + 2 \times \frac{t_{no}}{t_{pr}} \right) \times \frac{\pi}{2} \times \frac{P_O}{V_O} \quad (23)$$

The average current (I_{avg}) on the secondary side equals the load current, but the RMS current (I_{RMS}) equals:

$$I_{RMS} = \sqrt{\frac{I}{\frac{t_{pr}}{2} + t_{no}} \int_0^{\frac{t_{pr}}{2}} I_{amp}^2 \times \sin^2(\omega_1 \times t) = \frac{\pi}{2} \times \frac{P_O}{V_O} \times \sqrt{\frac{1}{2} + \frac{t_{no}}{t_{pr}}} \quad (24)$$

The voltage drop over the rectifier diode can be calculated with [Equation 25](#):

$$V_f(I_d) = V_{f0} + R_d \times I_d \quad (25)$$

The dissipation in the two diodes together equals:

$$\begin{aligned}
 P &= \left(\frac{2}{\pi} \times V_{f0} \times I_{amp} + \frac{1}{2} \times R_d \times I_{amp}^2 \right) \times \frac{I}{I + 2 \times \frac{t_{no}}{t_{pr}}} \\
 &= \left(V_{f0} \times \frac{P_O}{V_O} + \frac{\pi^2}{8} \times R_d \times \frac{P_O^2}{V_O^2} \times \left(1 + 2 \times \frac{t_{no}}{t_{pr}} \right) \right)
 \end{aligned}
 \tag{26}$$

When MOSFETs are used instead of diodes the power dissipation is calculated with [Equation 27](#):

$$\begin{aligned}
 P &= \frac{1}{2} \times R_{DSon} \times I_{amp}^2 \times \frac{I}{I + 2 \times \frac{t_{no}}{t_{pr}}} \\
 &= \frac{\pi^2}{8} \times R_{DSon} \times \frac{P_O^2}{V_O^2} \times \left(1 + 2 \times \frac{t_{no}}{t_{pr}} \right)
 \end{aligned}
 \tag{27}$$

If the MOSFETs are switched on too late (t_{delay}) or switched off prematurely (t_{early}), the dissipation can be calculated with [Equation 28](#):

$$\begin{aligned}
 P_{loss} &= \left[\begin{aligned} &2 \times V_f \times I_{amp} \times [2 - [\cos(\omega_1 \times t_{delay}) + \cos(\omega_1 \times t_{till0})]] + \\ &I_{amp}^2 \times \omega_1 \times (t_{delay} + t_{till0}) \times (R_d - R_{DSon}) - \\ &\frac{1}{2} \times (R_d - R_{DSon}) \times I_{amp}^2 \times (\sin(2 \times \omega_1 \times t_{delay}) + \sin(2 \times \omega_1 \times t_{till0})) + \\ &R_{DSon} \times I_{amp}^2 \times (\pi) \end{aligned} \right] \\
 &\times \frac{I}{\pi + t_{on} \times \omega_1}
 \end{aligned}
 \tag{28}$$


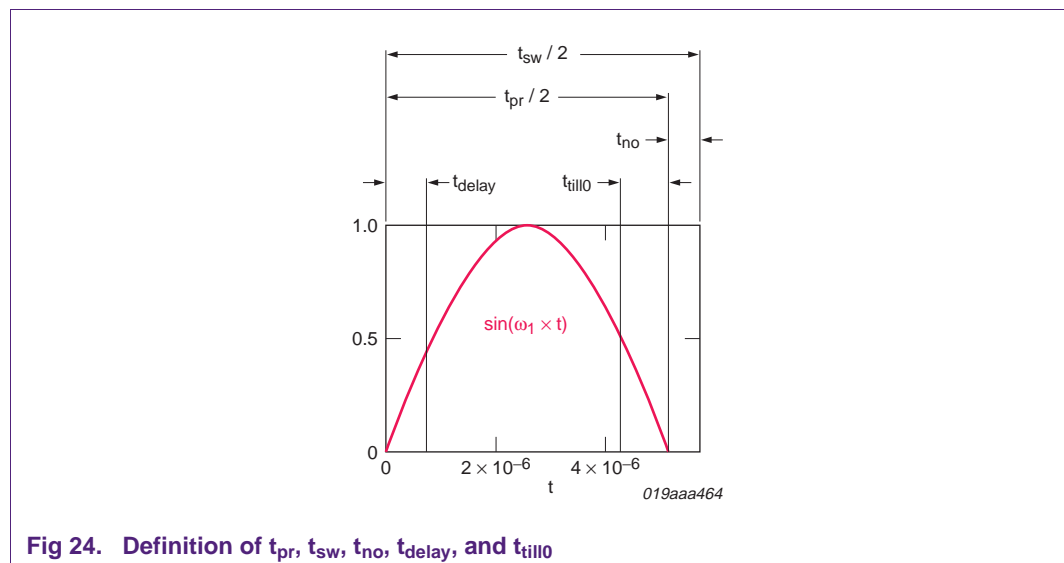


Fig 24. Definition of t_{pr} , t_{sw} , t_{no} , t_{delay} , and t_{till0}

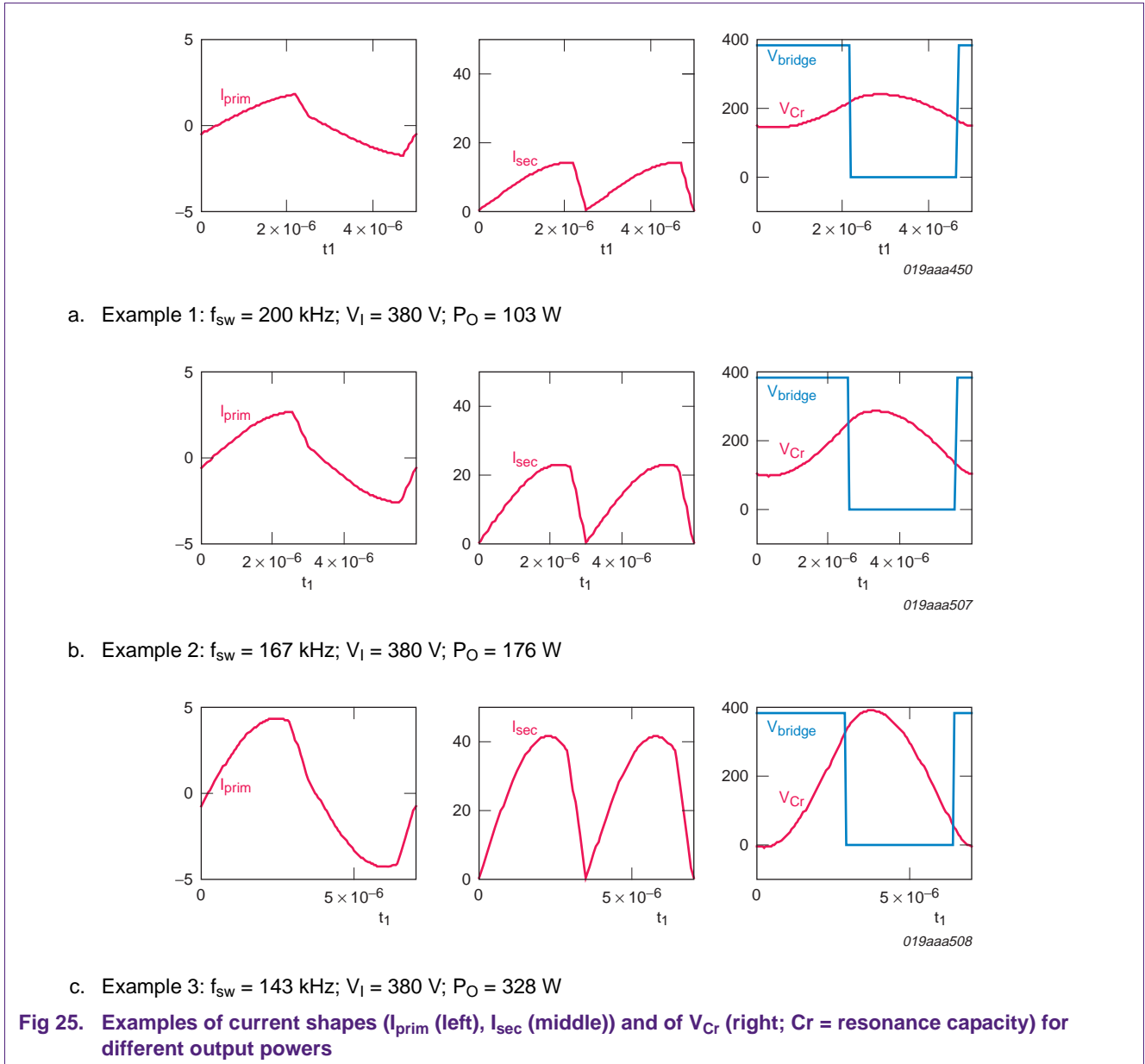11.2 CCM mode calculations

In case of CCM the secondary current has a slightly different shape. [Figure 25](#) shows three examples:



The secondary current can be approximated with [Equation 29](#):

$$I_{sec} = I_{amp} \times \left| \sin(\omega_I \times (t + k \times t_{tillo})) \right| \wedge k \times \frac{\pi}{\omega_I} \leq t < (k + 1) \times \left(\frac{\pi}{\omega_I} - t_{tillo} \right) \wedge k \in N \quad (29)$$

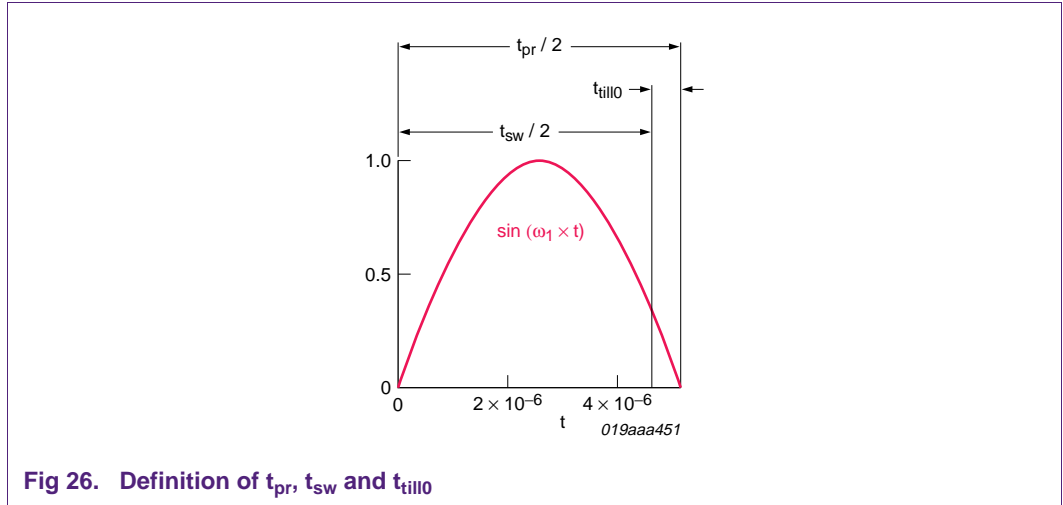


Fig 26. Definition of t_{pr} , t_{sw} and t_{tillo}

See [Figure 26](#) for the definition of the variables t_{sw} , t_{pr} and t_{tillo} .

The equivalent to the DCM case P_O can be written as [Equation 30](#):

$$\begin{aligned}
 P_O &= V_O \times \frac{2}{\frac{t_{pr}}{2} - t_{tillo}} \times \int_0^{\left(\frac{t_{pr}}{2} - t_{tillo}\right)} I_{amp} \times \sin(\omega_1 \times t) \times dt \\
 &= \frac{2}{\pi} \times V_O \times I_{amp} \times \frac{1 - \cos\left(\pi \times \left(1 - \frac{2 \times t_{tillo}}{t_{pr}}\right)\right)}{2 \times \left(1 - \frac{2 \times t_{tillo}}{t_{pr}}\right)}
 \end{aligned}
 \tag{30}$$

For a given P_O and V_O this expression can be rewritten as [Equation 31](#):

$$I_{amp} = \frac{\pi}{2} \times \frac{P_O}{V_O} \times \frac{2 \times \left(1 - \frac{2 \times t_{tillo}}{t_{pr}}\right)}{1 - \cos\left(\pi \times \left(1 - \frac{2 \times t_{tillo}}{t_{pr}}\right)\right)}
 \tag{31}$$

[Equation 31](#) is the expression for the effective current.

$$\begin{aligned}
 I_{RMS}(t_{tillo}) &= \sqrt{\frac{I}{2}} \times \frac{P_O}{V_O} \times \frac{\pi}{2} \times \frac{2 \times \left(1 - \frac{2 \times t_{tillo}}{t_{pr}}\right)}{1 - \cos\left[\pi \times \left(1 - \frac{2 \times t_{tillo}}{t_{pr}}\right)\right]} \times \\
 &\quad \sqrt{1 - \left[\frac{\sin\left[2 \times \pi \times \left(1 - \frac{2 \times t_{tillo}}{t_{pr}}\right)\right]}{2 \times \pi \times \left(1 - \frac{2 \times t_{tillo}}{t_{pr}}\right)} \right]}
 \end{aligned}
 \tag{32}$$

The voltage drop over the rectifier diode can be calculated with [Equation 33](#):

$$V_f(I_d) = V_{f0} + R_d \times I_d \tag{33}$$

The dissipation in the two diodes together equals:

$$P = V_{f0} \times \frac{P_O}{V_O} + \frac{1}{2} \times R_d \times \frac{P_O^2}{V_O^2} \times \frac{\pi^2 \times \left(1 - \frac{2 \times t_{\text{fall0}}}{t_{pr}}\right)}{\left(1 - \cos\left(\pi \times \left(1 - \frac{2 \times t_{\text{fall0}}}{t_{pr}}\right)\right)\right)^2} \times \left(1 - \frac{\sin\left(2 \times \pi \times \left(1 - \frac{2 \times t_{\text{fall0}}}{t_{pr}}\right)\right)}{2 \times \pi \times \left(1 - \frac{2 \times t_{\text{fall0}}}{t_{pr}}\right)}\right) \tag{34}$$

Example:

- $t_{pr} = 11 \mu\text{s}$
- $t_{\text{fall0}} = 500 \text{ ns}$
- $P_O = 240 \text{ W}$
- $V_O = 12 \text{ V}$
- $R_d = 5 \text{ m}\Omega$
- $V_{f0} = 280 \text{ mV}$

The dissipation in the diodes equals: 7.925 W.

11.3 Input filter

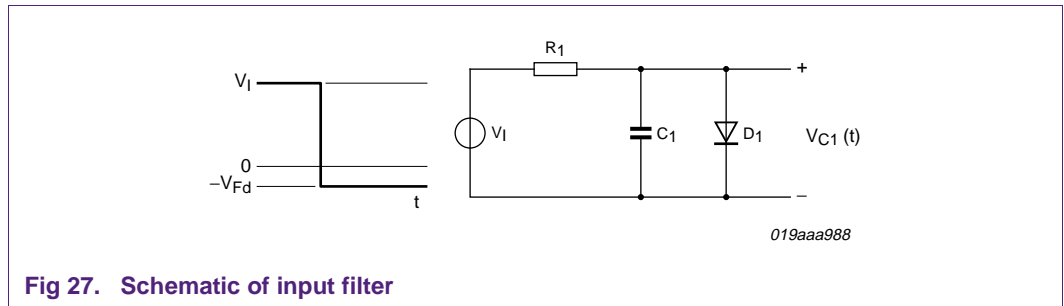


Fig 27. Schematic of input filter

The output voltage of the input filter shown in [Figure 27](#) can be calculated with [Equation 35](#):

$$V_{C1}(t) = V_{C10} \times \exp\left(-\frac{t}{R_1 \times C_1}\right) + V_I \times \left(1 - \exp\left(-\frac{t}{R_1 \times C_1}\right)\right) \tag{35}$$

Where:

- V_{C1} = voltage on capacitor C_1
- V_{C10} = boundary condition of the capacitor voltage
- V_I = input voltage

With [Equation 35](#) t_{delay} can be calculated.

When:

- $V_{C10} = V_{F(D1)}$ (forward voltage of diode D₁)
- $V_I = V_{F(MOSFET)}$ (diode of MOSFET Q₁ or Q₂) (see [Figure 11](#))
- $t = t_d$
- $V_{C1} = V_{th}$ (-220 mV)

[Equation 35](#) changes to [Equation 36](#):

$$V_{C1}(t_d) = V_{F(D1)} \times \exp\left(-\frac{t_d}{R_I \times C_I}\right) + V_{F(MOSFET)} \times \left(1 - \exp\left(-\frac{t_d}{R_I \times C_I}\right)\right) = V_{th} \quad (36)$$

Then t_{delay} can be calculated with [Equation 37](#)

$$t_d = -R_I \times C_I \times \ln\left(-\frac{(V_{th} - V_{F(MOSFET)})}{(V_{F(D1)} - V_{F(MOSFET)})}\right) \quad (37)$$

11.4 Parasitic inductance

$$V_L(t) = L_{par} \times \frac{di_{ds}}{dt} \quad (38)$$

If the secondary current can be calculated with [Equation 39](#):

$$I_{DS}(t) = I_{amp} \times \sin(\omega_I \times t) \quad (39)$$

then the induced voltage becomes:

$$V_L(t) = L_{par} \times \frac{d(I_{amp} \times \sin(\omega_I \times t))}{dt} = I_{amp} \times L_{par} \times \omega_I \times \cos(\omega_I \times \varphi) \quad (40)$$

The total voltage measured equals:

$$\left[\begin{aligned} V_{DS}(t) &= I_{amp} \times L_{par} \times \omega_I \times \cos(\omega_I \times t) + R_{DSon} \times I_{amp} \times \sin(\omega_I \times t) \\ &= I_{amp} \times \sqrt{(L_{par}^2 \times \omega_I^2 + R_{DSon}^2)} \times \cos(\omega_I \times t - \varphi) \\ \varphi &= \text{atan}\left(\frac{R_{DSon}}{L_{par} \times \omega_I}\right) \end{aligned} \right. \quad (41)$$

Finally, the premature turn-off time equals t_1 in:

$$\frac{t_{pr}}{2} - t_1 = \text{acos}\left(\frac{V_{th}}{I_{amp} \times \sqrt{L_{par}^2 \times \omega_I^2 + R_{DSon}^2}}\right) + \varphi \quad (42)$$

11.5 Compensation filter


$$\begin{cases} I_{sec}(s) = I_{ds}(s) + I_{RC}(s) \\ R_I \times I_{RC} + V_{CI} = L_{par} \times \frac{di_{ds}}{dt} + R_{DSon} \times I_{DS} \\ I_{RC} = C_I \times \frac{du_{CI}}{dt} \end{cases} \quad (43)$$

$$\frac{L_{par}}{R_{DSon}} = R_I \times C_I \quad (44)$$

$$V_{CI} = R_{DSon} \times I_{ds} \quad (45)$$

The voltage drop over the measuring points caused by the parasitic inductance equals:
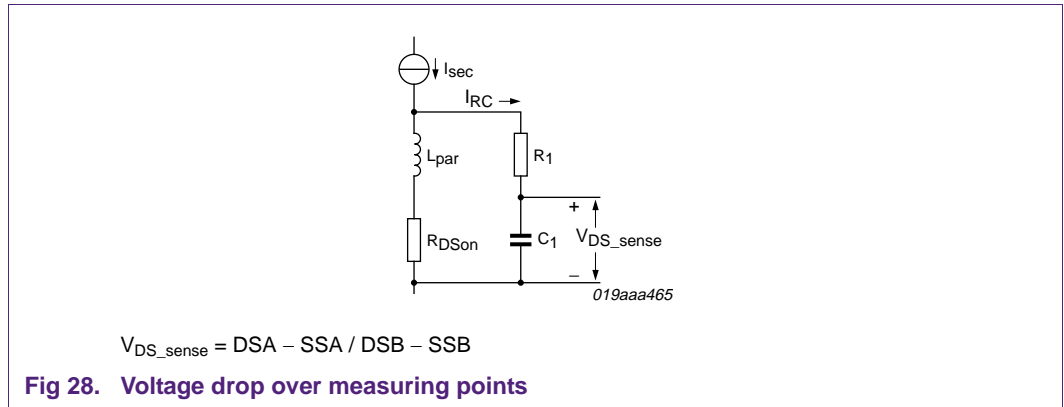
$$V_{DS}(t) = L_{par} \times \frac{di_{sec}}{dt} + R_{DSon} \times I_{sec} \quad (46)$$



$$\begin{cases} I_{sec} = I_{DS} + I_{RC} \\ R_I \times I_{RC} + V_{CI} = L_{par} \times \frac{di_{ds}}{dt} + R_{DSon} \times I_{ds} \Rightarrow \\ I_{RC} = C_I \times \frac{du_{CI}}{dt} \\ V_{CI} = V_{DS_sense} \end{cases} \quad (47)$$

$$\begin{cases} R_I \times I_{RC} + V_{DS_sense} = L_{par} \times \frac{d(I_{sec} - I_{RC})}{dt} + R_{DSon} \times (I_{sec} - I_{RC}) \Rightarrow \\ I_{RC} = C_I \times \frac{du_{ds_sense}}{dt} \end{cases}$$

$$\left[R_I \times C_I \times \frac{du_{ds_sense}}{dt} + V_{DS_sense} = L_{par} \times \frac{d(I_{sec} - I_{RC})}{dt} + R_{DSon} \times \left(I_{sec} - C_I \times \frac{du_{ds_sense}}{dt} \right) \right]$$

Laplace transformation

$$\begin{aligned}
 (R_I + R_{DSon}) \times C_I \times \frac{du_{ds_sense}}{dt} + V_{DS_sense} &= L_{par} \times \frac{d(I_{sec} - I_{RC})}{dt} + R_{DSon} \times I_{sec} \Rightarrow \\
 (R_I + R_{DSon}) \times C_I \times s \times V_{DS_sense} + V_{DS_sense} &= L_{par} \times s \times I_{DS^{-s}} \times I_{RC} + R_{DSon} \times I_{sec} \Rightarrow \\
 V_{DS_sense} &= I_{sec} \times R_{DSon} \times \left(\frac{\frac{L_{par}}{R_{DSon}} \times s + I}{(R_I + R_{DSon}) \times C_I \times s + I} \right) - \frac{s \times I_{RC}}{(R_I + R_{DSon}) \times C_I \times s + I}
 \end{aligned}
 \tag{48}$$

If the first term:

$$\frac{\frac{L_{par}}{R_{DSon}} \times s + I}{(R_I + R_{DSon}) \times C_I \times s + I} = I
 \tag{49}$$

and the second term:

$$\frac{s \times I_{RC}}{(R_I + R_{DSon}) \times C_I \times s + I}
 \tag{50}$$

are negligible, then:


$$V_{DS_sense} = I_{sec} \times R_{DSon}
 \tag{51}$$

The first term equals 1 if [Equation 52](#) is valid:

$$\begin{aligned}
 \frac{\frac{L_{par}}{R_{DSon}} \times s + I}{(R_I + R_{DSon}) \times C_I \times s + I} = I &\Rightarrow \frac{L_{par}}{R_{DSon}} = (R_I + R_{DSon}) \times C_I \Rightarrow \\
 C_I &= \frac{L_{par}}{R_{DSon} \times (R_I + R_{DSon})}
 \end{aligned}
 \tag{52}$$

The second term is small because I_{RC} is small.

11.6 Dimensioning of filter

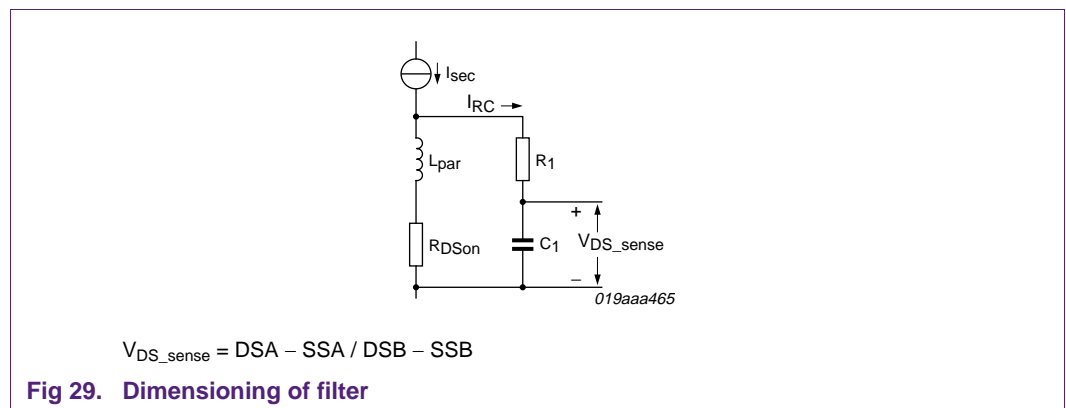

$$I_{\text{sec}} = A \times \sin(\omega_I \times t + \varphi) = A \times (\cos(\varphi) \times \sin(\omega_I \times t) + \sin(\varphi) \times \cos(\omega_I \times t)) \xrightarrow{s} A \times \frac{\cos(\varphi) \times \omega_I + \sin(\varphi) \times s}{s^2 + \omega_I^2} \quad (53)$$

$$\begin{cases} I_{\text{sec}} = I_{DS} + I_{RC} \\ R_I \times I_{RC} + V_{CI} = L_{par} \times \frac{di_{ds}}{dt} + R_{DSon} \times I_{DS} \\ I_{RC} = C_I \times \frac{du_{CI}}{dt} = \\ V_{CI} = V_{ds_sense} \end{cases} \Rightarrow \begin{cases} L_{par} \times \frac{di_{ds}}{dt} = -(R_{DSon} + R_I) \times I_{DS} + R_I \times I_{\text{sec}} \\ + u_{CI} \\ C_I \times \frac{du_{CI}}{dt} = I_{\text{sec}} - I_{DS} \end{cases}$$

$$\Rightarrow \begin{pmatrix} \frac{di_{ds}}{dt} \\ \frac{du_{CI}}{dt} \end{pmatrix} = \begin{pmatrix} L_{par} & 0 \\ 0 & C_I \end{pmatrix}^{-1} \times \begin{pmatrix} -(R_{DSon} + R_I) & +I \\ -I & 0 \end{pmatrix} \times \begin{pmatrix} I_{DS} \\ V_{CI} \end{pmatrix} + \begin{pmatrix} L_{par} & 0 \\ 0 & C_I \end{pmatrix}^{-1} \quad (54)$$

$$\times \begin{pmatrix} R_I & 0 \\ 1 & 0 \end{pmatrix} \times \begin{pmatrix} I_{\text{sec}} \\ 0 \end{pmatrix} \Rightarrow A \times \begin{pmatrix} \frac{di_{ds}}{dt} \\ \frac{du_{CI}}{dt} \end{pmatrix} = A_{mat} \times \begin{pmatrix} I_{DS} \\ V_{CI} \end{pmatrix} + B_{mat} \times \begin{pmatrix} I_{\text{sec}} \\ 0 \end{pmatrix}$$

$$A_{mat} = \begin{pmatrix} L_{par} & 0 \\ 0 & C_I \end{pmatrix}^{-1} \times \begin{pmatrix} R_{DSon} + R_I & -I \\ -I & 0 \end{pmatrix} \quad (55)$$

$$B_{mat} = \begin{pmatrix} L_{par} & 0 \\ 0 & C_I \end{pmatrix}^{-1} \times \begin{pmatrix} -R_I & 0 \\ 1 & 0 \end{pmatrix} \quad (56)$$

with Laplace transformation and T-matrix with eigenvectors.

$$\left. \begin{aligned} \dot{x} &= A_{mat} \times x + B_{mat} \times \begin{pmatrix} I_{sec} \\ 0 \end{pmatrix} \\ x &= T \times y \end{aligned} \right\} \Rightarrow T \times \dot{y} = A_{mat} \times T \times y + B_{mat} \times \begin{pmatrix} I_{sec} \\ 0 \end{pmatrix} \Rightarrow$$

$$\dot{y} = T^{-1} \times A_{mat} \times T \times y + T^{-1} \times B_{mat} \times \begin{pmatrix} I_{sec} \\ 0 \end{pmatrix} \Rightarrow$$

$$\Lambda = T^{-1} \times A_{mat} \times T \Rightarrow$$

$$\dot{y} = \Lambda \times y + T^{-1} \times B_{mat} \times \begin{pmatrix} I_{sec} \\ 0 \end{pmatrix} \quad \begin{matrix} s\text{-domain} \\ \rightarrow \end{matrix} \quad (57)$$

$$(s \times I - \Lambda) \times y = y_0 + T^{-1} \times B_{mat} \times \begin{pmatrix} I_{sec}(s) \\ 0 \end{pmatrix} \Rightarrow$$

$$y = (s \times I - \Lambda)^{-1} \times y_0 + (s \times I - \Lambda)^{-1} \times \frac{\cos(\varphi) \times \omega_1 + \sin(\varphi) \times s}{s^2 + \omega_1^2} \times T^{-1} \times B_{mat} \times \begin{pmatrix} I_{sec} \\ 0 \end{pmatrix} \Rightarrow$$

$$x = T \times (s \times I - \Lambda)^{-1} \times T^{-1} \times x_0 + (s \times I - \Lambda)^{-1} \times \frac{\cos(\varphi) \times \omega_1 + \sin(\varphi) \times s}{s^2 + \omega_1^2} \times T^{-1} \times B_{mat} \times \begin{pmatrix} I_{sec} \\ 0 \end{pmatrix}$$

$$x = T \times (sI - \Lambda)^{-1} \times T^{-1} \times x_0 + T \times (sI - \Lambda)^{-1} \times \frac{\cos(\varphi) \times \omega_1 + \sin(\varphi) \times s}{s^2 + \omega_1^2}$$

$$\times T^{-1} \times B_{mat} \times \begin{pmatrix} A \\ 0 \end{pmatrix} \quad \begin{matrix} \text{timedomain} \\ \rightarrow \end{matrix} \quad (58)$$

$$x(t) = T \times \exp(t) \times T^{-1} \times x_0 + T \times \exp2(t) \times T^{-1} \times B_{mat} \times \begin{pmatrix} A \\ 0 \end{pmatrix}$$

Where:

- x_0 = The boundary conditions
- p_1 and p_2 = The poles of the system
- T = the eigenvectors of the system
- I = the identity matrix

$$\exp(t) = \begin{pmatrix} \exp(p_1 \times t) & 0 \\ 0 & \exp(p_2 \times t) \end{pmatrix} \quad (59)$$

$$\exp2(t) = \begin{pmatrix} f_1(t) & 0 \\ 0 & f_2(t) \end{pmatrix} \quad (60)$$

$$f_1(t) = \frac{\omega_1 \times \cos(\varphi) + p_1 \times \sin(\varphi)}{\omega_1^2 + p_1^2} \times (\exp(p_1 \times t) - \cos(\omega_1 \times t)) +$$

$$\frac{\omega_1 \times \sin(\varphi) - p_2 \times \cos(\varphi)}{\omega_1^2 + p_1^2} \times \sin(\omega_1 \times t) \times T \quad (61)$$

$$f_2(t) = \frac{\omega_1 \times \cos(\varphi) + P_2 \times \sin(\varphi)}{\omega_1^2 + P_2^2} \times (\exp(p_1 \times t) - \cos(\omega_1 \times t)) + \frac{\omega_1 \times \sin(\varphi) - P_2 \times \cos(\varphi)}{\omega_1^2 + P_2^2} \times \sin(\omega_1 \times t) \quad (62)$$

With $t_{delay} = -RC \times \ln \left(\frac{V_{th} - V_I}{V_{DS0} - V_I} \right)$ φ can be calculated: $\varphi = \omega_1 \times t_{delay}$.

If t_1 is the time $V_c(t_1) = V_{th}$ and t_{pr} is the period time of secondary current then $t_{till0} = t_{pr} - t_1$.

The best choice for the capacitor value is when $t_{delay} = t_{till0}$

12. Legal information

12.1 Definitions

Draft — The document is a draft version only. The content is still under internal review and subject to formal approval, which may result in modifications or additions. NXP Semiconductors does not give any representations or warranties as to the accuracy or completeness of information included herein and shall have no liability for the consequences of use of such information.

12.2 Disclaimers

Limited warranty and liability — Information in this document is believed to be accurate and reliable. However, NXP Semiconductors does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information.

In no event shall NXP Semiconductors be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, NXP Semiconductors' aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the *Terms and conditions of commercial sale* of NXP Semiconductors.

Right to make changes — NXP Semiconductors reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

Suitability for use — NXP Semiconductors products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an NXP Semiconductors product can reasonably be expected

to result in personal injury, death or severe property or environmental damage. NXP Semiconductors accepts no liability for inclusion and/or use of NXP Semiconductors products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

Applications — Applications that are described herein for any of these products are for illustrative purposes only. NXP Semiconductors makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using NXP Semiconductors products, and NXP Semiconductors accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine whether the NXP Semiconductors product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

NXP Semiconductors does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using NXP Semiconductors products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). NXP does not accept any liability in this respect.

Export control — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from national authorities.

12.3 Trademarks

Notice: All referenced brands, product names, service names and trademarks are the property of their respective owners.

GreenChip — is a trademark of NXP B.V.

13. Contents

1	Introduction	3
2	Quick start-up.	3
3	Resonant converter versus flyback.	5
4	Diodes as rectifiers	6
5	MOSFETs as rectifiers.	8
6	Basic functionality of the TEA1795T	9
6.1	The turn-on function	9
6.2	The turn-off function	9
7	Improving the system	10
7.1	Turn-on	10
7.1.1	Immediate turn-off after turn-on	10
7.1.2	False turn-on	12
7.1.3	Parasitic turn-on	13
7.2	Turn-off	14
7.2.1	Premature turn-off	14
8	DCM versus CCM.	26
9	Issues	26
9.1	Unstable behavior of the control voltage at low output power	26
9.2	Fast discharging of the gate in Regulation mode.	27
9.3	Power supply in Off mode.	27
9.4	Double pulses.	28
10	Layout of the IC	28
11	Overview calculations	29
11.1	DCM mode calculations	29
11.2	CCM mode calculations	31
11.3	Input filter	33
11.4	Parasitic inductance	34
11.5	Compensation filter.	35
11.6	Dimensioning of filter	36
12	Legal information.	40
12.1	Definitions	40
12.2	Disclaimers	40
12.3	Trademarks	40
13	Contents	41

Please be aware that important notices concerning this document and the product(s) described herein, have been included in section 'Legal information'.

© NXP B.V. 2010.

All rights reserved.

For more information, please visit: <http://www.nxp.com>

For sales office addresses, please send an email to: salesaddresses@nxp.com

Date of release: 14 December 2010

Document identifier: AN10954