

**LINEAR  
APPLICATIONS  
HANDBOOK**

---

**NATIONAL  
SEMICONDUCTOR**





# LINEAR APPLICATIONS HANDBOOK

---

## NATIONAL SEMICONDUCTOR

The purpose of this handbook is to provide a fully indexed and cross-referenced collection of linear integrated circuit applications using both monolithic and hybrid circuits from National Semiconductor.

Individual application notes are normally written to explain the operation and use of one particular device or to detail various methods of accomplishing a given function. The organization of this handbook takes advantage of this innate coherence by keeping each application note intact, arranging them in numerical order, and providing a detailed Subject Index.

Many of the application schematics call out the generic family, which, by coincidence, is the military temperature range version of the device. Generally, any device in the generic family will work in the circuit. For example, an amplifier marked LM108 refers to the generic 108 family, and does not imply that only military-grade devices will work. Military (or industrial) grade devices need only be considered when their tighter electrical limits or wider temperature range warrant their use. As a reminder to our users, our numbering system is:

Device No.	Grade	Specified Temperature Range
LM1XX	Military	$-55^{\circ}\text{C} \leq T_A \leq +125^{\circ}\text{C}$
LM2XX	Industrial	$-25^{\circ}\text{C} \leq T_A \leq +85^{\circ}\text{C}$
LM3XX	Commercial	$0^{\circ}\text{C} \leq T_A \leq +70^{\circ}\text{C}$

Because commercial parts are less expensive than military or industrial, these points should be kept in mind when trying to determine the most cost-effective approach to a given design.

# Acknowledgements

D. Bohn  
J. E. Byerly  
G. Cleveland  
R. Dobkin  
J. Flink  
T. M. Frederiksen  
T. Hanna  
R. Hirschfeld  
W. M. Howard  
T. Isbell  
P. Lefferts  
D. Long  
E. L. Long  
J. Maxwell  
T. B. Mills  
D. Mishler  
W. B. Mitchell  
H. Mortensen  
D. Mrazek  
C. Nelson  
S. Ochi  
E. Papanicolaou

T. Regan  
W. S. Routh  
F. Sass  
N. Sevastopoulos  
J. Sherwin  
B. Siegel  
R. S. Sleeth  
T. Smathers  
J. Solomon  
R. Stump  
G. Taatjes  
W. Tuma  
R. K. Underwood  
L. VanDer Gaag  
M. K. Vander Kooi  
B. Welling  
R. J. Widlar  
M. Wilcox  
C. M. Wittmer  
D. L. Wollesen  
M. Yamatake

MICRO-DAC™ and BI-FET™ are trademarks of National Semiconductor Corporation. TRI-STATE® is a registered trademark of National Semiconductor Corporation.

**National Semiconductor Corporation** 2900 Semiconductor Drive, Santa Clara, California 95051 Tel: (408) 737-5000 TWX: (910) 339-9240  
National does not assume any responsibility for use of any circuitry described; no circuit patent licenses are implied; and National reserves the right, at any time without notice, to change said circuitry.

# Application Literature Numerical List

APPLICATION NOTES		DATE
AN-2	Designing Switching Regulators . . . . .	3/69
AN-3	Drift Compensation Techniques for Integrated DC Amplifiers . . . . .	11/67
AN-4	Monolithic Op Amp – The Universal Linear Component. . . . .	4/68
AN-13	Application of the LH0002 Current Amplifier . . . . .	9/68
AN-20	An Applications Guide for Op Amps. . . . .	2/69
AN-21	Designs for Negative Voltage Regulators . . . . .	12/68
AN-23	The LM105 – An Improved Positive Regulator . . . . .	1/69
AN-24	A Simplified Test Set for Op Amp Characterization. . . . .	6/69
AN-29	IC Op Amp Beats FETs on Input Current. . . . .	12/69
AN-30	Log Converters . . . . .	11/69
AN-31	Op Amp Circuit Collection . . . . .	2/70
AN-32	FET Circuit Applications . . . . .	2/70
AN-41	Precision IC Comparator Runs from +5V Logic Supply. . . . .	10/70
AN-42	IC Provides On-Card Regulation for Logic Circuits. . . . .	2/71
AN-46	The Phase Locked Loop IC as a Communication System Building Block . . . . .	6/71
AN-48	Applications for a New Ultra-High Speed Buffer . . . . .	8/71
AN-56	1.2 Volt Reference . . . . .	12/71
AN-64	LM381 Low Noise Dual Preamplifier. . . . .	5/72
AN-69	LM380 Power Audio Amplifier . . . . .	12/72
AN-70	LM381A Dual Preamplifier for Ultra-Low Noise Applications . . . . .	8/72
AN-71	Micropower Circuits Using the LM4250 Programmable Op Amp. . . . .	7/72
AN-72	The LM3900 – A New Current-Differencing Quad of $\pm$ Input Amplifiers . . . . .	9/72
AN-74	LM139/LM239/LM339 – A Quad of Independently Functioning Comparators. . . . .	1/73
AN-75	Applications for a High Speed FET Input Op Amp . . . . .	12/72
AN-79	IC Pre-Amp Challenges Choppers on Drift . . . . .	2/73
AN-81	LM1800 (LM1310, LM1310E) Phase Locked Loop FM Stereo Demodulator . . . . .	6/73
AN-82	LM125, LM126, LM127 Precision Dual Tracking Regulators . . . . .	5/74
AN-87	Comparing the High Speed Comparators . . . . .	6/73
AN-88	CMOS Linear Applications . . . . .	7/73
AN-97	Versatile Timer Operates from Microseconds to Hours . . . . .	12/73
AN-103	LM340 Series Three Terminal Positive Regulators . . . . .	3/74
AN-104	Noise Specs Confusing? . . . . .	5/74
AN-110	Fast IC Power Transistor with Thermal Protection. . . . .	5/74
AN-115	Wide Range Function Generator. . . . .	7/74
AN-116	Use the LM158/LM258/LM358 Dual, Single Supply Op Amp . . . . .	5/74
AN-125	LM377, LM378 and LM379 Dual Two, Four and Six Watt Power Amplifiers . . . . .	1/75
AN-127	LM143 Monolithic High Voltage Operational Amplifier Applications . . . . .	4/76
AN-129	A Linear Multiple Gain-Controlled Amplifier . . . . .	8/75
AN-132	The Monolithic Temperature Transducer—A New Interfacing Concept. . . . .	12/74
AN-146	FM Remote Speaker System . . . . .	6/75
AN-147	Low Cost IC Stereo Receiver. . . . .	6/75
AN-151	The Low Noise JFET—The Noise Problem Solver . . . . .	1/76
AN-153	Constant Current LED . . . . .	10/75
AN-154	1.3V IC Flasher, Oscillator, Trigger or Alarm . . . . .	12/75
AN-156	Specifying A/D and D/A Converters . . . . .	2/76
AN-161	IC Voltage Reference has 1 ppm per Degree Drift . . . . .	6/76
AN-162	LM2907 Tachometer/Speed Switch Building Block Applications . . . . .	6/76
AN-173	IC Zener Eases Reference Design . . . . .	11/76
AN-178	Applications for an Adjustable IC Power Regulator . . . . .	1/77
AN-179	Analog-to-Digital Converter Testing . . . . .	4/77
AN-181	3-Terminal Regulator is Adjustable. . . . .	3/77
AN-182	Improving Power Supply Reliability with IC Power Regulators. . . . .	4/77
AN-184	References for A/D Converters. . . . .	7/77
AN-193	Single Chip Data Acquisition System Simplifies Analog-to-Digital Conversion . . . . .	7/77
AN-210	New Phase-Locked-Loops Have Advantages as Frequency to Voltage Converters (and more) . . . . .	4/79
AN-211	New Op Amp Ideas . . . . .	12/78

# Application Literature Numerical List (Continued)

AN-222	Super Matched Bipolar Transistor Pair Sets New Standards for Drift and Noise . . . . .	7/79
AN-225	IC Temperature Sensor Provides Thermocouple Cold-Junction Compensation . . . . .	4/79
AN-233	The A/D Easily Allows Many Unusual Applications . . . . .	9/79
AN-234	A Microprocessor-Controlled Pressure Regulator . . . . .	7/79
AN-238	Improving Response Time of IC Temperature Transducers . . . . .	12/79
AN-240	Wide-Range Current-to-Frequency Converters . . . . .	5/80
AN-241	Working with High Impedance Op Amps . . . . .	2/80
AN-242	Applying a New Precision Op Amp . . . . .	4/80
<b>LINEAR BRIEFS</b>		<b>DATE</b>
LB-1	Instrumentation Amplifier . . . . .	3/69
LB-2	Feedforward Compensation Speeds Op Amp . . . . .	3/69
LB-3	Worst Case Power Dissipation in Linear Regulators . . . . .	4/69
LB-4	Fast Compensation Extends Power Bandwidth . . . . .	4/69
LB-5	High Q Notch Filter . . . . .	3/69
LB-6	Fast Voltage Comparators with Low Input Current . . . . .	5/69
LB-7	Tracking Voltage Regulators . . . . .	8/69
LB-8	Precision AC/DC Converters . . . . .	8/69
LB-9	Universal Balancing Techniques . . . . .	8/69
LB-10	IC Regulators Simplify Power Supply Design . . . . .	1/70
LB-11	The LM110 — An Improved IC Voltage Follower . . . . .	3/70
LB-12	An IC Voltage Comparator for High Impedance Circuitry . . . . .	1/70
LB-14	Speed Up the LM108 with Feedforward Compensation . . . . .	11/70
LB-15	High Stability Regulators . . . . .	1/71
LB-16	Easily Tuned Sine Wave Oscillators . . . . .	3/71
LB-17	LM118 Op Amp Slews 70V/ $\mu$ sec . . . . .	9/71
LB-18	+5 to -15 Volts DC Converter . . . . .	7/72
LB-19	Predicting Op Amp Slew Rate Limited Response . . . . .	8/72
LB-20	A Fully Differential Input Voltage Amplifier . . . . .	12/72
LB-21	Instrumentation Amplifiers . . . . .	6/73
LB-22	Low Drift Amplifiers . . . . .	6/73
LB-23	Precise Tri-Wave Generation . . . . .	6/73
LB-24	Versatile IC Pre-Amp Makes Thermocouple Amplifier with Cold Junction Compensation . . . . .	6/73
LB-25	True rms Detector . . . . .	6/73
LB-26	Specifying Selected Op Amps and Comparators . . . . .	10/73
LB-27	Micropower Thermometer . . . . .	1/74
LB-28	General Purpose Power Supply . . . . .	6/74
LB-29	Low Cost AM Radio System using LM1820 and LM386 . . . . .	2/75
LB-32	Microvolt Comparator . . . . .	6/76
LB-33	High Speed Warning Device for Automobiles . . . . .	6/76
LB-34	A Micropower Voltage Reference . . . . .	6/76
LB-35	Adjustable 3-Terminal Regulator for Low-Cost Battery Charging Systems . . . . .	8/76
LB-36	Simple Temperature Control . . . . .	12/76
LB-37	Low Current Ammeter . . . . .	2/77
LB-38	Wide Range Timer . . . . .	2/77
LB-39	Circuit Techniques for Avoiding Oscillations in Comparator Applications . . . . .	1/78
LB-40	Two Wire Current Transmitters . . . . .	12/78
LB-41	Precision Reference Uses Only Ten Microamperes . . . . .	6/78
LB-42	Get Fast Stable Response from Improved Unity-Gain Followers . . . . .	8/78
LB-44	Get More Power Out of Dual or Quad Op-Amps . . . . .	4/79
LB-45	Frequency-to-Voltage Converter Uses Sample-and-Hold to Improve Response and Ripple . . . . .	4/79
LB-46	A New Production Technique for Trimming Voltage Regulators . . . . .	7/79
LB-47	High Voltage Adjustable Power Supplies . . . . .	3/80
LB-48	Simple Voltmeter Monitors TTL Supplies . . . . .	2/80
LB-49	Programmable Power Regulators Help Check Out Computer System Operating Margins . . . . .	2/80
LB-50	Using the LM1524 in Switching Servo Amplifier Applications . . . . .	6/80
<b>APPENDICES</b>		
A	The Monolithic Operational Amplifier: A Tutorial Study . . . . .	12/74
B	A Color TV Primer for the E.E. . . . .	10/75
C	V/F Converter ICs Handle Frequency-to-Voltage Needs . . . . .	6/80
D	Versatile Monolithic V/Fs Can Compute as Well as Convert with High Accuracy . . . . .	6/80

## Device/Application Literature Cross-Reference

DEVICE NUMBER	APPLICATION LITERATURE
ADC0800	AN-159, AN-179
ADC0801/ADC0802/ADC0803/ADC0804	IAN-233
ADC0808	AN-193
ADC0816	AN-193
FETs	AN-32
LF353	LB-44
LH0002 (NH0002)	AN-13
LH0033	AN-48, AN-115
LH0062	AN-75
LM10	AN-211
LM11	AN-241
LM101	AN-3, AN-4, AN-20, AN-24, AN-132, LB-28
LM101A	AN-30, AN-31, LB-2, LB-4, LB-8, LB-16
LM104	AN-21, AN-110, LB-3, LB-7, LB-10, LB-40
LM105	AN-23, AN-110, LB-7, LB-10
LM106	LB-6
LM107	AN-31
LM108	AN-29, AN-30, AN-31, AN-79, AN-88, AN-110, AN-161, LB-14, LB-15, LB-24, LB-28
LM109	AN-42, AN-182, LB-15
LM110	AN-31, LB-11, LB-42
LM111	AN-41, AN-103, LB-12, LB-16, LB-32
LM113	AN-56, LB-21, LB-23, LB-28
LM114	LB-21, LB-25
LM216	AN-132, LB-37
LM117	AN-178, AN-181, AN-182, LB-35, LB-46, LB-47, LB-49
LM118	AN-110, AN-115, AN-129, LB-17, LB-21, LB-23
LM119	AN-115, LB-23
LM120	AN-103, AN-115, AN-182
LM121	AN-79, LB-24, LB-32
LM122	AN-97, LB-38
LM124	AN-88, AN-129
LM125	AN-82
LM126	AN-82
LM129	AN-173, AN-184
LM131	AN-210, AN-240, LB-45, Appendix C, Appendix D
LM134	LB-41
LM135	AN-255
LM137	LB-46, LB-49
LM138	LB-46, LB-49
LM139	AN-74
LM140	AN-103, AN-115, AN-182
LM143	AN-103, AN-127
LM158	AN-116
LM160	AN-87
LM161	AN-87
LM194	AN-222
LM195	AN-110, AN-129, AN-153, AN-161, LB-28
LM199	AN-161, AN-184, LB-31
LM317	AN-178, AN-181, AN-182, LB-35, LB-46
LM377	AN-125
LM378	AN-125, AN-147
LM379	AN-125
LM380	AN-69, AN-146
LM381	AN-64
LM381A	AN-70
LM382	AN-147
LM386	LB-29
LM565	AN-46, AN-146

## Device/Application Literature Cross-Reference (Continued)

LM566	.....	
LM709	.....	AN-146
LM1310	.....	AN-24
LM1558	.....	AN-81
LM1800	.....	AN-103, AN-116
LM1820	.....	AN-81, AN-147
LM1900	.....	AN-147, LB-29
LM2907	.....	LB-33
LM2917	.....	AN-162
LM3089	.....	AN-162
LM3900	.....	AN-147
LM3909	.....	AN-72, LB-20
LM3911	.....	AN-154
LM3914	.....	AN-132, LB-27, LB-36
LM4250	.....	LB-48
LM78LXX	.....	AN-71, AN-88, LB-34
MM74C04	.....	AN-146
NSL4944	.....	AN-88
	.....	AN-153



# Subject Index

A/D (See Analog-to-Digital)

**ABSOLUTE VALUE AMPLIFIER:** AN31-12

**AC AMPLIFIER:** AN31-1, AN31-18, AN48-4, AN72-6

**AC TO DC CONVERTER:** AN31-12, LB8

**ACTIVE FILTER (See Filter)**

## AGC

AGC/squelch amplifier: AN51

DC: AN72-7

Element comparison: AN51-1

Hints: AN51-4

Methods: AN51-1, AN72-7

Temperature compensation: AN51-11

## ALARM

Inexpensive IC: AN154

**AMBIENCE AMPLIFIER, REAR SPEAKER  
(4-CHANNEL) (See Amplifiers, Ambience)**

## AM/FM

Demodulators and detectors: AN46-11, AN54-8

Low cost AM radio: LB29

Stereo receiver: AN147

(See Also FM Stereo Amplifiers)

## AMMETER

AN71-5, AN71-6, LB37

## AMPLIFIERS

AC: AN31-1, AN31-18, AN48-4, AN72-6

Absolute value: AN31-12

Ambience: AN125-11

Anti-log generator: AN30-3, AN31-20

Audio: AN32-5, AN69, AN72-38

Battery powered: AN71-4, AN71-5, AN211

Bridge: AN29-12, AN31-11

Bridge, 4 watt: AN125-7

Buffered high current output: AN4-3, AN13-3,  
AN29-15, AN31-16, AN48-1, AN48-4

Cascode, FET: AN32-2, AN32-6

Cascode, RF: AN32-9

Chopper stabilized: AN38-4

Circuit description LH0002: AN13-2

Circuit description LH0033: AN48-1

Circuit description LM108/LM208/LM308: AN29-2,  
AN29-18

Circuit description LM118/LM218/LM318: LB17

Circuit description LM3900: AN72-1

Circuit description LM4250 micropower program-  
mable amp: AN71-1

Clamping: AN31-11, LB8-1

Class A audio: AN72-38

CMOS as linear amp: AN88

Difference: AN20-3, AN29-12, AN31-1, AN31-9,  
AN31-10, AN72-9

Differential input: LB20

Differentiator: AN20-3, AN31-2, AN72-34

Drift testing: AN79-3

Dual audio: AN125, AN147

Dual with single supply: AN116

Fet input: AN4-3, AN29-1, AN32-9, AN75

Follower (See Voltage Follower)

Frequency compensation: AN79-5

High current buffer: AN4-3, AN13, AN29-15,  
AN31-16, AN48-1, AN48-4

High input impedance: AN29-14, AN31-1, AN31-11,  
AN31-18, AN32-1, AN32-7, AN48-4, AN72-7,  
AN241, LB1-2

High speed: AN75, LB42

High voltage: AN72-37, AN127

Improved DC characteristics: AN79-1

Input guarding: AN29-16

Instrumentation: AN29-11, AN31-9, AN31-10,  
AN31-11, AN71-7, AN79-7, AN127-2, AN222,  
LB1, LB21

Instrumentation shield/line driver: AN48-3

Integrator: AN20-4, AN29-7, AN31-2, AN31-3,  
AN31-13, AN72-34, AN88-3

Integrator, J-FET AC coupled: AN32-1

Inverting: AN20-1, AN31-1, AN31-4, AN71-4,  
AN72-6, AN72-7, AN72-37, LB17-2

JFET: AN151-5

Level shifting: AN4-2, AN13-4, AN32-5, AN41-3, AN48-3

Line receiver: AN72-8

Linear multiple gain-controlled: AN129

Logarithmic converter: AN29-12, AN30, AN31-18,  
AN31-20

Low drift: AN79, AN222, LB22, LB24

Low Noise: AN222

Meter: AN71-5

Micropower: AN71

Nano-watt: AN71-4

Noise: AN63-2, AN70, AN241

Noise specifications: AN104, AN151, LB26

Non-inverting amplifier: AN20-2, AN31-1, AN31-4,  
AN72-6, AN72-9, AN72-37

Non-linear: AN4-4, AN31-16

Norton: AN72-1

Operational: AN4, AN20, AN29, AN31, AN241,  
Appendix A

Output resistance: AN29-5

Paralleling: LB44

Photocell: AN20-5, AN20-8

Photodiode: AN20-5, AN29-13, AN31-3, AN31-18,  
LB12-2

Photoresistor bridge: AN29-12

Piezoelectric transducer: AN29-13, AN31-17

Power: AN69, AN72-9, AN110-6, AN125, AN127-3,  
AN147 (See Also Buffer, High Current), LB44

Preamp: AN79, LB24

Pulse: AN13-4

Rejection, power supply: AN29-6

Reset stabilized: AN20-7

RF (See RF Amplifier)

Sample and hold: AN4-3, AN29-6, AN31-12, AN32-1,  
AN32-6, AN32-7, AN48-3, AN72-34, LB11-2

Single supply: AN72, AN211

Solar cell: AN4-5

Specifying selected parameters: LB26

Squaring: AN72-33

Squelch, AGC: AN51

Strain gauge: AN222

Summing: AN20-3, AN31-1, AN31-13

Temperature probe: AN31-17, AN56-3

Tutorial study of op amps: Appendix A

Variable gain: AN31-9, AN31-15, AN32-5, LB1-2  
(See Also AGC)

Very high current booster with high compliance:  
AN127-5

1A class AB current booster: AN127-4

100 mA current booster: AN127-4

90 watt audio: AN127-7

**ANALOG COMMUTATOR (See Analog Switches)**

**ANALOG DIVIDER:** AN4-5, AN30-4, AN31-19

**ANALOG MULTIPLIER:** AN4-5, AN20-8, AN30-4,  
AN31-15, AN31-17, AN31-19

**ANALOG SWITCH:** AN32-4, AN32-8, AN32-9,  
AN32-10, AN32-12

# Subject Index (Continued)

## ANALOG-TO-DIGITAL

Binary codes: AN156  
Converters: AN87-5, AN162, AN193, AN233, LB6-1, Appendix C, Appendix D  
Errors: AN156  
References: AN184  
Specifying: AN156  
Testing: AN179, AN233

**AND GATE:** AN72-27, AN74-9

**ANTI-LOG GENERATOR:** AN30-3, AN31-20

## ATTENUATION

Voltage controlled: AN129

**AUDIO AMPLIFIERS:** AN32-5, AN69, AN72-38

Audio power amps: AN125

Linear multiple gain controlled: AN129

Low cost IC stereo receiver: AN147

Low noise JFETs: AN151

90 watt: AN127-7

1A class AB current booster: AN127-4

100 mA current booster: AN127-4

(See Also FM Stereo, Amplifiers)

**AUDIO MIXER:** AN64-10, AN72-35

**AUTOMATIC GAIN CONTROL (See AGC)**

## AUTOMOTIVE

Anti-skid circuit: AN162

Tachometer: AN162

**BANDPASS FILTER:** AN72-15, LB11-2 (See Also

Notch Filter)

**BANDWIDTH, EXTENDED:** AN29-5, LB2, LB4, LB14, LB19

**BANDWIDTH, FULL POWER:** LB19-1

## BATTERY

Charger: LB35

Trickle charger: AN153-2

**BATTERY POWERED AMPLIFIERS:** AN71-4, AN71-5

**BI-QUAD FILTER:** AN72-17

**BIAS CURRENT COMPENSATION**

(See Drift Compensation)

**BIAS CURRENT TEST SET:** AN24-2

## BLINKER

Lamp: AN110-5

Low voltage IC: AN154-2

Two wire: AN154-4

**BOARD LAYOUT:** AN29-16

**BOLOMETER (COMPARATOR):** LB32

**BOOTSTRAPPED SHUNT FREQUENCY COMPENSATION:** AN29-16

**BREAKER POINT DWELL METER:** AN162

**BRIDGE AMPLIFIER:** AN29-12, AN31-11

## BUFFERS

Using CMOS amplifiers: AN88

(See Also Voltage Followers)

**BUFFER HIGH CURRENT:** AN4-3, AN13-3, AN29-15,

AN31-16, AN48-1, AN48-4, LB44

**BYPASSING, SUPPLY TERMINAL:** AN4-8, LB2-2, LB15-1

## CALIBRATOR

Oscilloscope square wave: AN154-8

**CAPACITANCE MULTIPLIER:** AN29-10, AN31-14, AN31-15

**CAPACITIVE TRANSDUCER:** AN162

## CAPACITORS

Bypass: AN4-8, LB2-2, LB15-1

Compensation: AN29-4 (See Also Frequency Compensation)

Dielectric polarization: AN29-7

Electrolytic as timing capacitor: AN97-5

Filter, power supply: AN23-7, LB10-2

Multiplier, capacitance: AN29-10, AN31-14, AN31-15

Switching regulator filter: AN21-11

Tantalum bypass: LB15-1

**CASCODE AMPLIFIER:** AN32-6, AN32-9

## CHARGER

Small battery trickle: AN153-2

**CHOPPER AMPLIFIERS, ALTERNATIVES:** AN79

## CIRCUIT DESCRIPTIONS

AM1000 Analog switch series: AN53-2

LH0002 Current amplifier: AN13-2

LH0033 Buffer amplifier: AN48-1

LM104/LM204/LM304 Negative voltage regulator: AN21-1, AN21-15

LM105/LM205/LM305 Positive voltage regulator: AN23-1, AN23-2

LM108/LM208/LM308 Operational amplifier: AN29-2, AN29-18

LM109/LM209/LM309 Three terminal regulator: AN42-1

LM110/LM210/LM310 Voltage follower: LB11

LM111/LM211/LM311 Voltage comparator: AN41-1, LB12

LM113 1.2 Volt reference diode: AN56

LM118/LM218/LM318 High slew rate op amp: LB17

LM381 Dual preamplifier: AN64-2

LM565 Phase locked loop: AN46-5

LM3900 Quad amplifier: AN72-1

LM4250 Micropower programmable op amp: AN71-1

## CLAMP

Precision: AN31-11, LB8-1

**CLASS A AUDIO AMPLIFIER:** AN72-38

**CMOS LINEAR AMPLIFIERS (See Amplifiers, CMOS)**

**CMOS LOGIC VOLTAGE REGULATOR:** AN71-7

**COLD JUNCTION COMPENSATION:** AN222, AN225

**COMPARATORS (See Voltage Comparators)**

**COMPENSATION, DRIFT (See Drift Compensation)**

**COMPENSATION, FREQUENCY (See Frequency Compensation)**

**COMPENSATION, TEMPERATURE (See Drift Compensation)**

**COMPONENT NOISE (See Noise, Component)**

**COMPRESSOR, VOLUME:** AN129-7

**CONTINUITY CHECKER, AUDIBLE:** AN154-5

## CONTROLLER

Temperature: AN132-7

## CONVERTER

100 MHz: AN32-3

AC to DC: AN31-12, LB8

Analog-to-digital: (See Analog-to-Digital)

Current-to-voltage: AN20-5, AN31-2, AN31-16, LB40

DC-to-DC: LB18 (See Also Switching Regulator)

Logarithmic: AN29-12, AN30, AN31-18, AN31-20

Voltage-to-current: LB40

**CONVERTER, FREQUENCY-TO-VOLTAGE:** AN97-10, AN210, LB45, Appendix C, Appendix D

**COUNTER, PULSE:** AN72-23

**CRYSTAL OSCILLATOR:** AN32-2, AN32-8, AN41-4

**CRYSTAL OVEN CONTROLLER:** LB31

**CUBE GENERATOR:** AN30-3, AN31-19

**CURRENT BOOSTER:** AN127-4, AN127-5

**CURRENT LIMITING:** AN103-3, AN153-3

Adjustable: AN21-7

External: AN21-9, AN29-16

External circuit: AN82-4

## Subject Index (Continued)

- Foldback: AN82 (See Foldback Current Limiting)
- Output short circuit: AN72-12
- Sense voltage reduction: AN21-4, AN21-7, AN31-16, AN32-11
- Switchback (See Foldback Current Limiting)
- Switching regulator: AN2-8, AN21-12
- Two terminal current limiter: AN110-4
- 1A 65V power supply with variable current limit: AN127-9
- CURRENT MIRROR:** AN72-2
- CURRENT MONITOR:** AN31-16, AN32-11 (See Also Current-to-Voltage Converter)
- CURRENT NOISE (See Noise, Current)**
- CURRENT SINK**
  - Fixed: AN72-31
  - Precision: AN20-6, AN31-8, AN32-6
- CURRENT SOURCE**
  - Bilateral: AN29-14, AN31-6
  - Constant current circuit element: AN153-3
  - High compliance: AN127-3
  - High current: AN42-6
  - Multiple: AN72-30
  - Precision: AN20-6, AN31-8, AN32-12
  - Two terminal: AN110-6
  - 200 mA: AN103-3
- CURRENT-TO-FREQUENCY CONVERTER:** AN240
- CURRENT-TO-VOLTAGE CONVERTER:** AN20-5, AN31-2, AN31-16
- CURRENT TRANSMITTER:** LB40
- D-TO-A CONVERTER (See Analog-to-Digital)**
- DC-TO-AC CONVERTER:** LB18
- DELAY SWITCH:** AN110-4
  - Two terminal: AN97-10 (See Also Timers)
- DEMODULATORS**
  - AM-FM: AN46-11
  - FM Stereo: AN81, AN147
  - Frequency shift keying: AN46-9
  - IRIG channel: AN46-8
  - Weather satellite picture: AN46-11
- DETECTORS**
  - Peak: AN87-5
  - Pulse width: (See Pulse Width Detectors)
  - True rms: LB25 (Also See Demodulators)
- DIELECTRIC POLARIZATION CAPACITOR:** AN29-7
- DIFFERENCE AMPLIFIER:** AN20-3, AN29-12, AN31-1, AN31-9, AN31-10, AN72-9
- DIFFERENCE INTEGRATOR:** AN72-34
- DIFFERENTIATOR:** AN20-3, AN31-2, AN72-34
- DIGITAL CIRCUITS**
  - Status Indicator: AN153-2
- DIGITAL SWITCHING CIRCUITS:** AN72-26
- DIGITAL-TO-ANALOG (See Analog-to-Digital)**
- DIGITAL-TO-ANALOG CONVERTER:** AN48-3
- DIODE**
  - Catch: AN21-11
  - Precision: AN31-11, AN173, LB8-1
  - Protective: AN21-8
  - Zener: AN-56
  - Zenered transistor base-emitter junction: AN71-8
- DISCRIMINATOR, MULTIPLE APERTURE WINDOW:** AN31-3
- DISTORTION**
  - Improving: AN129-3
- DIVIDER, ANALOG:** AN4-5, AN30-4, AN31-19, AN222
- DOUBLE ENDED LIMIT DETECTOR:** AN31-3
- DOUBLER, FREQUENCY:** AN41-4
- DRIFT**
  - Minimizing in amplifiers: LB-22, LB-32
- DRIFT COMPENSATION:** AN79-2
  - Bias current: AN3-1, AN20-1, AN29-8, AN31-3
  - Board layout: AN29-16
  - Gain, AGC: AN51-11
  - Gain, transistor: AN56-3
  - Guarding inputs: AN29-16
  - Integrator, low drift: AN31-13
  - Non-linear amplifiers: AN4-4, AN31-16
  - Offset voltage: AN3-3, AN20-1, AN31-4
  - Reset stabilized amplifier: AN20-7
  - Sample and hold: AN4-4, AN29-7
  - Transistor gain: AN56-3
  - Voltage regulator: AN21-4, AN23-4, AN42-6, LB15
- DRIFT, VOLTAGE AND CURRENT:** AN29-1 (See Also Drift Compensation)
- DRIVERS**
  - Lamp: AN125-9
  - Motor: AN125-9
  - Relay: AN125-9
  - Zero crossing detector and line driver: AN162 (Also See Voltage Followers, Buffers, Amplifiers)
- DUAL TRACKING REGULATORS (See Regulators, Dual Tracking)**
- DWELL METER:** AN162
- ECL (See Emitter Coupled Logic)**
- ELECTRONIC SHUTDOWN:** AN82, AN103-11
- EMITTER COUPLED LOGIC, DIRECT INTERFACING**
  - AN87-6
- ERRORS**
  - Low error amplifiers: LB21
  - Reducing comparator errors for 1  $\mu$ V sensitivity: LB32
- EXPANDER, VOLUME:** AN129-7
- FEEDFORWARD COMPENSATION:** LB2, LB14, LB17-2
- FERRITE BEAD:** AN23-6
- FET**
  - Amplifier: AN32
  - Operational amplifier input: AN4-3, AN29-1, AN32-9, AN75
  - Switches: AN32-4, AN32-8, AN32-9, AN32-10, AN32-12
  - Voltmeter, FET VM: AN32-2
- FILTER**
  - Adjustable Q: AN31-14, LB5-2
  - Bandpass: AN72-15, LB11-2 (See Also Filter, Notch)
  - Bi-quad: AN72-17
  - Full wave rectifying and averaging: AN20-8, AN31-12
  - High pass active filter: AN31-16, AN72-14, LB11-2
  - Low pass active filter: AN20-4, AN31-16, AN72-14
  - Notch: AN31-14, AN48-4, LB5, LB11-2
  - Notch, adjustable Q: AN31-14, LB5-2
  - Power supply: AN23-7, LB10-2
  - Sensitivity functions: AN72-13
  - Tone control: AN32-3, AN32-11, AN64-10
- FLASHER**
  - Inexpensive IC: AN154
  - Lamp: AN110-5
  - Two wire: AN154-4
- FLIP-FLOP, TRIGGER:** AN72-27
- FM STEREO**
  - Dual audio amplifier: AN125

## Subject Index (Continued)

- Expander block: AN129-8
- FM detector: AN147
- FM IF amplifier: AN147
- Low cost IC receiver: AN147
- Remote speaker: AN146
- Stereo demodulator: AN81, AN147
- Tone control: AN147
- 90 watt audio amplifier: AN127-7
  - (See Also Audio)
- FOLDBACK CURRENT LIMITING**
  - Negative voltage regulator: AN21-5, LB3-2
  - Positive voltage regulator: AN23-5, LB3-2
  - Power dissipation curve: AN23-6
  - Temperature sensitivity: AN23-6
    - (Also See Current Limiting, Foldback)
- FOLLOWERS, VOLTAGE (See Voltage Followers)**
- FREQUENCY COMPENSATION: AN79-5**
  - Bandwidth, extended: AN29-5, LB2, LB4, LB14, LB19, LB42
  - Bootstrapped shunt: AN29-16
  - Capacitance, stray: AN4-8, AN31-3
  - Capacitive loads: AN4-8, LB14-1, LB42
  - Differentiator: AN20-4
  - Feedforward: LB2, LB14, LB17-2
  - Ferrite bead: AN23-6
  - Hints: AN4-7, AN20-2, AN23-6, AN41-5, LB2, LB4, LB42
  - Multiplier: AN210
  - Multivibrator: AN4-1
  - Oscillation, involuntary: AN4-8, AN20-2, AN29-5
- FREQUENCY DOUBLER: AN41-4**
- FREQUENCY RESPONSE: LB19 (See Also Frequency Compensation)**
- FREQUENCY SHIFT KEYING DEMODULATOR: AN46-9**
- FREQUENCY-TO-CURRENT CONVERTER: AN162**
- FREQUENCY-TO-VOLTAGE CONVERTER: AN97-10, AN162, LB33, LB45, AN210**
- FULL POWER BANDWIDTH: LB19-1**
- FUNCTION GENERATOR (See Generator)**
- GAIN CONTROL**
  - Quad control: AN129-6
  - Voltage controlled: AN129
- GAIN TEST SET: AN24-4**
- GATES, OR AND AND: AN72-26**
- GENERATOR**
  - Multiple function: AN115, LB23
  - One shot: AN88-3
  - Sine wave: AN115
  - Square wave: AN88-3, AN115, AN154-8, LB23
  - Staircase: AN88-3, AN162
  - Triangle wave: AN115, LB23 (See Also Oscillator)
- GUARD DRIVER: AN48-3**
- GUARDING AMPLIFIER INPUTS: AN29-16**
- HALL EFFECT SENSOR (COMPARATOR): LB32**
- HIGH PASS ACTIVE FILTER: AN31-16, AN72-14, LB11-2**
- HIGH SPEED OP AMP: AN75, LB42**
- HIGH VOLTAGE**
  - Flasher: AN154-3
  - Op Amp: AN127
  - Regulator: AN103-9
- IF AMPLIFIER**
  - FM Stereo: AN147
- INDICATOR**
  - Applications: AN154
  - Universal: AN153
- INDUCTOR**
  - Core, switching regulator: AN21-11
  - Ferrite bead: AN23-6
  - Simulated: AN31-15
- INSTRUMENTATION AMPLIFIER: (See Amplifiers, Instrumentation)**
- INTEGRATOR: AN20-4, AN29-7, AN31-2, AN31-3, AN31-13, AN32-1, AN72-34, AN75-3**
- INTERNAL TIMER: AN31-17**
- INVERTING AMPLIFIER: AN20-1, AN31-1, AN31-4, AN71-4, AN72-6, AN72-7, AN72-37, LB17-2**
- ISOLATION, DIGITAL: AN41-3**
- JFETs**
  - Low noise: AN151
  - Selection guide: AN151
- LAMP DRIVER**
  - Ground referenced: AN72-36
  - Voltage comparator: AN4-2, AN72-29, LB12-2
- LARGE SIGNAL RESPONSE: LB19**
- LED (See Light Emitting Diode)**
- LEVEL DETECTOR WITH HYSTERESIS: AN87-6**
- LEVEL SHIFTING AMPLIFIER: AN4-2, AN13-4, AN32-5, AN41-3, AN48-3**
- LIGHT ACTIVATED SWITCH: AN110-5**
- LIGHT EMITTING DIODE**
  - AC operated: AN153
  - As an active load: AN153-3
  - Constant current: AN153
  - 1.5V LED flasher: AN154-1
- LIMIT DETECTOR: AN31-3**
- LIMITER (See Clamp)**
- LINE DRIVER: AN13-4, AN48-3**
- LINE RECEIVER AMPLIFIER: AN72-8**
- LINE RECEIVERS, COMPARATORS SUITABLE FOR: AN87**
- LIQUID DETECTOR: AN154-1, 4**
- LOGARITHMIC AMPLIFIER: AN29-12, AN30, AN31-18, AN31-20, AN211**
- LOW PASS ACTIVE FILTER: AN20-4, AN31-16, AN72-14**
- LOW DRIFT AMPLIFIERS (See Amplifiers, Low Drift)**
- MAGNETIC**
  - Variable reluctance pickup buffer: AN162
- MAGNETIC TRANSDUCER AMPLIFIER: AN74-6**
- METER AMPLIFIER: AN71-5, AN222**
- MICROPHONE PREAMPLIFIER: AN51-7**
- MICROPOWER**
  - Amplifier: AN71, AN211
  - Circuit description LM4250 programmable op amp: AN71-1
  - Voltage comparator: AN71-4
- MIXER**
  - Audio: AN64-10, AN72-35
  - Low frequency: AN72-35
- MODULATOR**
  - AM/IF: AN51-9
  - Pulse width: AN31-5
- MOISTURE DETECTOR: AN154-1, 4**
- MONOSTABLE MULTIVIBRATORS: AN72-27**
- MOTION DETECTOR (See Sensor, Air; Sensor, Liquid)**
- MOTOR DRIVE, 2 PHASE: AN125-9**
- MULTIPLEXER (See Analog Switch)**
- MULTIPLIER**
  - Analog: AN4-5, AN20-8, AN30-4, AN31-15, AN31-17, AN31-19, AN222
  - Capacitance: AN29-10, AN31-14, AN31-15
  - Cube generator: AN30-3, AN31-19

## Subject Index (Continued)

- Resistance: AN29-14
- MULTIVIBRATOR:** AN4-1, AN24-6, AN31-6, AN41-4, AN71-6, AN72-19
- NAB TAPE PLAYBACK PREAMPLIFIER:** AN64-4
- NAB TAPE RECORD PREAMPLIFIER:** AN64-7
- NEGATIVE AND POSITIVE VOLTAGE REGULATORS (See Symmetrical Voltage Regulators)**
- NEGATIVE VOLTAGE REGULATOR (See Negative Voltage Regulators)**
- NEGATIVE SWITCHING VOLTAGE REGULATORS:** AN2-10, AN21-10, AN21-11, AN21-12, AN21-13
- NEGATIVE VOLTAGE REFERENCE:** AN20-6, AN31-8
- NEGATIVE VOLTAGE REGULATOR**
  - Circuit description LM104/LM204/LM304: AN21-1, AN21-15
  - Drift compensation (See Drift Compensation, Voltage Regulator)
  - Foldback current limiting: AN21-5, LB3-2
  - High current: AN21-3, AN21-4, AN21-5, LB10
  - High voltage: AN21-9
  - Hints: LB10-2, LB15
  - Line regulation improvement: AN21-7
  - Low dropout voltage: AN211
  - Overvoltage protection: AN21-8
  - Power dissipation: AN21-3, AN21-5
  - Precision, stable: LB15-2
  - Programmable: AN20-11, AN31-7
  - Protective diodes: AN21-8
  - Remote sensing: AN21-4, AN21-9
  - Ripple: AN21-2, AN21-6
  - Three terminal: AN182
  - Transient response: AN21-2
- NIXIE DRIVER:** AN32-6
- NOISE**
  - Component: AN104
  - Current: AN104, AN151
  - Figure: AN104, AN151
  - Filtering in microvolt comparators: LB32
  - Generator, "buzz box": AN154-5
  - Solving noise problems with JFETs: AN151
  - Thermal: AN104
  - Theory: AN222
  - Voltage: AN104, AN151
  - I/F: AN104
- NOISE, AMPLIFIER AND RESISTOR:** AN70
- NON-INVERTING AMPLIFIER:** AN20-2, AN31-1, AN31-4, AN72-6, AN72-9, AN72-37
- NON-LINEAR AMPLIFIER:** AN4-4, AN31-6
- NORTON AMPLIFIER:** AN72-1
- NOTCH FILTER:** AN31-14, AN48-4, LB5, LB11-2
- OFFSET**
  - Adjusting offset and drift to almost zero: AN79, LB32
- OFFSET CURRENT TEST SET:** AN24-3
- OFFSET VOLTAGE ADJUSTMENT:** LB9
- OFFSET VOLTAGE COMPENSATION (See Drift Compensation)**
- OFFSET VOLTAGE TEST SET:** AN24-3
- ONE SHOT:** AN72-27, AN88-3
- OPERATIONAL AMPLIFIERS: (See Amplifiers, Operational)**
- OPERATIONAL AMPLIFIER TEST SET:** AN24
- OPTICALLY ISOLATED SWITCHES (See Switches, Optically Isolated)**
- OR GATE:** AN72-26, AN74-10
  - Regulator: AN103-11
- OSCILLATION, INVOLUNTARY (See Frequency Compensation)**
- OSCILLATOR**
  - Crystal: AN41-4, AN74-7
  - Crystal JFET: AN32-2, AN32-8
  - Inexpensive IC: AN154
  - Modulated RF: AN51-9
  - Morse code: AN154-6
  - Multivibrator: AN4-1, AN24-6, AN31-6, AN41-4, AN71-6, AN72-19
  - Piezoelectric driver: AN72-37
  - Programmable "unijunction": AN72-39
  - Pulse: AN97-10
  - Pulse output: AN71-6, AN72-20
  - Quadrature output: AN31-5, LB16
  - RF JFET: AN32-2, AN32-8
  - Sawtooth: AN72-22
  - Sine wave: AN20-9, AN29-9, AN31-5, AN31-6, AN31-7, AN32-7, AN32-8, AN51-8, AN72-19, AN115, LB16
  - Square wave: AN88-3
  - Staircase: AN72-23
  - Triangle wave: AN20-10, AN24-6, AN31-6, AN72-21
  - Tunable frequency: AN51-9, LB16
  - Voltage controlled: AN81-3, AN162
  - Wein bridge: AN20-9, AN31-6, AN31-7, AN32-7, AN51-8
  - Wein bridge power: AN125-9 (See Also Generator)
- OVEN CONTROLLER, TEMPERATURE:** LB31
- OVERSPEED LATCHES/INDICATORS (See Frequency To Voltage)**
- OVERVOLTAGE PROTECTION**
- PARALLELING OP AMP:** LB44
- PEAK DETECTOR:** AN4-4, AN31-12, AN51-5, AN51-6, AN72-36, AN74-16, AN75-3, AN87-5
  - Full wave precision: AN129-6
- PHASE**
  - Phase locked loop: AN81-3
  - Phase shift oscillator: AN88-3
  - PLL range extender: AN162
- PHASE COMPARATOR:** AN72-25
- PHASE LOCKED LOOP**
  - Advantages as voltage-to-frequency converter: AN210
  - Circuit description LM565: AN46-5
  - Damping: AN46-3
  - Locking: AN46-5
  - Loop filter: AN46-2
  - Multiamplifier: AN72-24, AN72-26
  - Noise performance: AN46-5
  - Phase comparator: AN72-25
  - Theory: AN46-1
  - VCO: AN72-24
  - Wide range: AN207
- PHASE SHIFTER:** AN32-8
- PHONE PREAMPLIFIER:** AN32-4, AN32-11, AN64-8, AN222
- PHOTOCELL AMPLIFIER:** AN20-5, AN20-8
- PHOTODIODE**
  - Amplifier: AN20-5, AN29-13, AN31-3, AN31-18, LB12-2
  - Level detector: AN41-2
- PHOTORESISTOR AMPLIFIER:** AN29-12
- POLARIZATION, DIELECTRIC:** AN29-7
- POSITION SENSOR:** AN129-9, AN162
- POSITIVE AND NEGATIVE VOLTAGE REGULATORS (See Symmetrical Voltage Regulators)**
- POSITIVE REGULATOR (See Regulator, Positive)**

# Subject Index (Continued)

**POSITIVE VOLTAGE REFERENCE:** AN20-6, AN31-2, AN31-8, AN56

## **POSITIVE VOLTAGE REGULATOR**

Adjustable output: AN42-5, AN178, AN181, AN182, LB35

Bootstrapped regulator: AN211

Circuit description LM105/LM205/LM305: AN23-1, AN23-2, AN211

Circuit description LM109/LM209/LM309: AN42-1  
CMOS compatible: AN71-7

Current limit: AN72-12, AN211

Drift compensation (See Drift Compensation, Voltage Regulator)

Failure mechanisms: AN23-7, LB3

Filtering, power supply: AN23-7, LB10-2

Fixed output: AN42-5

Foldback current limiting: AN23-5, LB3-2

Heat dissipation: AN1-8, AN23-3, AN23-6, AN23-7, LB3

High current: AN23-4, AN23-5, AN23-6, AN72-11, LB3, LB10-1

High voltage: AN72-11, AN211, LB47

Hints: AN23-7, LB3, LB10-2, LB15

Low voltage: AN56-3, AN211

Micropower quiescent power drain: AN71-7, AN211

NPN pass transistors: AN72-11, LB10-1

Power limitations: AN23-3, LB3

Precision: AN42-6, LB15

Programmable low power: AN20-11, AN31-7

Protection: AN23-7, AN72-11

Ripple induced failures: AN23-7, LB10-2

Switching regulator (See Switching Regulator)

Temperature compensation: AN42-6, LB15

Three terminal: AN103, AN178, AN182, LB35

Trimming output voltage: LB46

(See Also Voltage Regulators)

**POWER AMPLIFIER (See Buffer, High Current)**

## **POWER DISSIPATION**

Regulator: AN82-15, AN103-3

## **POWER SUPPLY**

General purpose: LB28

Monitor: LB48

Programmable: LB49 (See Also Regulators)

## **PREAMPLIFIER**

Circuit description LM381 dual preamplifier: AN64-2

Flatband: AN70-3

Low noise: AN70

Microphone, squelched: AN51-7

Phono: AN32-4, AN32-11, AN64-8

Servo: AN4-4, AN31-16

Stereo: AN64-10, AN64-11

Tape playback: AN64-4

Tape record: AN64-7

VOX: AN51-8 (See Also Amplifiers, Preamp)

**PROBE WITH SERVO'D SHIELD:** AN132-5

**PROGRAMMABLE OP AMP:** AN71

**PROGRAMMABLE "UNIUNCTION" OSCILLATOR:** AN72-39

**PROGRAMMABLE VOLTAGE REGULATOR:**

AN20-11, AN31-7

**PULSE AMPLIFIER:** AN13-4

**PULSE COUNTER:** AN72-23

**PULSE GENERATOR:** AN71-6, AN72-20, AN74-7

**PULSE WIDTH DETECTOR:** AN97-9

**PULSE WIDTH MODULATOR:** AN31-6, AN74-15

**QUAD AMPLIFIER:** AN72

**QUAD COMPARATOR:** AN74

**QUADRATURE OSCILLATOR:** AN31-5, LB16

## **RECEIVER**

FM remote speaker: AN146-2

Low cost AM receiver: LB29

Low cost FM stereo receiver: AN147

**RECTIFIER, FAST HALF-WAVE:** AN31-11, LB8-1

**RECTIFIER, FULL-WAVE:** AN20-8, LB8-2

## **REFERENCE**

Low drift precision 6.9V: AN161, AN173, AN184, LB31

Micropower: AN222, LB34, LB41

Precision: AN79-8, AN161, LB41

**REFERENCE VOLTAGE REGULATOR:** AN20-6, AN31-2, AN31-8

**REGULATORS (See Voltage Regulators)**

**RELAY DRIVER:** AN72-36

## **REMOTE SENSING**

High current negative regulator: AN21-4

High negative voltage: AN21-9

**REMOTE SPEAKER SYSTEM:** AN146

**RESET STABILIZED AMPLIFIER:** AN20-7

## **RESISTANCE**

Choice of resistors for op amps: AN79-3

Tester for low values of resistance: LB32

**RESISTANCE MULTIPLICATION:** AN29-14

**RESISTOR NOISE:** AN70-2

## **RF AMPLIFIER**

Cascade: AN32-9

**RF OSCILLATOR (See Oscillator, RF)**

**RIAA PHONE PREAMPLIFIER:** AN64-8

**RIPPLE, POWER SUPPLY:** AN21-2, AN21-6, AN23-7, LB10-2

**RISE TIME, AMPLIFIER:** LB19-2

## **RMS**

True rms detector: LB25

**ROOT EXTRACTOR:** AN4-6, AN31-18

**SAFE AREA PROTECTION:** AN103-2

**SAMPLE AND HOLD:** AN4-3, AN29-6, AN31-12, AN32-2, AN32-6, AN32-7, AN72-34, AN75-3, LB11-2, LB45

**SAWTOOTH GENERATOR:** AN72-22

**SCHMITT TRIGGER:** AN32-12, AN72-30

**SCR (See Silicon Controlled Rectifier)**

**SENSE VOLTAGE (See Current Limiting)**

**SENSITIVITY FUNCTIONS:** AN72-13

## **SENSOR**

Air velocity: AN132-7, AN132-8

Liquid: AN132-7

Mass velocity: AN162

Position: AN132-9

Rotational velocity: AN162

Servo'd shield: AN132-6

Speed: AN162, LB33

Temperature: AN132

**SERVO PREAMPLIFIER:** AN4-4, AN31-16

**SETTLING TIME:** LB17-2

**SHORT CIRCUIT PROTECTION (See Current Limiting)**

**SIGNAL TO NOISE RATIO:** AN104

**SILICON CONTROLLED RECTIFIER**

Short indicator: AN153-2

**SINE WAVE GENERATOR:** AN115

**SINE WAVE OSCILLATOR:** AN20-9, AN29-9, AN31-5, AN31-6, AN31-7, AN32-7, AN32-8, AN51-8, AN72-19, LB16

**SINE WAVE RESPONSE:** LB19

**SINGLE SUPPLY AMPLIFIER:** AN72

## Subject Index (Continued)

- SINGLE SUPPLY OPERATION:** AN31-2, AN48-4  
**SIREN OSCILLATOR:** AN154  
**SLEW RATE:** LB17, LB19, LB42 (See Also Frequency Compensation, Feedforward)  
**SLEW RATE LIMITING:** LB19  
**SMALL SIGNAL RESPONSE:** LB19  
**S/N RATIO (See Signal To Noise Ratio)**  
**SOLAR CELL AMPLIFIER:** AN4-5  
**SQUARE ROOT CIRCUIT:** AN4-6, AN31-18, AN222  
**SQUARE WAVE GENERATOR:** AN74-6  
**SQUARING AMPLIFIER:** AN72-33  
**SQUELCH AMPLIFIER, AGC:** AN51  
**SQUELCH RELEASE TIMING:** AN51-12  
**SQUELCHED PREAMPLIFIER:** AN51-7  
**STAIRCASE GENERATOR:** AN72-23, AN72-24  
(See Also Generator, Staircase)  
**SOUND**  
Sound effects oscillator: AN154-6, AN154-7  
**SPEED SENSOR (See Sensor, Speed)**  
**SPEED SWITCH (See Frequency To Voltage Converter)**  
**SQUARE WAVE GENERATOR:** AN88-3, AN115, AN154-8, AN222, LB23  
**SQUARING CIRCUITS:** AN222  
**STEP RESPONSE:** LB19-2  
**STEREO (See FM Stereo)**  
**STEREO PREAMPLIFIER:** AN64-10, AN64-11  
**SUBTRACTOR (See Difference Amplifier)**  
**SUMMING AMPLIFIER:** AN20-3, AN31-1, AN31-13  
**SUPPLY VOLTAGE SPLITTING:** AN31-2  
**SWITCHES**  
Optically isolated: AN110-5  
Two terminal time delay: AN97-10  
**SWITCH, ANALOG:** AN32-4, AN32-8, AN32-9, AN32-10, AN32-12  
**SWITCHBACK CURRENT LIMITING (See Foldback Current Limiting)**  
**SWITCHING AND LINEAR REGULATOR COMBINATION:** AN2-11  
**SWITCHING REGULATOR**  
Capacitor selection: AN21-11  
Catch diode selection: AN21-11  
Current limiting: AN2-8, AN21-12  
DC plus to DC minus converter: LB18  
Dissipation: AN21-11  
Driver: AN2-7, AN21-14  
Efficiency: AN2-5, AN2-6, AN2-7, AN21-10  
Frequency of operation: AN2-4, AN2-5, AN2-6, AN2-7  
High negative current: AN21-11, AN21-12, AN21-13  
High positive current: AN2-6  
High voltage: AN2-11  
Hints: AN21-11  
Inductor core selection: AN21-11  
Line regulation: AN2-6, AN21-11  
Negative: AN2-10, AN21-10, AN21-11, AN21-12, AN21-13  
Overload shutdown: AN21-13  
Polarity conversion: LB18  
Ripple: AN2-4, AN21-11  
Self-oscillating: AN2-2, AN21-10  
Shutdown: AN21-13  
Switching: AN97-9, AN110-4  
Symmetrical: AN2-10  
Synchronous: AN2-7, AN21-14  
Theory: AN2-2, AN21-10, LB18  
**SYMMETRICAL SWITCHING VOLTAGE REGULATOR:** AN2-10  
**SYMMETRICAL VOLTAGE REGULATOR**  
Regulation: AN21-6  
Tracking regulator: AN20-10, AN21-6, LB7  
**TACHOMETER:** AN72-32, AN97-10  
**TAPE PLAYBACK PREAMPLIFIER:** AN64-4  
**TAPE PLAYER**  
Amplifier: AN147  
**TAPE RECORD PREAMPLIFIER:** AN64-7  
**TELEVISION**  
A color TV primer for the E. E.: Appendix B  
**TEMPERATURE**  
Controller: LB36  
Timer used as controller: AN97-8  
Transducer: AN132, AN225  
Transducer, micropower: LB27  
**TEMPERATURE COMPENSATED ZENER DIODE:** AN56  
**TEMPERATURE COMPENSATION (See Drift Compensation)**  
**TEMPERATURE PROBE AMPLIFIER:** AN31-17, AN56-3  
**TEMPERATURE PROBE COMPARATOR:** AN72-38  
**TEMPERATURE TO FREQUENCY CONVERTER:** AN132-4  
**TEST SET, OPERATIONAL AMPLIFIER:** AN24  
**THERMAL FEEDBACK REDUCTION IN MICRO-VOLT COMPARATORS:** LB32  
**THERMAL NOISE (See Noise, Thermal)**  
**THERMAL SHUTDOWN:** AN82, AN103-2  
**THERMOCOUPLE**  
Amplifier with cold junction compensation: AN211, AN222, AN225, LB24  
Comparator: LB32  
Effects on IC's: AN79, LB22, LB32  
**THERMOMETER**  
Electronic: AN132-7, AN225, AN233  
Micropower: LB27, AN211  
Temperature controller: AN97-8  
Thermocouple: LB24  
**THERMOMETER, ELECTRONIC:** AN31-17, AN56-3  
**THRESHOLD DETECTOR:** AN20-10, AN31-3  
**TIME DELAY GENERATOR:** AN74-11  
**TIME, INTERVAL:** AN31-17  
**TIMERS**  
Chain of timers: AN97-11  
Cycle interrupt: AN97-6  
Dual supply operation: AN97-7  
Electrolytic timing capacitors: AN97-5  
Eliminating timing cycle upon initial application of power: AN97-5  
Inexpensive 6-second: AN153-3  
Linearizing charging sweep: AN97-7  
Negative pulse triggering: AN97-11  
Noise immunity: AN97-6  
One hour: AN97-9  
Time delay circuit: AN110-4  
Time out, power up: AN97-8  
Wide range timer: LB38  
Zero power dissipation between timing intervals: AN97-10  
5V logic supply driving 28V relay: AN97-7  
30V supply interfacing with 5V logic: AN97-8  
**TIMING ERROR:** AN97-4  
**TOPE CONTROL:** AN32-3, AN32-11, AN64-10  
Stereo: AN147

# Subject Index (Continued)

- TRACKING VOLTAGE REGULATOR:** LB7 (See Also Symmetrical Voltage Regulators)
- TRANSDUCER**  
Amplifier: LB24  
Crystal oven controller: LB31  
Temperature: AN132, LB27
- TRANSFER FUNCTION TEST SET:** AN24-4
- TRANSISTOR**  
Low noise: AN222  
Optically isolated: AN110-5  
Power, protected: AN110
- TRANSMITTER**  
FM remote speaker: AN146-1  
Two wire: AN211
- TRIAC TRIGGER:** AN154-7
- TRIANGLE WAVE GENERATOR:** AN115
- TRIANGLE WAVE OSCILLATOR:** AN20-10, AN24-6, AN31-6, AN72-21
- TRIGGER APPLICATIONS:** AN154
- TRIGGER FLIP-FLOP:** AN72-27
- TRIGGER, SCHMITT:** AN32-12, AN72-30
- TUNED RF CIRCUITS** (See Amplifiers)
- TV** (See Television)
- UNITY-GAIN BUFFER:** AN20-2
- VCO** (See Voltage Controlled Oscillator)
- VELOCITY SENSOR** (See Sensor, Velocity)
- VIDEO CIRCUITS**  
A color TV primer for the E. E.: Appendix B  
Low noise, very low input capacitance video amplifier: AN151-4
- VOLTAGE COMPARATOR**  
A-to-D converter circuit: LB6-1  
AC coupled: LB6-2  
Avoiding oscillations: LB39  
Buffered output: AN29-15  
Circuit description LM111/LM211/LM311: AN41-1, LB12  
Comparison: AN87, LB12-2  
DTL driver: AN4-2, AN29-15, AN31-3, LB12-2  
Dual limit, high speed: AN48-3  
Fast: LB-6  
High current: AN71-4  
Hints: AN41-5  
Lamp driver: AN4-2, AN72-29, LB12-2  
Micropower: AN71-4  
Microvolt: LB32  
MOS driver: AN41-2, AN41-3, LB12-2  
Op amp voltage comparator: AN4-2, AN71-4, AN72-29  
Preamplifier: LB32  
Power: AN125-9  
Quad array: AN74  
Specifying selected parameters: LB26  
Timers used as: AN97-6  
TTL driver: AN4-2, AN29-15, AN31-3, AN41-2, AN41-3, LB12-2  
Zero crossing: AN31-17, AN41-2, AN41-3, LB6-2, LB12-2
- VOLTAGE CONTROLLED OSCILLATOR:** AN72-24, AN74-8, AN81-3, AN162
- VOLTAGE FOLLOWER**  
Bias current: AN20-3  
Circuit description LH0033: AN48-1  
Circuit description LM110/LM210/LM310: LB11  
Comparison: LB11-2  
Frequency compensation: LB42  
Hints, operating: AN20-2  
Offset adjustment: AN31-4, LB9-2  
Single supply: AN72-10  
Voltage reference: AN20-6, AN31-2, AN31-8, AN56  
1 amp: AN110-6  
(See Also Followers, Voltage)
- VOLTAGE NOISE** (See Noise, Voltage)
- VOLTAGE REFERENCES** (See References, Voltage)
- VOLTAGE REGULATORS**  
(See Also Regulators, Voltage; Positive, Negative, or Switching Voltage Regulator)  
Adjustables: AN178, AN181, AN211, LB46  
Current: AN103-3, AN110-6, AN127-3  
Dual tracking: AN82, AN103-8, AN103-9, Appendix C  
High current: AN103-3, AN103-5, AN110-4, AN110-5  
High current dual tracking: AN82-4  
High input voltage: AN103-9, AN211  
Improving reliability: AN182  
Paralleling: Appendix C  
Power distribution and regulation can be simple, cheap and rugged: Appendix C  
Trimming: LB46  
Using audio power amp: AN125-9  
1A, 65V with variable current limit: AN127-9  
±32.5V dual tracking: AN127-9
- VOLTAGE-TO-FREQUENCY CONVERTER:** AN210, AN240, LB45, Appendix C, Appendix D  
(See Also Analog-to-Digital Converters)
- VOLTMETER:** AN32-2, AN71-6, AN75-4, LB45
- VOLUME COMPRESSOR/EXPANDER (COMPANDER):** AN129-7
- VOX PREAMPLIFIER:** AN51-8
- WEIN BRIDGE OSCILLATOR:** AN20-9, AN31-6, AN31-7, AN32-7 AN51-8
- WEIN BRIDGE POWER OSCILLATOR:** AN125-9
- WIND VELOCITY INDICATOR:** AN132-8
- WINDOW DISCRIMINATOR, MULTIPLE APERTURE:** AN31-3
- ZENER DIODE**  
IC: AN56  
Transistor base-emitter junction: AN71-8
- ZENERS** (See References, Voltage)
- ZERO CROSSING DETECTOR:** AN31-17, AN41-2, AN41-3, AN74-5, LB6-2, LB12-2  
Comparators suitable for "two shot": AN87, AN162
- ZEROING, AMPLIFIER:** AN63-8



# Designing Switching Regulators

National Semiconductor  
Application Note 2  
March 1969



## INTRODUCTION

The series pass element in a conventional series regulator operates as a variable resistance which drops an unregulated input voltage down to a fixed output voltage. This element, usually a transistor, must be able to dissipate the voltage difference between the input and output at the load current. The power generated can become excessive, particularly when the input voltage is not well regulated and the difference between the input and output voltages is large.

Switching regulators, on the other hand, are capable of high efficiency operation even with large differences between the input and output voltages. The efficiency is, in fact, negligibly affected by the voltage difference since this type of regulator acts as a continuously-variable power converter.

Switching regulators are, therefore, useful in battery-powered equipment where the required output voltage is considerably lower than the battery voltage. An example of this is a missile with a 30V battery as its only power source, containing a large number of integrated logic circuits which require a 5V supply. Switching regulators are also useful in space vehicles where conservation of power is extremely important. In addition, they are frequently the most economical solution in commercial and industrial applications where the increased efficiency reduces the cost of the series-pass transistors and simplifies heat sinking.

One of the disadvantages of switching regulators is that they are more complex than linear regulators, but this is often a substitution of electrical complexity for the thermal and mechanical complexity of high power linear regulators. Another disadvantage is higher output ripple. However, this can be held to a minimum (about 10 mV) and it is at a high enough frequency so that it can be easily filtered out. Another limitation is that the response to load transients is not always as fast as with linear regulators, but this can be largely overcome by proper design. The rejection of line transients, however, is every bit as good if not better than linear regulators. Lastly, switching regulators throw current transients back into the unregulated supply which are somewhat larger than the maximum load current. These, in some cases, can be troublesome unless adequate filtering is used.

This article will demonstrate the use of a monolithic voltage regulator in a number of switching regulator applications. These include both self-oscillating and synchronously driven regulators in the 0.1A to 5A range. Circuits are shown for both positive and negative regulators with output voltages in the 2V to 30V range. Methods of isolating the integrated circuit from the input voltage are given, permitting input voltages in excess of 100V. Further, current limiting schemes which keep peak currents and dissipation well within safe limits for both over-load and short-circuit conditions are presented. Finally, component selection details peculiar to switching regulators are covered.

## SWITCHING REGULATOR OPERATION

The method by which a switching regulator produces a voltage conversion with high efficiency can be explained with the aid of Figure 1.  $Q_1$  is a switch transistor which is turned on and off by a pulse waveform with a given duty cycle, and  $D_1$  is a catch diode which provides a continuous path for the inductor current when  $Q_1$  turns off. The voltage waveform on the collector of  $Q_1$  will be as shown in the figure. The output of the LC filter will be the average value of the switched waveform,  $V_1$ . If the voltage drops across the transistor and diode are neglected, the output voltage will be

$$V_{OUT} = V_{IN} \frac{t_{ON}}{T} \quad (1)$$

and it is independent of the load current. It is obvious from the equation that changes in input voltage can be compensated for by varying the duty cycle of the switched waveform. This is what is done in a switching regulator.

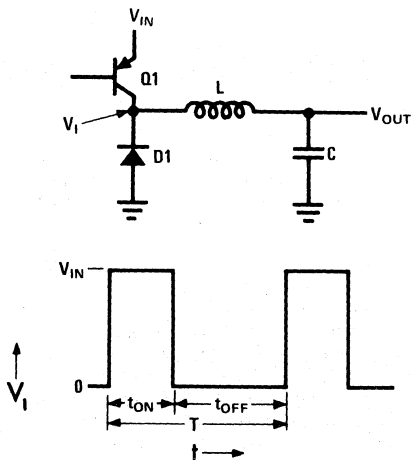


FIGURE 1  
Switching Circuit for Voltage Conversion

Figure 2 shows a self-oscillating switching regulator which produces this duty-cycle control. A reference voltage,  $V_{REF}$ , equal to the desired output voltage, is supplied to one input of an operational amplifier,  $A_1$ . The operational amplifier, in turn, drives the switch transistor. The resistive divider, arranged such that  $R_1 \gg R_2$ , provides a slight amount of positive feedback at high frequencies to make the circuit oscillate. At lower frequencies where the attenuation of the LC filter is less than the attenuation of the resistive divider, there is net negative feedback to the inverting input of the operational amplifier.

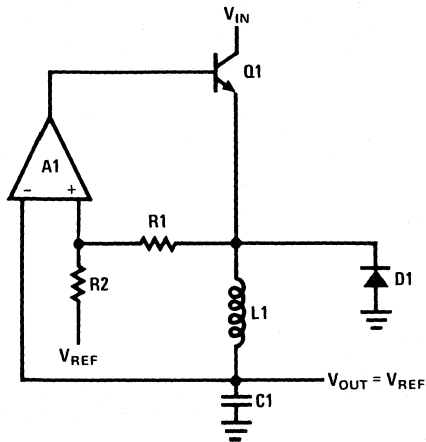


FIGURE 2  
Self-oscillating Switching Regulator



In operation, when the circuit is first turned on, the output voltage is less than the reference voltage so the switch transistor is turned on. When this happens, current flow through  $R_1$  raises the voltage on the non-inverting input of the operational amplifier slightly above the reference voltage. The circuit will remain switched on until the output rises to this voltage. The amplifier now goes into the active region, causing the switch to turn off. At this point, the reference voltage seen by the amplifier is lowered by feedback through  $R_1$ , and the circuit will stay off until the output voltage drops to this lower voltage. Hence, the output voltage oscillates about the reference voltage. The amplitude of this oscillation (or the output ripple) is nearly equal to the voltage fed back through  $R_1$  to  $R_2$  and can be made quite small.

## THE LM100

The switching regulator circuits described here use the LM100 integrated voltage regulator as the control element. This device contains, on a single silicon chip, the voltage reference, the operational amplifier and the circuitry for driving a PNP switch transistor. Discrete switch transistors, catch diodes and reactive elements are employed since these components are not easily integrated.

A complete circuit description of the LM100 is given in Application Note AN-1 along with a number of its applications as a linear regulator. However, a brief description will be included here in order to facilitate understanding of the regulator circuits which follow.


Figure 3 shows a schematic diagram of the LM100. The voltage reference portion of the circuit starts with a breakdown diode,  $D_1$ , which is supplied by a current source from the unregulated input (one of the collectors of  $Q_2$ ). The output of the reference diode, which has a positive temperature coefficient of  $2.4 \text{ mV}/^\circ\text{C}$ , is buffered by an emitter follower,  $Q_4$ , which increases the temperature coefficient to  $+4.7 \text{ mV}/^\circ\text{C}$ . This is further increased to  $7 \text{ mV}/^\circ\text{C}$  by the diode-connected transistor,  $Q_6$ . A resistor divider reduces this voltage as well as the temperature coefficient to exactly compensate for the negative temperature coefficient of  $Q_7$ , producing a temperature-compensated output of  $1.8 \text{ V}$ .

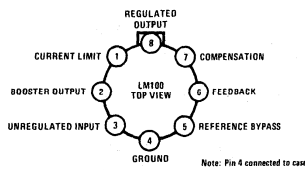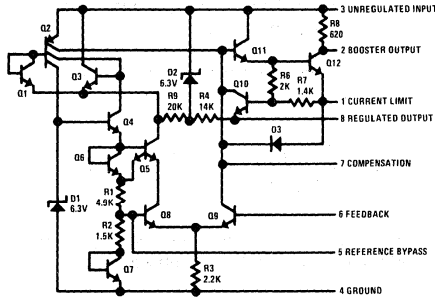

**FIGURE 3**  
Schematic and Connection Diagrams of the LM100 Voltage Regulator

The transistor pair,  $Q_8$  and  $Q_9$ , form the input stage of the operational amplifier. The gain of the stage is made high by the use of a current source, one of the collectors of  $Q_2$ , as a collector load. The output of this stage drives a compound emitter follower,  $Q_{11}$  and  $Q_{12}$ . The output of  $Q_{12}$  is taken across  $R_8$  to drive the PNP switch transistor. An additional transistor,  $Q_{10}$ , is used to limit the

output current of  $Q_{12}$  to the value required for driving a PNP transistor connected on the booster output. This current is determined by a resistor placed between the current limit and regulated output terminals. The value of the drive current can be determined from Figure 4 which plots the output current as a function of temperature for various current limit resistors.

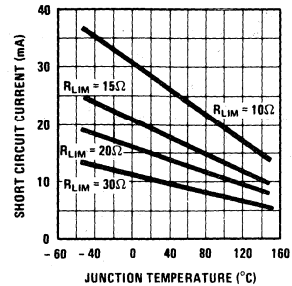


**FIGURE 4**  
Switched Output Current as a Function of Temperature for Various Values of Current Limit Resistors

As for the remaining details of the circuit,  $Q_5$ ,  $Q_3$  and  $Q_1$  are part of a bias stabilization circuit for  $Q_2$  to set its collector currents at the desired value.  $R_9$ ,  $R_4$  and  $D_2$  serve the sole function of starting the regulator. Lastly,  $D_3$  is a clamp diode which keeps  $Q_9$  from saturating when it is switching.

## SWITCHING REGULATOR CIRCUITS

Figure 5 demonstrates the use of the LM100 as a switching regulator. Feedback to the inverting input of the operational amplifier (Pin 6 of the LM100) is obtained through a resistive divider which can be used to set the output voltage anywhere in the  $2\text{-}30 \text{ V}$  range.  $R_3$  determines the base drive for the switch transistor,  $Q_1$ , providing enough drive to saturate it with maximum load current.  $R_4$  works into the  $1 \text{ k}\Omega$  impedance at the reference terminal, producing the positive feedback.  $C_2$  serves to minimize output ripple by causing the full ripple to appear on the feedback terminal. The remaining capacitor,  $C_3$ , removes the fast-risetime transients which would otherwise be coupled into Pin 5 through the shunt capacitance of  $R_4$ . It must be made small enough so that it does not seriously integrate the waveform at this point.

The circuit shown in Figure 5 is suitable for output currents as high as 500 mA. This limit is set by the output current available from the LM100 to saturate the switch transistor,  $Q_1$ . For lower currents, the value of  $R_3$  should be increased so that the base of  $Q_1$  is not driven unnecessarily hard.

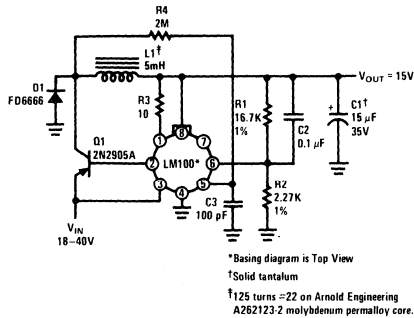

**FIGURE 5**  
Switching Regulator Using the LM100

The optimum switching frequency for these regulators has been determined to be between 20 kHz and 100 kHz. At lower frequencies, the core becomes unnecessarily large; and at higher frequencies, switching losses in  $Q_1$  and  $D_1$  become excessive. It is important, in this respect, that both  $Q_1$  and  $D_1$  be fast-switching devices to minimize switching losses.

The output ripple of the regulator at the switching frequency is mainly determined by  $R_4$ . It should be evident from the description of circuit operation that the peak-to-peak output ripple will be nearly equal to the peak-to-peak voltage fed back to Pin 5 of the LM100. Since the resistance looking into Pin 5 is approximately  $1000\Omega$ , this voltage will be

$$\Delta V_{\text{ref}} \approx \frac{1000 V_{\text{IN}}}{R_4} \quad (2)$$

In practice, the ripple will be somewhat larger than this. When the switch transistor shuts off, the current in the inductor will be greater than the load current so the output voltage will continue to rise above the value required to shut off the regulator. An important consideration in choosing the value of the inductor is that it be large enough so that the current through it does not change drastically during the switching cycle. If it does, the switch transistor and catch diode must be able to handle

peak currents which are significantly larger than the load current. The change in inductor current can be written as

$$\Delta I_L \approx \frac{V_{\text{OUT}} t_{\text{off}}}{L} \quad (3)$$

In order for the peak current to be about 1.2 times the maximum load current, it is necessary that

$$L_1 = \frac{2.5 V_{\text{OUT}} t_{\text{off}}}{I_{\text{OUT}} (\text{max})} \quad (4)$$

A value for  $t_{\text{off}}$  can be estimated from

$$t_{\text{off}} = \frac{1}{f} \left( 1 - \frac{V_{\text{OUT}}}{V_{\text{IN}}} \right) \quad (5)$$

where  $f$  is the desired switching frequency and  $V_{\text{IN}}$  is the nominal input voltage.

The size of the output capacitor can now be determined from

$$C_1 = \left( \frac{V_{\text{OUT}}}{2L_1 \Delta V_{\text{OUT}}} \right) \left( \frac{V_{\text{IN}} - V_{\text{OUT}}}{f V_{\text{IN}}} \right)^2 \quad (6)$$

where  $\Delta V_{\text{OUT}}$  is the peak-to-peak output ripple and  $V_{\text{IN}}$  is the nominal input voltage.

It now remains to determine if the component values obtained above give satisfactory load-transient response. The overshoot of the regulator can be determined from

$$\Delta V_{\text{OUT}} = \frac{L_1 (\Delta I_L)^2}{C_1 (V_{\text{IN}} - V_{\text{OUT}})} \quad (7)$$

for increasing loads, and

$$\Delta V_{\text{OUT}} = \frac{L_1 (\Delta I_L)^2}{C_1 V_{\text{OUT}}} \quad (8)$$

for decreasing loads, where  $\Delta I_L$  is the load-current transient. The recovery time is

$$t_r = \frac{2L_1 \Delta I_L}{V_{\text{IN}} - V_{\text{OUT}}} \quad (9)$$

and

$$t_r = \frac{2L_1 \Delta I_L}{V_{\text{OUT}}} \quad (10)$$

for increasing and decreasing loads respectively.

In order to improve the load transient response, it is necessary to allow larger peak to average current


ratios in the switch transistor and catch diode. Reducing the value of inductance given by Equation (4) by a factor of 2 will reduce the overshoot by 4 times and halve the response time. This, of course, assumes that the output capacitance is doubled to maintain a constant switching frequency.

The above equations outline a design procedure for determining the value for  $R_4$ ,  $L_1$ , and  $C_1$ , given the switching frequency and the output ripple. These equations are not exact, but they do provide a starting point for designing a regulator to fit a given application.

As an example, this design method will be applied to a regulator which must deliver 15V at a maximum current of 300 mA from a 28V supply. To start, a 40 kHz switching frequency will be selected along with an output ripple of 14 mV, peak-to-peak.

From (2),  $R_4$  is calculated to be  $2\text{ M}\Omega$ . In determining  $L_1$ ,  $t_{\text{off}}$  is found to be  $11.6\ \mu\text{s}$  from (5). Inserting this into (4) gives a value of 1.45 mH for  $L_1$ . The value of  $C_1$  obtained from (6) is then  $57.5\ \mu\text{F}$ .

In the actual circuit of Figure 5, a standard value of  $47\ \mu\text{F}$  is used for  $C_1$ ; and  $L_1$  is adjusted to 1.7 mH. The switching frequency obtained experimentally on this circuit is 60 kHz and the peak-to-peak output ripple is 20 mV. The fairly-large disagreement between the calculated and experimental values is not alarming since many simplifying assumptions were made in the derivation of the equations. They do, however, provide a convenient method of handling a large number of mutually-dependent variables to arrive at a working circuit.

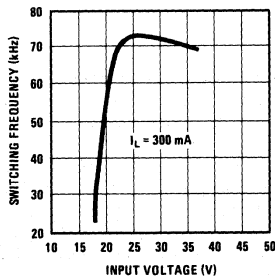


**FIGURE 6**  
Switching Frequency as a Function of Input Voltage


More exact expressions would involve a design procedure which is too cumbersome to be of practical value.

The variation of switching frequency with input voltage and load current is shown in Figures 6 and 7. The sharp rise in frequency at low output currents happens because the output transistor of the LM100 ( $Q_{12}$ ) begins to supply an appreciable portion of the load current directly.

The efficiency of the regulator over a wide range of input voltages and output currents is given in Figures 8 and 9.

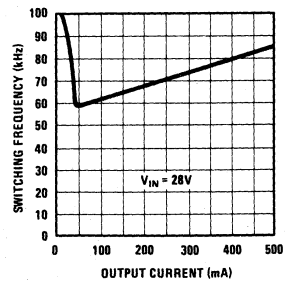

**FIGURE 7**  
Switching Frequency as a Function of Output Current

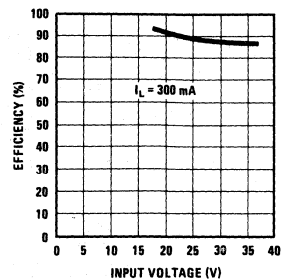

**FIGURE 8**  
Efficiency as a Function of Input Voltage


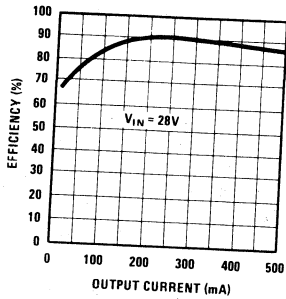


FIGURE 9  
Efficiency as a Function of Output Current
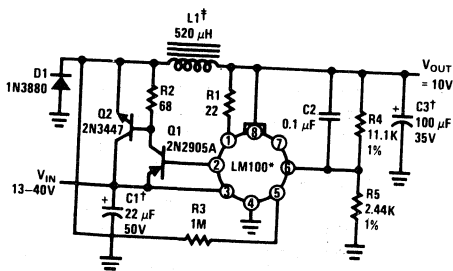
### HIGHER CURRENT REGULATORS

If output currents greater than about 500 mA are required, it is necessary to add another switch transistor to obtain more current gain. This is illustrated in Figure 10. With the exception of the added NPN power switch,  $Q_2$ , this circuit is the same as that described previously.

A photograph of a high-current regulator is shown in Figure 11. It is capable of delivering output currents of 3A continuously with only a small heat sink. Figure 12 shows that the efficiency is better than 80 percent at this level. Output currents to 5A can be obtained at reduced efficiency. However, the case temperature of the power switch and catch diode approach  $100^{\circ}\text{C}$  under this condition, so continuous operation is not recommended unless more heat sink is provided.



\*Basing diagram is Top View  
 †Solid tantalum  
 ‡60 turns = 20 on Arnold Engineering  
 A930157-2 molybdenum permalloy core

FIGURE 10  
Switching Regulator for Higher Output Currents

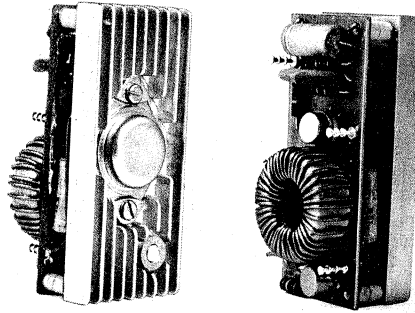


FIGURE 11  
High Current Switching Regulator



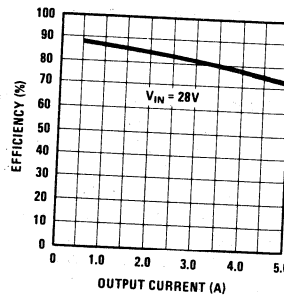


FIGURE 12  
Efficiency as a Function of Output Current


Figure 13 shows that the efficiency is not significantly affected by input voltage. In Figure 14 it can be seen that the switching frequency is fairly constant over a wide range of input voltages. Figure 15 shows that the switching frequency increases with increasing load current. The higher dc current through the inductor reduces the incremental inductance causing the frequency to go up. The last graph, Figure 16, illustrates the line regulation of the device. This can be improved by putting a small capacitor ( $0.01 \mu\text{F}$ ) in series with the positive feedback resistor,  $R_3$ , to isolate the reference terminal from the dc input voltage changes.

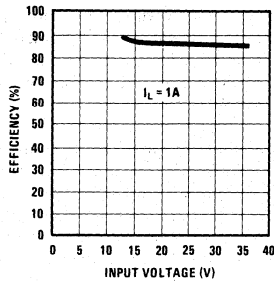


**FIGURE 13**  
Efficiency as a Function of Input Voltage

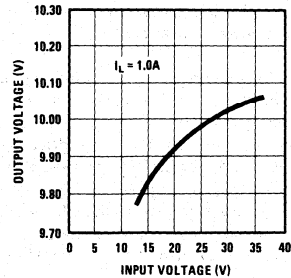

**FIGURE 16**  
Line Regulation

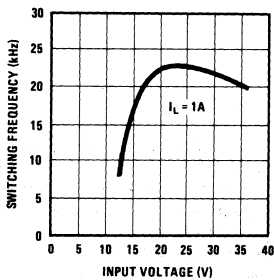

**FIGURE 14**  
Variation of Switching Frequency with Input Voltage

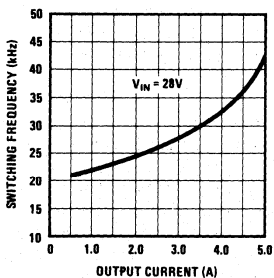

**FIGURE 15**  
Variation of Switching Frequency with Output Current

At low output currents the inductor current can drop to zero at some time after the switch transistor turns off. When this happens, ringing occurs on the switching waveform. This is perfectly normal and causes no ill effects.

The use of solid tantalum capacitors for  $C_1$  and  $C_3$  is recommended when the regulator is expected to perform over the full military temperature range. The reason for using 35V capacitors on the output, even though the output voltage is only 10V, is that the 40 mV peak-to-peak ripple on the output would, for example, exceed the ratings of a 100  $\mu$ F, 15V capacitor.

Aluminum electrolytic capacitors have been used successfully over a limited temperature range. And there is basically no reason why wet foil or wet slug tantalums could not be used as long as their equivalent series resistance is low enough so that they behave like capacitors with the high frequency switched-current waveform. It is also important that manufacturer's data be consulted to insure that they can withstand the high frequency ripple.


As was mentioned with the low current regulator, it is necessary to use fast-switching diodes and transistors in these circuits. Ordinary silicon rectifiers or low-frequency power transistors will operate at drastically-reduced efficiencies and will quickly overheat in these circuits.

#### DRIVEN SWITCHING REGULATOR

When a number of switching regulators are used together in a system it is sometimes desirable to synchronize their operation to more uniformly distribute the switched current waveforms on the input line. Synchronous operation is also wanted

when a switching regulator is operated in conjunction with a power converter.

A circuit for synchronizing the switching regulator with a square wave drive signal is shown in Figure 17. In this circuit, positive feedback is not used. Instead, the square wave drive signal is integrated; and the resulting triangular wave (about 40 mV peak-to-peak) is applied to the reference bypass terminal of the LM100. This triangular wave will cause the regulator to switch since its gain is so high that the waveform overdrives it. The duty cycle of the switched waveform is controlled by the voltage on the feedback terminal, Pin 6. If this voltage goes up, the duty cycle will decrease since it is picking off a smaller portion of the triangular wave on Pin 5. By the same token, the duty cycle will decrease if the voltage on Pin 6 drops.

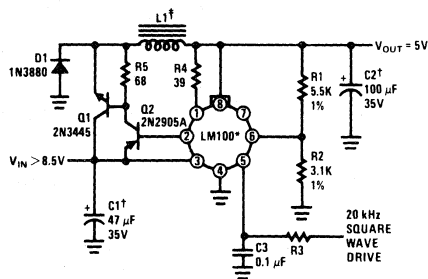

\*Basing diagram is Top View  
 †Solid tantalum  
 ‡100 turns #22 on Arnold Engineering  
 A930157-2 molybdenum permalloy core

**FIGURE 17**  
**Driven Switching Regulator**

This action produces the desired regulation: if the output voltage starts to go up, it will raise the voltage on Pin 6 such that a smaller portion of the triangular wave is picked off. This reduces the duty cycle, counteracting the output voltage increase.

In order for this circuit to work properly, the ripple voltage on Pin 6 should be less than a quarter of the peak-to-peak amplitude of the triangular wave. If this condition is not satisfied, the regulator will try to oscillate at its own frequency. Further, since the resistance looking into Pin 5 is

about 1 k $\Omega$ , the integrating capacitor, C<sub>3</sub>, should have a capacitive reactance of less than 100 $\Omega$  at the drive frequency. The value of R<sub>3</sub> is determined so that the amplitude of the triangular wave on Pin 5 is about 40 mV.

Driven regulators also have other advantages. For one, it is possible to design the LC filter independent of switching frequency considerations. Hence, lower output ripple and better transient response can be realized. A second advantage is the frequency stability. In a self-oscillating regulator, the switching frequency is controlled by a relatively large number of factors. As a result, it is not well determined when normal tolerances are taken into account. With low and medium power regulators, this is not usually a problem since the efficiency does not vary greatly with frequency. However, high power regulators tend to be more frequency sensitive and it is desirable to operate them at constant frequency.


## CURRENT LIMITING

In the circuits described previously, the regulator is not protected from overloads or short-circuited output. Providing short-circuit protection is no simple problem, since it is necessary to keep the regulator switching when the output is shorted. Otherwise, the dissipation will become excessive even though the current is limited.

A circuit that does this is shown in Figure 18. The peak current through the switch transistor is sensed by R<sub>6</sub>. When the voltage drop across this resistor becomes large enough to turn on Q<sub>3</sub>, the output voltage begins to fall since current is being supplied to the feedback terminal of the regulator from the collector of Q<sub>3</sub> so less has to be supplied from the output through R<sub>1</sub>. Furthermore, the circuit will continue to oscillate, even with a shorted output, because of positive feedback through R<sub>6</sub> and the relatively-long discharge time constant of C<sub>2</sub>.

It is necessary to put a resistor, R<sub>7</sub>, in series with the base of Q<sub>3</sub> to insure that excessive current will not be driven into the base. In addition, a capacitor, C<sub>4</sub>, must be added across the input of Q<sub>3</sub> so that it does not turn on prematurely on the large current spike (about twice the load current) through the switch transistor caused by pulling the stored charge out of the catch diode. A zener diode bias supply must also be used on the output of the LM100 since the current limiting will not work if the voltage on this point drops below about 1V.



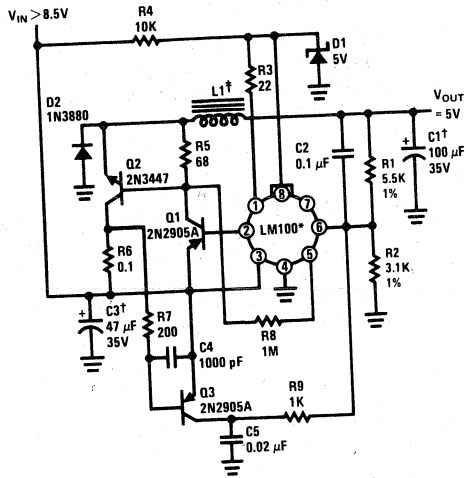

\*Basing diagram is Top View  
 †Solid tantalum  
 ‡70 turns #20 on Arnold Engineering  
 A930157-2 molybdenum permalloy core

FIGURE 18  
 Switching Regulator with Current Limiting

The current limiting characteristics of this circuit are shown in Figure 19. Figure 20 shows how the average input current actually drops off as the circuit goes into current limiting.

This current limiting scheme protects the switching transistors from overload or short-circuited output. However, the drop-out current and short-circuit current are not well controlled, so it is

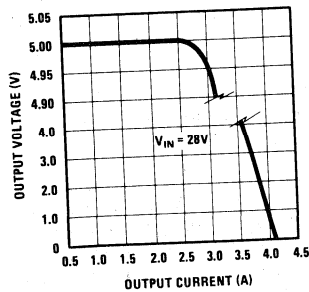


FIGURE 19  
 Current Limiting Characteristics


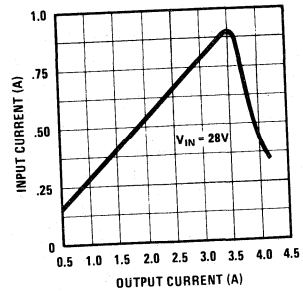


FIGURE 20  
 Illustrating Drop in Input Current as Regulator Goes Into Limiting


difficult to prove that the circuit will sustain a continuous short circuit under worst-case conditions. This is particularly true with high current regulators where the required amount of over-design can become quite expensive.

Figure 21 shows a circuit which is more easily designed for continuous short-circuit protection under worst-case conditions. In this circuit, the current-sensing resistor is located in series with the inductor. Therefore, the peak-limiting current can be more precisely determined since the current spike generated by pulling the stored charge out of the catch diode does not flow through the sense resistor.

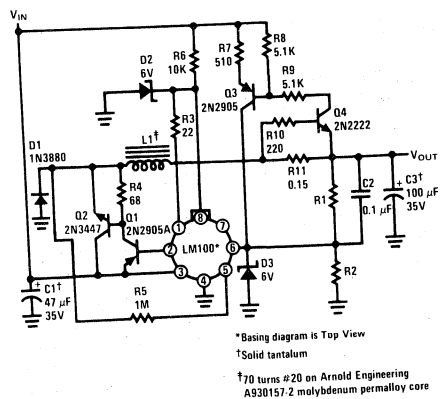


\*Basing diagram is Top View  
 †Solid tantalum  
 ‡70 turns #20 on Arnold Engineering  
 A930157-2 molybdenum permalloy core

FIGURE 21  
 Switching Regulator with Continuous Short-Circuit Protection

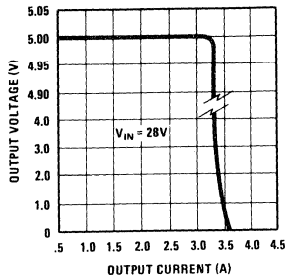

**FIGURE 22**  
Current Limiting Characteristics

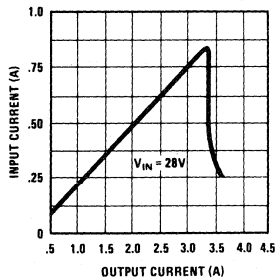

**FIGURE 23**  
Plot of Input Current as Regulator Goes Into Limiting


Operation of this circuit is essentially the same as the previous one in that an NPN transistor,  $Q_4$ , senses the overcurrent condition and turns on  $Q_3$  which supplies the current-limit signal to the feedback terminal. The zener diode,  $D_3$ , is required on the feedback terminal to guarantee that this terminal cannot go more than 0.5V higher than Pin 1. If this does happen, the circuit can latch up and burn out. The performance of this current-limiting scheme is illustrated in Figures 22 and 23.

With this circuit it is not only possible to more accurately determine the limiting current, but as can be seen from Figures 22 and 23, the limiting characteristic is considerably sharper. One disadvantage of this circuit is that the load current flows continuously through the current sense resistor, reducing efficiency. As an example, with a 5V regulated output the efficiency will be reduced by 10 percent at full load.

## NEGATIVE REGULATORS

All circuits discussed thus far are for regulators with positive outputs. Although negative regulators can be obtained by floating the unregulated supply and grounding the output, this is not always convenient.

Figure 24 shows a circuit for a negative switching regulator where the unregulated input and regulated output have a common ground. The only limitation of the circuit is that there must be a positive voltage greater than 3V available in order to properly bias the negative regulator.

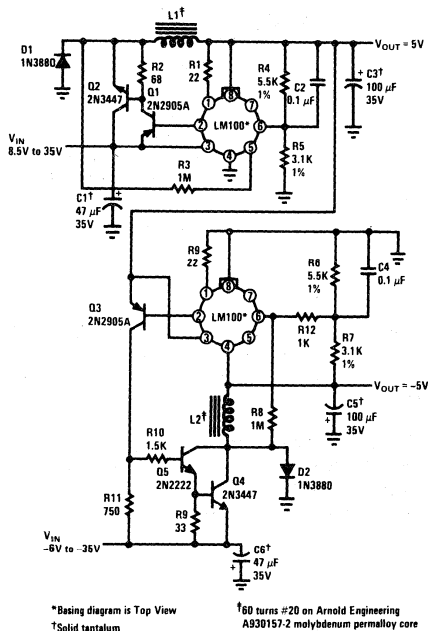

**FIGURE 24**  
Positive and Negative Switching Regulators


In this circuit, the normal output terminal of the LM100 (Pin 8) is grounded and the ground terminal (Pin 4) is connected to the regulated negative output. Hence, as before, it regulates the voltage between the output and ground terminals. The unregulated input terminal (Pin 3) is run from a positive voltage for proper biasing. A PNP booster

transistor,  $Q_3$ , is connected in the normal manner; and it drives a Darlington-connected NPN switch. Positive feedback is developed by the resistive divider,  $R_8$  and  $R_{12}$ .

It is necessary to use a Darlington switch even though the current gain is not needed. The power switch transistor,  $Q_4$ , cannot be operated with a fixed base drive: if the base drive is made large enough to insure saturation at maximum load current, it will overstore so badly at lower currents that the output ripple will increase radically. With the extra transistor, however, it is kept out of saturation at lower output currents, eliminating the problem.

### HIGH VOLTAGE REGULATORS

With switching regulators, an application can easily arise where the input voltage can be higher than the 40V maximum rating of the LM100, even though the output voltage is within the 30V maximum. As shown in Figure 25, it is possible to isolate the LM100 from the unregulated supply so that it can be used with input voltages limited only by the switch transistors and the catch diode.

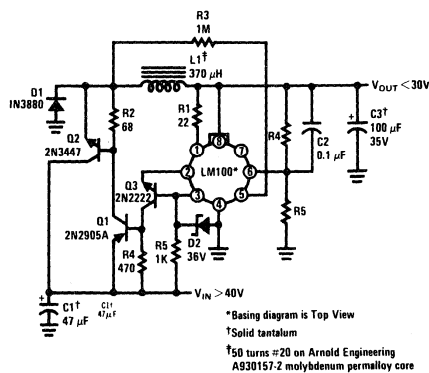


**FIGURE 25**  
Switching Regulator for High-voltage Inputs

In this circuit, the voltage seen by the LM100 is maintained at a fixed level within ratings by the zener diode,  $D_2$ . The zener voltage must be at least 3V greater than the output voltage. The output of the LM100 is level-shifted up to the input voltage by an additional NPN transistor,  $Q_3$ , which is operated common base. This drives the PNP switch driver in the normal manner.

### SWITCHING AND LINEAR REGULATOR COMBINATION

In certain applications, the output ripple and load transient response requirements rule out the use of a switching regulator, yet the input-output voltage differential is still high. In this case, a power converter might be used to reduce the input voltage and this reduced voltage would be regulated by a linear regulator. This arrangement, however, is not nearly as efficient as the switching and linear regulator combination shown in Figure 26. The switching regulator not only reduces the input voltage with high efficiency, but it also regulates it. Therefore, the linear regulator operates with a fixed input-output voltage differential which holds dissipation to a minimum.

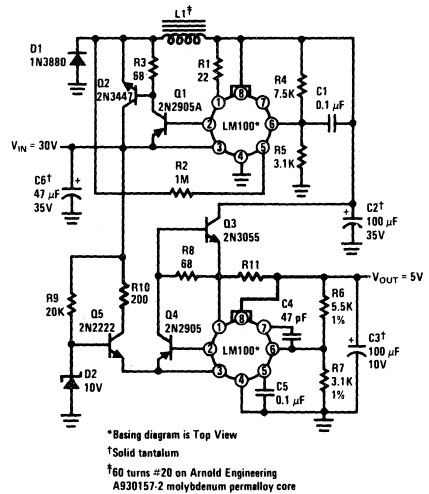

**FIGURE 26**  
Switching and Linear Regulator Combination for Obtaining Very Low Ripple and Fast Transient Response

In this circuit, the linear regulator is biased by a zener pre-regulator ( $R_9$ ,  $D_2$  and  $Q_5$ ) to isolate it from noise on the unregulated supply. This separate bias supply permits the linear pass transistor,  $Q_3$ , to operate right down into saturation. The collector of  $Q_3$  is supplied by the output of a switching regulator which is made enough higher than the linear regulator output to allow for the maximum overshoot of the switching regulator plus the saturation of  $Q_3$ .

## SUMMARY

A number of switching regulator circuits which use a readily-available monolithic voltage regulator as the voltage reference and control circuitry have been described. These regulators are useful over a 2V to 30V range for either positive or negative supplies. Although the discussion was limited to circuits providing maximum output currents from 100 mA to 5A, it is possible to obtain even higher output currents. The output current is, in fact, limited by the discrete components – not by the basic design or the integrated circuit.

The majority of the circuits shown were self-oscillating regulators; however, a method of

driving the regulator in synchronism with an external clock signal was given. In addition, circuits which provide overload protection, limiting both the output current as well as the power dissipation, were presented. The performance of the regulator circuits was described in detail, and a design procedure was outlined. Suggestions were also made on the selection of components for switching regulators.

The circuits which have been described here for the LM100 work equally well with the LM200 or the LM300. These devices are identical, except that the LM200 is specified over a  $-25^{\circ}\text{C}$  to  $85^{\circ}\text{C}$  temperature range and the LM300 is specified from  $0^{\circ}\text{C}$  to  $70^{\circ}\text{C}$  instead of the  $-55^{\circ}\text{C}$  to  $125^{\circ}\text{C}$  temperature range for the LM100.

# Drift Compensation Techniques for Integrated DC Amplifiers

National Semiconductor  
Application Note 3  
November 1967



## INTRODUCTION

With DC amplifiers, it is usually possible to substantially improve drift performance by using additional circuitry along with some form of adjustment. In fact, one of the reasons that discrete-component operational amplifiers have better input current specifications than monolithic amplifiers is that current compensation is used. Monolithic circuits cannot incorporate these techniques because it is not possible to select components or make adjustments. These adjustments can, however, be made external to the amplifier. This article will discuss a number of compensation methods which can substantially reduce the input currents of monolithic amplifiers, especially in limited-temperature-range applications.

Bias current compensation reduces offset and drift when the amplifier is operated from high source resistances. With low source resistances, such as a thermocouple, the drift contribution due to bias current can be made quite small. In this case, the offset voltage drift becomes important.

A technique is presented here by which offset voltage drifts better than  $0.5 \mu\text{V}/^\circ\text{C}$  can be realized. The compensation technique involves only a single room-temperature balance adjustment. Therefore, chopper-stabilized performance can be realized, with low source resistances, in a fairly-simple amplifier without tedious cut-and-try compensation methods.

## BIAS CURRENT COMPENSATION

The simplest and most effective way of compensating for bias currents is shown in Figure 1. Here,

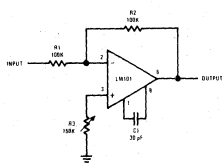


FIGURE 1. Summing Amplifier with Bias-Current Compensation for Fixed Source Resistances.

the offset produced by the bias current on the inverting input is cancelled by the offset voltage produced across the variable resistor,  $R_3$ . The main advantage of this scheme, besides its simplicity, is that the bias currents of the two input

transistors tend to track well over temperature so that low drift is also achieved. The disadvantage of the method is that a given compensation setting works only with fixed feedback resistors, and the compensation must be readjusted if the equivalent parallel resistance of  $R_1$  and  $R_2$  is changed.

Figure 2 shows a similar circuit for a non-inverting amplifier. The offset voltage produced across the DC resistance of the source due to the input

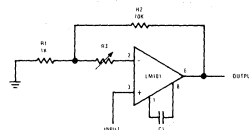


FIGURE 2. Non-Inverting Amplifier with Bias-Current Compensation for Fixed Source Resistances.

current is cancelled by the drop across  $R_3$ . For proper adjustment range,  $R_3$  should have a maximum value about three times the source resistance and the equivalent parallel resistance of  $R_1$  and  $R_2$  should be less than one-third the input source resistance.

This circuit has the same advantages as that in Figure 1, however, it can only be used when the input source has a fixed DC resistance. In many applications, such as long-interval integrators, sample-and-hold circuits, switched-gain amplifiers or voltage followers operating from unknown source, the source impedance is not defined. In these cases other compensation schemes must be used.

Figure 3 gives a compensation technique which does not depend upon having a fixed source resistance. A current is injected into the input terminal from the base of a PNP transistor. Since NPN input transistors are used on the integrated amplifier,\* the base current of the PNP balances out the base current of the NPN. Further, since a silicon-planar PNP transistor has approximately the same current-gain versus temperature characteristic as the integrated transistors, an improvement in temperature drift will also be realized.† However, perfect

\*This is true for all monolithic operational amplifiers presently available.

†If the operational amplifier uses a Darlington input stage, however, the drift compensation will not be nearly as good.

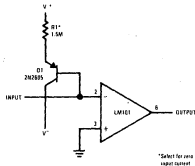


FIGURE 3. Summing Amplifier with Bias-Current Compensation.

compensation should not be expected because of unit-to-unit variations in the temperature characteristics of both the PNP transistor and the integrated circuit.

Although the circuit in Figure 3 works well for the summing amplifier connection, it does have limitations in other applications. It could, for example, be used for the voltage follower configuration by connecting the base of the PNP to the non-inverting input. However, this would reduce the input impedance (to about 150 M $\Omega$ ) because the current supplied by the PNP will vary with the input voltage level.

If this characteristic is objectionable, the more-complicated circuit shown in Figure 4 can be used.

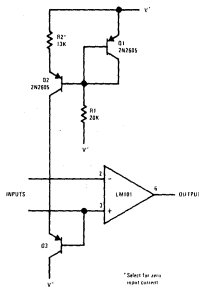


FIGURE 4. Bias-Current Compensation for Non-Inverting Amplifier Operated Over Large Common Mode Range.

The emitter of the PNP transistor is fed from a current source so that the compensating current does not vary with input-voltage level. The design of the current source is such as to give it about the same characteristics as those on the input stage of the better monolithic amplifiers<sup>‡</sup> to give closer compensation with changes in temperature and supply voltage. The circuit makes use of the emitter base voltage differential between two transistors operated at different collector currents.<sup>1,2</sup> Although it is recommended in the references that these transistors be well matched, it is not really necessary since the devices are operated at much different collector currents.

Figure 5 shows another compensation scheme for the voltage follower connection. This circuit is much simpler than that shown in Figure 4, but the temperature compensation is not quite as good. The compensating current is obtained through a resistor connected across a diode which is bootstrapped to the output. The diode acts as a regulator so that the

‡The 709 and the LM101.

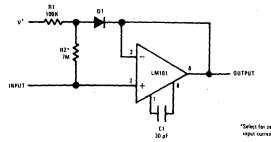


FIGURE 5. Voltage Follower with Bias-Current Compensation.

compensating current does not change appreciably with signal level, giving input impedances about 1000 M $\Omega$ . The negative temperature coefficient of the diode voltage also provides some temperature compensation.

All the circuits discussed thus far have been tailored for particular applications. Figure 6 shows a completely-general scheme wherein both inputs are

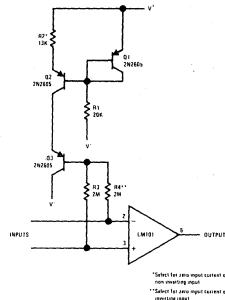


FIGURE 6. Bias-Current Compensation for Differential Inputs.

current compensated over the full common mode range as well as against power supply and temperature variations. This circuit is suitable for use either as a summing amplifier or as a non-inverting amplifier. It is not required that the DC impedance seen by both inputs be equal, although lower drift can be expected if they are.

As was mentioned earlier, all the bias compensation circuits require adjustment. With the circuits in Figures 1 and 2, this is merely a matter of adjusting the potentiometer for zero output with zero input. It is not so simple with the other circuits, however. For one, it is difficult to use potentiometers because a very wide range of resistance values are required to accommodate expected unit-to-unit variations. Resistor selection must therefore be used. Test circuits for selecting bias compensation resistors are given in Figure 7.

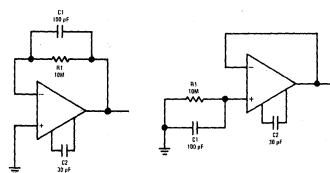


FIGURE 7. Test Circuits for Selecting Bias-Compensation Resistors.

## OFFSET VOLTAGE COMPENSATION

The highly predictable behavior of the emitter-base voltage of transistors has suggested a unique drift compensation method; it is shown in Reference 3 that the offset voltage drift of a differential transistor pair can be reduced by about an order of magnitude by unbalancing the collector currents such that the initial offset voltage is zero. The basis for this comes from the equation for the emitter-base voltage differential of two transistors operating at the same temperature:

$$\Delta V_{BE} = \frac{kT}{q} \log_e \frac{I_{S2}}{I_{S1}} - \frac{kT}{q} \log_e \frac{I_{C2}}{I_{C1}} \quad (1)$$

where  $k$  is Boltzmann's constant,  $T$  is the absolute temperature,  $q$  is the charge of an electron,  $I_S$  is a constant which depends only on how the transistor is made and  $I_C$  is the collector current. This equation is derived in Reference 2.

It is worthwhile noting here that these expressions make no assumptions about the current gain of the transistors. It is shown in Reference 5 and 6 that the emitter-base voltage is a function of collector current not emitter current. Therefore, the balance will not be upset by base current (except for interaction with the DC-source resistance).

The first term in Equation (1) is the offset voltage of the two transistors for equal collector currents. It can be seen that this offset voltage is directly proportional to the absolute temperature — a fact which is substantiated by experiment.<sup>4</sup> The second term is the change of offset voltage which arises from operating the transistors at unequal collector currents. For a fixed ratio of collector currents, this is also proportional to absolute temperature. Hence, if the collector currents are unbalanced in a fixed ratio to give a zero emitter-base voltage differential, the temperature drift will also be zero.

Experiment indicates that this is indeed true. Thermal drifts less than 100  $\mu\text{V}$  over the  $-55^\circ\text{C}$  to  $+125^\circ\text{C}$  temperature range have been realized consistently. In order to obtain these low drifts, however, it is almost necessary to use a monolithic transistor pair, since a  $0.05^\circ\text{C}$  temperature differential will give a 100  $\mu\text{V}$  drift. With a monolithic pair, the physical proximity of the devices as well as the high thermal conductivity of silicon holds this differential to an absolute minimum.

For low drift, the transistors must operate from a low enough source resistance that the voltage drop across the source due to base current (or base current differential if both bases see the same resistance) is insignificant. Furthermore, the transistors must be operated at a low enough collector current that the emitter-contact and base-spreading resistances are negligible, since Equation (1) assumes that they are zero.

A complete amplifier using this principle is shown in Figure 8. A monolithic transistor pair is used as a preamplifier for a conventional operational amplifier. A null potentiometer, which is set for zero

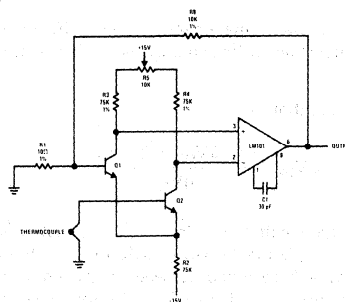


FIGURE 8. Example of a DC Amplifier Using the Drift-Compensation Technique.

output for zero input, unbalances the collector load resistors of the transistor pair such that the collector currents are unbalanced for zero offset. This gives minimum drift. An interesting feature of the circuit is that the performance is relatively unaffected by supply voltage variations: a 1V change in either supply causes an offset voltage change of about 10  $\mu\text{V}$ . This happens because neither term in Equation (1) is affected by the magnitude of the collector currents.

In order to get low drift, it is necessary that the gain of the preamplifier be high enough so that the drift of the operational amplifier does not degrade performance. The gain can be determined from the expression for the transconductance of the input transistors:

$$\frac{\partial I_C}{\partial V_{BE}} = \frac{qI_C}{kT} \quad (2)$$

The voltage gain is

$$A_V = \frac{\partial V_{OUT}}{\partial V_{IN}} \quad (3)$$

$$= \frac{\partial I_C}{\partial V_{BE}} R_L \quad (4)$$

where  $R_L$  is the average value of the two collector load resistors on the input stage and  $I_C$  is the average of the two collector currents.

Substituting Equation (2), this becomes

$$A_V = \frac{qI_C R_L}{kT} \quad (5)$$

$$= \frac{qV_{RL}}{kT} \quad (6)$$

The input referred drift is then

$$\Delta V_{IN} = \frac{\Delta V_{OS} + R_L \Delta I_{OS}}{A_V}$$

where  $\Delta V_{OS}$  is the offset voltage drift of the operational amplifier and  $\Delta I_{OS}$  is its offset current drift.

Using Equation (7),

$$\Delta V_{IN} = \frac{kT (\Delta V_{OS} + R_L \Delta I_{OS})}{qV_{RL}} \quad (8)$$

With the circuit shown in Figure 8, Equation (8) gives a 25  $\mu V$  input-referred drift for every 10 mV of offset voltage drift or for every 100 nA of offset current drift. It is obvious from this that the offset current drift is most important if an operational amplifier with bipolar input transistors is used.

Another important consideration is the matching of the collector load resistors on the preamplifier stage. A 0.1-percent imbalance in the load resistors due to thermal mismatches or any other cause will produce a 25  $\mu V$  shift in offset. This includes the balancing potentiometer which can introduce an error that will depend on how far it is set off midpoint if it has a different temperature coefficient than the resistors.

The most obvious use of this type of low drift amplifier is with thermocouples, magnetometers, current shunts, wire strain gauges or similar signal sources where very low drift is required and the source resistance is low enough that the bias currents do not cause a problem. The 0.5 to 1  $\mu V/^\circ C$  drift\* realized with this relatively simple amplifier over a  $-55^\circ C$  to  $+125^\circ C$  temperature range compares favorably with the drift figures achieved with chopper amplifiers: 0.4  $\mu V/^\circ C$  for mechanical choppers, 0.5  $\mu V/^\circ C$  with photoelectric choppers over a  $0^\circ C$  to  $55^\circ C$  temperature range and 2  $\mu V/^\circ C$  with field-effect-transistor choppers over a  $-55^\circ C$  to  $+125^\circ C$  temperature range. In order to give some appreciation of the level of performance, it is interesting to note that no substantial improvement in performance would be realized by operating the amplifier in a temperature-controlled oven. Any improvement would be masked by various thermoelectric effects not directly associated with the amplifier unless extreme care were taken in the choice of input lead material, the method of making connections and the balancing of thermal paths. These factors are, in fact, important when making oven tests to verify the drift of the amplifier since thermoelectric effects can easily produce drift voltages larger than those of the amplifier if they are not properly handled.

\*Drifts of 0.05  $\mu V/^\circ C$  over a  $0$ - $50^\circ C$  temperature range were reported in Reference 3 using matched discrete transistors in one can.

## SUMMARY

A number of compensation circuits designed to increase the DC resolution of monolithic operational amplifiers have been presented. Both current compensation techniques for high impedance levels as well as methods of achieving chopper-stabilized drift performance at low impedance levels have been covered.

Fairly-simple current compensation which requires that the impedance levels be fixed have been described along with compensation which is effective in cases where the source impedance is not well defined. This latter category includes long-interval integrators, sample-and-hold circuits, switched-gain amplifiers or voltage followers which operate from an unknown source. The application of these schemes is generally limited to integrated amplifiers since modular amplifiers almost always incorporate current compensation.

The drift-reduction techniques provide stabilities better than 0.5  $\mu V/^\circ C$  for low impedance sources, such as thermocouples, current shunts or strain gauges. With a properly designed circuit, compensation depends only on a single room temperature adjustment, so excellent performance can be obtained from a fairly-simple amplifier.

## REFERENCES

1. R. J. Widlar, "A Unique Circuit Design for a High Performance Operational Amplifier Especially Suited to Monolithic Construction," *Proc. of NEC*, Vol. XXI, pp. 85-89, October, 1965.
2. R. J. Widlar, "Some Circuit Design Techniques for Linear Integrated Circuits," *IEEE Trans. on Circuit Theory*, Vol. XII, pp. 586-590, December, 1965.
3. A. H. Hoffait and R. D. Thorton, "Limitations of Transistor DC Amplifiers," *IEEE Proc.*, Vol. 52, pp. 179-184, February, 1964.
4. A. Tuszynski, "Correlation Between the Base-Emitter Voltage and Its Temperature Coefficient," *Solid State Design*, pp. 32-35, July, 1962.
5. C. T. Sah, "Effect of Surface Recombination and Channel on P-N Junction and Transistor Characteristics," *IRE Trans. on Electron Devices*, Vol. ED-9, pp. 94-108, January, 1962.
6. J. E. Iwersen, A. R. Bray, and J. J. Kleimack, "Low-Current Alpha in Silicon Transistors," *IRE Trans. on Electron Devices*, Vol. ED-9, pp. 474-478, November, 1962.



# Monolithic Op Amp — The Universal Linear Component

National Semiconductor  
Application Note 4  
April 1968



## INTRODUCTION

Operational amplifiers are undoubtedly the easiest and best way of performing a wide range of linear functions from simple amplification to complex analog computation. The cost of monolithic amplifiers is now less than \$2.00, in large quantities, which makes it attractive to design them into circuits where they would not otherwise be considered. Yet low cost is not the only attraction of monolithic amplifiers. Since all components are simultaneously fabricated on one chip, much higher circuit complexities than can be used with discrete amplifiers are economical. This can be used to give improved performance. Further, there are no insurmountable technical difficulties to temperature stabilizing the amplifier chip, giving chopper-stabilized performance with little added cost.

Operational amplifiers are designed for high gain, low offset voltage and low input current. As a result, dc biasing is considerably simplified in most applications; and they can be used with fairly simple design rules because many potential error terms can be neglected. This article will give examples demonstrating the range of usefulness of operational amplifiers in linear circuit design. The examples are certainly not all-inclusive, and it is hoped that they will stimulate even more ideas from others. A few practical hints on preventing oscillations in operational amplifiers will also be given since this is probably the largest single problem that many engineers have with these devices.

Although the designs presented use the LM101 operational amplifier and the LM102 voltage follower produced by National Semiconductor, most are generally applicable to all monolithic devices if the manufacturer's recommended frequency compensation is used and differences in maximum ratings are taken into account. A complete description of the LM101 is given elsewhere;<sup>1</sup> but, briefly, it differs from most other monolithic amplifiers, such as the LM709,<sup>2</sup> in that it has a  $\pm 30V$  differential input voltage range, a  $+15V, -12V$  common mode range with  $\pm 15V$  supplies and it can be compensated with a single 30 pF capacitor. The LM102,<sup>3</sup> which is also used here, is designed specifically as a voltage follower and features a maximum input current of 10 nA and a  $10V/\mu s$  slew rate.

## OPERATIONAL-AMPLIFIER OSCILLATOR

The free-running multivibrator shown in Figure 1 is an excellent example of an application where one does not normally consider using an operational amplifier. However, this circuit operates at low frequencies with relatively small capacitors because it can use a longer portion of the capacitor time constant since the threshold point of the operational amplifier is well determined. In addition, it has a completely-symmetrical output waveform along with a buffered output, although the symmetry can be varied by returning R2 to some voltage other than ground.

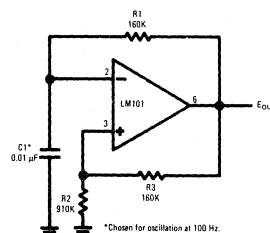


FIGURE 1. Free-Running Multivibrator

Another advantage of the circuit is that it will always self start and cannot hang up since there is more dc negative feedback than positive feedback. This can be a problem with many "textbook" multivibrators.

Since the operational amplifier is used open loop, the usual frequency compensation components are not required since they will only slow it down. But even without the 30 pF capacitor, the LM101 does have speed limitations which restrict the use of this circuit to frequencies below about 2 kHz.


The large input voltage range of the LM101 (both differential and single ended) permits large voltage swings on the input so that several time constants of the timing capacitor, C1, can be used. With most other amplifiers, R2 must be reduced to keep from exceeding these ratings, which requires that C1 be increased. Nonetheless, even when large values are needed for C1, smaller polarized capacitors may be used by returning them to the positive supply voltage instead of ground.

## LEVEL SHIFTING AMPLIFIER


Frequently, in the design of linear equipment, it is necessary to take a voltage which is referred to some dc level and produce an amplified output which is referred to ground. The most straightforward way of doing this is to use a differential amplifier similar to that shown in Figure 2a. This circuit, however, has the disadvantages that the signal source is loaded by current from the input divider, R3 and R4, and that the feedback resistors must be very well matched to prevent erroneous outputs from the common mode input signal.

A circuit which does not have these problems is shown in Figure 2b. Here, an FET transistor on the output of the operational amplifier produces a voltage drop across the feedback resistor, R1, which is equal to the input voltage. The voltage across R2 will then be equal to the input voltage multiplied by the ratio, R2/R1; and the common mode rejection will be as good as the basic rejection of the amplifier, independent of the resistor tolerances. This voltage is buffered by an LM102 voltage follower to give a low impedance output.

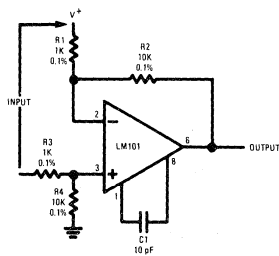An advantage of the LM101 in this circuit is that it will work with input voltages up to its positive supply voltages as long as the supplies are less than  $\pm 15V$ .



a. Standard Differential Amplifier

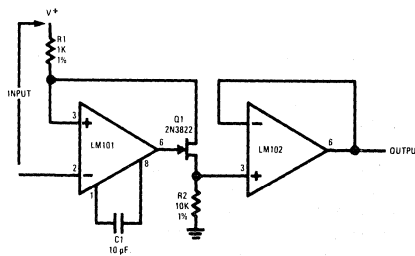


b. Level-Isolation Amplifier

FIGURE 2. Level-Shifting Amplifiers

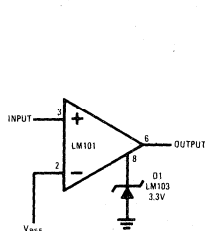
## VOLTAGE COMPARATORS

The LM101 is well suited to comparator applications for two reasons: first, it has a large differential input voltage range and, second, the output is easily clamped to make it compatible with various driver and logic circuits. It is true that it doesn't have the speed of the LM7104 ( $10 \mu s$  versus  $40 ns$ , under equivalent conditions); however, in many linear applications speed is not a problem and the lower input currents along with higher voltage capability of the LM101 is a tremendous benefit.

Two comparator circuits using the LM101 are shown in Figure 3. The one in Figure 3a shows a clamping scheme which makes the output signal directly compatible with DTL or TTL integrated circuits. An LM103 breakdown diode clamps the output at 0V or 4V in the low or high states, respectively. This particular diode was chosen because it has a sharp breakdown and low equivalent capacitance. When working as a comparator, the amplifier operates open loop so normally no frequency compensation is needed. Nonetheless, the stray capacitance between Pins 5 and 6 of the amplifier should be minimized to prevent low level oscillations when the comparator is in the active region. If this becomes a problem, a  $3 pF$  capacitor on the normal compensation terminals will eliminate it.



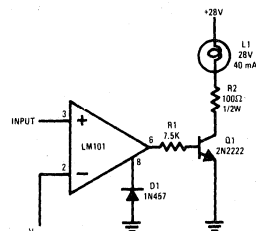a. Comparator for Driving DTL and TTL Integrated Circuits



b. Comparator and Lamp Driver

FIGURE 3. Voltage Comparator Circuits

Figure 3b shows the connection of the LM101 as a comparator and lamp driver. Q1 switches the lamp, with R2 limiting the current surge resulting from turning on a cold lamp. R1 determines the base drive to Q1 while D1 keeps the amplifier from putting excessive reverse bias on the emitter-base junction of Q1 when it turns off.

#### MORE OUTPUT CURRENT SWING

Because almost all monolithic amplifiers use class-B output stages, they have good loaded output voltage swings, delivering  $\pm 10V$  at 5 mA with  $\pm 15V$  supplies. Demanding much more current from the integrated circuit would require, for one, that the output transistors be made considerably larger. In addition, the increased dissipation could give rise to troublesome thermal gradients on the chip as well as excessive package heating in high-temperature applications. It is therefore advisable to use an external buffer when large output currents are needed.

A simple way of accomplishing this is shown in Figure 4. A pair of complementary transistors are used on the output of the LM101 to get the increased current swing. Although this circuit does have a dead zone, it can be neglected at frequencies below 100 Hz because of the high gain of the amplifier. R1 is included to eliminate parasitic oscillations from the output transistors. In addition, adequate bypassing should be used on the collectors of the output transistors to insure that the output signal is not coupled back into the amplifier. This circuit does not have current limiting, but it can be added by putting 50 $\Omega$  resistors in series with the collectors of Q1 and Q2.

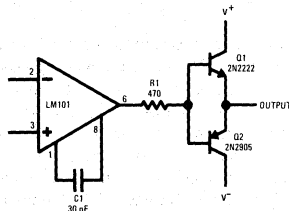


FIGURE 4. High Current Output Buffer

#### AN FET AMPLIFIER

For ambient temperatures less than about 70°C, junction field effect transistors can give exceptionally low input currents when they are used on the input stage of an operational amplifier. However, monolithic FET amplifiers are not now available since it is no simple matter to diffuse high quality FET's on the same chip as the amplifier. Nonetheless, it is possible to make a good FET amplifier using a discrete FET pair in conjunction with a monolithic circuit.

Such a circuit is illustrated in Figure 5. A matched FET pair, connected as source followers, is put in front of an integrated operational amplifier. The

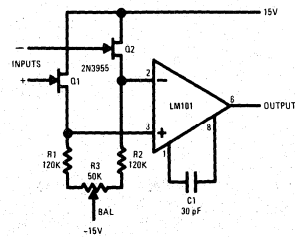


FIGURE 5. FET Operational Amplifier

composite circuit has roughly the same gain as the integrated circuit by itself and is compensated for unity gain with a 30 pF capacitor as shown. Although it works well as a summing amplifier, the circuit leaves something to be desired in applications requiring high common mode rejection. This happens both because resistors are used for current sources and because the FET's by themselves do not have good common mode rejection.

#### STORAGE CIRCUITS

A sample-and-hold circuit which combines the low input current of FET's with the low offset voltage of monolithic amplifiers is shown in Figure 6. The circuit is a unity gain amplifier employing an operational amplifier and an FET source follower. In operation, when the sample switch, Q2, is turned on, it closes the feedback loop to make the output equal to the input, differing only by the offset voltage of the LM101. When the switch is opened, the charge stored on C2 holds the output at a level equal to the last value of the input voltage.

Some care must be taken in the selection of the holding capacitor. Certain types, including paper and mylar, exhibit a polarization phenomenon which causes the sampled voltage to drop off by about 50 mV, and then stabilize, when the capacitor is exercised over a 5V range during the sample interval. This drop off has a time constant in the order of seconds. The effect, however, can be minimized by using capacitors with teflon, polyethylene, glass or polycarbonate dielectrics.

Although this circuit does not have a particularly low output resistance, fixed loads do not upset the accuracy since the loading is automatically compensated for during the sample interval. However, if the load is expected to change after sampling, a buffer such as the LM102 must be added between the FET and the output.

A second pole is introduced into the loop response of the amplifier by the switch resistance and the holding capacitor, C2. This can cause problems with overshoot or oscillation if it is not compensated for by adding a resistor, R1, in series with the LM101 compensation capacitor such that the breakpoint of the R1C1 combination is roughly equal to that of the switch and the holding capacitor.

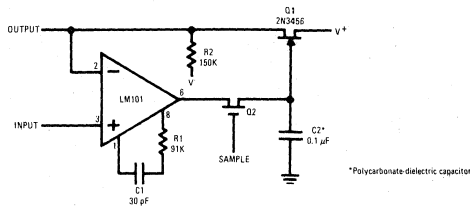


FIGURE 6. Low Drift Sample and Hold

It is possible to use an MOS transistor for Q1 without worrying about the threshold stability. The threshold voltage is balanced out during every sample interval so only the short-term threshold stability is important. When MOS transistors are used along with mechanical switches, drift rates less than 10 mV/min can be realized.

Additional features of the circuit are that the amplifier acts as a buffer so that the circuit does not load the input signal. Further, gain can also be provided by feeding back to the inverting input of the LM101 through a resistive divider instead of directly.

The peak detector in Figure 7 is similar in many respects to the sample-and-hold circuit. A diode is used in place of the sampling switch. Connected as shown, it will conduct whenever the input is greater than the output, so the output will be equal to the peak value of the input voltage. In this case, an LM102 is used as a buffer for the storage capacitor, giving low drift along with a low output resistance.

As with the sample and hold, the differential input voltage range of the LM101 permits differences between the input and output voltages when the circuit is holding.

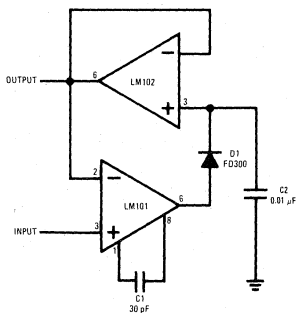


FIGURE 7. Positive Peak Detector with Buffered Output

## NON-LINEAR AMPLIFIERS

When a non-linear transfer function is needed from an operational amplifier, many methods of obtaining it present themselves. However, they usually require diodes and are therefore difficult to temperature compensate for accurate breakpoints. One way of getting around this is to make the output swing so large that the diode threshold is negligible by comparison, but this is not always practical.

A method of producing very sharp, temperature-stable breakpoints in the transfer function of an operational amplifier is shown in Figure 8. For small input signals, the gain is determined by R1 and R2. Both Q2 and Q3 are conducting to some degree, but they do not affect the gain because their current gain is high and they do not feed any appreciable current back into the summing mode. When the output voltage rises to 2V (determined by R3, R4 and V<sup>-</sup>), Q3 draws enough current to saturate, connecting R4 in parallel with R2. This cuts the gain in half. Similarly, when the output voltage rises to 4V, Q2 will saturate, again halving the gain.

Temperature compensation is achieved in this circuit by including Q1 and Q4. Q4 compensates the emitter-base voltage of Q2 and Q3 to keep the voltage across the feedback resistors, R4 and R6, very nearly equal to the output voltage while Q1 compensates for the emitter base voltage of these transistors as they go into saturation, making the voltage across R3 and R5 equal to the negative supply voltage. A detrimental effect of Q4 is that it causes the output resistance of the amplifier to increase at high output levels. It may therefore be necessary to use an output buffer if the circuit must drive an appreciable load.

## SERVO PREAMPLIFIER

In certain servo systems, it is desirable to get the rate signal required for loop stability from some sort of electrical, lead network. This can, for example, be accomplished with reactive elements in the feedback network of the servo preamplifier.

Many saturating servo amplifiers operate over an extremely wide dynamic range. For example, the maximum error signal could easily be 1000 times the signal required to saturate the system. Cases like this create problems with electrical rate networks because they cannot be placed in any part

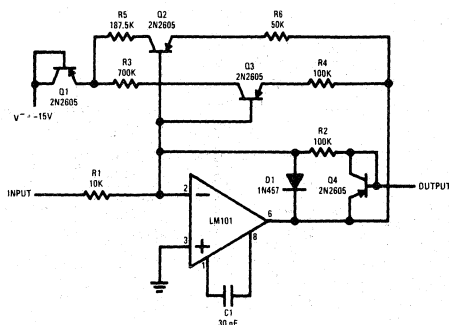


FIGURE 8. Nonlinear Operational Amplifier with Temperature-Compensated Breakpoints

of the system which saturates. If the signal into the rate network saturates, a rate signal will only be developed over a narrow range of system operation; and instability will result when the error becomes large. Attempts to place the rate networks in front of the error amplifier or make the error amplifier linear over the entire range of error signals frequently gives rise to excessive dc error from signal attenuation.

These problems can be largely overcome using the kind of circuit shown in Figure 9. This amplifier operates in the linear mode until the output voltage reaches approximately 3V with 30  $\mu$ A output current from the solar cell sensors. At this point the breakdown diodes in the feedback loop begin to conduct, drastically reducing the gain. However, a rate signal will still be developed because current is being fed back into the rate network (R1, R2 and C1) just as it would if the amplifier had remained in the linear operating region. In fact, the amplifier will not actually saturate until the error current reaches 6 mA, which would be the same as having a linear amplifier with a  $\pm$ 600V output swing.

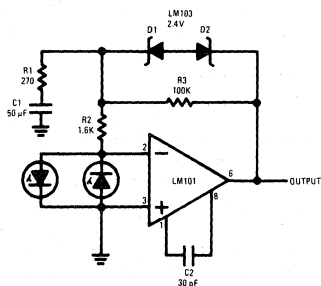


FIGURE 9. Saturating Servo Preamplifier with Rate Feedback

#### COMPUTING CIRCUITS

In analog computation it is a relatively simple matter to perform such operations as addition, subtraction, integration and differentiation by in-

corporating the proper resistors and capacitors in the feedback circuit of an amplifier. Many of these circuits are described in reference 5. Multiplication and division, however, are a bit more difficult. These operations are usually performed by taking the logarithms of the quantities, adding or subtracting as required and then taking the antilog.

At first glance, it might appear that obtaining the log of a voltage is difficult; but it has been shown<sup>6</sup> that the emitter-base voltage of a silicon transistor follows the log of its collector current over as many as nine decades. This means that common transistors can be used to perform the log and antilog operations.

A circuit which performs both multiplication and division in this fashion is shown in Figure 10. It gives an output which is proportional to the product of two inputs divided by a third, and it is about the same complexity as a divider alone.

The circuit consists of three log converters and an antilog generator. Log converters similar to these have been described elsewhere,<sup>7</sup> but a brief description follows. Taking amplifier A1, a logging transistor, Q1, is inserted in the feedback loop such that its collector current is equal to the input voltage divided by the input resistor, R1. Hence, the emitter-base voltage of Q1 will vary as the log of the input voltage, E1.

A2 is a similar amplifier operating with logging transistor, Q2. The emitter-base junctions of Q1 and Q2 are connected in series, adding the log voltages. The third log converter produces the log of E3. This is series-connected with the antilog transistor, Q4; and the combination is hooked in parallel with the output of the other two log converters. Therefore, the emitter-base of Q4 will see the log of E3 subtracted from the sum of the logs of E1 and E2. Since the collector current of a transistor varies as the exponent of the emitter-base voltage, the collector current of Q4 will be proportional to the product of E1 and E2 divided by E3. This current is fed to the summing amplifier, A4, giving the desired output.

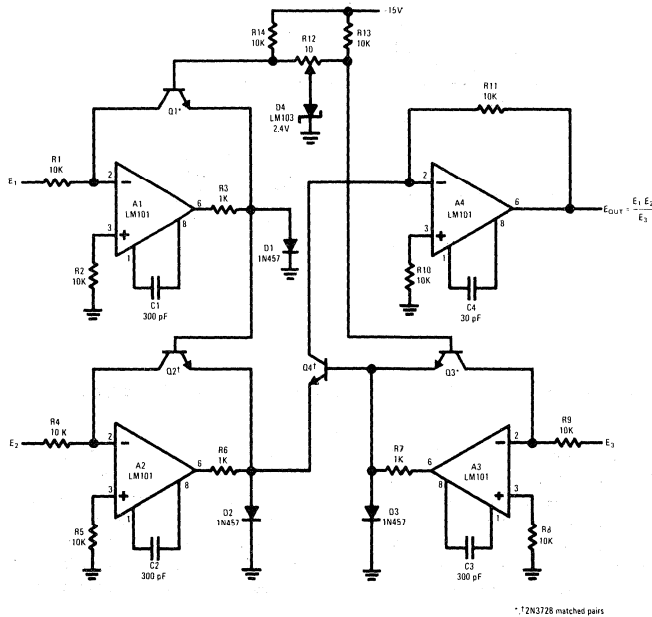


FIGURE 10. Analog Multiplier/Divider

This circuit can give 1-percent accuracy for input voltages from 500 mV to 50V. To get this precision at lower input voltages, the offset of the amplifiers handling them must be individually balanced out. The zener diode, D4, increases the collector-base voltage across the logging transistors to improve high current operation. It is not needed, and is in fact undesirable, when these transistors are running at currents less than 0.3 mA. At currents above 0.3 mA, the lead resistances of the transistors can become important ( $0.25\Omega$  is 1-percent at 1 mA) so the transistors should be installed with short leads and no sockets.

An important feature of this circuit is that its operation is independent of temperature because the scale factor change in the log converter with temperature is compensated by an equal change in the scale factor of the antilog generator. It is only required that Q1, Q2, Q3 and Q4 be at the same temperature. Dual transistors should be used and arranged as shown in the figure so that thermal mismatches between cans appear as inaccuracies in scale factor (0.3-percent/ $^{\circ}\text{C}$ ) rather than a balance error (8-percent/ $^{\circ}\text{C}$ ). R12 is a balance potentiometer which nulls out the offset voltages of all the logging transistors. It is adjusted by setting all input voltages equal to 2V and adjusting for a 2V output voltage.

The logging transistors provide a gain which is dependent on their operating level, which complicates frequency compensation. Resistors (R3, R6 and R7) are put in the amplifier output to limit the maximum loop gain, and the compensation capacitor is chosen to correspond with this gain. As a result, the amplifiers are not especially designed for speed, but techniques for optimizing this parameter are given in reference 6.

Finally, clamp diodes D1 through D3, prevent exceeding the maximum reverse emitter-base voltage of the logging transistors with negative inputs.

#### ROOT EXTRACTOR\*

Taking the root of a number using log converters is a fairly simple matter. All that is needed is to take the log of a voltage, divide it by, say 1/2 for the square root, and then take the antilog. A circuit which accomplishes this is shown in Figure 11. A1 and Q1 form the log converter for the input signal. This feeds Q2 which produces a level shift to give zero voltage into the R4, R5 divider for a 1V input. This divider reduces the log voltage by the ratio for the root desired and drives the buffer amplifier, A2. A2 has a second level shifting diode, Q3, its feedback network which gives the output voltage needed to get a 1V output from the antilog generator, consisting of A3 and Q4, with a unity

\*The "extraction" used here doubtless has origin in the dental operation most of us would fear less than having to find even a square root without tables or other aids.

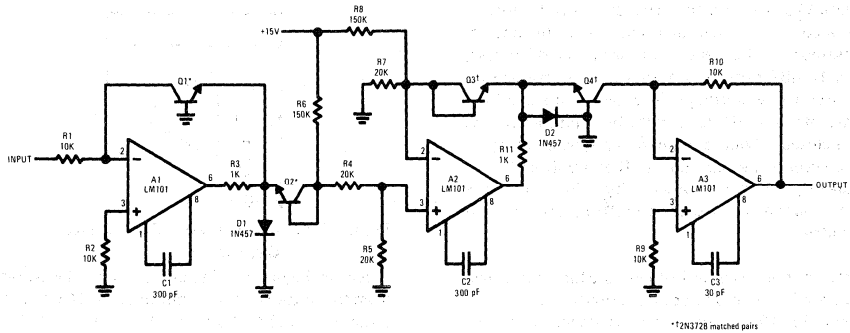


FIGURE 11. Root Extractor

input. The offset voltages of the transistors are nulled out by imbalancing R6 and R8 to give 1V output for 1V input, since any root of one is one.

Q2 and Q3 are connected as diodes in order to simplify the circuitry. This doesn't introduce problems because both operate over a very limited current range, and it is really only required that they match. R7 is a gain-compensating resistor which keeps the currents in Q2 and Q3 equal with changes in signal level.

As with the multiplier/divider, the circuit is insensitive to temperature as long as all the transistors are at the same temperature. Using transistor pairs and matching them as shown minimizes the effects of gradients.

The circuit has 1-percent accuracy for input voltages between 0.5 and 50V. For lower input voltages, A1 and A3 must have their offsets balanced out individually.


### FREQUENCY COMPENSATION HINTS

The ease of designing with operational amplifiers sometimes obscures some of the rules which must be followed with any feedback amplifier to keep it from oscillating. In general, these problems stem from stray capacitance, excessive capacitive load-


ing, inadequate supply bypassing or improper frequency compensation.

In frequency compensating an operational amplifier, it is best to follow the manufacturer's recommendations. However, if operating speed and frequency response is not a consideration, a greater stability margin can usually be obtained by increasing the size of the compensation capacitors. For example, replacing the 30 pF compensation capacitor on the LM101 with a 300 pF capacitor will make it ten times less susceptible to oscillation problems in the unity-gain connection. Similarly, on the LM709, using 0.05  $\mu$ F, 1.5 k $\Omega$ , 2000 pF and 51 $\Omega$  components instead of 5000 pF, 1.5 k $\Omega$ , 200 pF and 51 $\Omega$  will give 20 dB more stability margin. Capacitor values less than those specified by the manufacturer for a particular gain connection should not be used since they will make the amplifier more sensitive to strays and capacitive loading, or the circuit can even oscillate with worst-case units.

The basic requirement for frequency compensating a feedback amplifier is to keep the frequency roll-off of the loop gain from exceeding 12 dB/octave when it goes through unity gain. Figure 12a shows what is meant by loop gain. The feedback loop is broken at the output, and the input sources are replaced by their equivalent impedance. Then the response is measured such that the feedback network is included.

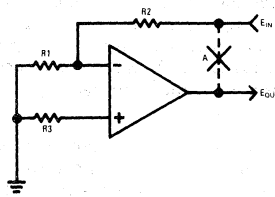

a. Measuring Loop Gain

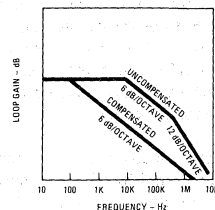


b. Typical Response

FIGURE 12. Illustrating Loop Gain

Figure 12b gives typical responses for both uncompensated and compensated amplifiers. An uncompensated amplifier generally rolls off at 6 dB/octave, then 12 dB/octave and even 18 dB/octave as various frequency-limiting effects within the amplifier come into play. If a loop with this kind of response were closed, it would oscillate. Frequency compensation causes the gain to roll off at a uniform 6 dB/octave right down through unity gain. This allows some margin for excess rolloff in the external circuitry.


Some of the external influences which can affect the stability of an operational amplifier is shown in Figure 13. One is the load capacitance which can come from wiring, cables or an actual capacitor on the output. This capacitance works against the output impedance of the amplifier to attenuate high frequencies. If this added rolloff occurs before the loop gain goes through zero, it can cause instability. It should be remembered that this single rolloff point can give more than 6 dB/octave rolloff since the output impedance of the amplifier can be increasing with frequency.

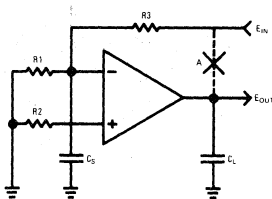

**FIGURE 13. External Capacitances That Affect Stability**


A second source of excess rolloff is stray capacitance on the inverting input. This becomes extremely important with large feedback resistors as might be used with an FET-input amplifier. A relatively simple method of compensating for this stray capacitance is shown in Figure 14: a lead capacitor, C1, put across the feedback resistor. Ideally, the ratio of the stray capacitance to the lead capacitor should be equal to the closed-loop gain of the amplifier. However, the lead capacitor can be made larger as long as the amplifier is compensated for unity gain. The only disadvantage of doing this is that it will reduce the bandwidth of the amplifier. Oscillations can also result if there is a large resistance on the non-inverting input of the amplifier. The differential input impedance of the amplifier falls off at high frequencies (especially with bipolar input transistors) so this resistor can produce troublesome rolloff if it is much greater than 10K, with most amplifiers. This is easily corrected by bypassing the resistor to ground.

When the capacitive load on an integrated amplifier is much greater than 100 pF, some consideration must be given to its effect on stability. Even though the amplifier does not oscillate readily, there may be a worst-case set of conditions under which it will. However, the amplifier can be stabilized for any value of capacitive loading using the circuit

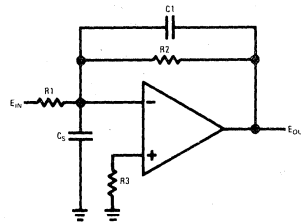

**FIGURE 14. Compensating Stray Input Capacitance**

shown in Figure 15. The capacitive load is isolated from the output of the amplifier with R4 which has a value of 50Ω to 100Ω for both the LM101 and the LM709. At high frequencies, the feedback path is through the lead capacitor, C1, so that the lag produced by the load capacitance does not cause instability. To use this circuit, the amplifier must be compensated for unity gain, regardless of the closed loop dc gain. The value of C1 is not too important, but at a minimum its capacitive reactance should be one-tenth the resistance of R2 at the unity-gain crossover frequency of the amplifier.

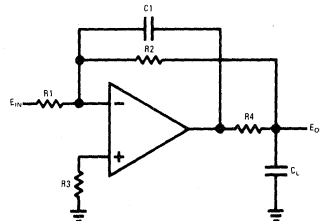

**FIGURE 15. Compensating for Very Large Capacitive Loads**

When an operational amplifier is operated open loop, it might appear at first glance that it needs no frequency compensation. However, this is not always the case because the external compensation is sometimes required to stabilize internal feedback loops.

The LM101 will not oscillate when operated open loop, although there may be problems if the capacitance between the balance terminal on pin 5 and the output is not held to an absolute minimum. Feedback between these two points is regenerative if it is not balanced out with a larger feedback capacitance across the compensation terminals. Usually a 3 pF compensation capacitor will completely eliminate the problem. The LM709 will oscillate when operated open loop unless a 10 pF capacitor is connected across the input compensation terminals and a 3 pF capacitor is connected on the output compensation terminals.

Problems encountered with supply bypassing are insidious in that they will hardly ever show up in a Nyquist plot. This problem has not really been thoroughly investigated, probably because one sure cure is known: bypass the positive and negative supply terminals of each amplifier to ground with at least a 0.01 μF capacitor.



For example, a LM101 can take over 1 mH inductance in either supply lead without oscillation. This should not suggest that they should be run without bypass capacitors. It has been established that 100 LM101's on a single printed circuit board with common supply busses will oscillate if the supplies are not bypassed about every fifth device. This happens even though the inputs and outputs are completely isolated.

The LM709, on the other hand, will oscillate under many load conditions with as little as 18 inches of wire between the negative supply lead and a bypass capacitor. Therefore, it is almost essential to have a set of bypass capacitors for every device.

Operational amplifiers are specified for power supply rejection at frequencies less than the first break frequency of the open loop gain. At higher frequencies, the rejection can be reduced depending on how the amplifier is frequency compensated. For both the LM101 and LM709, the rejection of high frequency signals on the positive supply is excellent. However, the situation is different for the negative supplies. These two amplifiers have compensation capacitors from the output down to a signal point which is referred to the negative supply, causing the high frequency rejection for the negative supply to be much reduced. It is therefore important to have sufficient bypassing on the negative supply to remove transients if they can cause trouble appearing on the output. One fairly large (22  $\mu$ F) tantalum capacitor on the negative power lead for each printed-circuit card is usually enough to solve potential problems.

When high-current buffers are used in conjunction with operational amplifiers, supply bypassing and decoupling are even more important since they can feed a considerable amount of signal back into the supply lines. For reference, bypass capacitors of at least 0.1  $\mu$ F are required for a 50 mA buffer.

When emitter followers are used to drive long cables, additional precautions are required. An emitter follower by itself — which is not contained in a feedback loop — will frequently oscillate when connected to a long length of cable. When an emitter follower is connected to the output of an operational amplifier, it can produce oscillations that will persist no matter how the loop gain is compensated. An analysis of why this happens is not very enlightening, so suffice it to say that these oscillations can usually be eliminated by putting a ferrite bead<sup>8</sup> between the emitter follower and the cable.

Considering the loop gain of an amplifier is a valuable tool in understanding the influence of various factors on the stability of feedback amplifiers. But

it is not too helpful in determining if the amplifier is indeed stable. The reason is that most problems in a well-designed system are caused by secondary effects — which occur only under certain conditions of output voltage, load current, capacitive loading, temperature, etc. Making frequency-phase plots under all these conditions would require unreasonable amounts of time, so it is invariably not done.

A better check on stability is the small-signal transient response. It can be shown mathematically that the transient response of a network has a one-for-one correspondence with the frequency domain response.<sup>†</sup> The advantage of transient response tests is that they are displayed instantaneously on an oscilloscope, so it is reasonable to test a circuit under a wide range of conditions.

Exact methods of analysis using transient response will not be presented here. This is not because these methods are difficult, although they are. Instead, it is because it is very easy to determine which conditions are unfavorable from the overshoot and ringing on the step response. The stability margin can be determined much more easily by how much greater the aggravating conditions can be made before the circuit oscillates than by analysis of the response under given conditions. A little practice with this technique can quickly yield much better results than classical methods even for the inexperienced engineer.

## SUMMARY

A number of circuits using operational amplifiers have been proposed to show their versatility in circuit design. These have ranged from low frequency oscillators through circuits for complex analog computation. Because of the low cost of monolithic amplifiers, it is almost foolish to design dc amplifiers without integrated circuits. Moreover, the price makes it practical to take advantage of operational-amplifier performance in a variety of circuits where they are not normally used.

Many of the potential oscillation problems that can be encountered in both discrete and integrated operational amplifiers were described, and some conservative solutions to these problems were presented. The areas discussed included stray capacitance, capacitive loading and supply bypassing. Finally, a simplified method of quickly testing the stability of amplifier circuits over a wide range of operating conditions was suggested.

---

<sup>†</sup>The frequency-domain characteristics can be determined from the impulse response of a network and this is directly relatable to the step response through the convolution integral.

## REFERENCES

1. R. J. Widlar, "Monolithic Op Amp with Simplified Frequency Compensation," *EEE*, Vol. 15, No. 7, pp. 58-63, July, 1967.
2. R. J. Widlar, "A Unique Circuit Design for a High Performance Operational Amplifier Especially Suited to Monolithic Construction," *Proc. of NEC*, Vol. XXI, pp. 85-89, October, 1965.
3. R. J. Widlar, "A Fast Integrated Voltage Follower with Low Input Current," *National Semiconductor AN-5*, March, 1968.
4. R. J. Widlar, "The Operation and Use of a Fast Integrated Circuit Comparator," *Fairchild Semiconductor APP-116*, February, 1966.
5. "Handbook of Operational Amplifier Applications," Burr-Brown Research Corporation, Tucson, Arizona.
6. J. F. Gibbons and H. S. Horn, "A Circuit with Logarithmic Transfer Response over Nine Decades," *IEEE Trans. on Circuit Theory*, Vol. CT-11, pp. 378-384, September, 1964.
7. R. J. Widlar and J. N. Giles, "Avoid Over-Integration," *Electronic Design*, Vol. 14, No. 3, pp. 56-62, Feb. 1, 1966.
8. Leslie Solomon, "Ferrite Beads," *Electronics World*, pp. 42-43, October, 1966.

# Application of the LH0002 Current Amplifier

National Semiconductor  
Application Note 13  
September 1968



## INTRODUCTION

The LH0002 Current Amplifier integrated building block provides a wide band unity gain amplifier capable of providing peak currents of up to  $\pm 200$  mA into a 50 ohm load.

The circuit uses thick film technology to integrate 2 NPN and 2 PNP complementary matched silicon transistors with 4 cermet resistors on a single alumina ceramic substrate. A circuit schematic is shown in Figure 1. The negative thermal feedback provided by the close proximity of the components on a single substrate eliminates any thermal runaway problem that could occur if this circuit were constructed using discrete components.

A typical circuit features a dynamic input impedance of 200 Kohms, an output impedance of 6 ohms, DC to 50 MHz bandwidth, and an output voltage swing that approaches supply voltage. A complete list of the guaranteed and typical values for the electrical characteristics under the stated conditions is given in Table 1. These features make the LH0002 ideal for integration with an operational amplifier inside a closed loop configuration

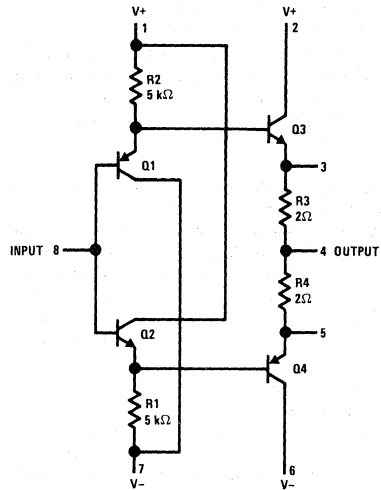


FIGURE 1. Circuit Schematic

TABLE 1. Electrical characteristics, specification applies for  $T_A = 25^\circ\text{C}$  with +12.0V on pins 1 and 2; -12.0V on pins 6 and 7.

PARAMETERS	CONDITIONS	MIN	TYP	MAX	UNITS
Voltage Gain	$R_S = 10 \text{ k}\Omega$ , $R_L = 1.0 \text{ k}\Omega$ $V_{IN} = 3.0 \text{ V}_{pp}$ , $f = 1.0 \text{ kHz}$ $T_A = -55^\circ\text{C}$ to $125^\circ\text{C}$	.95	.97		
Input Impedance	$R_S = 200 \text{ k}\Omega$ , $V_{IN} = 1.0 \text{ V}_{rms}$ , $f = 1.0 \text{ kHz}$ , $R_L = 1.0 \text{ k}\Omega$	180	200	—	$\text{k}\Omega$
Output Impedance	$V_{IN} = 1.0 \text{ V}_{rms}$ , $f = 1.0 \text{ kHz}$ $R_L = 50\Omega$ , $R_S = 10 \text{ k}\Omega$	—	6	10	$\Omega$
Output Voltage Swing	$R_L = 1.0 \text{ k}\Omega$ , $f = 1.0 \text{ kHz}$	$\pm 10$	$\pm 11$	—	V
DC Input Offset Voltage	$R_S = 10 \text{ k}\Omega$ , $R_L = 1.0 \text{ k}\Omega$ $T_A = -55^\circ\text{C}$ to $125^\circ\text{C}$	—	$\pm 40$	$\pm 100$	mV
DC Input Offset Current	$R_S = 10 \text{ k}\Omega$ , $R_L = 1.0 \text{ k}\Omega$ $T_A = -55^\circ\text{C}$ to $125^\circ\text{C}$	—	$\pm 6.0$	$\pm 10$	$\mu\text{A}$
Harmonic Distortion	$V_{IN} = 5.0 \text{ V}_{rms}$ , $f = 1.0 \text{ kHz}$	—	0.1	—	%
Bandwidth	$V_{IN} = 1.0 \text{ V}_{rms}$ , $R_L = 50\Omega$ , $f = 1 \text{ MHz}$	30	50	—	MHz
Positive Supply Current	$R_S = 10 \text{ k}\Omega$ , $R_L = 1 \text{ k}\Omega$	—	+6.0	+10.0	mA
Negative Supply Current	$R_S = 10 \text{ k}\Omega$ , $R_L = 1 \text{ k}\Omega$	—	-6.0	-10.0	mA

to increase its current output. The symmetrical class B output portion of the circuit also provides a constant low output impedance for both the positive and negative slopes of output pulses.

### CIRCUIT OPERATION

The majority of circuit applications will use symmetrical power supplies, with equal positive voltage being applied to pins 1 and 2, and equal negative voltage applied to pins 6 and 7. The reason that pin 2 and pin 6 are not connected internally to pin 1 and pin 7, respectively, is to increase the versatility of circuit operation by allowing a decreased voltage to be applied to pins 2 and 6 to minimize the power dissipation in Q3 and Q4. The larger voltage applied to the input stage also provides increased current drive as required to the output stage.

The operation of the circuit can be understood by considering that the input pin 8 is at  $V_{IN}$ . The emitter of Q1 will be approximately 0.6 volt more positive than  $V_{IN}$  at 25°C, and the converse is true for Q2. This 0.6 volt will provide a forward bias on Q3 to cancel out the Q1 base to emitter drop which in turn would provide  $V_{IN}$  at the output if all junctions, resistors, power supplies, etc., were electrically identical. The greatest error is introduced because the forward drops in the base-emitter junctions for the NPN and PNP devices are slightly different. For example, the  $V_{BE}$  of the NPN will be typically 0.6V and the  $V_{BE}$  of the PNP will be typically 0.64V under the same conditions of  $I_C = 2.4$  mA at  $V_{CE} = 12.0$ V at 25°C. These are the approximate input stage circuit conditions for Q1 and Q2 for plus and minus 12V supplies. Fortunately, this error in both input and output offset voltage is almost always negligible when it is used inside the closed loop of a high gain operational amplifier.

A plot of input impedance vs frequency is shown in Figure 2. Inspection of this plot shows that the input impedance can be closely approximated to that of a simple first order linear network with a 45° phase lag at 0.6 MHz and a 90° phase lag at approximately one decade higher in frequency. This information is very useful for designers who have to integrate circuits which have large source

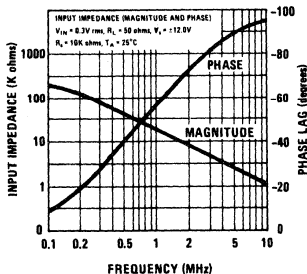


FIGURE 2. Input Impedance vs Frequency

impedances over a wide frequency range. The output impedance of the amplifier is very low, 6 ohms typically, and in conjunction with a voltage bandwidth of approximately 50 MHz can be considered to be insignificant for most applications for this type of device.

A plot of the voltage bandwidth is shown in Figure 3. Inspection of this plot shows that phase information as well as gain information was included to assist users of this device. For example, at 10 MHz, less than an 8° phase lag would be subtracted from the phase margin of an operational amplifier when it is integrated with this device. The open loop gain of the operational amplifier would be decreased by less than 10% at 10 MHz and therefore can be considered to be insignificant for most applications.

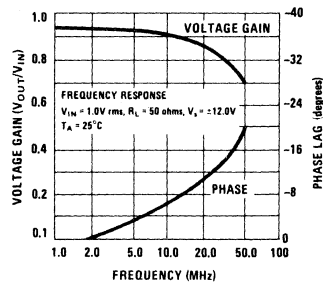


FIGURE 3. Frequency Response

### APPLICATIONS

Figure 4 shows the LH0002 integrated with the LH0005 to provide differential inputs and outputs. In order for this circuit to function properly, a load must be floated between the outputs of the two devices to provide a complete loop of feedback. A differential head on a scope across the load presents a true waveform of the actual signal being applied to it. If only one end of the load is displayed, it will appear distorted because this information is being fed back negatively to the input in order to cancel out the loop distortion of the overall amplifier. With the compensation shown, a 20V peak to peak signal can be applied to a 100 ohm load to 80 KHz. The overall circuit is approximately 33% efficient under these conditions. A derating factor and/or heat sink must be used at higher temperatures, as shown by the LH0002 and LH0005 data sheets.

Additional output power could also be obtained by connecting another LH0002 to pin 9 of the operational amplifier. The overall load distortion under high circuit voltage gain configurations would also be reduced using two LH0002's because the LH0002 is more linear than the simple output circuits of these particular operational amplifiers.

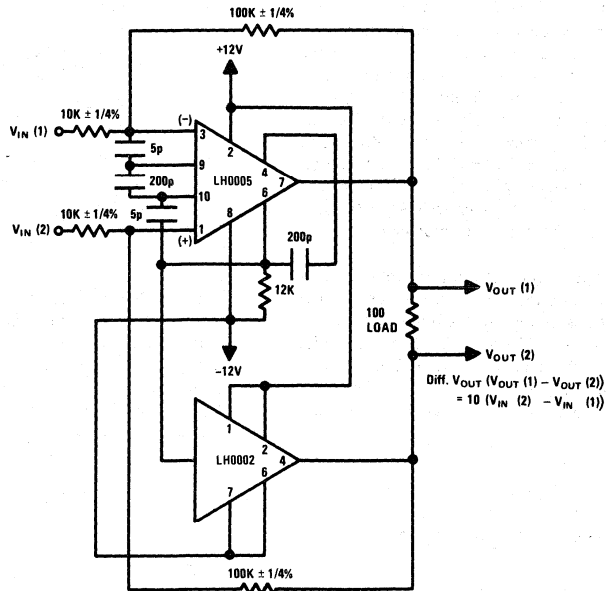


FIGURE 4. Differential Input-Output Operational Amplifier Integration

Figure 5 shows the LH0002 integrated with the LH101 in a booster follower configuration. The configuration is stable without the requirement for any external compensation; however, it would behoove the designer to be conservative and bypass both the negative and positive power supplies with at least a 0.01  $\mu$ f capacitor to cancel out any power supply lead inductance. A 100 ohm damping resistor, located right at the input of the LH0002, might also be required between the operational amplifier and the booster amplifier. The physical layout will determine the requirement for this type of oscillation suppression. Current limiting can be added by incorporating series resistors from pins 2 and 6 to their respective power supplies. The exact value would be a function of power supply voltage and required operating temperature.

A breadboard of this configuration was assembled to empirically check the increase in offset voltage due to the addition of the LH0002. The offset voltage was measured with and without an LH0002 inside the loop with a voltage gain of 100, at  $-55^{\circ}\text{C}$ ,  $25^{\circ}\text{C}$  and  $125^{\circ}\text{C}$ . The additional offset voltage was less than 0.3% for all three temperature conditions even though the offset voltage of the LH0002 is much higher than that of the LH101. The high open loop gain of the LH101 divides out this source of circuit error. The integration of this device also allows higher closed loop circuit gain without excessive cross-over distortion than would be obtainable with the simple booster amplifier shown in Figure 6.

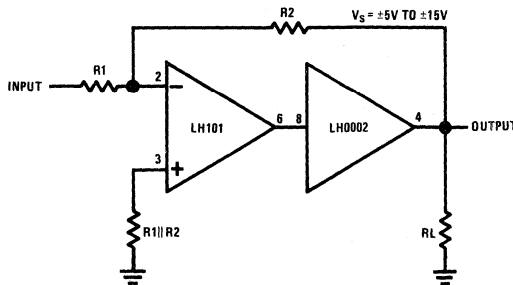


FIGURE 5. LH101-LH0002 Booster Amplifier Integration.

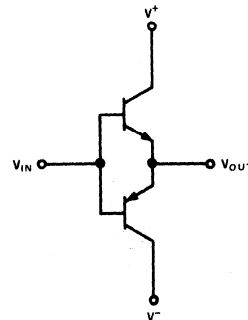


FIGURE 6. Simple Booster Amplifier

Figure 7 shows the LH0002 being used as a level shifter with a high pass filter on the input in order to reference the output to zero quiescent volts. The purpose of the 10 Kohm resistor is to provide current bias to the circuit's input transistors to reduce the output offset voltage. Figure 3, Input Impedance vs Frequency, provides a useful design aid in order to determine the value of the capacitor for the particular application. The 10 Kohm resistor, of course, has to be considered as being in parallel with the circuit's input impedance.

For a pulse input signal, the output impedance of the circuit remains low for both the positive and negative portions of the output pulse. This circuit provides both fast rise and fall times for pulse signals, even with capacitive loading. The LH0002 data sheet shows typical rise and fall times for both positive and negative pulses into a 50 ohm load.

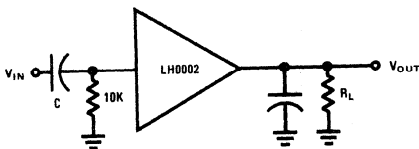


FIGURE 7. Level Shifter

Figure 8 shows the LH0002 being used to drive a pulse-transformer. The low output offset voltage allows the pulse transformer to be directly coupled to the amplifier without using a coupling capacitor to prevent saturation. The pulse transformer can be used to change the amplitude and impedance level of the pulse, the polarity of the pulses, or, with the aid of a center-tapped winding, positive and negative pulses simultaneously.

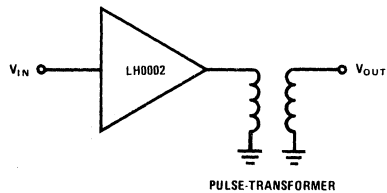


FIGURE 8. Driver for a Pulse-Transformer

The LH0002 can also be used to drive long transmission lines. Figure 9 shows a circuit configuration to match the output impedance of the amplifier to the load and coaxial cable for proper line termination to minimize reflections. A capacitor can be added to empirically adjust the time response of the waveform.

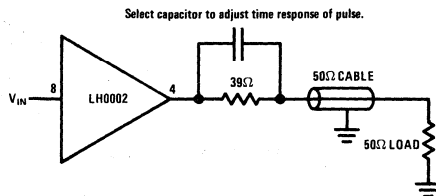


FIGURE 9. Transmission Line Driver

## SUMMARY

The multitude of different applications suggested in this article shows the versatility of the LH0002. The applications specially covered were for a differential input-output operational amplifier, booster amplifier, level shifter, driver for a pulse-transformer, and transmission line driver.

# An Applications Guide for Op Amps

National Semiconductor  
Application Note 20  
February 1969  
Revised August 1980



## INTRODUCTION

The general utility of the operational amplifier is derived from the fact that it is intended for use in a feedback loop whose feedback properties determine the feed-forward characteristics of the amplifier and loop combination. To suit it for this usage, the ideal operational amplifier would have infinite input impedance, zero output impedance, infinite gain and an open-loop 3 dB point at infinite frequency rolling off at 6 dB per octave. Unfortunately, the unit cost—in quantity—would also be infinite.

Intensive development of the operational amplifier, particularly in integrated form, has yielded circuits which are quite good engineering approximations of the ideal for finite cost. Quantity prices for the best contemporary integrated amplifiers are low compared with transistor prices of five years ago. The low cost and high quality of these amplifiers allows the implementation of equipment and systems functions impractical with discrete components. An example is the low frequency function generator which may use 15 to 20 operational amplifiers in generation, wave shaping, triggering and phase-locking.

The availability of the low-cost integrated amplifier makes it mandatory that systems and equipments engineers be familiar with operational amplifier applications. This paper will present amplifier usages ranging from the simple unity-gain buffer to relatively complex generator and wave-shaping circuits. The general theory of operational amplifiers is not within the scope of this paper and many excellent references are available in the literature.<sup>1,2,3,4</sup> The approach will be shaded toward the practical, amplifier parameters will be discussed as they affect circuit performance, and application restrictions will be outlined.

The applications discussed will be arranged in order of increasing complexity in five categories: simple amplifiers, operational circuits, transducer amplifiers, wave shapers and generators, and power supplies. The integrated amplifiers shown in the figures are for the most part internally compen-

sated so frequency stabilization components are not shown; however, other amplifiers may be used to achieve greater operating speed in many circuits as will be shown in the text. Amplifier parameter definitions are contained in Appendix I.

## THE INVERTING AMPLIFIER

The basic operational amplifier circuit is shown in Figure 1. This circuit gives closed-loop gain of  $R_2/R_1$  when this ratio is small compared with the amplifier open-loop gain and, as the name implies, is an inverting circuit. The input impedance is equal to  $R_1$ . The closed-loop bandwidth is equal to the unity-gain frequency divided by one plus the closed-loop gain.

The only cautions to be observed are that  $R_3$  should be chosen to be equal to the parallel combination of  $R_1$  and  $R_2$  to minimize the offset voltage error due to bias current and that there will be an offset voltage at the amplifier output equal to closed-loop gain times the offset voltage at the amplifier input.

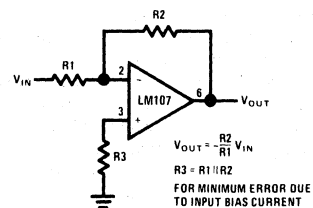


FIGURE 1. Inverting Amplifier

Offset voltage at the input of an operational amplifier is comprised of two components, these components are identified in specifying the amplifier as input offset voltage and input bias current. The input offset voltage is fixed for a particular amplifier, however the contribution due to input

bias current is dependent on the circuit configuration used. For minimum offset voltage at the amplifier input without circuit adjustment the source resistance for both inputs should be equal. In this case the maximum offset voltage would be the algebraic sum of amplifier offset voltage and the voltage drop across the source resistance due to offset current. Amplifier offset voltage is the predominant error term for low source resistances and offset current causes the main error for high source resistances.

In high source resistance applications, offset voltage at the amplifier output may be adjusted by adjusting the value of R3 and using the variation in voltage drop across it as an input offset voltage trim.

Offset voltage at the amplifier output is not as important in AC coupled applications. Here the only consideration is that any offset voltage at the output reduces the peak to peak linear output swing of the amplifier.

The gain-frequency characteristic of the amplifier and its feedback network must be such that oscillation does not occur. To meet this condition, the phase shift through amplifier and feedback network must never exceed  $180^\circ$  for any frequency where the gain of the amplifier and its feedback network is greater than unity. In practical applications, the phase shift should not approach  $180^\circ$  since this is the situation of conditional stability. Obviously the most critical case occurs when the attenuation of the feedback network is zero.

Amplifiers which are not internally compensated may be used to achieve increased performance in circuits where feedback network attenuation is high. As an example, the LM101 may be operated at unity gain in the inverting amplifier circuit with a 15 pF compensating capacitor, since the feedback network has an attenuation of 6 dB, while it requires 30 pF in the non-inverting unity gain connection where the feedback network has zero attenuation. Since amplifier slew rate is dependent on compensation, the LM101 slew rate in the inverting unity gain connection will be twice that for the non-inverting connection and the inverting gain of ten connection will yield eleven times the slew rate of the non-inverting unity gain connection. The compensation trade-off for a particular connection is stability versus bandwidth, larger values of compensation capacitor yield greater stability and lower bandwidth and vice versa.

The preceding discussion of offset voltage, bias current and stability is applicable to most amplifier applications and will be referenced in later sections. A more complete treatment is contained in Reference 4.

## THE NON-INVERTING AMPLIFIER

Figure 2 shows a high input impedance non-inverting circuit. This circuit gives a closed-loop gain equal to the ratio of the sum of R1 and R2 to R1 and a closed-loop 3 dB bandwidth equal to the amplifier unity-gain frequency divided by the closed-loop gain.

The primary differences between this connection and the inverting circuit are that the output is not inverted and that the input impedance is very high and is equal to the differential input impedance multiplied by loop gain. (Open loop gain/Closed loop gain.) In DC coupled applications, input impedance is not as important as input current and its voltage drop across the source resistance.

Applications cautions are the same for this amplifier as for the inverting amplifier with one exception. The amplifier output will go into saturation if the input is allowed to float. This may be important if the amplifier must be switched from source to source. The compensation trade off discussed for the inverting amplifier is also valid for this connection.

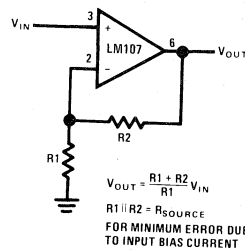


FIGURE 2. Non-Inverting Amplifier

## THE UNITY-GAIN BUFFER

The unity-gain buffer is shown in Figure 3. The circuit gives the highest input impedance of any operational amplifier circuit. Input impedance is equal to the differential input impedance multiplied by the open-loop gain, in parallel with common mode input impedance. The gain error of this circuit is equal to the reciprocal of the amplifier open-loop gain or to the common mode rejection, whichever is less.

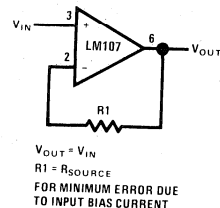


FIGURE 3. Unity Gain Buffer



Input impedance is a misleading concept in a DC coupled unity-gain buffer. Bias current for the amplifier will be supplied by the source resistance and will cause an error at the amplifier input due to its voltage drop across the source resistance. Since this is the case, a low bias current amplifier such as the LH1026 should be chosen as a unity-gain buffer when working from high source resistances. Bias current compensation techniques are discussed in Reference 5.

The cautions to be observed in applying this circuit are three: the amplifier must be compensated for unity gain operation, the output swing of the amplifier may be limited by the amplifier common mode range, and some amplifiers exhibit a latch-up mode when the amplifier common mode range is exceeded. The LM107 may be used in this circuit with none of these problems; or, for faster operation, the LM102 may be chosen.

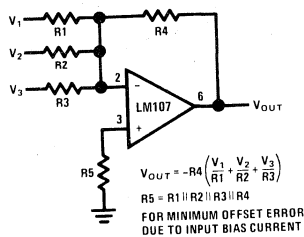


FIGURE 4. Summing Amplifier

### SUMMING AMPLIFIER

The summing amplifier, a special case of the inverting amplifier, is shown in Figure 4. The circuit gives an inverted output which is equal to the weighted algebraic sum of all three inputs. The gain of any input of this circuit is equal to the ratio of the appropriate input resistor to the feedback resistor, R4. Amplifier bandwidth may be calculated as in the inverting amplifier shown in Figure 1 by assuming the input resistor to be the parallel combination of R1, R2, and R3. Application cautions are the same as for the inverting amplifier. If an uncompensated amplifier is used, compensation is calculated on the basis of this bandwidth as is discussed in the section describing the simple inverting amplifier.

The advantage of this circuit is that there is no interaction between inputs and operations such as summing and weighted averaging are implemented very easily.

### THE DIFFERENCE AMPLIFIER

The difference amplifier is the complement of the summing amplifier and allows the subtraction of two voltages or, as a special case, the cancellation of a signal common to the two inputs. This circuit

is shown in Figure 5 and is useful as a computational amplifier, in making a differential to single-ended conversion or in rejecting a common mode signal.

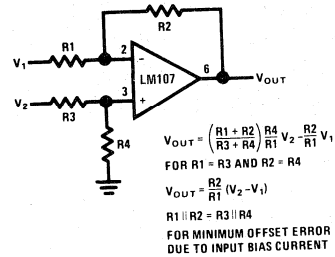


FIGURE 5. Difference Amplifier

Circuit bandwidth may be calculated in the same manner as for the inverting amplifier, but input impedance is somewhat more complicated. Input impedance for the two inputs is not necessarily equal; inverting input impedance is the same as for the inverting amplifier of Figure 1 and the non-inverting input impedance is the sum of R3 and R4. Gain for either input is the ratio of R1 to R2 for the special case of a differential input single-ended output where  $R_1 = R_3$  and  $R_2 = R_4$ . The general expression for gain is given in the figure. Compensation should be chosen on the basis of amplifier bandwidth.

Care must be exercised in applying this circuit since input impedances are not equal for minimum bias current error.

### DIFFERENTIATOR

The differentiator is shown in Figure 6 and, as the name implies, is used to perform the mathematical operation of differentiation. The form shown is not the practical form, it is a true differentiator and is extremely susceptible to high frequency noise since AC gain increases at the rate of 6 dB per octave. In addition, the feedback network of the differentiator,  $R_2C_1$ , is an RC low pass filter which contributes  $90^\circ$  phase shift to the loop and may cause stability problems even with an amplifier which is compensated for unity gain.

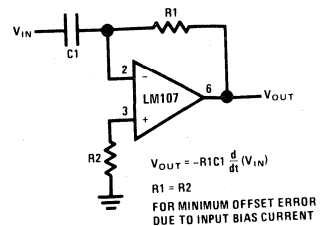


FIGURE 6. Differentiator

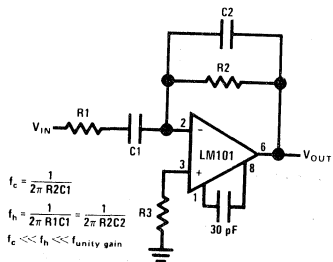


FIGURE 7. Practical Differentiator

A practical differentiator is shown in Figure 7. Here both the stability and noise problems are corrected by addition of two additional components, R1 and C2. R2 and C2 form a 6 dB per octave high frequency roll-off in the feedback network and R1C1 form a 6 dB per octave roll-off network in the input network for a total high frequency roll-off of 12 dB per octave to reduce the effect of high frequency input and amplifier noise. In addition R1C1 and R2C2 form lead networks in the feedback loop which, if placed below the amplifier unity gain frequency, provide 90° phase lead to compensate the 90° phase lag of R2C1 and prevent loop instability. A gain frequency plot is shown in Figure 8 for clarity.

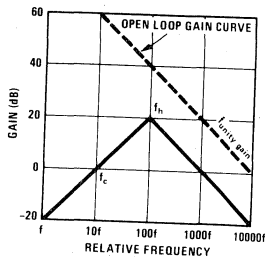


FIGURE 8. Differentiator Frequency Response

## INTEGRATOR

The integrator is shown in Figure 9 and performs the mathematical operation of integration. This

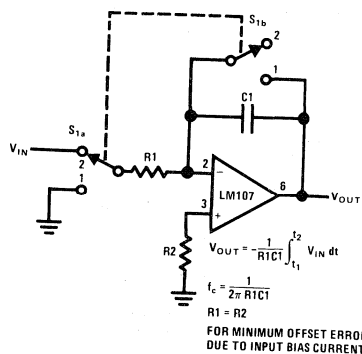


FIGURE 9. Integrator

circuit is essentially a low-pass filter with a frequency response decreasing at 6 dB per octave. An amplitude-frequency plot is shown in Figure 10.

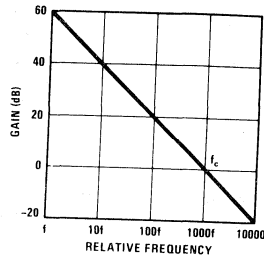


FIGURE 10. Integrator Frequency Response

The circuit must be provided with an external method of establishing initial conditions. This is shown in the figure as S<sub>1</sub>. When S<sub>1</sub> is in position 1, the amplifier is connected in unity-gain and capacitor C1 is discharged, setting an initial condition of zero volts. When S<sub>1</sub> is in position 2, the amplifier is connected as an integrator and its output will change in accordance with a constant times the time integral of the input voltage.

The cautions to be observed with this circuit are two: the amplifier used should generally be stabilized for unity-gain operation and R2 must equal R1 for minimum error due to bias current.

## SIMPLE LOW-PASS FILTER

The simple low-pass filter is shown in Figure 11. This circuit has a 6 dB per octave roll-off after a closed-loop 3 dB point defined by f<sub>c</sub>. Gain below this corner frequency is defined by the ratio of R3 to R1. The circuit may be considered as an AC integrator at frequencies well above f<sub>c</sub>; however, the time domain response is that of a single RC rather than an integral.

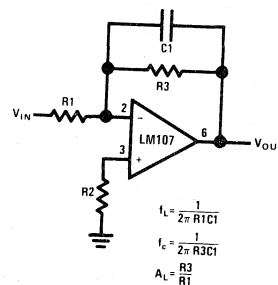


FIGURE 11. Simple Low Pass Filter

R2 should be chosen equal to the parallel combination of R1 and R3 to minimize errors due to bias current. The amplifier should be compensated for unity-gain or an internally compensated amplifier can be used.

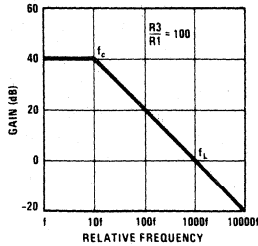


FIGURE 12. Low Pass Filter Response

A gain frequency plot of circuit response is shown in Figure 12 to illustrate the difference between this circuit and the true integrator.

### THE CURRENT-TO-VOLTAGE CONVERTER

Current may be measured in two ways with an operational amplifier. The current may be converted into a voltage with a resistor and then amplified or the current may be injected directly into a summing node. Converting into voltage is undesirable for two reasons: first, an impedance is inserted into the measuring line causing an error; second, amplifier offset voltage is also amplified with a subsequent loss of accuracy. The use of a current-to-voltage transducer avoids both of these problems.

The current-to-voltage transducer is shown in Figure 13. The input current is fed directly into the summing node and the amplifier output voltage changes to extract the same current from the summing node through  $R_1$ . The scale factor of this

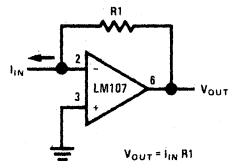


FIGURE 13. Current to Voltage Converter

circuit is  $R_1$  volts per amp. The only conversion error in this circuit is  $I_{bias}$  which is summed algebraically with  $I_{IN}$ .

This basic circuit is useful for many applications other than current measurement. It is shown as a photocell amplifier in the following section.

The only design constraints are that scale factors must be chosen to minimize errors due to bias current and since voltage gain and source impedance are often indeterminate (as with photocells) the amplifier must be compensated for unity-gain operation. Valuable techniques for bias current compensation are contained in Reference 5.

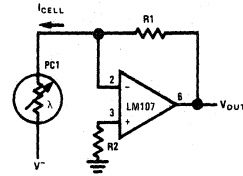


FIGURE 14. Amplifier for Photoconductive Cell

### PHOTOCELL AMPLIFIERS

Amplifiers for photoconductive, photodiode and photovoltaic cells are shown in Figures 14, 15, and 16 respectively.

All photogenerators display some voltage dependence of both speed and linearity. It is obvious that the current through a photoconductive cell will not display strict proportionality to incident light if the cell terminal voltage is allowed to vary with cell conductance. Somewhat less obvious is the fact that photodiode leakage and photovoltaic cell internal losses are also functions of terminal voltage. The current-to-voltage converter neatly sidesteps gross linearity problems by fixing a constant terminal voltage, zero in the case of photovoltaic cells and a fixed bias voltage in the case of photoconductors or photodiodes.

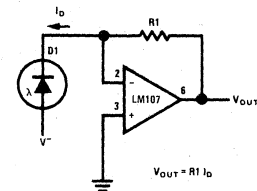


FIGURE 15. Photodiode Amplifier

Photodetector speed is optimized by operating into a fixed low load impedance. Currently available photovoltaic detectors show response times in the microsecond range at zero load impedance and photoconductors, even though slow, are materially faster at low load resistances.

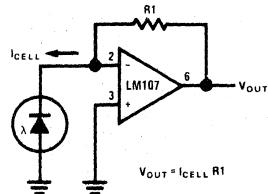


FIGURE 16. Photovoltaic Cell Amplifier

The feedback resistance, R1, is dependent on cell sensitivity and should be chosen for either maximum dynamic range or for a desired scale factor. R2 is elective: in the case of photovoltaic cells or of photodiodes, it is not required in the case of photoconductive cells, it should be chosen to minimize bias current error over the operating range.

### PRECISION CURRENT SOURCE

The precision current source is shown in Figures 17 and 18. The configurations shown will sink or source conventional current respectively.

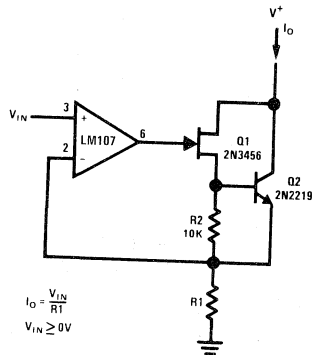


FIGURE 17. Precision Current Sink

Caution must be exercised in applying these circuits. The voltage compliance of the source extends from  $V_{CE}$  of the external transistor to approximately 1 volt more negative than  $V_{IN}$ . The compliance of the current sink is the same in the positive direction.

The impedance of these current generators is essentially infinite for small currents and they are accurate so long as  $V_{IN}$  is much greater than  $V_{OS}$  and  $I_O$  is much greater than  $I_{bias}$ .

The source and sink illustrated in Figures 17 and 18 use an FET to drive a bipolar output transistor. It is possible to use a Darlington connection in place of the FET-bipolar combination in cases

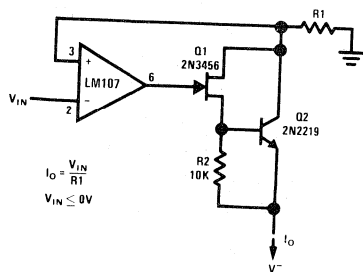


FIGURE 18. Precision Current Source

where the output current is high and the base current of the Darlington input would not cause a significant error.

The amplifiers used must be compensated for unity-gain and additional compensation may be required depending on load reactance and external transistor parameters.

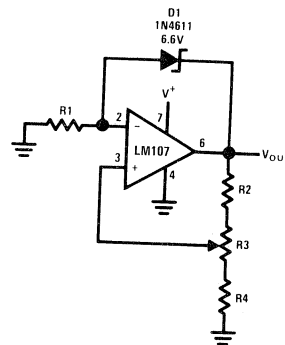


FIGURE 19a. Positive Voltage Reference

### ADJUSTABLE VOLTAGE REFERENCES

Adjustable voltage reference circuits are shown in Figures 19 and 20. The two circuits shown have different areas of applicability. The basic difference between the two is that Figure 19 illustrates a voltage source which provides a voltage greater than the reference diode while Figure 20 illustrates a voltage source which provides a voltage lower than the reference diode. The figures show both positive and negative voltage sources.

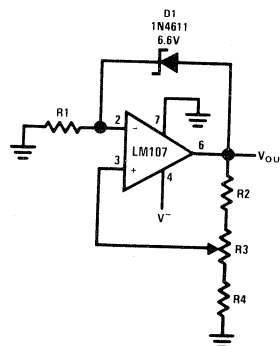


FIGURE 19b. Negative Voltage Reference

High precision extended temperature applications of the circuit of Figure 19 require that the range of adjustment of  $V_{OUT}$  be restricted. When this is done, R1 may be chosen to provide optimum zener current for minimum zener T.C. Since  $I_Z$  is not a function of  $V^+$ , reference T.C. will be independent of  $V^+$ .

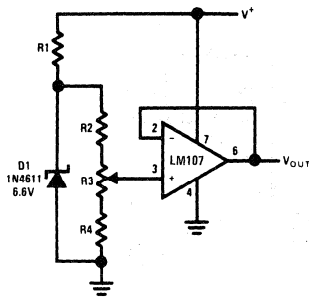


FIGURE 20a. Positive Voltage Reference

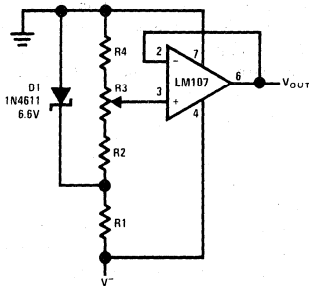


FIGURE 20b. Negative Voltage Reference

The circuit of Figure 20 is suited for high precision extended temperature service if  $V^+$  is reasonably constant since  $I_Z$  is dependent on  $V^+$ .  $R_1$ ,  $R_2$ ,  $R_3$ , and  $R_4$  are chosen to provide the proper  $I_Z$  for minimum T.C. and to minimize errors due to  $I_{bias}$ .

The circuits shown should both be compensated for unity-gain operation or, if large capacitive loads are expected, should be overcompensated. Output noise may be reduced in both circuits by bypassing the amplifier input.

The circuits shown employ a single power supply, this requires that common mode range be considered in choosing an amplifier for these applications. If the common mode range requirements are in excess of the capability of the amplifier, two power supplies may be used. The LH101 may be used with a single power supply since the common mode range is from  $V^+$  to within approximately 2 volts of  $V^-$ .

#### THE RESET STABILIZED AMPLIFIER

The reset stabilized amplifier is a form of chopper-stabilized amplifier and is shown in Figure 21. As shown, the amplifier is operated closed-loop with a gain of one.

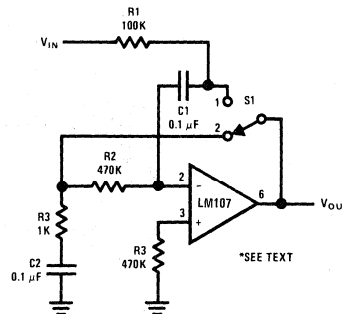


FIGURE 21. Reset Stabilized Amplifier

The connection is useful in eliminating errors due to offset voltage and bias current. The output of this circuit is a pulse whose amplitude is equal to  $V_{IN}$ . Operation may be understood by considering the two conditions corresponding to the position of  $S_1$ . When  $S_1$  is in position 2, the amplifier is connected in the unity gain connection and the voltage at the output will be equal to the sum of the input offset voltage and the drop across  $R_2$  due to input bias current. The voltage at the inverting input will be equal to input offset voltage. Capacitor  $C_1$  will charge to the sum of input offset voltage and  $V_{IN}$  through  $R_1$ . When  $C_1$  is charged, no current flows through the source resistance and  $R_1$  so there is no error due to input resistance.  $S_1$  is then changed to position 1. The voltage stored on  $C_1$  is inserted between the output and inverting input of the amplifier and the output of the amplifier changes by  $V_{IN}$  to maintain the amplifier input at the input offset voltage. The output then changes from  $(V_{OS} + I_{bias}R_2)$  to  $V_{IN} + I_{bias}R_2$  as  $S_1$  is changed from position 2 to position 1. Amplifier bias current is supplied through  $R_2$  from the output of the amplifier or from  $C_2$  when  $S_1$  is in position 2 and position 1 respectively.  $R_3$  serves to reduce the offset at the amplifier output if the amplifier must have maximum linear range or if it is desired to DC couple the amplifier.

An additional advantage of this connection is that input resistance approaches infinity as the capacitor  $C_1$  approaches full charge, eliminating errors due to loading of the source resistance. The time spent in position 2 should be long with respect to the changing time of  $C_1$  for maximum accuracy.

The amplifier used must be compensated for unity gain operation and it may be necessary to overcompensate because of the phase shift across  $R_2$  due to  $C_1$  and the amplifier input capacity. Since this connection is usually used at very low switching speeds, slew rate is not normally a practical consideration and overcompensation does not reduce accuracy.

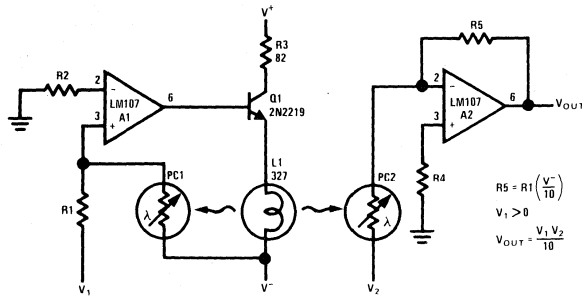


FIGURE 22. Analog Multiplier

### THE ANALOG MULTIPLIER

A simple embodiment of the analog multiplier is shown in Figure 22. This circuit circumvents many of the problems associated with the log-antilog circuit and provides three quadrant analog multiplication which is relatively temperature insensitive and which is not subject to the bias current errors which plague most multipliers.

Circuit operation may be understood by considering A2 as a controlled gain amplifier, amplifying  $V_2$ , whose gain is dependent on the ratio of the resistance of PC2 to R5 and by considering A1 as a control amplifier which establishes the resistance of PC2 as a function of  $V_1$ . In this way it is seen that  $V_{OUT}$  is a function of both  $V_1$  and  $V_2$ .

A1, the control amplifier, provides drive for the lamp, L1. When an input voltage,  $V_1$ , is present, L1 is driven by A1 until the current to the summing junction from the negative supply through PC1 is equal to the current to the summing junction from  $V_1$  through R1. Since the negative supply voltage is fixed, this forces the resistance of PC1 to a value proportional to R1 and to the ratio of  $V_1$  to  $V^-$ . L1 also illuminates PC2 and, if the photoconductors are matched, causes PC2 to have a resistance equal to PC1.

A2, the controlled gain amplifier, acts as an inverting amplifier whose gain is equal to the ratio of the resistance of PC2 to R5. If R5 is chosen equal to the product of R1 and  $V^-$ , then  $V_{OUT}$  becomes simply the product of  $V_1$  and  $V_2$ . R5 may be scaled in powers of ten to provide any required output scale factor.

PC1 and PC2 should be matched for best tracking over temperature since the T.C. of resistance is related to resistance match for cells of the same geometry. Small mismatches may be compensated by varying the value of R5 as a scale factor adjustment. The photoconductive cells should receive equal illumination from L1, a convenient method

is to mount the cells in holes in an aluminum block and to mount the lamp midway between them. This mounting method provides controlled spacing and also provides a thermal bridge between the two cells to reduce differences in cell temperature. This technique may be extended to the use of FET's or other devices to meet special resistance or environment requirements.

The circuit as shown gives an inverting output whose magnitude is equal to one-tenth the product of the two analog inputs. Input  $V_1$  is restricted to positive values, but  $V_2$  may assume both positive and negative values. This circuit is restricted to low frequency operation by the lamp time constant.

R2 and R4 are chosen to minimize errors due to input offset current as outlined in the section describing the photocell amplifier. R3 is included to reduce in-rush current when first turning on the lamp, L1.

### THE FULL-WAVE RECTIFIER AND AVERAGING FILTER

The circuit shown in Figure 23 is the heart of an average reading, rms calibrated AC voltmeter. As shown, it is a rectifier and averaging filter. Deletion of C2 removes the averaging function and provides a precision full-wave rectifier, and deletion of C1 provides an absolute value generator.

Circuit operation may be understood by following the signal path for negative and then for positive inputs. For negative signals, the output of amplifier A1 is clamped to +0.7V by D1 and disconnected from the summing point of A2 by D2. A2 then functions as a simple unity-gain inverter with input resistor, R1, and feedback resistor, R2, giving a positive going output.

For positive inputs, A1 operates as a normal amplifier connected to the A2 summing point through resistor, R5. Amplifier A1 then acts as a simple unity-gain inverter with input resistor, R3, and

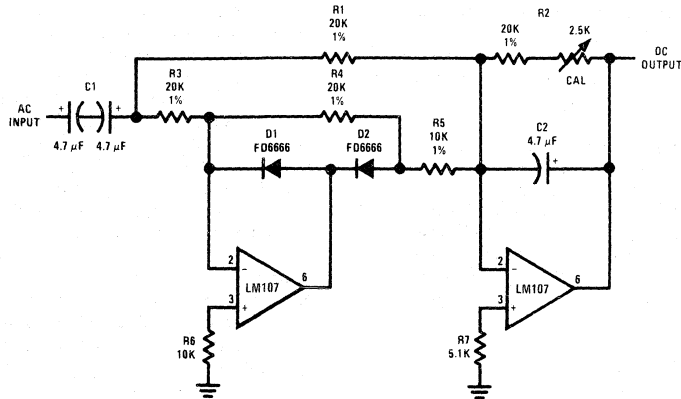


FIGURE 23. Full-Wave Rectifier and Averaging Filter

feedback resistor, R5. A1 gain accuracy is not affected by D2 since it is inside the feedback loop. Positive current enters the A2 summing point through resistor, R1, and negative current is drawn from the A2 summing point through resistor, R5. Since the voltages across R1 and R5 are equal and opposite, and R5 is one-half the value of R1, the net input current at the A2 summing point is equal to and opposite from the current through R1 and amplifier A2 operates as a summing inverter with unity gain, again giving a positive output.

The circuit becomes an averaging filter when C2 is connected across R2. Operation of A2 then is similar to the Simple Low Pass Filter previously described. The time constant R2C2 should be chosen to be much larger than the maximum period of the input voltage which is to be averaged.

Capacitor C1 may be deleted if the circuit is to be used as an absolute value generator. When this is done, the circuit output will be the positive absolute value of the input voltage.

The amplifiers chosen must be compensated for unity-gain operation and R6 and R7 must be chosen to minimize output errors due to input offset current.

### SINE WAVE OSCILLATOR

An amplitude-stabilized sine-wave oscillator is shown in Figure 24. This circuit provides high purity sine-wave output down to low frequencies with minimum circuit complexity. An important advantage of this circuit is that the traditional tungsten filament lamp amplitude regulator is eliminated along with its time constant and linearity problems.

In addition, the reliability problems associated with a lamp are eliminated.

The Wein Bridge oscillator is widely used and takes advantage of the fact that the phase of the voltage across the parallel branch of a series and a parallel RC network connected in series, is the same as the phase of the applied voltage across the two networks at one particular frequency and that the phase lags with increasing frequency and leads with decreasing frequency. When this network—the Wein Bridge—is used as a positive feedback element around an amplifier, oscillation occurs at the frequency at which the phase shift is zero. Additional negative feedback is provided to set loop gain to unity at the oscillation frequency. To stabilize the frequency of oscillation, and to reduce harmonic distortion.

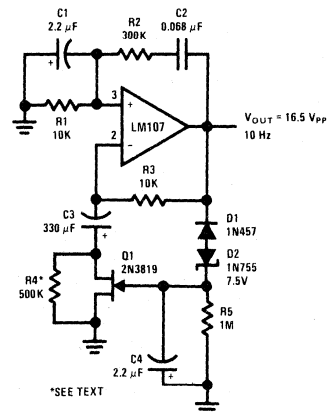


FIGURE 24. Wein Bridge Sine Wave Oscillator

The circuit presented here differs from the classic usage only in the form of the negative feedback stabilization scheme. Circuit operation is as follows: negative peaks in excess of  $-8.25V$  cause D1 and D2 to conduct, charging C4. The charge

stored in C4 provides bias to Q1, which determines amplifier gain. C3 is a low frequency roll-off capacitor in the feedback network and prevents offset voltage and offset current errors from being multiplied by amplifier gain.

Distortion is determined by amplifier open-loop gain and by the response time of the negative feedback loop filter, R5 and C4. A trade-off is necessary in determining amplitude stabilization time constant and oscillator distortion. R4 is chosen to adjust the negative feedback loop so that the FET is operated at a small negative gate bias. The circuit shown provides optimum values for a general-purpose oscillator.

### TRIANGLE-WAVE GENERATOR

A constant amplitude triangular-wave generator is shown in Figure 25. This circuit provides a variable frequency triangular wave whose amplitude is independent of frequency.

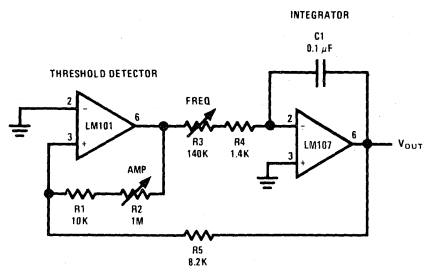


FIGURE 25. Triangular-Wave Generator

The generator embodies an integrator as a ramp generator and a threshold detector with hysteresis as a reset circuit. The integrator has been described in a previous section and requires no further explanation. The threshold detector is similar to a Schmitt Trigger in that it is a latch circuit with a large dead zone. This function is implemented by using positive feedback around an operational amplifier. When the amplifier output is in either the positive or negative saturated state, the positive feedback network provides a voltage at the non-inverting input which is determined by the attenuation of the feedback loop and the saturation voltage of the amplifier. To cause the amplifier to change states, the voltage at the input of the amplifier must be caused to change polarity by an amount in excess of the amplifier input offset voltage. When this is done the amplifier saturates in the opposite direction and remains in that state until the voltage at its input again reverses. The complete circuit operation may be understood by examining the operation with the output of the threshold detector in the positive state. The detector positive saturation voltage is applied to the integrator summing junction through the combination R3 and R4 causing a current  $I^+$  to flow.

The integrator then generates a negative-going ramp with a rate of  $I^+/C1$  volts per second until its output equals the negative trip point of the threshold detector. The threshold detector then changes to the negative output state and supplies a negative current,  $I^-$ , at the integrator summing point. The integrator now generates a positive-going ramp with a rate of  $I^-/C1$  volts per second until its output equals the positive trip point of the threshold detector where the detector again changes output state and the cycle repeats.

Triangular-wave frequency is determined by R3, R4 and C1 and the positive and negative saturation voltages of the amplifier A1. Amplitude is determined by the ratio of R5 to the combination of R1 and R2 and the threshold detector saturation voltages. Positive and negative ramp rates are equal and positive and negative peaks are equal if the detector has equal positive and negative saturation voltages. The output waveform may be offset with respect to ground if the inverting input of the threshold detector, A1, is offset with respect to ground.

The generator may be made independent of temperature and supply voltage if the detector is clamped with matched zener diodes as shown in Figure 26.

The integrator should be compensated for unity-gain and the detector may be compensated if power supply impedance causes oscillation during its transition time. The current into the integrator should be large with respect to  $I_{bias}$  for maximum symmetry, and offset voltage should be small with respect to  $V_{OUT}$  peak.

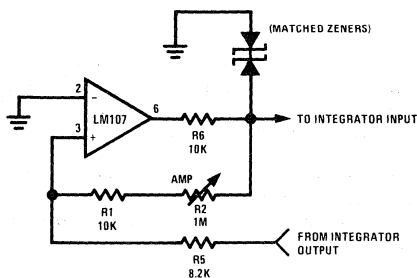


FIGURE 26. Threshold Detector with Regulated Output

### TRACKING REGULATED POWER SUPPLY

A tracking regulated power supply is shown in Figure 27. This supply is very suitable for powering an operational amplifier system since positive and negative voltages track, eliminating common mode signals originating in the supply voltage. In addition, only one voltage reference and a minimum number of passive components are required.



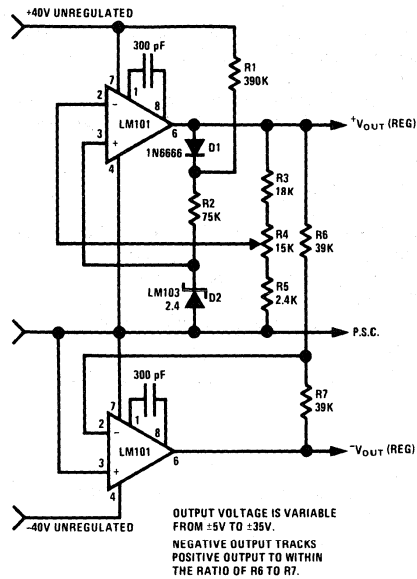


FIGURE 27. Tracking Power Supply

Power supply operation may be understood by considering first the positive regulator. The positive regulator compares the voltage at the wiper of R4 to the voltage reference, D2. The difference between these two voltages is the input voltage for the amplifier and since R3, R4, and R5 form a negative feedback loop, the amplifier output voltage changes in such a way as to minimize this difference. The voltage reference current is supplied from the amplifier output to increase power supply line regulation. This allows the regulator to operate from supplies with large ripple voltages. Regulating the reference current in this way requires a separate source of current for supply start-up. Resistor R1 and diode D1 provide this start-up current. D1 decouples the reference string from the amplifier output during start-up and R1 supplies the start-up current from the unregulated positive supply. After start-up, the low amplifier output impedance reduces reference current variations due to the current through R1.


The negative regulator is simply a unity-gain inverter with input resistor, R6, and feedback resistor, R7.

The amplifiers must be compensated for unity-gain operation.


The power supply may be modulated by injecting current into the wiper of R4. In this case, the output voltage variations will be equal and opposite at the positive and negative outputs. The power supply voltage may be controlled by replacing D1, D2, R1 and R2 with a variable voltage reference.
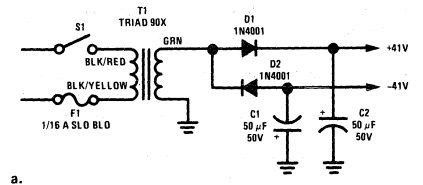
## PROGRAMMABLE BENCH POWER SUPPLY


The complete power supply shown in Figure 28 is a programmable positive and negative power supply. The regulator section of the supply comprises two voltage followers whose input is provided by the voltage drop across a reference resistor of a precision current source.



a.

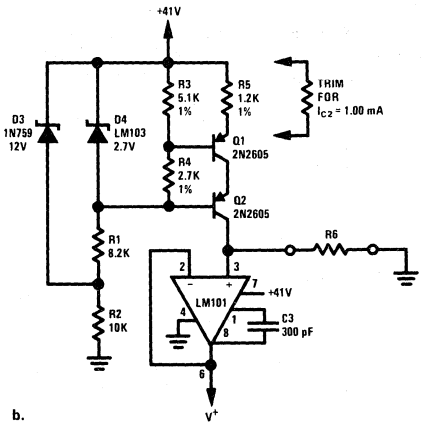

b.

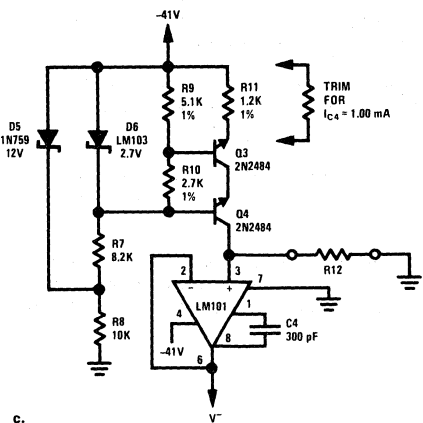

c.

FIGURE 28. Low-Power Supply for Integrated Circuit Testing

Programming sensitivity of the positive and negative supply is  $1V/1000\Omega$  of resistors R6 and R12 respectively. The output voltage of the positive regulator may be varied from approximately +2V to +38V with respect to ground and the negative regulator output voltage may be varied from -38V to 0V with respect to ground. Since LM107 amplifiers are used, the supplies are inherently short circuit proof. This current limiting feature also serves to protect a test circuit if this supply is used in integrated circuit testing.

Internally compensated amplifiers may be used in this application if the expected capacitive loading is small. If large capacitive loads are expected, an

externally compensated amplifier should be used and the amplifier should be overcompensated for additional stability. Power supply noise may be reduced by bypassing the amplifier inputs to ground with capacitors in the 0.1 to 1.0  $\mu F$  range.

## CONCLUSIONS

The foregoing circuits are illustrative of the versatility of the integrated operational amplifier and provide a guide to a number of useful applications. The cautions noted in each section will show the more common pitfalls encountered in amplifier usage.

## APPENDIX I DEFINITION OF TERMS

**Input Offset Voltage:** That voltage which must be applied between the input terminals through two equal resistances to obtain zero output voltage.

**Input Offset Current:** The difference in the currents into the two input terminals when the output is at zero.

**Input Bias Current:** The average of the two input currents.

**Input Voltage Range:** The range of voltages on the input terminals for which the amplifier operates within specifications.

**Common Mode Rejection Ratio:** The ratio of the input voltage range to the peak-to-peak change in input offset voltage over this range.

**Input Resistance:** The ratio of the change in input voltage to the change in input current on either input with the other grounded.

**Supply Current:** The current required from the power supply to operate the amplifier with no load and the output at zero.

**Output Voltage Swing:** The peak output voltage swing, referred to zero, that can be obtained without clipping.

**Large-Signal Voltage Gain:** The ratio of the output voltage swing to the change in input voltage required to drive the output from zero to this voltage.

**Power Supply Rejection:** The ratio of the change in input offset voltage to the change in power supply voltage producing it.

**Slew Rate:** The internally-limited rate of change in output voltage with a large-amplitude step function applied to the input.

## REFERENCES

1. D.C. Amplifier Stabilized for Zero and Gain; Williams, Tapley, and Clark; AIEE Transactions, Vol. 67, 1948.
2. Active Network Synthesis; K. L. Su, McGraw-Hill Book Co., Inc., New York, New York.
3. Analog Computation; A. S. Jackson, McGraw-Hill Book Co., Inc., New York, New York.
4. A Palimpsest on the Electronic Analog Art; H. M. Paynter, Editor. Published by George A. Philbrick Researches, Inc., Boston, Mass.
5. Drift Compensation Techniques for Integrated D.C. Amplifiers; R. J. Widlar, EDN, June 10, 1968.
6. A Fast Integrated Voltage Follower With Low Input Current; R. J. Widlar, Microelectronics, Vol. 1 No. 7, June 1968.

# Designs for Negative Voltage Regulators

National Semiconductor  
Application Note 21  
December 1968




## INTRODUCTION

A number of IC voltage regulators have been introduced to date, but these have been designed primarily to regulate positive voltages. Most can be adapted as negative regulators, at some sacrifice in complexity, performance and flexibility. This note, however, describes an IC, which is designed specifically as a negative regulator. It is intended to complement the LM100 and LM105 positive regulators, providing a line of IC's for practically every regulator application.

Unique features of the circuit are that it supplies any output voltage from 0V down to -40V, while operating from a single unregulated supply. The output voltage is proportional to a single programming resistor, and remote sensing can be done at the load. It also regulates within 0.01% in circuits using a separate, floating bias supply, where the maximum output voltage is limited only by the breakdown of external pass transistors. The device is designed for either linear or switching regulator applications.

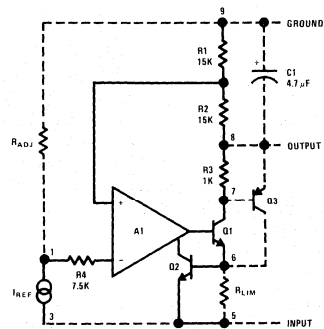In the circuits described, emphasis is placed on practical considerations for the design of reliable regulators. Many of the pitfalls which cause unexpected failures are explained, and protection schemes for many of the hazards facing regulators are given. Most of the design hints are sufficiently general to apply equally to other IC's or even regulators designed entirely with discrete components.



A functional diagram of the LM104 regulator and external circuitry (dash line) is shown in the figure. The internal reference is a temperature compensated current source,  $I_{ref}$ . A voltage which is proportional to an external programming resistor,  $R_{adj}$ , is fed into an error amplifier, A1. This drives an internal series pass transistor, Q1, to supply an output voltage equal to twice the voltage across the programming resistor. External pass transistors can be added, as is Q3, to increase the output-current capability. Short-circuit protection makes the circuit exhibit a constant-current characteristic when Q2 is turned on by the voltage drop across an external current-limit resistor,  $R_{lim}$ . A more complete description of the integrated circuit itself is given in the back of the text.


## LOW POWER REGULATOR OR BIAS SUPPLY

This circuit can provide output voltages between 0V and -40V at currents up to 25 mA. The output voltage is linearly dependent on the value of R2, giving approximately 2V for each 1 K $\Omega$  of resistance. The exact scale factor can be set up by trimming R1. This should be done at the maximum output voltage setting in order to compensate for any mismatch in the internal divider resistors of the integrated circuit.

Short-circuit protection is provided by R3. The value of this resistor should be chosen so that the voltage drop across it is 300 mV at the maximum load current. This insures worst-case operation up to full load over a -55°C to 125°C temperature range. With a lower maximum operating temperature, the design value for this voltage can be increased linearly to 525 mV at 25°C.

For an output voltage setting of 15V, the regulation, no load to full load, is better than 0.05%; and the line regulation is better than 0.2% for a  $\pm 20\%$  input voltage variation. Noise and ripple can be greatly reduced by bypassing R2 with a 10  $\mu$ F capacitor. This will keep the ripple on the output less than 0.5 mV for a 1V, 120 Hz ripple on the unregulated input. The capacitor also improves the line-transient response by a factor of five.

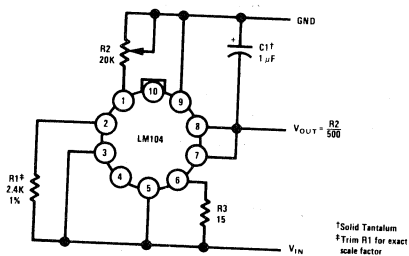
An output capacitor of at least 1  $\mu$ F is required to keep the regulator from oscillating. This should be a low inductance capacitor, preferably solid tantalum, installed with short leads. It is not usually necessary to bypass the input, but at least a 0.01  $\mu$ F bypass is advisable when there are long leads connecting the circuit to the unregulated power source.



It is important to watch power dissipation in the integrated circuit even with load currents of 25 mA or less. The dissipation can be in excess of 1W with large input-output voltage differentials, and this is above ratings for the device.
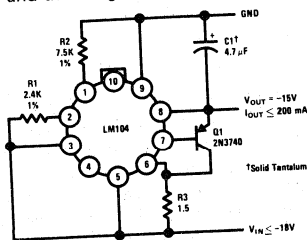
## INCREASED OUTPUT CURRENT

When output currents above 25 mA are required or when the dissipation in the series pass transistor can be higher than about 0.2W, under worst-case conditions, it is advisable to add an external transistor to the LM104 to handle the power. The connection of an external booster transistor is shown here. The output current capability of the regulator is increased by the current gain of the added PNP transistor, but it is still necessary to watch dissipation in the external pass transistor. Excessive dissipation can burn out both the series pass transistor and the integrated circuit.



For example, with the circuit shown, the worst-case input voltage can be 25V. With a shorted output at 125°C, the current through the pass

transistor will be 300 mA; and the dissipation in it will be 7.5W. This clearly establishes the need for an efficient heat sink.

For lower-power operation, a 2N2905 with a clip on heat sink can be used for the external pass transistor. However, when the worst case dissipation is above 0.5W, it is advisable to employ a power device such as the 2N3740 with a good heat sink.

The current limit resistor is chosen so that the voltage drop across it is 300 mV, with maximum load current, for operation to 125°C. With lower maximum ambients this voltage drop could be increased by 2.2 mV/°C. If possible, a fast-acting fuse rated about 25% higher than the maximum load current should be included in series with the unregulated input.

When a booster transistor is used, the minimum input-output voltage differential of the regulator will be increased by the emitter-base voltage of the added transistor. This establishes the minimum differential at 2 to 3V, depending on the base drive required by the external transistor.

## HIGH CURRENT REGULATOR

When output currents in the ampere range are needed, it is necessary to add a second booster transistor to the LM104 circuitry. This connection is shown in the accompanying figure. The output current capability of the LM104 is increased by the product of the current gains of Q1 and Q2. However, it is still necessary to watch the dissipation in both the series pass transistor, Q2, and its driver, Q1. A clip-on heat sink is definitely required for Q1, and it is advisable to replace the 2N2905 with a 2N3740 which has a good heat sink when output currents greater than 1A are needed. A 1000 pF capacitor should also be added between Pins 4 and 5 to compensate for the poorer frequency response of the 2N3740. The need for an efficient heat sink on Q2 should be obvious.

Experience shows that a single-diffused transistor such as a 2N3055 (or a 2N3772 for higher currents) is preferred over a double diffused, high-frequency transistor for the series pass element. The slower, single-diffused devices are less prone to secondary breakdown and oscillations in linear regulator applications.

As with the lower-current regulators, C1 is required to frequency compensate the regulator and prevent oscillations. It is also advisable to bypass the input with C2 if the regulator is located any distance from the output filter of the unregulated supply. The resistor across the emitter base junction of Q2 fixes the minimum collector current of Q1 to minimize oscillation problems with light loads. It is still possible to experience oscillations with certain physical layouts, but these can almost always be eliminated by stringing a ferrite bead, such as a Ferroxcube K5-001-00/3B, on the emitter lead of Q2.


The use of two booster transistors does not appreciably increase the minimum input-output voltage differential over that for a single transistor. The minimum differential will be 2 to 3V, depending on the drive current required from the integrated circuit.

With high current regulators, remote sensing is sometimes required to eliminate the effect of line

resistance between the regulator and the load. This can be accomplished by returning R2 and Pin 9 of the LM104 to the ground end of the load and connecting Pin 8 directly to the high end of the load.

The low resistance values required for the current limit resistor, R3, are sometimes not readily available. A suitable resistor can be made using a piece of resistance wire or even a short length of kovar lead wire from a standard TO-5 transistor.

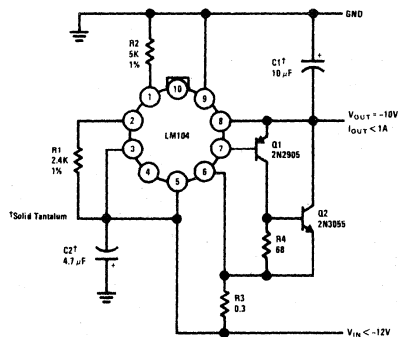
The current limit sense voltage can be reduced to about 400 mV by inserting a germanium diode (or a diode-connected germanium transistor) in series with Pin 6 of the LM104. This diode will also compensate the sense voltage and make the short circuit current essentially independent of temperature.



With high current regulators it is especially important to use a low-inductance capacitor on the output. The lead length on this capacitor must also be made short. Otherwise, the capacitor leads can resonate with smaller bypass capacitors (like 0.1 μF ceramic) which may be connected to the output. These resonances can lead to oscillations. With short leads on the output capacitor, the Q of the tuned circuit can be made low enough so that it cannot cause trouble.
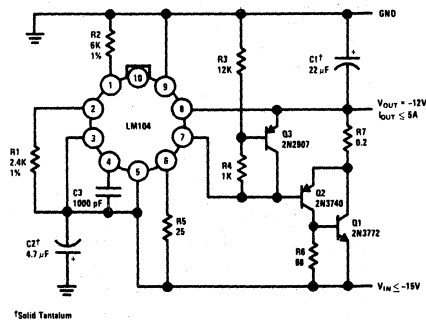
## FOLDBACK CURRENT LIMITING

High current regulators dissipate a considerable amount of power in the series pass transistor under full-load conditions. When the output is shorted, this dissipation can easily increase by a factor of four. Hence, with normal current limiting, the heat sink must be designed to handle much more power than the worst case full load dissipation if the circuit is to survive short-circuit conditions. This can increase the bulk of the regulator substantially.



This situation can be eased considerably by using foldback current limiting. With this method of current limiting, the available output current actually decreases as the maximum load on the regulator is exceeded and the output voltage falls off. The short-circuit current can be adjusted to be a frac-

tion of the full load current, minimizing dissipation in the pass transistor.

The circuit shown here accomplishes just this. Normally Q3 is held in a non-conducting state by the voltage developed across R4. However, when the voltage across the current limit resistor, R7, increases to where it equals the voltage across R4 (about 1V), Q3 turns on and begins to rob base drive from the driver transistor, Q1. This causes an increase in the output current of the LM104, and it will go into current limiting at a current determined by R5. Since the base drive to Q1 is clamped, the output voltage will drop with heavier loads. This reduces the voltage drop across R4 and, therefore, the available output current. With the output completely shorted, the current will be about one-fifth the full-load current.

In design, R7 is chosen so that the voltage drop across it will be 1 to 2V under full load conditions. The resistance of R3 should be one-thousand times the output voltage. R4 is then determined from

$$R_4 \cong \frac{R_7 R_3 I_{FL}}{V_{OUT} + 0.5}$$

where  $I_{FL}$  is the load current at which limiting will occur.


If it is desired to reduce the ratio of full load to short circuit current, this can be done by connecting a resistance of 2 to 10 K $\Omega$  across the emitter-base of Q3.

## SYMMETRICAL POWER SUPPLIES

In many applications, such as powering operational amplifiers, there is a need for symmetrical positive and negative supply voltages. A circuit which is a particularly-economical solution to this design problem is shown in the adjoining figure. It uses a minimum number of components, and the voltage at both outputs can be set up within  $\pm 1.5\%$  by a single adjustment. Further, the output voltages will tend to track with temperature and variations on the unregulated supply.

The positive voltage is regulated by an LM105, while an LM104 regulates the negative supply. The unusual feature is that the two regulators are interconnected by R3. This not only eliminates one precision resistor, but the reference current of the LM104 stabilizes the LM105 so that a  $\pm 10\%$  variation in its reference voltage is only seen as a  $\pm 3\%$  change in output voltage. This means that in many cases the output voltage of both regulators can be set up with sufficient accuracy by trimming a single resistor, R1.

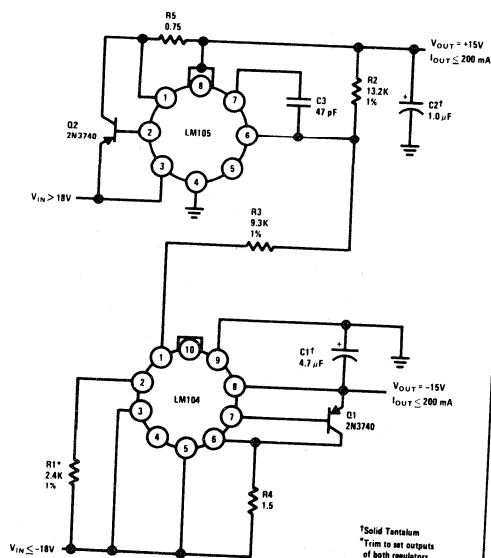The line regulation and temperature drift of the circuit is determined primarily by the LM104, so both output voltages will tend to track. Output ripple can be reduced by about a factor of five to less than  $2\text{mV/V}$  by bypassing Pin 1 of the




LM104 to ground with a  $10\mu\text{F}$  capacitor. A center-tapped transformer with a bridge rectifier can be used for the unregulated power source.


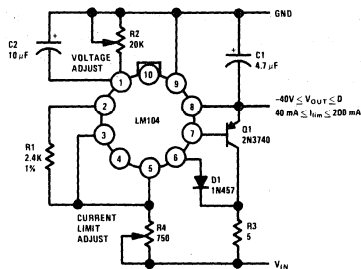
## ADJUSTABLE CURRENT LIMITING

In laboratory power supplies, it is often necessary to adjust the limiting current of a regulator. This, of course, can be done by using a variable resistance for the current limit resistor. However, the current-limit resistor can easily have a value below that of commercially-available potentiometers. Discrete resistance values can be switched to vary the limiting current, but this does not provide continuously-variable adjustment.




The circuit shown here solves this problem, giving a linear adjustment of limiting current over a five-to-one range. A silicon diode, D1, is included to reduce the current limit sense voltage to approximately 50 mV. Approximately 1.3 mA from the reference supply is passed through a potentiometer, R4, to buck out the diode voltage. Therefore, the effective current limit sense voltage is nearly proportional to the resistance of R4. The current through R4 is fairly insensitive to changes in ambient temperature, and D1 compensates for temperature variations in the current limit sense voltage of the LM104. Therefore, the limiting current will not be greatly affected by temperature.

It is important that a potentiometer be used for R4 and connected as shown. If a rheostat connection were used, it could open while it was being adjusted and momentarily increase the current limit sense voltage to many times its normal value. This could destroy the series pass transistors under short-circuit conditions.

The inclusion of R4 will soften the current limiting characteristics of the LM104 somewhat because it acts as an emitter-degeneration resistor for the current-limit transistor. This can be avoided by reducing the value of R4 and developing the voltage across R4 with additional bleed current to ground.
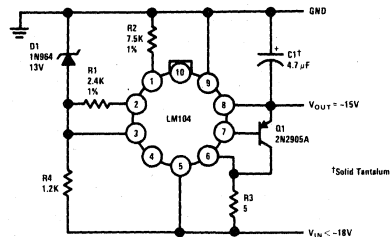
## IMPROVING LINE REGULATION

The line regulation for voltage variations on the reference supply terminal of the LM104 is about five times worse than it is for changes on the unregulated input. Therefore, a zener-diode pre-regulator can be used on the reference supply to improve line regulation. This is shown in the figure.



The design of this circuit is fairly simple. It is only necessary that the minimum current through R4 be greater than 2 mA with low input voltage. Further, the zener voltage of D1 must be five volts greater than one-half the maximum output voltage to keep the transistors in the reference current source from saturating.

## USING PROTECTIVE DIODES

It is a little known fact that most voltage regulators can be damaged by shorting out the unregulated input voltage while the circuit is operating—even though the output may have short-circuit protection. When the input voltage to the regulator falls instantaneously to zero, the output capacitor is still charged to the nominal output voltage. This applies voltage of the wrong polarity across the series pass transistor and other parts of the regulator, and they try to discharge the output capacitor into the short. The resulting current surge can damage or destroy these parts.

When the LM104 is used as the control element of the regulator, the discharge path is through internal junctions forward biased by the voltage reversal. If the charge on the output capacitor is in the order of  $40 \text{ volt} \cdot \mu\text{F}$ , the circuit can be damaged during the discharge interval. However, the problem is not only seen with integrated circuit regulators. It also happens with discrete regulators where the series-pass transistor usually gets blown out.


The problem can be eliminated by connecting a diode between the output and the input such that it discharges the output capacitor when the input is shorted. The diode should be capable of handling large current surges without excessive voltage drop, but it does not have to be a power diode since it does not carry current continuously. It should also be relatively fast. Ordinary rectifier diodes will not do because they look like an open circuit in the forward direction until minority carriers are injected into the intrinsic base region of the PIN structure.

This problem is not just caused by accidental physical shorts on the input. It has shown up more than once when regulators are driven from high-frequency dc-dc converters. Tantalum capacitors are frequently used as output filters for the rectifiers. When these capacitors are operated near their maximum voltage ratings with excessive high frequency ripple across them, they have a tendency to sputter—that is, short momentarily and clear themselves. When they short, they can blow out the regulator; but they look innocent after the smoke has cleared.

The solution to this problem is to use capacitors with conservative voltage ratings, to observe the maximum ripple ratings for the capacitor and to include a protective diode between the input and output of the regulator to protect it in case sputtering does occur.

Heavy loads operating from the unregulated supply can also destroy a voltage regulator. When the input power is switched off, the input voltage can drop faster than the output voltage, causing a voltage reversal across the regulator, especially when the output of the regulator is lightly loaded. Inductive loads such as a solenoid are particularly troublesome in this respect. In addition to causing a voltage reversal between the input and the output, they can reverse the input voltage causing additional damage.

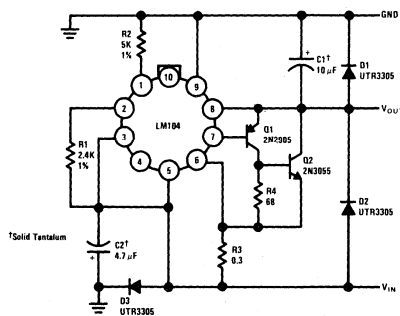In cases like this, it is advisable to use a multiple-pole switch or relay to disconnect the regulator from the unregulated supply separate from the other loads. If this cannot be done, it is necessary to put a diode across the input of the regulator to clamp any reverse voltages, in addition to the protective diode between the input and the output.




Yet another failure mode can occur if the regulated supply drives inductive loads. When power is shut off, the inductive current can reverse the output voltage polarity, damaging the regulator and the output capacitor. This can be cured with a clamp diode on the output. Even without inductive loads it is usually good practice to include this clamp diode to protect the regulator if its output is accidentally shorted to a negative supply.

A regulator with all these protective diodes is shown here. D1 protects against output voltage reversal. D2 prevents a voltage reversal between the input and the output of the regulator. And D3 prevents a reversal of the input-voltage polarity. In many cases, D3 is not needed if D1 and D2 are used, since these diodes will clamp the input voltage within two diode drops of ground. This is adequate if the input voltage reversals are of short duration.
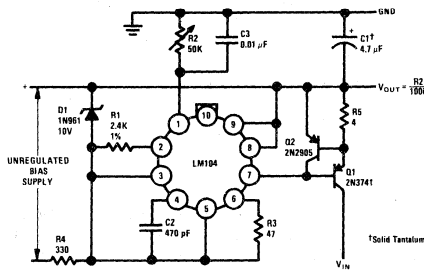
## HIGH VOLTAGE REGULATOR

In the design of commercial power supplies, it is common practice to use a floating bias supply to power the control circuitry of the regulator. As shown here, this connection can be used with the LM104 to regulate output voltages that are higher than the ratings of the integrated circuit. Better regulation can also be obtained because it is a simple matter to preregulate the low current bias supply so that the integrated circuit does not see ripple or line voltage variations and because the reduced operating voltage minimizes power dissipation and associated thermal effects from the current delivered to the booster transistor.



The bias for the LM104, which is normally obtained from a separate winding on the main power transformer, is preregulated by D1. R4 is selected so that it can provide the 3 mA operating current for the integrated circuit as well as the base drive of the booster transistor, Q1, with full load and minimum line voltage. The booster transistor regulates the voltage from the main

supply, and its breakdown voltage will determine the maximum operating voltage of the complete regulator.

The connection of the LM104 is somewhat different than usual: the internal divider for the error amplifier is shorted out by connecting Pins 8 and 9 together. This makes the output voltage equal to the voltage drop across the adjustment resistor, R2, instead of twice this voltage as is normally the case. C2 and C3 must also be added to prevent oscillation. The value of C3 can be increased to 4.7  $\mu$ F to reduce noise on the output.

It is necessary to add Q2 and R5 to provide current limiting. When the output current becomes high enough to turn on Q2, there will be an abrupt rise in the output current of the LM104 as Q2 tries to remove base drive from the booster transistor. Any further increases in load current will cause the LM104 to limit at a current determined by R3, and the output voltage will collapse. The value of R3 must be selected so that the integrated circuit can deliver the base current of Q1, at full load, without limiting.

A second, NPN booster transistor can be used in a compound connection with Q1 to increase the output current of the regulator. However, with very-high-voltage regulators, the most economical solution may be to use a high voltage PNP driving a vacuum tube for the series pass element.

Remote sensing, which eliminates the effects of voltage dropped in the leads connecting the regulator to the load, can be provided by connecting R2 to the ground end of the load and Pins 8 and 9 to the high end of the load.

## SWITCHING REGULATOR

Linear regulators have the advantages of fast response to load transients as well as low noise and ripple. However, since they must dissipate the difference between the unregulated-supply power and the output power, they sometimes have a low efficiency. This is not always a problem with ac line-operated equipment because the power loss is easily afforded, because the input voltage is already fairly-well regulated and because losses can be minimized by adjustment of transformer ratios in the power supply. In systems operating from a fixed dc input voltage, the situation is often much different. It might be necessary to regulate a 28V input voltage down to 5V. In this case, the power loss can quickly become excessive. This is true even if efficiency is not one of the more important criteria, since high power dissipation calls for expensive power transistors and elaborate heat sinking methods.


Switching regulators can be used to greatly reduce dissipation. Efficiencies approaching 90% can be realized even though the regulated output voltage is only a fraction of the input voltage. With proper design, transient response and ripple can also be made quite acceptable.

This circuit, which uses the LM104 as a self-oscillating switching regulator, operates in much the same way as a linear regulator. The reference current is set up at 1 mA with R1, and R2 determines the output voltage in the normal fashion. The circuit is made to oscillate by applying positive feedback through R5 to the non-inverting input on the error amplifier of the LM104. When the output voltage is low, the internal pass transistor of the integrated circuit turns on and drives Q1 into saturation. The current feedback through R5 then increases the magnitude of the reference voltage developed across R2. Q1 will remain on until the output voltage comes up to twice this reference voltage. At this point, the error amplifier goes into linear operation, and the positive feedback makes the circuit switch off. When this happens, the reference voltage is lowered by feedback through R5, and the circuit will stay off until the output voltage drops to where the error amplifier again goes into linear operation. Hence, the circuit regulates with the output voltage oscillating about the nominal value with a peak-to-peak ripple of around 40 mV.

The power conversion from the input voltage to a lower output voltage is obtained by the action of

the switch transistor, Q1, the catch diode, D1, and the LC filter. The inductor is made large enough so that the current through it is essentially constant throughout the switching cycle. When Q1 turns on, the voltage on its collector will be nearly equal to the unregulated input voltage. When it turns off, the magnetic field in L1 begins to collapse, driving the collector voltage of Q1 to ground where it is clamped by D1.

If, for example, the input voltage is 10V and the switch transistor is driven at a 50% duty cycle, the average voltage on the collector of Q1 will be 5V. This waveform will be filtered by L1 and C1 and appear as a 5V dc voltage on the output. Since the inductor current comes from the input while Q1 is on but from ground through D1 while Q1 is off, the average value of the input current will be half the output current. The power output will therefore equal the input power if switching losses are neglected.

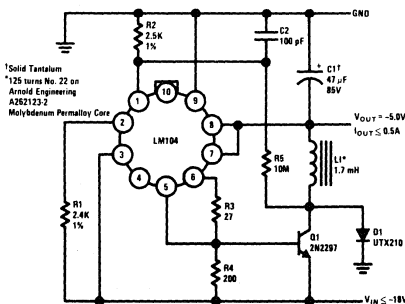


In design, the value of R3 is chosen to provide sufficient base drive to Q1 at the maximum load current. R4 must be low enough so that the bias current coming out of Pin 5 of the LM104 (approximately 300  $\mu$ A) does not turn on the switch transistor. The purpose of C2 is to remove transients that can appear across R2 and cause erratic switching. It should not be made so large that it severely integrates the waveform feedback to this point.

For additional information on switching regulators see "Designing Switching Regulators," National Semiconductor AN-2, August, 1968.
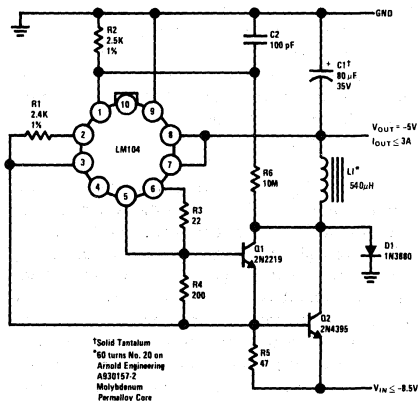
## HIGH CURRENT SWITCHING REGULATOR

Output currents up to 3A can be obtained using the switching regulator circuit shown here. The circuit is identical to the one described previously, except that Q2 has been added to increase the output current capability by about an order of magnitude. It should be noted that the reference supply terminal is returned to the base of Q2, rather than the unregulated input. This is done because the LM104 will not function properly if Pin 5 gets more than 2V more positive than Pin 3. The reference current, as well as the bias currents for Pins 3 and 5, is supplied from the unregulated input through R5, so its resistance must be low enough so that Q2 is not turned on with about 2 mA flowing through it.

The line regulation of this circuit is worsened somewhat by the unregulated input voltage being fed back into the reference for the regulator through R6. This effect can be eliminated by connecting a 0.01  $\mu$ F capacitor in series with R6 to remove the dc component of the feedback.



There are a number of precautions that should be observed with all switching regulators, although they are more inclined to cause problems in high-current applications:

For one, fast switching diodes and transistors must be used. If D1 is an ordinary junction rectifier, voltages in the order of 10V can be developed across it in the forward direction when the switch transistor turns off. This happens because low-frequency rectifiers are usually manufactured with a PIN structure which presents a high forward impedance until enough minority carriers are injected into the diode base region to increase its conductance. This not only causes excessive dis-

sipation in the diode, but the diode also presents a short circuit to the switch transistor, when it first turns on, until all the charge stored in the base region of the diode is removed. Similarly, a high frequency switch transistor must be used as excessive switching losses in low frequency transistors, like the 2N3055, make them overheat.

It is important that the core material used for the inductor have a soft saturation characteristic. Cores that saturate abruptly produce excessive peak currents in the switch transistor if the output current becomes high enough to run the core close to saturation. Powdered molybdenum-permalloy cores, on the other hand, exhibit a gradual reduction in permeability with excessive current, so the only effect of output currents above the design value is a gradual increase in switching frequency.


One thing that is frequently overlooked in the design of switching circuits is the ripple rating of the filter capacitors. Excessive high-frequency ripple can cause these capacitors to fail. This is an especially-important consideration for capacitors used on the unregulated input as the ripple current through them can be higher than the dc load current. The situation is eased somewhat for the filter capacitor on the output of the regulator since the ripple current is only a fraction of the load current. Nonetheless, proper design usually requires that the voltage rating of this capacitor be higher than that dictated by the dc voltage across it for reliable operation.

One unusual problem that has been noted in working with switching regulators is excessive dissipation in the switch transistors caused by high emitter-base saturation voltage. This can also show up as erratic operation if Q1 is the defective device. This saturation voltage can be as high as 5V and is the result of poor alloying on the base contact of the transistor. A defective transistor will not usually show up on a curve tracer because the low base current needed for linear operation does not produce a large voltage drop across the poorly-alloyed contact. However, a bad device can be spotted by probing on the bases of the switch transistors while the circuit is operating.

It is necessary that the catch diode, D1, and any bypass capacitance on the unregulated input be returned to ground separately from the other parts of the circuit. These components carry large current transients and can develop appreciable voltage transients across even a short length of wire. If C1, C2, or R2 have any common ground impedance with the catch diode or the input bypass capacitor, the transients can appear directly on the output.
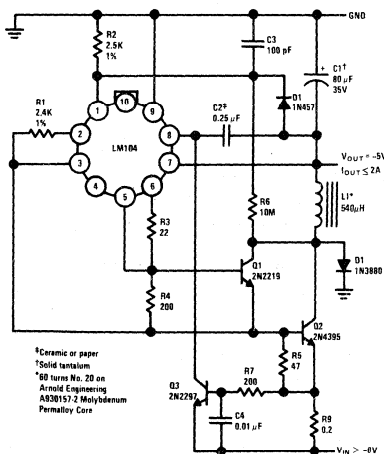
## SWITCHING REGULATOR WITH CURRENT LIMITING

The switching regulator circuits described previously are not protected from overloads or a short-circuited output. The current limiting of the LM104 is used to limit the base drive of the switch transistor, but this does not effectively protect the switch transistor from excessive current. Providing short circuit protection is no simple problem, since it is necessary to keep the regulator operating in the switching mode when the output is shorted. Otherwise, the dissipation in the switch transistor will become excessive even though the current is limited.



A circuit which provides current limiting and protects the regulator from short circuits is shown here. The current through the switch transistor produces a voltage drop across R9. When this volt-

age becomes large enough to turn on Q3, current limiting is initiated. This occurs because Q3 takes over as the control transistor and regulates the voltage on Pin 8 of the LM104. This point, which is the feedback terminal of the error amplifier, is separated from the actual output of the regulator by not shorting the regulated output and booster output terminals of the integrated circuit. Hence, with excessive output current, the circuit still operates as a switching regulator with Q3 regulating the voltage fed back to the error amplifier as the output voltage falls off.

A resistor, R7, is included so that excessive base current will not be driven into the base of Q3. C4 insures that Q3 does not turn on from the current spikes through the switch transistor caused by pulling the stored charge out of the catch diode (these are about twice the load current). This capacitor also operates in conjunction with C2 to produce sufficient phase delay in the feedback loop so that the circuit will oscillate in current limiting. However, C4 should not be made so large that it appreciably integrates the rectangular waveform of the current through the switch transistor.

As the output voltage falls below half the design value, D1 pulls down the reference voltage across R2. This permits the current limiting circuitry to keep operating when the unregulated input voltage drops below the design value of output voltage, with a short on the output of the regulator.

A transistor with good high-current capability was chosen for Q3 so that it does not suffer from secondary breakdown effects from the large peak currents (about 200 mA) through it. With a shorted output, these peak currents occur with the full input voltage across Q3. The average dissipation in Q3 is, however, low.


### SWITCHING REGULATOR WITH OVERLOAD SHUTOFF

An alternate method for protecting a switching regulator from excessive output currents is shown here. When the output current becomes too high, the voltage drop across the current-sense resistor, R8, fires an SCR which shuts off the regulator. The regulator remains off, dissipating practically

no power, until it is reset by removing the input voltage.


In the actual circuit, complementary transistors, Q3 and Q4, replace the SCR since it is difficult to find devices with a low enough holding current (about  $25 \mu\text{A}$ ). When the voltage drop across R8 becomes large enough to turn on Q4, this removes the base drive for the output transistors of the LM104 through Pin 4. When this happens Q3 latches Q4, holding the regulator off until the input voltage is removed. It will then start when power is applied if the overload has been removed.

With this circuit, it is necessary that the shutoff current be 1.5 times the full load current. Otherwise, the circuit will shut off when it is switched on with a full load because of the excess current required to charge the output capacitor. The shutoff current can be made closer to the full load current by connecting a  $10 \mu\text{F}$  capacitor across R2 which will limit the charging current for C1 by slowing the risetime of the output voltage when the circuit is turned on. However, this capacitor will also bypass the positive feedback from R6 which makes the regulator oscillate. Therefore, it is necessary to put a  $270 \Omega$  resistor in the ground end of the added capacitor and provide feedback to this resistor from the collector of Q1 through a  $1 \text{ M}\Omega$  resistor.

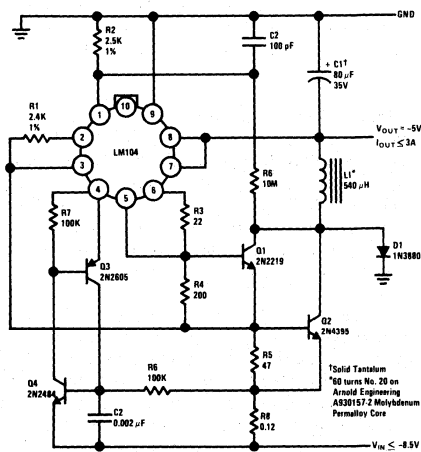
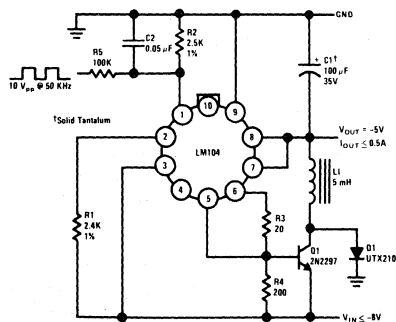
## DRIVEN SWITCHING REGULATOR

When a number of switching regulators are operated from a common power source, it is desirable to synchronize their operation to more uniformly distribute the switched current waveforms in the input line. Synchronous operation can also be beneficial when a switching regulator is operated in conjunction with a power converter.



A circuit which synchronizes the switching regulator with a square wave drive signal is shown here. It differs from the switching regulators described previously in that positive feedback is not used. Instead, a triangular wave with a peak-to-peak amplitude of 25 mV is applied to the noninverting

input of the error amplifier. The waveform is obtained by integrating the square wave synchronizing signal. This triangular wave causes the error amplifier to switch because its gain is high enough that the waveform easily overdrives it. The switching duty cycle is controlled by the output voltage fed back to the error amplifier. If the output voltage goes up, the duty cycle will decrease since the error amplifier will pick off a smaller portion of the triangular wave. Similarly, the duty cycle will decrease if the output voltage drops. Hence, the duty cycle is controlled to produce the desired output voltage.

Without a synchronous drive signal, the circuit will self oscillate at a frequency determined by L1 and C1. This self-oscillation frequency must be lower than the synchronous drive frequency. Therefore, more filtering is required for a driven regulator than for a self-oscillating regulator operating at the same frequency. This also means that a driven regulator will have less output ripple.

The value of C2 is chosen so that its capacitive reactance at the drive frequency is less than one-tenth the resistance of R2. The amplitude of the triangular wave is set at 25 mV with R5. It is advisable to ac couple the drive signal by putting a capacitor in series with R5 so that it does not disturb the dc reference voltage developed for the error amplifier.



## THE LM104 REGULATOR


The basic reference for the regulator is zener diode D1. The reference diode is supplied from a PNP current source, Q8, which has a fixed current gain of 2. This arrangement permits the circuit to operate with unregulated input voltages as low as 7V, substantially increasing the efficiency of low-voltage regulators.

The reference supply is temperature compensated by using the negative temperature coefficient of the transistor emitter-base voltages to cancel the positive coefficient of the zener diode. The design produces a nominal 2.4V between the reference and reference supply terminals of the integrated circuit. Connecting an external 2.4 K $\Omega$  resistor between those terminals gives a 1 mA reference current from the collectors of Q1 and Q2, which is independent of temperature. The reference voltage supplied to the error amplifier is developed across a second external resistor connected between the adjustment terminal and ground.

The reference supply terminal is normally connected to the unregulated supply. However, improved line regulation can be obtained by pre-regulating the voltage on this terminal. This improvement occurs because Q1, Q2, and Q7 do not see changes in input voltage. Normally, it is the change in the emitter-base voltage of these transistors with changes in collector-base voltage which determines the line regulation.

When the reference supply and unregulated input terminals are operated from separate voltage sources, it is important to make sure that the unregulated input terminal of the integrated circuit does not get more than 2V more positive than the reference supply terminal. If this happens, the collector-isolation junction of Q6 becomes forward biased and disrupts the reference.

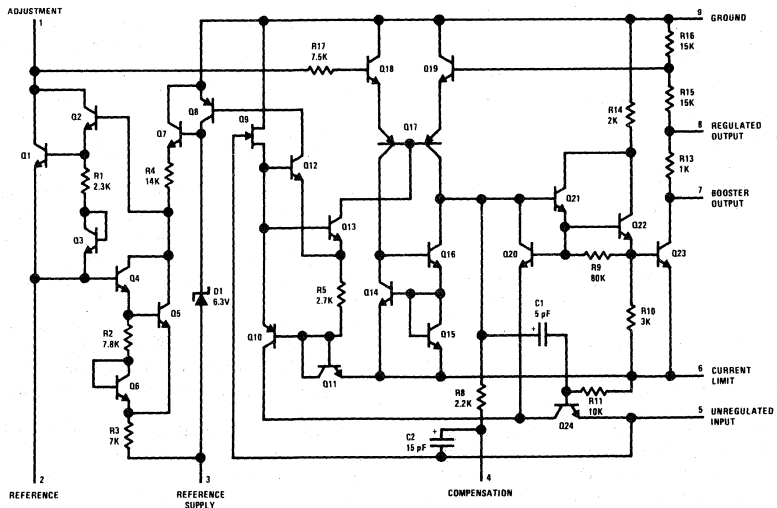The error amplifier of the regulator is quite similar to the LM101 operational amplifier. Emitter



follower input transistors, Q18 and Q19, drive a dual PNP which is operated in the common-base configuration. The current gain of these PNP transistors is fixed at 4 so that the base can be driven by a current source (Q13). Active collector loads are used for the input stage so that a voltage gain of 2000 is obtained. Q21 and Q22 provide enough current gain to keep the internal, series-pass transistor from loading the input stage. R14 limits the base drive on Q23 when it saturates with low, unregulated input voltages. The collector of Q23 is brought out separately so that an external booster transistor can be added for increased output current capability. R13 established the minimum operating current in Q23 when booster transistors are used.

One feature of the error amplifier is that it operates properly with common mode voltages all the way up to ground. Because of this, the circuit will regulate with output voltages to zero volts.

Current limiting is provided by Q24. When the voltage between the current limit and unregulated input terminals becomes large enough to turn on Q24, it will pull Q10 out of saturation and remove base drive from Q21 through Q20. This causes the series pass transistor to exhibit a constant current

characteristic. The pre-load current, provided for Q24 by Q10 before current limiting is initiated, gives a much sharper current-limit characteristic. C1 and R11 are included in the limiting circuitry to suppress oscillations.

The error amplifier is connected to a divider on the output (R15 and R16) to keep the reference current generator from saturating with low input-output voltage differentials. A compensating resistor, R17, which is equal to the equivalent resistance of the divider is included to minimize offset error in the error amplifier.

The major feedback loop is frequency compensated by the brute-force method of rolling off the response with a relatively large capacitor on the output. C2 is included on the integrated circuit to compensate for the effects of series resistance in the output capacitor. A compensation point is also brought out so that more capacitance can be added across C2 for certain regulator configurations. R8 improves the load-transient response, especially when compensation is added on Pin 4.

The purpose of Q9, which is a collector FET, is to bias the current-source transistors, Q12 and Q13. It also supplies the preload current for the current-limit transistor, Q24, through Q10.

## The LM105 — An Improved Positive Regulator

National Semiconductor  
Application Note 23  
January 1969



### INTRODUCTION

IC voltage regulators are seeing rapidly increasing usage. The LM100, one of the first, has already been widely accepted. Designed for versatility, this circuit can be used as a linear regulator, a switching regulator, a shunt regulator, or even a current regulator. The output voltage can be set between 2V and 30V with a pair of external resistors, and it works with unregulated input voltages down to 7V. Dissipation limitations of the IC package restrict the output current to less than 20 mA, but external transistors can be added to obtain output currents in excess of 5A. The LM100 and an extensive description of its use in many practical circuits are described in References 1-3.

One complaint about the LM100 has been that it does not have good enough regulation for certain applications. In addition, it becomes difficult to prove that the load regulation is satisfactory under worst-case design conditions. These problems prompted development of the LM105, which is nearly identical to the LM100 except that a gain stage has been added for improved regulation. In the great majority of applications, the LM105 is a plug-in replacement for the LM100.

### THE IMPROVED REGULATOR

The load regulation of the LM100 is about 0.1%, no load to full load, without current limiting. When short circuit protection is added, the regulation begins to degrade as the output current becomes greater than about half the limiting current. This is illustrated in Figure 1. The LM105, on the other hand, gives 0.1% regulation up to currents closely approaching the short circuit current. As shown in Figure 1b, this is particularly significant at high temperatures.

The current limiting characteristics of a regulator are important for two reasons: First, it is almost mandatory that a regulator be short-circuit protected because the output is distributed to enough

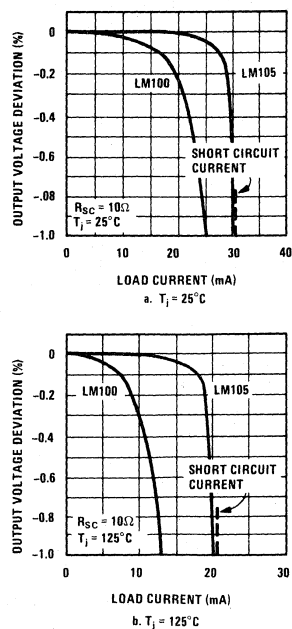


FIGURE 1. Comparison Between the Load Regulation of the LM100 and LM105 for Equal Short Circuit Currents

places that the probability of it becoming shorted is quite high. Secondly, the sharpness of the limiting characteristics is not improved by the addition of external booster transistors. External transistors can increase the maximum output current, but they do not improve the load regulation at currents approaching the short circuit current. Thus, it can be seen that the LM105 provides more than ten times better load regulation in practical power supply designs.

Figure 2 shows that the LM105 also provides better line regulation than the LM100. These curves give the percentage change in output voltage for an incremental change in the unregulated input voltage. They show that the line regulation is worst for small differences between the input and output voltages. The LM105 provides about three times better regulation under worst case conditions. Bypassing the internal reference of the regulator makes the ripple rejection of the LM105 almost a factor of ten better than the LM100 over the entire operating range, as shown in the figure. This bypass capacitor also eliminates noise generated in the internal reference zener of the IC.

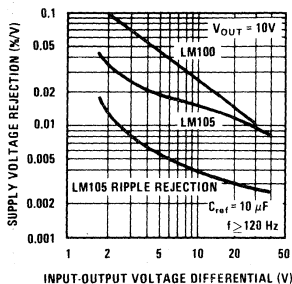


FIGURE 2. Comparison Between the Line Regulation Characteristics of the LM100 and LM105.

The LM105 has also benefited from the use of new IC components developed after the LM100 was designed. These have reduced the internal power consumption so that the LM105 can be specified for input voltages up to 50V and output voltages to 40V. The minimum preload current required by the LM100 is not needed on the LM105.

### CIRCUIT DESCRIPTION

The differences between the LM100 and the LM105 can be seen by comparing the schematic diagrams in Figures 3 and 4. Q4 and Q5 have been added to the LM105 to form a common-collector, common-base, common-emitter amplifier, rather than the single common-emitter differential amplifier on the LM100.

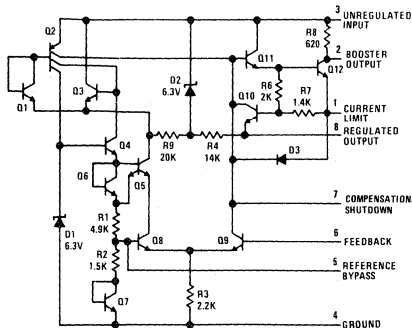


FIGURE 3. Schematic Diagram of the LM100 Regulator.

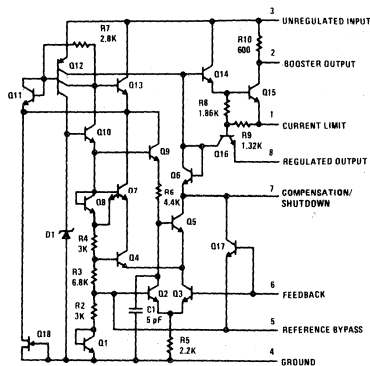


FIGURE 4. Schematic Diagram of the LM105 Regulator.

In the LM100, generation of the reference voltage starts with zener diode, D1, which is supplied with a fixed current from one of the collectors of Q2. This regulated voltage, which has a positive temperature coefficient, is buffered by Q4, divided down by R1 and R2 and connected in series with a diode-connected transistor, Q7. The negative temperature coefficient of Q7 cancels out the positive coefficient of the voltage across R2, producing a temperature-compensated 1.8V on the base of Q8. This point is also brought outside the circuit so that an external capacitor can be added to bypass any noise from the zener diode.

Transistors Q8 and Q9 make up the error amplifier of the circuit. A gain of 2000 is obtained from this single stage by using a current source, another collector on Q2, as a collector load. The output of the amplifier is buffered by Q11 and used to drive the series-pass transistor, Q12. The collector of Q12 is brought out so that an external PNP transistor, or PNP-NPN combination, can be added for increased output current.

Current limiting is provided by Q10. When the voltage across an external resistor connected between Pins 1 and 8 becomes high enough to turn on Q10, it removes the base drive from Q11 so the regulator exhibits a constant-current characteristic. Prebiasing the current limit transistor with a portion of the emitter-base voltage of Q12 from R6 and R7 reduces the current limit sense voltage. This increases the efficiency of the regulator, especially when foldback current limiting is used. With foldback limiting, the voltage dropped across the current sense resistor is about four times larger than the sense voltage.

As for the remaining details, the collector of the amplifier, Q9, is brought out so that external collector-base capacitance can be added to frequency-stabilize the circuit when it is used as a linear regulator. This terminal can also be grounded to shut the regulator off. R9 and R4 are used to start up the regulator, while the rest of the circuitry establishes the proper operating levels for the current source transistor, Q2.

The reference circuitry of the LM105 is the same, except that the current through the reference divider, R2, R3 and R4, has been reduced by a factor of two on the LM105 for reduced power consumption. In the LM105, Q2 and Q3 form an emitter coupled amplifier, with Q3 being the emitter-follower input and Q2 the common-base output amplifier. R6 is the collector load for this stage, which has a voltage gain of about 20. The second stage is a differential amplifier, using Q4 and Q5. Q5 actually provides the gain. Since it has a current source as a collector load, one of the collectors of Q12, the gain is quite high: about 1500. This gives a total gain in the error amplifier of about 30,000, which is ten times higher than the LM100.

It is not obvious from the schematic, but the first stage (Q2 and Q3) and second stage (Q4 and Q5) of the error amplifier are closely balanced when the circuit is operating. This will be true regardless of the absolute value of components and over the operating temperature range. The only thing affecting balance is component matching, which is good in a monolithic integrated circuit, so the error amplifier has good drift characteristics over a wide temperature range.

Frequency compensation is accomplished with an external integrating capacitor around the error amplifier, as with the LM100. This scheme makes the stability insensitive to loading conditions—resistive or reactive—while giving good transient response. However, an internal capacitor, C1, is added to prevent minor-loop oscillations due to the increased gain.

Additional differences between the LM100 and LM105 are that a field-effect transistor, Q18, connected as a current source starts the regulator when power is first applied. Since this current source is connected to ground, rather than the output, the minimum load current before the regulator drops out of operation with large input-output voltage differentials is greatly reduced. This also minimizes power dissipation in the integrated circuit when the difference between the input and output voltage is at the worst-case value. With the LM105 circuit configuration, it was also necessary to add Q17 to eliminate a latch-up mechanism which could exist with lower output-voltage settings. Without Q17, this could occur when Q3 saturated and cut off the second stage amplifiers, Q4 and Q5, causing the output to latch at a voltage nearly equal to the unregulated input.

#### POWER LIMITATIONS

Although it is desirable to put as much of the regulator as possible on the IC chip, there are certain basic limitations. For one, it is not a good idea to put the series pass transistor on the chip. The power that must be dissipated in the pass transistor is too much for practical IC packages. Further, IC's must be rated at a lower maximum operating temperature than power transistors. This means that even with a power package, a more-

massive heat sink would be required if the pass transistor was included in the IC.

Assuming that these problems could be solved, it is still not advisable to put the pass transistor on the same chip with the reference and control circuitry: changes in the unregulated input voltage or load current produce gross variations in chip temperature. These variations worsen load and line regulation due to temperature interaction with the control and reference circuitry.

To elaborate, it is reasonable to neglect the package problem since it is potentially solvable. The lower, maximum operating temperatures of IC's, however, present a more basic problem. The control circuitry in an IC regulator runs at fairly low currents. As a result, it is more sensitive to leakage currents and other phenomena which degrades the performance of semiconductors at high temperatures. Hence, the maximum operating temperature is limited to 150°C in military temperature range applications. On the other hand, a power transistor operating at high currents may be run at temperatures up to 200°C, because even a 1 mA leakage current would not affect its operation in a properly designed circuit. Even if the pass transistor developed a permanent 1 mA leakage from channeling, operating under these conditions of high stress, it would not affect circuit operation. These conditions would not trouble the pass transistor, but they would most certainly cause complete failure of the control circuitry.

These problems are not eliminated in applications with a lower maximum operating temperature. Integrated circuits are sold for limited temperature range applications at considerably lower cost. This is mainly based on a lower maximum junction temperature. They may be rated so that they do not blow up at higher temperatures, but they are not guaranteed to operate within specifications at these temperatures. Therefore, in applications with a lower maximum ambient temperature, it is necessary to purchase an expensive full temperature range part in order to take advantage of the theoretical maximum operating temperatures of the IC.

Figure 5 makes the point about dissipation limitations more strongly. It gives the maximum short circuit output current for an IC regulator in a TO 5 package, assuming a 25°C temperature rise between the chip and ambient and a quiescent current of 2 mA. Dual-in-line or flat packages give results which are, at best, slightly better, but are usually worse. If the short circuit current is not of prime concern, Figure 5 can also be used to give the maximum output current as a function of input-output voltage differential. However, the increased dissipation due to the quiescent current flowing at the maximum input voltage must be taken into account. In addition, the input-output differential must be measured with the maximum expected input voltages.

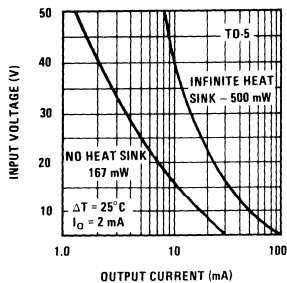


FIGURE 5. Dissipation Limited Short Circuit Output Current for an IC Regulator in a TO-5 Package.

The 25°C temperature rise assumed in arriving at Figure 5 is not at all unreasonable. With military temperature range parts, this is valid for a maximum junction temperature of 150°C with a 125°C ambient. For low cost parts, marketed for limited temperature range applications, this maximum differential appropriately derates the maximum junction temperature.

In practical designs, the maximum permissible dissipation will always be to the left of the curve shown for an infinite heat sink in Figure 5. This curve is realized with the package immersed in circulating acetone, freon or mineral oil. Most heat sinks are not quite as good.

To summarize, power transistors can be run with a temperature differential, junction to ambient, 3 to 5 times as great as an integrated circuit. This means that they can dissipate much more power, even with a smaller heat sink. This, coupled with the fact that low cost, multilead power packages are not available and that there can be thermal interactions between the control circuitry and the pass transistor, strongly suggests that the pass transistors be kept separate from the integrated circuit.

### USING BOOSTER TRANSISTORS

Figure 6 shows how an external pass transistor is added to the LM105. The addition of an external PNP transistor does not increase the minimum input output voltage differential. This would happen if an NPN transistor was used in a compound emitter follower connection with the NPN output transistor of the IC. A single-diffused, wide

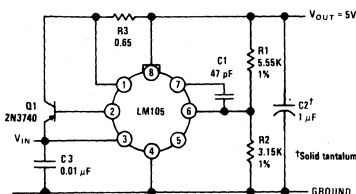


FIGURE 6. 0.2A Regulator.

base transistor like the 2N3740 is recommended because it causes fewer oscillation problems than double-diffused, planar devices. In addition, it seems to be less prone to failure under overload conditions; and low cost devices are available in power packages like the TO-66 or even TO-3.

When the maximum dissipation in the pass transistor is less than about 0.5W, a 2N2905 may be used as a pass transistor. However, it is generally necessary to carefully observe thermal deratings and provide some sort of heat sink.

In the circuit of Figure 6, the output voltage is determined by R1 and R2. The resistor values are selected based on a feedback voltage of 1.8V to Pin 6 of the LM105. To keep thermal drift of the output voltage within specifications, the parallel combination of R1 and R2 should be approximately 2K. However, this resistance is not critical. Variations of ±30% will not cause an appreciable degradation of temperature drift.

The 1 μF output capacitor, C2, is required to suppress oscillations in the feedback loop involving the external booster transistor, Q1, and the output transistor of the LM105. C1 compensates the internal regulator circuitry to make the stability independent for all loading conditions. C3 is not normally required if the lead length between the regulator and the output filter of the rectifier is short.

Current limiting is provided by R3. The current limit resistor should be selected so that the maximum voltage drop across it, at full load current, is equal to the voltage given in Figure 7 at the maximum junction temperature of the IC. This assures a no load to full load regulation better than 0.1% under worst-case conditions.

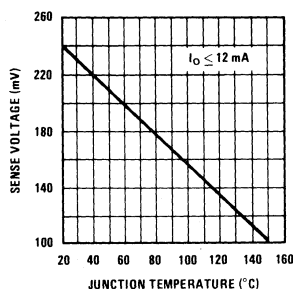


FIGURE 7. Maximum Voltage Drop Across Current Limit Resistor at Full Load for Worst Case Load Regulation of 0.1%.

The short circuit output current is also determined by R3. Figure 8 shows the voltage drop across this resistor, when the output is shorted, as a function of junction temperature in the IC.

With the type of current limiting used in Figure 6, the dissipation under short circuit conditions can be more than three times the worst-case full load dissipation. Hence, the heat sink for the pass tran-

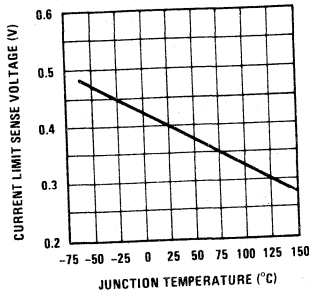


FIGURE 8. Voltage Drop Across Current Limit Resistor Required to Initiate Current Limiting.

sistor must be designed to accommodate the increased dissipation if the regulator is to survive more than momentarily with a shorted output. It is encouraging to note, however, that the short circuit current will decrease at higher ambient temperatures. This assists in protecting the pass transistor from excessive heating.

### FOLDBACK CURRENT LIMITING

With high current regulators, the heat sink for the pass transistor must be made quite large in order to handle the power dissipated under worst-case conditions. Making it more than three times larger to withstand short circuits is sometimes inconvenient in the extreme. This problem can be solved with foldback current limiting, which makes the output current under overload conditions decrease below the full load current as the output voltage is pulled down. The short circuit current can be made but a fraction of the full load current.

A high current regulator using foldback limiting is shown in Figure 9. A second booster transistor, Q1, has been added to provide 2A output current without causing excessive dissipation in the LM105. The resistor across its emitter base junction bleeds off any collector base leakage and establishes a minimum collector current for Q2 to make the circuit easier to stabilize with light loads. The foldback characteristic is produced with R4 and R5. The voltage across R4 bucks out the voltage dropped across the current sense resistor,

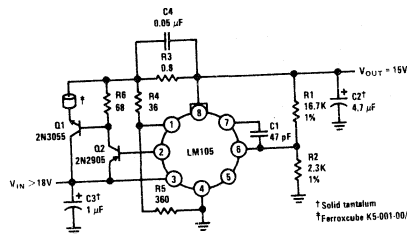


FIGURE 9. 2A Regulator with Foldback Current Limiting.

R3. Therefore, more voltage must be developed across R3 before current limiting is initiated. After the output voltage begins to fall, the bucking voltage is reduced, as it is proportional to the output voltage. With the output shorted, the current is reduced to a value determined by the current limit resistor and the current limit sense voltage of the LM105.

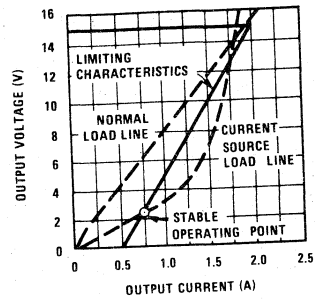


FIGURE 10. Limiting Characteristics of Regulator Using Foldback Current Limiting.

Figure 10 illustrates the limiting characteristics. The circuit regulates for load currents up to 2A. Heavier loads will cause the output voltage to drop, reducing the available current. With a short on the output, the current is only 0.5A.

In design, the value of R3 is determined from

$$R_3 = \frac{V_{lim}}{I_{sc}} \quad (1)$$

where  $V_{lim}$  is the current limit sense voltage of the LM105, given in Figure 8, and  $I_{sc}$  is the design value of short circuit current. R5 is then obtained from

$$R_5 = \frac{V_{OUT} + V_{sense}}{I_{bleed} + I_{bias}} \quad (2)$$

where  $V_{OUT}$  is the regulated output voltage,  $V_{sense}$  is maximum voltage across the current limit resistor for 0.1% regulation as indicated in Figure 7,  $I_{bleed}$  is the preload current on the regulator output provided by R5 and  $I_{bias}$  is the maximum current coming out of Pin 1 of the LM105 under full load conditions.  $I_{bias}$  will be equal to 2 mA plus the worst-case base drive for the PNP booster transistor, Q2.  $I_{bleed}$  should be made about ten times greater than  $I_{bias}$ .

Finally, R4 is given by

$$R_4 = \frac{I_{FL} R_3 - V_{sense}}{I_{bleed}} \quad (3)$$

where  $I_{FL}$  is the output current of the regulator at full load.

It is recommended that a ferrite bead be strung on the emitter of the pass transistor, as shown in Figure 9, to suppress oscillations that may show up with certain physical configurations. It is advisable to also include C4 across the current limit resistor.

In some applications, the power dissipated in Q2 becomes too great for a 2N2905 under worst-case conditions. This can be true even if a heat sink is used, as it should be in almost all applications. When dissipation is a problem, the 2N2905 can be replaced with a 2N3740. With a 2N3740, the ferrite bead and C4 are not needed because this transistor has a lower cutoff frequency.

One of the advantages of foldback limiting is that it sharpens the limiting characteristics of the IC. In addition, the maximum output current is less sensitive to variations in the current limit sense voltage of the IC: in this circuit, a 20% change in sense voltage will only affect the trip current by 5%. The temperature sensitivity of the full load current is likewise reduced by a factor of four, while the short circuit current is not.

Even though the voltage dropped across the sense resistor is larger with foldback limiting, the minimum input-output voltage differential of the complete regulator is not increased above the 3V specified for the LM105 as long as this drop is less than 2V. This can be attributed to the low sense voltage of the IC by itself.

Figure 10 shows that foldback limiting can only be used with certain kinds of loads. When the load looks predominately like a current source, the load line can intersect the foldback characteristic at a point where it will prevent the regulator from coming up to voltage, even without an overload. Fortunately, most solid state circuitry presents a load line which does not intersect. However, the possibility cannot be ignored, and the regulator must be designed with some knowledge of the load.

With foldback limiting, power dissipation in the pass transistor reaches a maximum at some point between full load and short circuited output. This is illustrated in Figure 11. However, if the maximum dissipation is calculated with the worst-case input voltage, as it should be, the power peak is not too high.

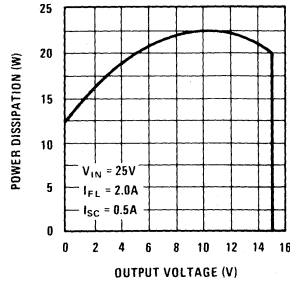


FIGURE 11. Power Dissipation in Series Pass Transistors Under Overload Conditions in Regulator Using Foldback Current Limiting.

### HIGH CURRENT REGULATOR

The output current of a regulator using the LM105 as a control element can be increased to any desired level by adding more booster transistors, increasing the effective current gain of the pass transistors. A circuit for a 10A regulator is shown in Figure 12. A third NPN transistor has been included to get higher current. A low frequency device is used for Q3 because it seems to better withstand abuse. However, high frequency transistors must be used to drive it. Q2 and Q3 are both double-diffused transistors with good frequency response. This insures that Q3 will present the dominant lag in the feedback loop through the booster transistors, and back around the output transistor of the LM105. This is further insured by the addition of C3.

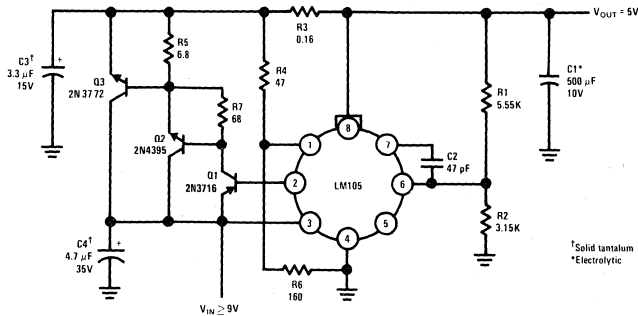


FIGURE 12. 10A Regulator with Foldback Current Limiting.



The circuit, as shown, has a full load capability of 10A. Foldback limiting is used to give a short circuit output current of 2.5A. The addition of Q3 increases the minimum input-output voltage differential, by 1V, to 4V.

### DOMINANT FAILURE MECHANISMS

By far, the biggest reason for regulator failures is overdissipation in the series pass transistors. This has been borne out by experience with the LM100. Excessive heating in the pass transistors causes them to short out, destroying the IC. This has happened most frequently when PNP booster transistors in a TO-5 can, like the 2N2905, were used. Even with a good heat sink, these transistors cannot dissipate much more than 1W. The maximum dissipation is less in many applications. When a single PNP booster is used and power can be a problem, it is best to go to a transistor like the 2N3740, in a TO-66 power package, using a good heat sink.

Using a compound PNP/NPN booster does not solve all problems. Even when breadboarding with transistors in TO-3 power packages, heat sinks must be used. The TO-3 package is not very good, thermally, without a heat sink. Dissipation in the PNP transistor driving the NPN series pass transistor cannot be ignored either. Dissipation in the driver with worst-case current gain in the pass transistor must be taken into account. In certain cases, this could require that a PNP transistor in a power package be used to drive the NPN pass transistor. In almost all cases, a heat sink is required if a PNP driver transistor in a TO-5 package is selected.

With output currents above 3A, it is good practice to replace a 2N3055 pass transistor with a 2N3772. The 2N3055 is rated for higher currents than 3A, but its current gain falls off rapidly. This is especially true at either high temperatures or low input-output voltage differentials. A 2N3772 will give substantially better performance at high currents, and it makes life much easier for the PNP driver.

The second biggest cause of failures has been the output filter capacitors on power inverters providing unregulated power to the regulator. If these capacitors are operated with excessive ripple across them, and simultaneously near their maximum dc voltage rating, they will sputter. That is, they short momentarily and clear themselves. When they short, the output capacitor of the regulator is discharged back through the reverse biased pass transistors or the control circuitry, frequently causing destruction. This phenomenon is especially prevalent when solid tantalum capacitors are used with high-frequency power inverters. The maximum ripple allowed on these capacitors decreases linearly with frequency.

The solution to this problem is to use capacitors with conservative voltage ratings. In addition, the maximum ripple allowed by the manufacturer at the operating frequency should also be observed.

The problem can be eliminated completely by installing a diode between the input and output of the regulator such that the capacitor on the output is discharged through this diode if the input is shorted. A fast switching diode should be used as ordinary rectifier diodes are not always effective.

Another cause of problems with regulators is severe voltage transients on the unregulated input. Even if these transients do not cause immediate failure in the regulator, they can feed through and destroy the load. If the load shorts out, as is frequently the case, the regulator can be destroyed by subsequent transients.

This problem can be solved by specifying all parts of the regulator to withstand the transient conditions. However, when ultimate reliability is needed, this is not a good solution. Especially since the regulator can withstand the transient, yet severely overstress the circuitry on its output by feeding the transients through. Hence, a more logical recourse is to include circuitry which suppresses the transients. A method of doing this is shown in Figure 13. A zener diode, which can handle

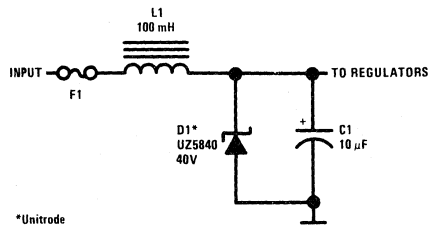


FIGURE 13. Suppression Circuitry to Remove Large Voltage Spikes from Unregulated Supplies.

large peak currents, clamps the input voltage to the regulator while an inductor limits the current through the zener during the transient. The size of the inductor is determined from

$$L = \frac{\Delta V \Delta t}{I} \quad (4)$$

where  $\Delta V$  is the voltage by which the input transient exceeds the breakdown voltage of the diode,  $\Delta t$  is the duration of the transient and  $I$  is the peak current the zener can handle while still clamping the input voltage to the regulator. As shown, the suppression circuit will clamp 70V, 4 ms transients on the unregulated supply.

### CONCLUSIONS

The LM105 is an exact replacement for the LM100 in the majority of applications, providing about ten times better regulation. There are, however, a few differences:

In switching regulator applications,<sup>2</sup> the size of the resistor used to provide positive feedback should be doubled as the impedance seen looking

back into the reference bypass terminal is twice that of the LM100 ( $2\text{ K}\Omega$  versus  $1\text{ K}\Omega$ ). In addition, the minimum output voltage of the LM105 is 4.5V, compared with 2V for the LM100. In low voltage regulator applications, the effect of this is obvious. However, it also imposes some limitations on current regulator and shunt regulator designs.<sup>3</sup> Lastly, clamping the compensation terminal (Pin 7) within a diode drop of ground or the output terminal will not guarantee that the regulator is shut off, as it will with the LM100. This restricts the LM105 in the overload shutoff schemes<sup>3</sup> which can be used with the LM100.

Dissipation limitations of practical packages dictate that the output current of an IC regulator be less than 20 mA. However, external booster transistors can be added to get any output current desired. Even with satisfactory packages, considerably larger heat sinks would be needed if the pass transistors were put on the same chip as the reference and control circuitry, because an IC must be run at a lower maximum temperature than a power transistor. In addition, heat dissipated in the pass transistor couples into the low level circuitry and degrades performance. All this suggests that the pass transistor be kept separate from the IC.

Overstressing series pass transistors has been the biggest cause of failures with IC regulators. This not only applies to the transistors within the IC, but also to the external booster transistors. Hence, in designing a regulator, it is of utmost importance to determine the worst-case power dissipation in

all the driver and pass transistors. Devices must then be selected which can handle the power. Further, adequate heat sinks must be provided as even power transistors cannot dissipate much power by themselves.

Normally, the highest power dissipation occurs when the output of the regulator is shorted. If this condition requires heat sinks which are so large as to be impractical, foldback current limiting can be used. With foldback limiting, the power dissipated under short circuit conditions can actually be made less than the dissipation at full load.

The LM105 is designed primarily as a positive voltage regulator. A negative regulator, the LM104, which is a functional complement to the LM105, is described in Reference 4.

#### REFERENCES

1. R. J. Widlar, "A Versatile, Monolithic Voltage Regulator," National Semiconductor AN-1, February, 1967.
2. R. J. Widlar, "Designing Switching Regulators," National Semiconductor AN-2, April, 1967.
3. R. J. Widlar, "New Uses for the LM100 Regulator," National Semiconductor AN-8, June, 1968.
4. R. J. Widlar, "Designs for Negative Voltage Regulators," National Semiconductor AN-21, October, 1968.

# A Simplified Test Set for Op Amp Characterization

National Semiconductor  
Application Note 24  
M. Yamatake  
June 1969



## INTRODUCTION

The test set described in this paper allows complete quantitative characterization of all dc operational amplifier parameters quickly and with a minimum of additional equipment. The method used is accurate and is equally suitable for laboratory or production test—for quantitative readout or for limit testing. As embodied here, the test set is conditioned for testing the LM709 and LM101 amplifiers; however, simple changes discussed in the text will allow testing of any of the generally available operational amplifiers.

Amplifier parameters are tested over the full range of common mode and power supply voltages with either of two output loads. Test set sensitivity and stability are adequate for testing all presently available integrated amplifiers.

The paper will be divided into two sections, i.e., a functional description, and a discussion of circuit operation. Complete construction information will be given including a layout for the tester circuit boards.

## FUNCTIONAL DESCRIPTION

The test set operates in one of three basic modes. These are: (1) Bias Current Test; (2) Offset Voltage, Offset Current Test; and (3) Transfer

Function Test. In the first two of these tests, the amplifier under test is exercised throughout its full common mode range. In all three tests, power supply voltages for the circuit under test may be set at  $\pm 5V$ ,  $\pm 10V$ ,  $\pm 15V$  or  $\pm 20V$ .

## POWER SUPPLY

Basic waveforms and dc operating voltages for the test set are derived from a power supply section comprising a positive and a negative rectifier and filter, a test set voltage regulator, a test circuit voltage regulator, and a function generator. The dc supplies will be discussed in the section dealing with detailed circuit description.

The waveform generator provides three output functions, a  $\pm 19V$  square wave, a  $-19V$  to  $+19V$  pulse with a 1% duty cycle, and a  $\pm 5V$  triangular wave. The square wave is the basic waveform from which both the pulse and triangular wave outputs are derived.

The square wave generator is an operational amplifier connected as an astable multivibrator. This amplifier provides an output of approximately  $\pm 19V$  at 16 Hz. This square wave is used to drive junction FET switches in the test set and to generate the pulse and triangular waveforms.

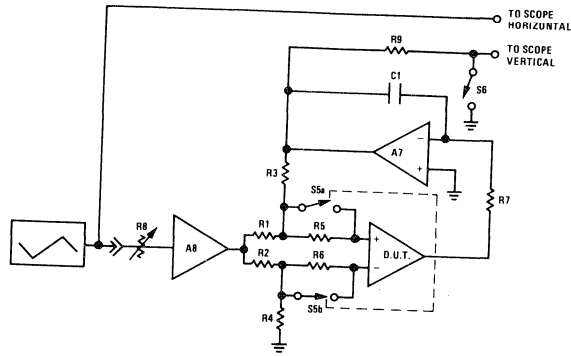


FIGURE 1. Functional Diagram of Bias Current Circuit

The pulse generator is a monostable multivibrator driven by the output of the square wave generator. This multivibrator is allowed to swing from negative saturation to positive saturation on the positive going edge of the square wave input and has a time constant which will provide a duty cycle of approximately 1%. The output is approximately  $-19V$  to  $+19V$ .

The triangular wave generator is a dc stabilized integrator driven by the output of the square wave generator and provides a  $\pm 5V$  output at the square wave frequency, inverted with respect to the square wave.

The purpose of these various outputs from the power supply section will be discussed in the functional description.

### BIAS CURRENT TEST

A functional diagram of the bias current test circuit is shown in Figure 1. The output of the triangular wave generator and the output of the test circuit, respectively, drive the horizontal and vertical deflection of an oscilloscope.


The device under test, (cascaded with the integrator, A7), is connected in a differential amplifier

configuration by  $R_1$ ,  $R_2$ ,  $R_3$ , and  $R_4$ . The inputs of this differential amplifier are driven in common from the output of the triangular wave generator through attenuator  $R_8$  and amplifier  $A_8$ . The inputs of the device under test are connected to the feedback network through resistors  $R_5$  and  $R_6$ , shunted by the switch  $S_{5a}$  and  $S_{5b}$ .

The feedback network provides a closed loop gain of 1,000 and the integrator time constant serves to reduce noise at the output of the test circuit as well as allowing the output of the device under test to remain near zero volts.

The bias current test is accomplished by allowing the device under test to draw input current to one of its inputs through the corresponding input resistor on positive going or negative going halves of the triangular wave generator output. This is accomplished by closing  $S_{5a}$  or  $S_{5b}$  on alternate halves of the triangular wave input. The voltage appearing across the input resistor is equal to input current times the input resistor. This voltage is multiplied by 1,000 by the feedback loop and appears at the integrator output and the vertical input of the oscilloscope. The vertical separation of the traces representing the two input currents of the amplifier under test is equivalent to the total bias current of the amplifier under test.

The bias current over the entire common mode range may be examined by setting the output of  $A_8$  equal to the amplifier common mode range. A photograph of the bias current oscilloscope display is given as Figure 2. In this figure, the total input

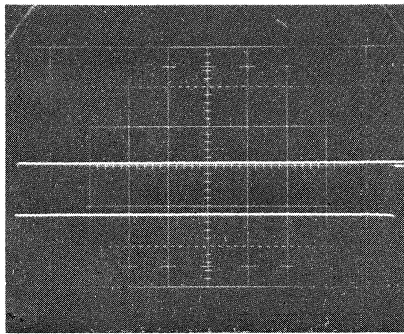

**FIGURE 2. Bias Current and Common Mode Rejection Display**

current of an amplifier is displayed over a  $\pm 10V$  common mode range with a sensitivity of 100 nA per vertical division.

The bias current display of Figure 2 has the added advantage that incipient breakdown of the input stage of the device under test at the extremes of the common mode range is easily detected.

If either or both the upper or lower trace in the bias current display exhibits curvature near the horizontal ends of the oscilloscope face, then the bias current of that input of the amplifier is shown to be dependent on common mode voltage. The usual causes of this dependency are low breakdown voltage of the differential input stage or current sink.

#### OFFSET VOLTAGE, OFFSET CURRENT TEST


The offset voltage and offset current tests are performed in the same general way as the bias

current test. The only difference is that the switches  $S_{5a}$  and  $S_{5b}$  are closed on the same half-cycle of the triangular wave input.

The synchronous operation of  $S_{5a}$  and  $S_{5b}$  forces the amplifier under test to draw its input currents through matched high and low input resistors on alternate halves of the input triangular wave. The difference between the voltage drop across the two values of input resistors is proportional to the difference in input current to the two inputs of the amplifier under test and may be measured as the vertical spacing between the two traces appearing on the face of the oscilloscope.

Offset voltage is measured as the vertical spacing between the trace corresponding to one of the two values of source resistance and the zero volt baseline. Switch  $S_6$  and Resistor  $R_9$  are a base line chopper whose purpose is to provide a baseline reference which is independent of test set and oscilloscope drift.  $S_6$  is driven from the pulse output of the function generator and has a duty cycle of approximately 1% of the triangular wave.

Figure 3 is a photograph of the various waveforms presented during this test. Offset voltage and offset current are displayed at a sensitivity of 1 mV and 100 nA per division, respectively, and both parameters are displayed over a common mode range of  $\pm 10V$ .

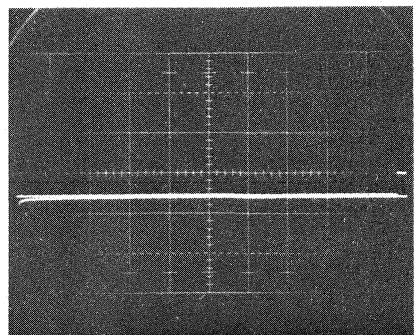

**FIGURE 3. Offset Voltage, Offset Current and Common Mode Rejection Display**

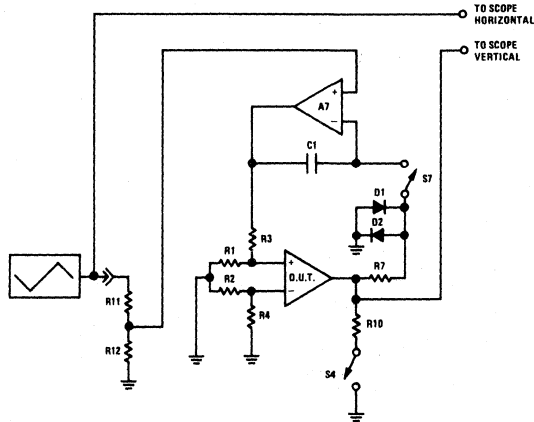


FIGURE 4. Functional Diagram of Transfer Function Circuit

### TRANSFER FUNCTION TEST

A functional diagram of the transfer function test is shown in Figure 4. The output of the triangular wave generator and the output of the circuit under test, respectively, drive the horizontal and vertical inputs of an oscilloscope.

The device under test is driven by a  $\pm 2.5$  mV triangular wave derived from the  $\pm 5$  V output of the triangular wave generator through the attenuators  $R_{11}$ ,  $R_{12}$ , and  $R_1$ ,  $R_3$  and through the voltage follower,  $A_7$ . The output of the device under test is fed to the vertical input of an oscilloscope.

Amplifier  $A_7$  performs a dual function in this test. When  $S_7$  is closed during the bias current test, a voltage is developed across  $C_1$  equal to the amplifier offset voltage multiplied by the gain of the feedback loop. When  $S_7$  is opened in the transfer function test, the charge stored in  $C_1$  continues to provide this offset correction voltage. In addition,  $A_7$  sums the triangular wave test signal with the offset correction voltage and applies this sum to the input of the amplifier under test through the attenuator  $R_1$ ,  $R_3$ . This input sweeps the input of the amplifier under test  $\pm 2.5$  mV around its offset voltage.

Figure 5 is a photograph of the output of the test set during the transfer function test. This figure illustrates the function of amplifier  $A_7$  in adjusting the dc input of the test device so that its transfer function is displayed on the center of the oscilloscope face.

The transfer function display is a plot of  $V_{in}$  vs  $V_{out}$  for an amplifier. This display provides information about three amplifier parameters: gain,

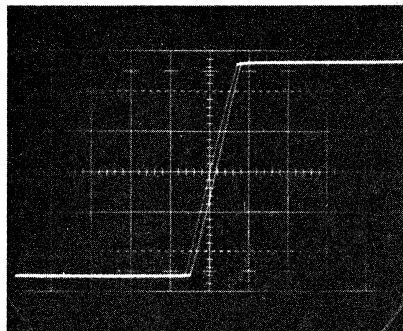


FIGURE 5. Transfer Function Display

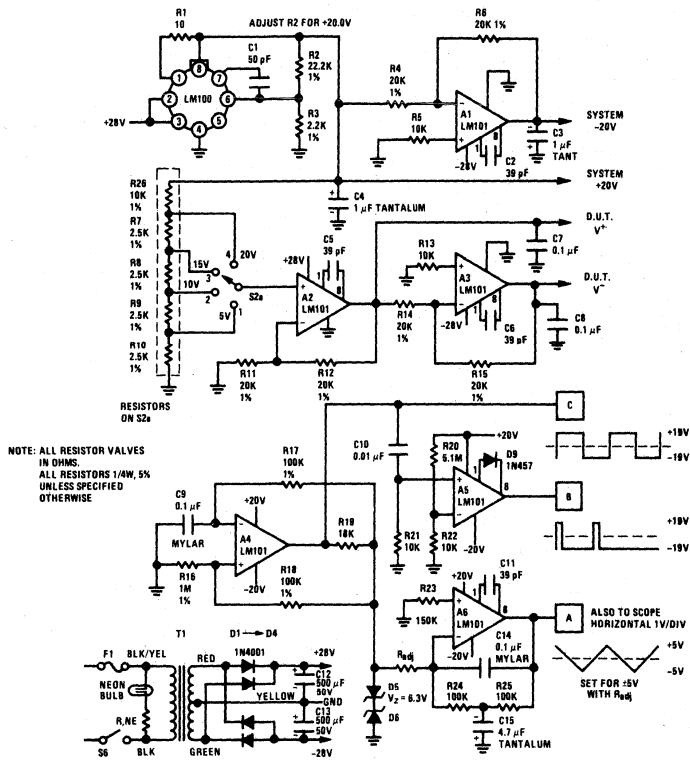


FIGURE 6. Power Supply and Function Generator

gain linearity, and output swing. Gain is displayed as the slope,  $\Delta V_{out}/\Delta V_{in}$  of the transfer function. Gain linearity is indicated change in slope of the  $V_{out}/V_{in}$  display as a function of output voltage. This display is particularly useful in detecting crossover distortion in a Class B output stage. Output swing is measured as the vertical deflection of the transfer function at the horizontal extremes of the display.

## DETAILED CIRCUIT DESCRIPTION

### POWER SUPPLIES

As shown in Figure 6, which is a complete schematic of the power supply and function generator,

two power supplies are provided in the test set. One supply provides a fixed  $\pm 20V$  to power the circuitry in the test set; the other provides  $\pm 5V$  to  $\pm 20V$  to power the circuit under test.

The test set power supply regulator accepts +28V from the positive rectifier and filter and provides +20V through the LM100 positive regulator. Amplifier A<sub>1</sub> is powered from the negative rectifier and filter and operates as a unity gain inverter whose input is +20V from the positive regulator, and whose output is -20V.

The test circuit power supply is referenced to the +20V output of the positive regulator through the

variable divider comprising  $R_7$ ,  $R_8$ ,  $R_9$ ,  $R_{10}$ , and  $R_{26}$ . The output of this divider is  $+10V$  to  $+2.5V$  according to the position of  $S_{2a}$  and is fed to the non-inverting, gain-of-two amplifier,  $A_2$ .  $A_2$  is powered from  $+28V$  and provides  $+20V$  to  $+5V$  at its output.  $A_3$  is a unity gain inverter whose input is the output of  $A_2$  and which is powered from  $-28V$ . The complementary outputs of amplifiers  $A_2$  and  $A_3$  provide dc power to the circuit under test.

LM101 amplifiers are used as  $A_2$  and  $A_3$  to allow operation from one ground referenced voltage each and to provide protective current limiting for the device under test.

### FUNCTION GENERATOR

The function generator provides three outputs, a  $\pm 19V$  square wave, a  $-19V$  to  $+19V$  pulse having a 1% duty cycle, and a  $\pm 5V$  triangular wave. The square wave is the basic function from which the pulse and triangular wave are derived, the pulse is referenced to the leading edge of the square wave, and the triangular wave is the inverted and integrated square wave.

Amplifier  $A_4$  is an astable multivibrator generating a square wave from positive to negative saturation. The amplitude of this square wave is approximately  $\pm 19V$ . The square wave frequency is determined by the ratio of  $R_{18}$  to  $R_{16}$  and by the time constant,  $R_{17}C_9$ . The operating frequency is stabilized against temperature and power regulation effects by regulating the feedback signal with the divider  $R_{19}$ ,  $D_5$  and  $D_6$ .

Amplifier  $A_5$  is a monostable multivibrator triggered by the positive going output of  $A_4$ . The pulse width of  $A_5$  is determined by the ratio of  $R_{20}$  to  $R_{22}$  and by the time constant  $R_{21}C_{10}$ . The output pulse of  $A_5$  is an approximately 1% duty cycle pulse from approximately  $-19V$  to  $+19V$ .

Amplifier  $A_6$  is a dc stabilized integrator driven from the amplitude-regulated output of  $A_4$ . Its output is a  $\pm 5V$  triangular wave. The amplitude of the output of  $A_6$  is determined by the square wave voltage developed across  $D_5$  and  $D_6$  and the time constant  $R_{adj}C_{14}$ . DC stabilization is accomplished by the feedback network  $R_{24}$ ,  $R_{25}$ , and  $C_{15}$ . The ac attenuation of this feedback network

is high enough so that the integrator action at the square wave frequency is not degraded.

Operating frequency of the function generator may be varied by adjusting the time constants associated with  $A_4$ ,  $A_5$ , and  $A_6$  in the same ratio.

### TEST CIRCUIT

A complete schematic diagram of the test circuit is shown in Figure 7. The test circuit accepts the outputs of the power supplies and function generator and provides horizontal and vertical outputs for an X-Y oscilloscope, which is used as the measurement system.

The primary elements of the test circuit are the feedback buffer and integrator, comprising amplifier  $A_7$  and its feedback network  $C_{16}$ ,  $R_{31}$ ,  $R_{32}$ , and  $C_{17}$ , and the differential amplifier network, comprising the device under test and the feedback network  $R_{40}$ ,  $R_{43}$ ,  $R_{44}$ , and  $R_{52}$ . The remainder of the test circuit provides the proper conditioning for the device under test and scaling for the oscilloscope, on which the test results are displayed.

The amplifier  $A_3$  provides a variable amplitude source of common mode signal to exercise the amplifier under test over its common mode range. This amplifier is connected as a non-inverting gain-of-3.6 amplifier and receives its input from the triangular wave generator. Potentiometer  $R_{37}$  allows the output of this amplifier to be varied from  $\pm 0$  volts to  $\pm 18$  volts. The output of this amplifier drives the differential input resistors,  $R_{43}$  and  $R_{44}$ , for the device under test.

The resistors  $R_{46}$  and  $R_{47}$  are current sensing resistors which sense the input current of the device under test. These resistors are switched into the circuit in the proper sequence by the field effect transistors  $Q_6$  and  $Q_7$ .  $Q_6$  and  $Q_7$  are driven from the square wave output of the function generator by the PNP pair,  $Q_{10}$  and  $Q_{11}$ , and the NPN pair,  $Q_8$  and  $Q_9$ . Switch sections  $S_{1b}$  and  $S_{1c}$  select the switching sequence for  $Q_8$  and  $Q_9$  and hence for  $Q_6$  and  $Q_7$ . In the bias current test, the FET drivers,  $Q_8$  and  $Q_9$ , are switched by out of phase signals from  $Q_{10}$  and  $Q_{11}$ . This opens the FET switches  $Q_6$  and  $Q_7$  on alternate half cycles of the square wave output of the function generator. During the offset voltage, offset current test, the FET drivers are operated synchronously



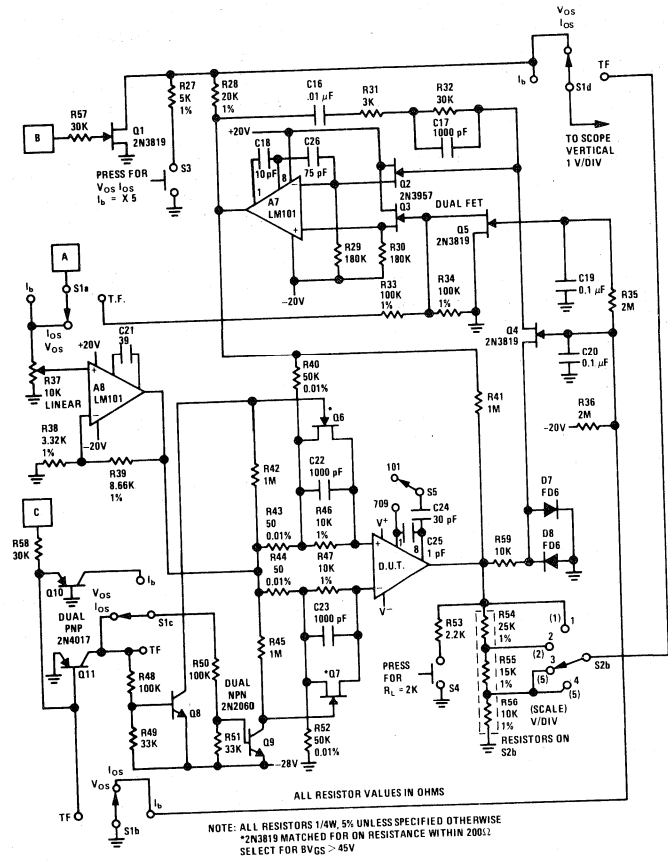


FIGURE 7. Test Circuit

from the output of Q<sub>11</sub>. During the transfer function test, Q<sub>6</sub> and Q<sub>7</sub> are switched on continuously by turning off Q<sub>11</sub>. R<sub>42</sub> and R<sub>45</sub> maintain the gates of the FET switches at zero gate to source voltage for maximum conductance during their on cycle. Since the sources of these switches are at the common mode input voltage of the device under test, these resistors are connected to the output of the common mode driver amplifier, A<sub>8</sub>.

The input for the integrator-feedback buffer, A<sub>7</sub>, is selected by the FET switches Q<sub>4</sub> and Q<sub>5</sub>. During the bias current and offset voltage offset current tests, A<sub>7</sub> is connected as an integrator and receives its input from the output of the device under test. The output of A<sub>7</sub> drives the feedback resistor, R<sub>40</sub>. In this connection, the integrator holds the output of the device under test near ground and serves to amplify the voltages corresponding to

bias current, offset current, and offset voltage by a factor of 1,000 before presenting them to the measurement system. FET switches  $Q_4$  and  $Q_5$  are turned on by switch section  $S_{1b}$  during these tests.

FET switches  $Q_4$  and  $Q_5$  are turned off during the transfer function test. This disconnects  $A_7$  from the output of the device under test and changes it from an integrator to a non-inverting unity gain amplifier driven from the triangular wave output of the function generator through the attenuator  $R_{33}$  and  $R_{34}$  and switch section  $S_{1a}$ . In this connection, amplifier  $A_7$  serves two functions; first, to provide an offset voltage correction to the input of the device under test and, second, to drive the input of the device under test with a  $\pm 2.5$  mV triangular wave centered about the offset voltage. During this test, the common mode driver amplifier is disabled by switch section  $S_{1a}$  and the vertical input of the measurement oscilloscope is transferred from the output of the integrator-buffer,  $A_7$ , to the output of the device under test by switch section  $S_{1d}$ .  $S_{2a}$  allows supply voltages for the device under test to be set at  $\pm 5$ ,  $\pm 10$ ,  $\pm 15$ , or  $\pm 20$  V.  $S_{2b}$  changes the vertical scale factor for the measurement oscilloscope to maintain optimum vertical deflection for the particular power supply voltage used.  $S_4$  is a momentary contact pushbutton switch which is used to change the load on the device under test from  $10k\Omega$  to  $2k\Omega$ .

A delay must be provided when switching from the input tests to the transfer function tests. The purpose of this delay is to disable the integrator function of  $A_7$  before driving it with the triangular wave. If this is not done, the offset correction voltage, stored on  $C_{16}$ , will be lost. This delay between opening FET switch  $Q_4$ , and switch  $Q_5$ , is provided by the RC filter,  $R_{35}$  and  $C_{19}$ .

Resistor  $R_{41}$  and diodes  $D_7$  and  $D_8$  are provided to control the integrator when no test device is present, or when a faulty test device is inserted.  $R_{41}$  provides a dc feedback path in the absence of a test device and resets the integrator to zero. Diodes  $D_7$  and  $D_8$  clamp the input to the integrator to approximately  $\pm 7$  volts when a faulty device is inserted.

FET switch  $Q_1$  and resistor  $R_{28}$  provide a ground reference at the beginning of the 50-ohm-source, offset-voltage trace. This trace provides a ground

reference which is independent of instrument or oscilloscope calibration. The gate of  $Q_1$  is driven by the output of monostable multivibrator  $A_5$ , and shorts the vertical oscilloscope drive signal to ground during the time that  $A_5$  output is positive.

Switch  $S_3$ ,  $R_{27}$ , and  $R_{28}$  provide a 5X scale increase during input parameter tests to allow measurement of amplifiers with large offset voltage, offset current, or bias current.

Switch  $S_5$  allows amplifier compensation to be changed for 101 or 709 type amplifiers.

## CALIBRATION

Calibration of the test system is relatively simple and requires only two adjustments. First, the output of the main regulator is set up for 20V. Then, the triangular wave generator is adjusted to provide  $\pm 5$  V output by selecting  $R_{adj}$ . This sets the horizontal sweep for the X-Y oscilloscope used as the measurement system. The oscilloscope is then set up for 1V/division vertical and for a full 10 division horizontal sweep.

Scale factors for the three test positions are:

### 1. Bias Current Display (Figure 2)

$I_{bias}$ total	100 nA/div. vertical
Common Mode Voltage	Variable horizontal

### 2. Offset Voltage-Offset Current (Figure 3)

$I_{offset}$	100 nA/div. vertical
$V_{offset}$	1 mV/div. vertical
Common Mode Voltage	Variable horizontal

### 3. Transfer Function (Figure 5)

$V_{in}$	0.5 mV/div.
$V_{out}$	5V/div. @ $V_s \pm 20$ V
	5V/div. @ $V_s \pm 15$ V
	2V/div. @ $V_s \pm 10$ V
	1V/div. @ $V_s \pm 5$ V

$$\text{Gain} = \frac{\Delta V_{out}}{\Delta V_{in}}$$

## CONSTRUCTION

Test set construction is simplified through the use of integrated circuits and etched circuit layout.

Figure 8 gives photographs of the completed tester. Figure 9 shows the parts location for the components on the circuit board layout of Figure 10. An attempt should be made to adhere to

this layout to insure that parasitic coupling between elements will not cause oscillations or give calibration problems.

Table 1 is a listing of special components which are needed to fit the physical layout given for the tester.

TABLE 1. Partial Parts List

T <sub>1</sub>	Triad F-90X
S <sub>1</sub>	Centralab PA2003 non-shorting
S <sub>2</sub>	Centralab PA2015 non-shorting

S<sub>3</sub>, S<sub>4</sub> Grayhill 30-1 Series 30 subminiature pushbutton switch

S<sub>5</sub>, S<sub>6</sub> Alcoswitch MST-105D SPDT

### CONCLUSIONS

A semi-automatic test system has been described which will completely test the important operational amplifier parameters over the full power supply and common mode ranges. The system is simple, inexpensive, easily calibrated, and is equally suitable for engineering or quality assurance usage.

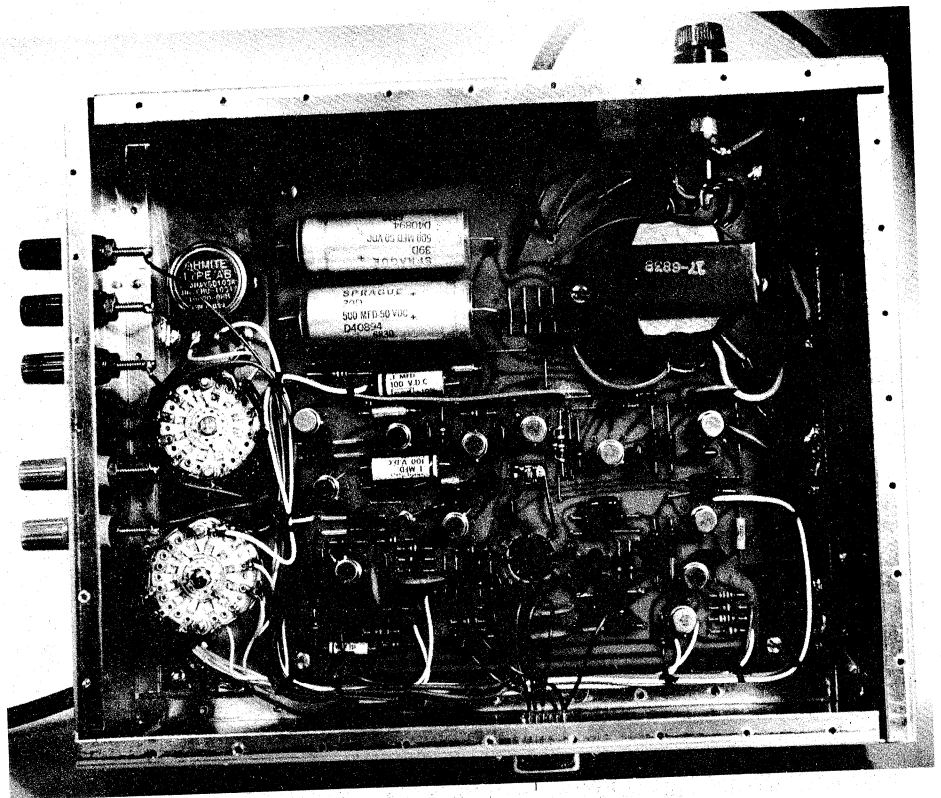


FIGURE 8a. Bottom of Test Set

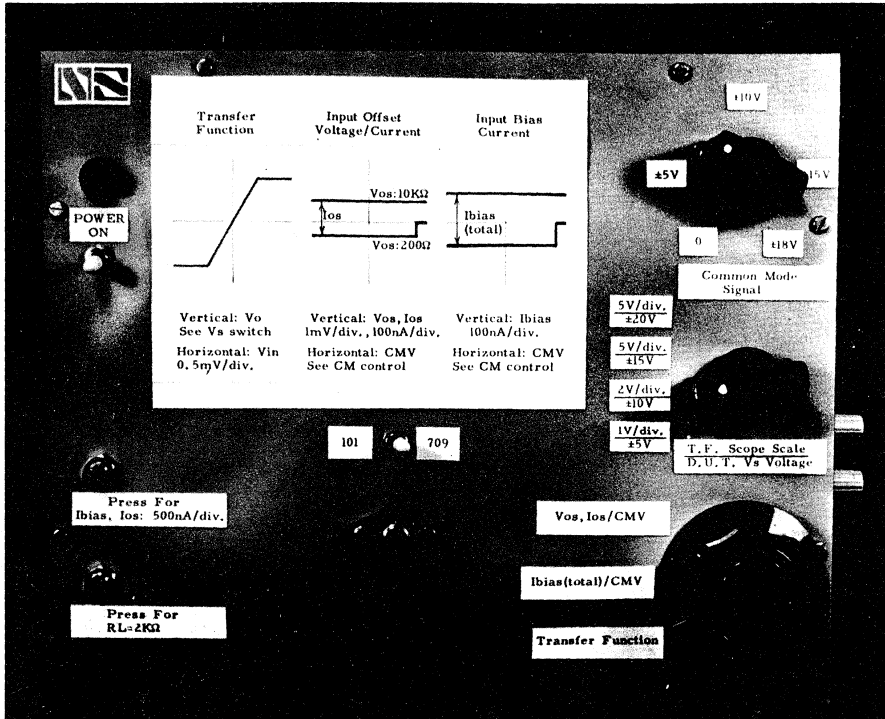


FIGURE 8b. Front Panel

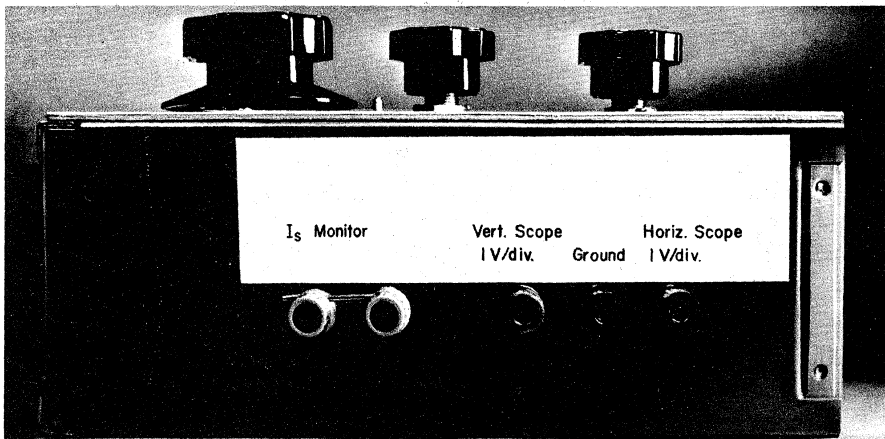


FIGURE 8c. Jacks

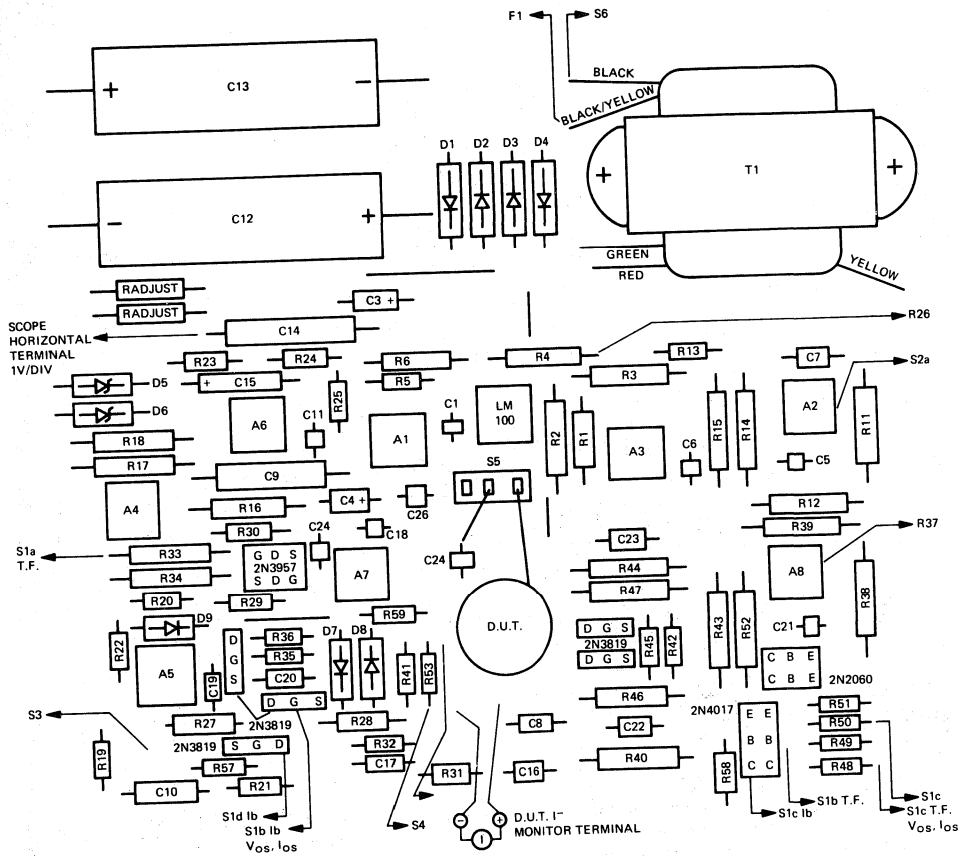


FIGURE 9. Component Location, Top View

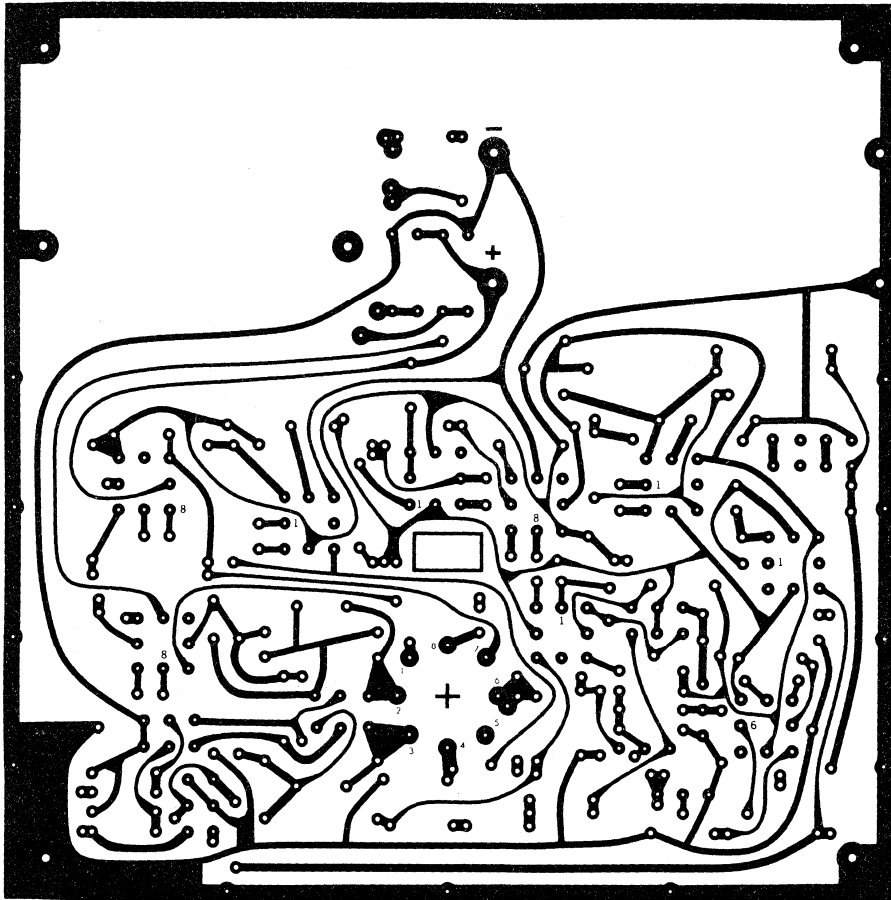


FIGURE 10. Circuit Board Layout

# IC Op Amp Beats FETs on Input Current

National Semiconductor  
Application Note 29  
December 1969



## ABSTRACT

A monolithic operational amplifier having input error currents in the order of 100 pA over a  $-55^{\circ}\text{C}$  to  $125^{\circ}\text{C}$  temperature range is described. Instead of FETs, the circuit uses bipolar transistors with current gains of 5000 so that offset voltage and drift are not degraded. A power consumption of 1 mW at low voltage is also featured.

A number of novel circuits that make use of the low current characteristics of the amplifier are given. Further, special design techniques required to take advantage of these low currents are explored. Component selection and the treatment of printed circuit boards is also covered.

## INTRODUCTION

A year ago, one of the loudest complaints heard about IC op amps was that their input currents were too high. This is no longer the case. Today ICs can provide the ultimate in performance for many applications—even surpassing FET amplifiers.

FET input stages have long been considered the best way to get low input currents in an op amp. Low-picoamp input currents can in fact be obtained at room temperature. However, this current, which is the leakage current of the gate junction, doubles every  $10^{\circ}\text{C}$ , so performance is severely degraded at high temperatures. Another disadvantage is that it is difficult to match FETs closely.<sup>1</sup> Unless expensive selection and trimming techniques are used, typical offset voltages of 50 mV and drifts of  $50\ \mu\text{V}/^{\circ}\text{C}$  must be tolerated.

Super gain transistors<sup>2</sup> are now challenging FETs. These devices are standard bipolar transistors which have been diffused for extremely high current gains. Typically, current gains of 5000 can be obtained at  $1\ \mu\text{A}$  collector currents. This makes it possible to get input currents which are competitive with FETs. It is also possible to operate these transistors at zero collector base voltage, eliminating the leakage currents that plague the FET. Hence they can provide lower error currents at elevated temperatures. As a bonus, super gain

transistors match much better than FETs with typical offset voltages of 1 mV and drifts of  $3\ \mu\text{V}/^{\circ}\text{C}$ .

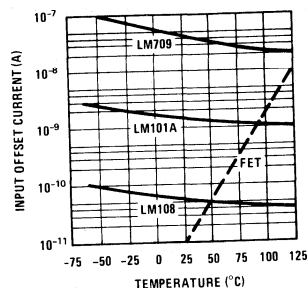


FIGURE 1. Comparing IC Op Amps With FET-Input Amplifier

Figure 1 compares the typical input offset currents of IC op amps and FET amplifiers. Although FETs give superior performance at room temperature, their advantage is rapidly lost as temperature increases. Still, they are clearly better than early IC amplifiers like the LM709.<sup>3</sup> Improved devices, like the LM101A,<sup>4</sup> equal FET performance over a  $-55^{\circ}\text{C}$  to  $125^{\circ}\text{C}$  temperature range. Yet they use standard transistors in the input stage. Super gain transistors can provide more than an order of magnitude improvement over the LM101A. The LM108 uses these to equal FET performance over a  $0^{\circ}\text{C}$  to  $70^{\circ}\text{C}$  temperature range.

In applications involving  $125^{\circ}\text{C}$  operation, the LM108 is about two orders of magnitude better than FETs. In fact, unless special precautions are taken, overall circuit performance is often limited by leakages in capacitors, diodes, analog switches or printed circuit boards, rather than by the op amp itself.

## EFFECTS OF ERROR CURRENT

In an operational amplifier, the input current produces a voltage drop across the source resis-

tance, causing a dc error. This effect can be minimized by operating the amplifier with equal resistances on the two inputs.<sup>5</sup> The error is then proportional to the difference in the two input currents, or the offset current. Since the current gains of monolithic transistors tend to match well, the offset current is typically a factor of ten less than the input currents.

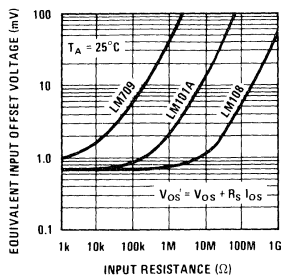


FIGURE 2. Illustrating The Effect Of Source Resistance On Typical Input Error Voltage

Naturally, error current has the greatest effect in high impedance circuitry. Figure 2 illustrates this point. The offset voltage of the LM709 is degraded significantly with source resistances greater than 10 kΩ. With the LM101A this is extended to source resistances high as 500 kΩ. The LM108, on the other hand, works well with source resistances above 10 MΩ.

High source resistances have an even greater effect on the drift of an amplifier, as shown in Figure 3. The performance of the LM709 is worsened with sources greater than 3 kΩ. The LM101A holds out to 100 kΩ sources, while the LM108 still works well at 3 MΩ.

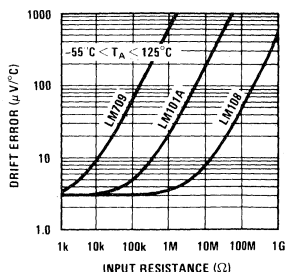


FIGURE 3. Degradation Of Typical Drift Characteristics With High Source Resistances

It is difficult to include FET amplifiers in Figure 3 because their drift is initially 50 μV/°C, unless

they are selected and trimmed. Even though their drift may be well controlled (5 μV/°C) over a limited temperature range, trimmed amplifiers generally exhibit a much higher drift over a -55°C to 125°C temperature range. At any rate, their average drift rate would, at best, be like that of the LM101A where 125°C operation is involved.

Applications that require low error currents include amplifiers for photodiodes or capacitive transducers, as these usually operate at megohm impedance levels. Sample-and-hold circuits, timers, integrators and analog memories also benefit from low error currents. For example, with the LM709, worst case drift rates for these kinds of circuits is in the order of 1.5V/sec. The LM108 improves this to 3 mV/sec.—worst case over a -55°C to 125°C temperature range. Low input currents are also helpful in oscillators and active filters to get low frequency operation with reasonable capacitor values. The LM108 can be used at a frequency of 1 Hz with capacitors no larger than 0.01 μF. In logarithmic amplifiers, the dynamic range can be extended by nearly 60 dB by going from the LM709 to the LM108. In other applications, having low error currents often permits an entirely different design approach which can greatly simplify circuitry.

#### THE LM108

Figure 4 shows a simplified schematic of the LM108. Two kinds of NPN transistors are used on the IC chip: super gain (primary) transistors which have a current gain of 5000 with a breakdown voltage of 4V and conventional (secondary) transistors which have a current gain of 200 with an 80V breakdown. These are differentiated on the schematic by drawing the secondaries with a wider base.

Primary transistors ( $Q_1$  and  $Q_2$ ) are used for the input stage; and they are operated in a cascode connection with  $Q_5$  and  $Q_6$ . The bases of  $Q_5$  and  $Q_6$  are bootstrapped to the emitters of  $Q_1$  and  $Q_2$  through  $Q_3$  and  $Q_4$ , so that the input transistors are operated at zero collector-base voltage. Hence, circuit performance is not impaired by the low breakdown of the primaries, as the secondary transistors stand off the common mode voltage. This configuration also improves the common mode rejection since the input transistors do not see variations in the common mode voltage. Further, because there is no voltage across their collector-base junctions, leakage currents in the input transistors are effectively eliminated.

The second stage is a differential amplifier using high gain lateral PNPs ( $Q_9$  and  $Q_{10}$ ).<sup>6</sup> These devices have current gains of 150 and a breakdown voltage of 80V.  $R_1$  and  $R_2$  are the collector load resistors for the input stage.  $Q_7$  and  $Q_8$  are diode connected laterals which compensate for the



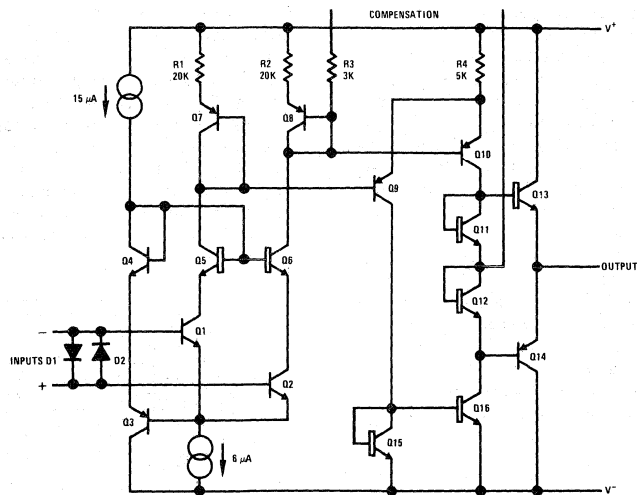


FIGURE 4. Simplified Schematic Of The LM108

emitter-base voltage of the second stage so that its operating current is set at twice that of the input stage by  $R_4$ .

The second stage uses an active collector load ( $Q_{15}$  and  $Q_{16}$ ) to obtain high gain. It drives a complementary class-B output stage which gives a substantial load driving capability. The dead zone of the output stage is eliminated by biasing it on the verge of conduction with  $Q_{11}$  and  $Q_{12}$ .

Two methods of frequency compensation are available for the amplifier. In one a 30 pF capacitor is connected from the input to the output of the second stage (between the compensation terminals). This method is pin-compatible with the LM101 or LM101A. It can also be compensated by connecting a 100 pF capacitor from the output of the second stage to ground. This technique has the advantage of improving the high frequency power supply rejection by a factor of ten.

A complete schematic of the LM108 is given in the Appendix along with a description of the circuit. This includes such essential features as overload protection for the inputs and output.

#### PERFORMANCE

The primary design objective for the LM108 was to obtain very low input currents without sacrificing offset voltage or drift. A secondary objective was to reduce the power consumption. Speed was of little concern, as long as it was comparable with the LM709. This is logical as it is quite difficult to

make high-impedance circuits fast; and low power circuits are very resistant to being made fast. In other respects, it was desirable to make the LM108 as much like the LM101A as possible.

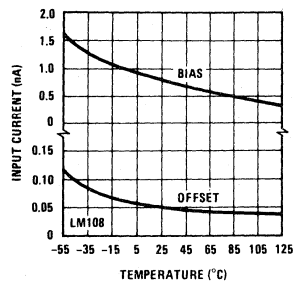


FIGURE 5. Input Currents

Figure 5 shows the input current characteristics of the LM108 over a  $-55^{\circ}\text{C}$  to  $125^{\circ}\text{C}$  temperature range. Not only are the input currents low, but also they do not change radically over temperature. Hence, the device lends itself to relatively simple temperature compensation schemes, that will be described later.

There has been considerable discussion about using Darlington input stages rather than super gain transistors to obtain low input currents.<sup>6,7</sup> It is appropriate to make a few comments about that here.

Darlington inputs can give about the same input bias currents as super gain transistors—at room temperature. However, the bias current varies as the square of the transistor current gain. At low temperatures, super gain devices have a decided advantage. Additionally, the offset current of super gain transistors is considerably lower than Darlington, when measured as a percentage of bias current. Further, the offset voltage and offset voltage drift of Darlington transistors is both higher and more unpredictable.

Experience seems to tell the real truth about Darlington. Quite a few op amps with Darlington input stages have been introduced. However, none have become industry standards. The reason is that they are more sensitive to variations in the manufacturing process. Therefore, satisfactory performance specifications can only be obtained by sacrificing the manufacturing yield.

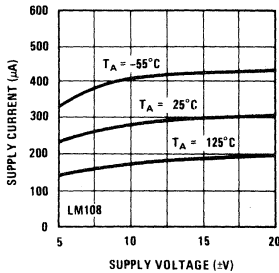


FIGURE 6. Supply Current

The supply current of the LM108 is plotted as a function of supply voltage in Figure 6. The operating current is about an order of magnitude lower than devices like the LM709. Furthermore, it does not vary radically with supply voltage which means that the device performance is maintained at low voltages and power consumption is held down at high voltages.

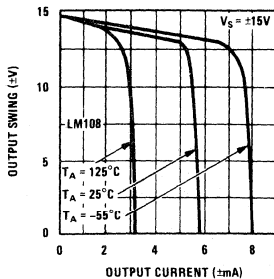


FIGURE 7. Output Swing

The output drive capability of the circuit is illustrated in Figure 7. The output swings to within a

volt of the supplies, which is especially important when operating at low voltages. The output falls off rapidly as the current increases above a certain level and the short circuit protection goes into effect. The useful output drive is limited to about  $\pm 2$  mA. It could have been increased by the addition of Darlington transistors on the output, but this would have restricted the voltage swing at low supply voltages. The amplifier, incidentally, works with common mode signals to within a volt of the supplies so it can be used with supply voltages as low as  $\pm 2$ V.



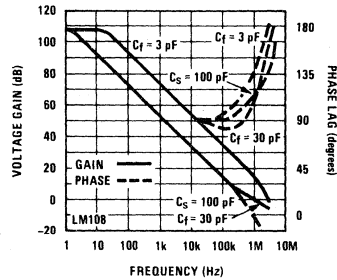


FIGURE 8. Open Loop Frequency Response

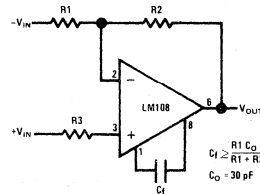The open loop frequency response, plotted in Figure 8, indicates that the frequency response is about the same as that of the LM709 or the LM101A. Curves are given for the two compensa-



a. Standard Compensation Circuit

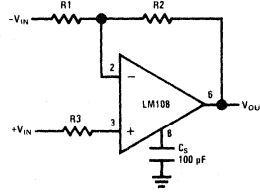

b. Alternate Compensation Circuit

FIGURE 9. Compensation Circuits

tion circuits shown in Figure 9. The standard compensation is identical to that of the LM101 or LM101A. The alternate compensation scheme gives much better rejection of high frequency power supply noise, as will be shown later.

With unity gain compensation, both methods give a 75-degree stability margin. However, the shunt compensation has a 300 kHz small signal bandwidth as opposed to 1 MHz for the other scheme. Because the compensation capacitor is not included on the IC chip, it can be tailored to fit the application. When the amplifier is used only at low frequencies, the compensation capacitor can be increased to give a greater stability margin. This makes the circuit less sensitive to capacitive loading, stray capacitances or improper supply bypassing. Overcompensation also reduces the high frequency noise output of the amplifier.

With closed-loop gains greater than one, the high frequency performance can be optimized by making the compensation capacitor smaller. If unity-gain compensation is used for an amplifier with a gain of ten, the gain error will exceed 1-percent at frequencies above 400 Hz. This can be extended to 4 kHz by reducing the compensation capacitor to 3 pF. The formula for determining the minimum capacitor value is given in Figure 9a. It should be noted that the capacitor value does not really depend on the closed-loop gain. Instead, it depends on the high frequency attenuation in the feedback networks and, therefore, the values of  $R_1$  and  $R_2$ . When it is desirable to optimize performance at high frequencies, the standard compensation should be used. With small capacitor values, the stability margin obtained with shunt compensation is inadequate for conservative designs.

The frequency response of an operational amplifier is considerably different for large output signals than it is for small signals. This is indicated in Figure 10. With unity-gain compensation, the small signal bandwidth of the LM108 is 1 MHz. Yet full output swing cannot be obtained above 2 kHz. This corresponds to a slew rate of  $0.3V/\mu s$ . Both the full-output bandwidth and the slew rate can be increased by using smaller compensation capacitors, as is indicated in the figure. However, this is only applicable for higher closed loop gains. The results plotted in Figure 10 are for standard compensations. With unity gain compensation, the same curves are obtained for the shunt compensation scheme.

Classical op amp theory establishes output resistance as an important design parameter. This is not true for IC op amps: The output resistance of most devices is low enough that it can be ignored, because they use class-B output stages. At low frequencies, thermal feedback between the output

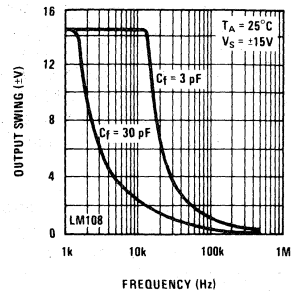


FIGURE 10. Large Signal Frequency Response

and input stages determines the effective output resistance, and this cannot be accounted for by conventional design theories. Semiconductor manufacturers take care of this by specifying the gain under full load conditions, which combines output resistance with gain as far as it affects overall circuit performance. This avoids the fictitious problem that can be created by an amplifier with infinite gain, which is good, that will cause the open loop output resistance to appear infinite, which is bad, although none of this affects overall performance significantly.

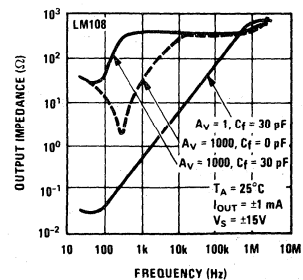


FIGURE 11. Closed Loop Output Impedance

The *closed loop* output impedance is, nonetheless, important in some applications. This is plotted for several operating conditions in Figure 11. It can be seen that the output impedance rises to about  $500\Omega$  at high frequencies. The increase occurs because the compensation capacitor rolls off the open loop gain. The output resistance can be reduced at the intermediate frequencies, for closed loop gains greater than one, by making the capacitor smaller. This is made apparent in the figure by comparing the output resistance with and without frequency compensation for a closed loop gain of 1000.

The output resistance also tends to increase at low frequencies. Thermal feedback is responsible for this phenomenon. The data for Figure 11 was taken under large-signal conditions with  $\pm 15\text{V}$  supplies, the output at zero and a  $\pm 1\text{ mA}$  current swing. Hence, the thermal feedback is accentuated more than would be the case for most applications.

In an op amp, it is desirable that performance be unaffected by variations in supply voltage. IC amplifiers are generally better than discrete in this respect because it is necessary for one single design to cover a wide range of uses. The LM108 has a power supply rejection which is typically in excess of 100 dB, and it will operate with supply voltages from  $\pm 2\text{V}$  to  $\pm 20\text{V}$ . Therefore, well-regulated supplies are unnecessary, for most applications, because a 20-percent variation has little effect on performance.

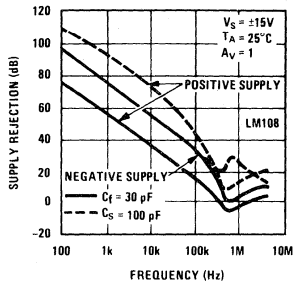


FIGURE 12. Power Supply Rejection

The story is different for high-frequency noise on the supplies, as is evident from Figure 12. Above 1 MHz, practically all the noise is fed through to the output. The figure also demonstrates that shunt compensation is about ten times better at rejecting high frequency noise than is standard compensation. This difference is even more pronounced with larger capacitor values. The shunt compensation has the added advantage that it makes the circuit virtually unaffected by the lack of supply bypassing.

Power supply rejection is defined as the ratio of the change in offset voltage to the change in the supply voltage producing it. Using this definition, the rejection at low frequencies is unaffected by the closed loop gain. However, at high frequencies, the opposite is true. The high frequency rejection is increased by the closed loop gain. Hence, an amplifier with a gain of ten will have an order of magnitude better rejection than that shown in Figure 12 in the vicinity of 100 kHz to 1 MHz.

The overall performance of the LM108 is summarized in Table 1\*. It is apparent from the table and the previous discussion that the device is ideally suited for applications that require low input currents or reduced power consumption. The speed of the amplifier is not spectacular, but this is not usually a problem in high-impedance circuitry. Further, the reduced high frequency performance makes the amplifier easier to use in that less attention need be paid to capacitive loading, stray capacitances and supply bypassing.

## APPLICATIONS

Because of its low input current, the LM108 opens up many new design possibilities. However, extra care must be taken in component selection and the assembly of printed circuit boards to take full advantage of its performance. Further, unusual design techniques must often be applied to get around the limitations of some components.

## SAMPLE AND HOLD CIRCUITS

The holding accuracy of a sample and hold is directly related to the error currents in the components used. Therefore, it is a good circuit to start off with in explaining the problems in-

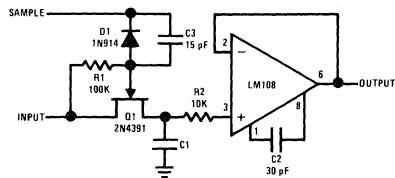


FIGURE 13. Sample And Hold Circuit


olved. Figure 13 shows one configuration for a sample and hold. During the sample interval,  $Q_1$  is turned on, charging the hold capacitor,  $C_1$ , up to the value of the input signal. When  $Q_1$  is turned off,  $C_1$  retains this voltage. The output is obtained from an op amp that buffers the capacitor so that it is not discharged by any loading. In the holding mode, an error is generated as the capacitor loses charge to supply circuit leakages. The accumulation rate for error is given by

$$\frac{dV}{dt} = \frac{I_E}{C_1}$$

where  $dV/dt$  is the time rate of change in output voltage and  $I_E$  is the sum of the input current to the op amp, the leakage current of the holding capacitor, board leakages and the "off" current of the FET switch.

\*See Appendix, page AN29-19.

When high-temperature operation is involved, the FET leakage can limit circuit performance. This can be minimized by using a junction FET, as indicated, because commercial junction FETs have lower leakage than their MOS counterparts. However, at 125°C even junction devices are a problem. Mechanical switches, such as reed relays, are quite satisfactory from the standpoint of leakage. However, they are often undesirable because they are sensitive to vibration, they are too slow or they require excessive drive power. If this is the case, the circuit in Figure 14 can be used to eliminate the FET leakage.

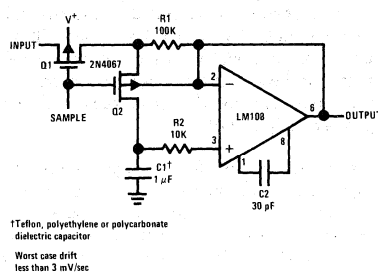

**FIGURE 14. Sample And Hold That Eliminates Leakage In FET Switches**

When using P-channel MOS switches, the substrate must be connected to a voltage which is always more positive than the input signal. The source-to-substrate junction becomes forward biased if this is not done. The troublesome leakage current of a MOS device occurs across the substrate-to-drain junction. In Figure 14, this current is routed to the output of the buffer amplifier through R<sub>1</sub> so that it does not contribute to the error current.

The main sample switch is Q<sub>1</sub>, while Q<sub>2</sub> isolates the hold capacitor from the leakage of Q<sub>1</sub>. When the sample pulse is applied, both FETs turn on charging C<sub>1</sub> to the input voltage. Removing the pulse shuts off both FETs, and the output leakage of Q<sub>1</sub> goes through R<sub>1</sub> to the output. The voltage drop across R<sub>1</sub> is less than 10 mV, so the substrate of Q<sub>2</sub> can be bootstrapped to the output of the LM108. Therefore, the voltage across the substrate-drain junction is equal to the offset voltage of the amplifier. At this low voltage, the leakage of the FET is reduced by about two orders of magnitude.

It is necessary to use MOS switches when bootstrapping the leakages in this fashion. The gate leakage of a MOS device is still negligible at

high temperatures; this is not the case with junction FETs. If the MOS transistors have protective diodes on the gates, special arrangements must be made to drive Q<sub>2</sub> so the diode does not become forward biased.

In selecting the hold capacitor, low leakage is not the only requirement. The capacitor must also be free of dielectric polarization phenomena.<sup>8</sup> This rules out such types as paper, mylar, electrolytic, tantalum or high-K ceramic. For small capacitor values, glass or silvered-mica capacitors are recommended. For the larger values, ones with teflon, polyethylene or polycarbonate dielectrics should be used.

The low input current of the LM108 gives a drift rate, in hold, of only 3 mV/sec when a 1 μF hold capacitor is used. And this number is worst case over the military temperature range. Even if this kind of performance is not needed, it may still be beneficial to use the LM108 to reduce the size of the hold capacitor. High quality capacitors in the larger sizes are bulky and expensive. Further, the switches must have a low "on" resistance and be driven from a low impedance source to charge large capacitors in a short period of time.

If the sample interval is less than about 100 μs, the LM108 may not be fast enough to work properly. If this is the case, it is advisable to substitute the LM102A,<sup>9</sup> which is a voltage follower designed for both low input current and high speed. It has a 30V/μs slew rate and will operate with sample intervals as short as 1 μs.

When the hold capacitor is larger than 0.05 μF, an isolation resistor should be included between the capacitor and the input of the amplifier (R<sub>2</sub> in Figure 14). This resistor insures that the IC will not be damaged by shorting the output or abruptly shutting down the supplies when the capacitor is charged. This precaution is not peculiar to the LM108 and should be observed on any IC op amp.

## INTEGRATORS

Integrators are a lot like sample-and-hold circuits and have essentially the same design problems. In an integrator, a capacitor is used as a storage element; and the error accumulation rate is again proportional to the input current of the op amp.

Figure 15 shows a circuit that can compensate for the bias current of the amplifier. A current is fed into the summing node through R<sub>1</sub> to supply the bias current. The potentiometer, R<sub>2</sub>, is adjusted so that this current exactly equals the bias current, reducing the drift rate to zero.


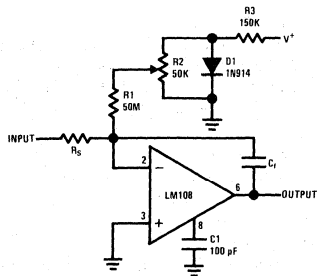


FIGURE 15. Integrator With Bias Current Compensation

The diode is used for two reasons. First, it acts as a regulator, making the compensation relatively insensitive to variations in supply voltage. Secondly, the temperature drift of diode voltage is approximately the same as the temperature drift of bias current. Therefore, the compensation is more effective if the temperature changes. Over a 0°C to 70°C temperature range, the compensation will give a factor of ten reduction in input current. Even better results are achieved if the temperature change is less.

Normally, it is necessary to reset an integrator to establish the initial conditions for integration. Resetting to zero is readily accomplished by shorting the integrating capacitor with a suitable switch. However, as with the sample and hold circuits, semiconductor switches can cause problems because of high-temperature leakage.

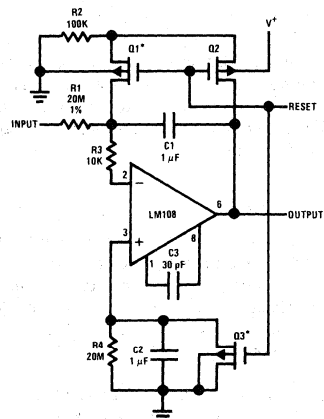A connection that gets rid of switch leakages is shown in Figure 16. A negative-going reset pulse



\*Q1 and Q3 should not have internal gate-protection diodes.

FIGURE 16. Low Drift Integrator With Reset

turns on  $Q_1$  and  $Q_2$ , shorting the integrating capacitor. When the switches turn off, the leakage current of  $Q_2$  is absorbed by  $R_1$  while  $Q_1$  isolates the output of  $Q_2$  from the summing node.  $Q_1$  has practically no voltage across its junctions because the substrate is grounded; hence, leakage currents are negligible.

The additional circuitry shown in Figure 16 makes the error accumulation rate proportional to the offset current, rather than the bias current. Hence, the drift is reduced by roughly a factor of 10. During the integration interval, the bias current of the non-inverting input accumulates an error across  $R_4$  and  $C_2$  just as the bias current on the inverting input does across  $R_1$  and  $C_1$ . Therefore, if  $R_4$  is matched with  $R_1$  and  $C_2$  is matched with  $C_1$  (within about 5 percent) the output will drift at a rate proportional to the difference in these currents. At the end of the integration interval,  $Q_3$  removes the compensating error accumulated on  $C_2$  as the circuit is reset.

In applications involving large temperature changes, the circuit in Figure 16 gives better results than the compensation scheme in Figure 15—especially under worst case conditions. Over a -55°C to 125°C temperature range, the worst case drift is reduced from 3 mV/sec to 0.5 mV/sec when a 1 μF integrating capacitor is used. If this reduction in drift is not needed, the circuit can be simplified by eliminating  $R_4$ ,  $C_2$  and  $Q_3$  and returning the non-inverting input of the amplifier directly to ground.

In fabricating low drift integrators, it is again necessary to use high quality components and minimize leakage currents in the wiring. The comments made on capacitors in connection with the sample-and-hold circuits also apply here. As an additional precaution, a resistor should be used to isolate the inverting input from the integrating capacitor if it is larger than 0.05 μF. This resistor prevents damage that might occur when the supplies are abruptly shut down while the integrating capacitor is charged.

Some integrator applications require both speed and low error current. The output amplifiers for photomultiplier tubes or solid-state radiation detectors are examples of this. Although the LM108 is relatively slow, there is a way to speed it up when it is used as an inverting amplifier. This is shown in Figure 17.

The circuit is arranged so that the high-frequency gain characteristics are determined by  $A_2$ , while  $A_1$  determines the dc and low-frequency characteristics. The non-inverting input of  $A_1$  is connected to the summing node through  $R_1$ .  $A_1$  is operated as an integrator, going through unity gain at 500 Hz. Its output drives the non-inverting input

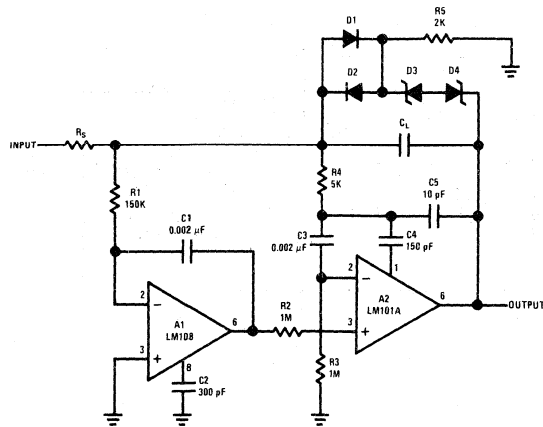


FIGURE 17. Fast Integrator

of  $A_2$ . The inverting input of  $A_2$  is also connected to the summing node through  $C_3$ .  $C_3$  and  $R_3$  are chosen to roll off below 750 Hz. Hence, at frequencies above 750 Hz, the feedback path is directly around  $A_2$ , with  $A_1$  contributing little. Below 500 Hz, however, the direct feedback path to  $A_2$  rolls off; and the gain of  $A_1$  is added to that of  $A_2$ .

The high frequency amplifier,  $A_2$ , is an LM101A connected with feed-forward compensation.<sup>10</sup> It has a 10 MHz equivalent small-signal bandwidth, a  $10\text{V}/\mu\text{s}$  slew rate and a 250 kHz large-signal bandwidth, so these are the high-frequency characteristics of the complete amplifier. The bias current of  $A_2$  is isolated from the summing node by  $C_3$ . Hence, it does not contribute to the dc drift of the integrator. The inverting input of  $A_1$  is the only dc connection to the summing junction. Therefore, the error current of the composite amplifier is equal to the bias current of  $A_1$ .

If  $A_2$  is allowed to saturate,  $A_1$  will then start towards saturation. If the output of  $A_1$  gets far off zero, recovery from saturation will be slowed drastically. This can be prevented by putting zener clamp diodes across the integrating capacitor. A suitable clamping arrangement is shown in Figure 17.  $D_1$  and  $D_2$  are included in the clamp circuit along with  $R_5$  to keep the leakage currents of the zeners from introducing errors.

In addition to increasing speed, this circuit has other advantages. For one, it has the increased output drive capability of the LM101A. Further,

thermal feedback is virtually eliminated because the LM108 does not see load variations. Lastly, the open loop gain is nearly infinite at low frequencies as it is the product of the gains of the two amplifiers.

### SINE WAVE OSCILLATOR

Although it is comparatively easy to build an oscillator that approximates a sine wave, making one that delivers a high-purity sinusoid with a stable frequency and amplitude is another story. Most satisfactory designs are relatively complicated and require individual trimming and temperature compensation to make them work. In addition, they generally take a long time to stabilize to the final output amplitude.

A unique solution to most of these problems is shown in Figure 18.  $A_1$  is connected as a two-pole low-pass active filter, and  $A_2$  is connected as an integrator. Since the ultimate phase lag introduced by the amplifiers is 270 degrees, the circuit can be made to oscillate if the loop gain is high enough at the frequency where the lag is 180 degrees. The gain is actually made somewhat higher than is required for oscillation to insure starting. Therefore, the amplitude builds up until it is limited by some nonlinearity in the system.

Amplitude stabilization is accomplished with zener clamp diodes,  $D_1$  and  $D_2$ . This does introduce distortion, but it is reduced by the subsequent low pass filters. If  $D_1$  and  $D_2$  have equal breakdown voltages, the resulting symmetrical clipping will

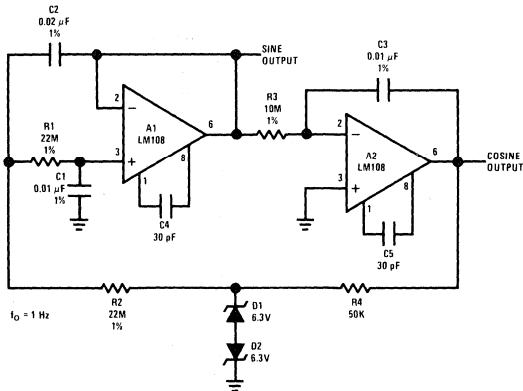


FIGURE 18. Sine Wave Oscillator

virtually eliminate the even-order harmonics. The dominant harmonic is then the third, and this is about 40 dB down at the output of  $A_1$  and about 50 dB down on the output of  $A_2$ . This means that the total harmonic distortion on the two outputs is 1 percent and 0.3 percent, respectively.

The frequency of oscillation and the oscillation threshold are determined by  $R_1$ ,  $R_2$ ,  $R_3$ ,  $C_1$ ,  $C_2$  and  $C_3$ . Therefore precision components with low temperature coefficients should be used. If  $R_3$  is made lower than shown, the circuit will accept looser component tolerances before dropping out of oscillation. The start up will also be quicker. However, the price paid is that distortion is increased. The value of  $R_4$  is not critical, but it should be made much smaller than  $R_2$  so that the effective resistance at  $R_2$  does not drop when the clamp diodes conduct.

The output amplitude is determined by the breakdown voltages of  $D_1$  and  $D_2$ . Therefore, the clamp level should be temperature compensated for stable operation. Diode-connected (collector shorted to base) NPN transistors with an emitter-base breakdown of about 6.3V work well, as the positive temperature coefficient of the diode in reverse breakdown nearly cancels the negative temperature coefficient of the forward-biased diode. Added advantages of using transistors are that they have less shunt capacitance and sharper breakdowns than conventional zeners.

The LM108 is particularly useful in this circuit at low frequencies, since it permits the use of small capacitors. The circuit shown oscillates at 1 Hz,

but uses capacitors in the order of  $0.01 \mu\text{F}$ . This makes it much easier to find temperature-stable precision capacitors. However, some judgment must be used as large value resistors with low temperature coefficients are not exactly easy to come by.\*

The LM108s are useful in this circuit for output frequencies up to 1 kHz. Beyond that, better performance can be realized by substituting an LM102A for  $A_1$  and an LM101A with feed-forward compensation for  $A_2$ . The improved high-frequency response of these devices extends the operating frequency out to 100 kHz.

#### CAPACITANCE MULTIPLIER

Large capacitor values can be eliminated from most systems just by raising the impedance levels, if suitable op amps are available. However, sometimes it is not possible because the impedance levels are already fixed by some element of the system like a low impedance transducer. If this is the case, a capacitance multiplier can be used to increase the effective capacitance of a small capacitor and couple it into a low impedance system.

Previously, IC op amps could not be used effectively as capacitance multipliers because the equivalent leakages generated due to offset current were significantly greater than the leakages of large tantalum capacitors. With the LM108, this has changed. The circuit shown in Figure 19 generates

\*Large-value resistors are available from Victoreen Instrument, Cleveland, Ohio and Pyrofilm Resistor Co., Whippany, New Jersey.



an equivalent capacitance of 100,000  $\mu\text{F}$  with a worst case leakage of 8  $\mu\text{A}$ —over a  $-55^\circ\text{C}$  to  $125^\circ\text{C}$  temperature range.

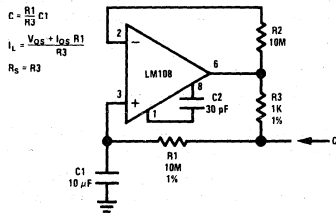


FIGURE 19. Capacitance Multiplier

The performance of the circuit is described by the equations given in Figure 19, where  $C$  is the effective output capacitance,  $I_L$  is the leakage current of this capacitance and  $R_S$  is the series resistance of the multiplied capacitance. The series resistance is relatively high, so high-Q capacitors cannot be realized. Hence, such applications as tuned circuits and filters are ruled out. However, the multiplier can still be used in timing circuits or servo compensation networks where some resistance is usually connected in series with the capacitor or the effect of the resistance can be compensated for.

One final point is that the leakage current of the multiplied capacitance is not a function of the applied voltage. It persists even with no voltage on the output. Therefore, it can generate offset errors in a circuit, rather than the scaling errors caused by conventional capacitors.

### INSTRUMENTATION AMPLIFIER

In many instrumentation applications there is frequently a need for an amplifier with a high-impedance differential input and a single ended output. Obvious uses for this are amplifiers for bridge-type signal sources such as strain gages, temperature sensors or pressure transducers. General purpose op amps have satisfactory input characteristics, but feedback must be added to determine the effective gain. And the addition of feedback can drastically reduce the input resistance and degrade common mode rejection.

Figure 20 shows the classical op amp circuit for a differential amplifier. This circuit has three main disadvantages. First, the input resistance on the inverting input is relatively low, being equal to  $R_1$ . Second, there usually is a large difference in the input resistance of the two inputs, as is indicated by the equations on the schematic. Third, the common mode rejection is greatly affected by re-

sistor matching and by balancing of the source resistances. A 1-percent deviation in any one of the resistor values reduces the common mode rejection to 46 dB for a closed loop gain of 1, to 60 dB for a gain of 10 and to 80 dB for a gain of 100.

Clearly, the only way to get high input impedance is to use very large resistors in the feedback network. The op amp must operate from a source resistance which is orders of magnitude larger than the resistance of the signal source. Older IC op amps introduced excessive offset and drift when operating from higher resistances and could not be used successfully. The LM108, however, is relatively unaffected by the large resistors, so this approach can sometimes be employed.

With large input resistors, the feedback resistors,  $R_3$  and  $R_4$ , can get quite large for higher closed loop gains. For example, if  $R_1$  and  $R_2$  are 1  $\text{M}\Omega$ ,  $R_3$  and  $R_4$  must be 100  $\text{M}\Omega$  for a gain of 100. It is difficult to accurately match resistors that are this high in value, so common mode rejection may suffer. Nonetheless, any one of the resistors can be trimmed to take out common mode feedthrough caused either by resistor mismatches or the amplifier itself.

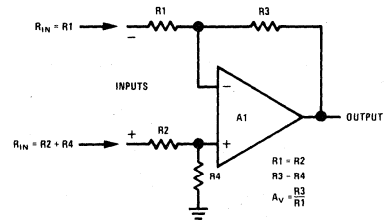


FIGURE 20. Feedback Connection For a Differential Amplifier

Another problem caused by large feedback resistors is that stray capacitance can seriously affect the high frequency common mode rejection. With 1  $\text{M}\Omega$  input resistors, a 1 pF mismatch in stray capacitance from either input to ground can drop the common mode rejection to 40 dB at 1500 Hz. The high frequency rejection can be improved at the expense of frequency response by shunting  $R_3$  and  $R_4$  with matched capacitors.

With high impedance bridges, the feedback resistances become prohibitively large even for the LM108, so the circuit in Figure 20 cannot be used. One possible alternative is shown in Figure 21.  $R_2$  and  $R_3$  are chosen so that their equivalent parallel resistance is equal to  $R_1$ . Hence, the output of the amplifier will be zero when the bridge is balanced.

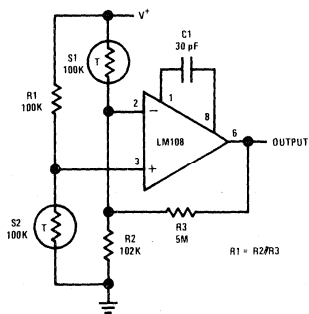


FIGURE 21. Amplifier For Bridge Transducers

When the bridge goes off balance, the op amp maintains the voltage between its input terminals at zero with current fed back from the output through  $R_3$ . This circuit does not act like a true differential amplifier for large imbalances in the bridge. The voltage drops across the two sensor resistors,  $S_1$  and  $S_2$ , become unequal as the bridge goes off balance, causing some non-linearity in the transfer function. However, this is not usually objectionable for small signal swings.

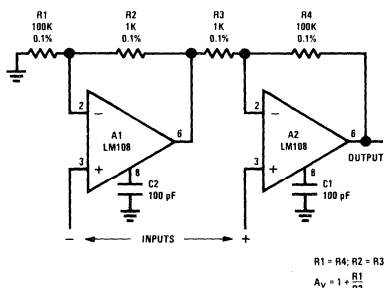


FIGURE 22. Differential Input Instrumentation Amplifier

Figure 22 shows a true differential connection that has few of the problems mentioned previously. It has an input resistance greater than  $10^{10} \Omega$ , yet it does not need large resistors in the feedback circuitry. With the component values shown,  $A_1$  is connected as a non-inverting amplifier with a gain of 1.01; and it feeds into  $A_2$  which has an inverting gain of 100. Hence, the total gain from the input of  $A_1$  to the output of  $A_2$  is 101, which is equal to the non-inverting gain of  $A_2$ . If all the resistors are matched, the circuit responds only to the differential input signal—not the common mode voltage.

This circuit has the same sensitivity to resistor matching as the previous circuits, with a 1 percent mismatch between two resistors lowering the common mode rejection to 80 dB. However, matching is more easily accomplished because of the lower resistor values. Further, the high frequency common mode rejection is less affected by stray capacitances. The high frequency rejection is limited, though, by the response of  $A_1$ .

## LOGARITHMIC CONVERTER

A logarithmic amplifier is another circuit that can take advantage of the low input current of an op amp to increase dynamic range. Most practical log converters make use of the logarithmic relationship between the emitter-base voltage of standard double-diffused transistors and their collector current. This logarithmic characteristic has been proven true for over 9 decades of collector current. The only problem involved in using transistors as logging elements is that the scale factor has a temperature sensitivity of 0.3 percent/ $^{\circ}\text{C}$ . However, temperature compensating resistors have been developed to compensate for this characteristic, making possible log converters that are accurate over a wide temperature range.

Figure 23 gives a circuit that uses these techniques.  $Q_1$  is the logging transistor, while  $Q_2$  provides a fixed offset to temperature compensate the emitter-base turn on voltage of  $Q_1$ .  $Q_2$  is operated at a fixed collector current of  $10 \mu\text{A}$  by  $A_2$ , and its emitter-base voltage is subtracted from that of  $Q_1$  in determining the output voltage of the circuit. The collector current of  $Q_2$  is established by  $R_3$  and  $V^+$  through  $A_2$ .

The collector current of  $Q_1$  is proportional to the input current through  $R_s$  and, therefore, proportional to the input voltage. The emitter-base voltage of  $Q_1$  varies as the log of the input voltage. The fixed emitter-base voltage of  $Q_2$  subtracts from the voltage on the emitter of  $Q_1$  in determining the voltage on the top end of the temperature-compensating resistor,  $S_1$ .

The signal on the top of  $S_1$  will be zero when the input current is equal to the current through  $R_3$  at any temperature. Further, this voltage will vary logarithmically for changes in input current, although the scale factor will have a temperature coefficient of  $-0.3\%/^{\circ}\text{C}$ . The output of the converter is essentially multiplied by the ratio of  $R_1$  to  $S_1$ . Since  $S_1$  has a positive temperature coefficient of 0.3 percent/ $^{\circ}\text{C}$ , it compensates for the change in scale factor with temperature.

In this circuit, an LM101A with feedforward compensation is used for  $A_2$  since it is much faster than the LM108 used for  $A_1$ . Since both amplifiers are cascaded in the overall feedback loop, the reduced phase shift through  $A_2$  insures stability.

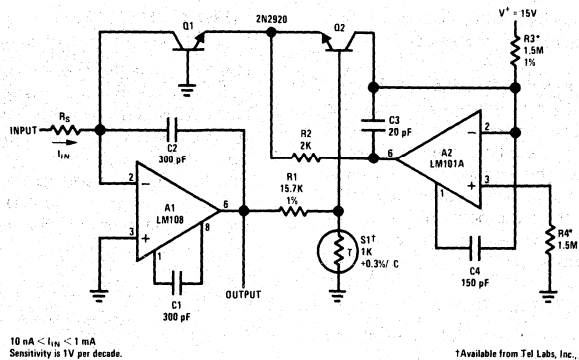


FIGURE 23. Temperature Compensated One-Quadrant Logarithmic Converter

Certain things must be considered in designing this circuit. For one, the sensitivity can be changed by varying  $R_1$ . But  $R_1$  must be made considerably larger than the resistance of  $S_1$  for effective temperature compensation of the scale factor.  $Q_1$  and  $Q_2$  should also be matched devices in the same package, and  $S_1$  should be at the same temperature as these transistors. Accuracy for low input currents is determined by the error caused by the bias current of  $A_1$ . At high currents, the behavior of  $Q_1$  and  $Q_2$  limits accuracy. For input currents approaching 1 mA, the 2N2920 develops logging errors in excess of 1 percent. If larger input currents are anticipated, bigger transistors must be used; and  $R_2$  should be reduced to insure that  $A_2$  does not saturate.

#### TRANSDUCER AMPLIFIERS

With certain transducers, accuracy depends on the choice of the circuit configuration as much as it does on the quality of the components. The amplifier for photodiode sensors, shown in Figure 24, illustrates this point. Normally, photodiodes are

operated with reverse voltage across the junction. At high temperatures, the leakage currents can approach the signal current. However, photodiodes deliver a short-circuit output current, unaffected by leakage currents, which is not significantly lower than the output current with reverse bias.

The circuit shown in Figure 24 responds to the short-circuit output current of the photodiode. Since the voltage across the diode is only the offset voltage of the amplifier, inherent leakage is reduced by at least two orders of magnitude. Neglecting the offset current of the amplifier, the output current of the sensor is multiplied by  $R_1$  plus  $R_2$  in determining the output voltage.

Figure 25 shows an amplifier for high-impedance ac transducers like a piezoelectric accelerometer. These sensors normally require a high-input-resistance amplifier. The LM108 can provide input resistances in the range of 10 to 100 M $\Omega$ , using conventional circuitry. However, conventional designs are sometimes ruled out either because

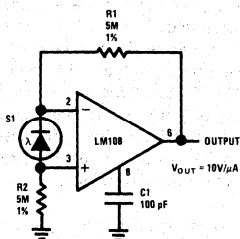


FIGURE 24. Amplifier For Photodiode Sensor

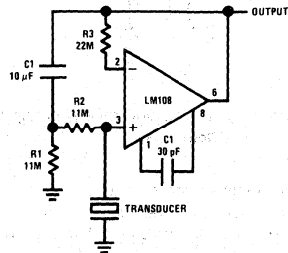


FIGURE 25. Amplifier For Piezoelectric Transducers

large resistors cannot be used or because prohibitively large input resistances are needed.

Using the circuit in Figure 25, input resistances that are orders of magnitude greater than the values of the dc return resistors can be obtained. This is accomplished by bootstrapping the resistors to the output. With this arrangement, the lower cutoff frequency of a capacitive transducer is determined more by the RC product of  $R_1$  and  $C_1$  than it is by resistor values and the equivalent capacitance of the transducer.

### RESISTANCE MULTIPLICATION

When an inverting operational amplifier must have high input resistance, the resistor values required can get out of hand. For example, if a  $2\text{ M}\Omega$  input resistance is needed for an amplifier with a gain of 100, a  $200\text{ M}\Omega$  feedback resistor is called for. This resistance can, however, be reduced using the circuit in Figure 26. A divider with a ratio of 100 to 1 ( $R_3$  and  $R_4$ ) is added to the output of the amplifier: Unity-gain feedback is applied from the output of the divider, giving an overall gain of 100 using only  $2\text{ M}\Omega$  resistors.

This circuit does increase the offset voltage somewhat. The output offset voltage is given by

$$V_{OUT} = \left( \frac{R_1 + R_2}{R_2} \right) A_V V_{OS}$$

The offset voltage is only multiplied by  $A_V + 1$  in a conventional inverter. Therefore, the circuit in Figure 26 multiplies the offset by 200, instead of 101. This multiplication factor can be reduced to 110 by increasing  $R_2$  to  $20\text{ M}\Omega$  and  $R_3$  to  $5.55\text{ k}\Omega$ .

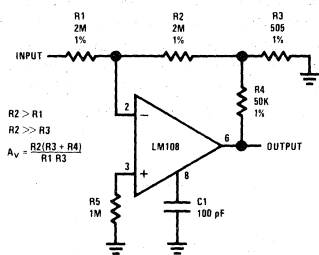


FIGURE 26. Inverting Amplifier With High Input Resistance

Another disadvantage of the circuit is that four resistors determine the gain, instead of two. Hence, for a given resistor tolerance, the worst-case gain deviation is greater, although this is probably more than offset by the ease of getting better tolerances in the low resistor values.

### CURRENT SOURCES

Although there are numerous ways to make current sources with op amps, most have limitations as far as their application is concerned. Figure 27, however, shows a current source which is fairly flexible and has few restrictions as far as its use is concerned. It supplies a current that is proportional to the input voltage and drives a load referred to ground or any voltage within the output-swing capability of the amplifier.

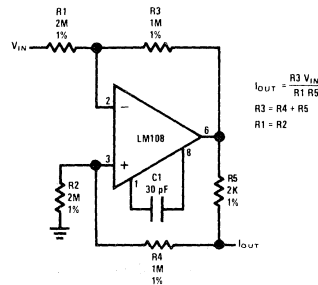


FIGURE 27. Bilateral Current Source

With the output grounded, it is relatively obvious that the output current will be determined by  $R_5$  and the gain setting of the op amp, yielding

$$I_{OUT} = - \frac{R_3 V_{IN}}{R_1 R_5}$$

When the output is not at zero, it would seem that the current through  $R_2$  and  $R_4$  would reduce accuracy. Nonetheless, if  $R_1 = R_2$  and  $R_3 = R_4 + R_5$ , the output current will be independent of the output voltage. For  $R_1 + R_3 \gg R_5$ , the output resistance of the circuit is given by

$$R_{OUT} \cong R_5 \left( \frac{R}{\Delta R} \right)$$

where  $R$  is any one of the feedback resistors ( $R_1$ ,  $R_2$ ,  $R_3$  or  $R_4$ ) and  $\Delta R$  is the incremental change in the resistor value from design center. Hence, for the circuit in Figure 27, a 1 percent deviation in one of the resistor values will drop the output resistance of  $200\text{ k}\Omega$ . Such errors can be trimmed out by adjusting one of the feedback resistors. In design, it is advisable to make the feedback resistors as large as possible. Otherwise, resistor tolerances become even more critical.

The circuit must be driven from a source resistance which is low by comparison to  $R_1$ , since this resistance will imbalance the circuit and affect both gain and output resistance. As shown, the circuit

gives a negative output current for a positive input voltage. This can be reversed by grounding the input and driving the ground end of  $R_2$ . The magnitude of the scale factor will be unchanged as long as  $R_4 \gg R_5$ .

### VOLTAGE COMPARATORS

Like most op amps, it is possible to use the LM108 as a voltage comparator. Figure 28 shows the device used as a simple zero-crossing detector. The inputs of the IC are protected internally by back-

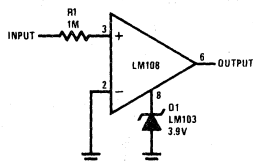


FIGURE 28. Zero Crossing Detector

to-back diodes connected between them, therefore, voltages in excess of 1V cannot be impressed directly across the inputs. This problem is taken care of by  $R_1$  which limits the current so that input voltages in excess of 1 kV can be tolerated. If absolute accuracy is required or if  $R_1$  is made much larger than 1 M $\Omega$ , a compensating resistor of equal value should be inserted in series with the other input.

In Figure 28, the output of the op amp is clamped so that it can drive DTL or TTL directly. This is accomplished with a clamp diode on pin 8. When the output swings positive, it is clamped at the breakdown voltage of the zener. When it swings negative, it is clamped at a diode drop below ground. If the 5V logic supply is used as a positive supply for the amplifier, the zener can be replaced with an ordinary silicon diode. The maximum fan out that can be handled by the device is one for standard DTL or TTL under worst case conditions.

As might be expected, the LM108 is not very fast when used as a comparator. The response time is up in the tens of microseconds. An LM103<sup>11</sup> is recommended for  $D_1$ , rather than a conventional alloy zener, because it has lower capacitance and will not slow the circuit further. The sharp breakdown of the LM103 at low currents is also an advantage as the current through the diode in clamp is only 10  $\mu$ A.

Figure 29 shows a comparator for voltages of opposite polarity. The output changes state when the voltage on the junction of  $R_1$  and  $R_2$  is equal to  $V_{TH}$ . Mathematically, this is expressed by

$$V_{TH} = V_2 + \frac{R_2 (V_1 - V_2)}{R_1 + R_2}$$

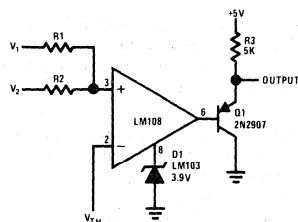


FIGURE 29. Voltage Comparator With Output Buffer

The LM108 can also be used as a differential comparator, going through a transition when two input voltages are equal. However, resistors must be inserted in series with the inputs to limit current and minimize loading on the signal sources when the input-protection diodes conduct. Figure 29 also shows how a PNP transistor can be added on the output to increase the fan out to about 20 with standard DTL or TTL.

### POWER BOOSTER

The LM108, which was designed for low power consumption, is not able to drive heavy loads. However, a relatively simple booster can be added to the output to increase the output current to  $\pm 50$  mA. This circuit, shown in Figure 30, has the added advantage that it swings the output up to the supplies, within a fraction of a volt. The increased voltage swing is particularly helpful in low voltage circuits.

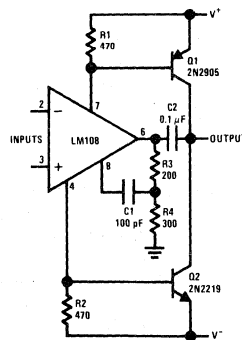


FIGURE 30. Power Booster

In Figure 30, the output transistors are driven from the supply leads of the op amp. It is important that  $R_1$  and  $R_2$  be made low enough so  $Q_1$  and  $Q_2$  are not turned on by the *worst case* quiescent current of the amplifier. The output of the op amp is loaded heavily to ground with  $R_3$  and  $R_4$ .

When the output swings about 0.5V positive, the increasing positive supply current will turn on  $Q_1$  which pulls up the load. A similar situation occurs with  $Q_2$  for negative output swings.

The bootstrapped shunt compensation shown in the figure is the only one that seems to work for all loading conditions. This capacitor,  $C_1$ , can be made inversely proportional to the closed loop gain to optimize frequency response. The value given is for a unity-gain follower connection.  $C_2$  is also required for loop stability.

The circuit does have a dead zone in the open loop transfer characteristic. However, the low frequency gain is high enough so that it can be neglected. Around 1 kHz, though, the dead zone becomes quite noticeable.

Current limiting can be incorporated into the circuit by adding resistors in series with the emitters of  $Q_1$  and  $Q_2$  because the short circuit protection of the LM108 limits the maximum voltage drop across  $R_1$  and  $R_2$ .

#### BOARD CONSTRUCTION

As indicated previously, certain precautions must be observed when building circuits that are sensitive to very low currents. If proper care is not taken, board leakage currents can easily become much larger than the error currents of the op amp. To prevent this, it is necessary to thoroughly clean printed circuit boards. Even experimental breadboards must be cleaned with trichloroethylene or alcohol to remove solder fluxes, and blown dry with compressed air. These fluxes may be insulators at low impedance levels—like in electric motors—but they certainly are not in high impedance circuits. In addition to causing gross errors, their presence can make the circuit behave erratically, especially as the temperature is changed.

At elevated temperatures, even the leakage of clean boards can be a headache. At 125°C the leakage resistance between adjacent runs on a printed circuit board is about  $10^{11}\Omega$  (0.05-inch separation parallel for 1 inch) for high quality epoxy-glass boards that have been properly cleaned. Therefore, the boards can easily produce error currents in the order of 200 pA and much more if they become contaminated. Conservative practice dictates that the boards be coated with epoxy or silicone rubber after cleaning to prevent contamination. Silicone rubber is the easiest to use. However, if the better durability of epoxy is needed, care must be taken to make sure that it gets thoroughly cured. Otherwise, the epoxy will make high temperature leakage much worse.

Care must also be exercised to insure that the circuit board is protected from condensed water

vapor when operating in the vicinity of 0°C. This can usually be accomplished by coating the board as mentioned above.

#### GUARDING

Even with properly cleaned and coated boards, leakage currents are on the verge of causing trouble at 125°C. The standard pin configuration of most IC op amps has the input pins adjacent to pins which are at the supply potentials. Therefore, it is advisable to employ guarding to reduce the voltage difference between the inputs and adjacent metal runs.


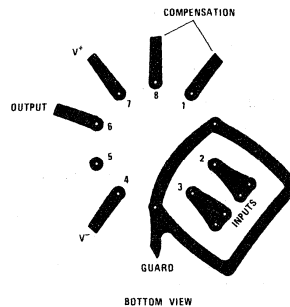



FIGURE 31. Printed Circuit Layout For Input Guarding With TO-5 Package

A board layout that includes input guarding is shown in Figure 31 for the eight lead TO-5 package. A ten-lead pin circle is used, and the leads of the IC are formed so that the holes adjacent to the inputs are vacant when it is inserted in the board. The guard, which is a conductive ring surrounding the inputs, is then connected to a low impedance point that is at the same potential as the inputs. The leakage currents from the pins at the supply potentials are absorbed by the guard. The voltage difference between the guard and the inputs can be made approximately equal to the offset voltage, reducing the effective leakage by more than three orders of magnitude. If the leads of the integrated circuit, or other components connected to the input, go through the board, it may be necessary to guard both sides.


Figure 32 shows how the guard is committed on the more-common op amp circuits. With an integrator or inverting amplifier, where the inputs are close to ground potential, the guard is simply grounded. With the voltage follower, the guard is bootstrapped to the output. If it is desirable to put a resistor in the inverting input to compensate for the source resistance, it is connected as shown in Figure 32b.

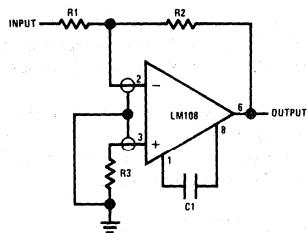

a. Inverting Amplifier

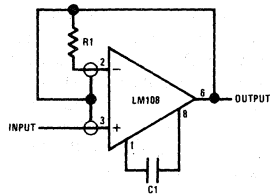

b. Follower

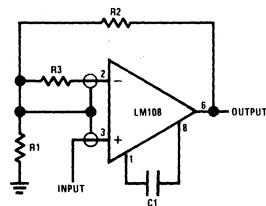

c. Non-Inverting Amplifier

FIGURE 32. Connection Of Input Guards


Guarding a non-inverting amplifier is a little more complicated. A low impedance point must be created by using relatively low value feedback resistors to determine the gain ( $R_1$  and  $R_2$  in Figure 32c). The guard is then connected to the junction of the feedback resistors. A resistor,  $R_3$ , can be connected as shown in the figure to compensate for large source resistances.

With the dual-in-line and flat packages, it is far more difficult to guard the inputs, if the standard pin configuration of the LM709 or LM101A is used, because the pin spacings on these packages are fixed. Therefore, the pin configuration of the LM108 was changed, as shown in Figure 33.

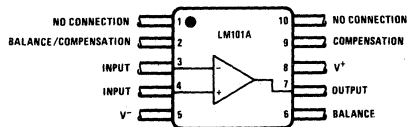
### CONCLUSIONS

IC op amps are now available that equal the input current specifications of FET amplifiers in all but the most restricted temperature range applications. At operating temperatures above  $85^\circ\text{C}$ , the IC is clearly superior as it uses bipolar transistors that make it possible to eliminate the leakage currents that plague FETs. Additionally, bipolar transistors match better than FETs, so low offset voltage and drifts can be obtained without expensive adjustments or selection. Further, the bipolar devices lend themselves more readily to low-cost monolithic construction.


These amplifiers open up new application areas and vastly improve performance in others. For example, in analog memories, holding intervals can be extended to minutes, even where  $-55^\circ\text{C}$  to  $125^\circ\text{C}$  operation is involved. Instrumentation amplifiers and low frequency waveform generators also benefit from the low error currents.



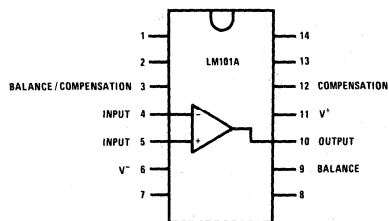
NOTE: Pin 5 Connected to bottom of package.  
TOP VIEW



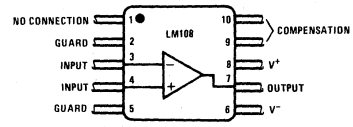NOTE: Pin 6 connected to bottom of package.  
TOP VIEW



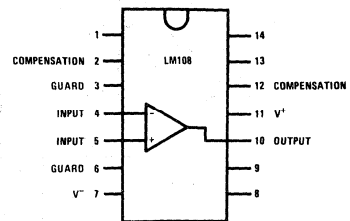NOTE: Pin 6 connected to bottom of package  
TOP VIEW



NOTE: Pin 7 connected to bottom of package  
TOP VIEW

FIGURE 33. Comparing Connection Diagrams Of The LM101A And LM108, Showing Addition Of Guarding

When operating above 85°C, overall performance is frequently limited by components other than the op amp, unless certain precautions are observed. It is generally necessary to redesign circuits using semiconductor switches to reduce the effect of their leakage currents. Further, high quality capacitors must be used, and care must be exercised in selecting large value resistors. Printed circuit board leakages can also be troublesome unless the boards are properly treated. And above 100°C, it is almost mandatory to employ guarding on the boards to protect the inputs, if the full potential of the amplifier is to be realized.

#### APPENDIX

A complete schematic of the LM108 is given in Figure A1. A description of the basic circuit is presented along with a simplified schematic earlier in the text. The purpose of this Appendix is to explain some of the more subtle features of the design.

The current source supplying the input transistors is Q<sub>29</sub>. It is designed to supply a total input stage current of 6 μA at 25°C. This current drops to 3 μA at -55°C but increases to only 7.5 μA at 125°C. This temperature characteristic tends to

compensate for the current gain falloff of the input transistors at low temperatures without creating stability problems at high temperatures.

The biasing circuitry for the input current source is nearly identical to that in the LM101A, and a complete description is given in Reference 4. However, a brief explanation follows.

A collector FET,<sup>6</sup> Q<sub>23</sub>, which has a saturation current of about 30 μA, establishes the collector current of Q<sub>24</sub>. This FET provides the initial turn-on current for the circuit and insures starting under all conditions. The purpose of R<sub>14</sub> is to compensate for production and temperature variations in the FET current. It is a collector resistor (indicated by the T through it) made of the same semiconductor material as the FET channel. As the FET current varies, the drop across R<sub>14</sub> tends to compensate for changes in the emitter base voltage of Q<sub>24</sub>.

The collector-emitter voltage of Q<sub>24</sub> is equal to the emitter base voltage of Q<sub>24</sub> plus that of Q<sub>25</sub>. This voltage is delivered to Q<sub>26</sub> and Q<sub>29</sub>. Q<sub>25</sub> and Q<sub>24</sub> are operated at substantially higher currents than Q<sub>26</sub> and Q<sub>29</sub>. Hence, there is a differential in

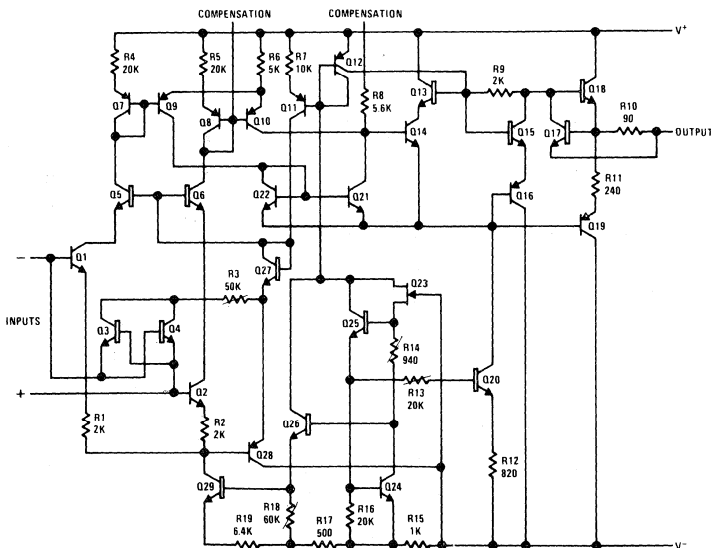


FIGURE A1. Complete Schematic Of The LM108



their emitter base voltages that is dropped across  $R_{19}$  to determine the input stage current.  $R_{18}$  is a pinched base resistor, as is indicated by the slash bar through it. This resistor, which has a large positive temperature coefficient, operates in conjunction with  $R_{17}$  to help shape the temperature characteristics of the input stage current source.

The output currents of  $Q_{26}$ ,  $Q_{25}$  and  $Q_{23}$  are fed to  $Q_{12}$ , which is a controlled-gain lateral PNP.<sup>6</sup> It delivers one-half of the combined currents to the output stage.  $Q_{11}$  is also connected to  $Q_{12}$ , with its output current set at approximately  $15 \mu\text{A}$  by  $R_7$ . Since this type of current source makes use of the emitter-base voltage differential between similar transistors operating at different collector currents, the output of  $Q_{11}$  is relatively independent of the current delivered to  $Q_{12}$ .<sup>1,2</sup> This current is used for the input stage bootstrapping circuitry.

$Q_{20}$  also supplies current to the class-B output stage. Its output current is determined by the ratio of  $R_{15}$  to  $R_{12}$  and the current through  $R_{12}$ .  $R_{13}$  is included so that the biasing circuitry is not upset when  $Q_{20}$  saturates.

One major departure from the simplified schematic is the bootstrapping of the second stage active loads,  $Q_{21}$  and  $Q_{22}$ , to the output. This makes the second stage gain dependent only on how well  $Q_9$  and  $Q_{10}$  match with variations in output voltage. Hence, the second stage gain is quite high. In fact, the overall gain of the amplifier is typically in excess of  $10^6$  at dc.

The second stage active loads drive  $Q_{14}$ . A high-gain primary transistor is used to prevent loading of the second stage. Its collector is bootstrapped by  $Q_{13}$  to operate it at zero collector-base voltage. The class-B output stage is actually driven by the emitter of  $Q_{14}$ .

A dead zone in the output stage is prevented by biasing  $Q_{18}$  and  $Q_{19}$  on the verge of conduction with  $Q_{15}$  and  $Q_{16}$ .  $R_9$  is used to compensate for the transconductance of  $Q_{15}$  and  $Q_{16}$ , making the output stage quiescent current relatively independent of the output current of  $Q_{12}$ . The drop across this resistor also reduces quiescent current.

For positive-going outputs, short circuit protection is provided by  $R_{10}$  and  $Q_{17}$ . When the voltage drop across  $R_{10}$  turns on  $Q_{17}$ , it removes base drive from  $Q_{18}$ . For negative-going outputs, current limiting is initiated when the voltage drop across  $R_{11}$  becomes large enough for the collector base junction of  $Q_{17}$  to become forward biased. When this happens, the base of  $Q_{19}$  is clamped so the output current cannot increase further.

Input protection is provided by  $Q_3$  and  $Q_4$  which act as clamp diodes between the inputs. The collectors of these transistors are bootstrapped to the emitter of  $Q_{28}$  through  $R_3$ . This keeps the collector-isolation leakage of the transistors from showing up on the inputs.  $R_3$  is included so that the bootstrapping is not disrupted when  $Q_3$  or  $Q_4$  saturate with an input overload. Current-limiting resistors were not connected in series with the inputs, since diffused resistors cannot be employed such that they work effectively, without causing high temperature leakages.

**Table I. Typical Performance of the LM108 Operational Amplifier ( $T_A = 25^\circ\text{C}$  and  $V_S = \pm 15\text{V}$ ).**

Input Offset Voltage	0.7 mV
Input Offset Current	50 pA
Input Bias Current	0.8 nA
Input Resistance	70 M $\Omega$
Input Common Mode Range	$\pm 14\text{V}$
Common Mode Rejection	100 dB
Offset Voltage Drift	3 $\mu\text{V}/^\circ\text{C}$
Offset Current Drift	0.5 pA/ $^\circ\text{C}$
Voltage Gain	300V/mV
Small Signal Bandwidth	1.0 MHz
Slew Rate	0.3V/ $\mu\text{s}$
Output Swing	$\pm 14\text{V}$
Supply Current	300 $\mu\text{A}$
Power Supply Rejection	100 dB
Operating Voltage Range	$\pm 2\text{V}$ to $\pm 20\text{V}$

## REFERENCES

1. R. J. Widlar, "Future Trends in Integrated Operational Amplifiers," *EDN*, Vol. 13, No. 6, pp. 24-29, June, 1968.
2. R. J. Widlar, "Super Gain Transistors for ICs," *IEEE Journal of Solid-State Circuits*, Vol. SC-4, No. 4, August, 1969.
3. R. J. Widlar, "A Unique Circuit Design for a High Performance Operational Amplifier Especially Suited to Monolithic Construction," *Proc. of NEC*, Vol. XXI, pp. 85-89, October, 1965.
4. R. J. Widlar, "I.C. Op Amp with Improved Input-Current Characteristics," *EEE*, pp. 38-41, December, 1968.
5. R. J. Widlar, "Linear IC's: part 6; Compensating for Drift," *Electronics*, Vol. 41, No. 3, pp. 90-93, February, 1968.

6. R. J. Widlar, "Design Techniques for Monolithic Operational Amplifiers," *IEEE Journal of Solid-State Circuits*, Vol. SC-4, No. 4, August, 1969.
7. D. R. Sullivan and M. A. Maidique, "Characterization and Application of a New High Input Impedance Monolithic Amplifier," *Transitron Electronic Corporation Application Brief*.
8. Paul C. Dow, Jr., "An Analysis of Certain Errors in Electronic Differential Analyzers, II—Capacitor Dielectric Absorption," *IRE Trans. on Electronic Computers*, pp. 17-22, March, 1958.
9. R. J. Widlar, "A Fast Integrated Voltage Follower with Low Input Current," *Microelectronics*, Vol. 1, No. 7, June, 1968.
10. R. C. Dobkin, "Feedforward Compensation Speeds Op Amp," *National Semiconductor LB-2*, March, 1969.
11. R. J. Widlar, "A New Low Voltage Breakdown Diode," *National Semiconductor TP-5*, April, 1968.
12. R. J. Widlar, "Some Circuit Design Techniques for Linear Integrated Circuits," *IEEE Transactions on Circuit Theory*, Vol. CT-12, No. 4, pp. 586-590, December, 1965.

# Log Converters

National Semiconductor  
Application Note 30  
Robert C. Dobkin  
November 1969



One of the most predictable non-linear elements commonly available is the bipolar transistor. The relationship between collector current and emitter base voltage is precisely logarithmic from currents below one picoamp to currents above one milliamp. Using a matched pair of transistors and integrated circuit operational amplifiers, it is relatively easy to construct a linear to logarithmic converter with a dynamic range in excess of five decades.

The circuit in Figure 1 generates a logarithmic output voltage for a linear input current. Transistor  $Q_1$  is used as the non-linear feedback element around an LM108 operational amplifier. Negative feedback is applied to the emitter of  $Q_1$  through divider,  $R_1$  and  $R_2$ , and the emitter base junction of  $Q_2$ . This forces the collector current of  $Q_1$  to be exactly equal to the current through the input resistor. Transistor  $Q_2$  is used as the feedback element of an LM101A operational amplifier. Negative feedback forces the collector current of  $Q_2$  to equal the current through  $R_3$ . For the values shown, this current is  $10 \mu\text{A}$ . Since the collector current of  $Q_2$  remains constant, the emitter base voltage also remains constant. Therefore, only the  $V_{BE}$  of  $Q_1$  varies with a change of input current. However, the output voltage is a function of the difference in emitter base voltages of  $Q_1$  and  $Q_2$ :

$$E_{OUT} = \frac{R_1 + R_2}{R_2} (V_{BE2} - V_{BE1}). \quad (1)$$

For matched transistors operating at different collector currents, the emitter base differential is given by

$$\Delta V_{BE} = \frac{kT}{q} \log_e \frac{I_{C1}}{I_{C2}}, \quad (2)$$

where  $k$  is Boltzmann's constant,  $T$  is temperature in degrees Kelvin and  $q$  is the charge of an elec-

tron. Combining these two equations and writing the expression for the output voltage gives

$$E_{OUT} = \frac{-kT}{q} \left[ \frac{R_1 + R_2}{R_2} \right] \log_e \left[ \frac{E_{IN} R_3}{E_{REF} R_{IN}} \right] \quad (3)$$

for  $E_{IN} \geq 0$ . This shows that the output is proportional to the logarithm of the input voltage. The coefficient of the log term is directly proportional to absolute temperature. Without compensation, the scale factor will also vary directly with temperature. However, by making  $R_2$  directly proportional to temperature, constant gain is obtained. The temperature compensation is typically 1% over a temperature range of  $-25^\circ\text{C}$  to  $100^\circ\text{C}$  for the resistor specified. For limited temperature range applications, such as  $0^\circ\text{C}$  to  $50^\circ\text{C}$ , a  $430\Omega$  sensistor in series with a  $570\Omega$  resistor may be substituted for the  $1\text{K}$  resistor, also with 1% accuracy. The divider,  $R_1$  and  $R_2$ , sets the gain while the current through  $R_3$  sets the zero. With the values given, the scale factor is  $1\text{V}/\text{decade}$  and

$$E_{OUT} = - \left[ \log_{10} \left| \frac{E_{IN}}{R_{IN}} \right| + 5 \right] \quad (4)$$

where the absolute value sign indicates that the dimensions of the quantity inside are to be ignored.

Log generator circuits are not limited to inverting operation. In fact, a feature of this circuit is the ease with which non-inverting operation is obtained. Supplying the input signal to  $A_2$  and the reference current to  $A_1$  results in a log output that is not inverted from the input. To achieve the same 100 dB dynamic range in the non-inverting configuration, an LM108 should be used for  $A_2$ , and an LM101A for  $A_1$ . Since the LM108 cannot use feedforward compensation, it is frequency compensated with the standard 30 pF capacitor.

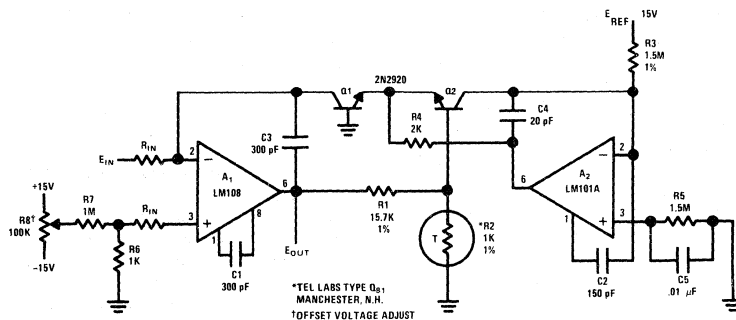


FIGURE 1. Log Generator with 100 dB Dynamic Range

The only other change is the addition of a clamp diode connected from the emitter of  $Q_1$  to ground. This prevents damage to the logging transistors if the input signal should go negative.

The log output is accurate to 1% for any current between 10 nA and 1 mA. This is equivalent to about 3% referred to the input. At currents over 500  $\mu$ A the transistors used deviate from log characteristics due to resistance in the emitter, while at low currents, the offset current of the LM108 is the major source of error. These errors occur at the ends of the dynamic range, and from 40 nA to 400  $\mu$ A the log converter is 1% accurate referred to the input. Both of the transistors are used in the grounded base connection, rather than the diode connection, to eliminate errors due to base current. Unfortunately, the grounded base connection increases the loop gain. More frequency compensation is necessary to prevent oscillation, and the log converter is necessarily slow. It may take 1 to 5 ms for the output to settle to 1% of its final value. This is especially true at low currents.

the transfer function. With the values shown the scale factor is 1V/decade and

$$E_{OUT} = - \left[ \log_{10} \left| \frac{E_{IN}}{R_{IN}} \right| + 4 \right] \quad (5)$$

from less than 100 nA to 1 mA.

Anti-log or exponential generation is simply a matter of rearranging the circuitry. Figure 3 shows the circuitry of the log converter connected to generate an exponential output from a linear input. Amplifier  $A_1$  in conjunction with transistor  $Q_1$  drives the emitter of  $Q_2$  in proportion to the input voltage. The collector current of  $Q_2$  varies exponentially with the emitter-base voltage. This current is converted to a voltage by amplifier  $A_2$ . With the values given

$$E_{OUT} = 10^{-[E_{IN}]} \quad (6)$$

Many non-linear functions such as  $X^{1/2}$ ,  $X^2$ ,  $X^3$ ,  $1/X$ ,  $XY$ , and  $X/Y$  are easily generated with the use of logs. Multiplication becomes addition, division

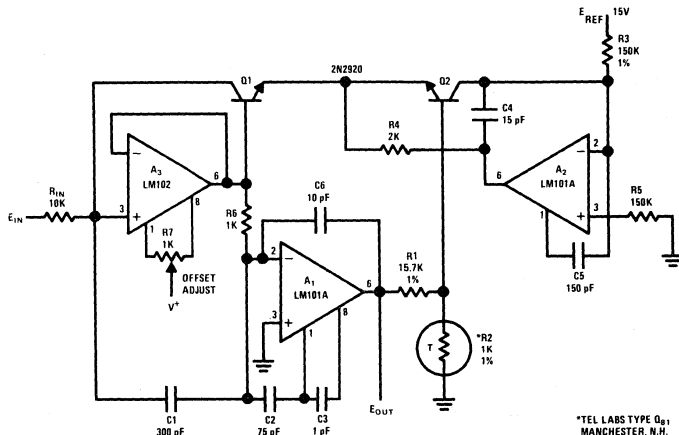


FIGURE 2. Fast Log Generator

The circuit shown in Figure 2 is two orders of magnitude faster than the previous circuit and has a dynamic range of 80 dB. Operation is the same as the circuit in Figure 1, except the configuration optimizes speed rather than dynamic range. Transistor  $Q_1$  is diode connected to allow the use of feedforward compensation<sup>1</sup> on an LM101A operational amplifier. This compensation extends the bandwidth to 10 MHz and increases the slew rate. To prevent errors due to the finite  $h_{FE}$  of  $Q_1$  and the bias current of the LM101A, an LM102 voltage follower buffers the base current and input current. Although the log circuit will operate without the LM102, accuracy will degrade at low input currents. Amplifier  $A_2$  is also compensated for maximum bandwidth. As with the previous log converter,  $R_1$  and  $R_2$  control the sensitivity; and  $R_3$  controls the zero crossing of

becomes subtraction and powers become gain coefficients of log terms. Figure 4 shows a circuit whose output is the cube of the input. Actually, any power function is available from this circuit by changing the values of  $R_9$  and  $R_{10}$  in accordance with the expression:

$$E_{OUT} = E_{IN} \frac{16.7 R_9}{R_9 + R_{10}} \quad (7)$$

Note that when log and anti-log circuits are used to perform an operation with a linear output, no temperature compensating resistors at all are needed. If the log and anti-log transistors are at the same temperature, gain changes with temperature cancel. It is a good idea to use a heat sink which couples the two transistors to minimize thermal gradients. A 1°C temperature difference between

the log and anti-log transistors results in a 0.3% error. Also, in the log converters, a 1°C difference between the log transistors and the compensating resistor results in a 0.3% error.

Either of the circuits in Figures 1 or 2 may be used as dividers or reciprocal generators. Equation 3 shows the outputs of the log generators are actually the ratio of two currents: the input current and the current through  $R_3$ . When used as a log

tional to the log of  $E_1/E_2$ . Transistor  $Q_3$  adds a voltage proportional to the log of  $E_3$  and drives the anti-log transistor,  $Q_4$ . The collector current of  $Q_4$  is converted to an output voltage by  $A_4$  and  $R_7$ , with the scale factor set by  $R_7$  at  $E_1 E_3/10E_2$ .

Measurement of transistor current gains over a wide range of operating currents is an application particularly suited to log multiplier/dividers. Using the circuit in Figure 5, PNP current gains can be

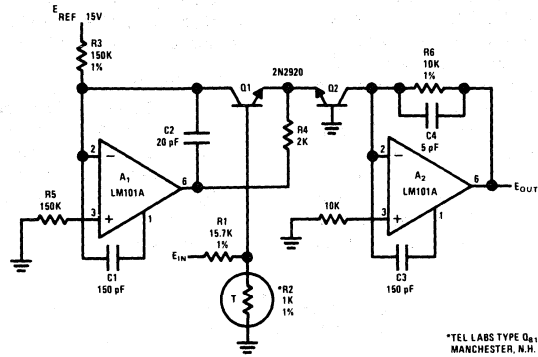


FIGURE 3. Anti-log Generator

generator, the current through  $R_3$  was held constant by connecting  $R_3$  to a fixed voltage. Hence, the output was just the log of the input. If  $R_3$  is driven by an input voltage, rather than the 15V reference, the output of the log generator is the log ratio of the input current to the current through  $R_3$ . The anti-log of this voltage is the quotient. Of course, if the divisor is constant, the output is the reciprocal.

measured at currents from  $0.4 \mu A$  to 1 mA. The collector current is the input signal to  $A_1$ , the base current is the input signal to  $A_2$ , and a fixed voltage to  $R_5$  sets the scale factor. Since  $A_2$  holds the base at ground, a single resistor from the emitter to the positive supply is all that is needed to establish the operating current. The output is proportional to collector current divided by base current, or  $h_{FE}$ .

A complete one quadrant multiplier/divider is shown in Figure 5. It is basically the log generator shown in Figure 1 driving the anti-log generator shown in Figure 3. The log generator output from  $A_1$  drives the base of  $Q_3$  with a voltage propor-

In addition to their application in performing functional operations, log generators can provide a significant increase in the dynamic range of signal processing systems. Also, unlike a linear system, there is no loss in accuracy or resolution when the

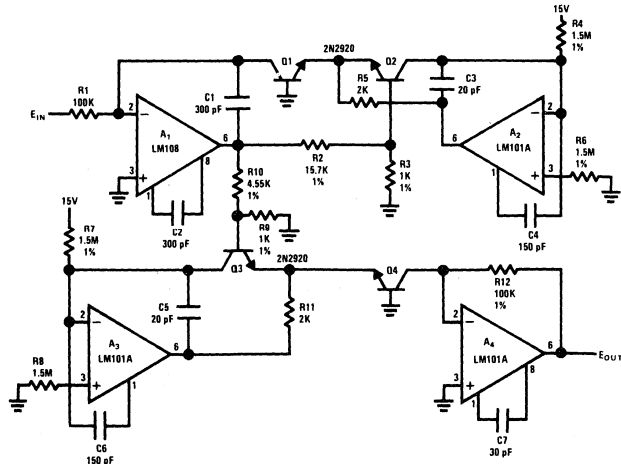


FIGURE 4. Cube Generator

input signal is small compared to full scale. Over most of the dynamic range, the accuracy is a percent-of-signal rather than a percent-of-full-scale. For example, using log generators, a simple meter can display signals with 100 dB dynamic range or an oscilloscope can display a 10 mV and 10V pulse simultaneously. Obviously, without the log generator, the low level signals are completely lost.

To achieve wide dynamic range with high accuracy, the input operational amplifier necessarily must have low offset voltage, bias current and offset current. The LM108 has a maximum bias current of  $3\text{ nA}$  and offset current of  $400\text{ pA}$  over a  $-55^{\circ}\text{C}$  to  $125^{\circ}\text{C}$  temperature range. By using equal source resistors, only the offset current of the LM108 causes an error. The offset current of the LM108 is as low as many FET amplifiers. Further, it has a low and constant temperature coefficient rather than doubling every  $10^{\circ}\text{C}$ . This results in greater accuracy over temperature than can be achieved with FET amplifiers. The offset voltage may be

zeroed, if necessary, to improve accuracy with low input voltages.

The log converters are low level circuits and some care should be taken during construction. The input leads should be as short as possible and the input circuitry guarded against leakage currents. Solder residues can easily conduct leakage currents, therefore circuit boards should be cleaned before use. High quality glass or mica capacitors should be used on the inputs to minimize leakage currents. Also, when the  $+15\text{V}$  supply is used as a reference, it must be well regulated.

#### REFERENCES:

1. R. C. Dobkin, "Feedforward Compensation Speeds Op Amp," National Semiconductor Corporation, Linear Brief 2, April, 1969.
2. R. J. Widlar, "Monolithic Operational Amplifiers—The Universal Linear Component," National Semiconductor Corporation, AN-4, April, 1968.

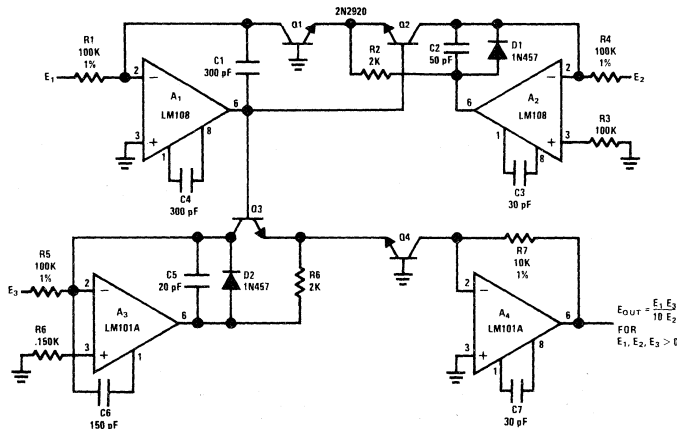



FIGURE 5. Multiplier/Divider

# Op Amp Circuit Collection


National Semiconductor  
Application Note 31  
Robert C. Dobkin  
February 1978




## section 1 — basic circuits

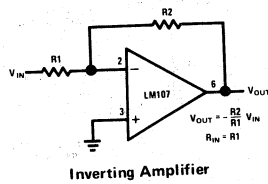


Inverting Amplifier

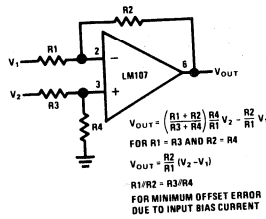


Difference Amplifier

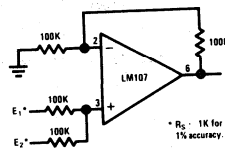


Non-Inverting Summing Amplifier

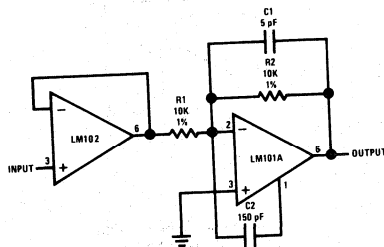

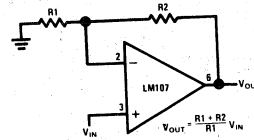
Fast Inverting Amplifier With High Input Impedance




Non-Inverting Amplifier

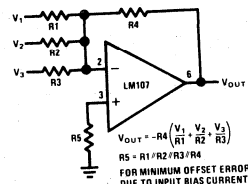


Inverting Summing Amplifier

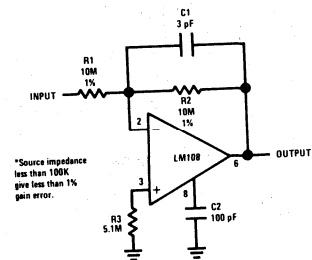

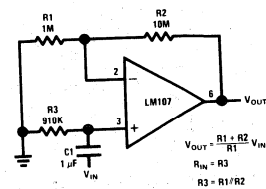
Inverting Amplifier with High Input Impedance




Non-Inverting AC Amplifier

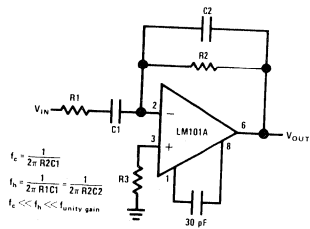


Practical Differentiator

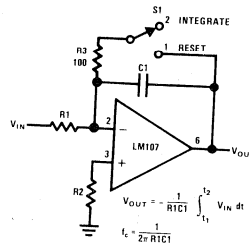


Integrator

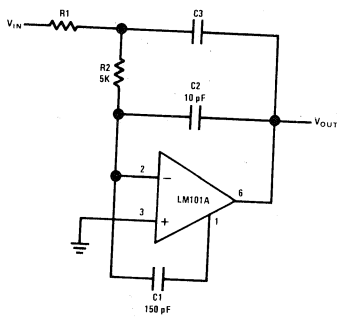


Fast Integrator

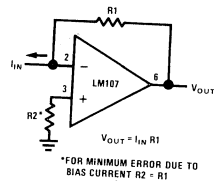

Current to Voltage Converter

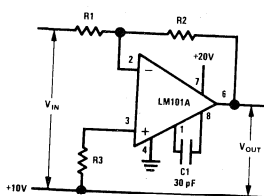


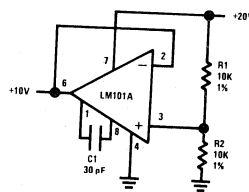Circuit for Operating the LM101 without a Negative Supply




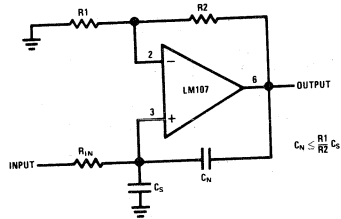Circuit for Generating the Second Positive Voltage






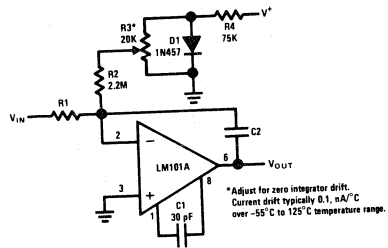Neutralizing Input Capacitance to Optimize Response Time




Integrator with Bias Current Compensation

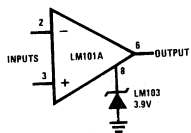
\*Adjust for zero integrator drift. Current drift typically 0.1 nA/°C over -55°C to 125°C temperature range.



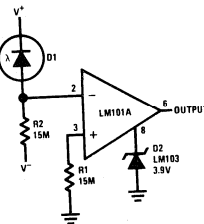Voltage Comparator for Driving DTL or TTL Integrated Circuits




Threshold Detector for Photodiodes

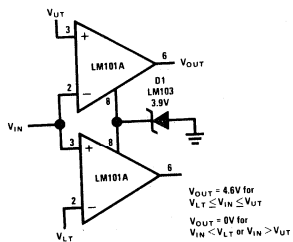


Double-Ended Limit Detector

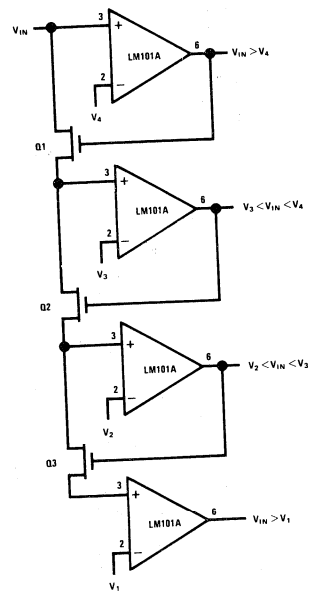
$V_{OUT} = 4.5V$  for  $V_{LT} \leq V_{IN} \leq V_{UT}$   
 $V_{OUT} = 0V$  for  $V_{IN} < V_{LT}$  or  $V_{IN} > V_{UT}$




Multiple Aperture Window Discriminator

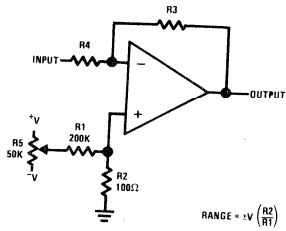

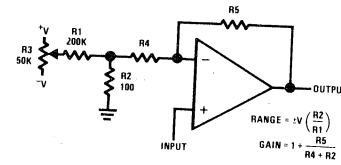
Offset Voltage Adjustment for Inverting Amplifiers Using Any Type of Feedback Element



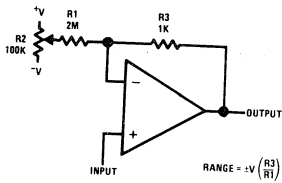
Offset Voltage Adjustment for Non-Inverting Amplifiers



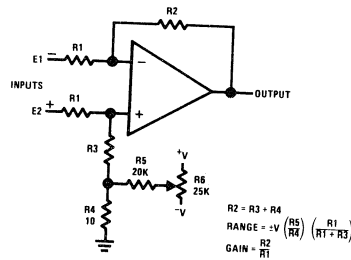Offset Voltage Adjustment for Voltage Followers




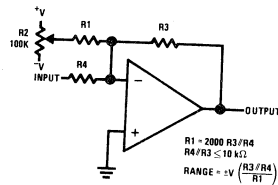Offset Voltage Adjustment for Differential Amplifiers




Offset Voltage Adjustment for Inverting Amplifiers Using 10 kΩ Source Resistance or Less


## section 2 – signal generation

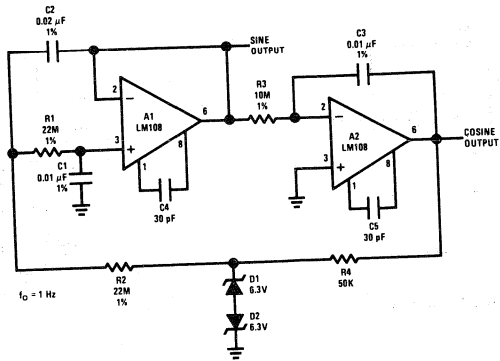

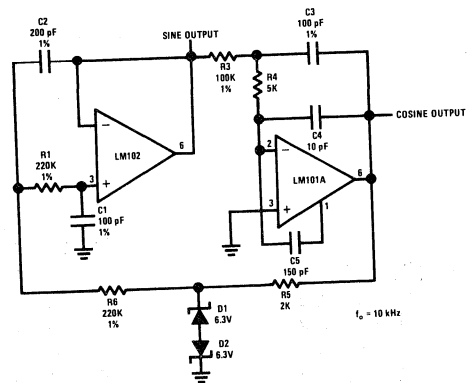
Low Frequency Sine Wave Generator with Quadrature Output



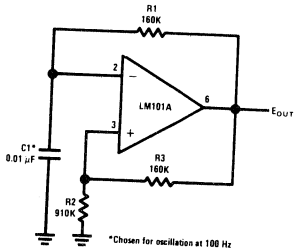
High Frequency Sine Wave Generator with Quadrature Output




Free-Running Multivibrator

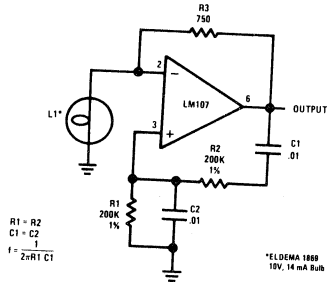


Wein Bridge Sine Wave Oscillator

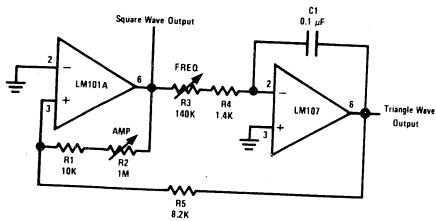


Function Generator

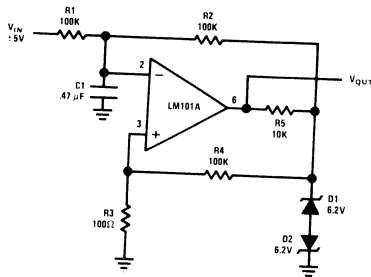


Pulse Width Modulator

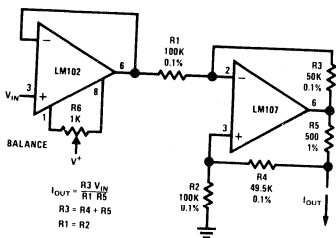



Bilateral Current Source

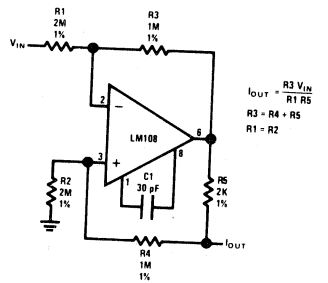


Bilateral Current Source

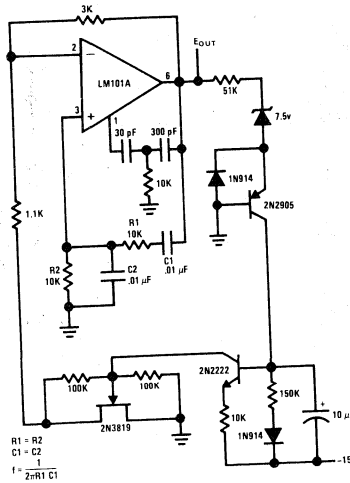

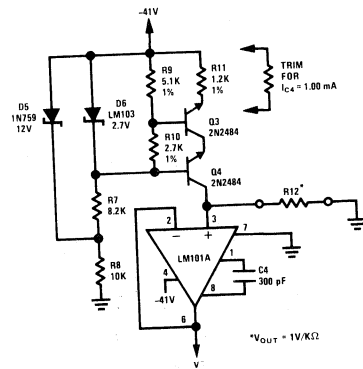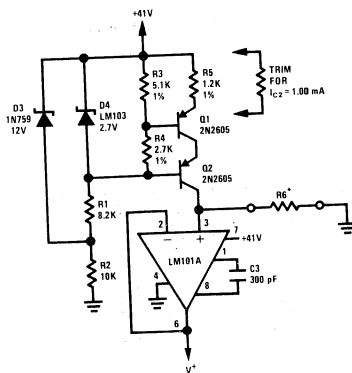
Wein Bridge Oscillator with FET Amplitude Stabilization



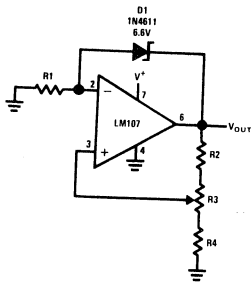
Low Power Supply for Integrated Circuit Testing




Positive Voltage Reference

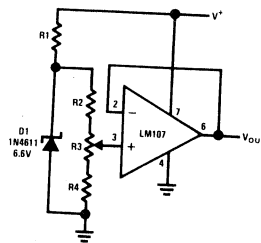


Positive Voltage Reference

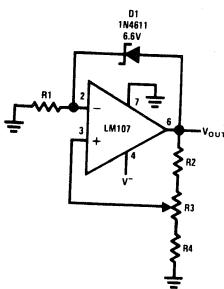

Negative Voltage Reference

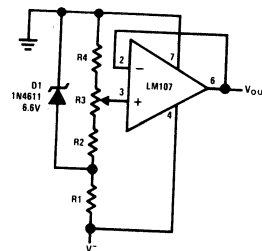


Negative Voltage Reference

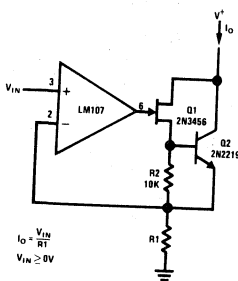

$$I_o = \frac{V_{IN}}{R_1}$$

$$V_{IN} \geq 0V$$

Precision Current Sink

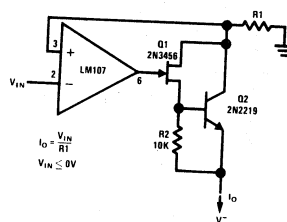


$$I_o = \frac{V_{IN}}{R_1}$$


$$V_{IN} \leq 0V$$

Precision Current Source


## section 3 — signal processing

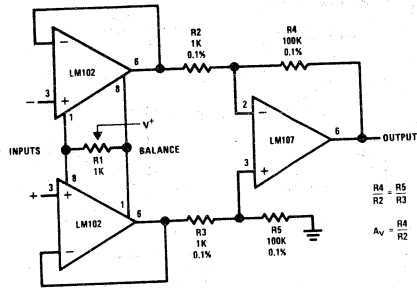

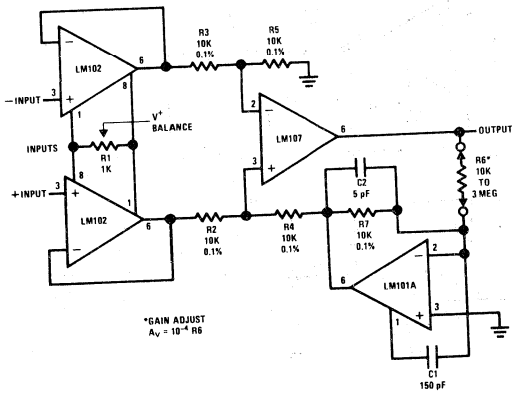
Differential-Input Instrumentation Amplifier



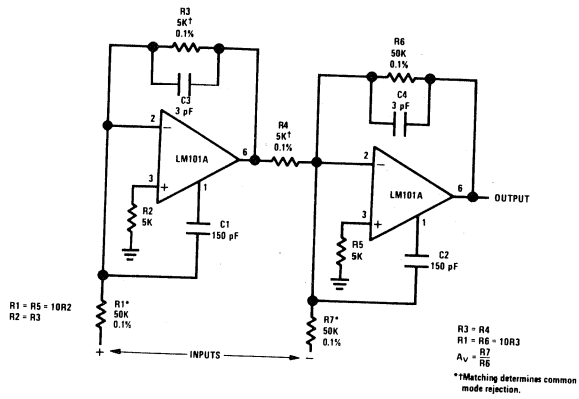Variable Gain, Differential-Input Instrumentation Amplifier




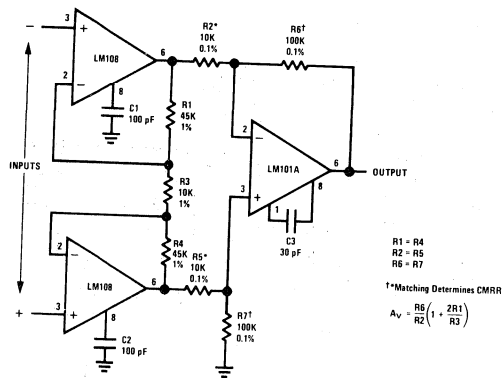Instrumentation Amplifier with  $\pm 100$  Volt Common Mode Range




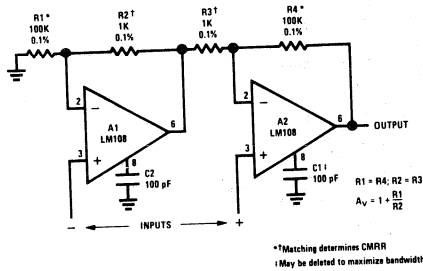Differential Input Instrumentation Amplifier with High Common Mode Rejection






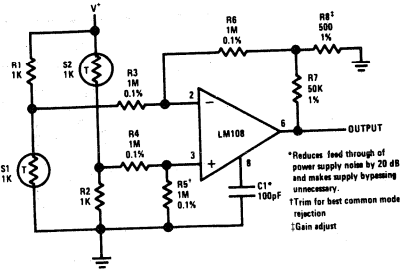
High Input Impedance Instrumentation Amplifier



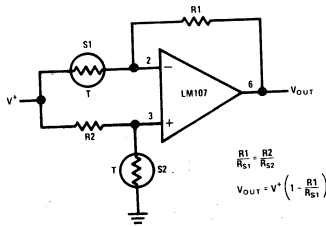
Bridge Amplifier with Low Noise Compensation




Bridge Amplifier

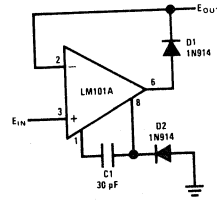


Precision Diode

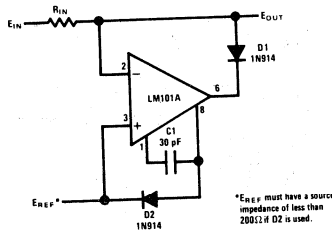


Precision Clamp

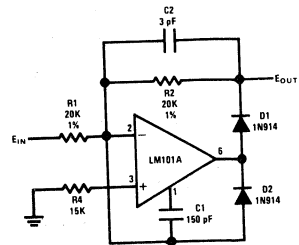


Fast Half Wave Rectifier

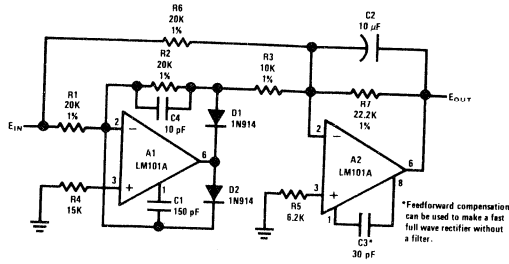


Precision AC to DC Converter

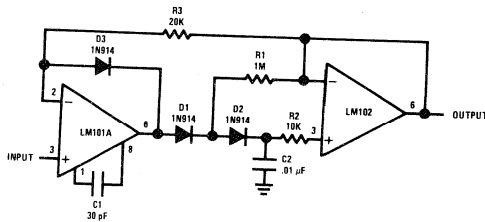


Low Drift Peak Detector

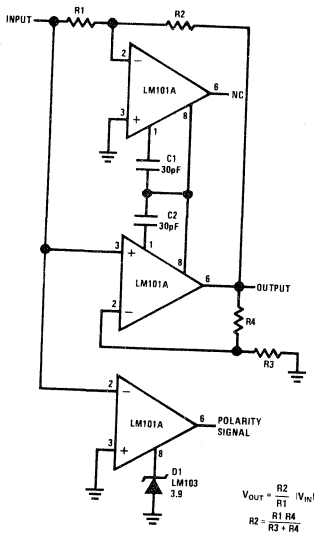

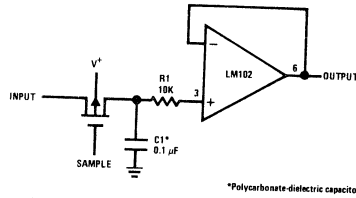
Absolute Value Amplifier with Polarity Detector



Sample and Hold

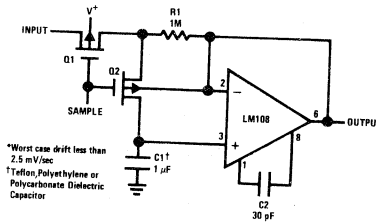


Sample and Hold

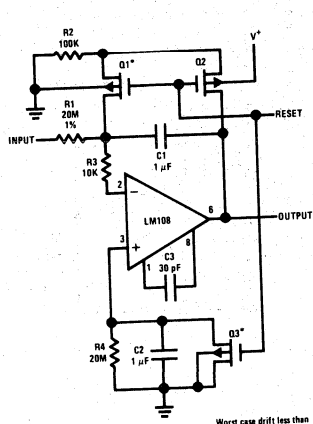

\*D1 and D3 should not have internal gate-protection diodes.

Worst case drift less than 500 μV/sec over -55°C to +125°C.


Low Drift Integrator

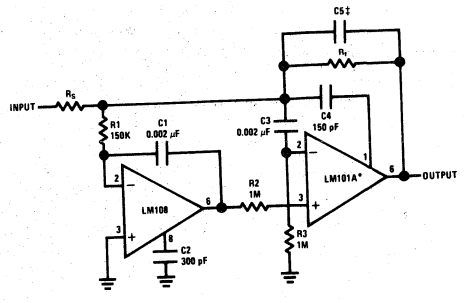


\* In addition to increasing speed, the LM101A raises high and low frequency gain, increases output drive capability and eliminates thermal feedback.

† Power Bandwidth: 250 KHz  
Small Signal Bandwidth: 3.5 MHz  
Slew Rate: 10V/μs  
‡  $C_5 = 6 \times 10^{-6} \frac{R_1}{R_2}$

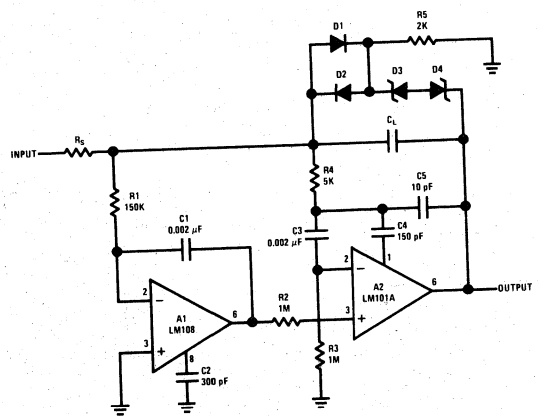
Fast<sup>†</sup> Summing Amplifier with Low Input Current




Fast Integrator with Low Input Current

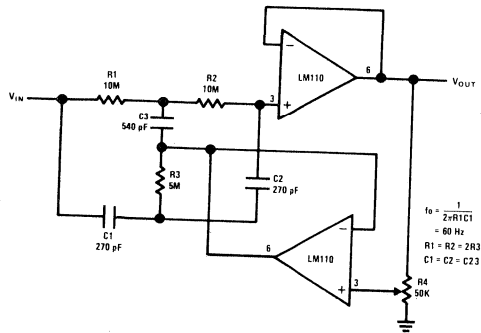


Adjustable Q Notch Filter

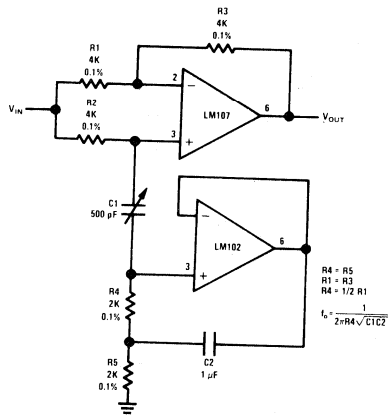


Easily Tuned Notch Filter

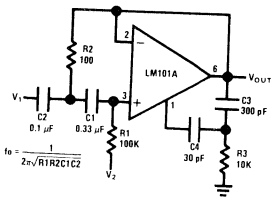


Tuned Circuit

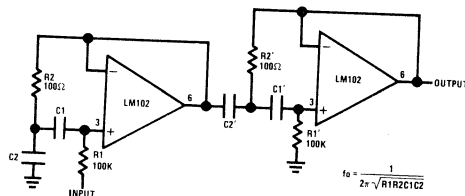


Two-Stage Tuned Circuit

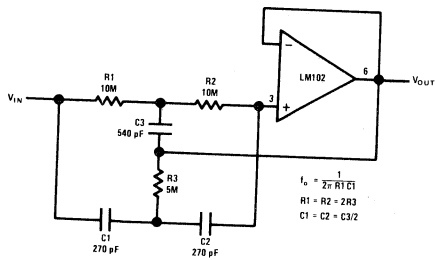


High Q Notch Filter

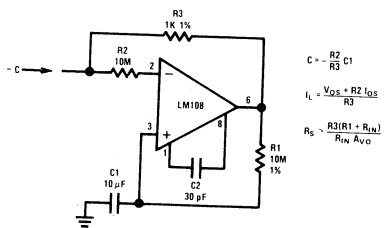


Negative Capacitance Multiplier

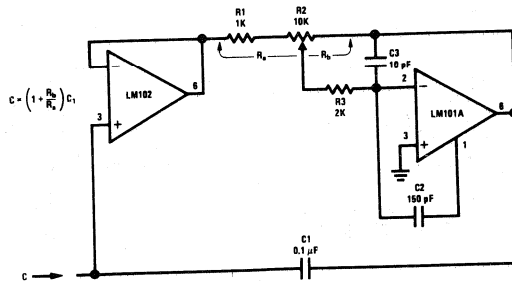


Variable Capacitance Multiplier

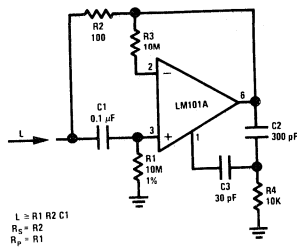


Simulated Inductor

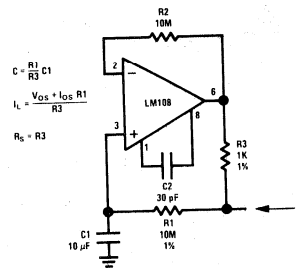


Capacitance Multiplier

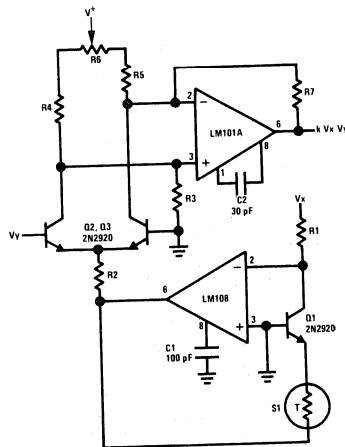

Two Quadrant Multiplier

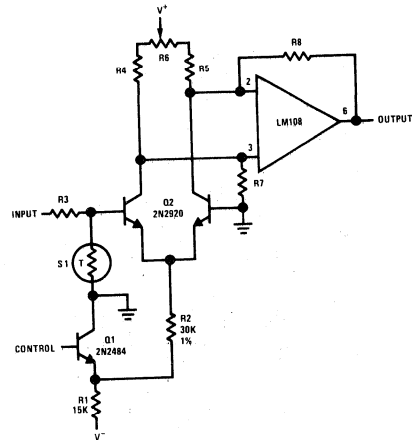


Voltage Controlled Gain Circuit

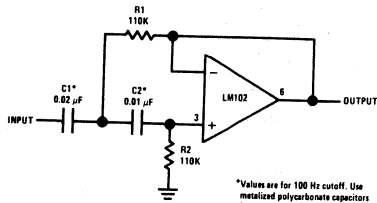


\*Values are for 100 Hz cutoff. Use metallized polycarbonate capacitors for good temperature stability.

High Pass Active Filter

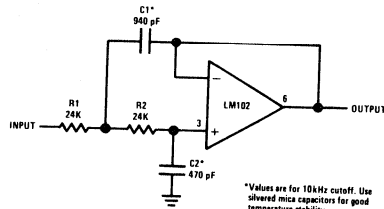


\*Values are for 10kHz cutoff. Use silvered mica capacitors for good temperature stability.


Low Pass Active Filter

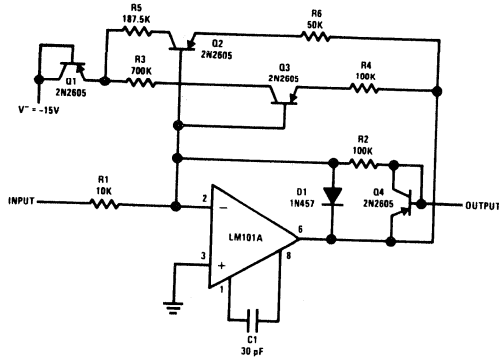

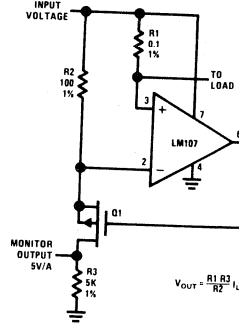
Nonlinear Operational Amplifier with Temperature Compensated Breakpoints



Current Monitor

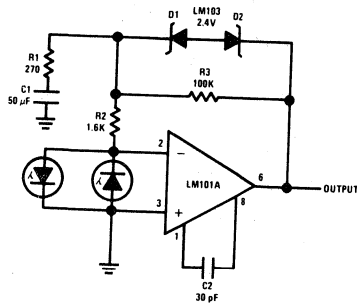


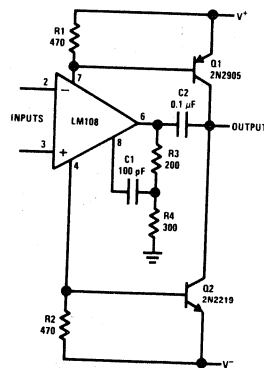Saturating Servo Preamplifier with Rate Feedback




Power Booster



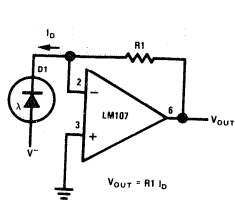


Photodiode Amplifier

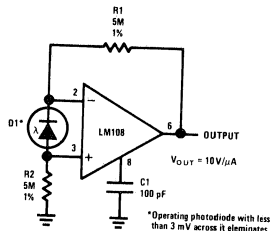


Photodiode Amplifier

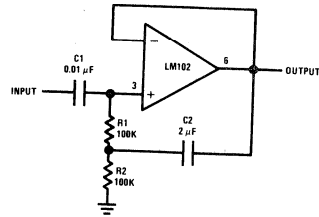\*Operating photodiode with less than 3 mV across it eliminates leakage currents.




High Input Impedance AC Follower

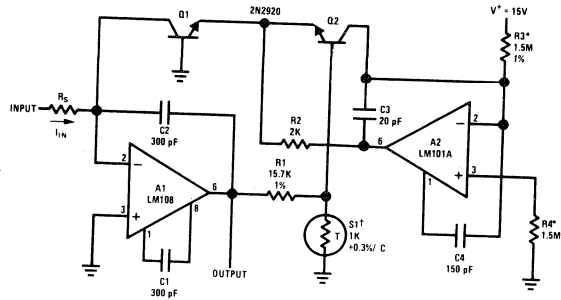

10 nA < I<sub>N</sub> < 1 mA  
Sensitivity is 1V per decade.

†Available from Tel Labs, Inc.,  
Manchester, N.H., Type 081.  
\*Determines current for zero  
crossing on output: 10 μA  
as shown.

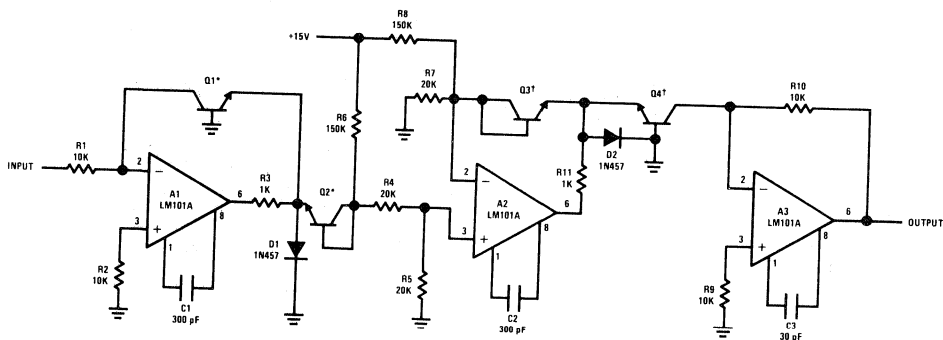
Temperature Compensated Logarithmic Converter




Root Extractor

\* 12N3728 matched pairs




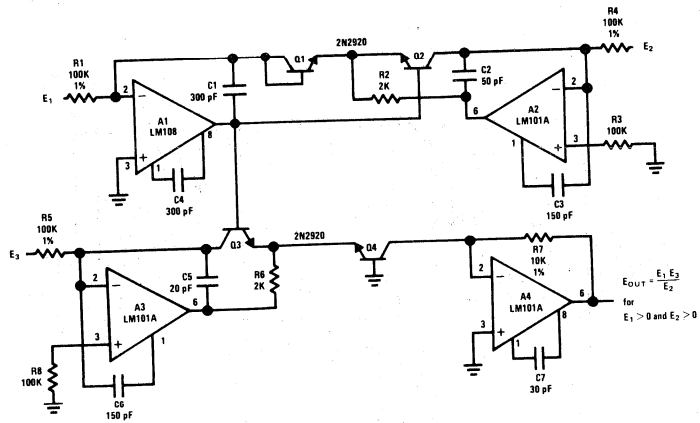

Multiplier/Divider

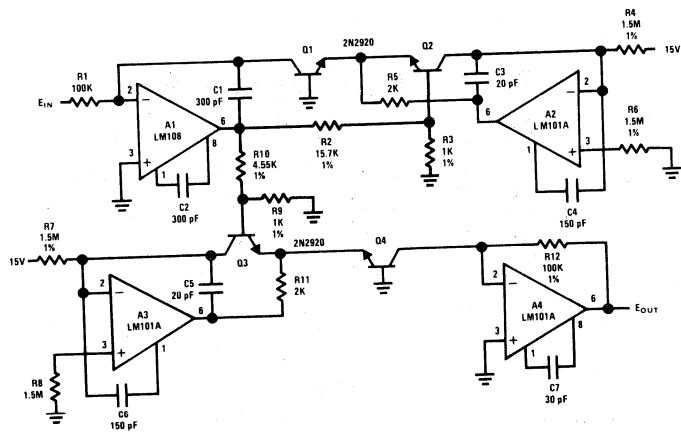


Cube Generator

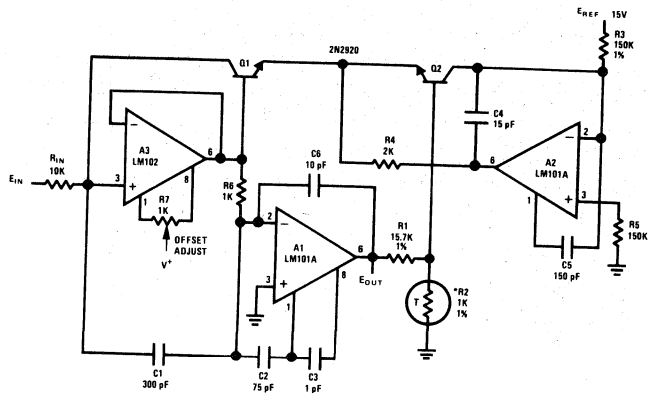

\*Tel-Labs Type Q81  
Manchester, N.H.

Fast Log Generator

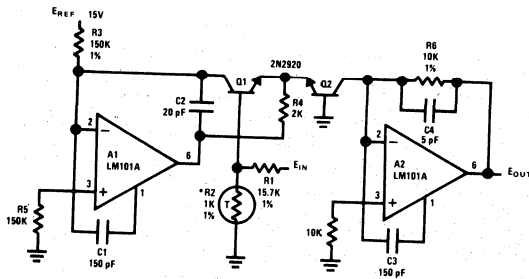


\*Tel-Labs Type Q81  
Manchester, N.H.

Anti-log Generator

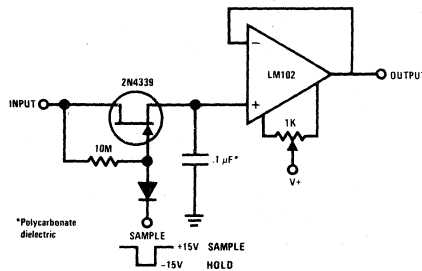
# FET Circuit Applications

National Semiconductor  
Application Note 32  
February 1970




Sample and Hold With Offset Adjustment

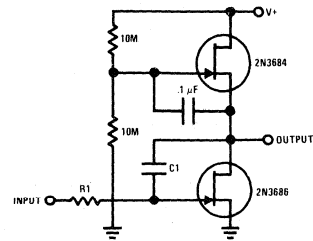The 2N4339 JFET was selected because of its low  $I_{GSS}$  ( $<100$  pA), very-low  $I_{D(OFF)}$  ( $<50$  pA) and low pinchoff voltage. Leakages of this level put the burden of circuit performance on clean, solder-resin free, low leakage circuit layout.




JFET AC Coupled Integrator

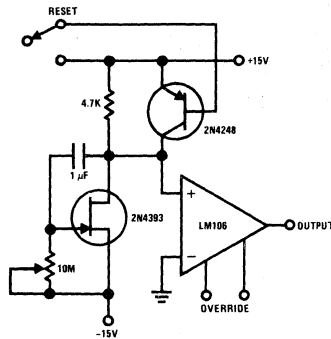This circuit utilizes the "μ-amp" technique to achieve very high voltage gain. Using  $C_1$  in the circuit as a Miller integrator, or capacitance multiplier, allows this simple circuit to handle very long time constants.




Long Time Comparator

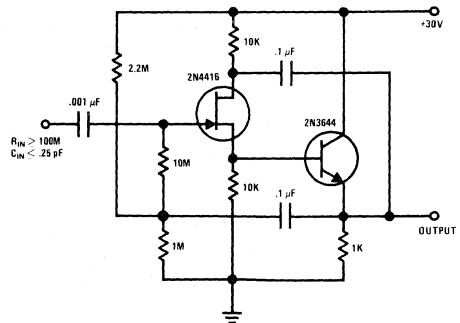The 2N4393 is operated as a Miller integrator. The high  $Y_{fs}$  of the 2N4393 (over 12,000 μmhos @ 5 mA) yields a stage gain of about 60. Since the equivalent capacitance looking into the gate is  $C$  times gain and the gate source resistance can be as high as 10 MΩ, time constants as long as a minute can be achieved.




Ultra-High  $Z_{IN}$  AC Unity Gain Amplifier

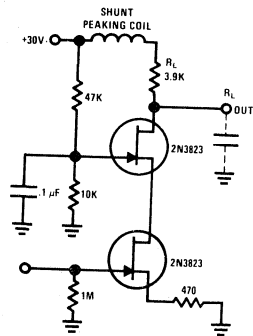Nothing is left to chance in reducing input capacitance. The 2N4416, which has low capacitance in the first place, is operated as a source follower with bootstrapped gate bias resistor and drain. Any input capacitance you get with this circuit is due to poor layout techniques.




FET Cascode Video Amplifier

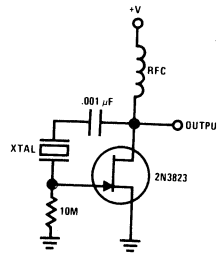The FET cascode video amplifier features very low input loading and reduction of feedback to almost zero. The 2N3823 is used because of its low capacitance and high  $Y_{fs}$ . Bandwidth of this amplifier is limited by  $R_L$  and load capacitance.



JFET Pierce Crystal Oscillator

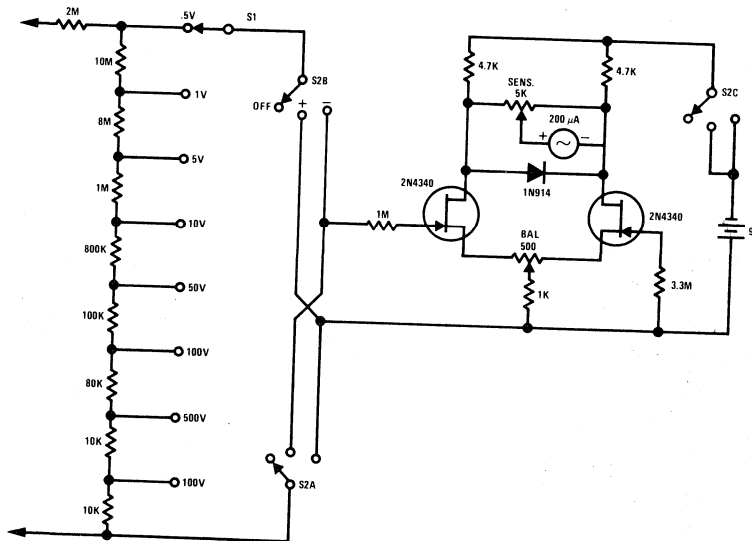
The JFET Pierce crystal oscillator allows a wide frequency range of crystals to be used without circuit modification. Since the JFET gate does not load the crystal, good  $Q$  is maintained thus insuring good frequency stability.



FETVM-FET Voltmeter

This FETVM replaces the function of the VTVM while at the same time ridding the instrument of the usual line cord. In addition, drift rates are far superior to vacuum tube circuits allowing a 0.5 volt

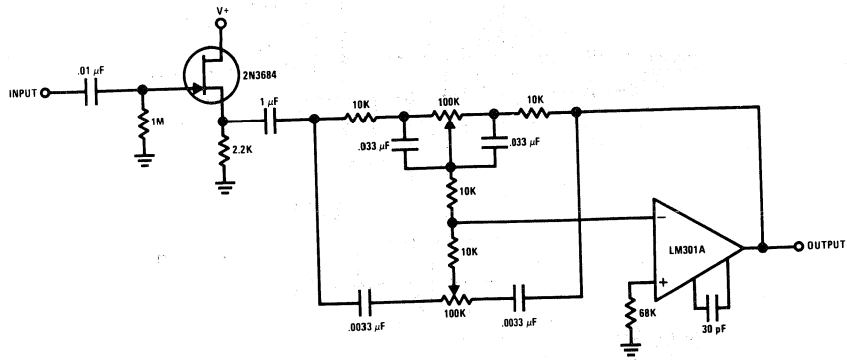
full scale range which is impractical with most vacuum tubes. The low-leakage, low-noise 2N4340 is an ideal device for this application.



HI-FI Tone Control Circuit (High Z Input)

The 2N3684 JFET provides the function of a high input impedance and low noise characteristics to

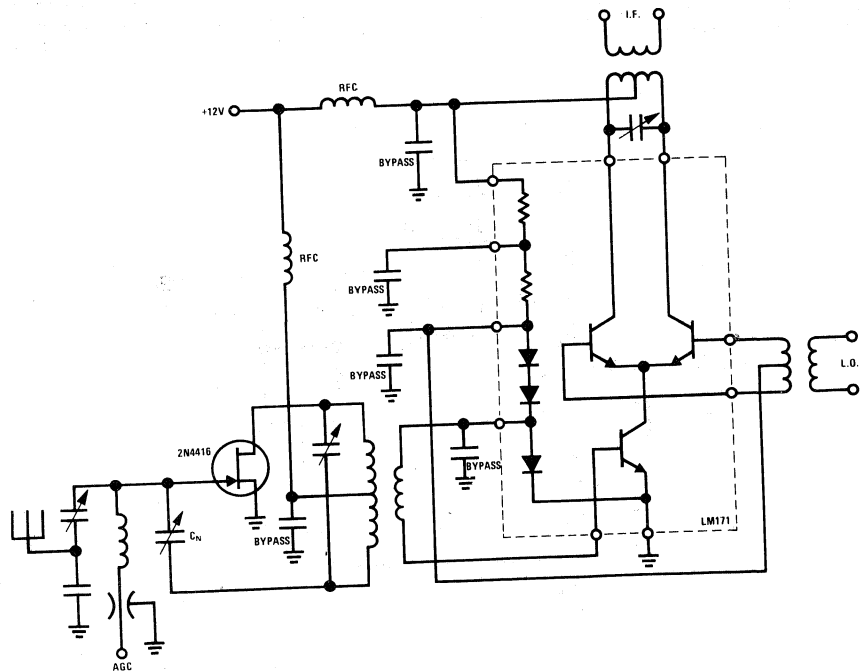
buffer an op amp-operated feedback type tone control circuit.



100 MHz Converter

The 2N4416 JFET will provide noise figures of less than 3 dB and power gain of greater than 20 dB. The JFET's outstanding low crossmodulation and low intermodulation distortion provides an ideal characteristic for an input stage. The output feeds

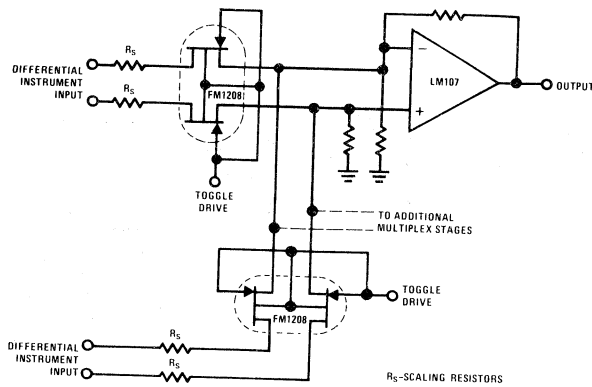
into an LM171 used as a balanced mixer. This configuration greatly reduces L.O. radiation both into the antenna and into the I.F. strip and also reduces RF signal feedthrough.



Differential Analog Switch

The FM1208 monolithic dual is used in a differential multiplexer application where  $R_{DS(ON)}$  should be closely matched. Since  $R_{DS(ON)}$  for the monolithic dual tracks at better than  $\pm 1\%$  over

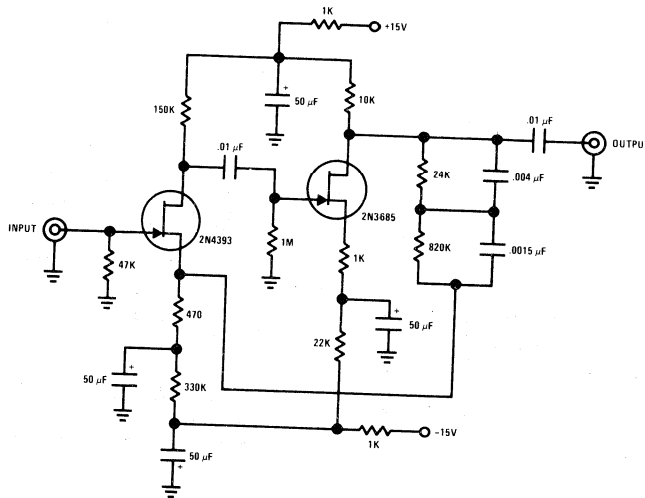
wide temperature ranges ( $-25$  to  $+125^\circ\text{C}$ ), this makes it an unusual but ideal choice for an accurate multiplexer. This close tracking greatly reduces errors due to common mode signals.



Magnetic-Pickup Phono Preamplifier


This preamplifier provides proper loading to a reluctance phono cartridge. It provides approximately 35 dB of gain at 1 kHz (2.2 mV input for 100 mV output), it features S + N/N ratio of better than

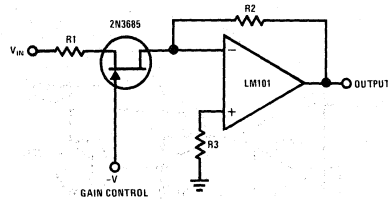-70 dB (referenced to 10 mV input at 1 kHz) and has a dynamic range of 84 dB (referenced to 1 kHz). The feedback provides for RIAA equalization.



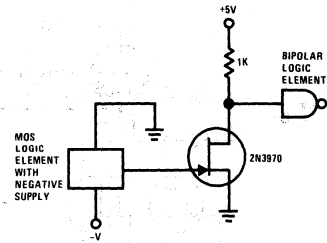
**Variable Attenuator**

The 2N3685 acts as a voltage variable resistor with an  $R_{DS(ON)}$  of  $800\Omega$  max. The 2N3685 JFET will have linear resistance over several decades of resistance providing an excellent electronic gain control.



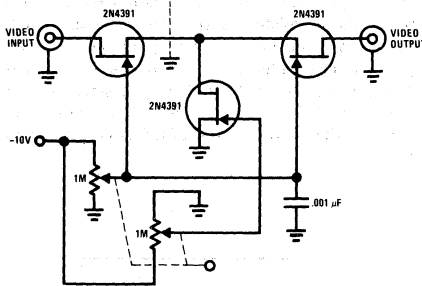
**Negative to Positive Supply Logic Level Shifter**

This simple circuit provides for level shifting from any logic function (such as MOS) operating from minus to ground supply to any logic level (such as TTL) operating from a plus to ground supply. The 2N3970 provides a low  $r_{ds(ON)}$  and fast switching times.



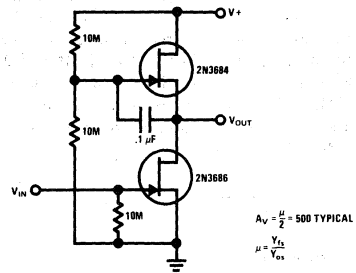**Voltage Controlled Variable Gain Amplifier**

The 2N4391 provides a low  $R_{DS(ON)}$  (less than  $30\Omega$ ). The tee attenuator provides for optimum dynamic linear range for attenuation and if complete turnoff is desired, attenuation of greater than 100 dB can be obtained at 10 MHz providing proper RF construction techniques are employed.




**Ultra-High Gain Audio Amplifier**

Sometimes called the "JFET  $\mu$  amp," this circuit provides a very low power, high gain amplifying function. Since  $\mu$  of a JFET increases as drain current decreases, the lower drain current is, the more gain you get. You do sacrifice input dynamic range with increasing gain, however.

$$A_v = \frac{\mu}{2} = 500 \text{ TYPICAL}$$


$$\mu = \frac{V_{in}}{V_{out}}$$

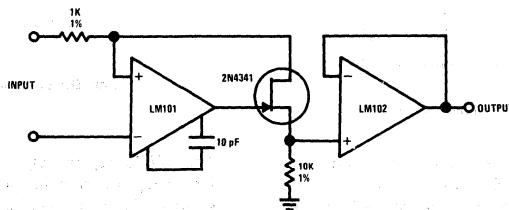

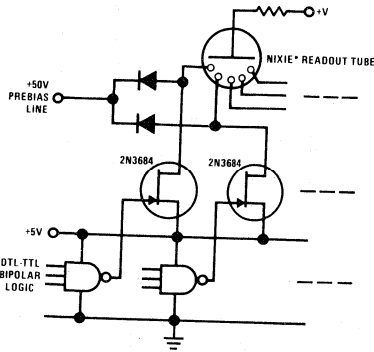**Level-Shifting-Isolation Amplifier**


The 2N4341 JFET is used as a level shifter between two op amps operated at different power

supply voltages. The JFET is ideally suited for this type of application because  $I_D = I_S$ .




FET Nixie\* Drivers

The 2N3684 JFETs are used as Nixie tube drivers. Their  $V_P$  of 2.5 volts ideally matches DTL-TTL logic levels. Diodes are used to a +50 volt prebias line to prevent breakdown of the JFETs. Since the 2N3684 is in a TO-72 (4 lead TO-18) package, none of the circuit voltages appear on the can. The JFET is immune to almost all of the failure mechanisms found in bipolar transistors used for this application.

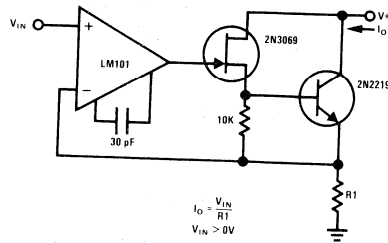


Precision Current Sink

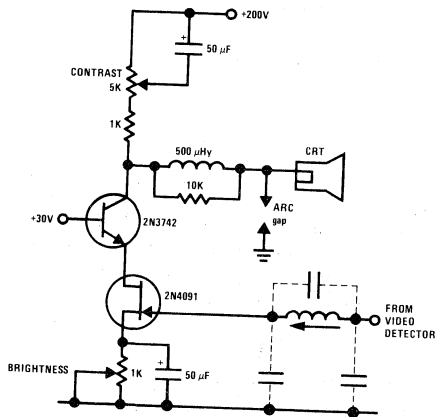The 2N3069 JFET and 2N2219 bipolar have inherently high output impedance. Using  $R_1$  as a current sensing resistor to provide feedback to the LM101 op amp provides a large amount of loop gain for negative feedback to enhance the true current sink nature of this circuit. For small current values, the 10k resistor and 2N2219 may be eliminated if the source of the JFET is connected to  $R_1$ .



JFET-Bipolar Cascode Circuit

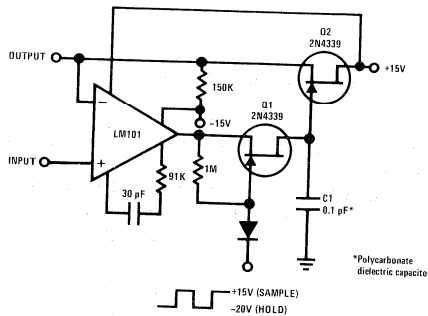
The JFET-Bipolar cascode circuit will provide full video output for the CRT cathode drive. Gain is about 90. The cascode configuration eliminates Miller capacitance problems with the 2N4091 JFET, thus allowing direct drive from the video detector. An m derived filter using stray capacitance and a variable inductor prevents 4.5 MHz sound frequency from being amplified by the video amplifier.



Low Drift Sample and Hold


The JFETs,  $Q_1$  and  $Q_2$ , provide complete buffering to  $C_1$ , the sample and hold capacitor. During sample,  $Q_1$  is turned on and provides a path,  $r_{DS(ON)}$ , for charging  $C_1$ . During hold,  $Q_1$  is turned off thus leaving  $Q_1 I_{D(OFF)}$  (<50 pA) and  $Q_2 I_{GSS}$  (<100 pA) as the only discharge paths.  $Q_2$  serves a buffering function so feedback to the LM101 and output current are supplied from its source.



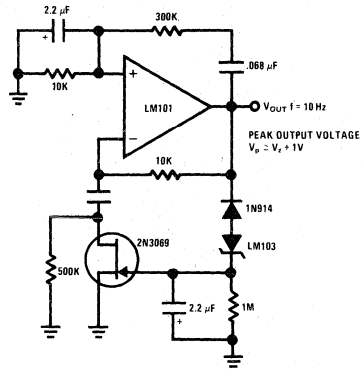


Wein Bridge Sine Wave Oscillator

The major problem in producing a low distortion, constant amplitude sine wave is getting the amplifier loop gain just right. By using the 2N3069 JFET as a voltage variable resistor in the amplifier feedback loop, this can be easily achieved. The LM103 zener diode provides the voltage reference for the peak sine wave amplitude; this is rectified and fed to the gate of the 2N3069, thus varying its channel resistance and, hence, loop gain.

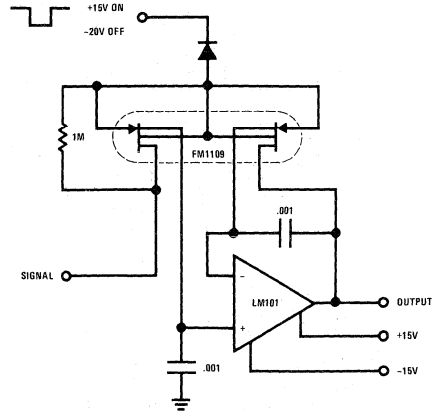


JFET Sample and Hold Circuit

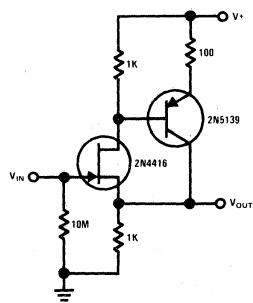The logic voltage is applied simultaneously to the sample and hold JFETs. By matching input impedance and feedback resistance and capacitance, errors due to  $r_{ds(ON)}$  of the JFETs is minimized. The inherent matched  $r_{ds(ON)}$  and matched leakage currents of the FM1109 monolithic dual greatly improve circuit performance.




High Impedance Low Capacitance Wideband Buffer

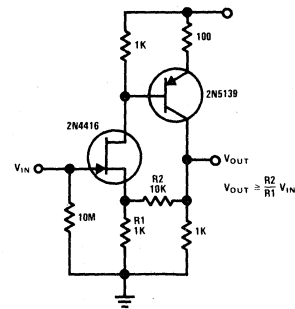The 2N4416 features low input capacitance which makes this compound-series feedback buffer a wide-band unity gain amplifier.




High Impedance Low Capacitance Amplifier

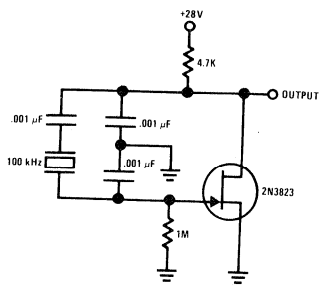This compound series-feedback circuit provides high input impedance and stable, wide-band gain for general purpose video amplifier applications.



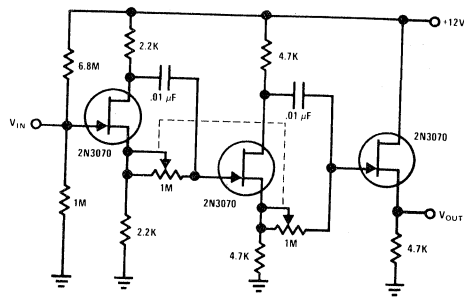
**Stable Low Frequency Crystal Oscillator**

This Colpitts-Crystal oscillator is ideal for low frequency crystal oscillator circuits. Excellent stability is assured because the 2N3823 JFET circuit loading does not vary with temperature.



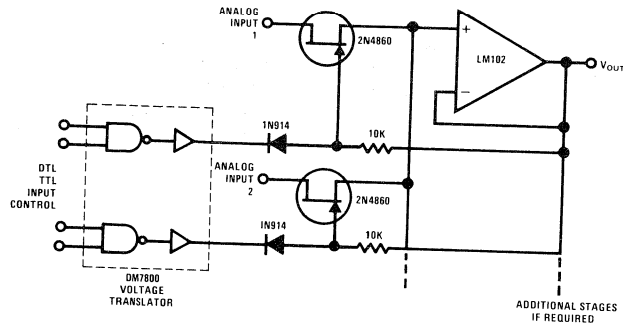**0 to 360° Phase Shifter**


Each stage provides 0° to 180° phase shift. By ganging the two stages, 0° to 360° phase shift is achieved. The 2N3070 JFETs are ideal since they do not load the phase shift networks.



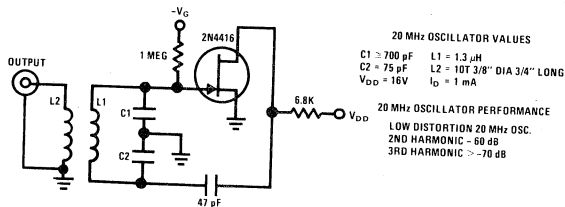**DTL-TTL Controlled Buffered Analog Switch**

This analog switch uses the 2N4860 JFET for its 25 ohm  $r_{ON}$  and low leakage. The LM102 serves as a voltage buffer. This circuit can be adapted to


a dual trace oscilloscope chopper. The DM7800 monolithic I.C. provides adequate switch drive controlled by DTL-TTL logic levels.



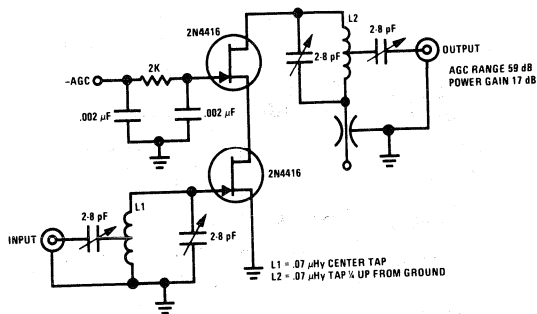**Low Distortion Oscillator**

The 2N4416 JFET is capable of oscillating in a circuit where harmonic distortion is very low. The


JFET local oscillator is excellent when a low harmonic content is required for a good mixer circuit.



200 MHz Cascode Amplifier

This 200 MHz JFET cascode circuit features low crossmodulation, large-signal handling ability, no neutralization, and AGC controlled by biasing the

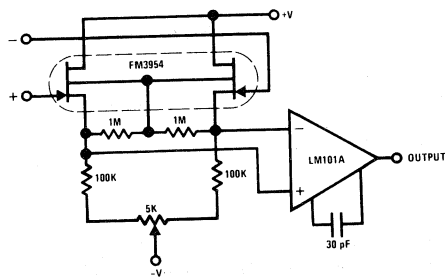
upper cascode JFET. The only special requirement of this circuit is that  $I_{DSS}$  of the upper unit must be greater than that of the lower unit.



FET Op Amp

The FM3954 monolithic-dual provides an ideal low-offset, low-drift buffer function for the LM101A op amp. The excellent matching charac-

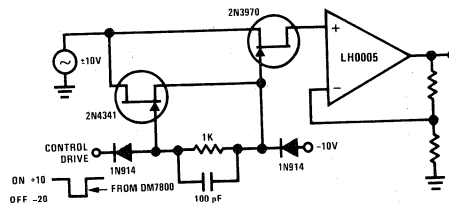
teristics of the FM3954 track well over its bias current range thus improving common mode rejection.



High Toggle Rate High Frequency Analog Switch

This commutator circuit provides low impedance gate drive to the 2N3970 analog switch for both on and off drive conditions. This circuit also approaches the ideal gate drive conditions for high

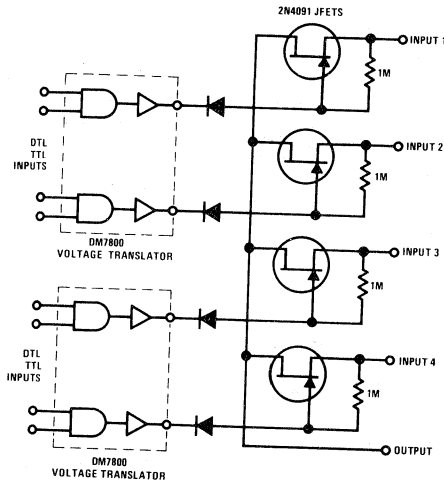
frequency signal handling by providing a low ac impedance for off drive and high ac impedance for on drive to the 2N3970. The LH0005 op amp does the job of amplifying megahertz signals.



4-Channel Commutator

This 4-channel commutator uses the 2N4091 to achieve low channel ON resistance ( $<30\Omega$ ) and low OFF current leakage. The DM7800 voltage translator is a monolithic device which provides

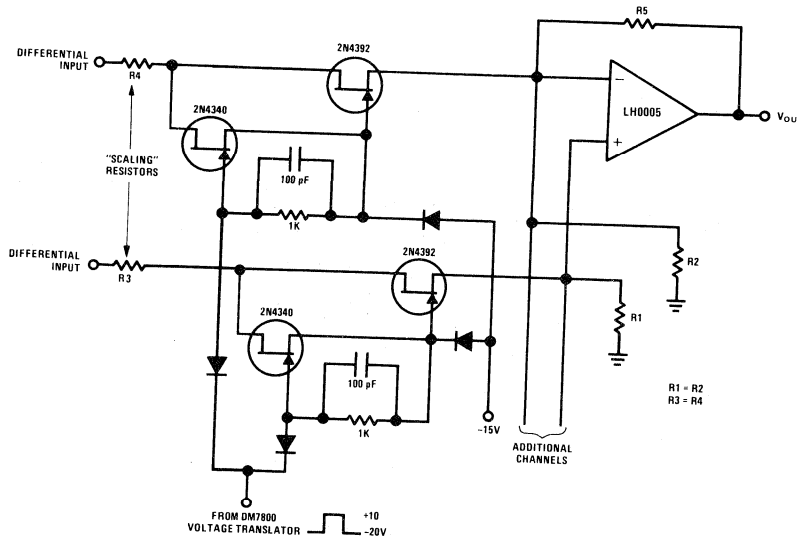
from +10V to -20V gate drive to the JFETs while at the same time providing DTL-TTL logic compatibility.



Wide Band Differential Multiplexer

This design allows high frequency signal handling and high toggle rates simultaneously. Toggle rates

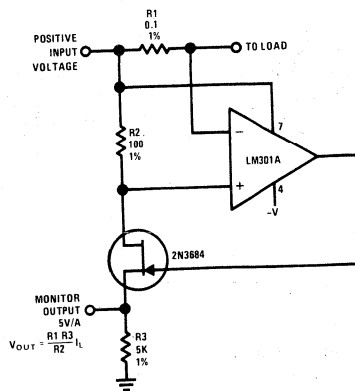
up to 1 MHz and MHz signals are possible with this circuit.



Current Monitor

$R_1$  senses current flow of a power supply. The JFET is used as a buffer because  $I_D = I_S$ , therefore

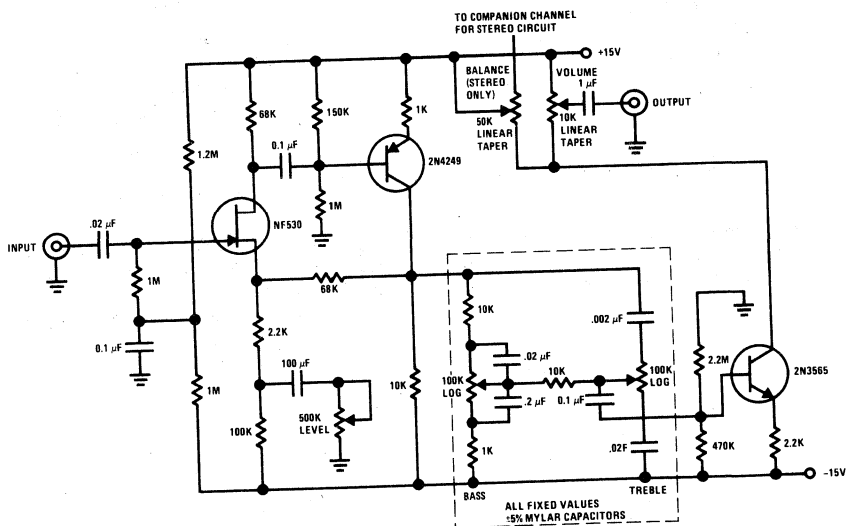
the output monitor voltage accurately reflects the power supply current flow.



Low Cost High Level Preamp and Tone Control Circuit


This preamp and tone control uses the JFET to its best advantage; as a low noise high input impedance device. All device parameters are non-critical yet the circuit achieves harmonic distortion levels

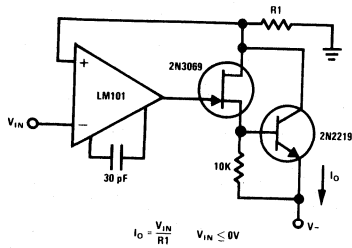of less than .05% with a S/N ratio of over 85 dB. The tone controls allow 18 dB of cut and boost; the amplifier has a 1-volt output for 100 mV input at maximum level.



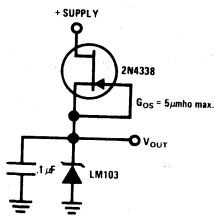
**Precision Current Source**

The 2N3069 JFET and 2N2219 bipolar serve as voltage isolation devices between the output and the current sensing resistor,  $R_1$ . The LM101 provides a large amount of loop gain to assure that the circuit acts as a current source. For small values of current, the 2N2219 and 10k resistor may be eliminated with the output appearing at the source of the 2N3069.



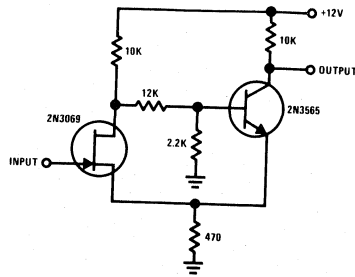
**Low Power Regulator Reference**

This simple reference circuit provides a stable voltage reference almost totally free of supply voltage hash. Typical power supply rejection exceeds 100 dB.



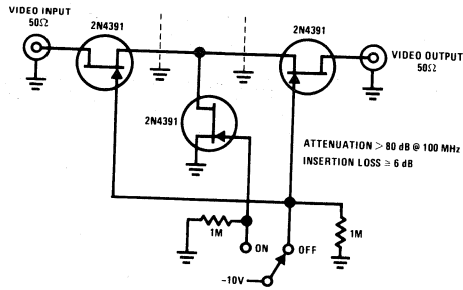**Schmitt Trigger**

This Schmitt trigger circuit is "emitter coupled" and provides a simple comparator action. The 2N3069 JFET places very little loading on the measured input. The 2N3565 bipolar is a high  $h_{FE}$  transistor so the circuit has fast transition action and a distinct hysteresis loop.



**High Frequency Switch**

The 2N4391 provides a low on-resistance of 30 ohms and a high off-impedance ( $<.2$  pF) when off. With proper layout and an "ideal" switch, the performance stated above can be readily achieved.

# Precision IC Comparator Runs from +5V Logic Supply

National Semiconductor  
Application Note 41  
October 1970



## INTRODUCTION

In digital systems, it is sometimes necessary to convert low level analog signals into digital information. An example of this might be a detector for the illumination level of a photodiode. Another would be a zero crossing detector for a magnetic transducer such as a magnetometer or a shaft-position pickoff. These transducers have low-level outputs, with currents in the low microamperes or voltages in the low millivolts. Therefore, low level circuitry is required to condition these signals before they can drive logic circuits.

A voltage comparator can perform many of these precision functions. A comparator is essentially a high-gain op amp designed for open loop operation. The function of a comparator is to produce a logic "one" on the output with a positive signal between its two inputs or a logic "zero" with a negative signal between the inputs. Threshold detection is accomplished by putting a reference voltage on one input and the signal on the other. Clearly, an op amp can be used as a comparator, except that its response time is in the tens of microseconds which is often too slow for many applications.

A unique comparator design will be described here along with some of its applications in digital systems. Unlike older IC comparators or op amps, it will operate from the same 5V supply as DTL or TTL logic circuits. It will also operate with the single negative supply used with MOS logic. Hence, low level functions can be performed without the extra supply voltages previously required.

The versatility of the comparator along with the minimal circuit loading and considerable precision recommend it for many uses, in digital systems, other than the detection of low level signals. It can be used as an oscillator or multivibrator, in digital interface circuitry and even for low voltage analog circuitry. Some of these applications will also be discussed.

## CIRCUIT DESCRIPTION

In order to understand how to use this comparator, it is necessary to look briefly at the circuit configuration. Figure 1 shows a simplified schematic of the device. PNP transistors buffer the

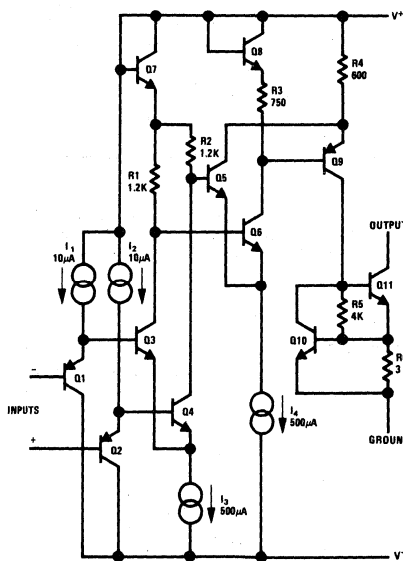


FIGURE 1. Simplified Schematic of the Comparator

differential input stage to get low input currents without sacrificing speed. The PNP's drive a standard NPN differential stage, Q<sub>3</sub> and Q<sub>4</sub>. The output of this stage is further amplified by the Q<sub>5</sub>-Q<sub>6</sub> pair. This feeds Q<sub>9</sub>, which provides additional gain and drives the output stage. Current sources are used to determine the bias currents, so that performance is not greatly affected by supply voltages.

The output transistor is  $Q_{11}$ , and it is protected by  $Q_{10}$  and  $R_6$  which limit the peak output current. The output lead, since it is not connected to any other point in the circuit, can either be returned to the positive supply through a pull-up resistor or switch loads that are connected to a voltage higher than the positive supply voltage. The circuit will operate from a single supply if the negative supply lead is connected to ground. However, if a negative supply is available, it can be used to increase the input common mode range.

Table 1 summarizes the performance of the comparator when operating from a 5V supply. The circuit will work with supply voltages up to  $\pm 15V$


**Table 1. Important Electrical Characteristics of the LM111 Comparator when Operating from Single, 5V Supply ( $T_A = 25^\circ C$ ).**

Parameter	Limits			Units
	Min	Typ	Max	
Input Offset Voltage		0.7	3	mV
Input Offset Current		4	10	nA
Input Bias Current		60	100	nA
Voltage Gain		100		V/mV
Response Time		200		ns
Common Mode Range	0.3		3.8	V
Output Voltage Swing			50	V
Output Current			50	mA
Fan Out (DTL/TTL)	8			
Supply Current		3	5	mA

with a corresponding increase in the input voltage range. Other characteristics are essentially unchanged at the higher voltages.

### LOW LEVEL APPLICATIONS

A circuit that will detect zero crossing in the output of a magnetic transducer within a fraction of a millivolt is shown in Figure 2. The magnetic

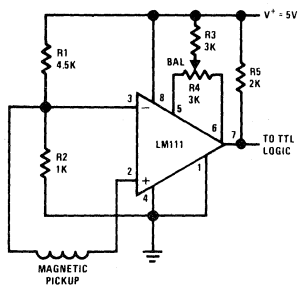


**FIGURE 2. Zero Crossing Detector for Magnetic Transducer**

pickup is connected between the two inputs of the comparator. The resistive divider,  $R_1$  and  $R_2$ , biases the inputs 0.5V above ground, within the

common mode range of the IC. The output will directly drive DTL or TTL. The exact value of the pull up resistor,  $R_5$ , is determined by the speed required from the circuit since it must drive any capacitive loading for positive-going output signals. An optional offset-balancing circuit using  $R_3$  and  $R_4$  is included in the schematic.


Figure 3 shows a connection for operating with MOS logic. This is a level detector for a photodiode that operates off a  $-10V$  supply. The output changes state when the diode current reaches  $1 \mu A$ . Even at this low current, the error contributed by the comparator is less than 1%.

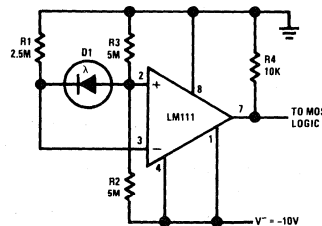

**FIGURE 3. Level Detector for Photodiode**

Higher threshold currents can be obtained by reducing  $R_1$ ,  $R_2$  and  $R_3$  proportionally. At the switching point, the voltage across the photodiode is nearly zero, so its leakage current does not cause an error. The output switches between ground and  $-10V$ , driving the data inputs of MOS logic directly.

The circuit in Figure 3 can, of course, be adapted to work with a 5V supply. At any rate, the accuracy of the circuit will depend on the supply-voltage regulation, since the reference is derived from the supply. Figure 4 shows a method

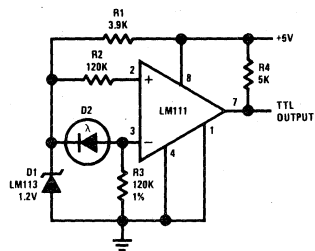

**FIGURE 4. Precision Level Detector for Photodiode**

of making performance independent of supply voltage.  $D_1$  is a temperature-compensated reference diode with a 1.23V breakdown voltage. It acts as a shunt regulator and delivers a stable voltage to the comparator. When the diode current is large enough (about  $10 \mu A$ ) to make the voltage drop across  $R_3$  equal to the breakdown voltage



of  $D_1$ , the output will change state.  $R_2$  has been added to make the threshold error proportional to the offset current of the comparator, rather than the bias current. It can be eliminated if the bias current error is not considered significant.

A zero crossing detector that drives the data input of MOS logic is shown in Figure 5. Here, both a

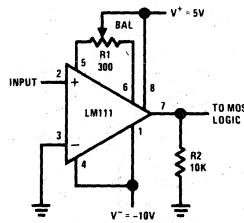


FIGURE 5. Zero Crossing Detector Driving MOS Logic

positive supply and the  $-10V$  supply for MOS circuits are used. Both supplies are required for the circuit to work with zero common-mode voltage. An alternate balancing scheme is also shown in the schematic. It differs from the circuit in Figure 2 in that it raises the input-stage current by a factor of three. This increases the rate at which the input voltage follows rapidly-changing signals from  $7V/\mu s$  to  $18V/\mu s$ . This increased common-mode slew can be obtained without the balancing potentiometer by shorting both balance terminals to the positive-supply terminal. Increased input bias current is the price that must be paid for the faster operation.

### DIGITAL INTERFACE CIRCUITS

Figure 6 shows an interface between high-level logic and DTL or TTL. The input signal, with 0V and 30V logic states is attenuated to 0V and 5V by  $R_1$  and  $R_2$ .  $R_3$  and  $R_4$  set up a 2.5V threshold

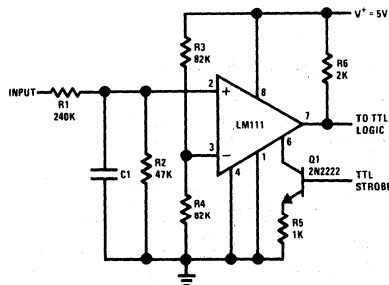


FIGURE 6. Circuit for Transmitting Data Between High-Level Logic and TTL

level for the comparator so that it switches when the input goes through 15V. The response time of the circuit can be controlled with  $C_1$ , if desired, to

make it insensitive to fast noise spikes. Because of the low error currents of the LM111, it is possible to get input impedances even higher than the  $300\text{ k}\Omega$  obtained with the indicated resistor values.

The comparator can be strobed, as shown in Figure 6, by the addition of  $Q_1$  and  $R_5$ . With a logic one on the base of  $Q_1$ , approximately 2.5 mA is drawn out of the strobe terminal of the LM111, making the output high independent of the input signal.

Sometimes it is necessary to transmit data between digital equipments, yet maintain a high degree of electrical isolation. Normally, this is done with a transformer. However, transformers have problems with low-duty-cycle pulses since they do not preserve the dc level.

The circuit in Figure 7 is a more satisfactory method of obtaining isolation. At the transmitting

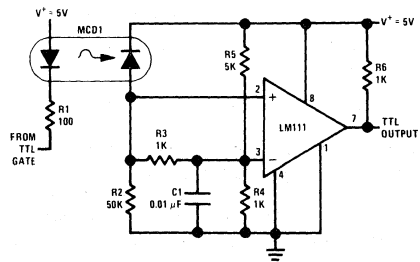


FIGURE 7. Data Transmission System with Near-Infinite Ground Isolation

end, a TTL gate drives a gallium-arsenide light-emitting diode. The light output is optically coupled to a silicon photodiode, and the comparator detects the photodiode output. The optical coupling makes possible electrical isolation in the thousands of megohms at potentials in the thousands of volts.

The maximum data rate of this circuit is 1 MHz. At lower rates ( $\sim 200\text{ kHz}$ )  $R_3$  and  $C_1$  can be eliminated.

### MULTIVIBRATORS AND OSCILLATORS

The free-running multivibrator in Figure 8 is another example of the versatility of the comparator. The inputs are biased within the common mode range by  $R_1$  and  $R_2$ . DC stability, which insures starting, is provided by negative feedback through  $R_3$ . The negative feedback is reduced at high frequencies by  $C_1$ . At some frequency, the positive feedback through  $R_4$  will be greater than the negative feedback; and the circuit will oscillate. For the component values shown, the circuit delivers a 100 kHz square wave output. The

frequency can be changed by varying  $C_1$  or by adjusting  $R_1$  through  $R_4$ , while keeping their ratios constant.

Because of the low input current of the comparator, large circuit impedances can be used. Therefore, low frequencies can be obtained with relatively-small capacitor values: it is no problem to get down to 1 Hz using a  $1 \mu\text{F}$  capacitor. The speed of the comparator also permits operation at frequencies above 100 kHz.

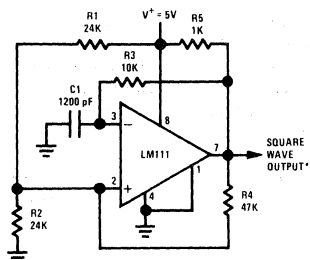


FIGURE 8. Free-Running Multivibrator

The frequency of oscillation depends almost entirely on the resistance and capacitor values because of the precision of the comparator. Further, the frequency changes by only 1% for a 10% change in supply voltage. Waveform symmetry is also good, but the symmetry can be varied by changing the ratio of  $R_1$  to  $R_2$ .

A crystal-controlled oscillator that can be used to generate the clock in slower digital systems is shown in Figure 9. It is similar to the free running

multivibrator, except that the positive feedback is obtained through a quartz crystal. The circuit oscillates when transmission through the crystal is at a maximum, so the crystal operates in its series-resonant mode. The high input impedance of the comparator and the isolating capacitor,  $C_2$ ,

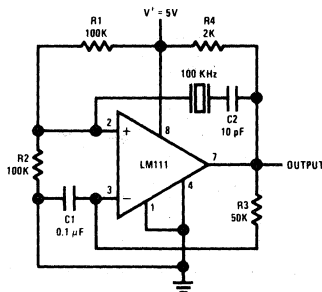


FIGURE 9. Crystal-Controlled Oscillator

minimize loading of the crystal and contribute to frequency stability. As shown, the oscillator delivers a 100 kHz square-wave output.

### FREQUENCY DOUBLER

In a digital system, it is a relatively simple matter to divide by any integer. However, multiplying by an integer is quite another story especially if operation over a wide frequency range and waveform symmetry are required.

A frequency doubler that satisfies the above requirements is shown in Figure 10. A compar-

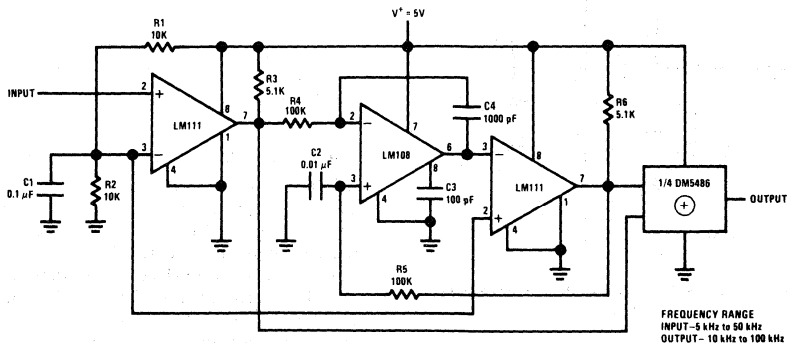


FIGURE 10. Frequency Doubler

FREQUENCY RANGE  
INPUT - 5 kHz to 50 kHz  
OUTPUT - 10 kHz to 100 kHz

ator is used to shape the input signal and feed it to an integrator. The shaping is required because the input to the integrator must swing between the supply voltage and ground to preserve symmetry in the output waveform. An LM108 op amp, that works from the 5V logic supply, serves as the integrator. This feeds a triangular waveform to a second comparator that detects when the waveform goes through a voltage equal to its average value. Hence, as shown in Figure 11, the output

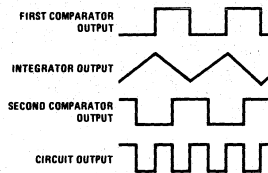


FIGURE 11. Waveforms for the Frequency Doubler

of the second comparator is delayed by half the duration of the input pulse. The two comparator outputs can then be combined through an exclusive-OR gate to produce the double-frequency output.

With the component values shown, the circuit operates at frequencies from 5 kHz to 50 kHz. Lower frequency operation can be secured by increasing both  $C_1$  and  $C_2$ .

#### APPLICATION HINTS

One of the problems encountered in using earlier IC comparators like the LM710 or LM106 was that they were prone to erratic operation caused by oscillations. This was a direct result of the high speed of the devices, which made it mandatory to provide good input-output isolation and low-inductance bypassing on the supplies. These oscillations could be particularly puzzling when they occurred internally, showing up at the external terminals only as erratic dc characteristics.

In general, the LM111 is less susceptible to spurious oscillations both because of its lower speed (200 ns response time vs 40 ns) and because of its better power supply rejection. Feedback between the output and the input is a lesser problem with a given source resistance. However, the LM111 can operate with source resistances that are orders of magnitude higher than the earlier devices, so stray coupling between the input and output should be minimized. With source resistances between 1 k $\Omega$  and 10 k $\Omega$ , the impedance (both capacitive and resistive) on both inputs should be made equal, as this tends to reject the signal fed back. Even so, it is difficult to completely eliminate oscillations in the linear region with source resistances above

10 k $\Omega$ , because the 1 MHz open loop gain of the comparator is about 80 dB. However, this does not affect the dc characteristics and is not a problem unless the input signal dwells within 200  $\mu$ V of the transition level. But if the oscillation does cause difficulties, it can be eliminated with a small amount of positive feedback around the comparator to give a 1 mV hysteresis.

Stray coupling between the output and the balance terminals can also cause oscillations, so an attempt should be made to keep these leads apart. It is usually advisable to tie the balance pins together to minimize the effect of this feedback. If balancing is used, the same result can be accomplished by connecting a 0.1  $\mu$ F capacitor between these pins.

Normally, individual supply bypasses on every device are unnecessary, although long leads between the comparator and the bypass capacitors are definitely not recommended. If large current spikes are injected into the supplies in switching the output, bypass capacitors should be included at these points.

When driving the inputs from a low impedance source, a limiting resistor should be placed in series with the input lead to limit the peak current to something less than 100 mA. This is especially important when the inputs go outside a piece of equipment where they could accidentally be connected to high voltage sources. Low impedance sources do not cause a problem unless their output voltage exceeds the negative supply voltage. However, the supplies go to zero when they are turned off, so the isolation is usually needed.

Large capacitors on the input (greater than 0.1  $\mu$ F) should be treated as a low source impedance and isolated with a resistor. A charged capacitor can hold the inputs outside the supply voltage if the supplies are abruptly shut off.

Precautions should be taken to insure that the power supplies for this or any other IC never become reversed—even under transient conditions. With reverse voltages greater than 1V, the IC can conduct excessive current, fusing internal aluminum interconnects. This usually takes more than 0.5A. If there is a possibility of reversal, clamp diodes with an adequate peak current rating should be installed across the supply bus.

No attempt should be made to operate the circuit with the ground terminal at a voltage exceeding either supply voltage. Further, the 50V output-voltage rating applies to the potential between the output and the  $V^-$  terminal. Therefore, if the comparator is operated from a negative supply, the maximum output voltage must be reduced by an amount equal to the voltage on the  $V^-$  terminal.

The output circuitry is protected for shorts across the load. It will not, for example, withstand a

short to a voltage more negative than the ground terminal. Additionally, with a sustained short, power dissipation can become excessive if the voltage across the output transistor exceeds about 10V.

The input terminals can exceed the positive supply voltage without causing damage. However, the 30V maximum rating between the inputs and the  $V^-$  terminal must be observed. As mentioned earlier, the inputs should not be driven more negative than the  $V^-$  terminal.

### CONCLUSIONS

A versatile voltage comparator that can perform many of the precision functions required in digital systems has been produced. Unlike older comparators, the IC can operate from the same supply voltage as the digital circuits. The comparator is particularly useful in circuits requiring considerable sensitivity and accuracy, such as threshold detectors for low level sensors, data transmission circuits or stable oscillators and multivibrators.

The comparator can also be used in many analog systems. It operates from standard  $\pm 15V$  op amp supplies, and its dc accuracy equals some of the best op amps. It is also an order of magnitude faster than op amps used as comparators.

The new comparator is considerably more flexible than older devices. Not only will it drive RTL, DTL and TTL logic; but also it can interface with MOS logic or deliver  $\pm 15V$  to FET analog switches. The output can switch 50V, 50 mA loads, making it useful as a driver for relays, lamps or light-emitting diodes. Further, a unique output stage enables it to drive loads referred to either supply or to ground and provide ground isolation between the comparator inputs and the load.

The LM111 is a plug-in replacement for comparators like the LM710 and LM106 in applications where speed is not of prime concern. Compared to its predecessors in other respects, it has many improved electrical specifications, more design flexibility and fewer application problems.

## IC Provides On-Card Regulation for Logic Circuits

National Semiconductor  
Application Note 42  
February 1971



### INTRODUCTION

Because of the relatively high current requirements of digital systems, there are a number of problems associated with using one centrally-located regulator. Heavy power busses must be used to distribute the regulated voltage. With low voltages and currents of many amperes, voltage drops in connectors and conductors can cause an appreciable percentage change in the voltage delivered to the load. This is aggravated further with TTL logic, as it draws transient currents many times the steady-state current when it switches.

These problems have created a considerable interest in on-card regulation, that is, to provide local regulation for the subsystems of the computer. Rough preregulation can be used, and the power distributed without excessive concern for line drops. The local regulators then smooth out the voltage variations due to line drops and absorb transients.

A monolithic regulator is now available to perform this function. It is quite simple to use in that it requires no external components. The integrated circuit has three active leads—input, output and ground—and can be supplied in standard transistor power packages. Output currents in excess of 1A can be obtained. Further, no adjustments are required to set up the output voltage, and overload protection is provided that makes it virtually impossible to destroy the regulator. The simplicity of the regulator, coupled with low-cost fabrication and improved reliability of monolithic circuits, now makes on-card regulation quite attractive.

### DESIGN CONCEPTS

A useful on-card regulator should include everything within one package—including the power-control element, or pass transistor. The author has previously advanced arguments against including the pass transistor in an integrated circuit regulator.<sup>1</sup> First, there are no standard multi-lead power packages. Second, integrated circuits necessarily have a lower maximum operating temperature, because they contain low-level circuitry. This means that an IC regulator needs a more massive heat sink. Third, the gross variations in chip temperature due to dissipation in the pass transistors worsen load and line regulation. However, for a logic-card regulator, these arguments can be answered effectively.

For one, if the series pass transistor is put on the chip, the integrated circuit need only have three terminals. Hence, an ordinary transistor power package can be used. The practicality of this approach depends on eliminating the adjustments usually required to set up the output voltage and limiting current for the particular application, as external adjustments require extra pins. A new solid-state reference, to be described later, has sufficiently-tight manufacturing tolerances that output voltages do not always have to be individually trimmed. Further, thermal overload protection can protect an IC regulator for virtually any set of operating conditions, making current-limit adjustments unnecessary.

Thermal protection limits the maximum junction temperature and protects the regulator regardless of input voltage, type of overload or degree of heat sinking. With an external pass transistor, there is no convenient way to sense junction temperature so it is much more difficult to provide thermal limiting. Thermal protection is, in itself, a very good reason for putting the pass transistor on the chip.

When a regulator is protected by current limiting alone, it is necessary to limit the output current to a value substantially lower than is dictated by dissipation under normal operating conditions to prevent excessive heating when a fault occurs. Thermal limiting provides virtually absolute protection for any overload condition. Hence, the maximum output current under normal operating conditions can be increased. This tends to make up for the fact that an IC has a lower maximum junction temperature than discrete transistors.

Additionally, the 5V regulator works with relatively low voltage across the integrated circuit. Because of the low voltage, the internal circuitry can be operated at comparatively high currents without causing excessive dissipation. Both the low voltage and the larger internal currents permit higher junction temperatures. This can also reduce the heat sinking required—especially for commercial-temperature-range parts.

Lastly, the variations in chip temperature caused by dissipation in the pass transistor do not cause serious problems for a logic-card regulator. The tolerance in output voltage is loose enough that it

is relatively easy to design an internal reference that is much more stable than required, even for temperature variations as large as 150°C.

### CIRCUIT DESCRIPTION

The internal voltage reference for this logic-card regulator is probably the most significant departure from standard design techniques. Temperature-compensated zener diodes are normally used for the reference. However, these have breakdown voltages between 7V and 9V which puts a lower limit on the input voltage to the regulator. For low voltage operation, a different kind of reference is needed.

The reference in the LM109 does not use a zener diode. Instead, it is developed from the highly-predictable emitter-base voltage of the transistors. In its simplest form, the reference developed is equal to the energy-band-gap voltage of the semiconductor material. For silicon, this is 1.205V, so the reference need not impose minimum input voltage limitations on the regulator. An added advantage of this reference is that the output voltage is well determined in a production environment so that individual adjustment of the regulators is frequently unnecessary.

A simplified version of this reference is shown in Figure 1. In this circuit, Q<sub>1</sub> is operated at a

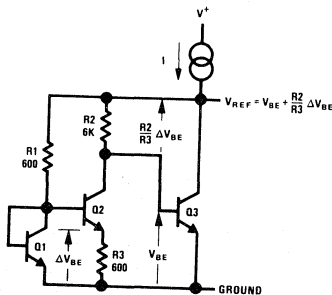


Figure 1. The Low Voltage Reference in One of Its Simpler Forms.

relatively high current density. The current density of Q<sub>2</sub> is about ten times lower, and the emitter-base voltage differential ( $\Delta V_{BE}$ ) between the two devices appears across R<sub>3</sub>. If the transistors have high current gains, the voltage across R<sub>2</sub> will also be proportional to  $\Delta V_{BE}$ . Q<sub>3</sub> is a gain stage that will regulate the output at a voltage equal to its emitter base voltage plus the drop across R<sub>2</sub>. The emitter base voltage of Q<sub>3</sub> has a negative temperature coefficient while the  $\Delta V_{BE}$  component across R<sub>2</sub> has a positive temperature coefficient. It will be shown that the output voltage will be temperature compensated when the sum of the two voltages is equal to the energy-band-gap voltage.

Conditions for temperature compensation can be derived starting with the equation for the emitter-base voltage of a transistor which is<sup>2</sup>

$$V_{BE} = V_{g0} \left(1 - \frac{T}{T_0}\right) + V_{BE0} \left(\frac{T}{T_0}\right) + \frac{nkT}{q} \log_e \frac{T_0}{T} + \frac{kT}{q} \log_e \frac{I_C}{I_{C0}} \quad (1)$$

Where  $V_{g0}$  is the extrapolated energy-band-gap voltage for the semiconductor material at absolute zero,  $q$  is the charge of an electron,  $n$  is a constant which depends on how the transistor is made (approximately 1.5 for double-diffused, NPN transistors),  $k$  is Boltzmann's constant,  $T$  is absolute temperature,  $I_C$  is collector current and  $V_{BE0}$  is the emitter-base voltage at  $T_0$  and  $I_{C0}$ .

The emitter-base voltage differential between two transistors operated at different current densities is given by<sup>3</sup>

$$\Delta V_{BE} = \frac{kT}{q} \log_e \frac{J_1}{J_2} \quad (2)$$

where  $J$  is current density.

Referring to Equation (1), the last two terms are quite small and are made even smaller by making  $I_C$  vary as absolute temperature. At any rate, they can be ignored for now because they are of the same order as errors caused by nontheoretical behavior of the transistors that must be determined empirically.

If the reference is composed of  $V_{BE}$  plus a voltage proportional to  $\Delta V_{BE}$ , the output voltage is obtained by adding (1) in its simplified form to (2):

$$V_{ref} = V_{g0} \left(1 - \frac{T}{T_0}\right) + V_{BE0} \left(\frac{T}{T_0}\right) + \frac{kT}{q} \log_e \frac{J_1}{J_2} \quad (3)$$

Differentiating with respect to temperature yields

$$\frac{\partial V_{ref}}{\partial T} = -\frac{V_{g0}}{T_0} + \frac{V_{BE0}}{T_0} + \frac{k}{q} \log_e \frac{J_1}{J_2} \quad (4)$$

For zero temperature drift, this quantity should equal zero, giving

$$V_{g0} = V_{BE0} + \frac{kT_0}{q} \log_e \frac{J_1}{J_2} \quad (5)$$

The first term on the right is the initial emitter-base voltage while the second is the component proportional to emitter-base voltage differential. Hence, if the sum of the two are equal to the energy-band-gap voltage of the semiconductor, the reference will be temperature-compensated.

A simplified schematic for a 5V regulator is given in Figure 2. The circuitry produces an output voltage that is approximately four times the basic reference voltage. The emitter-base voltage of  $Q_3$ ,  $Q_4$ ,  $Q_5$  and  $Q_8$  provide the negative-temperature-coefficient component of the output voltage. The voltage dropped across  $R_3$  provides the positive-temperature-coefficient component.  $Q_6$  is operated at a considerably higher current density than  $Q_7$ , producing a voltage drop across  $R_4$  that is proportional to the emitter-base voltage differential of the two transistors. Assuming large current gain in the transistors, the voltage drop across  $R_3$  will be proportional to this differential, so a temperature-compensated output voltage can be obtained.

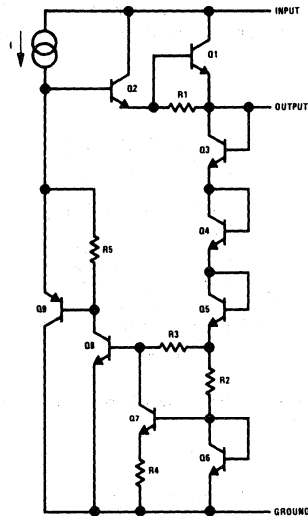


Figure 2. Schematic Showing Essential Details of The 5V Regulator.

In this circuit,  $Q_8$  is the gain stage providing regulation. Its effective gain is increased by using a vertical PNP,  $Q_9$ , as a buffer driving the active collector load represented by the current source.  $Q_9$  drives a modified Darlington output stage ( $Q_1$  and  $Q_2$ ) which acts as the series pass element. With this circuit, the minimum input voltage is not limited by the voltage needed to supply the reference. Instead, it is determined by the output voltage and the saturation voltage of the Darlington output stage.

Figure 3 shows a complete schematic of the LM109, 5V regulator. The  $\Delta V_{BE}$  component of

the output voltage is developed across  $R_8$  by the collector current of  $Q_7$ . The emitter-base voltage differential is produced by operating  $Q_4$  and  $Q_5$  at high current densities while operating  $Q_6$  and  $Q_7$  at much lower current levels. The extra transistors improve tolerances by making the emitter-base voltage differential larger.  $R_3$  serves to compensate the transconductance<sup>4</sup> of  $Q_6$ , so that the  $\Delta V_{BE}$  component is not affected by changes in the regulator output voltage or the absolute value of components.

The voltage gain for the regulating loop is provided by  $Q_{10}$ , with  $Q_9$  buffering its input and  $Q_{11}$  its output. The emitter base voltage of  $Q_9$  and  $Q_{10}$  is added to that of  $Q_{12}$  and  $Q_{13}$  and the drop across  $R_8$  to give a temperature-compensated, 5V output. An emitter-base-junction capacitor,  $C_1$ , frequency compensates the circuit so that it is stable even without a bypass capacitor on the output.

The active collector load for the error amplifier is  $Q_{17}$ . It is a multiple-collector lateral PNP<sup>4</sup>. The output current is essentially equal to the collector current of  $Q_2$ , with current being supplied to the zener diode controlling the thermal shutdown,  $D_2$ , by an auxiliary collector.  $Q_1$  is a collector FET<sup>4</sup> that, along with  $R_1$ , insures starting of the regulator under worst-case conditions.

The output current of the regulator is limited when the voltage across  $R_{14}$  becomes large enough to turn on  $Q_{14}$ . This insures that the output current cannot get high enough to cause the pass transistor to go into secondary breakdown or damage the aluminum conductors on the chip. Further, when the voltage across the pass transistor exceeds 7V, current through  $R_{15}$  and  $D_3$  reduces the limiting current, again to minimize the

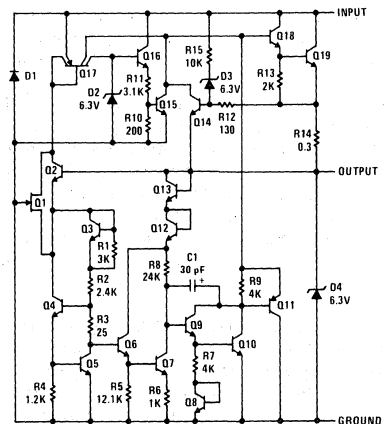


Figure 3. Detailed Schematic of The Regulator.

chance of secondary breakdown. The performance of this protection circuitry is illustrated in Figure 4.

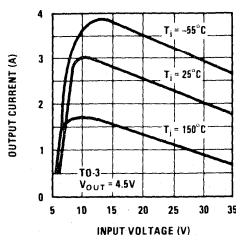


Figure 4. Current-Limiting Characteristics.

Even though the current is limited, excessive dissipation can cause the chip to overheat. In fact, the dominant failure mechanism of solid state regulators is excessive heating of the semiconductor, particularly the pass transistor. Thermal protection attacks the problem directly by putting a temperature regulator on the IC chip. Normally, this regulator is biased below its activation threshold; so it does not affect circuit operation. However, if the chip approaches its maximum operating temperature, for any reason, the temperature regulator turns on and reduces internal dissipation to prevent any further increase in chip temperature.

The thermal protection circuitry develops its reference voltage with a conventional zener diode,  $D_2$ .  $Q_{16}$  is a buffer that feeds a voltage divider, delivering about 300 mV to the base of  $Q_{15}$  at 175°C. The emitter-base voltage,  $Q_{15}$ , is the actual temperature sensor because, with a constant voltage applied across the junction, the collector current rises rapidly with increasing temperature.

Although some form of thermal protection can be incorporated in a discrete regulator, IC's have a distinct advantage: the temperature sensing device detects increases in junction temperature within milliseconds. Schemes that sense case or heat-sink temperature take several seconds, or longer. With the longer response times, the pass transistor usually blows out before thermal limiting comes into effect.

Another protective feature of the regulator is the crowbar clamp on the output. If the output voltage tries to rise for some reason,  $D_4$  will break down and limit the voltage to a safe value. If this rise is caused by failure of the pass transistor such that the current is not limited, the aluminum conductors on the chip will fuse, disconnecting the load. Although this destroys the regulator, it does

protect the load from damage. The regulator is also designed so that it is not damaged in the event the unregulated input is shorted to ground when there is a large capacitor on the output. Further, if the input voltage tries to reverse,  $D_1$  will clamp this for currents up to 1A.

The internal frequency compensation of the regulator permits it to operate with or without a bypass capacitor on the output. However, an output capacitor does improve the transient response and reduce the high frequency output impedance. A plot of the output impedance in Figure 5 shows that it remains low out to 10 kHz even without a capacitor. The ripple rejection also remains high out to 10 kHz, as shown in Figure 6. The irregularities in this curve around 100 Hz are caused by thermal feedback from the pass transistor to the reference circuitry. Although an output capacitor is not required, it is necessary to bypass the input of the regulator with at least a 0.22  $\mu$ F capacitor to prevent oscillations under all conditions.

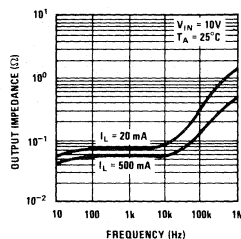


Figure 5. Plot of Output Impedance As A Function of Frequency.

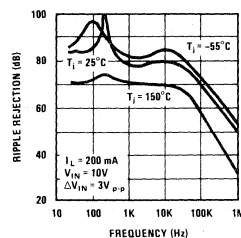


Figure 6. Ripple Rejection of The Regulator.

Figure 7 is a photomicrograph of the regulator chip. It can be seen that the pass transistors, which must handle more than 1A, occupy most of the chip area. The output transistor is actually broken into segments. Uniform current distribution is insured by also breaking the current limit resistor into segments and using them to equalize the



currents. The overall electrical performance of this IC is summarized in Table 1.

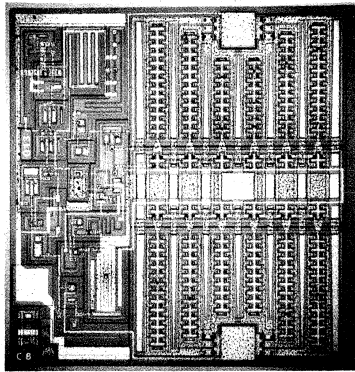


Figure 7. Photomicrograph of The Regulator Shows That High Current Pass Transistor (Right) Takes More Area Than Control Circuitry (Left).

PARAMETER	CONDITIONS	TYP
Output Voltage		5.0V
Output Current		1.5A
Output Resistance		0.03Ω
Line Regulation	$7.0V \leq V_{IN} \leq 35V$	0.005%/V
Temperature Drift	$-55^{\circ}C \leq T_A \leq 125^{\circ}C$	0.02%/°C
Minimum Input Voltage	$I_{OUT} = 1A$	6.5V
Output Noise Voltage	$10 \text{ Hz} \leq f \leq 100 \text{ kHz}$	40 μV
Thermal Resistance	LM109H (TO-5)	15°C/W
Junction to Case	LM109K (TO-3)	3°C/W

Table 1. Typical Characteristics of The Logic-Card Regulator:  $T_A = 25^{\circ}C$ .

### APPLICATIONS

Because it was designed for virtually foolproof operation and because it has a singular purpose, the LM109 does not require a lot of application information, as do most other linear circuits. Only one precaution must be observed: it is necessary to bypass the unregulated supply with a 0.22 μF capacitor, as shown in Figure 8, to prevent

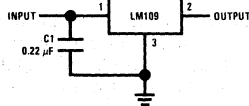


Figure 8. Fixed 5V Regulator

oscillations that can cause erratic operation. This, of course, is only necessary if the regulator is located an appreciable distance from the filter capacitors on the output of the dc supply.

Although the LM109 is designed as a fixed 5V regulator, it is also possible to use it as an adjustable regulator for higher output voltages. One circuit for doing this is shown in Figure 9.

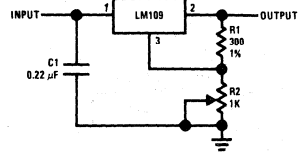


Figure 9. Using The LM109 As An Adjustable-Output Regulator.

The regulated output voltage is impressed across  $R_1$ , developing a reference current. The quiescent current of the regulator, coming out of the ground terminal, is added to this. These combined currents produce a voltage drop across  $R_2$  which raises the output voltage. Hence, any voltage above 5V can be obtained as long as the voltage across the integrated circuit is kept within ratings.

The LM109 was designed so that its quiescent current is not greatly affected by variations in input voltage, load or temperature. However, it is not completely insensitive, as shown in Figures 10 and 11, so the changes do affect regulation somewhat. This tendency is minimized by making the reference current through  $R_1$  larger than the quiescent current. Even so, it is difficult to get the regulation tighter than a couple percent.

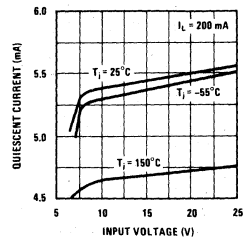


Figure 10. Variation of Quiescent Current With Input Voltage At Various Temperatures.

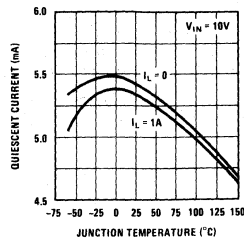


Figure 11. Variation of Quiescent Current With Temperature For Various Load Currents.

The LM109 can also be used as a current regulator as is shown in Figure 12. The regulated output voltage is impressed across  $R_1$ , which determines the output current. The quiescent current is added to the current through  $R_1$ , and this puts a lower limit of about 10 mA on the available output current.

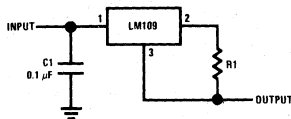


Figure 12. Current Regulator.

The increased failure resistance brought about by thermal overload protection make the LM109 attractive as the pass transistor in other regulator circuits. A precision regulator that employs the IC thusly is shown in Figure 13. An operational amplifier compares the output voltage with the output voltage of a reference zener. The op amp controls the LM109 by driving the ground terminal through an FET.

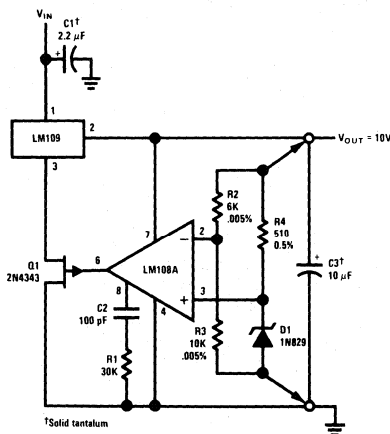


Figure 13. High Stability Regulator.

The load and line regulation of this circuit is better than 0.001%. Noise, drift and long term stability are determined by the reference zener,  $D_1$ . Noise can be reduced by inserting 100 k $\Omega$ , 1% resistors in series with both inputs of the op amp and

bypassing the non-inverting input to ground. A 100 pF capacitor should also be included between the output and the inverting input to prevent frequency instability. Temperature drift can be reduced by adjusting  $R_4$ , which determines the zener current, for minimum drift. For best performance, remote sensing directly to the load terminals, as shown in the diagram, should be used.

## CONCLUSIONS

The LM109 performs a complete regulation function on a single silicon chip, requiring no external components. It makes use of some unique advantages of monolithic construction to achieve performance advantages that cannot be obtained in discrete-component circuits. Further, the low cost of the device suggests its use in applications where single-point regulation could not be justified previously.

Thermal overload protection significantly improves the reliability of an IC regulator. It even protects the regulator for unforeseen fault conditions that may occur in field operation. Although this can be accomplished easily in a monolithic regulator, it is usually not completely effective in a discrete or hybrid device.

The internal reference developed for the LM109 also advances the state of the art for regulators. Not only does it provide a low voltage, temperature-compensated reference for the first time, but also it can be expected to have better long term stability than conventional zeners. Noise is inherently much lower, and it can be manufactured to tighter tolerances.

## REFERENCES

1. R.J. Widlar, "Designing Positive Voltage Regulators," *EEE*, Vol. 17, No. 6, pp. 90-97, June 1969.
2. J.S. Brugler, "Silicon Transistor Biasing for Linear Collector Current Temperature Dependence," *IEEE Journal of Solid State Circuits*, pp. 57-58, June, 1967.
3. R.J. Widlar, "Some Circuit Design Techniques for Linear Integrated Circuits," *IEEE Trans. on Circuit Theory*, Vol. X11, pp. 586-590, December, 1965.
4. R.J. Widlar, "Design of Monolithic Linear Circuits," *Handbook of Semiconductor Electronics*, Chapter X, pp 10.1-10.32, L.P. Hunter, ed., McGraw-Hill Inc., New York, 1970.

# The Phase Locked Loop IC as a Communication System Building Block

National Semiconductor  
 Application Note 46  
 Thomas B. Mills  
 June 1971



## INTRODUCTION

The phase locked loop has been found to be a useful element in many types of communication systems. It is used in two fundamentally different ways: (1) as a demodulator, where it is used to follow phase or frequency modulation and (2) to track a carrier or synchronizing signal which may vary in frequency with time.

When operating as a demodulator, the phase locked loop may be thought of as a matched filter operating as a coherent detector. When used to track a carrier, it may be thought of as a narrow-band filter for removing noise from a signal.

Recently, a phase locked loop has been built on a monolithic integrated circuit, incorporating the basic elements necessary for operation: a double balanced phase detector and a highly linear voltage controlled oscillator, the frequency of which can be varied with either a resistor or capacitor.

## BASIC PHASE LOCK LOOP OPERATION

Figure 1 shows the basic blocks of a phase locked loop. The input signal  $e_i$  is a sinusoid of arbitrary frequency, while the VCO output signal,  $e_o$ , is a sinusoid of the same frequency as the input but of arbitrary phase. If

$$e_i = \sqrt{2} E_i [\sin \omega_o t + \theta_1(t)] \quad (1)$$

$$e_o = \sqrt{2} E_o [\sin \omega_o t + \theta_2(t)] \quad (2)$$

the output of the multiplier (phase detector) is

$$\begin{aligned} e_d &= e_i \cdot e_o = 2E_i E_o \sin [\omega_o t + \theta_1(t)] \\ &\quad \cos [\omega_o t + \theta_2(t)] \\ &= E_i E_o \sin [\theta_1(t) - \theta_2(t)] \\ &\quad + \sin [2\omega_o t + \theta_1(t) + \theta_2(t)] \end{aligned} \quad (3)$$

the low pass filter of the loop removes the ac components of the multiplier output; the dc term is seen to be a function of the phase angle between the VCO and the input signal.

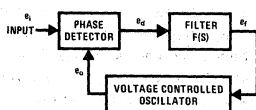


FIGURE 1. Basic Phase Locked Loop

The output of the VCO is related to its input control voltage by

$$\dot{\theta}_2(t) = K_o e_f \quad (4)$$

for  $e_f = 0$ , let  $\dot{\theta}_2 = \omega\theta$ , then

$$\theta_2(t) = \int e_f(t) dt \quad (5)$$

It can be seen that the action of the VCO is that of an integrator in the feedback loop when the phase locked loop is considered in servo theory.

A better understanding of the operation of the loop may be obtained by considering that initially, the loop is not in lock, but that the frequency of the input signal  $e_i$  and VCO  $e_o$  are very close in frequency. Under these conditions  $e_d$  will be a beat note, the frequency of which is equal to the frequency difference of  $e_o$  and  $e_i$ . This signal is also applied to the VCO input, since it is low enough to pass through the filter. The instantaneous frequency of the VCO is therefore changing and at some point in time, if the VCO frequency equals the input frequency, lock will result. At this instant,  $e_f$  will assume a level sufficient to hold the VCO frequency in lock with the input frequency. If the tuning of the VCO is changed (such as by varying the value of the tuning capacitor) the frequency output of the VCO will attempt to change; however, this will result in an instantaneous change in phase angle between  $e_i$  and  $e_o$ , resulting in a change in the dc level of  $e_d$  which will act to maintain frequency lock: no average frequency change will result.

Similarly, if  $e_i$  changes frequency, an instantaneous change will result in a phase change between  $e_i$  and  $e_o$  and hence a dc level change in  $e_d$ . This level shift will change the frequency of the VCO to maintain lock.

The amount of phase error resulting from a given frequency shift can be found by knowing the "dc" loop gain of the system. Considering the phase detector to have a transfer function:

$$E_d = K_D (\theta_1 - \theta_2)$$

and the voltage controlled oscillator to have a transfer function:

$$\dot{\theta}_2 = K_o e_f \quad (6)$$

or taking the Laplace transform

$$\theta_2(s) = \frac{K_o e_f}{s} \quad (7)$$

the phase of the VCO output will be proportional to the integral of the control voltage.

Combining these equations:

$$\frac{\theta_2(s)}{\theta_1(s)} = \frac{K_o K_d F(s)}{s + K_o K_D F(s)} \quad (8)$$

$$\frac{\theta_1(s) - \theta_2(s)}{\theta_1(s)} = \frac{s}{s + K_o K_D F(s)} \quad (9)$$

Application of the final value theorem of Laplace transforms yields

$$\lim_{t \rightarrow \infty} \theta_1(s) - \theta_2(s) = \lim_{s \rightarrow 0} \frac{s^2 \theta_1(s)}{s + K_o K_D F(s)} \quad (10)$$

With a step change in phase of the input  $\Delta\theta_1$ , the Laplace transform of the input is

$$\theta_1(s) = \frac{\Delta\theta_1}{s} \text{ which gives } \theta_e(s) = \theta_1(s) - \theta_2(s)$$

$$\lim_{t \rightarrow \infty} \theta_e(t) = \lim_{s \rightarrow 0} \frac{s \Delta\theta_1}{s + K_o K_D F(s)} = 0 \quad (11)$$

the loop will eventually track out any change of input phase, and there will be no phase error in the steady state solution.

If the input is a step in frequency, of magnitude  $\Delta\omega$ , the change in input phase will be a ramp:

$$\theta_1(s) = \Delta\omega/s^2$$

substitution of this value  $\theta_1$  into (10) results in

$$\lim_{t \rightarrow \infty} \theta_e(t) = \lim_{s \rightarrow 0} \frac{\Delta\omega}{s + K_o K_D F(s)} = \frac{\Delta\omega}{K_o K_D F(0)} \quad (12)$$

this result shows the resulting phase error is dependent on the magnitude of the frequency step and the "dc" loop gain  $K_o K_D$ , which is also called the velocity error coefficient  $K_v$ . It should be noted that the dimensions of  $K_o K_D$  are 1/sec. This can also be seen by considering  $K_D = \text{volts/radian}$ , while  $K_o = \text{radians/sec/volt}$ . The product is

$$\frac{\text{volts}}{\text{radian}} \times \frac{\text{radians/sec}}{\text{volt}} = \frac{1}{\text{sec}}$$

this can be thought of as the "dc" loop gain. (Note that additional dc gain between the phase detector and the voltage controlled oscillator will increase the loop gain and hence reduce the steady state phase error resulting from a change in frequency of the input.)

### THE LOOP FILTER

In working with phase locked loops, it is necessary to consider not only the "dc" performance de-

scribed above, but the "ac" or transient performance which is governed by the components of the loop filter placed between the phase detector and the voltage controlled oscillator. In fact, it is this loop filter that makes the phase locked loop so powerful: only a resistor and capacitor are all that is needed to produce an arbitrarily narrow bandwidth at any selected center frequency.

The simplest filter is a single capacitor, Figure 2, and is used for wide bandwidth applications, such as where wideband data modulation must be followed. The transfer function of the filter is simply:

$$\frac{e_f}{e_d} = \frac{1}{1 + sR_1C_1} \quad (13)$$

substitution into (8) results in

$$\frac{\theta_2(s)}{\theta_1(s)} = \frac{K_o K_D / \tau_1}{s^2 + s/\tau_1 + K_o K_D / \tau_1} \quad (14)$$

$$\tau_1 = R_1 C_1$$

In terms of servo theory, the damping factor and natural frequencies are

$$\omega_n = \left[ \frac{K_o K_D}{R_1 C_1} \right]^{1/2} \quad (15)$$

$$\zeta = \frac{1}{2} \left[ \frac{1}{(R_1 C_1 K_o K_D)} \right]^{1/2} \quad (16)$$

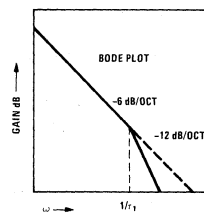
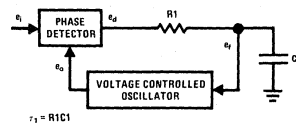


FIGURE 2. Phase Locked Loop with Simple Filter

From this it can be seen that large time constants for  $R_1 C_1$  or high loop gain will reduce the damping factor and hence decrease stability. Therefore, if a narrow bandwidth is desired, the damping factor will become very small and instability will result. It is not possible to adjust bandwidth, loop gain, and damping independently with this simple filter.

With the addition of a damping resistor  $R_2$  as shown in Figure 3, it is possible to choose bandwidth, damping factor and loop gain independently; the transfer function of this filter is

$$\frac{e_d}{e_f} = \frac{s\tau_2 + 1}{s(\tau_1 + \tau_2)} \quad (17)$$

the loop transfer function becomes:

$$\frac{\theta_2(s)}{\theta_1(s)} = \frac{K_o K_D (s\tau_2 + 1)(\tau_1 + \tau_2)}{s^2 + s(1 + K_o K_D \tau_2)/(\tau_1 + \tau_2) + K_o K_D/(\tau_1 + \tau_2)} \quad (18)$$

the loop natural frequency is

$$\omega_n = \left[ \frac{K_o K_D}{\tau_1 + \tau_2} \right]^{1/2} \quad (19)$$

while the damping factor becomes

$$\delta = \frac{1}{2} \left[ \frac{K_o K_D}{\tau_1 + \tau_2} \right]^{1/2} \left[ \tau_2 + \frac{1}{K_o K_D} \right] \quad (20)$$

$$\approx \frac{\omega_n \tau_2}{2} \quad (21)$$

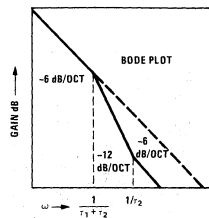
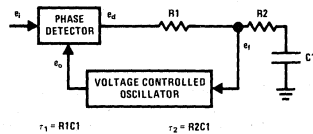


FIGURE 3. Phase Locked Loop with Damping Resistor Added

In practice, for a fixed loop gain  $K_o K_D$ , the natural frequency of the loop may be chosen and will be dependent mainly on  $\tau_1$ , since  $\tau_2 \ll \tau_1$  in most cases. Then, according to (21), damping may be determined by  $\tau_2$  and for all practical purposes, will be an independent adjustment. These equations are plotted in Figures 4 and 5 and may be used for design purposes.

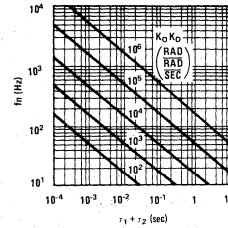


FIGURE 4. Filter Time Constant vs Natural Frequency

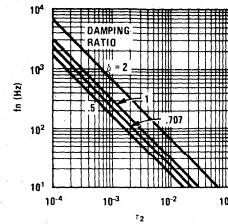


FIGURE 5. Damping Time Constant vs Natural Frequency

## DESIGN CONSIDERATIONS

Considering the above discussion, there are really two primary considerations in designing a phase locked loop. The use to which the loop is to be put will affect the design criterion of the loop components. The two primary factors to consider are:

1. Loop gain. As pointed out previously, this affects the phase error between the input signal and the voltage controlled oscillator for a given frequency shift of the input signal. It also determines the "hold in range" of the loop providing no components of the loop go into limiting or saturation. This is because the loop will remain in lock as long as the phase difference between the input and the VCO is less than  $\pm 90^\circ$ . The higher the loop gain, the further the input can change in frequency before the  $90^\circ$  phase error is reached. The hold in range is

$$\Delta\omega_H = \pm K_o K_D \quad (22)$$

(providing saturation or limiting does not occur).

2. Natural Frequency. The bandwidth of the loop is determined by the filter components  $R_1$ ,  $R_2$  and  $C_1$  and the loop gain. Since the loop gain is normally selected by the criterion in 1. above, the filter components are used to select the bandwidth. The selection of loop bandwidth may be governed by several things: noise bandwidth, modulation rates if the loop is to be

used as an FM demodulator, pull-in time and hold-in range. There are two conflicting requirements that will have an affect on loop bandwidth:

- (a) Loop bandwidth must be as narrow as possible to minimize output phase jitter due to external noise.
- (b) The loop bandwidth should be made as large as possible to minimize transient error due to signal modulation, output jitter due to internal oscillator (VCO) noise, and to obtain best tracking and acquisition properties.

These two principles are in direct opposition and, depending on what it is that the loop is to accomplish, an optimum solution will lie somewhere between the two extremes.

If the phase locked loop is to be used to demodulate frequency modulation, the design should proceed with the criterion of b above. It is necessary to provide sufficient loop bandwidth to accommodate the expected modulation. It must be remembered that at all times, the loop must remain in lock, (peak phase error less than  $90^\circ$ ), even under extremes of modulation, such as peaks or step changes in frequency.

For the case of sinusoidal frequency modulation, the peak phase error as a function of frequency deviation and damping factor is shown in Figure 6.

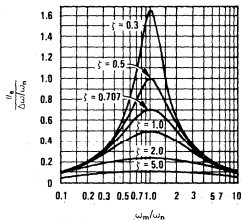


FIGURE 6. Steady-State Peak Phase Error Due to Sinusoidal FM (High-Gain, Second-Order Loop.)

It can be seen that the maximum phase error occurs when the modulating frequency  $\omega_m$  equals the loop natural frequency  $\omega_n$ ; if the loop has been designed with a damping factor of .707, the peak phase error (in radians) will be  $.71 \Delta\omega/\omega_n$  ( $\Delta\omega$  = frequency deviation). From this plot, it is possible to choose  $\omega_n$  for a given deviation and modulation frequency.

If the loop is to demodulate frequency shift keying (FSK), it must follow step changes in frequency. The filter components must then be chosen in accordance with the transient phase error shown in Figure 7. It must be remembered that the loop filter must be wide enough so the loop will not lose lock when a step change in frequency occurs: the greater the frequency step, the wider the loop filter must be to maintain lock.

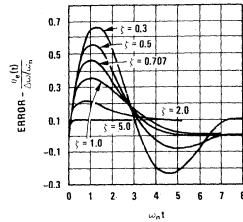


FIGURE 7. Transient Phase Error  $\theta_p(t)$  Due to a Step in Frequency  $\Delta\omega$ . (Steady-State Velocity Error,  $\Delta\omega/K_v$ , Neglected.)

There is some frequency-step limit below which the loop does not skip cycles, but remains in lock, called the "pull-out frequency"  $\omega_{po}$ . Viterbi has analyzed this and his results are shown in Figure 8, which plots normalized pull out frequency for various damping factors for high gain second order loops. Peak phase errors for other types of input signals are shown in Figures 8 and 9.

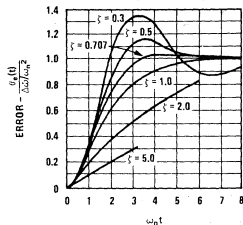


FIGURE 8. Transient Phase Error  $\theta_p(t)$  Due to a Ramp in Frequency  $\Delta\omega$ . (Steady-State Acceleration Error,  $\Delta\omega/\omega_n^2$ , included. Velocity Error,  $\Delta\omega t/K_v$ , Neglected)

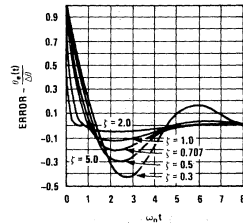


FIGURE 9. Phase Error  $\theta_p(t)$  Due to a Step in Phase  $\Delta\theta$

In designing loops to track a carrier or synchronizing signal, it is desirable to make the loop bandwidth narrow so that phase error due to external noise will be small. However, it is necessary to make the loop bandwidth wide enough so that any frequency jitter on the input signal will be followed.

## NOISE PERFORMANCE

Since one of the main uses of phase locked loops is to demodulate or track signals in noise, it is helpful to look at how noise affects the operation of the phase locked loop.

The phase locked loop, as mentioned earlier, may be thought of as a filter with a fixed, adjustable bandwidth. We have seen how to calculate the loop natural frequency  $\omega_n$  (15), (19), and the damping factor  $\zeta$  (16), (20). Without going through a derivation, the loop noise bandwidth  $B_L$  may be shown to be

$$B_L = \int_0^{\infty} |H(j\omega)|^2 df = \frac{\omega_n}{2} \left[ \zeta + \frac{1}{4\zeta} \right] \text{ Hz} \quad (23)$$

for a high gain, second order loop. This equation is plotted in Figure 10. It should be noted that the dimensions of noise bandwidth are cycles per second while the dimensions of  $\omega_n$  are radians per second.

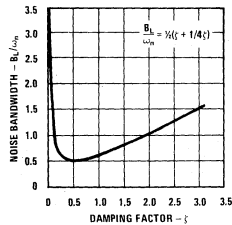


FIGURE 10. Loop-Noise Bandwidth (For High-Gain, Second-Order Loop)

Noise threshold is a difficult thing to analyze in a phase locked loop, since we are talking about a statistical quantity. Noise will show up in the input signal as both amplitude and phase modulation. It can be shown that near optimum performance of a phase locked loop can be obtained if a limiter is used ahead of the phase detector, or if the phase detector is allowed to operate in limiting. With the use of a limiter, amplitude modulation of the input signal by noise is removed, and the noise appears as phase modulation. As the input signal to noise ratio decreases, the phase jitter of the input signal due to noise increases, and the probability of losing lock due to instantaneous phase excursions will increase. In practice it is nearly impossible to acquire lock if the signal to noise ratio in the loop  $(\text{SNR})_L = 0$  dB. In general,  $(\text{SNR})_L$  of +6 dB is needed for acquisition. If modulation or transient phase error is present, a higher signal to noise ratio is needed to acquire and hold lock.

A computer simulation performed by Sanneman and Rowbotham has shown the probability of skipping cycles for various loop signal to noise ratios for high gain, second order loops. Their data is shown in Figure 11.

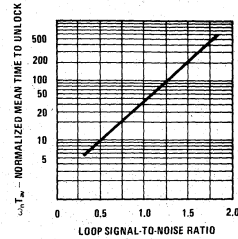


FIGURE 11. Unlock Behavior of High-Gain, Second-Order Loop,  $\zeta = 0.707$

When designing the loop filter components, enough bandwidth in the loop must be allowed for instantaneous phase change due to input noise. In the previous section, the filter was selected on the basis that the peak error due to modulation would be less than  $90^\circ$  (so the loop would not lose lock). However, if noise is present, the peak phase error will increase due to the noise. So if the loop is not to lose lock on these noise peaks, the peak allowable error due to modulation must be reduced to something less, on the order of  $40^\circ$  to  $50^\circ$ .

## LOCKING

Initially, a loop is unlocked and the VCO is running at some frequency. If a signal is applied to the input, locking may or may not occur depending on several things.

If the signal is within the bandwidth of the loop filter, locking will occur without a beat note being generated or any cycles being skipped. This frequency is given by

$$\Delta\omega_L = \frac{K_0 K_D \tau_2}{\tau_1 + \tau_2} \approx 2\zeta \omega_n \quad (24)$$

If the frequency of the input signal is further away from the VCO frequency, locking may still occur, with a beat note being generated. The greatest frequency that can be pulled in is called the "pull in frequency" and is found from the approximation

$$\Delta\omega_p \approx \sqrt{2} (2\zeta \omega_n K_0 K_D - \omega_n^2)^{1/2} \quad (25)$$

which works well for moderate and high gain loops ( $\omega_n/K_0 K_D < .4$ ).

An approximate expression for pull in time (the time required to achieve lock from some frequency offset  $\Delta\omega$ ) is given by:

$$T_P \approx \frac{(\Delta\omega)^2}{2\zeta \omega_n^3}$$

## A MONOLITHIC PHASE LOCKED LOOP

A complete phase locked loop has been built on a monolithic integrated circuit. It features a very

linear voltage controlled oscillator and a double balanced phase detector.

A simplified schematic of this voltage controlled oscillator is shown in Figure 12.  $Q_2$  is a voltage controlled current source whose collector current is a linear function of the control voltage  $e_c$ . Initially  $Q_5$  is OFF and the collector current of  $Q_2$  passes through  $D_2$  and changes  $C$  in a linear fashion. The voltage across  $C$  is therefore a ramp, and continues to increase until  $Q_7$  is turned ON; this turns OFF  $Q_8$ , causing  $Q_9$  and  $Q_{11}$  to turn ON. This in turn turns ON  $Q_5$ . With  $Q_5$  ON, the anode of  $D_1$  is clamped close to  $-V_{CC}$  and  $D_2$  stops conducting, since its cathode is more positive than its anode.

All of the current supplied by  $Q_2$  is diverted through  $D_1$  and  $Q_3$ , which sets up an equal current in  $Q_4$ . This current is supplied by the charged capacitor  $C$  (which now discharges linearly), causing the voltage across it to decrease. This continues until a lower trip point is reached and  $Q_7$  turns OFF and the cycle repeats. Due to the matching of  $Q_3$  and  $Q_4$ , the charge current of  $C$  is equal to the discharge current and therefore the duty cycle is very nearly 50%. Figure 13 shows the wave forms at (1) and (2).

Figure 14 shows the double balanced phase detector and amplifier used in the microcircuit. Transistors  $Q_1$  through  $Q_4$  are switched with the output

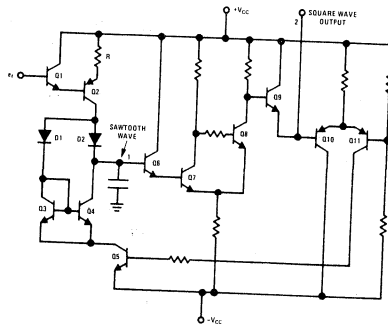


FIGURE 12. Simplified Voltage Controlled Oscillator

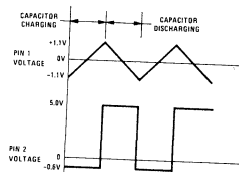


FIGURE 13. VCO Waveforms

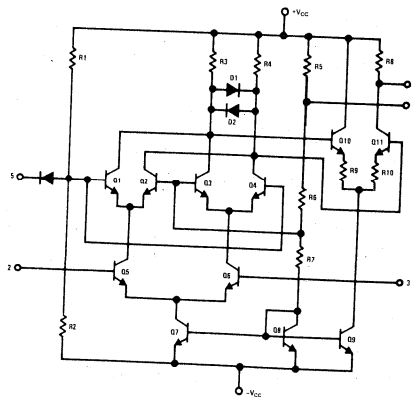


FIGURE 14. Phase Detector and Amplifier



of the VCO, while the input signal is applied to the bases of  $Q_5$  and  $Q_6$ . The output current in resistors  $R_3$  and  $R_4$  is then proportional to the difference in phase between the VCO output and the input; the ac component of this current will be at twice the frequency of the VCO due to the full wave switching action transistors  $Q_1$  through  $Q_4$ . The waveforms of Figure 15 illustrate how the phase detector works. Diodes  $D_1$  and  $D_2$  serve to limit the peak to peak amplitude of the collector voltage. The output of the phase detector is further amplified by  $Q_{10}$  and  $Q_{11}$ , and is taken as a voltage at pin 7.

$R_8$  serves as the resistive portion of the loop filter, and additional resistance and capacitance may be added here to fix the loop bandwidth. For use as an FM demodulator, the voltage at pin 7 will be the demodulated output; since the dc level here is fairly high, a reference voltage has been provided so that an operational amplifier with differential input can be used for additional gain and level shifting.

The complete microcircuit, called the LM565, is shown in Figure 16.

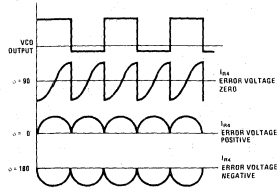


FIGURE 15. Phase Detector Waveforms, Showing Limit Cases for Phase Shift Between Input and VCO Signals

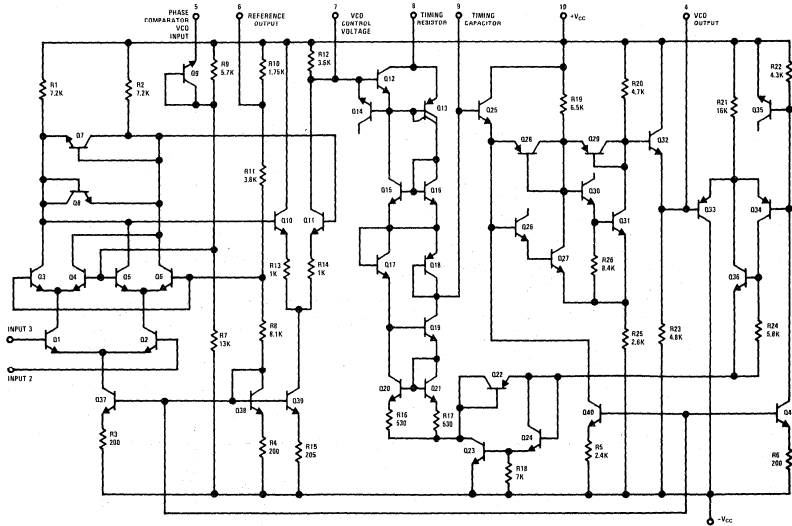


FIGURE 16. LM565 Phase Locked Loop

## USING THE LM565

Some of the important operating characteristics of the LM565 are shown in the table below. ( $V_{CC} = \pm 6V$ ,  $T_A = 25^\circ C$ ).

<b>Phase Detector</b>	
Input Impedance	5 k $\Omega$
Input Level for Limiting	10 mV
Output Resistance	3.6 k $\Omega$
Output Common Mode Voltage	4.5V
Offset Voltage (Between pins 6 and 7)	100 mV
Sensitivity $K_D$	.68V/rad
<b>Voltage Controlled Oscillator</b>	
Stability	
Temperature	200 ppm/ $^\circ C$
Supply Voltage	200 ppm/%
Square Wave Output Pin 4	5.4 V <sub>pp</sub>
Triangle Wave Output Pin 9	2.4 V <sub>pp</sub>
Maximum Operating Frequency	500 kHz
Sensitivity $K_o$	4.1 $f_o$ rad/sec/V
	( $f_o$ : osc. freq. in Hz)
<b>Closed Loop Performance</b>	
Loop Gain $K_o K_D$	2.8 $f_o$ /sec
Demod. Output, $\pm 10\%$ Deviation	300 mV
(A .001 $\mu F$ capacitor is needed between pins 7 and 8 to stop parasitic oscillations).	

To best illustrate how the LM565 is used, several applications are covered in detail, and should provide insight into the selection of external components for use with the LM565.

### IRIG CHANNEL DEMODULATOR

In the field of missile telemetry, it is necessary to send many channels of relatively narrow band data via a radio link. It has been found convenient to frequency modulate this information on a set of subcarriers with center frequencies in the range of 400 Hz to 200 kHz. Standardization of these frequencies was undertaken by the Inter-Range Instrumentation Group (IRIG) and has resulted in several sets of subcarrier channels, some based on deviations that are a fixed percentage of center frequency and other sets that have a constant devia-

tion regardless of center frequency. IRIG channel 13 has been selected as an example of demonstrate the usefulness of the LM565 as an FM demodulator.

IRIG Channel	13
Center Frequency	14.5 kHz
Max Deviation	$\pm 7.5\%$
Frequency Response	220 Hz
Deviation Ratio	5

Since with a deviation of  $\pm 10\%$ , the LM565 will produce approximately 300 mV peak to peak output, with a deviation of 7.5%, we can expect an output of 225 mV. It is desirable to amplify and level shift this signal to ground so that plus and minus output voltages can be obtained for frequency shifts above and below center frequency.

An LM107 can be used to provide the necessary additional gain and the level shift. In Figure 17,  $R_4$  is used to set the output at zero volts with no input signal. The frequency of the VCO can be adjusted with  $R_3$  to provide zero output voltage when an input signal is present.

The design of the filter network proceeds as follows:

It is necessary to choose  $\omega_n$  such that the peak phase error in the loop is less than  $90^\circ$  for all conditions of modulation. Allowing for noise modulation at low levels of signal to noise, a desirable peak phase error might be 1 radian or 57 degrees, leaving a 33 degree margin for noise. Assuming sinusoidal modulation, Figure 6 can be used to estimate the peak normalized phase error. It will be necessary to make several sample calculations, since the normalized phase error is a function of  $\omega_n$ .

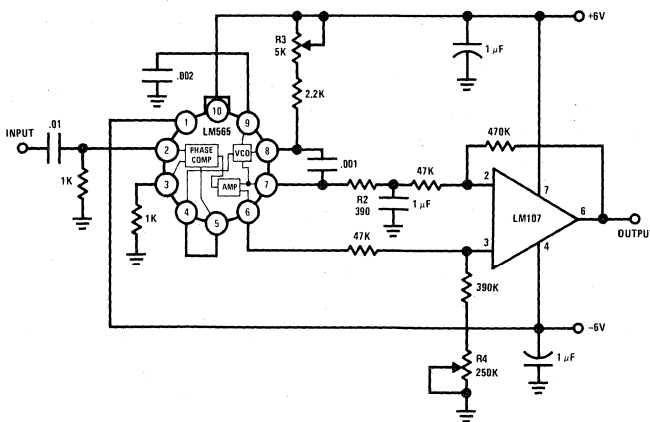


FIGURE 17. IRIG Channel 13 Demodulator

Selecting a worst case of  $\omega_n/\omega_m = 1$ ,  $\omega_n = 2\pi \times 220$  Hz; selecting a damping factor of .707,

$$\frac{\theta}{\Delta\omega/\omega_n} = .702$$

or

$$\theta_e = .702 \frac{\Delta\omega}{\omega_n} = .702 \frac{2\pi \times 1088 \text{ Hz}}{2\pi \times 220 \text{ Hz}} = 3.45 \text{ radians}$$

this is unacceptable, since it would throw the loop out of lock, so it is necessary to try a higher value of  $\omega_n$ . Let  $\omega_n = 2\pi \times 500$  Hz, then  $\omega_m/\omega_n = .44$ , and

$$\theta_e = .44 \frac{\Delta\omega}{\omega_n} = .44 \times \frac{2\pi \times 1088}{2\pi \times 500} = .95 \text{ radians}$$

this should be a good choice, since it is close to radian. Operating at 14.5 kHz, the LM565 has a loop gain  $K_o K_D$  of

$$2.8 \times 14.5 \times 10^3 = 33 \times 10^3 \text{ sec}$$

the value of the loop filter capacitor,  $C_1$ , can be found from Figure 4:

$$\tau_1 + \tau_2 = 3.5 \times 10^{-3} \text{ sec}$$

from Figure 5, the value of  $\tau_2$  can be found (for a damping factor of .707)

$$\begin{aligned} \tau_2 &= 4.4 \times 10^{-4} \text{ sec} \\ \tau_1 &= (35 - 4.4) \times 10^{-4} \text{ sec} = 31.4 \times 10^{-4} \text{ sec} \\ C_1 &= \frac{\tau_1}{R} = \frac{31.4 \times 10^{-4} \text{ sec}}{3.6 \text{ k}\Omega} \cong 1 \mu\text{F} \\ R_2 &= \frac{4.4 \times 10^{-4} \text{ sec}}{1 \times 10^{-6} \mu\text{F}} = 440 \Omega \end{aligned}$$

Looking at Figure 10, the noise bandwidth  $B_L$  can be estimated to be

$$\begin{aligned} B_L &= .6 \omega_n = .6 \times 3150 \text{ rad/sec} \\ &= 1890 \text{ Hz} \end{aligned}$$

the complete circuit is shown in Figure 17. Measured performance of the circuit is summarized below with a fully modulated signal as described above and an input level of 40 mVrms:

f 3 dB	200
$\zeta$	0.8
Output Level	770 mVrms
Distortion	0.4%
Signal to Noise at verge of loss of lock (bandwidth of noise = 100 kHz)	-8.4 dB

It will be noted that the loop is capable of demodulating signals lower in level than the noise; this is not in disagreement with earlier statements that loss of lock occurs at signal to noise ratios

of approximately +6 dB because of the bandwidths involved. The above number of -8.4 dB signal to noise for threshold was obtained with a noise spectrum 100 kHz wide. The noise power in the loop will be reduced by the ratio of loop noise bandwidth to input noise bandwidth

$$\frac{B_{\text{LOOP}}}{B_{\text{INPUT}}} = \frac{1890 \text{ Hz}}{100 \text{ kHz}} = .02 \text{ or } -17 \text{ dB}$$

the equivalent signal to noise in the loop is -8.4 dB +17 dB = +8.6 dB which is close to the above-mentioned limit of +6 dB. It should also be noted that loss of lock was noted with full modulation of the signal which will degrade threshold somewhat (although the measurement is more realistic).

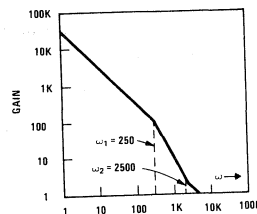


FIGURE 18. Bode Plot for Circuit of Figure 17

## FSK DEMODULATOR

Frequency shift keying (FSK) is widely used for the transmission of Teletype information, both in the computer peripheral and communications field. Standards have evolved over the years, and the commonly used frequencies are as follows:

a)	mark	2125	Hz
	space	2975	Hz
b)	mark	1070	Hz
	space	1270	Hz
c)	mark	2025	Hz
	space	2225	Hz

a) is commonly used as subcarrier tones for radio Teletype, while b) and c) are used as carriers for data transmission over telephone and land lines.

As a design example, a demodulator for the 2025 Hz and 2225 Hz mark the space frequencies will be discussed.

Since this is an FM system employing square wave modulation, the natural frequency of the loop must be chosen again so that peak phase errors do not exceed 90° under all conditions. Figure 7 shows peak phase error for a step in frequency; if a damping factor of .707 is selected, the peak phase error is

$$\frac{\theta_e}{\Delta\omega/\omega_n} = .45$$

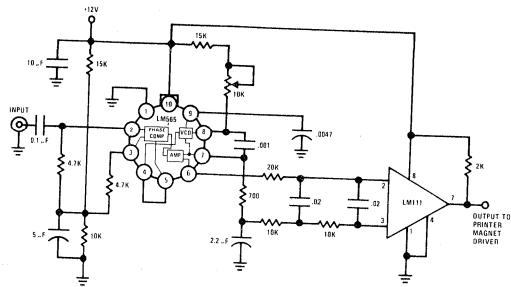


FIGURE 19. FSK Demodulator (2025-2225 cps)

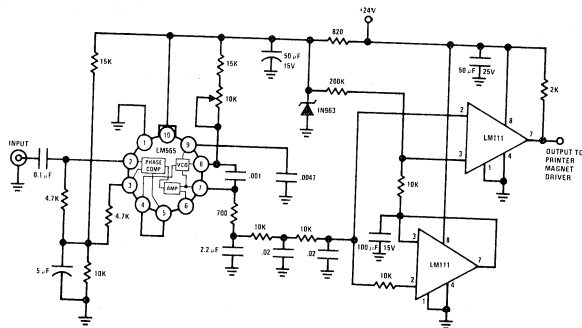


FIGURE 20. FSK Demodulator with DC Restoration

or

$$\theta_e = .45 \frac{\Delta\omega}{\omega_n}$$

$$\omega_n = .45 \frac{\Delta\omega}{\theta_e}$$

in our case,  $\Delta\omega = 2 \pi \times 200 \text{ Hz} = 1250$ , if  $\theta_e = 1$  radian,

$$\omega_n = .45 \frac{1250 \text{ rad/sec}}{1 \text{ radian}} = 500 \text{ rad/sec}$$

$$f_n = 80 \text{ Hz}$$

The final circuit is shown in Figure 19. The values of the loop filter components ( $C_1 = 2.2 \mu\text{F}$  and  $R_1 = 700\Omega$ ) were changed to accommodate a keying rate of 300 bauds (150 Hz), since the

values calculated above caused too much roll off of a square wave modulation signal of 150 Hz. The two 10K resistors and .02  $\mu\text{F}$  capacitors at the input to the LM111 comparator provide further filtering of the carrier, and hence smoother operation of the circuit.

A problem encountered with this simple demodulator is that of dc drift. The frequency must be adjusted to provide zero volts to the input of the comparator so that with modulation, switching occurs. Since the deviation of the signal is small (approximately 10%), the peak to peak demodulated output is only 150 mV. It should be apparent that any drift in frequency of the VCO will cause a dc change and hence may lock the comparator in one state or the other. A circuit to overcome this problem is shown in Figure 20. While using the same basic demodulator configuration, an

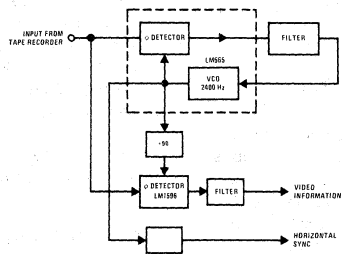


FIGURE 21. Block Diagram of Weather Satellite Demodulator

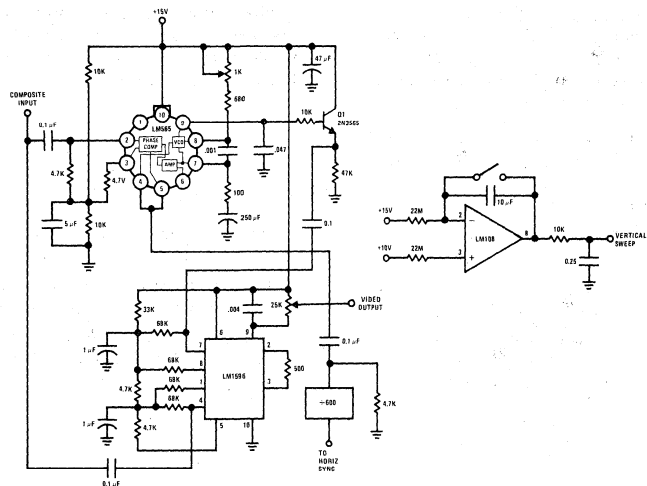


FIGURE 22. Weather Satellite Picture Demodulator

LM111 is used as an accurate peak detector to provide a dc bias for one input to the comparator. When a "space" frequency is transmitted, and the output at pin 7 of the LM565 goes negative and switching occurs, the detected and filtered voltage of pin 3 to the comparator will not follow the change. This is a form of "dc restorer" circuit: it will track changes in drift, making the comparator self compensating for changes in frequency, etc.

#### WEATHER SATELLITE PICTURE DEMODULATOR

As a last example of how a phase locked loop can be used in communications systems, a weather satellite picture demodulator is shown. Weather satellites of the Nimbus, ESSA, and ITOS series continually photograph the earth from orbits of 100 to 800 miles. The pictures are stored immediately after exposure in an electrostatic storage vidicon, and read out during a succeeding 200 second period. The video information is AM modu-

lated on a 2.4 kHz subcarrier which is frequency modulated on a 137.5 MHz RF carrier. Upon reception, the output from the receiver FM detector will be the 2.4 kHz tone containing AM video information. It is common practice to record the tone on an audio quality tape recorder for subsequent demodulation and display. The 2.4 kHz subcarrier frequency may be divided by 600 to obtain the horizontal sync frequency of 4 Hz.

Due to flutter in the tape recorder, noise during reception, etc., it is desirable to reproduce the 2.4 kHz subcarrier with a phase locked loop, which will track any flutter and instability in the recorder, and effectively filter out noise, in addition to providing a signal large enough for the digital frequency divider. In addition, an in phase component of the VCO signal may be used to drive a synchronous demodulator to detect the video information. A block diagram of the system is shown in Figure 21, and a complete schematic in Figure 22.

The design of the loop parameters was based on the following objectives

$$f_n = 10 \text{ Hz}, \omega_n = 75 \text{ rad/sec}$$

$$B_L = 40 \text{ Hz (from Figure 10)}$$

the complete loop filter, calculated from Figures 4 and 5, is shown in Figure 22. When the loop is in lock and the free running frequency of the VCO is 2.4 kHz, the VCO square wave at pin 4 of the 565 will be in quadrature ( $90^\circ$ ) from the input signal; however, the zero crossings of the triangle wave across the timing capacitor will be in phase, and if their signal is applied to a double balanced demodulator, such as an LM1596, switching will occur in the demodulator in phase with the 2.4 kHz subcarrier. The double balanced demodulator will produce an output proportional to the amplitude of the subcarrier applied to its signal input. An emitter follower,  $Q_1$ , is used to buffer the triangle wave across the timing capacitor so excessive loading does not occur.

The demodulated video signal from the LM1596 is taken across a 25k potentiometer and filtered to a bandwidth of 1.4 kHz, the bandwidth of the transmitted video. Depending on the type of display to be used (oscilloscope, slow scan TV monitor, of facsimile reproducer), it may be necessary to further buffer or amplify the signal obtained. If desired, another load resistor may be used between pin 6 and VCO to obtain a differential output; an operational amp could then be used to provide more gain, level shift, etc.

A vertical sweep circuit is shown using an LM308 low input current op amp as a Miller rundown circuit. The values are chosen to produce an output voltage ramp of  $-4.5V/220 \text{ sec}$ , although this may be adjusted by means of the 22 meg. charging resistor. If an oscilloscope is used as a readout, the horizontal sync can be supplied to the trigger input with the sweep set to provide a total sweep time of something less than 250 ms. A camera is used to photograph the 200 second picture.

## SUMMARY AND CONCLUSIONS

A brief review of phase lock techniques has been presented and several useful design tools have been presented that may be useful in predicting the performance of phase locked loops.

A phase locked loop integrated circuit has been described and several applications have been given to illustrate the use of the circuit and the design techniques presented.

## REFERENCES

1. Floyd M. Gardner, "Phaselock Techniques", John Wiley and Sons, 1966.
2. Elliot L. Greenberg, "Handbook of Telemetry and Remote Control", McGraw-Hill, 1967.
3. Andrew Viterbi, "Principles of Coherent Communication", McGraw-Hill, 1966.

# Applications for a New Ultra-High Speed Buffer

National Semiconductor  
 Application Note 48  
 Barry Siegel  
 Leonard Van Der Gaag  
 August 1971



## INTRODUCTION

Voltage followers have gained in popularity in applications such as sample and hold circuits, general purpose buffers, and active filters since the introduction of IC operational amplifiers. Since they were not specifically designed as followers, these early IC's had limited usage due to low bandwidth, low slew rate and high input current. Usage of voltage followers was expanded in 1967 with the introduction of the LM102, the first IC designed specifically as a voltage follower. With the LM102, engineers were able to obtain an order of magnitude improvement in performance and extend usage into medium speed applications. The LM110, an improved LM102, was introduced in late 1969. However, even higher speeds and lower input currents were needed for very fast sample and holds, A to D and D to A converters, coax cable drivers, and other video applications.

The solution to this application problem was attained by combining technologies into a single package. The result, the LH0033 high speed buffer, utilizes JFET and bipolar technology to produce a ultra-fast voltage follower and buffer whose propagation delay closely approaches speed-of-light delay across its package, while not compromising input impedance or drive characteristics. Table I compares various voltage followers and illustrates the superiority of the LH0033 in both low input current or high speed video applications.

## CIRCUIT CONSIDERATIONS

The junction FET makes a nearly ideal input device for a voltage follower, reducing input bias current to the picoamp range. However, FET's exhibit moderate voltage offsets and offset drifts which tend to be difficult to compensate. The simple voltage follower of Figure 1 eliminates initial offset and offset drift if  $Q_1$  and  $Q_2$  are identically matched transistors. Since the gate to source voltage of  $Q_2$  equals zero volts, then  $Q_1$ 's gate to source voltage equals zero volts. Furthermore as  $V_{P1}$  changes with temperature (approximately  $2.2 \text{ mV}/^\circ\text{C}$ ),  $V_{P2}$  will change by a corresponding amount. However, as load current is drawn

from the output,  $Q_1$  and  $Q_2$  will drift at different rates. A circuit which overcomes offset voltage drift is used in a new high speed buffer amplifier, the LH0033. Initial offset is typically 5 mV and offset drift is  $20 \mu\text{V}/^\circ\text{C}$ . Resistor  $R_2$  is used to establish the drain current of current source transistor,  $Q_2$  at 10 mA.

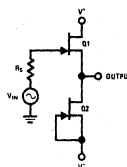


FIGURE 1. Simple Voltage Follower Schematic

The same drain current flows through  $Q_1$  causing a voltage at the source of approximately 1.1V. The 10 mA flowing through  $R_1$  plus  $Q_3$ 's  $V_{BE}$  of 0.6V causes the output to sit at zero volts for zero volts in.  $Q_3$  and  $Q_4$  eliminate loading the input stage (except for base current) and  $CR_1$  and  $CR_2$  establish the output stage collector current.

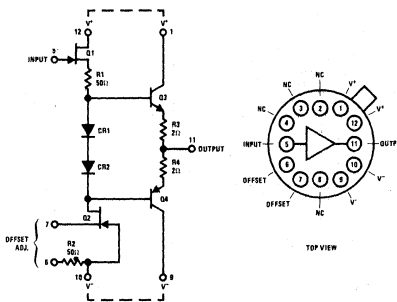


FIGURE 2. LH0033 Schematic

If  $Q_1$  and  $Q_2$  are matched, the resulting drift is reduced to a few  $\mu\text{V}/^\circ\text{C}$ .

TABLE I COMPARISON OF VOLTAGE FOLLOWERS

PARAMETER	CONVENTIONAL MONOLITHIC OP AMP LM741	FIRST GENERATION VOLTAGE FOLLOWER LM102	SECOND GENERATION VOLTAGE FOLLOWER LM110	SPECIALLY DESIGNED VOLTAGE FOLLOWER LH0033
INPUT BIAS CURRENT	200 nA	3.0 nA	1.0 nA	0.05 nA
SLEW RATE	0.5V/ $\mu\text{s}$	10V/ $\mu\text{s}$	30V/ $\mu\text{s}$	1500V/ $\mu\text{s}$
BANDWIDTH	1.0 MHz	10 MHz	20 MHz	100 MHz
PROP. DELAY TIME	350 ns	35 ns	18 ns	1.2 ns
OUTPUT CURRENT CAPABILITY	$\pm 5 \text{ mA}$	$\pm 2 \text{ mA}$	$\pm 2 \text{ mA}$	$\pm 100 \text{ mA}$

## PERFORMANCE OF THE LH0033 FAST VOLTAGE FOLLOWER/BUFFER

The major electrical characteristics of the LH0033 are summarized in Table II. All the virtues of an ultra-high speed buffer have been incorporated. Figure 3 is a plot of input bias current vs temperature and shows the typical FET input character-

istics. Other typical performance curves are illustrated in Figures 4 through 10. Of particular interest is Figure 8, which demonstrates the performance of the LH0033 in video applications to over 100 MHz.

TABLE II

PARAMETER	CONDITIONS	VALUE	PARAMETER	CONDITIONS	VALUE
Output Offset Voltage	$R_B = 100 \text{ k}\Omega$	5 mV	Output Current Capability		$\pm 100 \text{ mA peak}$
Input Bias Current		50 pA	Slew Rate	$R_B = 50\Omega, R_L = 1\text{k}$	1500V/ $\mu\text{s}$
Input Impedance	$V_{IN} = 1.0 \text{ Vrms}$ $R_L = 1\text{k}, f = 1 \text{ kHz}$	$10^{11} \Omega$	Propagation Delay		1.2 ns
Voltage Gain	$V_{IN} = 1.0 \text{ Vrms}$ $R_L = 1\text{k}, f = 1 \text{ kHz}, R_B = 100\text{k}$	0.98	Bandwidth	$V_{IN} = 1.0 \text{ Vrms}$ $R_B = 50\Omega, R_L = 1\text{k}$	100 MHz
Output Voltage Swing	$V_S = \pm 15\text{V}, R_B = 100\text{k}$ $R_L = 1\text{k}$	$\pm 13\text{V}$			

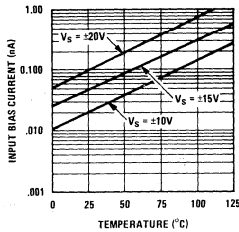


FIGURE 3. Input Bias Current vs Temperature

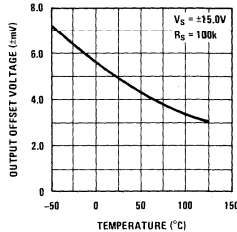


FIGURE 4. Output Offset Voltage vs Temperature

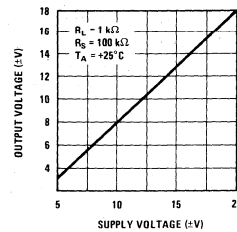


FIGURE 5. Output Voltage vs Supply Voltage

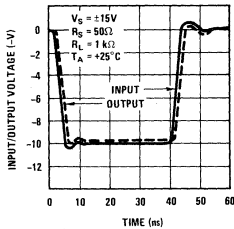


FIGURE 6. Negative Pulse Response

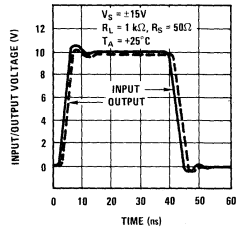


FIGURE 7. Positive Pulse Response

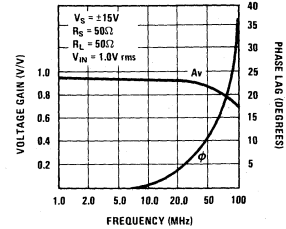


FIGURE 8. Frequency Response

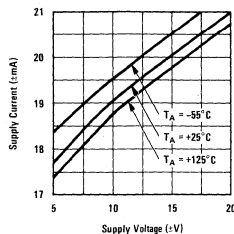


FIGURE 9. Supply Current vs Supply Voltage

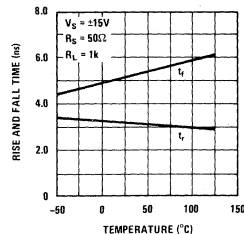


FIGURE 10. Rise and Fall Time vs Temperature



## APPLICATIONS FOR ULTRA-FAST FOLLOWERS

The LH0033's high input impedance ( $10^{11} \Omega$ , shunted by 2 pF) and high slew rate assure minimal loading and high fidelity in following high speed pulses and signals. As shown below, the LH0033 is used as a buffer between MOS logic and a high speed dual limit comparator. The device's high input impedance prevents loading of the MOS logic signal (even a conventional scope probe will distort high output impedance MOS). The LH0033 adds about a 1.5 ns to the total delay of the comparator. Adjustment of voltage divider  $R_1, R_2$  allows interface to TTL, DTL and other high speed logic forms.

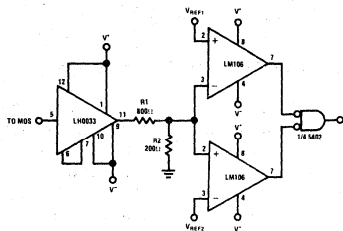


FIGURE 11. High Speed Dual Limit Comparator for MOS Logic

The LH0033 was designed to drive long cables, shielded cables, coaxial cables and other generally stringent line driving requirements. It will typically drive 200 pF with no degradation in slew rate and several thousand pF at a reduced rate. In order to prevent oscillations with large capacitive loads, provision has been made to insert damping resistors between  $V^+$  and pin 1, and  $V^-$  and pin 9. Values between 47 and  $100 \Omega$  work well for  $C_L > 1000$  pF. For non-reactive loads, pin 12 should be shorted to pin 1 and pin 10 shorted to pin 9. A coaxial driver is shown in Figure 13. Pin 6 is shorted to pin 7, obtaining an initial offset of 5.0 mV, and the  $43 \Omega$  coupled with the LH0033's output impedance (about  $6 \Omega$ ) match the coaxial cable's characteristic impedance.  $C_1$  is adjusted as a function of cable length to optimize rise and fall time. Rise time for the circuit as shown in Figure 12, is 10 ns.

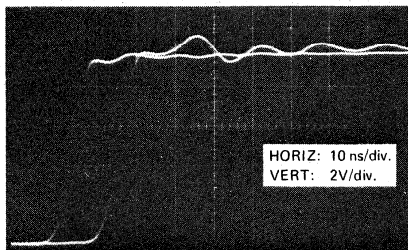


FIGURE 12. LH0033 Pulse Response into 10 Foot Open Ended Coaxial Cable

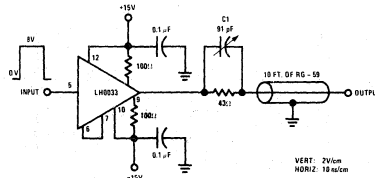


FIGURE 13.

Another application that utilizes the low input current, high speed and high capacitance drive capabilities of the LH0033 is a shield or line driver for high speed automatic test equipment. In this example, the LH0033 is mounted close to the device under test and drives the cable shield thus allowing higher speed operation since the device under test does not have to charge the cable.

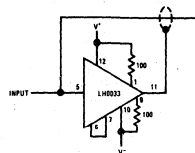


FIGURE 14. Instrumentation Shield/Line Driver

The LH0033's high input impedance and low input bias current may be utilized in medium speed circuits such as Sample and Hold, and D to A converters. Figure 15 shows an LH0033 used as a buffer in medium speed D to A converter.

Offset null is accomplished by connecting a  $100 \Omega$  pot between pin 7 and  $V^-$ . It is generally a good idea to insert  $20 \Omega$  in series with the pot to prevent excessive power dissipation in the LH0033 when the pot is shorted out. In non-critical or AC coupled applications, pin 6 should be shorted to pin 7. The resulting output offset is typically 5 mV at  $25^\circ \text{C}$ .

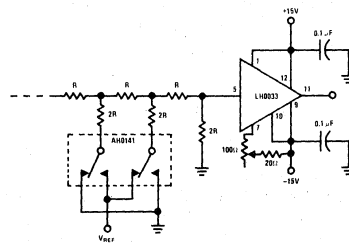


FIGURE 15.

The high output current capability and slew rate of the LH0033 are utilized in the sample and hold circuit of Figure 16. Amplifier, A1 is used to buffer high speed analog signals. With the configuration shown, acquisition time is limited by the time constant of the switch "ON" resistance and sampling capacitor, and is typically 200 or 300 ns.  $A_2$ 's low input bias current, results in drifts in hold mode of  $\frac{50 \text{ mV}}{\text{sec}}$  at  $25^\circ \text{C}$  and  $\frac{1 \text{ V}}{\text{sec}}$  at  $125^\circ \text{C}$ .

The LH0033 may be utilized in AC applications such as video amplifiers and active filters. The circuit of Figure 17 utilizes boot strapping to achieve input impedances in excess of  $10 \text{ M}\Omega$ .

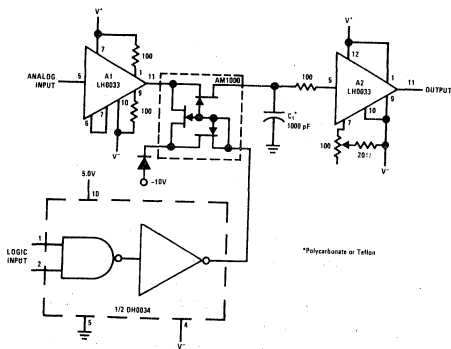


FIGURE 16. High Speed Sample & Hold

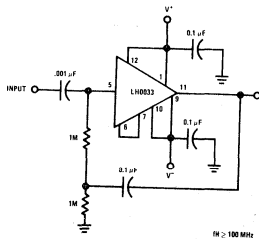


FIGURE 17. High Input Impedance AC Coupled Amplifier

A single supply, AC coupled amplifier is shown in Figure 18. Input impedance is approximately 500k and output swing is in excess of 8V peak-to-peak with a 12V supply.

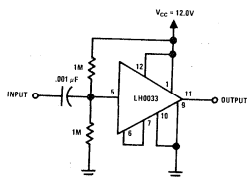


FIGURE 18. Single Supply AC Amplifier

The LH0033 may be readily used in applications where symmetrical supplies are unavailable or may not be desirable. A typical application might be an interface to a MOS shift register where  $V^+ = 5.0V$  and  $V^- = -25V$ . In this case, an apparent output offset occurs. In reality, the output voltage is due to the LH0033's voltage gain of less than unity. The output voltage shift due to asymmetric supplies may be predicted by:

$$\Delta V_O \cong (1 - A_v) \frac{(V^+ - V^-)}{2} = .005 (V^+ - V^-)$$

where:  $A_v$  = No load voltage gain, typically 0.99.  
 $V^+$  = Positive Supply Voltage.  
 $V^-$  = Negative Supply Voltage.

For the foregoing application,  $\Delta V_O$  would be  $-100$  mV. This apparent "offset" may be adjusted to zero as outlined above.

Figure 19 shows a high  $Q$ , notch filter which takes advantage of the LH0033's wide bandwidth. For the values shown, the center frequency is 4.5 MHz.

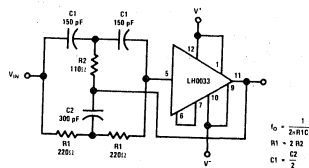


FIGURE 19. 4.5 MHz Notch Filter

The LH0033 can also be used in conjunction with an operational amplifier as current booster as shown in Figure 20. Output currents in excess of 100 mA may be obtained. Inclusion of  $150\Omega$  resistors between pins 1 and 12, and 9 and 10 provide short circuit protection, while decoupling pins 1 and 9 with 1000 pF capacitors allow near full output swing.

The value for the short circuit current is given by:

$$I_{SC} \cong \frac{V^+}{R_{LIMIT}} = \frac{V^-}{R_{LIMIT}}$$

where:  $I_{SC} \leq 100$  mA.

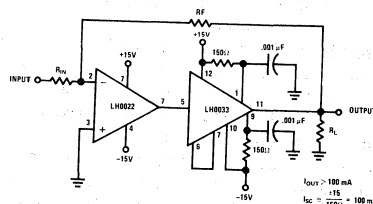


FIGURE 20. Using LH0033 as an Output Buffer

## SUMMARY

The advantages of a FET input buffer have been demonstrated. The LH0033 combines very high input impedance, wide bandwidth, very high slew rate, high output capability, and design flexibility, making it an ideal buffer for applications ranging from DC to in excess of 100 MHz.

## 1.2 Volt Reference

National Semiconductor  
Application Note 56  
Robert C. Dobkin  
December 1971



### INTRODUCTION

Temperature compensated zener diodes are the most easily used voltage reference. However, the lowest voltage temperature-compensated zener is 6.2 volts. This makes it inconvenient to obtain a zero temperature-coefficient reference when the operating supply voltage is 6 volts or lower. With the availability of the LM113, this problem no longer exists.

The LM113 is a 1.2V temperature compensated shunt regulator diode. The reference is synthesized using transistors and resistors rather than a breakdown mechanism. It provides extremely tight regulation over a wide range of operating currents in addition to unusually low breakdown voltage and low temperature coefficient.

### DESIGN CONCEPTS

The reference in the LM113 is developed from the highly-predictable emitter-base voltage of integrated transistors. In its simplest form, the voltage is equal to the energy-band-gap voltage of the semiconductor material. For silicon, this is 1.205V. Further, the output voltage is well determined in a production environment.

A simplified version of this reference<sup>1</sup> is shown in Figure 1. In this circuit, Q<sub>1</sub> is operated at a relatively high current density. The current density of Q<sub>2</sub> is about ten times lower, and the emitter-base voltage differential ( $\Delta V_{BE}$ ) between the two devices appears across R<sub>3</sub>. If the transistors have high current gains, the voltage across R<sub>2</sub> will also

be proportional to  $\Delta V_{BE}$ . Q<sub>3</sub> is a gain stage that will regulate the output at a voltage equal to its emitter base voltage plus the drop across R<sub>2</sub>. The emitter base voltage of Q<sub>3</sub> has a negative temperature coefficient while the  $\Delta V_{BE}$  component across R<sub>2</sub> has a positive temperature coefficient. It will be shown that the output voltage will be temperature compensated when the sum of the two voltages is equal to the energy-band-gap voltage.

Conditions for temperature compensation can be derived starting with the equation for the emitter-base voltage of a transistor which is<sup>2</sup>

$$V_{BE} = V_{g0} \left( 1 - \frac{T}{T_0} \right) + V_{BE0} \left( \frac{T}{T_0} \right) + \frac{nkT}{q} \log_e \frac{T_0}{T} + \frac{kT}{q} \log_e \frac{I_C}{I_{C0}} \quad (1)$$

where  $V_{g0}$  is the extrapolated energy-band-gap voltage for the semiconductor material at absolute zero,  $q$  is the charge of an electron,  $n$  is a constant which depends on how the transistor is made (approximately 1.5 for double-diffused, NPN transistors),  $k$  is Boltzmann's constant,  $T$  is absolute temperature,  $I_C$  is collector current and  $V_{BE0}$  is the emitter-base voltage at  $T_0$  and  $I_{C0}$ .

The emitter-base voltage differential between two transistors operated at different current densities is given by

$$\Delta V_{BE} = \frac{kT}{q} \log_e \frac{J_1}{J_2} \quad (2)$$

where  $J$  is current density.

Referring to Equation (1), the last two terms are quite small and are made even smaller by making  $I_C$  vary as absolute temperature. At any rate, they can be ignored for now because they are of the same order as errors caused by nontheoretical behavior of the transistors that must be determined empirically.

If the reference is composed of  $V_{BE}$  plus a voltage proportional to  $\Delta V_{BE}$ , the output voltage is obtained by adding (1) in its simplified form to (2):

$$V_{ref} = V_{g0} \left( 1 - \frac{T}{T_0} \right) + V_{BE0} \left( \frac{T}{T_0} \right) + \frac{kT}{q} \log_e \frac{J_1}{J_2} \quad (3)$$

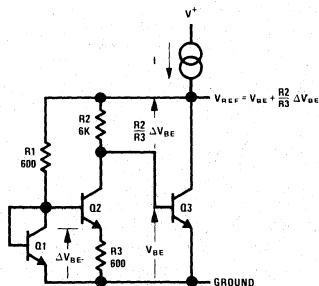


FIGURE 1. The Low Voltage Reference in One of Its Simpler Forms.

Differentiating with respect to temperature yields

$$\frac{\partial V_{ref}}{\partial T} = -\frac{V_{g0}}{T_0} + \frac{V_{BE0}}{T_0} + \frac{k}{q} \log_e \frac{J_1}{J_2} \quad (4)$$

For zero temperature drift, this quantity should equal zero, giving

$$V_{g0} = V_{BE0} + \frac{kT_0}{q} \log_e \frac{J_1}{J_2} \quad (5)$$

The first term on the right is the initial emitter-base voltage while the second is the component proportional to emitter-base voltage differential. Hence, if the sum of the two are equal to the energy-band-gap voltage of the semiconductor, the reference will be temperature-compensated.

Figure 2 shows the actual circuit of the LM113. Q<sub>1</sub> and Q<sub>2</sub> provide the  $\Delta V_{BE}$  term and Q<sub>4</sub> provides the V<sub>BE</sub> term as in the simplified circuit. The additional transistors are used to decrease the dynamic resistance, improving the regulation of the reference against current changes. Q<sub>3</sub> in conjunction with current inverter, Q<sub>5</sub> and Q<sub>6</sub>, provide a current source load for Q<sub>4</sub> to achieve high gain.

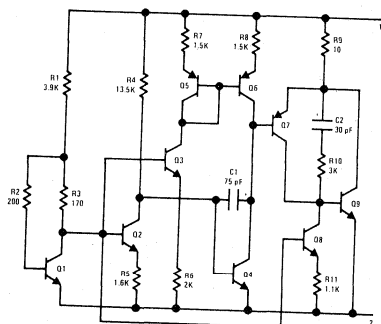


FIGURE 2. Schematic of the LM113

Q<sub>7</sub> and Q<sub>9</sub> buffer Q<sub>4</sub> against changes in operating current and give the reference a very low output resistance. Q<sub>8</sub> sets the minimum operating current of Q<sub>7</sub> and absorbs any leakage from Q<sub>9</sub>. Capacitors C<sub>1</sub>, C<sub>2</sub> and resistors R<sub>9</sub> and R<sub>10</sub> frequency compensate the regulator diode.

## PERFORMANCE

The most important features of the regulator diode are its good temperature stability and low dynamic resistance. Figure 3 shows the typical change in output voltage over a -55°C to +125°C temperature range. The reference voltage changes less than 0.5% with temperature, and the temperature coefficient is relatively independent of operating current.

Figure 4 shows the output voltage change with operating current. From 0.5 mA to 20 mA there is only about 6 mV of change. A good portion of the output change is due to the resistance of the aluminum bonding wires and the Kovar leads on the package. At currents below about 0.3 mA the diode no longer regulates. This is because there is insufficient current to bias the internal transistors into their active region. Figure 5 illustrates the breakdown characteristic of the diode.

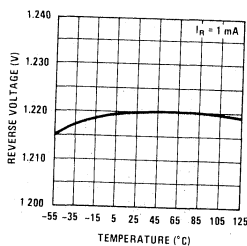


FIGURE 3. Output Voltage Change with Temperature

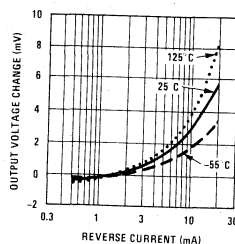


FIGURE 4. Output Voltage Change with Current

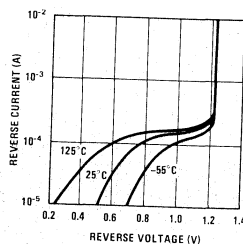


FIGURE 5. Reverse Breakdown Characteristics

## APPLICATIONS

The applications for zener diodes are so numerous that no attempt to delineate them will be made. However, the low breakdown voltage and the fact that the breakdown voltage is equal to a physical property of silicon — the energy band gap voltage — makes it useful in several interesting applications.

Also the low temperature coefficient makes it useful in regulator applications — especially in battery powered systems where the input voltage is less than 6V.

Figure 6 shows a 2V voltage regulator which will operate on input voltages of only 3V. An LM113 is the voltage reference and is driven by a FET current source,  $Q_1$ . An operational amplifier compares a fraction of the output voltage with the reference. Drive is supplied to output transistor  $Q_2$  through the  $V^+$  power lead of the operational amplifier. Pin 6 of the op amp is connected to the LM113 rather than the output since this allows a lower minimum input voltage. The dynamic resistance of the LM113 is so low that current changes from the output of the operational amplifier do not appreciably affect regulation. Frequency compensation is accomplished with both the 50 pF and the 1  $\mu$ F output capacitor.

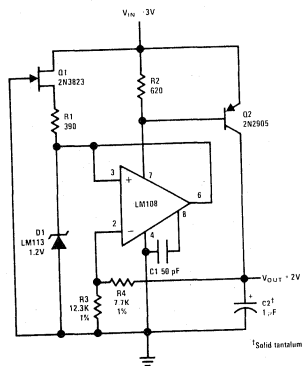


FIGURE 6. Low Voltage Regulator Circuit

It is important to use an operational amplifier with low quiescent current such as an LM108. The quiescent current flows through  $R_2$  and tends to turn on  $Q_2$ . However, the value shown is low enough to insure that  $Q_2$  can be turned off at worst case condition of no load and 125°C operation.

Figure 7 shows a differential amplifier with the current source biased by an LM113. Since the LM113 supplies a reference voltage equal to the energy band gap of silicon, the output current of the 2N2222 will vary as absolute temperature. This compensates the temperature sensitivity of the transconductance of the differential amplifier making the gain temperature stable. Further, the operating current is regulated against supply variations keeping the gain stable over a wide supply range.

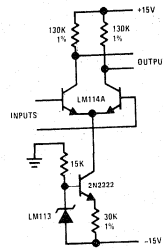


FIGURE 7. Amplifier Biasing for Constant Gain with Temperature

As shown, the gain will change less than two per cent over a -55°C to +125°C temperature range. Using the LM114A monolithic transistor and low drift metal film resistors, the amplifier will have less than 2  $\mu$ V/°C voltage drift. Even lower drift may be obtained by unbalancing the collector load resistors to null out the initial offset. Drift under nullled condition will be typically less than 0.5  $\mu$ V/°C.

The differential amplifier may be used as a pre-amplifier for a low-cost operational amplifier such as an LM101A to improve its voltage drift characteristics. Since the gain of the operational amplifier is increased by a factor of 100, the frequency compensation capacitor must also be increased from 30 pF to 3000 pF for unity gain operation. To realize low voltage drift, care must be taken to minimize thermoelectric potentials due to temperature gradients. For example, the thermoelectric potential of some resistors may be more than 30  $\mu$ V/°C, so a 1°C temperature gradient across the resistor on a circuit board will cause much larger errors than the amplifier drift alone. Wirewound resistors such as Evenohm are a good choice for low thermoelectric potential.

Figure 8 illustrates an electronic thermometer using an inexpensive silicon transistor as the temperature sensor. It can provide better than 1°C

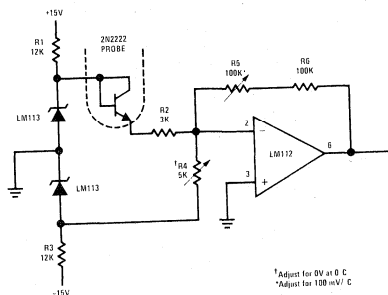


FIGURE 8. Electronic Thermometer

accuracy over a  $100^{\circ}\text{C}$  range. The emitter-base turn-on voltage of silicon transistors is linear with temperature. If the operating current of the sensing transistor is made proportional to absolute temperature the nonlinearity of emitter-base voltage can be minimized. Over a  $-55^{\circ}\text{C}$  to  $125^{\circ}\text{C}$  temperature range the nonlinearity is less than 2 mV or the equivalent of  $1^{\circ}\text{C}$  temperature change.

An LM113 diode regulates the input voltage to 1.2V. The 1.2V is applied through  $R_2$  to set the operating current of the temperature-sensing transistor.

Resistor  $R_4$  biases the output of the amplifier for zero output at  $0^{\circ}\text{C}$ . Feedback resistor  $R_5$  is then used to calibrate the output scale factor to  $100\text{ mV}/^{\circ}\text{C}$ . Once the output is zeroed, adjusting the scale factor does not change the zero.

#### CONCLUSION

A new two terminal low voltage shunt regulator has been described. It is electrically equivalent to a temperature-stable 1.2V breakdown diode. Over a  $-55^{\circ}\text{C}$  to  $125^{\circ}\text{C}$  temperature range and operating currents of 0.5 mA to 20 mA the LM113

has one hundred times better reverse characteristics than breakdown diodes. Additionally, wide-band noise and long term stability are good since no breakdown mechanism is involved.

The low temperature coefficient and low regulation voltage make it especially suitable for a low voltage regulator or battery operated equipment. Circuit design is eased by the fact that the output voltage and temperature coefficient are largely independent of operating current. Since the reference voltage is equal to the extrapolated energy-band-gap of silicon, the device is useful in many temperature compensation and temperature measurement applications.

#### REFERENCES

1. R.J. Widlar, "On Card Regulator for Logic Circuits," National Semiconductor AN-42, February, 1971.
2. J.S. Brugler, "Silicon Transistor Biasing for Linear Collector Current Temperature Dependence," IEEE Journal of Solid State Circuits, pp. 57-58, June, 1967.

# LM381 Low Noise Dual Preamplifier

National Semiconductor  
Application Note 64  
Joe E. Byerly  
Ernest L. Long  
May 1972



## INTRODUCTION

The LM381 is a dual preamplifier expressly designed to meet the requirements of amplifying low level signals in low noise applications. Total equivalent input noise is typically  $0.5 \mu\text{V rms}$  ( $R_S = 600\Omega$ , 10-10, 000 Hz).

Each of the two amplifiers is completely independent, with an internal power supply decoupler-regulator, providing 120 dB supply rejection and 60 dB channel separation. Other outstanding features include high gain (112 dB), large output voltage swing ( $V_{CC} - 2V$ ) p-p, and wide power bandwidth (75 kHz, 20  $V_{pp}$ ). The LM381 operates from a single supply across the wide range of 9 to 40V. The amplifier is internally compensated and short-circuit protected.

Attempts have been made to fill this function with selected operational amplifiers. However, due to the many special requirements of this application, these recharacterizations have not adequately met the need.

With the low output level of magnetic tape heads and phonograph cartridges, amplifier noise becomes critical in achieving an acceptable signal-to-noise ratio. This is a major deficiency of the op amp in this application. Other inadequacies of the op amp are insufficient power supply rejection, limited small-signal and power bandwidths, and excessive external components.

TABLE 1.  $T_A = 25^\circ\text{C}$ ,  $V_{CC} = 14V$ , unless otherwise stated.

PARAMETER	CONDITIONS	MIN	TYP	MAX	UNITS
Voltage Gain	Open Loop (Differential Input)		160,000		V/V
	Open Loop (Single Ended Input)		320,000		V/V
Supply Current	$V_{CC}$ 9 to 40V, $R_L = \infty$		10		mA
Input Resistance (Positive Input)			100		k $\Omega$
	(Negative Input)		200		k $\Omega$
Input Current (Positive Input)			0.2		$\mu\text{A}$
	(Negative Input)		0.5		$\mu\text{A}$
Output Resistance	Open Loop		150		$\Omega$
Output Current	Source		8		mA
	Sink		2		mA
Output Voltage Swing	Peak-to-peak		$V_{CC} - 2$		V
Small Signal Bandwidth			15		MHz
Power Bandwidth	20 $V_{pp}$ ( $V_{CC} = 24V$ )		75		kHz
Maximum Input Voltage	Linear Operation			300	mVrms
Supply Rejection Ratio	$f = 1$ kHz		120		dB
Channel Separation	$f = 1$ kHz		60		dB
Total Harmonic Distortion	75 dB Gain, $f = 1$ kHz		0.1%		%
Total Equivalent Input Noise	$R_S = 600\Omega$ , 10-10, 000 Hz (Single Ended Input)		0.55		$\mu\text{Vrms}$
Noise Figure	50 k $\Omega$ , 10-10, 000 Hz		1.0		dB
	10 k $\Omega$ , 10-10, 000 Hz	(Single Ended Input)	1.3		dB
	5 k $\Omega$ , 10-10, 000 Hz		1.6		dB

## CIRCUIT DESCRIPTION

To achieve low noise performance, special consideration must be taken in the design of the input stage. First, the input should be capable of being operated single ended; since both transistors contribute noise in a differential stage degrading input noise by the factor  $\sqrt{2}$ . Secondly, both the load and biasing elements must be resistive; since active components would each contribute as much noise as the input device.

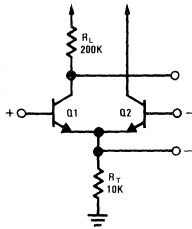


FIGURE 1. Input Stage

The basic input stage, Figure 1, can operate as a differential or single ended amplifier. For optimum noise performance  $Q_2$  is turned OFF and feedback is brought to the emitter of  $Q_1$ .

In applications where noise is less critical,  $Q_1$  and  $Q_2$  can be used in the differential configuration. This has the advantage of higher impedance at the feedback summing point, allowing the use of larger resistors and smaller capacitors in the tone control and equalization networks.

The voltage gain of the single ended input stage is given by:

$$A_{V(AC)} = \frac{R_L}{r_e} = \frac{200k}{1.25k} = 160 \quad (1)$$

Where:

$$r_e = \frac{KT}{qI_E} \approx 1.25 \times 10^3 \text{ at } 25^\circ\text{C } I_E \approx 20 \mu\text{A}$$

The voltage gain of the differential input stage is:

$$A_V = \frac{1}{2} \frac{R_L}{r_e} = \frac{1}{2} \frac{R_L q I_E}{KT} \approx 80 \quad (2)$$

The schematic diagram of the LM381, Figure 2, is divided into separate groups by function; first and second voltage gain stages, third current gain stage, and the bias regulator.

The second stage is a common-emitter amplifier ( $Q_5$ ) with a current source load ( $Q_6$ ). The Darlington emitter-follower  $Q_3, Q_4$  provides level shifting and current gain to the common-emitter stage ( $Q_5$ ) and the output current sink ( $Q_7$ ). The voltage gain of the second stage is approximately 2000 making the total gain of the amplifier typically 160,000 in the differential input configuration.

The preamplifier is internally compensated with the pole-splitting capacitor,  $C_1$ . This compensates to unity gain at 15 MHz. The compensation is adequate to preserve stability to a closed loop gain of 10. Compensation for unity gain closure may be provided with the addition of an external capacitor in parallel with  $C_1$  between Pins 5 and 6, 10 and 11.

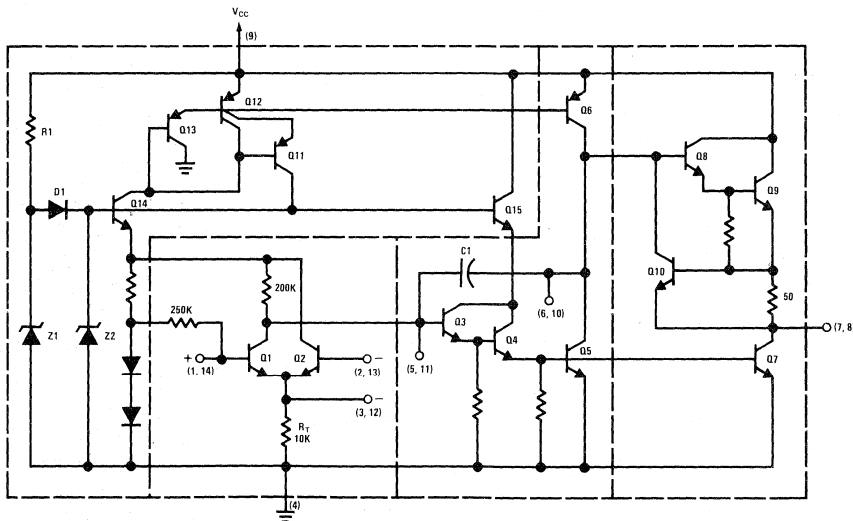


FIGURE 2. Schematic Diagram



Three basic compensation schemes are possible for this amplifier: first stage pole, second stage pole and pole-splitting. First stage compensation will cause an increase in high frequency noise because the first stage gain is reduced, allowing the second stage to contribute noise. Second stage compensation causes poor slew rate (power bandwidth) because the capacitor must swing the full output voltage. Pole-splitting overcomes both these deficiencies and has the advantage that a small monolithic compensation capacitor can be used.

The output stage is a Darlington emitter-follower ( $Q_8, Q_9$ ) with an active current sink ( $Q_7$ ). Transistor  $Q_{10}$  provides short-circuit protection by limiting the output to 12 mA.

The biasing reference is a zener diode ( $Z_2$ ) driven from a constant current source ( $Q_{11}$ ). Supply decoupling is the ratio of the current source impedance to the zener impedance. To achieve the high current source impedance necessary for 120 dB supply rejection, a cascode configuration is used ( $Q_{11}$  and  $Q_{12}$ ). The reference voltage is used to power the first stages of the amplifier through emitter-followers  $Q_{14}$  and  $Q_{15}$ . Resistor  $R_1$  and zener  $Z_1$  provide the starting mechanism for the regulator. After starting, zero volts appears across  $D_1$  taking it out of conduction.

### Biasing

Figure 3 shows an AC equivalent circuit of the LM381. The non-inverting input,  $Q_1$ , is referenced to a voltage source two  $V_{BE}$  above ground. The output quiescent point is established by negative DC feedback through the external divider  $R_4/R_5$  (Figure 4).

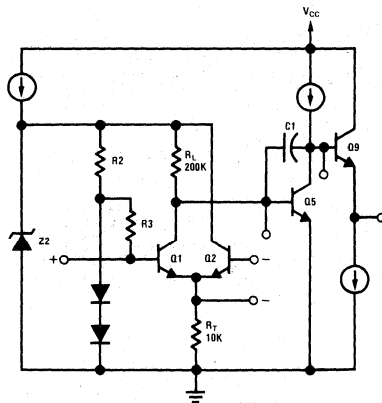


FIGURE 3. AC Equivalent Circuit

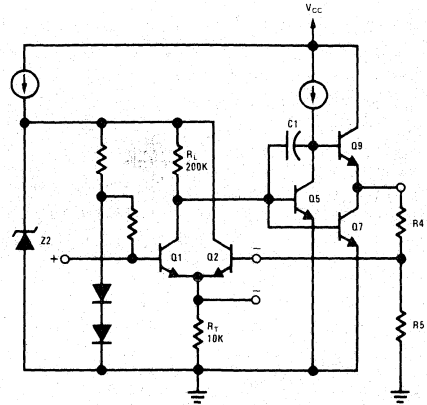


FIGURE 4. Differential Input Biasing

For bias stability, the current through  $R_5$  is made ten times the input current of  $Q_2$  ( $\approx 0.5 \mu A$ ). Then, for the differential input, resistors  $R_5$  and  $R_4$  are:

$$R_5 = \frac{2V_{BE}}{10 I_{Q2}} = \frac{1.2}{5 \times 10^{-6}} = 240 \text{ k}\Omega \text{ MAXIMUM} \quad (3)$$

$$R_4 = \left( \frac{V_{CC}}{2.4} - 1 \right) R_5. \quad (4)$$

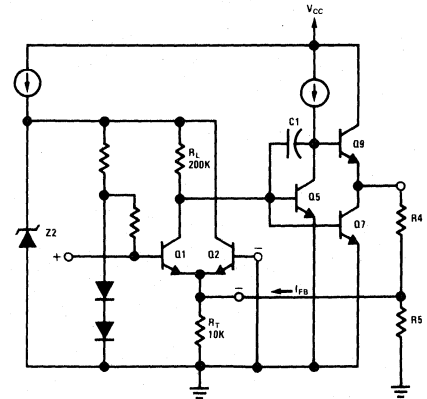


FIGURE 5. Single Ended Input Biasing

When using the single ended input,  $Q_2$  is turned OFF and DC feedback is brought to the emitter of  $Q_1$  (Figure 5). The impedance of the feedback summing point is now two orders of magnitude lower than the base of  $Q_2$  ( $\approx 10 \text{ k}\Omega$ ). Therefore, to preserve bias stability, the impedance of the

feedback network must be decreased. In keeping with reasonable resistance values, the impedance of the feedback voltage source can be 1/5 the summing point impedance.

The feedback current is <100  $\mu$ A worst case. Therefore, for single ended input, resistors  $R_5$  and  $R_4$  are:

$$R_5 = \frac{V_{BE}}{5 I_{FB}} = \frac{0.6}{5 \times 10^{-4}} = 1200\Omega \text{ MAXIMUM} \quad (5)$$

$$R_4 = \left( \frac{V_{CC}}{1.2} - 1 \right) R_5. \quad (6)$$

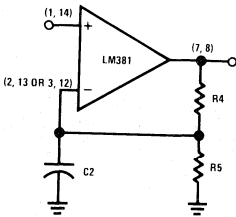


FIGURE 6. AC Open Loop

The circuits of Figures 4 and 5 have an AC and DC gain equal to the ratio  $R_4/R_5$ . To open the AC gain, capacitor  $C_2$  is used to shunt  $R_5$  (Figure 6). The AC gain now approaches open loop. The low frequency 3 dB corner,  $f_o$ , is given by:

$$f_o = \frac{A_o}{2\pi C_2 R_4} \text{ where: } A_o = \text{open loop gain} \quad (7)$$

#### Tape Playback Preamp

Figure 7 shows the LM381 in a flat response tape playback configuration. The mid-band gain is set by resistor ratio

$$(R_4 + R_6)/R_6 \quad (8)$$

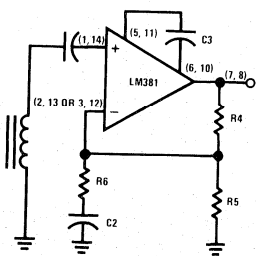


FIGURE 7. Flat Response Tape Amplifier

Capacitor  $C_2$  sets the low frequency 3 dB corner where  $X_{C2} = R_6$

$$C_2 = \frac{1}{2\pi f_o R_6} \quad (9)$$

The small-signal bandwidth of the LM381 is 15 MHz making the preamp suitable for wide-band instrumentation applications. However, in narrow band applications it is desirable to limit the amplifier bandwidth and thus eliminate high frequency noise. Capacitor  $C_3$  accomplishes this by shunting the internal pole-splitting capacitor ( $C_1$ ), limiting the bandwidth of the amplifier. Thus, the high frequency 3 dB corner is set by  $C_3$  according to equation 10.

$$C_3 = \frac{1}{2\pi f_3 \text{ re } 10^{\frac{A}{20}}} \approx 4 \times 10^{-12} \quad (10)$$

$f_3$  = high frequency 3 dB corner

re = first stage small-signal emitter resistance  $\approx 2.6 \text{ k}\Omega$

A = mid-band gain in dB

For music applications, response shaping is required to provide the NAB standard tape playback equalization. Figure 8 shows the NAB equalization characteristic.

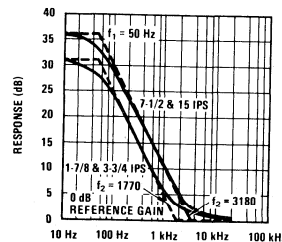


FIGURE 8. NAB Equalization Characteristic

The NAB response is achieved with the circuit of Figure 9. Resistors  $R_4$  and  $R_5$  set the DC bias and are chosen according to equations 3 and 4 for

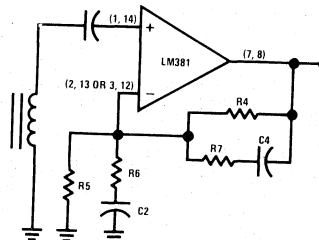


FIGURE 9. NAB Tape Preamp.

differential input operation and equations 5 and 6 for the single ended input. The reference gain of

the preamp, above corner frequency  $f_2$  (Figure 8), is set by the ratio:

$$0 \text{ dB reference gain} = \frac{R_7 + R_6}{R_6} \quad (11)$$

The corner frequency  $f_2$  (Figure 8) is determined where  $X_{C4} = R_7$  and is given by:

$$f_2 = \frac{1}{2\pi C_4 R_7} \quad (12)$$

Corner frequency  $f_1$  is determined where  $X_{C4} = R_4$ :

$$f_1 = \frac{1}{2\pi C_4 R_4} \quad (13)$$

The low frequency 3 dB roll-off point,  $f_0$ , is set where  $X_{C2} = R_6$ :

$$f_0 = \frac{1}{2\pi C_2 R_6} \quad (14)$$

**Example:** Design a NAB equalized preamp for a tape player requiring 0.5V rms output from a head sensitivity of 800  $\mu\text{V}$  at 1 kHz, 3-3/4 IPS. The power supply voltage is 24V and the differential input configuration is used.

- From equation (3) let  $R_5 = 240 \text{ k}\Omega$ .
- Equation (4)  $R_4 = \left( \frac{V_{CC}}{2.4} - 1 \right) R_5$   
 $R_4 = \left( \frac{24}{2.4} - 1 \right) 2.4 \times 10^5$   
 $R_4 = 2.16 \times 10^5 \approx 2.2 \text{ M}\Omega$
- For a corner frequency,  $f_1$  equal to 50 Hz, equation (13) is used.

$$(13) \quad C_4 = \frac{1}{2\pi f_1 R_4} = \frac{1}{6.28 \times 50 \times 2.2 \times 10^5}$$

$$= 1.44 \times 10^{-9}$$

$$C_4 \approx 1500 \text{ pF.}$$

- From Figure 8, the corner frequency  $f_2 = 1770 \text{ Hz}$  at 3-3/4 IPS. Resistor  $R_7$  is found from equation (12).

$$(12) \quad C_4 = \frac{1}{2\pi f_2 R_7}$$

$$R_7 = \frac{1}{6.28 \times 1770 \times 1.5 \times 10^{-9}} = 6 \times 10^4$$

$$R_7 \approx 62 \text{ k}\Omega.$$

- The required voltage gain at 1 kHz is:

$$A_V = \frac{0.5 \text{ V rms}}{800 \mu\text{V rms}} = 6.25 \times 10^2 \text{ V/V} = 56 \text{ dB.}$$

- From Figure 8 we see the reference frequency gain, above  $f_2$ , is 5 dB down from the 1 kHz value or 51 dB (355 V/V).

Equation (11)

$$0 \text{ dB Reference Gain} = \frac{R_7 + R_6}{R_6} = 355$$

$$R_6 = \frac{R_7}{355 - 1} = \frac{62 \text{ k}}{354} = 175$$

$$R_6 \approx 180 \Omega.$$

- For low frequency corner  $f_0 = 40 \text{ Hz}$ , equation (14)

$$C_2 = \frac{1}{2\pi f_0 R_6} = \frac{1}{6.28 \times 40 \times 180} = 2.21 \times 10^{-5}$$

$$C_2 \approx 20 \mu\text{F.}$$

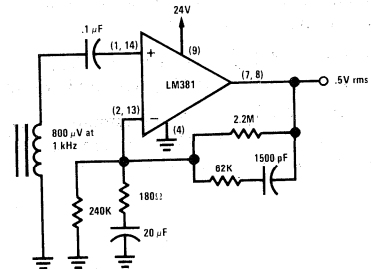


FIGURE 10. Typical Tape Playback Amplifier

This circuit is shown in Figure 10 and requires approximately 5 seconds to turn-ON for the gain and supply voltage chosen in the example. Turn-ON time can closely be approximated by:

$$t_{ON} \approx -R_4 C_2 \ln \left( 1 - \frac{2.4}{V_{CC}} \right) \quad (15)$$

As seen by equation (15), increasing the supply voltage decreases turn-ON time. Decreasing the amplifier gain also decreases turn-ON time by reducing the  $R_4 C_2$  product.

Where the turn-ON time of the circuit of Figure 9 is too long, the time may be shortened by using the circuit of Figure 11. The addition of resistor  $R_D$  forms a voltage divider with  $R_6$ . This divider is chosen so that zero DC voltage appears across

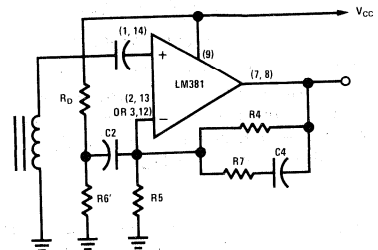


FIGURE 11. Fast Turn-On NAB Tape Preamp.

C<sub>2</sub>. The parallel resistance of R<sub>6</sub>' and R<sub>D</sub> is made equal to the value of R<sub>6</sub> found by equation (11). In most cases the shunting effect of R<sub>D</sub> is negligible and R<sub>6</sub>' ≈ R<sub>6</sub>.

For differential input, R<sub>D</sub> is given by:

$$R_D = \frac{(V_{CC} - 1.2) R_6'}{1.2} \quad (16)$$

For single ended input:

$$R_D = \frac{(V_{CC} - 0.6) R_6'}{0.6} \quad (17)$$

In cases where power supply ripple is excessive, the circuit of Figure 11 cannot be used since the ripple is coupled into the input of the preamplifier through the divider.

The circuit of Figure 12 provides fast turn-ON while preserving the 120 dB power supply rejection.

The DC operating point is still established by R<sub>4</sub>/R<sub>5</sub>. However, equations (3) and (5) are modified by a factor of 10 to preserve DC bias stability.

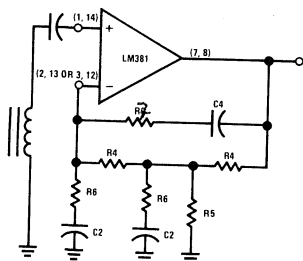


FIGURE 12. Two-Pole Fast Turn-On NAB Tape Preamp.

For differential input, equation (3) is modified as:

$$(3A) R_5 = \frac{2 V_{BE}}{100 I_{O2}} = \frac{1.2}{50 \times 10^{-8}} \\ = 24 \text{ k}\Omega \text{ MAXIMUM.}$$

For single ended input:

$$\text{Equation (5A) } R_5 = \frac{V_{BE}}{50 I_{FB}} = \frac{0.6}{50 \times 10^{-4}} \\ = 120\Omega \text{ MAXIMUM.}$$

Equations (11), (12) and (14) describe the high frequency gain and corner frequencies  $f_2$  and  $f_0$  as before. Frequency  $f_1$  now occurs where  $X_{C4}$  equals the composite impedance of the R<sub>4</sub>, R<sub>6</sub>, C<sub>2</sub> network as given by equation (18).

$$C_4 = \frac{1}{2\pi f_1 R_6 \left[ \left( \frac{R_4 + R_6}{R_6} \right)^2 - 1 \right]} \quad (18)$$

The turn-ON time becomes:

$$t_{ON} \approx -2\sqrt{R_4 C_2} \ln \left( 1 - \frac{2.4}{V_{CC}} \right) \quad (19)$$

*Example:* Design an NAB equalized preamp with the fast turn-ON circuit of Figure 12 for the same requirements as the previous example.

1. From equation (3A) let R<sub>5</sub> = 24 kΩ.

$$2. \text{ Equation (4) } R_4 = \left( \frac{V_{CC}}{2.4} - 1 \right) R_5 \\ = \left( \frac{24}{2.4} - 1 \right) 24 \times 10^3 \\ R_4 = 2.16 \times 10^5 \approx 220 \text{ k}\Omega.$$

3. From the previous example the reference frequency gain, above  $f_2$ , was found to be 51 dB or 355 V/V.

$$\text{Equation (11) } \frac{R_7 + R_6}{R_6} = 355.$$

4. The corner frequency  $f_2$  is 1770 Hz for 3-3/4 IPS.

$$\text{Equation (12) } C_4 = \frac{1}{2\pi f_2 R_7}$$

5. The corner frequency  $f_1$  is 50 Hz and is given by equation (18).

$$(18) \quad C_4 = \frac{1}{2\pi f_1 R_6 \left[ \left( \frac{R_4 + R_6}{R_6} \right)^2 - 1 \right]}$$

6. Solving equations (11), (12), and (18) simultaneously gives:

$$R_6 = \frac{R_4 (f_1 + \sqrt{f_1^2 + f_1 f_2 (\text{Ref. Gain})})}{f_2 (\text{Ref. Gain})} \quad (20)$$

$$R_6 = \frac{2.2 \times 10^5 (50 + \sqrt{2500 + 50 \times 1770 \times 355})}{1770 \times 355}$$

$$= 1.98 \times 10^3$$

$$R_6 \approx 2 \text{ k}\Omega.$$

7. From equation (11) R<sub>7</sub> = 354 R<sub>6</sub> = 708 × 10<sup>3</sup>  
R<sub>7</sub> ≈ 680 kΩ.

$$8. \text{ Equation (12) } C_4 = \frac{1}{2\pi f_2 R_7} \\ = \frac{1}{6.28 \times 1770 \times 680 \times 10^3}$$

$$C_4 = 1.32 \times 10^{-10} \approx 120 \text{ pF.}$$

$$9. \text{ Equation (14) } C_2 = \frac{1}{2\pi f_0 R_6} \\ = \frac{1}{6.28 \times 40 \times 2 \times 10^3}$$

$$C_2 = 1.99 \times 10^{-6} \approx 2 \mu\text{F.}$$

This circuit is shown in Figure 13 and requires only 0.1 seconds to turn-ON.

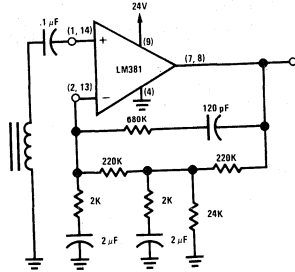


FIGURE 13

### TAPE RECORD PREAMPLIFIER

When recording, the frequency response is the complement of the NAB playback equalization, making the composite record and playback response flat. Figure 14 shows the record character superimposed on the NAB playback response.

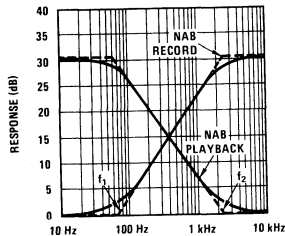


FIGURE 14. NAB Record & Playback Equalization

Curve A of Figure 15 shows the response characteristics of a typical laminated core, quarter-track head.

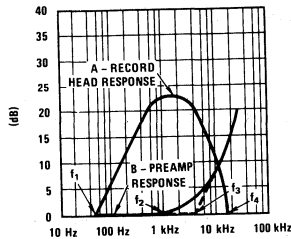


FIGURE 15. Recording Head & Preamp. Response for NAB Equalization

Curve B shows the required preamplifier response to make the composite, A + B, provide the NAB recording characteristic. This response is obtained with the circuit of Figure 16. Resistors  $R_4$  and  $R_5$

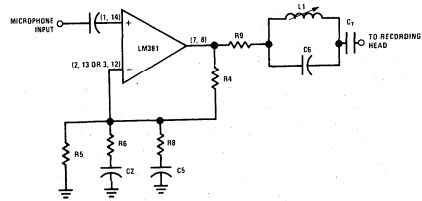


FIGURE 16. Tape Recording Preamp.

set the DC bias as before using equations (3) and (4) for the differential input and equations (5) and (6) for the single ended input. Resistor  $R_6$  and capacitor  $C_2$  set the mid-band gain as before (equations (8) and (9)). Capacitor  $C_5$  sets the high frequency 3 dB point,  $f_3$ , (Figure 15) as:

$$f_3 = \frac{1}{2\pi C_5 R_6} \quad (21)$$

The preamp gain increases at 6 dB/octave above  $f_3$  until  $R_8 = X_{C_5}$ .

$$R_8 = \frac{1}{2\pi f_4 C_5} \quad (22)$$

$f_4$  = desired high frequency cutoff

Resistor  $R_9$  is chosen to provide the proper recording head current.

$$R_9 = \frac{V_o}{I_{RECORD HEAD}} \quad (23)$$

$L_1$  and  $C_6$  form a parallel resonant bias trap to present a high impedance to the recording bias frequency and prevent intermodulation distortion.

*Example:* A recorder having a 24V power supply uses recording heads requiring 30  $\mu$ A AC drive current. A microphone of 10 mV peak output is used. Single ended input is desired for optimum noise performance.

1. From equation (5) let  $R_5 = 1200\Omega$ .

$$2. \text{ Equation (6) } R_4 = \left( \frac{V_{CC}}{1.2} - 1 \right) R_5$$

$$R_4 = \left( \frac{24}{1.2} - 1 \right) 1200.$$

$$R_4 = 2.28 \times 10^4 \approx 22 \text{ k}\Omega.$$

3. The maximum output of the LM381 is  $(V_{CC} - 2V)_{P-P}$ . For a 24V power supply, the maximum output is 22V<sub>P-P</sub> or 7.8V rms. Therefore, an output swing of 6V rms is reasonable.

From equation (23)  $R_9 = \frac{V_o}{I_{\text{RECORD HEAD}}}$

$$R_9 = \frac{6V}{30 \mu A} = 200 \text{ k}\Omega.$$

4. Let the high frequency cutoff  $f_4 = 16 \text{ kHz}$  (Figure 15). The recording head frequency response begins falling off at approximately 4 kHz. Therefore, the preamp gain must increase at this frequency to obtain the proper composite characteristic. The slope is 6 dB/octave for the two octaves between  $f_3$  (4 kHz) and the cutoff frequency  $f_4$  (16 kHz). Therefore, the mid-band gain lies 12 dB below the peak gain.

We are allowing 6V rms output voltage swing.

Therefore, the peak gain =  $\frac{6V}{10 \text{ mV}} = 600$  or 55.6 dB.

The mid-band gain = 43.6 dB or 150.

5. From equation (8) the mid-band gain =

$$\frac{R_4 + R_6}{R_6} = 150.$$

$$R_6 = \frac{R_4}{149} = \frac{22 \times 10^3}{149} = 147.7$$

$$R_6 \approx 150 \Omega$$

6. Equation (9)  $C_2 = \frac{1}{2\pi f_o R_6}$

$$= \frac{1}{6.28 \times 50 \times 150}$$

$$= 2.12 \times 10^{-5}$$

$$C_2 \approx 20 \mu F.$$

7. Equation (21)  $C_5 = \frac{1}{2\pi f_3 R_6}$

$$= \frac{1}{6.28 \times 4 \times 10^3 \times 150}$$

$$= 2.66 \times 10^{-7}$$

$$C_5 \approx 0.27 \mu F.$$

8. Equation (22)  $R_8 = \frac{1}{2\pi f_4 C_5}$

$$= \frac{1}{6.28 \times 16 \times 10^3 \times 2.7 \times 10^{-7}}$$

$$= 36.8$$

$$R_8 \approx 33 \Omega.$$

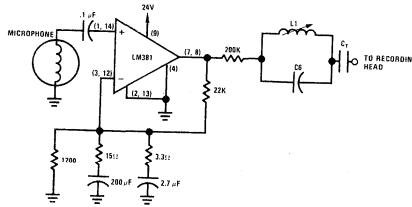


FIGURE 17. Typical Tape Recording Amplifier

### PHONO PREAMPLIFIER

Crystal and ceramic phono cartridges provide output levels of 100 mV to 2V and therefore do not require preamplification. Magnetic cartridges, however, provide much lower outputs as shown in Table 2.

TABLE 2.

MANUFACTURER	MODEL	OUTPUT AT 5 cm/sec
Empire Scientific	999	5 mV
	888	8 mV
Shure	V-15	3.5 mV
	M91	5 mV
Pickering	V-15 AT3	5 mV

Output voltage is specified for a given modulation velocity. The magnetic pickup is a velocity device, therefore, output is proportional to velocity. For example, a cartridge producing 5 mV at 5 cm/sec will produce 1 mV at 1 cm/sec and is specified as having a sensitivity of 1 mV/cm/sec.

In order to transform cartridge sensitivity into useful preamp design information, we need to know typical and maximum modulation velocity limits of stereo records.

The RIAA recording characteristic establishes a maximum recording velocity of 25 centimeters per second in the range of 800 to 2500 Hz. Typically, good quality records are recorded at a velocity of 3 to 5 cm/sec.

Figure 18 shows the RIAA playback equalization. This response is obtained with the circuit of Figure 19.

Resistors  $R_4$  and  $R_5$  set the DC bias (equations (3) and (4), or (5) and (6)). The 0 dB reference gain is set by the ratio:

$$0 \text{ dB Ref Gain} = \frac{R_{10} + R_6}{R_6} \quad (24)$$

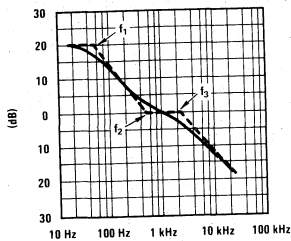


FIGURE 18. RIAA Playback Equalization

The corner frequency,  $f_1$ , (Figure 18) is established where  $X_{C7} = R_4$  or:

$$C_7 = \frac{1}{2\pi f_1 R_4} \quad (25)$$

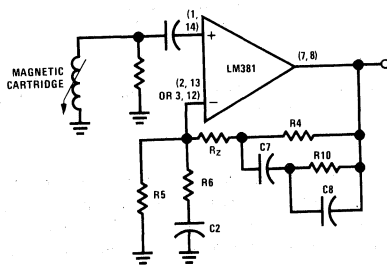


FIGURE 19. RIAA Phono Preamp.

Likewise, frequency,  $f_2$  occurs where  $X_{C7} = R_{10}$  or:

$$C_7 = \frac{1}{2\pi f_2 R_{10}} \quad (26)$$

The third corner frequency,  $f_3$ , is determined where  $X_{C8} = R_{10}$ :

$$C_8 = \frac{1}{2\pi f_3 R_{10}} \quad (27)$$

Resistor  $R_Z$  is used to insert a zero in the feedback loop since the LM381 is not compensated for unity gain. Either  $R_Z$  is required to provide a zero at or above a gain of 20 dB ( $R_Z = 10 R_6$ ), or external compensation is provided for unity gain stability according to equation (10).

**Example:** Design a phonograph preamp operating from a 30 volt supply, with a cartridge of 0.5 mV/cm/sec sensitivity, to drive a power amplifier of 5V rms input overload limit.

1. From equation (3) let  $R_5 = 100 \text{ k}\Omega$ .

$$\begin{aligned} 2. \text{ Equation (4) } R_4 &= \left( \frac{V_{CC}}{2.4} - 1 \right) R_5 \\ &= \left( \frac{30}{2.4} - 1 \right) 10^5 \\ R_4 &= 11.5 \times 10^5 \approx 1.2 \text{ M}\Omega. \end{aligned}$$

$$\begin{aligned} 3. \text{ Equation (25) } C_7 &= \frac{1}{2\pi f_1 R_4} \\ &= \frac{1}{6.28 \times 50 \times 1.2 \times 10^6} \\ &= 2.65 \times 10^{-9} \\ C_7 &\approx .003 \mu\text{F}. \end{aligned}$$

$$\begin{aligned} 4. \text{ Equation (26) } C_7 &= \frac{1}{2\pi f_2 R_{10}} \\ R_{10} &= \frac{1}{6.28 \times 500 \times 3 \times 10^{-9}} \\ &= 1.03 \times 10^5 \\ R_{10} &\approx 100 \text{ k}\Omega. \end{aligned}$$

5. The maximum cartridge output at 25cm/sec is:  
(.5 mV/cm/sec)  $\times$  (25 cm/sec) = 12.5 mV. The required mid-band gain is therefore:

$$\frac{5\text{V rms}}{12.5 \text{ mV rms}} = 400.$$

6. Equation (24)

$$0 \text{ dB Ref. Gain} = \frac{R_{10} + R_6}{R_6} = 400;$$

$$R_6 = \frac{100\text{k}}{399} = 251 \approx 240\Omega$$

$$R_Z = 10 R_6 = 2400\Omega.$$

7. Equation (9)

$$C_2 = \frac{1}{2\pi f_o R_6} = \frac{1}{6.28 \times 40 \times 240} = 1.7 \times 10^{-5}$$

$$C_2 \approx 20 \mu\text{F}.$$

8. Equation (27)

$$C_8 = \frac{1}{2\pi f_3 R_{10}} = \frac{1}{6.28 \times 2200 \times 6.8 \times 10^4}$$

$$= 7.23 \times 10^{-10}$$

$$C_8 \approx 0.001 \mu\text{F}.$$

The completed design is shown in Figure 20 where a 47 kΩ input resistor has been included to provide the RIAA standard cartridge load.

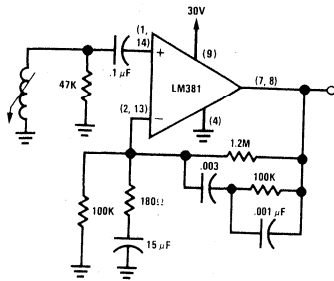


FIGURE 20. Typical Magnetic Phono Preamp.

## TONE CONTROLS

Most tape and phonograph applications require bass and treble tone controls. Due to the insertion loss of the tone control, (equal to the available boost), it has been normal to use two preamplifiers with the control placed between them. However, due to the excellent gain and large output capability of the LM381, only a single preamp is required.

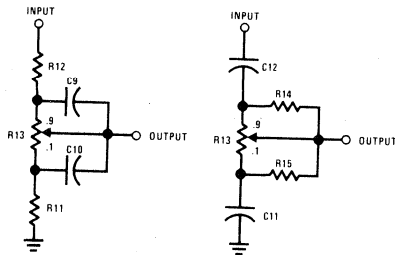


FIGURE 21. Bass & Treble Controls

Figure 21 shows the bass and treble tone controls. The potentiometers,  $R_{13}$ , are audio taper; i.e., at the center of shaft rotation the wiper is at the 90%–10% point of the total resistance. Both controls are simple AC dividers, with the flat response position where the signal is attenuated from the "full boost".

In the bass control the ratio of resistors  $R_{11}/R_{12}$  and  $R_{12}/R_{13}$  determine the degree of "boost" and

"cut". For example, if 20 dB of "boost" and "cut" is desired, the ratio  $R_{11}/R_{12}$  and  $R_{12}/R_{13}$  is 20 dB or 10:1. The low frequency control point,  $f_1$ , (Figure 22) is set where  $X_{C9} = R_{12}$  and  $X_{C10} = R_{11}$ .

$$C_9 = \frac{1}{2\pi f_1 R_{12}} \quad (28)$$

$$C_{10} = \frac{1}{2\pi f_1 R_{11}} \quad (29)$$

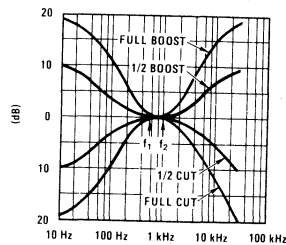


FIGURE 22. Bass & Treble Tone Control Response for 20 dB Boost & Attenuation

The treble control is the analogue of the bass control with the resistor and capacitor dividers reversed. The ratio of reactance of  $C_{11}/C_{12}$  is set equal to the amount of "boost" and "cut". The high frequency control point,  $f_2$ , is established where  $X_{C12} = R_{13}$ .

$$C_{12} = \frac{1}{2\pi f_2 R_{13}} \quad (30)$$

$$R_{14} = \frac{1}{2\pi f_2 C_{12}} \quad (31)$$

$$R_{15} = \frac{1}{2\pi f_2 C_{11}} \quad (32)$$

Figure 23 shows one channel of a practical preamplifier for a stereo phonograph. The preamp is complete with RIAA equalization, bass and treble tone control, balance control and volume control.

## AUDIO MIXER

In many audio applications it is desirable to provide a mixer to combined or select several inputs. Such applications include public address systems where more than one microphone is used; tape recorders, high fidelity phonographs, guitar amplifiers, etc.



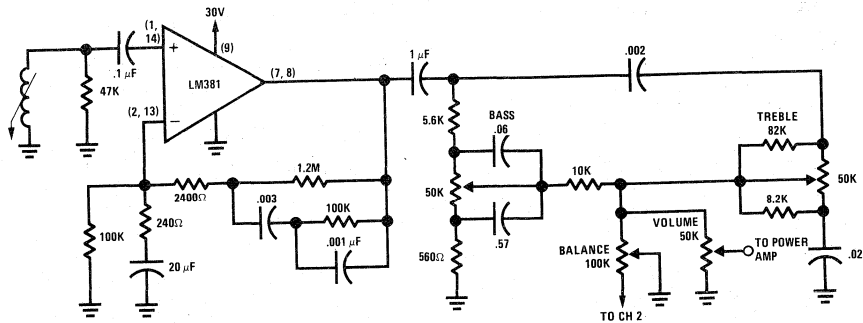


FIGURE 23. Single Channel of Complete Phono Preamp.

Figure 24 shows the LM381 in a mixer configuration. Inputs at A, B, C, -N can be selected and combined (summed) with potentiometers  $R_A$ ,  $R_B$ ,  $R_C$ ,  $-R_N$ . Resistors  $R_4$  and  $R_5$  establish the DC quiescent point in accordance with equations (3A) and (4). (Only the differential input configuration is used in the mixer application since the high source impedance of the input potentiometers would negate any advantage of the single ended input.) Input bias current is supplied through resistor  $R_F$ . Therefore, an upper limit of  $R_F$  should be established to avoid output offset voltage problems. A safe upper limit is to let:

$$R_F = R_4 \text{ MAXIMUM} \quad (33)$$

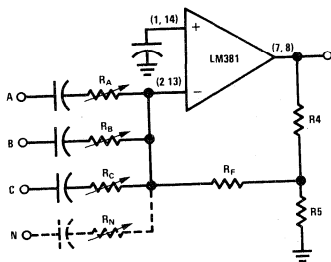


FIGURE 24. Audio Mixer

The voltage gain of the mixer is:

$$|A_{V_{A,B,C}}| = \frac{R_4 R_F + R_4 R_5 + R_5 R_F}{R_5 (R_{A,B,C} + R_{S_{A,B,C}})} \quad (34)$$

Where the values of  $R_F$  and the source impedance,  $R_S$ , are such that the gain of the circuit of Figure 24 is inadequate, the configuration of Figure 25 may be used.

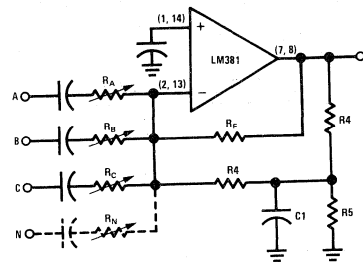


FIGURE 25.

The voltage gain of the mixer is now:

$$|A_V| = \frac{R_F}{R_{A,B,C} + R_{S_{A,B,C}}} \quad (35)$$

Since resistor  $R_F$  is no longer required to supply the input bias current, it does not have the upper limit as in the previous circuit. Therefore, the open loop gain of the LM381 can be realized. Capacitor  $C_1$ , shunts the AC feedback of the  $R_4 - R_5$  network and is found by:

$$C_1 = \frac{10^{\frac{A_o}{20}}}{2\pi f_o R_4}$$

$A_o$  = amplifier open loop gain in dB

$f_o$  = low frequency 3 dB corner

Example: Design a microphone mixer for use with 600Ω dynamic microphones with an output level of 10 mV. The mixer should operate from a 24V supply and deliver 5 volts output. A dynamic range of 80 dB is desired.

1. From equation (3A)  $R_5 = 24 \text{ k}\Omega$

2. Equation (4)

$$R_4 = \left( \frac{V_{CC}}{2.4} - 1 \right) R_5$$

$$R_4 = \left( \frac{24}{2.4} - 1 \right) 24 \times 10^3$$

$$R_4 = 2.16 \times 10^5 \approx 220 \text{ k}\Omega$$

3. For 5V output:

$$\text{Gain} = \frac{5V}{10 \text{ mV}} = 500$$

4. For 80 dB dynamic range:

$$\text{Attenuation} = \frac{500}{80 \text{ dB}} = 5 \times 10^{-2}$$

5. Equation (34)

$$|A_V| = \frac{R_4 R_F + R_4 R_5 + R_5 R_F}{R_5 (R_{A,B,C} + R_5)}$$

$$R_F = \frac{|A_V| R_5 (R_{A,B,C} + R_5) - R_4 R_5}{R_4 + R_5}$$

At maximum volume:  $R_{A,B,C} = 0$ , Gain = 500

$$R_F = \frac{500 \times 2.4 \times 10^4 (0 + 600) - (2.2 \times 10^5)(2.4 \times 10^4)}{2.2 \times 10^5 + 2.4 \times 10^4}$$

$$R_F = 7.87 \text{ k} \approx 8.2 \text{ k}$$

At maximum attenuation:

$$R_{A,B,C} = \frac{R_4 R_F + R_4 R_5 + R_5 R_F - |A_V| R_5 R_5}{A_V R_5}$$

$$R_{A,B,C} = 5.99 \times 10^6 \approx 5 \text{ M}\Omega$$

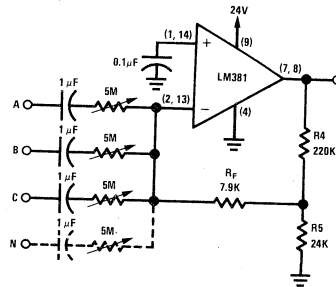


FIGURE 26.

#### CONCLUSION:

The applications presented in this note are by no means exhaustive. The LM381 is a widely versatile low noise, high gain, wide band gain block and, as such has many applications outside the audio spectrum.

# LM380 Power Audio Amplifier

National Semiconductor  
Application Note 69  
Joe E. Byerly  
Marvin K. Vander Kooi  
December 1972



## INTRODUCTION

The LM380 is a power audio amplifier intended for consumer applications. It features an internally fixed gain of 50 (34 dB) and an output which automatically centers itself at one-half of the supply voltage. A unique input stage allows inputs to be ground referenced or AC coupled as required. The output stage of the LM380 is protected with both short circuit current limiting and thermal shutdown circuitry. All of these internally provided features result in a minimum external parts count integrated circuit for audio applications.

This paper describes the circuit operation of the LM380, its power handling capability, methods of volume and tone control, distortion, and various application circuits such as a bridge amplifier, a power supply splitter, and a high input impedance audio amplifier.

## CIRCUIT DESCRIPTION

Figure 1 shows a simplified circuit schematic of the LM380. The input stage is a PNP emitter-follower

driving a PNP differential pair with a slave current-source load. The PNP input is chosen to reference the input to ground, thus enabling the input transducer to be directly coupled.

The output is biased to half the supply voltage by resistor ratio  $R_1/R_2$ . Negative DC feedback, through resistor  $R_2$ , balances the differential stage with the output at half supply, since  $R_1 = 2 R_2$  (Figure 1).

The second stage is a common emitter voltage gain amplifier with a current-source load. Internal compensation is provided by the pole-splitting capacitor  $C'$ . Pole-splitting compensation is used to preserve wide power bandwidth (100 kHz at 2W, 8Ω). The output is a quasi-complementary pair emitter-follower.

The amplifier gain is internally fixed to 34 dB or 50. This is accomplished by the internal feedback network  $R_2-R_3$ . The gain is twice that of the ratio  $R_2/R_3$  due to the slave current-source which provides the full differential gain of the input stage.

TABLE 1. Electrical Characteristics (Note 1)

PARAMETER	CONDITIONS	MIN	TYP	MAX	UNITS
Power Output (rms)	8Ω load, 3% T.H.D. (Notes 3, 4)	2.5			Wrms
Gain		40	50	60	V/V
Output Voltage Swing	8Ω load		14		V <sub>pp</sub>
Input Resistance			150k		Ω
Total Harmonic Distortion	P <sub>O</sub> = 1W, (Notes 4 & 5)		0.2		%
Power Supply Rejection	C <sub>bypass</sub> = 5 μF, f = 120 Hz (Note 2)		38		dB
Supply Voltage Range		8		22	V
Bandwidth	P <sub>O</sub> = 2W, R <sub>L</sub> = 8Ω		100k		Hz
Quiescent Output Voltage		8	9	10	V
Quiescent Supply Current			7	25	mA
Short Circuit Current			1.3		A

Note 1: V<sub>S</sub> = 18V; T<sub>A</sub> = 25°C unless otherwise specified.

Note 2: Rejection ratio referred to output.

Note 3: With device Pins 3, 4, 5, 10, 11, 12 soldered into a 1/16" epoxy glass board with 2 ounce copper foil with a minimum surface of six square inches.

Note 4: If oscillation exists under some load conditions, add a 2.7k resistor and 0.1 μF series network from Pin 8 to ground.

Note 5: C<sub>bypass</sub> = 0.47 μF on Pin 1.

Note 6: Pins 3, 4, 5, 10, 11, 12 at 50°C derates 25°C/W above 50°C case.

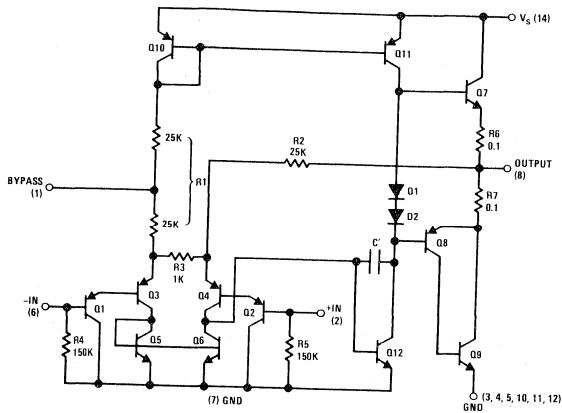


FIGURE 1.

### GENERAL OPERATING CHARACTERISTICS

The output current of the LM380 is rated at 1.3A peak. The 14 pin dual-in-line package is rated at  $35^{\circ}\text{C}/\text{W}$  when soldered into a printed circuit board with 6 square inches of 2 ounce copper foil (Figure 2). Since the device junction temperature is limited to  $150^{\circ}\text{C}$  via the thermal shutdown circuitry, the package will support 3 watts dissipation at  $50^{\circ}\text{C}$  ambient or 3.7 watts at  $25^{\circ}\text{C}$  ambient.

Figure 2 shows the maximum package dissipation versus ambient temperature for various amounts of heat sinking.

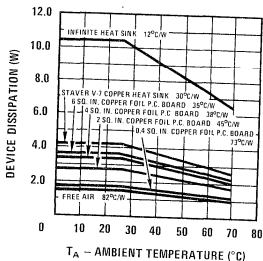


FIGURE 2. Device Dissipation vs Ambient Temperature

Figures 3A, B, and C show device dissipation versus output power for various supply voltages and loads.

The maximum device dissipation is obtained from Figure 2 for the heat sink and ambient temperature conditions under which the device will be operating. With this maximum allowed dissipation, Figures 3A, B and C show the maximum power supply allowed (to stay within dissipation limits) and the output power delivered into 4, 8 or 16 ohm loads. The three percent total-harmonic-distortion line is approximately the on-set of clipping.

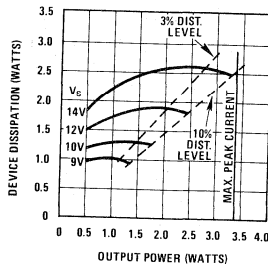


FIGURE 3A. Device Dissipation vs Output Power – 4Ω Load

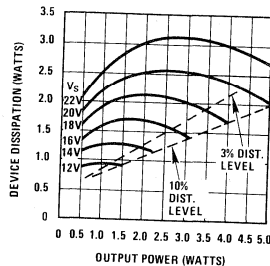


FIGURE 3B. Device Dissipation vs Output Power – 8Ω Load

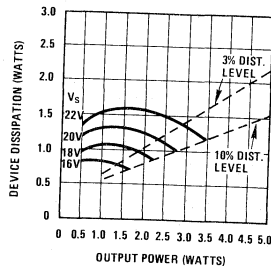


FIGURE 3C. Device Dissipation vs Output Power – 16Ω Load

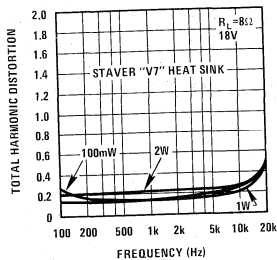


FIGURE 4. Total Harmonic Distortion vs Frequency

Figure 4 shows total harmonic distortion versus frequency for various output levels, while Figure 5 shows the power bandwidth of the LM380.

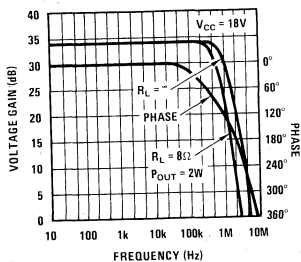


FIGURE 5. Output Voltage Gain vs Frequency

Power supply decoupling is achieved through the AC divider formed by  $R_1$  (Figure 1) and an external bypass capacitor. Resistor  $R_1$  is split into two

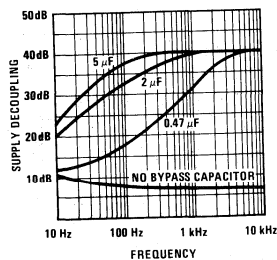


FIGURE 6. Supply Decoupling vs Frequency

25 k $\Omega$  halves providing a high source impedance for the integrator. Figure 6 shows supply decoupling versus frequency for various bypass capacitors.

## BIASING

The simplified schematic of Figure 1 shows that the LM380 is internally biased with the 150 k $\Omega$  resistance to ground. This enables input transducers which are referenced to ground to be direct-coupled to either the inverting or non-inverting inputs of the amplifier. The unused input may be either: 1) left floating, 2) returned to ground through a resistor or capacitor or 3) shorted to ground. In most applications where the non-inverting input is used, the inverting input is left floating. When the inverting input is used and the non-inverting input is left floating, the amplifier may be found to be sensitive to board layout since stray coupling to the floating input is positive feedback. This can be avoided by employing one of three alternatives: 1) AC grounding the unused input with a small capacitor. This is preferred when using high source impedance transducers. 2) Returning the unused input to ground through a resistor. This is preferred when using moderate to low DC source impedance transducers and when output offset from half supply voltage is critical. The resistor is made equal to the resistance of the input transducer, thus maintaining balance in the input differential amplifier and minimizing output offset. 3) Shorting the unused input to ground. This is used with low DC source impedance transducers or when output offset voltage is non-critical.

## OSCILLATION

The normal power supply decoupling precautions should be taken when installing the LM380. If  $V_S$  is more than 2" to 3" from the power supply filter capacitor it should be decoupled with a 0.1 $\mu$ F disc ceramic capacitor at the  $V_S$  terminal of the IC.

The  $R_C$  and  $C_C$  shown as dotted line components on Figure 7 and throughout this paper suppresses a

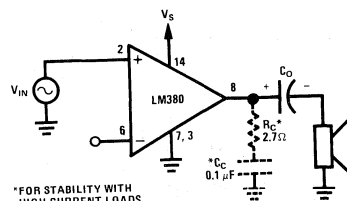


FIGURE 7. Minimum Component Configuration

5 to 10 MHz small amplitude oscillation which can occur during the negative swing into a load which draws high current. The oscillation is of course at too high of a frequency to pass through a speaker, but it should be guarded against when operating in an RF sensitive environment.

## APPLICATIONS

With the internal biasing and compensation of the LM380, the simplest and most basic circuit configuration requires only an output coupling capacitor as seen in Figure 7.

An application of this basic configuration is the phonograph amplifier where the addition of volume and tone controls is required. Figure 8 shows the LM380 with a voltage divider volume control and high frequency roll-off tone control.

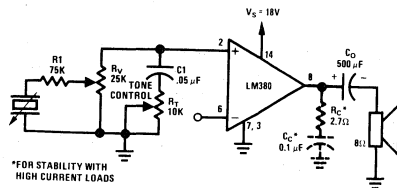


FIGURE 8. Phono Amp

When maximum input impedance is required or the signal attenuation of the voltage divider volume control is undesirable, a "common mode" volume control may be used as seen in Figure 9.

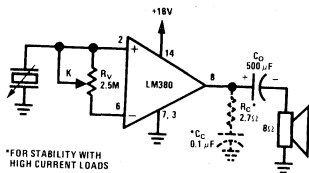


FIGURE 9. "Common Mode" Volume Control

With this volume control the source loading impedance is only the input impedance of the amplifier when in the full-volume position. This reduces to one-half the amplifier input impedance at the zero volume position. Equation 1 describes the output voltage as a function of the potentiometer setting.

$$V_{OUT} = 50 V_{IN} \left( 1 - \frac{150 \times 10^3}{k_1 R_V + 150 \times 10^3} \right) \quad 0 \leq k_1 \leq 1 \quad (1)$$

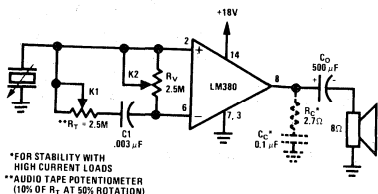


FIGURE 10. "Common Mode" Volume and Tone Control

This "common mode" volume control can be combined with a "common mode" tone control as seen in Figure 10.

This circuit has a distinct advantage over the circuit of Figure 7 when transducers of high source impedance are used, in that, the full input impedance of the amplifier is realized. It also has an advantage with transducers of low source impedance since the signal attenuation of the input voltage divider is eliminated. The transfer function of the circuit of Figure 10 is given by:

$$\frac{V_{OUT}}{V_{IN}} = 50 \left( 1 - \frac{150k}{150k + \frac{k_1 R_T + k_2 R_V}{j2\pi f c_1}} \right) \quad (2)$$

$$0 \leq k_1 \leq 1$$

$$0 \leq k_2 \leq 1$$

Figure 11 shows the response of the circuit of Figure 10.

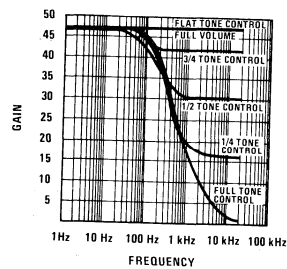


FIGURE 11. Tone Control Response

Most phonograph applications require frequency response shaping to provide the RIAA equalization characteristic. When recording, the low frequencies are attenuated to prevent large undulations from destroying the record groove walls. (Bass tones have higher energy content than high frequency tones.) Conversely, the high frequencies are emphasized to achieve greater signal-to-noise ratio. Therefore, when played back the phono amplifier should have the inverse frequency response as shown in Figure 12.

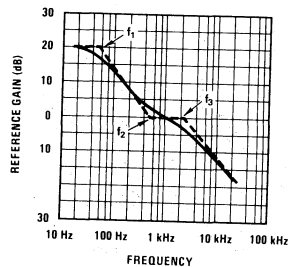


FIGURE 12. RIA Playback Equalization

This response is achieved with the circuit of Figure 13.

The mid-band gain, between frequencies  $f_2$  and  $f_3$ , Figure 12, is established by the ratio of  $R_1$  to the input resistance of the amplifier (150 k $\Omega$ ).

$$\text{Mid-band Gain} = \frac{R_1 + 150 \text{ k}\Omega}{150 \text{ k}\Omega} \quad (3)$$

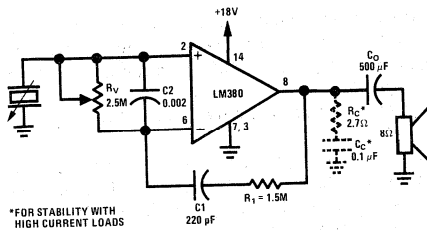


FIGURE 13. RIAA Phono Amplifier

Capacitor  $C_1$  sets the corner frequency  $f_2$  where  $R_1 = X_{C1}$ .

$$C_1 = \frac{1}{2\pi f_2 R_1} \quad (4)$$

Capacitor  $C_2$  establishes the corner frequency  $f_3$  where  $X_{C2}$  equals the impedance of the inverting input. This is normally 150 k $\Omega$ . However, in the circuit of Figure 13 negative feedback reduces the impedance at the inverting input as:

$$Z = \frac{Z_o}{1 + A_o\beta} \quad (5)$$

Where:

$Z_o$  = impedance at node 6 without external feedback (150 k $\Omega$ )

$A_o$  = gain without external feedback (50)

$\beta$  = feedback transfer function  $\beta = \frac{A_o - A}{A_o A}$

$A$  = closed loop gain with external feedback.

Therefore:

$$C_2 = \frac{1}{2\pi f_3 \left( \frac{Z_o}{1 + A_o\beta} \right)} = \frac{1}{2\pi f_3 \left( \frac{150\text{k}}{1 + 50\beta} \right)} \quad (6)$$

### BRIDGE AMPLIFIER

Where more power is desired than can be provided with one amplifier, two amps may be used in the bridge configuration shown in Figure 14.

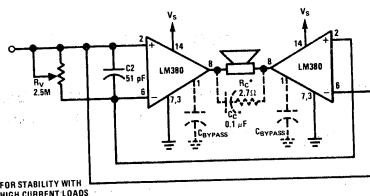


FIGURE 14. Bridge Configuration

This provides twice the voltage swing across the load for a given supply, thereby, increasing the

power capability by a factor of four over the single amplifier. However, in most cases the package dissipation will be the first parameter limiting power delivered to the load. When this is the case, the power capability of the bridge will be only

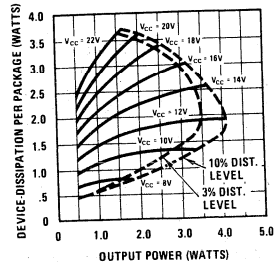


FIGURE 15A. 8 $\Omega$  Load

twice that of the single amplifier. Figures 15A and B show output power versus device package dissipation for both 8 and 16 $\Omega$  loads in the bridge con-

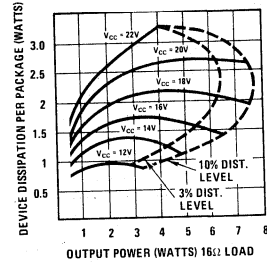


FIGURE 15B. 16 $\Omega$  Load

figuration. The 3% and 10% harmonic distortion contours double back due to the thermal limiting of the LM380. Different amounts of heat sinking will change the point at which the distortion contours bend.

The quiescent output voltage of the LM380 is specified at  $9 \pm 1$  volts with an 18 volt supply. Therefore, under the worst case condition, it is possible to have two volts DC across the load.


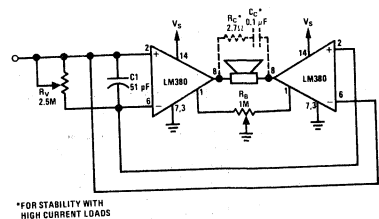


FIGURE 16. Quiescent Balance Control

With an 8 $\Omega$  speaker this is 0.25A which may be excessive. Three alternatives are available; 1) care can be taken to match the quiescent voltages, 2) a non-polar capacitor may be placed in series with the load, 3) the offset balance control of Figure 16 may be used.

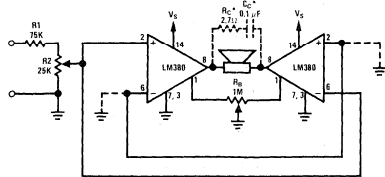The circuits of Figures 14 and 16 employ the "common mode" volume control as shown before. However, any of the various input connection schemes discussed previously may be used. Figure 17 shows the bridge configuration with the voltage divider input. As discussed in the "Biasing"




\*FOR STABILITY WITH HIGH CURRENT LOADS

FIGURE 17. Voltage Divider Input

section the undriven input may be AC or DC grounded. If  $V_S$  is an appreciable distance from the power supply ( $>3'$ ) filter capacitor it should be decoupled with a  $1\mu\text{F}$  tantalum capacitor.
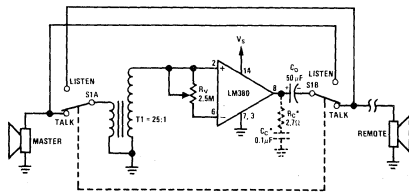
### INTERCOM

The circuit of Figure 18 provides a minimum component intercom. With switch  $S_1$  in the talk position, the speaker of the master station acts as the microphone with the aid of step-up transformer  $T_1$ .



\*FOR STABILITY WITH HIGH CURRENT LOADS

FIGURE 18. Intercom

A turns ratio of 25 and a device gain of 50 allows a maximum loop gain of 1250.  $R_V$  provides a "common mode" volume control. Switching  $S_1$  to the listen position reverses the role of the master and remote speakers.

### LOW COST DUAL SUPPLY

The circuit shown in Figure 19 demonstrates a minimum parts count method of symmetrically

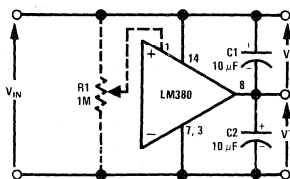


FIGURE 19. Dual Supply

splitting a supply voltage. Unlike the normal  $R$ ,  $C$ , and power zener diode technique the LM380

circuit does not require a high standby current and power dissipation to maintain regulation.

With a 20 volt input voltage ( $\pm 10$  volt output) the circuit exhibits a change in output voltage of approximately 2% per 100 mA of unbalanced load change. Any balanced load change will reflect only the regulation of the source voltage  $V_{IN}$ .

The theoretical plus and minus output tracking ability is 100% since the device will provide an output voltage at one-half of the instantaneous supply voltage in the absence of a capacitor on the bypass terminal. The actual error in tracking will be directly proportional to the unbalance in the quiescent output voltage. An optional potentiometer may be placed at pin 1 as shown in Figure 19 to null output offset. The unbalanced current output for the circuit of Figure 18 is limited by the power dissipation of the package.

In the case of sustained unbalanced excess loads, the device will go into thermal limiting as the temperature sensing circuit begins to function. For instantaneous high current loads or short circuits the device limits the output current to approximately 1.3 amperes until thermal shut-down takes over or until the fault is removed.

### HIGH INPUT IMPEDANCE CIRCUIT

The junction FET isolation circuit shown in Figure 20 raises the input impedance to  $22\text{M}\Omega$  for low frequency input signals. The gate to drain

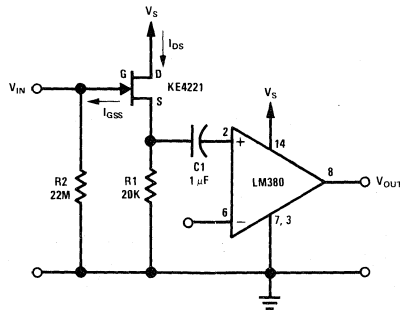


FIGURE 20.

capacitance (2 pF maximum for the KE4221 shown) of the FET limits the input impedance as frequency increases.

At 20 kHz the reactance of this capacitor is approximately  $-j4\text{M}\Omega$  giving a net input impedance magnitude of  $3.9\text{M}\Omega$ . The values chosen for  $R_1$ ,  $R_2$  and  $C_1$  provide an overall circuit gain of at least 45 for the complete range of parameters specified for the KE4221.



When using another FET device the relevant design equations are as follows:

$$A_V = \left( \frac{R_1}{R_1 + \frac{1}{g_m}} \right) \quad (7)$$

$$g_m = g_{m0} \left( 1 - \frac{V_{GS}}{V_P} \right) \quad (8)$$

$$V_{GS} = I_{DS} R_1 \quad (9)$$

$$I_{DS} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 \quad (10)$$

The maximum value of  $R_2$  is determined by the product of the gate reverse leakage  $I_{GSS}$  and  $R_2$ . This voltage should be 10 to 100 times smaller than  $V_P$ . The output impedance of the FET source follower is:

$$R_o = \frac{1}{g_m} \quad (11)$$

so that the determining resistance for the interstage RC time constant is the input resistance of the LM380.

### BOOSTED GAIN USING POSITIVE FEEDBACK

For applications requiring gains higher than the internally set gain of 50, it is possible to apply

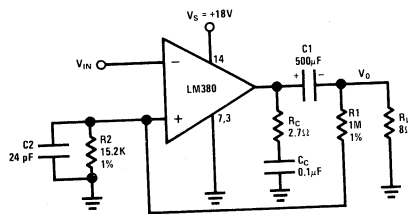


FIGURE 21. Boosted Gain of 200 Using Positive Feedback

positive feedback around the LM380 for closed loop gains of up to 300. Figure 21 shows a practical example of an LM380 in a gain of 200 circuit.

The equation describing the closed loop gain is:

$$A_{VCL} = \frac{-A_V(\omega)}{1 - \frac{A_V(\omega)}{1 + \frac{R_1}{R_2}}} \quad (12)$$

where  $A_V(\omega)$  is complex at high frequencies but is nominally the 40 to 60 specified on the data sheet for the pass band of the amplifier. If  $1 + R_1/R_2$  approaches the value of  $A_V(\omega)$ , the denominator of equation 12 approaches zero, the closed loop gain increases toward infinity, and the circuit oscillates. This is the reason for limiting the closed loop gain values to 300 or less. Figure 22 shows the loaded and unloaded bode plot for the circuit shown in Figure 21.

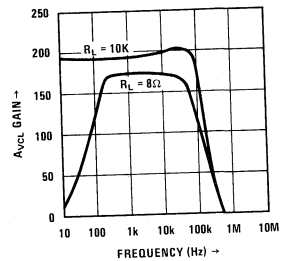


FIGURE 22. Boosted Gain Bode Plot

The 24 pF capacitor  $C_2$  shown on Figure 21 was added to give an overdamped square wave response under full load conditions. It causes a high frequency roll-off of:

$$f_2 = \frac{1}{2\pi R_2 C_2} \quad (13)$$

The circuit of Figure 21 will have a very long (1000 sec) turn on time if  $R_L$  is not present, but only a 0.01 second turn on time with an  $8\Omega$  load.



# LM381A Dual Preamp for Ultra-Low Noise Applications

National Semiconductor  
 Application Note 70  
 Joe E. Byerly  
 Dennis Bohn  
 August 1972



## INTRODUCTION

The LM381A is a dual preamplifier expressly designed to meet the requirements of amplifying low level signals in noise critical applications. Such applications include hydrophones, scientific and instrumentation recorders, low level wideband gain blocks, tape recorders, studio sound equipment, etc.

The LM381A can be externally biased for optimum noise performance in ultra-low noise applications. When this is done the LM381A provides a wideband, high gain amplifier with noise performance that exceeds that of today's best transistors.

The amplifier can be operated in either the differential or single ended input configuration. However, for optimum noise performance, the input must be operated single ended, since both transistors contribute noise in a differential stage, degrading input noise by the factor  $\sqrt{2}$ . A second consideration is the design of the input bias circuitry. Both the load and biasing elements must be resistive, since active components would each contribute additional noise equal to that of the input device. Thirdly, the current density of the input device should be optimized for the source resistance of the input transducer.

Figure 1 shows the schematic diagram of one channel of LM381A (a detailed explanation of the circuit operation is given in application note AN-64). To operate the input single ended, transistor Q<sub>2</sub> is turned OFF by returning the base of Q<sub>2</sub> (Pins 2, 13) to ground.

Figures 2A and 2B show the wide-band (10 Hz – 10 kHz) input noise voltage and input noise current versus collector current for the single ended

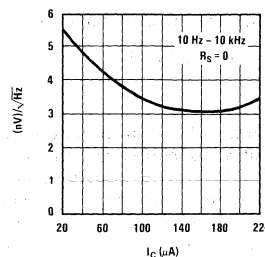


FIGURE 2A. Wideband Equivalent Input Noise Voltage vs Collector Current

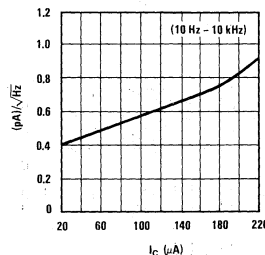


FIGURE 2B. Wideband Equivalent Input Noise Current vs Collector Current

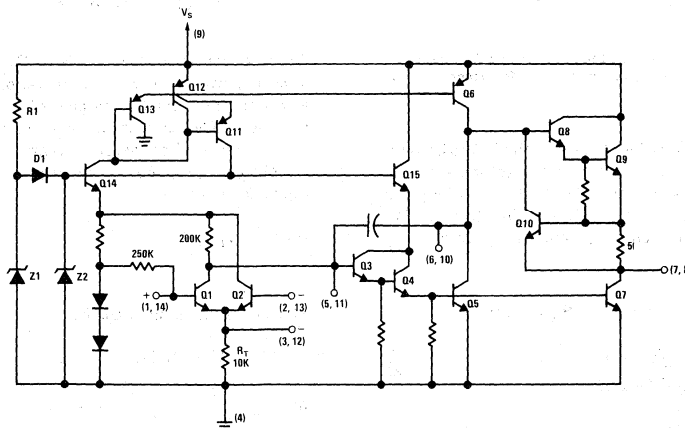


FIGURE 1. LM381A Schematic Diagram

input configuration of the LM381A. Total input noise of the amplifier is found by:

$$E_T = \sqrt{[e_n^2 + (i_n R_S)^2 + 4kTR_S]} \text{ B.W.} \quad (1)$$

Where:

$e_n$  = amplifier noise voltage/ $\sqrt{\text{Hz}}$

$i_n$  = amplifier noise current/ $\sqrt{\text{Hz}}$

$R_S$  = source resistance  $\Omega$

$k$  = Boltzmann's constant =  $1.38 \times 10^{-23}$  J/ $^\circ\text{K}$

$T$  = source resistance temperature  $^\circ\text{K}$

B.W. = noise bandwidth

Figure 3 shows a plot of input transistor ( $Q_1$ ) collector current versus source resistance for optimum noise performance of the LM381A. For source impedances less than  $3 \text{ k}\Omega$  the noise voltage term ( $e_n$ ) dominates and the input is biased at  $170 \mu\text{A}$  which is optimum for noise voltage. In the region between  $3 \text{ k}\Omega$  and  $15 \text{ k}\Omega$ , both the  $e_n$  and  $i_n R_S$  terms contribute and the input should be biased as indicated by Figure 3. Above  $15 \text{ k}\Omega$ , the  $i_n R_S$  term is dominant and the amplifier is operated without additional external biasing.

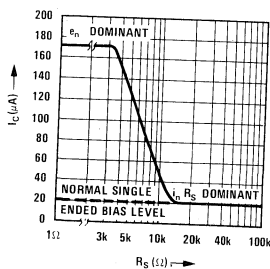


FIGURE 3. Collector Current vs Source Resistance for Optimum Noise Performance

Figure 4 shows the input stage of the LM381A with the external components added to increase the current density of transistor  $Q_1$ . Resistors  $R_1$  and  $R_2$  supply the additional current ( $I_2$ ) to the existing collector current ( $I_1$ ) which is approximately  $18 \mu\text{A}$ .

The sum of resistors  $R_1$  &  $R_2$  is given by:

$$(R_1 + R_2) = \frac{V_S - 2.1}{I_C - 18 \times 10^{-6}} \quad (2)$$

For DC considerations, only the sum ( $R_1 + R_2$ ) is important. When considering the AC effects, however, the values of  $R_1$  and  $R_2$  become significant.

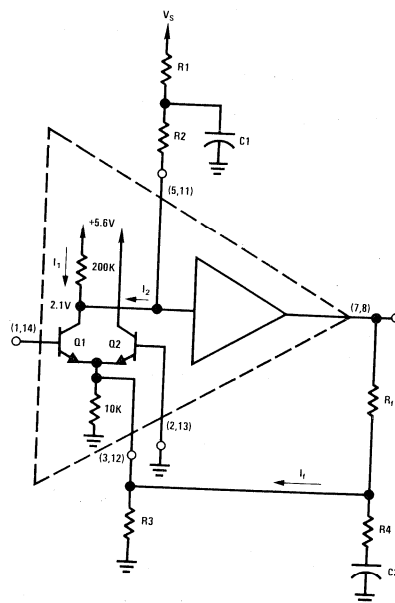


FIGURE 4. LM381A with Biasing Components for Increasing  $Q_1$  Current Density

Since resistors  $R_1$  and  $R_2$  are biased from the power supply, the decoupling capacitor,  $C_1$ , is required to preserve supply rejection. The value of  $C_1$  is given by:

$$C_1 = \frac{\frac{\text{P.S.R.}}{10^{20}}}{2\pi f_S R_1 A_1} \quad (3)$$

Where:

P.S.R. = Supply rejection in dB referred to input

$f_S$  = Frequency of supply ripple

$A_1$  = Voltage gain of first stage

As  $R_1$  becomes smaller capacitor  $C_1$  increases for a given power supply rejection ratio. Conversely, as  $R_2$  becomes smaller the gain of the input stage decreases, adversely affecting noise performance. For the range of collector currents over which the LM381A is operating, a reasonable compromise is obtained with:

$$R_2 = 3 R_1 \quad (4)$$

The gain of the input stage is:

$$A_1 = \frac{(2 \times 10^5) R_2}{R_2 + 2 \times 10^5} \left( \frac{1}{I_C} + \frac{1}{10^4} + \frac{1}{R_3} + \frac{1}{R_4} \right) \quad (5)$$

Resistor divider  $R_f/R_3$  provides negative DC feedback around the amplifier establishing the quiescent operating point.  $R_f$  is found by:

$$R_f = \frac{1}{2} \left[ \frac{V_S R_3 \times 10^4}{.55(R_3 + 1 \times 10^4) + I_C (R_3 \times 10^4)} - \frac{R_3 \times 10^4}{R_3 + 1 \times 10^4} \right] \quad (6)$$

For DC stability let:

$$R_3 = 1 \text{ k}\Omega \text{ Maximum} \quad (7)$$

$R_f$  can then be found from:

$$R_f = \frac{1}{2} \left[ \frac{V_S \times 10^7}{6.05 \times 10^3 + I_C \times 10^7} \right] - 910 \quad (8)$$

Where:

$V_S$  = Supply Voltage

$I_C$  =  $Q_1$  Collector Current

The AC closed loop gain is set by the ratio:

$$(R_f + R_4)/R_4 \quad (9)$$

Capacitor  $C_2$  sets the low frequency 3 dB corner where:

$$f_o = \frac{1}{2\pi C_2 R_4} \quad (10)$$

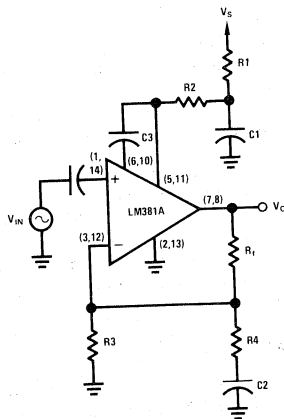


FIGURE 5. Single Ended Input Configuration with External Biasing Components

Figure 5 shows the LM381A in the single ended input configuration with the additional biasing components. Capacitor  $C_3$  may be added to limit the amplifier bandwidth to the frequency range of interest, thus eliminating excess noise outside the pertinent bandwidth.

$$C_3 = \frac{1}{2\pi f_1 \left( \frac{.026}{I_C} \right) 10^{20}} - 4 \times 10^{-12} \quad (11)$$

Where:

$f_1$  = high frequency 3 dB corner

$I_C$  =  $Q_1$  collector current

$A$  = mid band gain dB

*Example:* Design an ultra-low noise preamplifier with a gain of 1,000 operating from a 24 volt supply and a 600 $\Omega$  source impedance. Bandwidth of interest is 20 Hz to 10 kHz.

1. From Figure 3 the optimum collector current for 600 $\Omega$  source resistance is 170  $\mu$ A.
2. From equation (2),

$$R_1 + R_2 = \frac{V_S - 2.1}{I_C - 18 \times 10^{-6}} = \frac{24 - 2.1}{(170 - 18) \times 10^{-6}}$$

$$R_1 + R_2 = 1.44 \times 10^5.$$

3. From equation (4),

$$R_2 = 3 R_1 = \frac{1.44 \times 10^5}{1.333} = 1.08 \times 10^5$$

$$R_2 \approx 100 \text{ k}\Omega.$$

$$R_1 = 36 \times 10^3 \approx 39 \text{ k}\Omega.$$

4. From equation (7) let  $R_8 = 1 \text{ k}\Omega$ .

5. From equation (8),

$$R_f = \frac{1}{2} \left[ \frac{V_S \times 10^7}{6.05 \times 10^3 + I_C \times 10^7} \right] - 910$$

$$R_f = \frac{1}{2} \left[ \frac{24 \times 10^7}{6.05 \times 10^3 + 1.7 \times 10^3} \right] - 910$$

$$R_f = 2.67 \times 10^4 \approx 27 \text{ k}\Omega.$$

6. For a gain of 1,000; equation (9),

$$\text{Amplifier Gain} = \frac{(R_f + R_4)}{R_4} = 1,000$$

$$R_4 = \frac{27 \times 10^3}{10^3} = 27\Omega.$$

7. For a low corner frequency,  $f_o$ , of 20 Hz; equation (10),

$$C_2 = \frac{1}{2\pi f_o R_4} = \frac{1}{6.28 \times 20 \times 27}$$

$$= 2.95 \times 10^{-4}$$

$$C_2 \approx 300 \mu\text{F}.$$

8. From equation (5) the gain of the input stage is:

$$A_1 = \frac{(2 \times 10^5) R_2}{R_2 + 2 \times 10^5} \cdot \frac{1}{\frac{1}{I_C} + \frac{1}{10^4} + \frac{1}{R_3} + \frac{1}{R_4}}$$

$$A_1 = \frac{2 \times 10^5 \times 10^5}{10^5 + 2 \times 10^5} \cdot \frac{.026}{1.7 \times 10^{-4} + \frac{1}{10^4} + \frac{1}{10^3} + \frac{1}{27}}$$

$$A_1 = 372.$$

9. For 100 dB supply rejection at 120 Hz. Equation (3),

$$C_1 = \frac{\frac{P.S.R.}{10^{\frac{P.S.R.}{20}}}}{2\pi f R_1 A_1} = \frac{100}{2\pi \times 120 \times 39 \times 10^3 \times 372}$$

$$C_1 = \frac{10^5}{1.09 \times 10^{10}} = 9.1 \times 10^{-6}$$

$$C_1 \approx 10 \mu F.$$

10. For a high frequency corner,  $f_1$ , of 10 kHz; equation (11),

$$C_3 = \frac{1}{2\pi f_1 \left( \frac{.026}{I_C} \right) 10^{\frac{A}{20}}} \cdot 4 \times 10^{-12}$$

$$C_3 = \frac{1}{6.28 \times 10^4 \times 1.53 \times 10^2 \times 10^4} \cdot 4 \times 10^{-12}$$

$$C_3 = 6.4 \times 10^{-12} \approx 6.8 \text{ pF}.$$

The noise performance of the circuit of Figure 6 can be found with the aid of Figures 2A and 2B and equation (1). From Figures 2A and 2B the noise voltage ( $e_n$ ) and noise current ( $i_n$ ) at  $170 \mu A$   $I_C$  are:  $e_n = 3.0 \text{ nV}/\sqrt{\text{Hz}}$ ,  $i_n = .72 \text{ pA}/\sqrt{\text{Hz}}$ . From equation (1)

$$E_T = \sqrt{[e_n^2 + (i_n R_S)^2 + 4KTR_S]} \text{ B.W.}$$

$$= \sqrt{[(3.0 \times 10^9)^2 + (7.2 \times 10^{-13} \times 600)^2 + 9.94 \times 10^{-18}] \times 10^4}$$

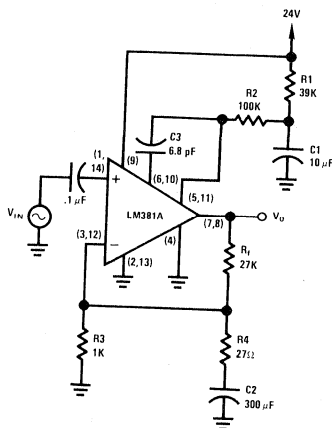


FIGURE 6. Typical Application with Increased Current Density of Input Stage

$$\text{Total Wideband Noise Voltage} = 4.37 \times 10^{-7} \text{ V}.$$

$$\text{Wideband Noise Figure} = 10 \log \frac{4KTR_S + e_n^2 + (i_n R_S)^2}{4KTR_S}$$

$$= 10 \log \frac{9.94 \times 10^{-18} + 9.0 \times 10^{-18} + 1.86 \times 10^{-19}}{9.94 \times 10^{-18}}$$

$$= 10 \log 1.92 = 2.83 \text{ dB}.$$

## CONCLUSION

In applications requiring a wide band, high gain preamplifier where noise performance is critical, the LM381A is unsurpassed. In addition to ultra low noise performance, the LM381A offers two completely independent amplifiers, each with an internal power supply decoupler-regulator providing 120 dB supply rejection and 60 dB channel separation.

Other outstanding features include, high gain (112 dB) large output voltage swing ( $V_S - 2V$ ) peak to peak, wide supply operating range (9 - 40V), wide power bandwidth (75 kHz, 20  $V_{p-p}$ ), internal frequency compensation, and short-circuit protection

## REFERENCE

J.E. Byerly and E.L. Long — "LM381 Low Noise Dual Preamplifier" National Semiconductor Corporation AN-64, May 1972.

# Micropower Circuits Using the LM4250 Programmable Op Amp

National Semiconductor  
Application Note 71  
Marvin K. Vander Kooi  
George Cleveland  
July 1972



## INTRODUCTION

The LM4250 is a highly versatile monolithic operational amplifier. A single external programming resistor determines the quiescent power dissipation, input offset and bias currents, slew rate, gain-bandwidth product, and input noise characteristics of the amplifier. Since the device is in effect a different op amp for each externally programmed set current, it is possible to use a single stock item for a variety of circuit functions in a system.

This paper describes the circuit operation of the LM4250, various methods of biasing the device, frequency response considerations, and some circuit applications exercising the unique characteristics of the LM4250.

## CIRCUIT DESCRIPTION LM4250

The LM4250 has two special features when compared with other monolithic operational amplifiers. One is the ability to externally set the bias current levels of the amplifiers, and the other is the use of PNP transistors as the differential input pair.

$R_1$  and  $R_2$  provide emitter degeneration for greater stability at high bias currents.  $Q_3$  and  $Q_4$  are used as active loads for  $Q_1$  and  $Q_2$  to provide high gain and also form a current inverter to provide the maximum drive for the single ended output into  $Q_5$ .  $Q_5$  is an emitter follower which prevents loading of the input stage by the succeeding amplifier stage.

One advantage of this lateral PNP input stage is a common mode swing to within 200 mV of the negative supply. This feature is especially useful in single supply operation with signals referred to ground. Another advantage is the almost constant input bias current over a wide temperature range. The input resistance  $R_{IN}$  is approximately equal to  $2\beta(R_E + r_e)$  where  $\beta$  is the current gain,  $r_e$  is the emitter resistance of one of the input lateral PNPs, and  $R_E$  is the resistance of one of the 10 k $\Omega$  emitter resistors. Using a DC beta of 100 and the normal temperature dependent expression for  $r_e$  gives:

$$R_{IN} \approx 2 M\Omega + 2 \frac{kT}{qI_B} \quad (1)$$

where  $I_B$  is input bias current. At room temperature this formula becomes:

$$R_{IN} \approx 2 M\Omega + \frac{52 mV}{I_B} \quad (2)$$

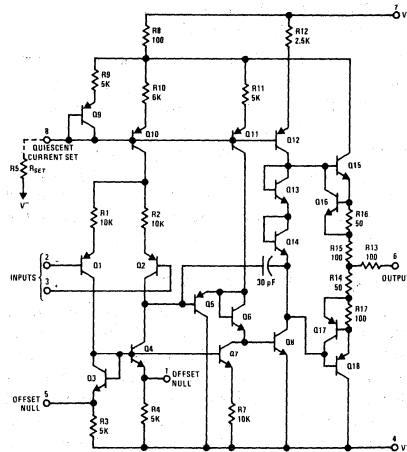


FIGURE 1. LM4250 Schematic Diagram

Referring to Figure 1,  $Q_1$  and  $Q_2$  are high current gain lateral PNPs connected as a differential pair.

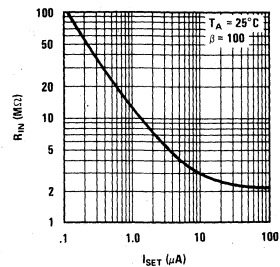


FIGURE 2. Input Resistance vs  $I_{SET}$

Figure 2 gives a typical plot of  $R_{IN}$  vs  $I_{SET}$  derived from the above equation.

Continuing with the circuit description,  $Q_8$  level shifts downward to the base of  $Q_8$  which is the second stage amplifier.  $Q_8$  is run as a common emitter amplifier with a current source load ( $Q_{12}$ ) to provide maximum gain. The output of  $Q_8$  drives the class B complementary output stage composed of  $Q_{15}$  and  $Q_{18}$ .

The bias current levels in the LM4250 are set by the amount of current ( $I_{SET}$ ) drawn out of Pin 8. The constant current sources  $Q_{10}$ ,  $Q_{11}$ , and  $Q_{12}$  are controlled by the amount of  $I_{SET}$  current through the diode connected transistor  $Q_9$  and resistor  $R_9$ . The constant collector current from  $Q_{10}$  biases the differential input stage. Therefore, the level  $Q_{10}$  is set at will control such amplifier characteristics as input bias current, input resistance, and amplifier slew rate. Current source  $Q_{11}$  biases  $Q_5$  and  $Q_6$ . The current ratio between  $Q_5$  and  $Q_6$  is controlled by constant current sink  $Q_7$ . Current source  $Q_{12}$  sets the currents in diodes  $Q_{13}$  and  $Q_{14}$  which bias the output stage to the verge of conduction thereby eliminating the dead zone in the class B output.  $Q_{12}$  also acts as the load for  $Q_8$  and limits the drive current to  $Q_{15}$ .

The output current limiting is provided by  $Q_{16}$  and  $Q_{17}$  and their associated resistors  $R_{16}$  and  $R_{17}$ . When enough current is drawn from the output,  $Q_{16}$  turns on and limits the base drive of  $Q_{15}$ . Similarly  $Q_{17}$  turns on when the LM4250 attempts to sink too much current, limiting the base drive of  $Q_{18}$  and therefore output current. Frequency compensation is provided by the 30 pF capacitor across the second stage amplifier,  $Q_8$ , of the LM4250. This provides a 6 dB per octave rolloff of the open loop gain.

### BIAS CURRENT SETTING PROCEDURE

The single set resistor shown in Figure 3a offers the most straightforward method of biasing the LM4250. When the set resistor is connected from Pin 8 to ground the resistance value for a given set current is:

$$R_{SET} = \frac{V^+ - 0.5}{I_{SET}} \quad (3)$$

The 0.5 volts shown in Equation 3 is the voltage drop of the master bias current diode connected transistor on the integrated circuit chip. In applications where the regulation of the  $V^+$  supply with respect to the  $V^-$  supply (as in the case of tracking regulators) is better than the  $V^+$  supply with respect to ground the set resistor should be connected from Pin 8 to  $V^-$ .  $R_{SET}$  is then:

$$R_{SET} = \frac{V^+ + |V^-| - 0.5}{I_{SET}} \quad (4)$$

The transistor and resistor scheme shown in Figure 3b allows one to switch the amplifier off without disturbing the main  $V^+$  and  $V^-$  power supply connections. Attaching  $C_1$  across the circuit prevents any switching transient from appearing at the amplifier output. The dual scheme shown in Figure 3c has a constant set current flowing through  $R_{S1}$  and a variable current through  $R_{S2}$ . Transistor

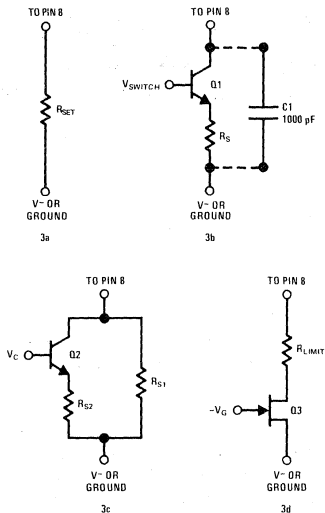


FIGURE 3. Biasing Schemes

$Q_2$  acts as an emitter follower current sink whose value depends on the control voltage  $V_c$  on the base. This circuit provides a method of varying the amplifier's characteristics over a limited range while the amplifier is in operation. The FET circuit shown in Figure 3d covers the full range of set currents in response to as little as a 0.5V gate potential change on a low pinch-off voltage FET such as the 2N3687. The limit resistor prevents excessive current flow out of the LM4250 when the FET is fully turned on.

### FREQUENCY RESPONSE OF A PROGRAMMABLE OP AMP

This section provides a method of determining the sine and step voltage response of a programmable op amp. Both the sine and step voltage responses of an amplifier are modified when the rate of change of the output voltage reaches the slew rate limit of the amplifier. The following analysis develops the Bode plot as well as the small signal and slew rate limited responses of an amplifier to these two basic categories of waveforms.

#### Small Signal Sine Wave Response

The key to constructing the Bode plot for a programmable op amp is to find the gain bandwidth product, GBWP, for a given set current. Quiescent power drain, input bias current, or slew rate considerations usually dictate the desired set current. The data sheet curve relating GBWP to set current provides the value of GBWP which when divided by one yields the unity gain crossover of  $f_u$ . Assuming a set current of  $6 \mu A$  gives a GBWP of 200,000 Hz and therefore an  $f_u$  of 200 kHz for the example shown in Figure 4. Since the device has a single dominant pole, the rolloff slope is -20 dB of gain per decade of frequency (-6 dB/octave). The dotted line shown



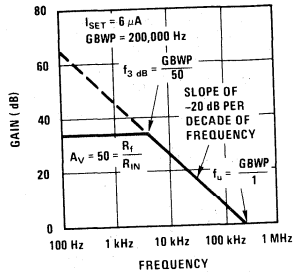


FIGURE 4. Bode Plot

on Figure 4 has this slope and passes through the 200 kHz  $f_u$  point. Arbitrarily choosing an inverting amplifier with a closed loop gain magnitude of 50 determines the height of the 34 dB horizontal line shown in Figure 4. Graphically finding the intersection of the sloped line and the horizontal line or mathematically dividing GBWP by 50 determines the 3 dB down frequency of 4 kHz for the closed loop response of this amplifier configuration. Therefore, the amplifier will now apply a gain of -50 to all small signal sine waves at frequencies up to 4 kHz. For frequencies above 4 kHz, the gain will be as shown on the sloped portion of the Bode plot.

#### Small Signal Step Input Response

The amplifier's response to a positive step voltage change at the input will be an exponentially rising waveform whose rise time is a function of the closed loop 3 dB down bandwidth of the amplifier. The amplifier may be modeled as a single pole low pass filter followed by a gain of 50 wideband amplifier. From basic filter theory\*, the 10% to 90% rise time of a single pole low pass filter is:

$$t_r = \frac{0.35}{f_{3\text{ dB}}} \quad (5)$$

For the example shown in Figure 4 the 4 kHz 3 dB down frequency would give a rise time of 87.5  $\mu\text{s}$ .

#### Slew Rate Limited Large Signal Response

The final consideration, which determines the upper speed limitation on the previous two types of signal responses, is the amplifier slew rate. The slew rate of an amplifier is the maximum rate of change of the output signal which the amplifier is capable of delivering. In the case of sinusoidal signals, the maximum rate of change occurs at the zero crossing and may be derived as follows:

$$v_o = V_p \sin 2\pi f t \quad (6)$$

$$\frac{dv_o}{dt} = 2\pi f V_p \cos 2\pi f t \quad (7)$$

$$\left. \frac{dv_o}{dt} \right|_{t=0} = 2\pi f V_p \quad (8)$$

$$S_r = 2\pi f_{\text{MAX}} V_p \quad (9)$$

\*See reference.

where:

$v_o$  = output voltage

$V_p$  = peak output voltage

$S_r$  = maximum  $\frac{dv_o}{dt}$

The maximum sine wave frequency an amplifier with a given slew rate will sustain without causing the output to take on a triangular shape is therefore a function of the peak amplitude of the output and is expressed as:

$$f_{\text{MAX}} = \frac{S_r}{2\pi V_p} \quad (10)$$

Figure 5 shows a quick reference graphical presentation of this formula with the area below any  $V_{\text{PEAK}}$  line representing an undistorted small signal sine wave response for a given frequency and amplifier slew rate and the area above the  $V_{\text{PEAK}}$  line representing a distorted sine wave response due to slew rate limiting for a sine wave with the given  $V_{\text{PEAK}}$ .

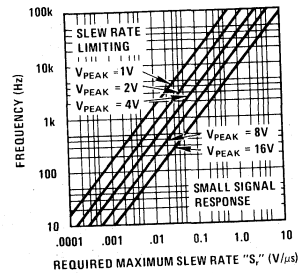


FIGURE 5. Frequency vs Slew Rate Limit vs Peak Output Voltage

Large signal step voltage changes at the output will have a rise time as shown in equation 5 until a signal with a rate of output voltage change equal to the slew rate of the amplifier occurs. At this point the output will become a ramp function with a slope equal to  $S_r$ . This action occurs when:

$$S_r \leq \frac{V_{\text{STEP}}}{t_r} \quad (11)$$

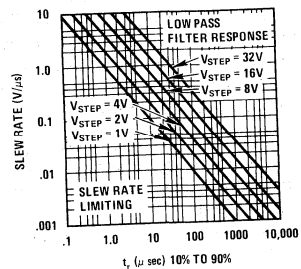


FIGURE 6. Slew Rate vs Rise Time vs Step Voltage

Figure 6 graphically expresses this formula and shows the maximum amplitude of undistorted step voltage for a given slew rate and rise time.

The area above each step voltage line represents the undistorted low pass filter type response mode of the amplifier. If the intersection of the rise time and slew rate values of a particular amplifier configuration falls below the expected step voltage amplitude line, the rise time will be determined by the slew rate of the amplifier. The rise time will then be equal to the amplitude of the step divided by the slew rate  $S_r$ .

### Full Power Bandwidth

The full power bandwidth often found on amplifier specification sheets is the range of frequencies from zero to the frequency found at the intersection on Figure 5 of the maximum rated output voltage and the slew rate  $S_r$  of the amplifier. Mathematically this is:

$$f_{\text{full power}} = \frac{S_r}{2\pi V_{\text{rated}}} \quad (12)$$

The full power bandwidth of a programmable amplifier such as the LM4250 varies with the master bias set current.

The above analysis of sine wave and step voltage amplifier responses applies for all single dominant pole op amps such as the LM101A, LM107, LM108A, LM112, LM118, and LM741 as well as the LM4250 programmable op amp.

### 500 NANO-WATT X10 AMPLIFIER

The X10 inverting amplifier shown in Figure 7 demonstrates the low power capability of the LM4250 at extremely low values of supply voltage and set current. The circuit draws 260 nA from the +1.0V supply of which 50 nA flows through the 12 M $\Omega$  set resistor. The current into the -1.0V supply is only 210 nA since the set resistor is tied to ground rather than  $V^-$ . Total quiescent power dissipation is:

$$P_D = (260 \text{ nA})(1\text{V}) + (210 \text{ nA})(1\text{V}) \quad (13)$$

$$P_D = 470 \text{ nW} \quad (14)$$

The slew rate determined from the data sheet typical performance curve is 1 V/ms for a .05  $\mu\text{A}$  set current. Samples of actual values observed were 1.2 V/ms for the negative slew rate and 0.85 V/ms for the positive slew rate. This difference occurs due to the non-symmetry in the current sources used for charging and discharging the internal 30 pF compensation capacitor.

The 3 dB down (gain of -7.07) frequency observed for this configuration was approximately 300 Hz which agrees fairly closely with the 3.5 kHz GBWP divided by 10 taken from an extrapolation of the data sheet typical GBWP versus set current curve.

Peak-to-peak output voltage swing into a 100 k $\Omega$  load is 0.7V or  $\pm 0.35\text{V}$  peak. An increase in supply voltage to  $\pm 1.35\text{V}$  such as delivered by a pair of mercury cells directly increases the output swing by  $\pm 0.35\text{V}$  to 1.4V peak-to-peak. Although this

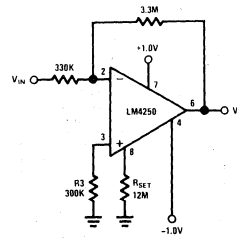


FIGURE 7. 500 nW x 10 Amplifier

increases the power dissipation to approximately 1  $\mu\text{W}$  per battery, a power drain of 15  $\mu\text{W}$  or less will not affect the shelf life of a mercury cell.

### MICRO-POWER MONITOR WITH HIGH CURRENT SWITCH

Figure 8 shows the combination of a micro-power comparator and a high current switch run from a separate supply. This circuit provides a method of continuously monitoring an input voltage while dissipating only 100  $\mu\text{W}$  of power and still being capable of switching a 500 mA load if the input exceeds a given value. The reference voltage can be any value between +8.5V and -8.5V. With a minimum gain of approximately 100,000 the comparator can resolve input voltage differences down into the 0.2 mV region.

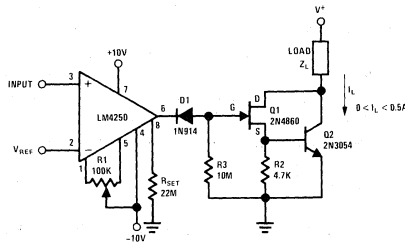


FIGURE 8.  $\mu$ -Power Comparator with High Current Switch

The bias current for the LM4250 shown in Figure 8 is set at 0.44  $\mu\text{A}$  by the 22 M $\Omega$   $R_{\text{SET}}$  resistor. This results in a total comparator power drain of 100  $\mu\text{W}$  and a slew rate of approximately 11 V/ms in the positive direction and 12.8 V/ms in the negative direction. Potentiometer  $R_1$  provides input offset nulling capability for high accuracy applications. When the input voltage is less than the reference voltage, the output of the LM4250 is at approximately -9.5V causing diode  $D_1$  to conduct. The gate of  $Q_1$  is held at -8.8V by the voltage developed across  $R_3$ . With a large negative voltage on the gate of  $Q_1$  it turns off and removes the base drive from  $Q_2$ . This results in a high voltage or open switch condition at the collector of  $Q_2$ . When the input voltage exceeds the reference voltage, the LM4250 output goes to +9.5V causing  $D_1$  to be reverse biased.  $Q_1$  turns on as does  $Q_2$ , and the collector of  $Q_2$  drops to approximately 1V while sinking the 500 mA of load current.

The load denoted as  $Z_L$  can be resistor, relay coil, or indicator lamp as required; but the load current should not exceed 500 mA. For  $V^+$  values of less than 15V and  $I_L$  values of less than 25 mA both  $Q_2$  and  $R_2$  may be omitted. With only the 2N4860 JFET as an output device the circuit is still capable of driving most common types of indicator lamps.

### IC METER AMPLIFIER RUNS ON TWO FLASHLIGHT BATTERIES

Meter amplifiers normally require one or two 9V transistor batteries. Due to the heavy current drain on these supplies, the meters must be switched to the OFF position when not in use. The meter circuit described here operates on two 1.5V flashlight batteries and has a quiescent power drain so low that no ON-OFF switch is needed. A pair of Eveready No. 950 "D" cells will serve for a minimum of one year without replacement. As a DC ammeter, the circuit will provide current ranges as low as 100 nA full-scale.

The basic meter amplifier circuit shown in Figure 9 is a current-to-voltage converter. Negative feedback around the amplifier insures that currents  $I_{IN}$  and  $I_f$  are always equal, and the high gain of the op amp insures that the input voltage between Pins 2 and 3 is in the microvolt region. Output

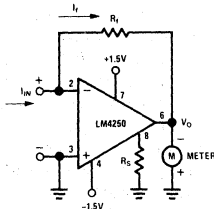


FIGURE 9. Basic Meter Amplifier

voltage  $V_o$  is therefore equal to  $-I_f R_f$ . Considering the  $\pm 1.5V$  sources ( $\pm 1.2V$  end-of-life) a practical value of  $V_o$  for full scale meter deflection is 300 mV. With the master bias-current setting resistor ( $R_f$ ) set at 10 M $\Omega$ , the total quiescent current drain of the circuit is 0.6  $\mu A$  for a total power supply drain of 1.8  $\mu W$ . The input bias current, required by the amplifier at this low level of quiescent current, is in the range of 600 pA.

#### The Complete Nanoammeter

The complete meter amplifier shown in Figure 10 is a differential current-to-voltage converter with input protection, zeroing and full scale adjust provisions, and input resistor balancing for minimum offset voltage. Resistor  $R'_f$  (equal in value to  $R_f$  for measurements of less than 1  $\mu A$ ) insures that the input bias currents for the two input terminals of the amplifier do not contribute significantly to an output error voltage. The output voltage  $V_o$  for the differential current-to-voltage converter is equal to  $-2I_f R_f$  since the floating input current  $I_{IN}$  must flow through  $R_f$  and  $R'_f$ .  $R'_f$  may be omitted for  $R_f$  values of 500 k $\Omega$  or less,

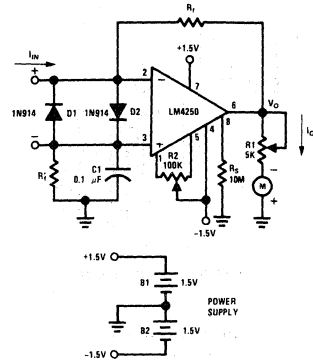


FIGURE 10. Complete Meter Amplifier

#### Resistance Values for DC Nano and Micro Ammeter

I FULL SCALE	$R_f$ [ $\Omega$ ]	$R'_f$ [ $\Omega$ ]
100 nA	1.5M	1.5M
500 nA	300k	300k
1 $\mu A$	300k	0
5 $\mu A$	60k	0
10 $\mu A$	30k	0
50 $\mu A$	6k	0
100 $\mu A$	3k	0

since a resistance of this value contributes an error of less than 0.1% in output voltage. Potentiometer  $R_2$  provides an electrical meter zero by forcing the input offset voltage  $V_{os}$  to zero. Full scale meter deflection is set by  $R_1$ . Both  $R_1$  and  $R_2$  only need to be set once for each op amp and meter combination. For a 50 microamp 2 k $\Omega$  meter movement,  $R_1$  should be about 4 k $\Omega$  to give full scale meter deflection in response to a 300 mV output voltage. Diodes  $D_1$  and  $D_2$  provide full input protection for overcurrents up to 75 mA.

With an  $R_f$  resistor value of 1.5M the circuit in Figure 10 becomes a nanometer with a full scale reading capability of 100 nA. Reducing  $R_f$  to 3 k $\Omega$  in steps, as shown in Figure 10 increases the full scale deflection to 100  $\mu A$ , the maximum for this circuit configuration. The voltage drop across the two input terminals is equal to the output voltage  $V_o$  divided by the open loop gain. Assuming an open loop gain of 10,000 gives an input voltage drop of 30  $\mu V$  or less.

#### Circuit for Higher Current Readings

For DC current readings higher than 100  $\mu A$ , the inverting amplifier configuration shown in Figure 11 provides the required gain. Resistor  $R_A$  develops a voltage drop in response to input current  $I_A$ . This voltage is amplified by a factor equal to the ratio of  $R_f/R_B$ .  $R_B$  must be sufficiently larger than  $R_A$ , so as not to load the input signal. Figure 11 also shows the proper values of  $R_A$ ,  $R_B$  and  $R_f$  for full scale meter deflections of from 1 mA to 10A.

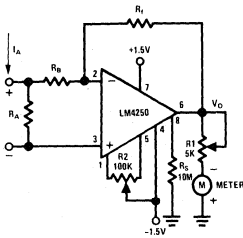


FIGURE 11. Ammeter

Resistance Values for DC Ammeter

I FULL SCALE	RA [Ω]	RB [Ω]	RF [Ω]
1 mA	3.0	3k	300k
10 mA	.3	3k	300k
100 mA	.3	30k	300k
1A	.03	30k	300k
10A	.03	30k	30k

#### A 10 mV to 100V Full-Scale Voltmeter

A resistor inserted in series with one of the input leads of the basic meter amplifier converts it to a wide range voltmeter circuit, as shown in Figure 12. This inverting amplifier has a gain varying from -30 for the 10 mV full scale range to -0.003 for the 100V full scale range. Figure 12 also lists the proper values of  $R_V$ ,  $R_f$ , and  $R'_f$  for each range. Diodes  $D_1$  and  $D_2$  provide complete

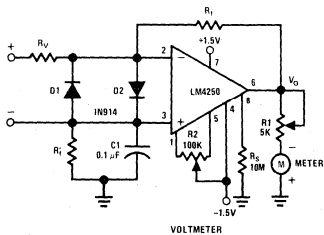


FIGURE 12. Voltmeter

Resistance Values for a DC Voltmeter

V FULL SCALE	RV [Ω]	Rf [Ω]	R'f [Ω]
10 mV	100k	1.5M	1.5M
100 mV	1M	1.5M	1.5M
1V	10M	1.5M	1.5M
10V	10M	300k	0
100V	10M	30k	0

amplifier protection for input overvoltages as high as 500V on the 10 mV range, but if overvoltages of this magnitude are expected under continuous operation, the power rating of  $R_V$  should be adjusted accordingly.

#### LOW FREQUENCY PULSE GENERATOR USING A SINGLE +5V SUPPLY

The variable frequency pulse generator shown in Figure 13 provides an example of the LM4250 operated from a single supply. The circuit is a buffered output free running multivibrator with a constant width output pulse occurring with a frequency determined by potentiometer  $R_2$ .

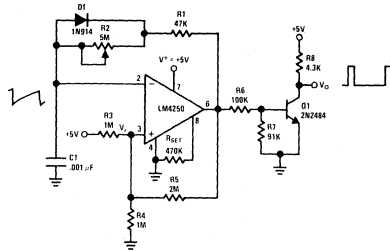


FIGURE 13. Pulse Generator

The LM4250 acts as a comparator for the voltages found at the upper plate of capacitor  $C_1$  and at the reference point denoted as  $V_r$  on Figure 13. Capacitor  $C_1$  charges and discharges with a peak-to-peak amplitude of approximately 1V determined by the shift in reference voltage  $V_r$  at Pin 3 of the op amp. The charge path of  $C_1$  is from the amplifier output, which is at its maximum positive voltage  $V_{HIGH}$  (approximately  $V^+ - 0.5V$ ), through  $R_1$  and through the potentiometer  $R_2$ . Diode  $D_1$  is reverse biased during the charge period. When  $C_1$  charges to the  $V_r$  value determined by the net result of  $V_{HIGH}$  through resistor  $R_5$  and  $V^+$  through the voltage divider made up of resistors  $R_3$  and  $R_4$  the amplifier swings to its lower limit of approximately 0.5V causing  $C_1$  to begin discharging. The discharge path is through the forward biased diode  $D_1$ , through resistor  $R_1$ , and into Pin 6 of the op amp. Since the impedance in the discharge path does not vary for  $R_2$  settings of from 3 kΩ to 5 MΩ, the output pulse maintains a constant pulse width of  $41 \mu s \pm 1.5 \mu s$  over this range of potentiometer settings. Figure 14 shows the output pulse frequency variation from 6 kHz down to 360 Hz as  $R_2$  places from 100 kΩ up to 5 MΩ of additional resistance in the charge path of  $C_1$ . Setting  $R_2$  to zero ohms will short out diode  $D_1$  and cause a symmetrical square wave output at a frequency of 10 kHz. Increasing the value of  $C_1$  will lower the range of frequencies available in response to the  $R_2$  variation shown on Figure 14. Electrolytic capacitors may be used for the larger values of  $C_1$  since it has only positive voltages applied to it.

The output buffer  $Q_1$  presents a constant load to the op amp output thereby preventing frequency variations caused by  $V_{HIGH}$  and  $V_{LOW}$  voltages changing as a function of load current. The output of  $Q_1$  will interface directly with a standard TTL or DTL logic device. Reversing diode  $D_1$  will invert

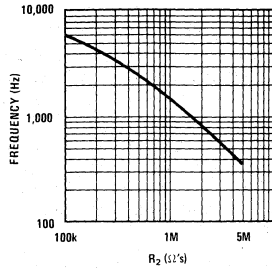


FIGURE 14. Pulse Frequency vs R<sub>2</sub>

the polarity of the generator output providing a series of negative going pulses dropping from +5V to the saturation voltage of Q<sub>1</sub>.

The change in output frequency as a function of supply voltage is less than ±4% for a V<sup>+</sup> change of from 4V to 10V. This stability of frequency versus supply voltage is due to the fact that the reference voltage V<sub>r</sub> and the drive voltage for the capacitor are both direct functions of V<sup>+</sup>.

The power dissipation of the free running multivibrator is 300 μW and the power dissipation of the buffer circuit is approximately 5.8 mW.

#### X100 INSTRUMENTATION AMPLIFIER

The instrumentation amplifier circuit shown in Figure 15 has a full differential input center tapped to ground. With the bias current set at approximately 0.1 μA, the impedance looking into either V<sub>IN1</sub> or V<sub>IN2</sub> is 100 MΩ with respect to ground, and the input bias current at either terminal is 0.2 nA. The two non-inverting input

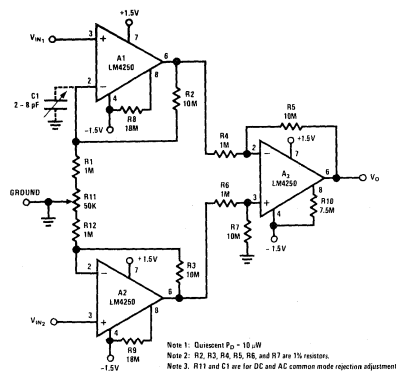


FIGURE 15. x 100 Instrumentation Amplifier

stages A<sub>1</sub> and A<sub>2</sub> apply a gain of 10 to the input signal, and the differential output stage applies an additional gain of -10 for a net amplifier gain of -100:

$$V_o = -100 (V_{IN1} - V_{IN2}) \quad (15)$$

The entire circuit can run from two 1.5V batteries connected directly (no power switch) to the V<sup>+</sup> and V<sup>-</sup> terminals. With a total current drain of 2.8 μA the quiescent power dissipation of the circuit is 8.4 μW. This is low enough to have no significant effect on the shelf life of most batteries.

Potentiometer R<sub>11</sub> provides a means for matching the gains of A<sub>1</sub> and A<sub>2</sub> to achieve maximum DC common mode rejection ratio CMRR. With R<sub>11</sub> adjusted to its null point for DC common mode rejection the small AC CMRR trimmer capacitor C<sub>1</sub> will normally give an additional 10 to 20 dB of CMRR over the operating frequency range. Since C<sub>1</sub> actually balances wiring capacitance rather than amplifier frequency characteristics, it may be necessary to attach it to Pin 2 of either A<sub>1</sub> or A<sub>2</sub> as required. Figure 16 shows the variation of CMRR (referred to the input) with frequency for

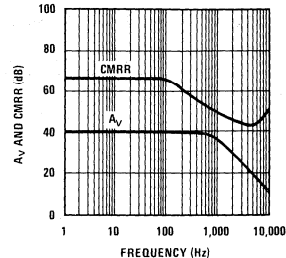


FIGURE 16. A<sub>v</sub> and CMRR vs Frequency

this configuration. Since the circuit applies a gain of 100 or 40 dB to an input signal, the actual observed rejection ratio is the difference between the CMRR curve and A<sub>v</sub> curve. For example, a 60 Hz common mode signal will be attenuated by 67 dB minus 40 dB or 27 dB for an actual rejection ratio of V<sub>IN</sub>/V<sub>O</sub> equal to 22.4.

The maximum peak-to-peak output signal into a 100 kΩ load resistor is approximately 1.8V. With no input signal, the noise seen at the output is approximately 0.8 mV<sub>RMS</sub> or 8 μV<sub>RMS</sub> referred to the input. When doing power dissipation measurements on this circuit, it should be kept in mind that even a 1 MΩ oscilloscope probe placed between +1.5V and -1.5V will more than double the power drawn from the batteries.

#### 5V REGULATOR FOR CMOS LOGIC CIRCUITS

The ideal regulator for low power CMOS logic elements should dissipate essentially no power when the CMOS devices are running at low frequencies, but be capable of delivering full output power on demand when the CMOS devices are running in the 0.1 MHz to 10 MHz region. With a 10V input voltage, the regulator shown in Figure 17 will dissipate 350 μW in the stand-by mode but will deliver up to 50 mA of continuous load current when required.

The circuit is basically a boosted output voltage-follower referenced to a low current zener diode.

The voltage divider consisting of  $R_2$  and  $R_3$  provides a 5V tap voltage from the 6.5V reference diode to determine the regulator output. Since a standard 6.5V zener diode does not exhibit good regulation in the  $2\ \mu\text{A}$  to  $60\ \mu\text{A}$  reverse current region,  $Q_2$  must be a special device. An NPN

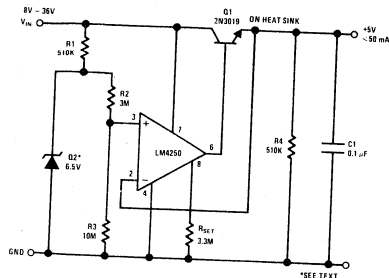


FIGURE 17. 350  $\mu\text{W}$  Quiescent Drain 5 Volt Regulator

transistor with its collector and base terminals grounded and its emitter tied to the junction of  $R_1$  and  $R_2$  exhibits a well-controlled base emitter

reverse breakdown voltage. A National Semiconductor process 25 small signal NPN transistor sorted to a 2N registration such as 2N3252 has a  $BV_{EBO}$  at  $10\ \mu\text{A}$  specified as 5.5V minimum, 6.5V typical, and 7.0V maximum. Using a diode connected 2N3252 as a reference, the regulator output voltage changed 78 mV in response to an 8V to 36V change in the input voltage. This test was done under both no load and full load conditions and represents a line regulation of better than 1.6%.

A load change from  $10\ \mu\text{A}$  to 50 mA caused a 1 mV change in output voltage giving a load regulation value of .05%. When operating the regulator at load currents of less than 25 mA, no heat sink is required for  $Q_1$ . For load currents in excess of 50 mA,  $Q_1$  should be replaced by a Darlington pair with the 2N3019 acting as a driver for a higher power device such as a 2N3054.

#### REFERENCES

Millman, J. and Hawkias, C.C.: "Electronic Device and Circuits," pp. 465-466, McGraw-Hill Book Company, New York, 1967.

# The LM3900 — A New Current-Differencing Quad of $\pm$ Input Amplifiers

National Semiconductor  
 Application Note 72  
 T. M. Frederiksen  
 W. M. Howard  
 R. S. Sleeth  
 September 1972



## PREFACE

With all the existing literature on "how to apply op amps" why should another application note be produced on this subject? There are two answers to this question; 1) the LM3900 operates in quite an unusual manner (compared to a conventional op amp) and therefore needs some explanation to familiarize a new user with this product, and 2) the standard op amp applications assume a split power supply ( $\pm 15 V_{DC}$ ) is available and our emphasis here is directed toward circuits for lower cost single power supply control systems. Some of these circuits are simply "re-biased" versions of conventional handbook circuits but many are new approaches which are made possible by some of the unique features of the LM3900.

## TABLE OF CONTENTS

SECTION	SUBJECT	PAGE
1.0	An Introduction to the New "Norton" Amplifier .....	AN72-1
	1.1 Basic Gain Stage .....	AN72-1
	1.2 Obtaining a Non-inverting Input Function .....	AN72-2
	1.3 The Complete Single-supply Amplifier .....	AN72-2
2.0	Introduction to Applications of the LM3900 .....	AN72-4
3.0	Designing AC Amplifiers .....	AN72-6
	3.1 Single Power Supply Biasing .....	AN72-6
	3.2 A Non-inverting Amplifier .....	AN72-6
	3.3 "N $V_{BE}$ " Biasing .....	AN72-7
	3.4 Biasing Using a Negative Supply .....	AN72-7
	3.5 Obtaining High Input Impedance and High Gain .....	AN72-7
	3.6 An Amplifier with a DC Gain Control .....	AN72-7
	3.7 A Line-receiver Amplifier .....	AN72-8
4.0	Designing DC Amplifiers .....	AN72-8
	4.1 Using Common-mode Biasing for $V_{IN} = 0 V_{DC}$ .....	AN72-8
	4.2 Adding an Output Diode for $V_O = 0 V_{DC}$ .....	AN72-9
	4.3 A DC Coupled Power Amplifier ( $I_L \leq 3$ Amps) .....	AN72-9
	4.4 Ground Referencing a Differential Voltage .....	AN72-9
	4.5 A Unity Gain Buffer Amplifier .....	AN72-10
5.0	Designing Voltage Regulators .....	AN72-10
	5.1 Reducing the Input-output Voltage .....	AN72-11
	5.2 Providing High Input Voltage Protection .....	AN72-11
	5.3 High Input Voltage Protection and Low ( $V_{IN} - V_{OUT}$ ) .....	AN72-12
	5.4 Reducing Input Voltage Dependence and Adding Short-circuit Protection .....	AN72-12
6.0	Designing RC Active Filters .....	AN72-13
	6.1 Biasing the Amplifiers .....	AN72-13
	6.2 A High Pass Active Filter .....	AN72-14
	6.3 A Low Pass Active Filter .....	AN72-14
	6.4 A Single-amplifier Bandpass Active Filter .....	AN72-15
	6.5 A Two-amplifier Bandpass Active Filter .....	AN72-16

## TABLE OF CONTENTS (Con't)

SECTION	SUBJECT	PAGE
6.0	Designing RC Active Filters (continued)	
	6.6 A Three-amplifier Bandpass Active Filter .....	AN72-17
	6.7 Conclusions .....	AN72-18
7.0	Designing Waveform Generators .....	AN72-18
	7.1 Sinewave Oscillator .....	AN72-19
	7.2 Squarewave Generator .....	AN72-19
	7.3 Pulse Generator .....	AN72-20
	7.4 Triangle Waveform Generator .....	AN72-21
	7.5 Sawtooth Waveform Generator .....	AN72-22
	7.5.1 Generating a Very Slow Sawtooth Waveform .....	AN72-22
	7.6 Staircase Waveform Generators .....	AN72-23
	7.7 A Pulse Counter and a Voltage Variable Pulse Counter .....	AN72-23
	7.8 An Up-down Staircase Waveform Generator .....	AN72-24
8.0	Designing Phase-locked Loops and Voltage Controlled Oscillators .....	AN72-24
	8.1 Voltage Controlled Oscillators (VCO) .....	AN72-24
	8.2 Phase Comparator .....	AN72-25
	8.3 A Complete Phase-locked Loop .....	AN72-26
	8.4 Conclusions .....	AN72-26
9.0	Designing Digital and Switching Circuits .....	AN72-26
	9.1 An "OR" Gate .....	AN72-26
	9.2 An "AND" Gate .....	AN72-27
	9.3 A Bi-stable Multivibrator .....	AN72-27
	9.4 Trigger Flip Flops .....	AN72-27
	9.5 Monostable Multivibrators (One-shots) .....	AN72-27
	9.5.1 A Two-amplifier One-shot .....	AN72-28
	9.5.2 A Combination One-shot/Comparator Circuit .....	AN72-28
	9.5.3 A One-amplifier One-shot (Positive Pulse) .....	AN72-28
	9.5.4 A One-amplifier One-shot (Negative Pulse) .....	AN72-29
	9.6 Comparators .....	AN72-29
	9.6.1 A Comparator for Positive Input Voltages .....	AN72-29
	9.6.2 A Comparator for Negative Input Voltages .....	AN72-29
	9.6.3 A Power Comparator .....	AN72-29
	9.6.4 A More Precise Comparator .....	AN72-29
	9.7 Schmitt-Triggers .....	AN72-30
10.0	Some Special Circuit Applications .....	AN72-30
	10.1 Current Sources and Sinks .....	AN72-30
	10.1.1 A Fixed Current Source .....	AN72-30
	10.1.2 A Voltage Variable Current Source .....	AN72-31
	10.1.3 A Fixed Current Sink .....	AN72-31
	10.1.4 A Voltage Variable Current Sink .....	AN72-31
	10.2 Operation From $\pm 15 V_{DC}$ Power Supplies .....	AN72-31
	10.2.1 An AC Amplifier Operating with $\pm 15 V_{DC}$ Power Supplies .....	AN72-32
	10.2.2 A DC Amplifier Operating with $\pm 15 V_{DC}$ Power Supplies .....	AN72-32
	10.3 Tachometers .....	AN72-32
	10.3.1 A Basic Tachometer .....	AN72-32
	10.3.2 Extending $V_{OUT}$ (Minimum) to Ground .....	AN72-33
	10.3.3 A Frequency Doubling Tachometer .....	AN72-33
	10.4 A Squaring Amplifier .....	AN72-33
	10.5 A Differentiator .....	AN72-34
	10.6 A Difference Integrator .....	AN72-34



## TABLE OF CONTENTS (Con't)

SECTION	SUBJECT	PAGE
10.0	Some Special Circuit Applications (continued)	
	10.7 A Low Drift Sample and Hold Circuit .....	AN72-34
	10.7.1 Reducing the "Effective" Input Biasing Current .....	AN72-34
	10.7.2 A Low Drift Ramp and Hold .....	AN72-34
	10.7.3 Sample-hold and Compare with New $+V_{IN}$ .....	AN72-35
	10.8 Audio Mixer or Channel Selector .....	AN72-35
	10.9 A Low Frequency Mixer .....	AN72-35
	10.10 A Peak Detector .....	AN72-36
	10.11 Power Circuits .....	AN72-36
	10.11.1 Lamp and/or Relay Drivers ( $\leq 30$ mA) .....	AN72-36
	10.11.2 Lamp and/or Relay Drivers ( $\leq 300$ mA) .....	AN72-36
	10.11.3 Positive Feedback Oscillators .....	AN72-37
	10.12 High Voltage Operation .....	AN72-37
	10.12.1 A High Voltage Inverting Amplifier .....	AN72-37
	10.12.2 A High Voltage Non-inverting Amplifier .....	AN72-37
	10.12.3 A Line Operated Audio Amplifier .....	AN72-38
	10.13 A Dual-channel Class-A Driver for Auto Radios .....	AN72-38
	10.14 Temperature Sensing .....	AN72-38
	10.15 A "Programmable Unijunction" .....	AN72-39
	10.16 Adding a Differential Input Stage .....	AN72-39

## LIST OF ILLUSTRATIONS

FIGURE NUMBER	TITLE	PAGE
1	Basic Gain Stage .....	AN72-1
2	Adding a PNP Transistor to the Basic Gain Stage .....	AN72-2
3	Adding a Current Mirror to Achieve a Non-inverting Input .....	AN72-2
4	The Amplifier Stage .....	AN72-3
5	Open-loop Gain Characteristics .....	AN72-3
6	Schematic Diagram of the LM3900 .....	AN72-4
7	An Equivalent Circuit of a Standard IC Op Amp .....	AN72-4
8	An Equivalent Circuit of the "Norton" Amplifier .....	AN72-4
9	Applying the LM3900 Equivalent Circuit .....	AN72-5
10	Biasing Equivalent Circuit .....	AN72-5
11	AC Equivalent Circuit .....	AN72-5
12	Inverting AC Amplifier Using Single-supply Biasing .....	AN72-6
13	Non-inverting AC Amplifier Using Voltage Reference Biasing .....	AN72-6
14	Inverting AC Amplifier Using N $V_{BE}$ Biasing .....	AN72-7
15	Negative Supply Biasing .....	AN72-7
16	A High $Z_{IN}$ High Gain Inverting AC Amplifier .....	AN72-7
17	An Amplifier with a DC Gain Control .....	AN72-8
18	A Line-receiver Amplifier .....	AN72-8
19	A DC Amplifier Employing Common-mode Biasing .....	AN72-8
20	An Ideal Circuit Model of a DC Amplifier with Zero Input Voltage .....	AN72-9
21	A Non-inverting DC Amplifier with Zero Volts Output for Zero Volts Input .....	AN72-9
22	Voltage Transfer Function for a DC Amplifier with a Voltage Gain of 10 .....	AN72-9
23	A DC Power Amplifier .....	AN72-9
24	Ground Referencing a Differential Input DC Voltage .....	AN72-9
25	A Network to Invert and to Ground Reference a Negative DC Differential Input Voltage .....	AN72-10
26	A Unity-gain DC Buffer Amplifier .....	AN72-10
27	Simple Voltage Regulators .....	AN72-11
28	Reducing $(V_{IN} - V_{OUT})$ .....	AN72-11
29	High $V_{IN}$ Protection and Self-regulation .....	AN72-12
30	A High $V_{IN}$ Protected, Low $(V_{IN} - V_{OUT})$ Regulator .....	AN72-12
31	Reducing $V_{IN}$ Dependence .....	AN72-12
32	Adding Short-circuit Current Limiting .....	AN72-12
33	Biasing Considerations .....	AN72-13
34	A High Pass Active Filter .....	AN72-14
35	A Low Pass Active Filter .....	AN72-14
36	Biasing the Low Pass Filter .....	AN72-15

## LIST OF ILLUSTRATIONS (Con't)

FIGURE NUMBER	TITLE	PAGE
37	Biasing Equivalent Circuit .....	AN72-15
38	A One Op amp Bandpass Filter .....	AN72-16
39	A Two Op amp Bandpass Filter .....	AN72-16
40	The "Bi-quad" RC Active Bandpass Filter .....	AN72-17
41	A Sinewave Oscillator .....	AN72-19
42	A Squarewave Oscillator .....	AN72-19
43	A Pulse Generator .....	AN72-20
44	A Triangle Waveform Generator .....	AN72-21
45	Gated Sawtooth Generators .....	AN72-22
46	Generating Very Slow Sawtooth Waveforms .....	AN72-22
47	Pumping the Staircase Via Input Differentiator .....	AN72-23
48	A Free Running Staircase Generator .....	AN72-23
49	An Up-down Staircase Generator .....	AN72-24
50	A Voltage Controlled Oscillator .....	AN72-24
51	Adding Input Common-mode Biasing Resistors .....	AN72-25
52	Reducing Temperature Drift .....	AN72-25
53	Improving Mark/Space Ratio .....	AN72-25
54	Phase Comparator .....	AN72-26
55	A Phase-locked Loop .....	AN72-26
56	An "OR" Gate .....	AN72-26
57	An "AND" Gate .....	AN72-27
58	A Large Fan-in "AND" Gate .....	AN72-27
59	A Bi-stable Multivibrator .....	AN72-27
60	A Trigger Flip Flop .....	AN72-27
61	A Two-amplifier Trigger Flip Flop .....	AN72-27
62	A One-shot Multivibrator .....	AN72-28
63	A One-shot Multivibrator with an Input Comparator .....	AN72-28
64	A One-amplifier One-shot (Positive Output) .....	AN72-28
65	A One-amplifier One-shot (Negative Output) .....	AN72-29
66	An Inverting Voltage Comparator .....	AN72-29
67	A Non-inverting Low-voltage Comparator .....	AN72-29
68	A Non-inverting Power Comparator .....	AN72-29
69	A More Precise Comparator .....	AN72-30
70	Schmitt-Triggers .....	AN72-30
71	Fixed Current Sources .....	AN72-31
72	A Voltage Controlled Current Source .....	AN72-31
73	Fixed Current Sinks .....	AN72-31
74	A Voltage Controlled Current Sink .....	AN72-31
75	An AC Amplifier Operating with $\pm 15 V_{DC}$ .....	AN72-32
76	DC Biasing for $\pm 15 V_{DC}$ Operation .....	AN72-32
77	A DC Amplifier Operating with $\pm 15 V_{DC}$ .....	AN72-32
78	A Basic Tachometer .....	AN72-33
79	Adding Biasing to Provide $V_O = 0 V_{DC}$ .....	AN72-33
80	A Frequency Doubling Tachometer .....	AN72-33
81	A Squaring Amplifier with Hysteresis .....	AN72-33
82	A Differentiator Circuit .....	AN72-34
83	A Difference Integrator .....	AN72-34
84	Reducing $I_B$ "Effective" to Zero .....	AN72-34
85	A Low-drift Ramp and Hold Circuit .....	AN72-35
86	Sample-hold and Compare with New $+V_{IN}$ .....	AN72-35
87	Audio Mixing or Selection .....	AN72-35
88	A Low Frequency Mixer .....	AN72-36
89	A Peak Detector .....	AN72-36
90	Sinking 20 to 30 mA Loads .....	AN72-36
91	Boosting to 300 mA Loads .....	AN72-37
92	Positive Feedback Power Oscillators .....	AN72-37
93	A High Voltage Inverting Amplifier .....	AN72-37
94	A High Voltage Non-inverting Amplifier .....	AN72-37
95	A Line Operated Audio Amplifier .....	AN72-38
96	A Dual Channel IC Driver for Class A Car Radios .....	AN72-38
97	Temperature Sensing .....	AN72-38
98	A "Programmable Unijunction" .....	AN72-39
99	Adding a Differential Input Stage .....	AN72-39

## THE LM3900—A NEW CURRENT-DIFFERENCING QUAD OF $\pm$ INPUT AMPLIFIERS

### 1.0 AN INTRODUCTION TO THE NEW "NORTON" AMPLIFIER

The LM3900 represents a departure from conventional amplifier designs. Instead of using a standard transistor differential amplifier at the input, the non-inverting input function has been achieved by making use of a "current-mirror" to "mirror" the non-inverting input current about ground and then to extract this current from that which is entering the inverting input terminal. Whereas the conventional op amp differences input voltages, this amplifier differences input currents and therefore the name "Norton Amp" has been used to indicate this new type of operation. Many biasing advantages are realized when operating with only a single power supply voltage. The fact that currents can be passed between the input terminals allows some unusual applications. If external, large valued input resistors are used (to convert from input voltages to input currents) most of the standard op amp applications can be realized.

Many industrial electronic control systems are designed that operate off of only a single power supply voltage. The conventional integrated-circuit operational amplifier (IC op amp) is typically designed for split power supplies ( $\pm 15 V_{DC}$ ) and suffers from a poor output voltage swing and a rather large minimum common-mode input voltage range (approximately  $+2 V_{DC}$ ) when used in a single power supply application. In addition, some of the performance characteristics of these op amps could be sacrificed—especially in favor of reduced costs.

To meet the needs of the designers of low-cost, single-power-supply control systems, a new internally compensated amplifier has been designed that operates over a power supply voltage range of  $+4 V_{DC}$  to  $36 V_{DC}$  with small changes in performance characteristics and provides an output peak-to-peak voltage swing that is only 1V less than the magnitude of the power supply voltage. Four of these amplifiers have been fabricated on a single chip and are provided in the standard 14-pin dual-in-line package.

The cost, application and performance advantages of this new quad amplifier will guarantee it a place in many single power supply electronic systems. Many of the "housekeeping" applications which are now handled by standard IC op amps can also be handled by this "Norton" amplifier operating off the existing  $\pm 15 V_{DC}$  power supplies.

### 1.1 Basic Gain Stage

The gain stage is basically a single common-emitter amplifier. By making use of current source loads, a large voltage gain has been achieved which is very constant over temperature changes. The output voltage has a large dynamic range, from essentially ground to one  $V_{BE}$  less than the power supply voltage. The output stage is biased class A for small signals but converts to class B to increase the load current which can be "absorbed" by the amplifier under large signal conditions. Power supply current drain is essentially independent of the power supply voltage and ripple on the supply line is also rejected. A very small input biasing current allows high impedance feedback elements to be used and even lower "effective" input biasing currents can be realized by using one of the amplifiers to supply essentially all of the bias currents for the other amplifiers by making use of the "matching" which exists between the 4 amplifiers which are on the same IC chip (see Figure 84).

The simplest inverting amplifier is the common-emitter stage. If a current source is used in place of a load resistor, a large open-loop gain can be obtained, even at low power-supply voltages. This basic stage (Figure 1) is used for the amplifier.

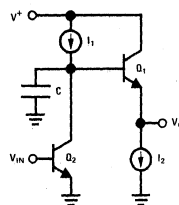


FIGURE 1. Basic Gain Stage

All of the voltage gain is provided by the gain transistor,  $Q_2$ , and an output emitter-follower transistor,  $Q_1$ , serves to isolate the load impedance from the high impedance that exists at the collector of the gain transistor,  $Q_2$ . Closed-loop stability is guaranteed by an on-chip capacitor  $C=3$  pF, which provides the single dominant open-loop pole. The output emitter-follower is biased for class-A operation by the current source  $I_2$ .

This basic stage can provide an adequate open-loop voltage gain (70 dB) and has the desired

large output voltage swing capability. A disadvantage of this circuit is that the DC input current,  $I_{IN}$ , is large; as it is essentially equal to the maximum output current,  $I_{OUT}$ , divided by  $\beta^2$ . For example, for an output current capability of 10 mA the input current would be at least 1  $\mu$ A (assuming  $\beta^2 = 10^4$ ). It would be desirable to further reduce this by adding an additional transistor to achieve an overall  $\beta^3$  reduction. Unfortunately, if a transistor is added at the output (by making  $Q_1$  a Darlington pair) the peak-to-peak output voltage swing would be somewhat reduced and if  $Q_2$  were made a Darlington pair the DC input voltage level would be undesirably doubled.

To overcome these problems, a lateral PNP transistor has been added as shown in Figure 2. This connection neither reduces the output voltage swing nor raises the DC input voltage, but does provide the additional gain that was needed to reduce the input current.

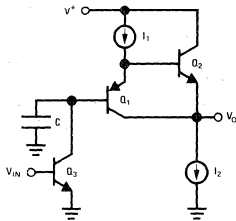


FIGURE 2. Adding a PNP Transistor to the Basic Gain Stage

Notice that the collector of this PNP transistor,  $Q_1$ , is connected directly to the output terminal. This "bootstraps" the output impedance of  $Q_1$  and therefore reduces the loading at the high-impedance collector of the gain transistor,  $Q_3$ .

In addition, the collector-base junction of the PNP transistor becomes forward biased under a large-signal negative output voltage swing condition. The design of this device has allowed  $Q_1$  to convert to a vertical PNP transistor during this operating mode which causes the output to change from the class A bias to a class B output stage. This allows the amplifier to sink more current than that provided by the current source,  $I_2$ , (1.3 mA) under large signal conditions.

### 1.2 Obtaining a Non-inverting Input Function

The circuit of Figure 2 has only the inverting input. A general purpose amplifier requires two input terminals to obtain both an inverting and a non-inverting input. In conventional op amp designs, an input differential amplifier provides these required inputs. The output

voltage then depends upon the difference (or error) between the two input voltages. An input common-mode voltage range specification exists and, basically, input voltages are compared.

For circuit simplicity, and ease of application in single power supply systems, a non-inverting input can be provided by adding a standard IC "current-mirror" circuit directly across the inverting input terminal, as shown in Figure 3.

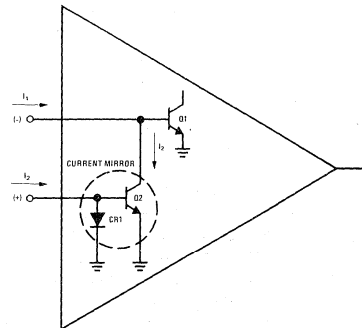



FIGURE 3. Adding a Current Mirror to Achieve a Non-inverting Input

This operates in the current mode as now input currents are compared or differenced (this can be thought of as a Norton differential amplifier). There is essentially no input common-mode voltage range directly at the input terminals (as both inputs will bias at one diode drop above ground) but if the input voltages are converted to currents (by use of input resistors), there is then no limit to the common-mode input voltage range. This is especially useful in high-voltage comparator applications. By making use of the input resistors, to convert input voltages to input currents, all of the standard op amp applications can be realized. Many additional applications are easily achieved, especially when operating with only a single power supply voltage. This results from the built-in voltage biasing that exists at both inputs (each input biases at  $+V_{BE}$ ) and additional resistors are not required to provide a suitable common-mode input DC biasing voltage level. Further, input summing can be performed at the relatively low impedance level of the input diode of the current-mirror circuit.

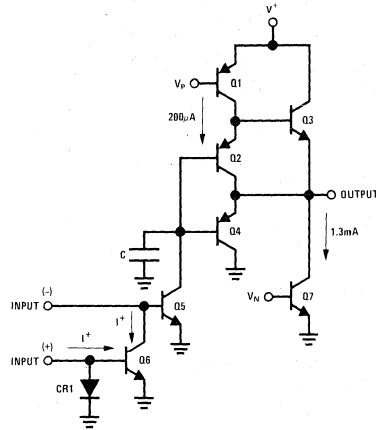
### 1.3 The Complete Single-supply Amplifier

The circuit schematic for a single amplifier stage is shown in Figure 4a). Due to the circuit simplicity, four of these amplifiers can be fabricated on a single chip. One common biasing circuit is used for all of the individual amplifiers.

A new symbol for this "Norton" amplifier is shown in Figure 4b). This is recommended to avoid using the standard op amp symbol as the basic operation is different. The current source symbol between the inputs implies this new current-mode of operation. In addition, it



(a) Circuit Schematic

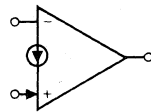

(b) New "NORTON" Amplifier Symbol

FIGURE 4. The Amplifier Stage

signifies that current is removed from the (-) input terminal. Also, the current arrow on the (+) input lead is used to indicate that this functions as a current input. The use of this symbol is helpful in understanding the operation of the application circuits and also in doing additional design work with the LM3900.

The bias reference for the PNP current source,  $V_p$  which biases  $Q_1$ , is designed to cause the upper current source ( $200 \mu\text{A}$ ) to change with temperature to give first order compensation for the  $\beta$  variations of the NPN output transistor,  $Q_3$ . The bias reference for the NPN "pull-down" current sink,  $V_n$ , (which biases  $Q_7$ ) is designed to stabilize this current ( $1.3 \text{ mA}$ ) to reduce the variation when the temperature is changed. This provides a more constant pull-down capability for the amplifier over the temperature range. The transistor,  $Q_4$ , provides the class B action which exists under large signal operating conditions.

The performance characteristics of each amplifier stage are summarized below:

Power-supply voltage range	4 to $36 V_{DC}$ or $\pm 2$ to $\pm 18 V_{DC}$
Bias current drain per amplifier stage	1.3 mA <sub>DC</sub>
Open loop:	
Voltage gain ( $R_L = 10k$ )	70 dB
Unity-gain frequency	2.5 MHz
Phase margin	40 degrees
Input resistance	1 M $\Omega$
Output resistance	8 k $\Omega$
Output voltage swing	$(V_{CC} - 1) V_{PP}$
Input bias current	30 nA <sub>DC</sub>
Slew rate	0.5V/ $\mu\text{s}$

As the bias currents are all derived from diode forward voltage drops, there is only a small change in bias current magnitude as the power-supply voltage is varied. The open-loop gain changes only slightly over the complete power supply voltage range and is essentially independent of temperature changes. The open-loop frequency response is compared with the "741" op amp in Figure 5. The higher unity-gain crossover frequency is seen to provide an additional 10 dB of gain for all frequencies greater than 1 kHz.

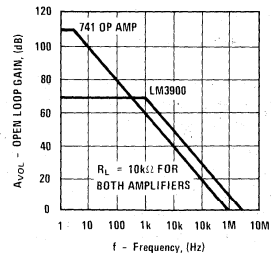


FIGURE 5. Open-loop Gain Characteristics

The complete schematic diagram of the LM3900 is shown in Figure 6. The one resistor,  $R_5$ , establishes the power consumption of the circuit as it controls the conduction of transistor  $Q_{28}$ . The emitter current of  $Q_{28}$  is used to bias the NPN output class-A biasing current sources and the collector current of  $Q_{28}$  is the reference for the PNP current source of each amplifier.

The biasing circuit is initially "started" by  $Q_{20}$ ,  $Q_{30}$  and  $CR_6$ . After start-up is achieved,  $Q_{30}$  goes OFF and the current flow through the reference diodes:  $CR_5$ ,  $CR_7$  and  $CR_8$ , is dependent only on  $V_{BE}/(R_6 + R_7)$ . This guarantees that the power supply current drain is essentially independent of the magnitude of the power supply voltage.

The input clamp for negative voltages is provided by the multi-emitter NPN transistor  $Q_{21}$ .

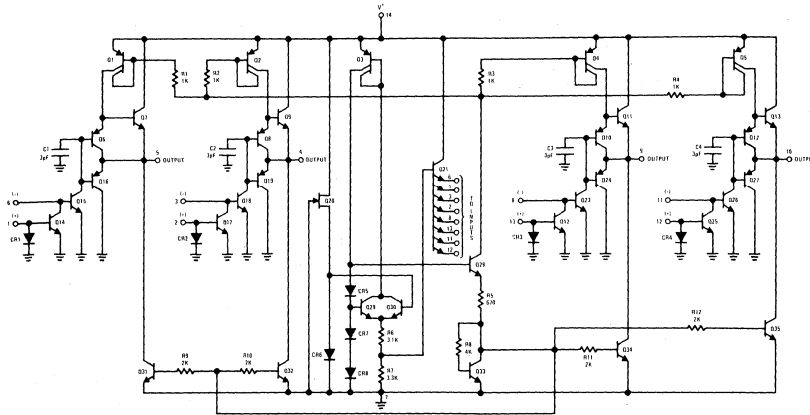


FIGURE 6. Schematic Diagram of the LM3900

One of the emitters of this transistor goes to each of the input terminals. The reference voltage for the base of  $Q_{21}$  is provided by  $R_6$  and  $R_7$  and is approximately  $V_{BE} / 2$ .

## 2.0 INTRODUCTION TO APPLICATIONS OF THE LM3900

Like the standard IC op amp, the LM3900 has a wide range of applications. A new approach must be taken to design circuits with this "Norton" amplifier and the object of this note is to present a variety of useful circuits to indicate how conventional and unique new applications can be designed—especially when operating with only a single power supply voltage.

To understand the operation of the LM3900 we will compare it with the more familiar standard IC op amp. When operating on a single power supply voltage, the minimum input common-mode voltage range of a standard op amp limits the smallest value of voltage which can be applied to both inputs and still have the amplifier respond to a differential input signal. In addition, the output voltage will not swing completely from ground to the power supply voltage. The output voltage depends upon the difference between the input voltages and a bias current must be supplied to both inputs. A simplified diagram of a standard IC op amp operating from a single power supply is shown in Figure 7. The (+) and (-) inputs go only to current sources and therefore are free to be biased or operated at any voltage values which are within the input common-mode voltage range. The current sources at the input terminals,  $I_{B^+}$  and  $I_{B^-}$ , represent the bias currents which must be supplied to both of the input transistors of the

op amp (base currents). The output circuit is modeled as an active voltage source which depends upon the open-loop gain of the amplifier,  $A_v$ , and the difference which exists between the input voltages,  $(V^+ - V^-)$ .

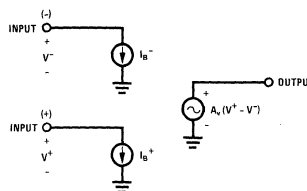


FIGURE 7. An Equivalent Circuit of a Standard IC Op Amp

An equivalent circuit for the "Norton" amplifier is shown in Figure 8. The (+) and (-) inputs are both clamped by diodes to force them to be one-diode drop above ground—always! They are not free to move and the "input common-mode voltage range" directly at these input terminals is very small—a few hundred mV centered about  $0.5 V_{DC}$ . This is

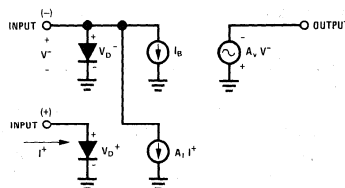


FIGURE 8. An Equivalent Circuit of the "Norton" Amplifier

why external voltages must be first converted to currents (using resistors) before being applied to the inputs—and is the basis for the

current-mode (or Norton) type of operation. With external input resistors—there is *no limit* to the "input common-mode voltage range". The diode shown across the (+) input actually exists as a diode in the circuit and the diode across the (-) input is used to model the base-emitter junction of the transistor which exists at this input.

Only the (-) input must be supplied with a DC biasing current,  $I_B$ . The (+) input couples only to the (-) input and then to extract from this (-) input terminal the same current ( $A_1$ , the mirror gain, is approximately equal to 1) which is entered (by the external circuitry) into the (+) input terminal. This operation is described as a "current-mirror" as the current entering the (+) input is "mirrored" or "reflected" about ground and is then extracted from the (-) input. There is a maximum or near saturation value of current which the "mirror" at the (+) input can handle. This is listed on the data sheet as "maximum mirror current" and ranges from approximately 6 mA at 25°C to 3.8 mA at 70°C.

This fact that the (+) input current modulates or effects the (-) input current causes this amplifier to pass currents between the input terminals and is the basis for many new application circuits—especially when operating with only a single power supply voltage.

The output is modeled as an active voltage source which also depends upon the open-loop voltage gain,  $A_v$ , but only the (-) input voltage,  $V^-$ , (not the differential input voltage). Finally, the output voltage of the LM3900 can swing from essentially ground (+90 mV) to within one  $V_{BE}$  of the power supply voltage.

As an example of the use of the equivalent circuit of the LM3900, the AC coupled inverting amplifier of Figure 9a will be analyzed. Figure 9b shows the complete equivalent circuit which, for convenience, can be separated into a biasing equivalent circuit (Figure 10) and an AC equivalent circuit (Figure 11). From the biasing model of Figure 10 we find the output quiescent voltage,  $V_O$ , is:

$$V_O = V_D^- + (I_B + I^+) R_2 \quad (1)$$

and

$$I^+ = \frac{V^+ - V_D^+}{R_3} \quad (2)$$

where

$$V_D^+ \cong V_D^- \cong 0.5 V_{DC}$$

$$I_B = \text{INPUT bias current (30 nA)}$$


and

$$V^+ = \text{Power supply voltage.}$$


If (2) is substituted into (1)

$$V_O = V_D^- + \left( I_B + \frac{V^+ - V_D^+}{R_3} \right) R_2 \quad (3)$$

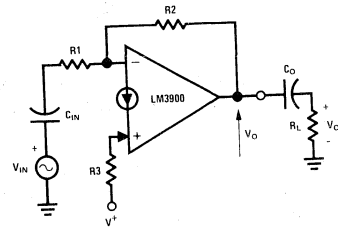which is an exact expression for  $V_O$ .



(a) A Typical Biased Amplifier

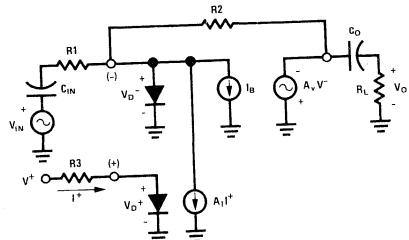

(b) Using the LM3900 Equivalent Circuit

FIGURE 9. Applying the LM3900 Equivalent Circuit

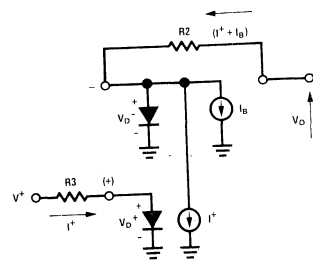


FIGURE 10. Biasing Equivalent Circuit

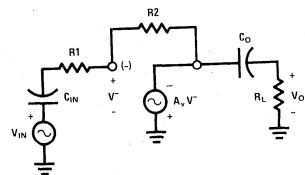


FIGURE 11. AC Equivalent Circuit

As the second term usually dominates ( $V_O \gg V_D^-$ ) and  $I^+ \gg I_B$  and  $V^+ \gg V_D^+$  we can simplify (3) to provide a more useful design relationship

$$V_O \cong \frac{R_2}{R_3} V^+ \quad (4)$$

Using (4), if  $R_3 = 2R_2$  we find

$$V_O \cong \frac{R_2}{2R_2} V^+ = \frac{V^+}{2} \quad (5)$$

which shows that the output is easily biased to one-half of the power supply voltage by using  $V^+$  as a biasing reference at the (+) input.

The AC equivalent circuit of Figure 11 is the same as that which would result if a standard IC op amp were used with the (+) input grounded. The closed-loop voltage gain  $A_{vCL}$  is given by:

$$A_{vCL} \cong \frac{V_O}{V_{IN}} \cong - \frac{R_2}{R_1} \quad (6)$$

If  $A_v$  (open-loop)  $\gg \frac{R_2}{R_1}$ .

The design procedure for an AC coupled inverting amplifier using the LM3900 is therefore to first select  $R_1$ ,  $C_{IN}$ ,  $R_2$ , and  $C_O$  as with a standard IC op amp and then to simply add  $R_3 = 2R_2$  as a final biasing consideration. Other biasing techniques are presented in the following sections of this note. For the switching circuit applications, the biasing model of Figure 10 is adequate to predict circuit operation.

Although the LM3900 has four independent amplifiers, the use of the label "¼LM3900" will be shortened to simply "LM3900" for the application drawings contained in this note.

### 3.0 DESIGNING AC AMPLIFIERS

The LM3900 readily lends itself to use as an AC amplifier because the output can be biased to any desired DC level within the range of the output voltage swing and the AC gain is independent of the biasing network. In addition, the single power supply requirement makes the LM3900 attractive for any low frequency gain application. For lowest noise performance, the (+) input should be grounded (Figure 9a) and the output will then bias at  $+V_{BE}$ . Although the LM3900 is not suitable as an ultra low noise tape pre-amp, it is useful in most other applications. The restriction to only shunt feedback causes a small input impedance. Transducers which can be loaded can operate with this low input impedance. The noise degradation which would result from the use of a large input resistor limits the usefulness where low noise and high input impedance are both required.

### 3.1 Single Power Supply Biasing

The LM3900 can be biased in several different ways. The circuit in Figure 12 is a standard inverting AC amplifier which has been biased

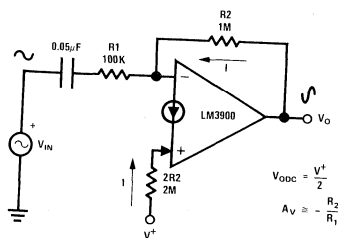


FIGURE 12. Inverting AC Amplifier Using Single-supply Biasing

from the same power supply which is used to operate the amplifier. (The design of this amplifier has been presented in the previous section.) Notice that if AC ripple voltages are present on the  $V^+$  power supply line they will couple to the output with a "gain" of 1/2. To eliminate this, one source of ripple filtered voltage can be provided and then used for many amplifiers. This is shown in the next section.

### 3.2 A Non-inverting Amplifier

The amplifier in Figure 13 shows both a non-inverting AC amplifier and a second method for DC biasing. Once again the AC gain of the amplifier is set by the ratio of feedback resistor to input resistor. The small signal impedance of the diode at the (+) input should be added to the value of  $R_1$  when calculating gain, as shown in Figure 13.

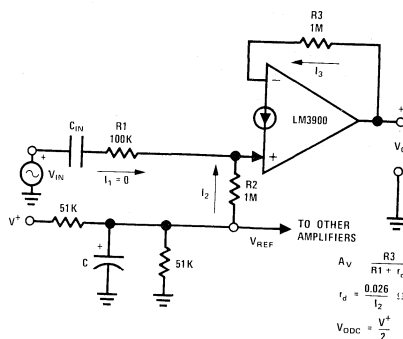


FIGURE 13. Non-inverting AC Amplifier Using Voltage Reference Biasing

By making  $R_2 = R_3$ ,  $V_{O_{DC}}$  will be equal to the reference voltage which is applied to the resistor  $R_2$ . The filtered  $V^+/2$  reference shown can also be used for other amplifiers.



### 3.3 "N V<sub>BE</sub>" Biasing

A third technique of output DC biasing is best described as the "N V<sub>BE</sub>" method. This technique is shown in Figure 14 and is most useful with inverting AC amplifier applications. The

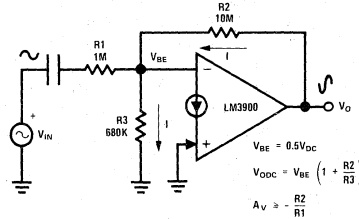


FIGURE 14. Inverting AC Amplifier Using N V<sub>BE</sub> Biasing

input bias voltage (V<sub>BE</sub>) at the inverting input establishes a current through resistor R<sub>3</sub> to ground. This current must come from the output of the amplifier. Therefore, V<sub>O</sub> must rise to a level which will cause this current to flow through R<sub>2</sub>. The bias voltage, V<sub>O</sub>, may be calculated from the ratio of R<sub>2</sub> to R<sub>3</sub> as follows:

$$V_{ODC} = V_{BE} \left( 1 + \frac{R_2}{R_3} \right)$$

When NV<sub>BE</sub> biasing is employed, values for resistors R<sub>1</sub> and R<sub>2</sub> are first established and then resistor R<sub>3</sub> is added to provide the desired DC output voltage.

For a design example (Figure 14), a Z<sub>in</sub> = 1M and A<sub>v</sub> ≈ 10 are required.

Select R<sub>1</sub> = 1M.

Calculate R<sub>2</sub> ≈ A<sub>v</sub>R<sub>1</sub> = 10M.

To bias the output voltage at 7.5 V<sub>DC</sub>, R<sub>3</sub> is found as:

$$R_3 = \frac{R_2}{\frac{V_O}{V_{BE}} - 1} = \frac{10M}{\frac{7.5}{0.5} - 1}$$

or

$$R_3 \cong 680 \text{ k}\Omega$$

### 3.4 Biasing Using a Negative Supply

If a negative power supply is available, the circuit of Figure 15 can be used. The DC biasing current, I<sub>1</sub>, is established by the negative supply voltage via R<sub>3</sub> and provides a very stable output quiescent point for the amplifier.

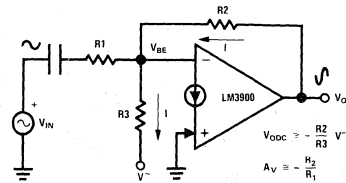


FIGURE 15. Negative Supply Biasing

### 3.5 Obtaining High Input Impedance and High Gain

For the AC amplifiers which have been presented, a designer is able to obtain either high gain or high input impedance with very little difficulty. The application which requires both and still employs only one amplifier presents a new problem. This can be achieved by the use of a circuit similar to the one shown in Figure 16. When the A<sub>v</sub> from the input to point A

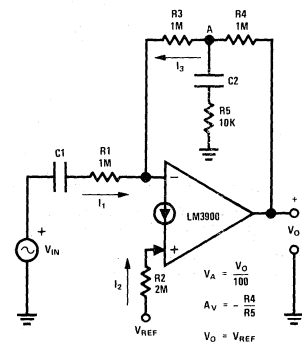


FIGURE 16. A High Z<sub>IN</sub> High Gain Inverting AC Amplifier

is unity (R<sub>1</sub> = R<sub>3</sub>), the A<sub>v</sub> of the complete stage will be set by the voltage divider network composed of R<sub>4</sub>, R<sub>5</sub>, and C<sub>2</sub>. As the value of R<sub>5</sub> is decreased, the A<sub>v</sub> of the stage will approach the AC open loop limit of the amplifier. The insertion of capacitor C<sub>2</sub> allows the DC bias to be controlled by the series combination of R<sub>3</sub> and R<sub>4</sub> with no effect from R<sub>5</sub>. Therefore, R<sub>2</sub> may be selected to obtain the desired output DC biasing level using any of the methods which have been discussed. The circuit in Figure 16 has an input impedance of 1M and a gain of 100.

### 3.6 An Amplifier with a DC Gain Control

A DC gain control can be added to an amplifier as shown in Figure 17. The output of the amplifier is kept from being driven to saturation as the DC gain control is varied by providing a minimum biasing current via R<sub>3</sub>. For

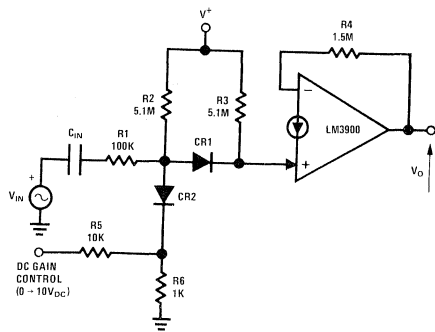


FIGURE 17. An Amplifier with a DC Gain Control

maximum gain, CR<sub>2</sub> is OFF and both the current through R<sub>2</sub> and R<sub>3</sub> enter the (+) input and cause the output of the amplifier to bias at approximately 0.6 V<sup>+</sup>. For minimum gain, CR<sub>2</sub> is ON and only the current through R<sub>3</sub> enters the (+) input to bias the output at approximately 0.3 V<sup>+</sup>. The proper output bias for large output signal accommodation is provided for the maximum gain situation. The DC gain control input ranges from 0V<sub>DC</sub> for minimum gain to less than 10V<sub>DC</sub> for maximum gain.

### 3.7 A Line-receiver Amplifier

A line-receiver amplifier is shown in Figure 18. The use of both inputs cancels out common-mode signals. The line is terminated by R<sub>LINE</sub> and the larger input impedance of the amplifier will not effect this matched loading.

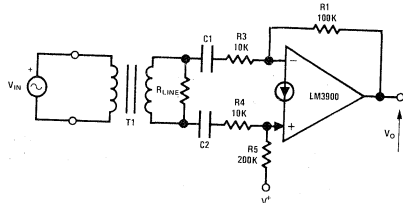


FIGURE 18. A Line-receiver Amplifier

## 4.0 DESIGNING DC AMPLIFIERS

The design of DC amplifiers using the LM3900 tends to be more difficult than the design of AC amplifiers. These difficulties occur when designing a DC amplifier which will operate from only a single power supply voltage and yet provide an output voltage which goes to zero volts DC and also will accept input voltages of zero volts DC. To accomplish this, the inputs must be biased into the linear region (+V<sub>BE</sub>) with DC input signals of zero volts and the output must be modified if operation to actual ground (and not V<sub>SAT</sub>) is required. Therefore,

the problem becomes one of determining what type of network is necessary to provide an output voltage (V<sub>O</sub>) equal to zero when the input voltage (V<sub>IN</sub>) is equal to zero. (See also section 10.16, "adding a Differential Input Stage").

We will start with a careful evaluation of what actually takes place at the amplifier inputs. The mirror circuit demands that the current flowing into the positive input (+) be equaled by a current flowing into the negative input (-). The difference between the current demanded and the current provided by an external source must flow in the feedback circuit. The output voltage is then forced to seek the level required to cause this amount of current to flow. If, in the steady state condition V<sub>O</sub> = V<sub>IN</sub> = 0, the amplifier will operate in the desired manner. This condition can be established by the use of common-mode biasing at the inputs.

### 4.1 Using Common-mode Biasing for V<sub>IN</sub> = 0 V<sub>DC</sub>

Common-mode biasing is achieved by placing equal resistors between the amplifier input terminals and the supply voltage (V<sup>+</sup>), as shown in Figure 19. When V<sub>IN</sub> is set to 0 volts

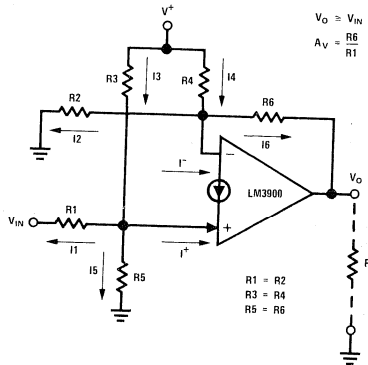


FIGURE 19. A DC Amplifier Employing Common-mode Biasing

the circuit can be modeled as shown in Figure 20, where:

$$R_{EQ1} = R_1 \parallel R_5$$

$$R_{EQ2} = R_2 \parallel R_6$$

and

$$R_3 = R_4$$

Because the current mirror demands that the two current sources be equal, the current in the two equivalent resistors must be identical.

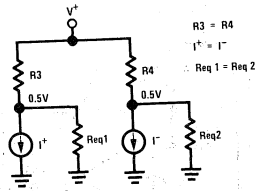


FIGURE 20. An Ideal Circuit Model of a DC Amplifier with Zero Input Voltage

If this is true, both  $R_2$  and  $R_6$  must have a voltage drop of 0.5 volt across them, which forces  $V_O$  to go to  $V_{O\text{ MIN}}$  ( $V_{SAT}$ ).

#### 4.2 Adding an Output Diode for $V_O = 0\text{ V}_{DC}$

For many applications a  $V_{O\text{ MIN}}$  of 100 mV may not be acceptable. To overcome this problem a diode can be added between the output of the amplifier and the output terminal (Figure 21).

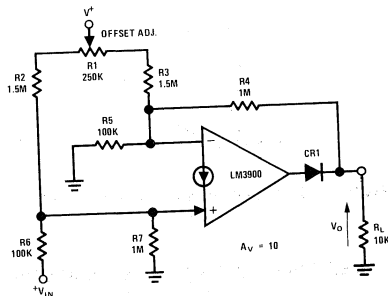


FIGURE 21. A Non-inverting DC Amplifier with Zero Volts Output for Zero Volts Input

The function of the diode is to provide a DC level shift which will allow  $V_O$  to go to ground. With a load impedance ( $R_L$ ) connected,  $V_O$  becomes a function of the voltage divider formed by the series connection of  $R_4$  and  $R_L$ .

$$\text{If } R_4 = 100 R_L, \text{ then } V_{O\text{ MIN}} = \frac{0.5 R_L}{101 R_1}$$

$$\text{or } V_{O\text{ MIN}} \cong 5\text{ mV}_{DC}$$

An offset voltage adjustment can be added as shown ( $R_1$ ) to adjust  $V_O$  to  $0\text{ V}_{DC}$  with  $V_{IN} = 0\text{ V}_{DC}$ .

The voltage transfer functions for the circuit in Figure 21, both with and without the diode, are shown in Figure 22. While the diode greatly improves the operation around 0 volts, the voltage drop across the diode will reduce the peak output voltage swing of the stage by approximately 0.5 volt.

When using a DC amplifier similar to the one in Figure 21, the load impedance should be large

enough to avoid excessively loading the amplifier. The value of  $R_L$  may be significantly reduced by replacing the diode with an NPN transistor.

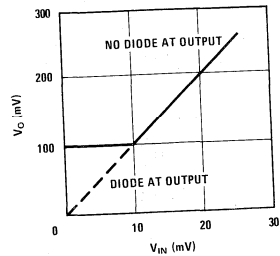


FIGURE 22. Voltage Transfer Function for a DC Amplifier with a Voltage Gain of 10

#### 4.3 A DC Coupled Power Amplifier ( $I_L \leq 3\text{ Amps}$ )

The LM3900 may be used as a power amplifier by the addition of a Darlington pair at the output. The circuit shown in Figure 23 can deliver in excess of 3 amps to the load when the transistors are properly mounted on heat sinks.

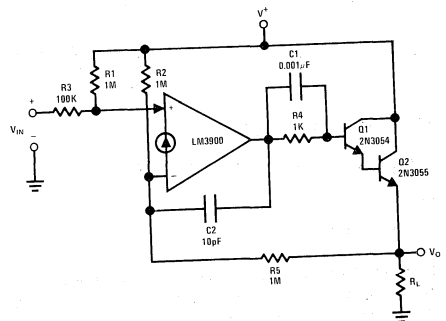


FIGURE 23. A DC Power Amplifier

#### 4.4 Ground Referencing a Differential Voltage

The circuit in Figure 24 employs the LM3900 to ground reference a DC differential input voltage. Current  $I_1$  is larger than current  $I_3$  by a

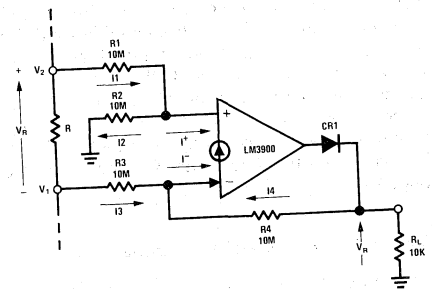


FIGURE 24. Ground Referencing a Differential Input DC Voltage

factor proportional to the differential voltage,  $V_R$ . The currents labeled on Figure 24 are given by:

$$I_1 = \frac{V_1 + V_R - \phi}{R_1}$$

$$I_2 = \phi/R_2$$

$$I_3 = \frac{(V_1 - \phi)}{R_3}$$

and

$$I_4 = \frac{V_O - \phi}{R_4}$$

where

$\phi \equiv V_{BE}$  at either input terminal of the LM3900.

Since the input current mirror demands that

$$I^- = I^+;$$

and

$$I^+ = I_1 - I_2$$

and

$$I^- = I_3 + I_4$$

Therefore

$$I_4 = I_1 - I_2 - I_3.$$

Substituting in from the above equation

$$\frac{V_O - \phi}{R_4} = \frac{(V_1 + V_R - \phi)}{R_1} - \frac{(\phi)}{R_2} - \frac{(V_1 - \phi)}{R_3}$$

and as  $R_1 = R_2 = R_3 = R_4$

$$V_O = (V_1 + V_R - \phi) - (\phi) - V_1 + \phi + \phi$$

or

$$V_O = V_R.$$

The resistors are kept large to minimize loading. With the 10 M $\Omega$  resistors which are shown on the figure, an error exists at small values of  $V_1$  due to the input bias current at the (-) input. For simplicity this has been neglected in the circuit description. Smaller R values reduce the percentage error or the bias current can be supplied by an additional amplifier (see Section 10.7.1).

For proper operation, the differential input voltage must be limited to be within the output dynamic voltage range of the amplifier and the input voltage  $V_2$  must be greater than 1 volt. For example; if  $V_2 = 1$  volt, the input voltage  $V_1$  may vary over the range of 1 volt to -13 volts when operating from a 15 volt supply. Common-mode biasing may be added as shown in Figure 25 to allow both  $V_1$  and  $V_2$  to be negative.

#### 4.5 A Unity Gain Buffer Amplifier

The buffer amplifier with a gain of one is the simplest DC application for the LM3900. The voltage applied to the input (Figure 26) will be reproduced at the output. However, the input

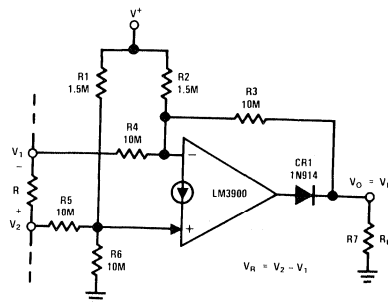


FIGURE 25. A Network to Invert and to Ground Reference a Negative DC Differential Input Voltage

voltage must be greater than one  $V_{BE}$  but less than the maximum output swing. Common-mode biasing can be added to extend  $V_{IN}$  to 0  $V_{DC}$ , if desired.

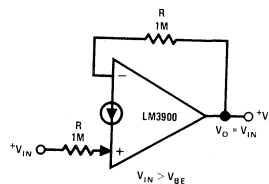


FIGURE 26. A Unity-gain DC Buffer Amplifier

## 5.0 DESIGNING VOLTAGE REGULATORS

Many voltage regulators can be designed which make use of the basic amplifier of the LM3900. The simplest is shown in Figure 27a where only a Zener diode and a resistor are added. The voltage at the (-) input (one  $V_{BE} \cong 0.5 V_{DC}$ ) appears across R and therefore a resistor value of 510 $\Omega$  will cause approximately 1 mA of bias current to be drawn through the Zener. This biasing is used to reduce the noise output of the Zener as the 30 nA input current is too small for proper Zener biasing. To compensate for a positive temperature coefficient of the Zener, an additional resistor can be added,  $R_2$ , (Figure 27b) to introduce an arbitrary number, N, of "effective"  $V_{BE}$  drops into the expression for the output voltage. The negative temperature coefficient of these diodes will also be added to temperature compensate the DC output voltage. For a larger output current, an emitter follower ( $Q_1$  of Figure 27c) can be added. This will multiply the 10 mA (max.) output current of the LM3900 by the  $\beta$  of the added transistor. For example, a  $\beta = 30$  will provide a max. load current of 300 mA. This added transistor also reduces the output impedance. An output frequency compensation capacitor is generally not required but may be added, if desired, to reduce the output impedance at high frequencies.

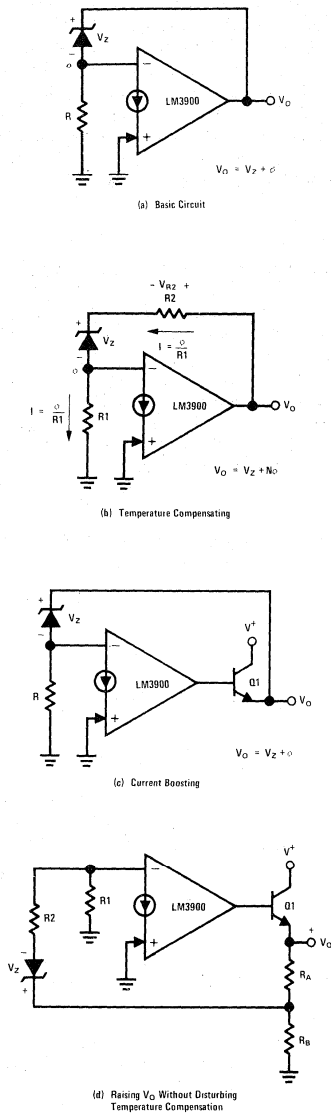


FIGURE 27. Simple Voltage Regulators

The DC output voltage can be increased and still preserve the temperature compensation of Figure 27b by adding resistors  $R_A$  and  $R_B$  as shown in Figure 27d. This also can be accomplished without the added transistor,  $Q_1$ . The unregulated input voltage, which is applied to pin 14 of the LM3900 (and to the collector of  $Q_1$ , if used) must always exceed the regulated DC output voltage by approximately 1V, when the unit is not current boosted or approximately 2V when the NPN current boosting transistor is added.

## 5.1 Reducing the Input-output Voltage

The use of an external PNP transistor will reduce the required  $(V_{IN} - V_{OUT})$  to a few tenths of a volt. This will depend on the saturation characteristics of the external transistor at the operating current level. The circuit, shown in Figure 28, uses the LM3900 to supply base drive to the PNP transistor. The resistors  $R_1$  and  $R_2$  are used to allow the output of the amplifier to turn OFF the PNP transistor. It is important that pin 14 of the LM3900 be tied to the  $+V_{IN}$  line to allow this OFF control to properly operate. Larger voltages are permissible (if the base-emitter junction of  $Q_1$  is prevented from entering a breakdown by a shunting diode, for example), but smaller voltages will not allow the output of the amplifier to raise enough to give the OFF control.

The resistor,  $R_3$ , is used to supply the required bias current for the amplifier and  $R_4$  is again used to bias the Zener diode. Due to a larger gain, a compensation capacitor,  $C_O$ , is required. Temperature compensation could be added as was shown in Figure 27b.

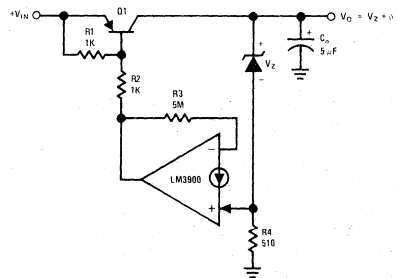


FIGURE 28. Reducing  $(V_{IN} - V_{OUT})$

## 5.2 Providing High Input Voltage Protection

One of the four amplifiers can be used to regulate the supply line for the complete package (pin 14), to provide protection against large input voltage conditions, and in addition, to supply current to an external load. This circuit is shown in Figure 29. The regulated output voltage is the sum of the Zener voltage,  $CR_2$ , and the  $V_{BE}$  of the inverting input terminal. Again, temperature compensation can be added as in Figure 27b. The second Zener,  $CR_1$ , is a low tolerance component which simply serves as a DC level shift to allow the output voltage of the amplifier to control the conduction of the external transistor,  $Q_1$ . This Zener voltage should be approximately one-half of the  $CR_2$  voltage to position the DC output voltage level of the amplifier approximately in the center of the dynamic range.

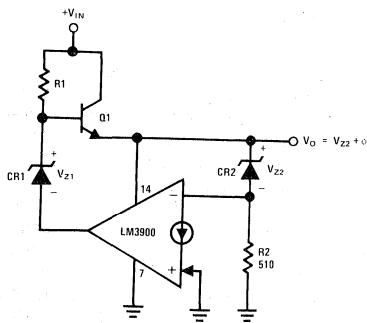


FIGURE 29. High  $V_{IN}$  Protection and Self-regulation

The base drive current for  $Q_1$  is supplied via  $R_1$ . The maximum current through  $R_1$  should be limited to 10 mA as

$$I_{MAX} = \frac{V_{IN (MAX)} - (V_O + V_{BE})}{R_1}$$

To increase the maximum allowed input voltage, reduce the output ripple, or to reduce the  $(V_{IN} - V_{OUT})$  requirements of this circuit, the connection described in the next section is recommended.

### 5.3 High Input Voltage Protection and Low $(V_{IN} - V_{OUT})$

The circuit shown in Figure 30 basically adds one additional transistor to the circuit of Figure 29 to improve the performance. In this circuit both transistors ( $Q_1$  and  $Q_2$ ) absorb any high input voltages (and therefore need to be high voltage devices) without any increases in current (as with  $R_1$  of Figure 29). The resistor  $R_1$  (of Figure 30) provides a "start-up" current into the base of  $Q_2$ .

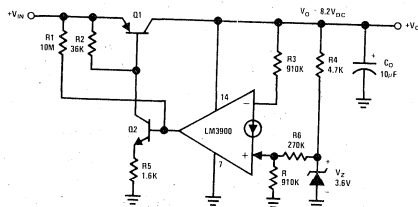


FIGURE 30. A High  $V_{IN}$  Protected, Low  $(V_{IN} - V_{OUT})$  Regulator

A new input connection is shown on this regulator (the type on Figure 29 could also be used) to control the DC output voltage. The Zener is biased via  $R_4$  (at approximately 1 mA). The

resistors  $R_3$  and  $R_6$  provide gain (non-inverting) to allow establishing  $V_O$  at any desired voltage larger than  $V_Z$ . Temperature compensation of either sign ( $\pm TC$ ) can be obtained by shunting a resistor from either the (+) input to ground (to add + TC to  $V_O$ ) or from the (-) input to ground (to add - TC to  $V_O$ ). To understand this, notice that the resistor,  $R$ , from the (+) input to ground will add  $-N V_{BE}$  to  $V_O$  where

$$N = 1 + \frac{R_3}{R}$$

and  $V_{BE}$  is the base emitter voltage of the transistor at the (+) input. This then also adds a positive temperature change at the output to provide the desired temperature correction.

The added transistor,  $Q_2$ , also increases the gain (which reduces the output impedance) and if a power device is used for  $Q_1$  large load currents (amps) can be supplied. This regulator also supplies the power to the other three amplifiers of the LM3900.

### 5.4 Reducing Input Voltage Dependence and Adding Short-circuit Protection

To reduce ripple feedthrough and input voltage dependence, diodes can be added as shown in Figure 31 to drop-out the start circuit once

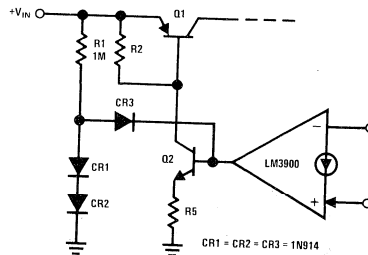


FIGURE 31. Reducing  $V_{IN}$  Dependence

start-up has been achieved. Short-circuit protection can also be added as shown in Figure 32.

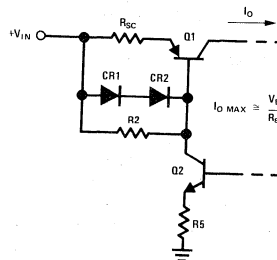


FIGURE 32. Adding Short-circuit Current Limiting

The emitter resistor of  $Q_2$  will limit the maximum current of  $Q_2$  to  $(V_O - 2 V_{BE})/R_5$ .

## 6.0 DESIGNING RC ACTIVE FILTERS

Recent work in RC active filters has shown that the performance characteristics of multiple-amplifier filters are relatively insensitive to the tolerance of the RC components used. This makes the performance of these filters easier to control in production runs. In many cases where gain is needed in a system design it is now relatively easy to also get frequency selectivity.

The basis of active filters is a gain stage and therefore a multiple amplifier product is a valuable addition to this application area. When additional amplifiers are available, less component selection and trimming is needed as the performance of the filter is less disturbed by the tolerance and temperature drifts of the passive components.

The *passive components* do control the *performance* of the filter and for this reason carbon composition resistors are useful mainly for room temperature breadboarding or for final trimming of the more stable metal film or wire-wound resistors. Capacitors present more of a problem in range of values available, tolerance and stability (with temperature, frequency, voltage and time). For example, the disk ceramic type of capacitors are generally not suited to active filter applications due to their relatively poor performance.

The impedance level of the passive components can be scaled without (theoretically) affecting the filter characteristics. In an actual circuit; if the resistor values become too small ( $\leq 10 \text{ k}\Omega$ ) an excessive loading may be placed on the output of the amplifier which will reduce gain or actually exceed either the output current or the package dissipation capabilities of the amplifier. This can easily be checked by calculating (or noticing) the impedance which is presented to the output terminal of the amplifier at the highest operating frequency. A second limit sets the upper range of impedance levels, this is due to the DC bias currents ( $\approx 30 \text{ nA}$ ) and the input impedance of actual amplifiers. The solution to this problem is to reduce the impedance levels of the passive components ( $\leq 10 \text{ M}\Omega$ ). In general, better performance is obtained with relatively low passive component impedance levels and in filters which do not demand high gain, high Q ( $Q \geq 50$ ) and high frequency ( $f_o > 1 \text{ kHz}$ ) simultaneously.

A measure of the effects of changes in the values of the passive components on the filter performance has been given by "sensitivity functions". These assume infinite amplifier gain and relate the percentage change in a parameter of the filter, such as center frequency ( $f_o$ ), Q, or gain to a percentage change in a particular passive component. Sensitivity functions which are small are desirable (as 1 or 1/2).

Negative signs simply mean an increase in the value of a passive component causes a decrease in that filter performance characteristic. As an example, if a bandpass filter listed the following sensitivity factor

$$S_{\omega_o}^{C_3} = -\frac{1}{2}$$

This states that "if  $C_3$  were to increase by 1%, the center frequency,  $\omega_o$ , would decrease by 0.5%." Sensitivity functions are tabulated in the reference listed at the end of this section and will therefore not be included here.

A brief look at low pass, high pass and band-pass filters will indicate how the LM3900 can be applied in these areas. A recommended text (which provided these circuits) is, "Operational Amplifiers", Tobey, Graeme, and Huelsman, McGraw Hill, 1971.

### 6.1 Biasing the Amplifiers

Active filters can be easily operated off of a single power supply when using these multiple single supply amplifiers. The general technique is to use the (+) input to accomplish the biasing function. The power supply voltage,  $V^+$ , is used as the DC reference to bias the output voltage of each amplifier at approximately  $V^+/2$ . As shown in Figure 33, undesired AC components on the power supply line may have to be removed (by a filter capacitor,

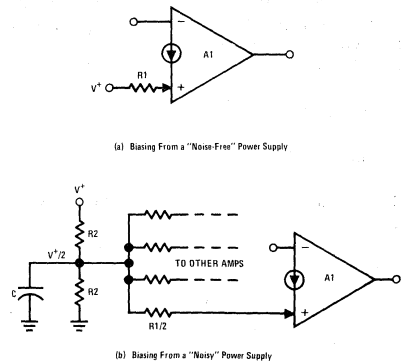


FIGURE 33. Biasing Considerations

Figure 31b) to keep the filter output free of this noise. One filtered DC reference can generally be used for all of the amplifiers as there is essentially no signal feedback to this bias point.

In the filter circuits presented here, all amplifiers will be biased at  $V^+/2$  to allow the maximum AC voltage swing for any given DC power supply voltage. The inputs to these filters will also be assumed at a DC level of  $V^+/2$  (for those which are direct coupled).

## 6.2 A High Pass Active Filter

A single amplifier high pass RC active filter is shown in Figure 34. This circuit is easily biased using the (+) input of the LM3900. The resistor,  $R_3$ , can be simply made equal to  $R_2$  and a bias reference of  $V^+/2$  will establish the output Q point at this value ( $V^+/2$ ). The input is capacitively coupled ( $C_1$ ) and there are therefore no further DC biasing problems.

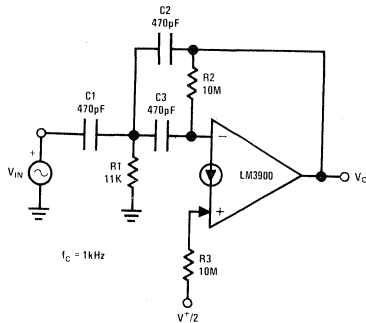


FIGURE 34. A High Pass Active Filter

The design procedure for this filter is to select the pass band gain,  $H_0$ , the Q and the corner frequency,  $f_c$ . A Q value of 1 gives only a slight peaking near the bandedge (<2 dB) and smaller Q values decrease this peaking. The slope of the skirt of this filter is 12 dB/octave (or 40 dB/decade). If the gain,  $H_0$ , is unity all capacitors have the same value. The design proceeds as:

Given:  $H_0$ , Q and  $\omega_c = 2\pi f_c$

To find:  $R_1$ ,  $R_2$ ,  $C_1$ ,  $C_2$ , and  $C_3$

let  $C_1 = C_3$  and choose a convenient starting value.

Then:

$$R_1 = \frac{1}{Q \omega_c C_1 (2H_0 + 1)} \quad (1)$$

$$R_2 = \frac{Q}{\omega_c C_1} (2H_0 + 1), \quad (2)$$

and

$$C_2 = \frac{C_1}{H_0} \quad (3)$$

As a design example,

Require:  $H_0 = 1$ ,

$Q = 10$ ,

and  $f_c = 1 \text{ kHz}$  ( $\omega_c = 6.28 \times 10^3 \text{ rps}$ ).

Start by selecting  $C_1 = 300 \text{ pF}$  and then from equation (1)

$$R_1 = \frac{1}{(10)(6.28 \times 10^3)(3 \times 10^{-10})} \quad (3)$$

$$R_1 = 17.7 \text{ k}\Omega$$

and from equation (2)

$$R_2 = \frac{10}{(6.28 \times 10^3)(3 \times 10^{-10})}$$

$$R_2 = 15.9 \text{ M}\Omega$$

and from equation (3)

$$C_2 = \frac{C_1}{1} = C_1$$

Now we see that the value of  $R_2$  is quite large; but the other components look acceptable. Here is where impedance scaling comes in. We can reduce  $R_2$  to the more convenient value of  $10 \text{ M}\Omega$  which is a factor of 1.59:1. Reducing  $R_1$  by this same scaling factor gives:

$$R_{1\text{NEW}} = \frac{17.7 \times 10^3}{1.59} = 11.1 \text{ k}\Omega$$

and the capacitors are similarly reduced in impedance as:

$$(C_1 = C_2 = C_3)_{\text{NEW}} = (1.59)(300) \text{ pF}$$

$$C_{1\text{NEW}} = 477 \text{ pF.}$$

To complete the design,  $R_3$  is made equal to  $R_2$  ( $10 \text{ M}\Omega$ ) and a  $V_{\text{REF}}$  of  $V^+/2$  is used to bias the output for large signal accommodation.

Capacitor values should be adjusted to use standard valued components by using impedance scaling as a wider range of standard resistor values is generally available.

## 6.3 A Low Pass Active Filter

A single amplifier low pass filter is shown in Figure 35. The resistor,  $R_4$ , is used to set the

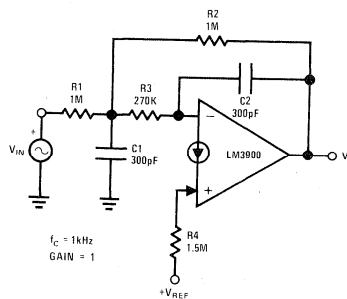


FIGURE 35. A Low Pass Active Filter

output bias level and is selected after the other resistors have been established.



The design procedure is as follows:

Given:  $H_O$ ,  $Q$ , and  $\omega_c = 2\pi f_c$

To find:  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$ ,  $C_1$ , and  $C_2$

Let  $C_1$  be a convenient value,

then

$$C_2 = K C_1 \quad (4)$$

where  $K$  is a constant which can be used to adjust component values. For example, with  $K = 1$ ,  $C_1 = C_2$ . Larger values of  $K$  can be used to reduce  $R_2$  and  $R_3$  at the expense of a larger value for  $C_2$ .

$$R_1 = \frac{R_2}{H_O} \quad (5)$$

$$R_2 = \frac{1}{2Q \omega_c C_1} \left[ 1 \pm \sqrt{1 + \frac{4Q^2 (H_O + 1)}{K}} \right] \quad (6)$$

and

$$R_3 = \frac{1}{\omega_c^2 C_1^2 R_2 (K)} \quad (7)$$

As a design example;

Require:  $H_O = 1$ ,

$Q = 1$ ,

and  $f_c = 1 \text{ kHz}$  ( $\omega_c = 6.28 \times 10^3 \text{ rps}$ ).

Start by selecting  $C_1 = 300 \text{ pF}$  and  $K = 1$  so  $C_2$  is also  $300 \text{ pF}$  (equation 4).

Now from equation (6)

$$R_2 = \frac{1}{2(1) (6.28 \times 10^3) (3 \times 10^{-10})} \left[ 1 \pm \sqrt{1 + 4(2)} \right]$$

$$R_2 = 1.06 \text{ M}\Omega$$

Then from equation (5)

$$R_1 = R_2 = 1.06 \text{ M}\Omega$$

and finally from equation (7)

$$R_3 = \frac{1}{(6.28 \times 10^3)^2 (3 \times 10^{-10})^2 (1.06 \times 10^6) (1)}$$

$$R_3 = 266 \text{ k}\Omega.$$

To select  $R_4$ , we assume the DC input level is  $7 \text{ V}_{DC}$  and the DC output of this filter is to also be  $7 \text{ V}_{DC}$ . This gives us the circuit of Figure 36. Notice that  $H_O = 1$  gives us not only

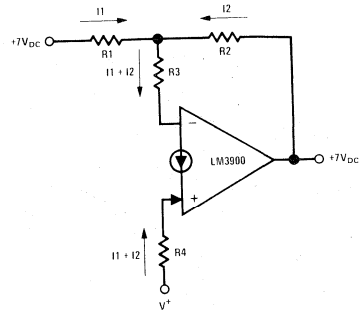


FIGURE 36. Biasing the Low Pass Filter

equal resistor values ( $R_1$  and  $R_2$ ) but simplifies the DC bias calculation as  $I_1 = I_2$  and we have a DC amplifier with a gain of  $-1$  (so if the DC input voltage increases  $1 \text{ V}_{DC}$  the output voltage decreases  $1 \text{ V}_{DC}$ ). The resistors  $R_1$  and  $R_2$  are in parallel so that the circuit simplifies to that shown in Figure 37 where the actual resistance values have been added. The resistor  $R_4$  is given by

$$R_4 = 2 \left( \frac{R_1}{2} + R_3 \right) + R_3$$

or, using values

$$R_4 = 2 \left( \frac{1\text{M}\Omega}{2} + 266 \text{ k} \right) \cong 1.5 \text{ M}\Omega$$

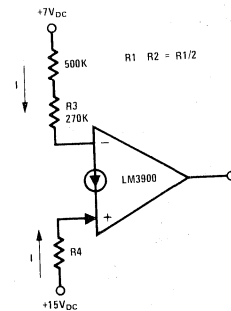


FIGURE 37. Biasing Equivalent Circuit

#### 6.4 A Single-amplifier Bandpass Active Filter

The bandpass filter is perhaps the most interesting. For low frequencies, low gain and low  $Q$  ( $\leq 10$ ) requirements, a single amplifier realization can be used. A one amplifier circuit is shown in Figure 38 and the design procedure is as follows:

Given:  $H_O$ ,  $Q$  and  $\omega_o = 2\pi f_o$ .

To find:  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$ ,  $C_1$  and  $C_2$ .

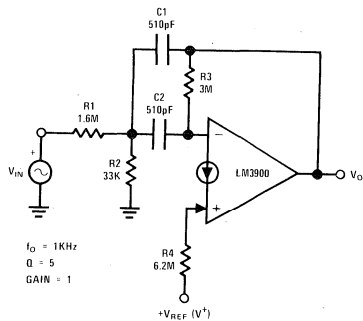


FIGURE 38. A One Op Amp Bandpass Filter

Let  $C_1 = C_2$  and select a convenient starting value.

Then

$$R_1 = \frac{Q}{H_0 \omega_0 C_1} \quad (8)$$

$$R_2 = \frac{Q}{(2Q^2 - H_0) \omega_0 C_1} \quad (9)$$

$$R_3 = \frac{2Q}{\omega_0 C_1} \quad (10)$$

and

$$R_4 = 2R_3 \text{ (for } V_{REF} = V^+) \quad (11)$$

As a design example;

Require:  $H_0 = 1$

$Q = 5$

$f_0 = 1 \text{ kHz } (\omega_0 = 6.28 \times 10^3 \text{ rps})$ .

Start by selecting

$$C_1 = C_2 = 510 \text{ pF.}$$

Then using equation (8)

$$R_1 = \frac{5}{(6.28 \times 10^3) (5.1 \times 10^{-10})}$$

$$R_1 = 1.57 \text{ M}\Omega,$$

and using equation (9)

$$R_2 = \frac{5}{[2(25) - 1] (6.28 \times 10^3) (5.1 \times 10^{-10})}$$

$$R_2 = 32 \text{ k}\Omega$$

from equation (10)

$$R_3 = \frac{2(5)}{(6.28 \times 10^3) (5.1 \times 10^{-10})}$$

$$R_3 = 3.13 \text{ M}\Omega,$$

and finally, for biasing, using equation (11)

$$R_4 = 6.2 \text{ M}\Omega.$$

## 6.5 A Two-amplifier Bandpass Active Filter

To allow higher  $Q$  (between 10 and 50) and higher gain, a two amplifier filter is required. This circuit, shown in Figure 39, uses only two capacitors. It is similar to the previous single amplifier bandpass circuit and the added amplifier supplies a controlled amount of positive feedback to improve the response characteristics. The resistors  $R_5$  and  $R_8$  are used to bias the output voltage of the amplifiers at  $V^+/2$ .

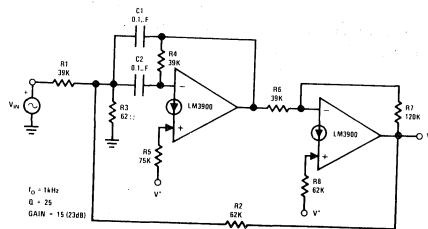


FIGURE 39. A Two Op Amp Bandpass Filter

Again,  $R_5$  is simply chosen as twice  $R_4$  and  $R_8$  must be selected after  $R_6$  and  $R_7$  have been assigned values. The design procedure is as follows:

Given:  $Q$  and  $f_0$

To find:  $R_1$  through  $R_7$ , and  $C_1$  and  $C_2$

Let:  $C_1 = C_2$  and choose a convenient starting value and choose a value for  $K$  to reduce the spread of element values or to optimize sensitivity ( $1 \leq K$ , Typically  $\leq 10$ ).

Then

$$R_1 = R_4 = R_6 = \frac{Q}{\omega_0 C_1} \quad (12)$$

$$R_2 = R_1 \frac{KQ}{(2Q - 1)} \quad (13)$$

$$R_3 = \frac{R_1}{Q^2 - 1 - 2/K + 1/KQ} \quad (14)$$

and

$$R_7 = KR_1 \quad (15)$$

$$H_0 = \sqrt{Q} K \quad (16)$$

As a design example:

Require:  $Q = 25$  and  $f_0 = 1 \text{ kHz}$ .

Select:  $C_1 = C_2 = 0.1 \mu\text{F}$

and  $K = 3$ .

Then from equation (12)

$$R_1 = R_4 = R_6 = \frac{25}{(2\pi \times 10^3)^2 (10^{-7})}$$

$$R_1 = 40 \text{ k}\Omega$$

and from equation (13)

$$R_2 = \frac{(40 \times 10^3)^2}{2(25) - 1} \cdot \frac{3(25)}{3(25)}$$

$$R_2 = 61 \text{ k}\Omega$$

and from equation (14)

$$R_3 = \frac{40 \times 10^3}{(25)^2 - 1 - 2/3 + \frac{1}{3(25)}}$$

$$R_3 = 64 \Omega$$

And  $R_7$  is given by equation (15)

$$R_7 = 3(40 \text{ k}\Omega) = 120 \text{ k}\Omega,$$

and the gain is obtained from equation (16)

$$H_0 = \sqrt{25} (3) = 15 (23 \text{ dB}).$$

To properly bias the first amplifier

$$R_5 = 2R_4 = 80 \text{ k}\Omega$$

and the second amplifier is biased by  $R_8$ . Notice that the outputs of both amplifiers will be at  $V^+/2$ . Therefore  $R_6$  and  $R_7$  can be paralleled and

$$R_8 = 2(R_6 \parallel R_7)$$

or

$$R_8 = 2 \left[ \frac{(40)(120 \times 10^3)}{160} \right] = 59 \text{ k}\Omega$$

These values, to the closest standard resistor values, have been added to Figure 39.

## 6.6 A Three-amplifier Bandpass Active Filter

To reduce  $Q$  sensitivity to element variation even further or to provide higher  $Q$  ( $Q > 50$ ) a three amplifier bandpass filter can be used. This circuit, Figure 40, pre-dates most of the literature on RC active filters and has been used on analog computers. Due to the use of three amplifiers it often is considered too costly—especially for low  $Q$  applications. The multiple amplifiers of the LM3900 make this a very useful circuit. It has been called the "Bi-Quad" as it can produce a transfer function which is "Quad" — radic in both numerator and denominator (to give the "Bi"). A newer realization technique for this type of filter is the "second-degree state-variable network." Outputs can be taken at any of three points to give low pass, high pass or bandpass response characteristics (see the reference cited).

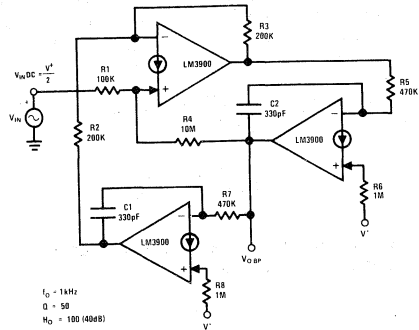


FIGURE 40. The "Bi-quad" RC Active Bandpass Filter

The bandpass filter is shown in Figure 40 and the design procedure is:

Given:  $Q$  and  $f_0$ .

To simplify: Let  $C_1 = C_2$  and choose a convenient starting value and also let  $2R_1 = R_2 = R_3$  and choose a convenient starting value.

Then:

$$R_4 = R_1 (2Q - 1), \quad (17)$$

$$R_5 = R_7 = \frac{1}{\omega_0 C_1}, \quad (18)$$

and for biasing the amplifiers we require

$$R_6 = R_8 = 2R_5. \quad (19)$$

The mid-band gain is:

$$H_0 = \frac{R_4}{R_1}. \quad (20)$$

As a design example;

Require:  $f_0 = 1 \text{ kHz}$  and  $Q = 50$ .

To find:  $C_1, C_2$  and  $R_1$  through  $R_8$ .

Choose:  $C_1 = C_2 = 330 \text{ pF}$

and  $2R_1 = R_2 = R_3 = 360 \text{ k}\Omega$ , and  $R_1 = 180 \text{ k}\Omega$ .

Then from equation (17),

$$R_4 = (1.8 \times 10^5) [2(50) - 1]$$

$$R_4 = 17.8 \text{ M}\Omega.$$

From equation (18),

$$R_5 = R_7 = \frac{1}{(2\pi \times 10^3)(3.3 \times 10^{-10})}$$

$$R_5 = 483 \text{ k}\Omega.$$

And from equation (19),

$$R_6 = R_8 \cong 1 \text{ M}\Omega.$$

From equation (20) the midband gain is 100 (40 dB). The value of  $R_4$  is high and can be lowered by scaling only  $R_1$  through  $R_4$  by the factor 1.78 to give:

$$2R_1 = R_2 = R_3 = \frac{360 \times 10^3}{1.78} = 200 \text{ k}\Omega, R_1 = 100 \text{ k}\Omega.$$

and

$$R_4 = \frac{17.8 \times 10^6}{1.78} = 10 \text{ M}\Omega.$$

These values (to the nearest 5% standard) have been added to Figure 40.

## 6.7 Conclusions

The unity-gain cross frequency of the LM3900 is 2.5 MHz which is approximately three times that of a "741" op amp. The performance of the amplifier does limit the performance of the filter. Historically, RC active filters started with little concern for these practical problems. The sensitivity functions were a big step forward as these demonstrated that many of the earlier suggested realization techniques for RC active filters had passive component sensitivity functions which varied as Q or even Q<sup>2</sup>. The Bi-Quad circuit has reduced the problems with the passive components (sensitivity functions of 1 or 1/2) and recently the contributions of the amplifier on the performance of the filter are being investigated. An excellent treatment ("The Biquad: Part I — Some Practical Design Considerations," L.C. Thomas, IEEE Transactions on Circuit Theory, Vol. CT-18, No. 3, May 1971) has indicated the limits imposed by the characteristics of the amplifier by showing that the design value of Q ( $Q_D$ ) will differ from the actual measured value of Q ( $Q_A$ ) by the given relationship

$$Q_A = \frac{Q_D}{1 + \frac{2Q_D}{A_O \omega_a} (\omega_a - 2\omega_p)} \quad (21)$$

where  $A_O$  is the open loop gain of the amplifier,  $\omega_a$  is the dominant pole of the amplifier and  $\omega_p$  is the resonant frequency of the filter. The result is that the trade-off between Q and center frequency ( $\omega_p$ ) can be determined for a given set of amplifier characteristics. When  $Q_A$  differs significantly from  $Q_D$  excessive dependence on amplifier characteristics is indicated. An estimate of the limitations of an amplifier can be made by arbitrarily allowing approximately a 10% effect on  $Q_A$  which results in

$$\frac{2Q_D}{A_O \omega_a} (\omega_a - 2\omega_p) = 0.1$$

or

$$\left(\frac{\omega_p}{\omega_a}\right) = 2.5 \times 10^{-2} \left(\frac{A_O}{Q_D}\right) + 0.5. \quad (22)$$

As an example, using  $A_O = 2800$  for the LM3900 we can estimate the maximum frequency where a  $Q_D = 50$  would be reasonable as

$$\frac{f_p}{f_a} = 2.5 \times 10^{-2} \left(\frac{2.8 \times 10^3}{5 \times 10}\right) + 0.5$$

or

$$\frac{f_p}{f_a} = 1.9$$

therefore

$$f_p = 1.9 f_a.$$

Again, using data of the LM3900,  $f_a = 1$  kHz so this upper frequency limit is approximately 2 kHz for the assumed Q of 50. As indicated in equation (26) the value of  $Q_A$  can actually exceed the value of  $Q_D$  (Q enhancement) and, as expected, the filter can even provide its own input (oscillating). Excess phase shift in the high frequency characteristics of the amplifier typically cause unexpected oscillations. Phase compensation can be used in the Bi-Quad network to reduce this problem (see L.C. Thomas paper).

Designing for large passband gain also increases filter dependency on the characteristics of the amplifier and finally signal to noise ratio can usually be improved by taking gain in an input RC active filter (again see L.C. Thomas paper).

Somewhat larger Q's can be achieved by adding more filter sections in either a synchronously tuned cascade (filters tuned to same center frequency and taking advantage of the bandwidth shrinkage factor which results from the series connection) or as a standard multiple pole filter. All of the conventional filters can be realized and selection is based upon all of the performance requirements which the application demands. The cost advantages of the LM3900, the relatively large bandwidth and the ease of operation on a single power supply voltage make this product an excellent "building block" for RC active filters.

## 7.0 DESIGNING WAVEFORM GENERATORS

The multiple amplifiers of the LM3900 can be used to easily generate a wide variety of waveforms in the low frequency range ( $f \leq 10$  kHz). Voltage controlled oscillators (VCO's) are also possible and are presented in section 8.0 "Designing Phase-locked Loops and Voltage Controlled Oscillators." In addition, power oscillators (such as noise makers, etc.) are presented in section 10.11.3. The waveform generators which will be presented in this section are mainly of the switching type, but for completeness a sinewave oscillator has been included.

### 7.1 A Sinewave Oscillator

The design of a sinewave oscillator presents problems in both amplitude stability (and predictability) and output waveform purity (THD). If an RC bandpass filter is used as a high Q resonator for the oscillator circuit we can obtain an output waveform with low distortion and eliminate the problem of relative center frequency drift which exists if the active filter were used simply to filter the output of a separate oscillator.

A sinewave oscillator which is based on this principle is shown in Figure 41. The two-amplifier RC active filter is used as it requires only two capacitors and provides an overall non-inverting phase characteristic. If we add a non-inverting gain controlled amplifier around the filter we obtain the desired oscillator configuration. Finally, the sinewave output voltage is sensed and regulated as the average value is compared to a DC reference voltage,  $V_{REF}$ , by use of a differential averaging circuit. It can be shown that with the values selected for  $R_{15}$  and  $R_{16}$  (ratio of 0.64/1) that there is first order temperature compensation for  $CR_3$  and the internal input diodes of the IC amplifier which is used for the "difference averager". Further, this also provides a simple way to regulate and to predict the magnitude of the output sinewave as

$$V_{O \text{ peak}} = 2 V_{REF}$$

which is essentially independent of both temperature and the magnitude of the power supply voltage (if  $V_{REF}$  is derived from a stable voltage source).

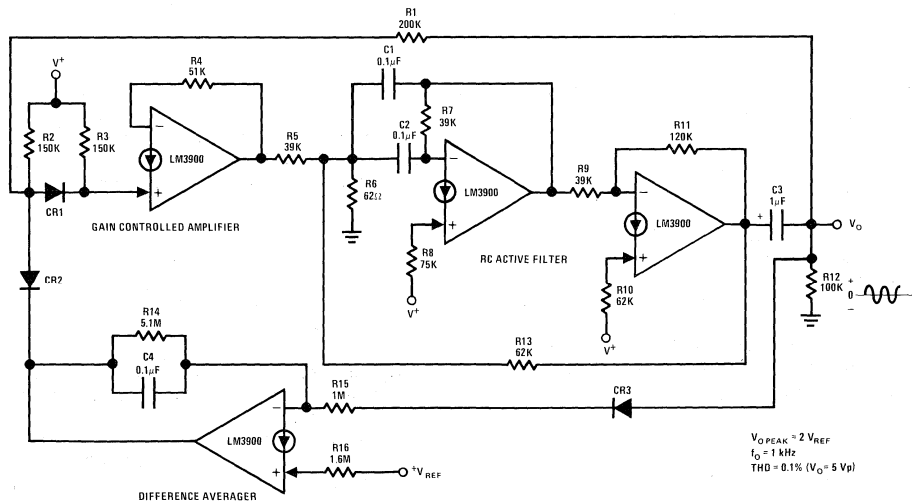


FIGURE 41. A Sinewave Oscillator

### 7.2 Squarewave Generator

The standard op amp squarewave generator has been modified as shown in Figure 42. The

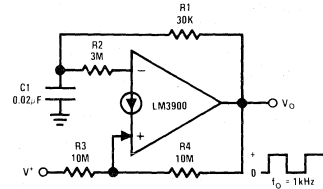


FIGURE 42. A Squarewave Oscillator

capacitor,  $C_1$ , alternately charges and discharges (via  $R_1$ ) between the voltage limits which are established by the resistors  $R_2$ ,  $R_3$  and  $R_4$ . This combination produces a Schmitt-Trigger circuit and the operation can be understood by noticing that when the output is low (and if we neglect the current flow through  $R_4$ ) the resistor  $R_2$  (3M) will cause the trigger to fire when the current through this resistor equals the current which enters the (+) input (via  $R_3$ ). This gives a firing voltage of approximately  $R_2/(R_3) V^+$  (or  $V^+/3$ ). The other trip point, when the output voltage is high, is approximately  $[2(R_2/R_3)] V^+$ , as  $R_3 = R_4$ , or  $2/3(V^+)$ . Therefore the voltage across the capacitor,  $C_1$ , will be the first one-half of an exponential waveform between these voltage trip limits and will have good symmetry and be essentially independent of the magnitude of the power supply voltage. If an unsymmetrical squarewave is desired, the trip points can be shifted to produce any desired mark/space ratio.

### 7.3 Pulse Generator

The squarewave generator can be slightly modified to provide a pulse generator. The slew rate limits of the LM3900 (0.5V/μsec) must be kept in mind as this limits the ability to produce a narrow pulse when operating at a high power supply voltage level. For example, with a +15 V<sub>DC</sub> power supply the rise time,  $t_r$ , to change 15V is given by:

$$t_r = \frac{15V}{\text{Slew Rate}} = \frac{15V}{0.5V/\mu\text{sec}}$$

$$t_r = 30 \mu\text{sec.}$$

The schematic of a pulse generator is shown in Figure 43. A diode has been added, CR<sub>1</sub>, to allow separating the charge path to C<sub>1</sub> (via R<sub>1</sub>)

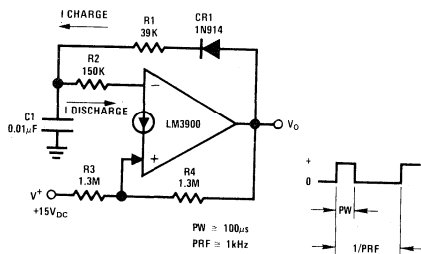


FIGURE 43. A Pulse Generator

from the discharge path (via R<sub>2</sub>). The circuit operates as follows, assume first that the output voltage has just switched low (and we will neglect the current flow through R<sub>4</sub>). The voltage across C<sub>1</sub> is high and the magnitude of the discharge current (through R<sub>2</sub>) is given by

$$I_{\text{Discharge}} \cong \frac{V_{C_1} - V_{BE}}{R_2}$$

This current is larger than that entering the (+) input which is given by

$$I_{R_3} = \frac{V^+ - V_{BE}}{R_3}$$

The excess current entering the (-) input terminal causes the amplifier to be driven to a low output voltage state (saturation). This condition remains for the long time interval (1/Pulse Repetition Frequency) until the R<sub>2</sub>C<sub>1</sub> discharge current equals the I<sub>R<sub>3</sub></sub> value (as CR<sub>1</sub> is OFF during this interval). The voltage across C<sub>1</sub> at the trip point, V<sub>L</sub>, is given by

$$V_L = (I_{R_3})(R_2),$$

or

$$V_L = (V^+ - V_{BE}) \left( \frac{R_2}{R_3} \right) \quad (1)$$

At this time the output voltage will switch to a high state, V<sub>OHi</sub>, and the current entering the (+) input will increase to

$$I_M^+ = \frac{V^+ - V_{BE}}{R_3} + \frac{V_{OHi} - V_{BE}}{R_4}$$

Also CR<sub>1</sub> goes ON and the capacitor, C<sub>1</sub>, charges via R<sub>1</sub>. Some of this charge current is diverted via R<sub>2</sub> to ground (the (-) input is at V<sub>CEsat</sub> during this interval as the current mirror is demanding more current than the (-) input terminal can provide). The high trip voltage, V<sub>H</sub>, is given by

$$V_H = (I_M^+) R_2 \quad \text{or}$$

$$V_H = \left( \frac{V^+ - V_{BE}}{R_3} + \frac{V_{OHi} - V_{BE}}{R_4} \right) R_2 \quad (2)$$

A design proceeds by first choosing the trip points for the voltage across C<sub>1</sub>. The resistors R<sub>3</sub> and R<sub>4</sub> are used only for this trip voltage control. The resistor R<sub>2</sub> affects the discharge time (the long interval) and also both of the trip voltages so this resistor is determined first from the required pulse repetition frequency (PRF). The value of R<sub>2</sub> is determined by the RC exponential discharge from V<sub>H</sub> to V<sub>L</sub> as this time interval, T<sub>1</sub>, controls the PRF (T<sub>1</sub> = 1/PRF). If we start with the equation for the RC discharge we have

$$V_L = V_H e^{-\frac{T_1}{R_2 C_1}}$$

or

$$\ln \frac{V_L}{V_H} = -\frac{T_1}{R_2 C_1}$$

or

$$T_1 = R_2 C_1 \ln \frac{V_H}{V_L} \quad (3)$$

To provide a low duty cycle pulse train we select small values for both V<sub>H</sub> and V<sub>L</sub> (such as 3V and 1.5V) and choose a starting value for C<sub>1</sub>. Then R<sub>2</sub> is given by

$$R_2 = \frac{T_1}{C_1 \ln \frac{V_H}{V_L}} \quad (4)$$

If R<sub>2</sub> from (4) is not in the range of approximately 100 kΩ to 1 MΩ, choose another value for C<sub>1</sub>. Now equation (1) can be used to find a value for R<sub>3</sub> to provide the V<sub>L</sub> which was initially assumed. Similarly equation (2) allows R<sub>4</sub> to be calculated. Finally R<sub>1</sub> is determined by the required pulse width (PW) as the capacitor, C<sub>1</sub>, must be charged from V<sub>L</sub> to V<sub>H</sub> by R<sub>1</sub>.

This RC charging is given by (neglecting the loading due to  $R_2$ )

$$V_H \cong (V_{OH_i} - V_D) \left( 1 - e^{-\frac{T_2}{R_1 C_1}} \right)$$

or

$$T_2 \cong -R_1 C_1 \ln \left[ 1 - \frac{V_H}{V_{OH_i} - V_D} \right], \text{ and finally}$$

$$R_1 \cong \frac{T_2}{-C_1 \ln \left[ 1 - \frac{V_H}{V_{OH_i} - V_D} \right]} \quad (5)$$

where  $T_2$  is the pulse width desired and  $V_D$  is the forward voltage drop across  $CR_1$ .

As a design example:

Required: Provide a  $100\mu\text{s}$  pulse every 1 ms. The power supply voltage is  $+15 V_{DC}$

1.0 Start by choosing  $V_L = 1.5V$

and  $V_H = 3.0V$

2.0 Find  $R_2$  from equation (4) assuming  $C_1 = 0.01\mu\text{F}$ ,

$$R_2 = \frac{10^{-3}}{10^{-8} \ln \left( \frac{3.0}{1.5} \right)}$$

$$R_2 = \frac{10^5}{0.694} = 144 \text{ k}\Omega$$

3.0 Find  $R_3$  from equation (1)

$$R_3 = \frac{(V^+ - V_{BE}) R_2}{V_L}$$

$$R_3 = \frac{(15 - 0.5) 1.44 \times 10^5}{1.5}$$

$$R_3 = 1.39 \text{ M}\Omega$$

4.0 Find  $R_4$  from equation (2),

$$R_4 = \frac{(V_{OH_i} - V_{BE})}{\frac{V_H}{R_2} - \frac{V^+ - V_{BE}}{R_3}}$$

$$R_4 = \frac{(14.2 - 0.5)}{\frac{3}{1.44 \times 10^5} - \frac{15 - 0.5}{1.39 \times 10^6}}$$

$$R_4 = 1.32 \text{ M}\Omega$$

5.0 Find  $R_1$  from equation (5),

$$R_1 = \frac{10^{-4}}{-10^{-8} \ln \left( 1 - \frac{3}{14.2 - 0.7} \right)}$$

$$R_1 = \frac{10^4}{-\ln \left( 1 - \frac{3}{13.5} \right)}$$

$$R_1 = \frac{10^4}{0.252} = 39.7 \text{ k}\Omega$$

These values (to the nearest 5% standard) have been added to Figure 43.

## 7.4 Triangle Waveform Generator

Triangle waveforms are usually generated by an integrator which receives first a positive DC input voltage. The LM3900 easily provides this operation in a system which operates with only a single power supply voltage by making use of the current mirror which exists at the (+) input. This allows the generation of a triangle waveform without requiring a negative DC input voltage.

The schematic diagram of a triangle waveform generator is shown in Figure 44. One amplifier

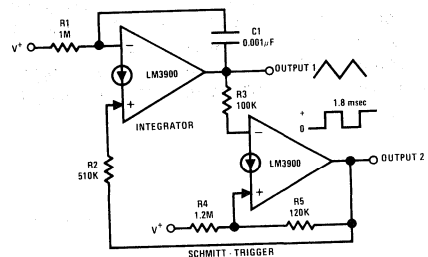


FIGURE 44. A Triangle Waveform Generator

is doing the integration by operating first with the current through  $R_1$ , to produce the negative output voltage slope, and then when the output of the second amplifier (the Schmitt-Trigger) is high, the current through  $R_2$  causes the output voltage to increase. If  $R_1 = 2R_2$ , the output waveform will have good symmetry. The timing for one-half of the period ( $T/2$ ) is given by

$$\frac{T}{2} = \frac{(R_1 C_1) \Delta V_O}{V^+ - V_{BE}}$$

or the output frequency becomes

$$f_o = \frac{V^+ - V_{BE}}{2R_1 C_1 \Delta V_O}$$

where we have assumed  $R_1 = 2R_2$ ,  $V_{BE}$  is the DC voltage at the (-) input ( $0.5 V_{DC}$ ), and  $\Delta V_O$

is the difference between the trip points of the Schmitt-Trigger. The design of the Schmitt-Trigger has been presented in the section on Digital and Switching Circuits (9.0) and the trip voltages control the peak-to-peak excursion of the triangle output waveform. The output of the Schmitt circuit provides a squarewave of the same frequency.

### 7.5 Sawtooth Waveform Generator

The previously described triangle waveform generator, Figure 44, can be modified to produce a sawtooth waveform. Two types of waveforms can be provided, both a positive ramp and a negative ramp sawtooth waveform by selecting  $R_1$  and  $R_2$ . The reset time is also controlled by the ratio of  $R_1$  to  $R_2$ . For example, if  $R_1 = 10 R_2$  a positive ramp sawtooth results and if  $R_2 = 10 R_1$  a negative ramp sawtooth can be obtained. Again, the slew rate limits of the amplifier ( $0.5V/\mu s$ ) will limit the minimum retrace time, and the increased slew rate of a negative going output will allow a faster retrace for a positive ramp sawtooth waveform.

To provide a gated sawtooth waveform, the circuits shown in Figure 45 can be used. In Figure 45(a), a positive ramp is generated by integrating the current,  $I$ , which is entering the (+) input. Reset is provided via  $R_1$  and  $CR_1$  keeps  $R_1$  from loading at the (-) input during the sweep interval. This will sweep from  $V_{O\ MIN}$  to  $V_{O\ MAX}$  and will remain at  $V_{O\ MAX}$  until reset. The interchange of the input leads, Figure 45(b), will generate a negative ramp, from  $V_{O\ MAX}$  to  $V_{O\ MIN}$ .

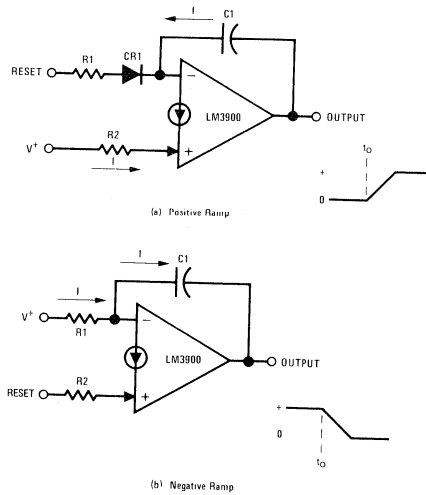


FIGURE 45. Gated Sawtooth Generators

#### 7.5.1 Generating a Very Slow Sawtooth Waveform

The LM3900 can be used to generate a very slow sawtooth waveform which can be used to generate long time delay intervals. The circuit is shown in Figure 46 and uses four amplifiers. Amps 1 and 2 are cascaded to increase the gain of the integrator and the output is the desired very slow sawtooth waveform. Amp 3 is used to exactly supply the bias current to Amp 1.

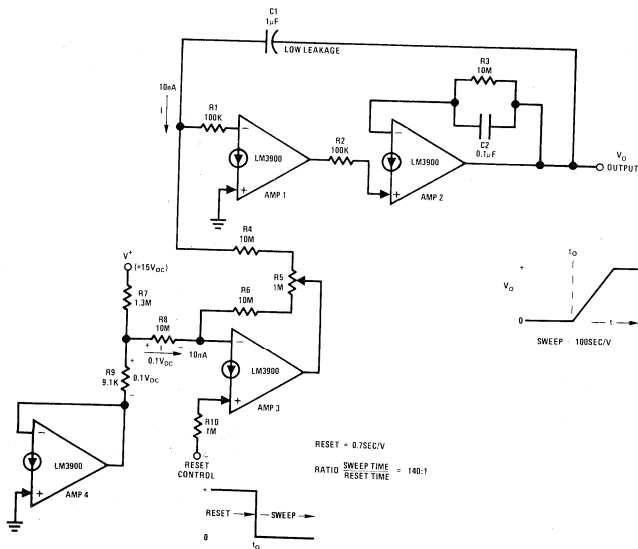


FIGURE 46. Generating Very Slow Sawtooth Waveforms



With resistor  $R_8$  opened up and the reset control at zero volts, the potentiometer,  $R_5$ , is adjusted to minimize the drift in the output voltage of Amp 2 (this output must be kept in the linear range to insure that Amp 2 is not in saturation). Amp 4 is used to provide a bias reference which equals the DC voltage at the (-) input of Amp 3. The resistor divider,  $R_7$  and  $R_9$ , provides a  $0.1 V_{DC}$  reference voltage across  $R_9$  which also appears across  $R_8$ . The current which flows through  $R_8$ ,  $I$ , enters the (-) input of Amp 3 and causes the current through  $R_6$  to drop by this amount. This causes an imbalance as now the current flow through  $R_4$  is no longer adequate to supply the input current of Amp 1. The net result is that this same current,  $I$ , is drawn from capacitor  $C_1$  and causes the output voltage of Amp 2 to sweep slowly positive. As a result of the high impedance values used, the PC component board used for this circuit must first be cleaned and then coated with silicone rubber to eliminate the effects of leakage currents across the surface of the board. The DC leakage currents of the capacitor,  $C_1$ , must also be small compared to the 10 nA charging current. For example, an insulation resistance of 100,000  $M\Omega$  will leak 0.1 nA with 10  $V_{DC}$  across the capacitor and this leakage rapidly increases at higher temperatures. Dielectric polarization of the dielectric material may not cause problems if the circuit is not rapidly cycled. The resistor,  $R_8$ , and the capacitor,  $C_1$ , can be scaled to provide other basic sweep rates. For the values shown on Figure 46 the 10 nA current and the  $1\mu F$  capacitor establish a sweep rate of 100 sec/volt. The reset control pulse (Amp 3 (+) input) causes Amp 3 to go to the positive output saturation state and the 10  $M\Omega$  ( $R_4$ ) gives a reset rate of 0.7 sec/volt. The resistor,  $R_1$ , prevents a large discharge current of  $C_1$  from overdriving the (-) input and overloading the input clamp device. For larger charging currents, a resistor divider can be placed from the output of Amp 4 to ground and  $R_8$  can tie from this tap point directly to the (-) input of Amp 1.

## 7.6 Staircase Waveform Generators

A staircase generator can be realized by supplying pulses to an integrator circuit. The LM-3900 also can be used with a squarewave input signal and a differentiating network where each transition of the input squarewave causes a step in the output waveform (or two steps per input cycle). This is shown in Figure 47. These pulses of current are the charge and discharge currents of the input capacitor,  $C_1$ . The charge current,  $I_C$ , enters the (+) input and is mirrored about ground and is "drawn into" the (-) input. The discharge current,  $I_D$ , is drawn through the diode at the input,  $CR_1$ , and therefore also causes a step in the output staircase.

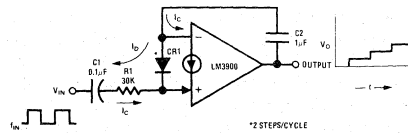


FIGURE 47. Pumping the Staircase Via Input Differentiator

A free running staircase generator is shown in Figure 48. This uses all four of the amplifiers which are available in one LM3900 package.

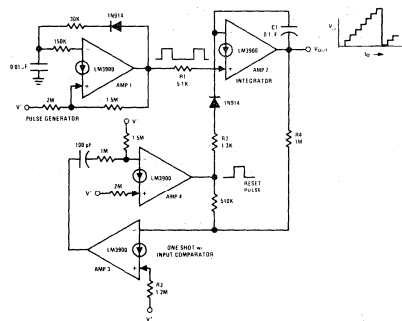


FIGURE 48. A Free Running Staircase Generator

Amp 1 provides the input pulses which "pump up" the staircase via resistor  $R_1$  (see section 7.3 for the design of this pulse generator). Amp 2 does the integrate and hold function and also supplies the output staircase waveform. Amps 3 and 4 provide both a compare and a one-shot multivibrator function (see the section on Digital and Switching Circuits for the design of this dual function one-shot). Resistor  $R_4$  is used to sample the staircase output voltage and to compare it with the power supply voltage ( $V^+$ ) via  $R_3$ . When the output exceeds approximately 80% of  $V^+$  the connection of Amps 3 and 4 cause a 100  $\mu$  sec reset pulse to be generated. This is coupled to the integrator (Amp 2) via  $R_2$  and causes the staircase output voltage to fall to approximately zero volts. The next pulse out of Amp 1 then starts a new stepping cycle.

## 7.7 A Pulse Counter and a Voltage Variable Pulse Counter

The basic circuit of Figure 48 can be used as a pulse counter simply by omitting Amp 1 and feeding input voltage pulses directly to  $R_1$ . A simpler one-shot/comparator which requires only one amplifier can also be used in place of Amps 3 and 4 (again, see the section on Digital and Switching Circuits). To extend the time interval between pulses, an additional amplifier can be used to supply base current to

Amp 2 to eliminate the tendency for the output voltage to drift up due to the 30 nA input current (see section 7.5.1). The pulse count can be made voltage variable simply by removing the comparator reference ( $R_3$ ) from  $V^+$  and using this as a control voltage input. Finally, the input could be derived from differentiating a squarewave input as was shown in Figure 47 and if only one step per cycle were desired, the diode, CR<sub>1</sub> of Figure 47, can be eliminated.

### 7.8 An Up-down Staircase Waveform Generator

A staircase waveform which first steps up and then steps down is provided by the circuit shown in Figure 49. An input pulse generator

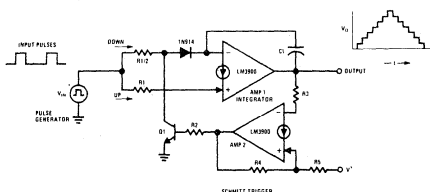


FIGURE 49. An Up-down Staircase Generator

provides the pulses which cause the output to step up or down depending on the conduction of the clamp transistor, Q<sub>1</sub>. When this is ON, the "down" current pulse is diverted to ground and the staircase then steps "up". When the upper voltage trip point of Amp 2 (Schmitt-Trigger—see section on Digital and Switching Circuits) is reached, Q<sub>1</sub> goes OFF and as a result of the smaller "down" input resistor (one-half the value of the "up" resistor, R<sub>1</sub>) the staircase steps "down" to the low voltage trip point of Amp 2. The output voltage therefore steps up and down between the trip voltages of the Schmitt-Trigger.

## 8.0 DESIGNING PHASE-LOCKED LOOPS AND VOLTAGE CONTROLLED OSCILLATORS

The LM3900 can be connected to provide a low frequency ( $f < 10$  kHz) phase-locked loop (PL<sup>2</sup>). This is a useful circuit for many control applications. Tracking filters, frequency to DC converters, FM modulators and demodulators are applications of a PL<sup>2</sup>.

### 8.1 Voltage Controlled Oscillators (VCO)

The heart of a PL<sup>2</sup> is the voltage controlled oscillator (VCO). As the PL<sup>2</sup> can be used for

many functions, the required linearity of the transfer characteristic (frequency out to DC voltage in) depends upon the application. For low distortion demodulation of an FM signal, a high degree of linearity is necessary whereas a tracking filter application would not require this performance in the VCO.

A VCO circuit is shown in Figure 50. Only two amplifiers are required, one is used to integrate the DC input control voltage,  $V_C$ , and the other is connected as a Schmitt-trigger which monitors the output of the integrator. The trigger circuit is used to control the clamp transistor, Q<sub>1</sub>. When Q<sub>1</sub> is conducting, the input current,  $I_2$ , is shunted to ground. During this one-half cycle the input current,  $I_1$ , causes the output voltage of the integrator to ramp down. At the minimum point of the triangle waveform (output 1), the Schmitt circuit changes state and transistor Q<sub>1</sub> goes OFF. The current,  $I_2$ , is exactly twice the value of  $I_1$  ( $R_2 = R_1/2$ ) such that a charge current (which is equal to the magnitude of the discharge current) is drawn through the capacitor, C, to provide the increasing portion of the triangular waveform (output 1).

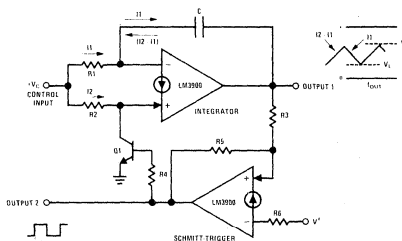


FIGURE 50. A Voltage Controlled Oscillator

The output frequency for a given DC input control voltage depends on the trip voltages of the Schmitt circuit ( $V_H$  and  $V_L$ ) and the components  $R_1$  and  $C_1$  (as  $R_2 = R_1/2$ ). The time to ramp down from  $V_H$  to  $V_L$  corresponds to one-half the period (T) of the output frequency and can be found by starting with the basic equation of the integrator

$$V_O = -\frac{1}{C} \int I_1 dt \quad (1)$$

as  $I_1$  is a constant (for a given value of  $V_C$ ) which is given by

$$I_1 = \frac{V_C - V_{BE}}{R_1} \quad (2)$$

equation (1) simplifies to

$$\Delta V_O = - \frac{I_1}{C} (\Delta t)$$

or

$$\frac{\Delta V_O}{\Delta t} = - \frac{I_1}{C} \quad (3)$$

Now the time,  $\Delta t$ , to sweep from  $V_H$  to  $V_L$  becomes

$$\Delta t_1 = \frac{(V_H - V_L) C}{I_1} \text{ or}$$

$$T = \frac{2(V_H - V_L) C}{I_1} \text{ and}$$

$$f = \frac{1}{T} = \frac{I_1}{2(V_H - V_L) C} \quad (4)$$

Therefore, once  $V_H$ ,  $V_L$ ,  $R_1$  and  $C$  are fixed in value, the output frequency,  $f$ , is a linear function of  $I_1$  (as desired for a VCO).

The circuit shown in Figure 50 will require  $V_C > V_{BE}$  to oscillate. A value of  $V_C = 0$  provides  $f_{OUT} = 0$ , which may or may not be desired. Two common-mode input biasing resistors can be added as shown in Figure 51 to allow  $f_{OUT} = f_{MIN}$  for  $V_C = 0$ . In general, if these resistors are a factor of 10 larger than their corresponding resistor ( $R_1$  or  $R_2$ ) a large control frequency ratio can be realized. Actually,  $V_C$  could range outside the supply voltage limit of  $V^+$  and this circuit will still function properly.

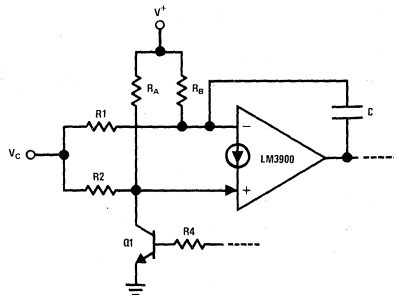


FIGURE 51. Adding Input Common-mode Biasing Resistors

The output frequency of this circuit can be increased by reducing the peak-to-peak excursion of the triangle waveform (output 1) by design of the trip points of the Schmitt circuit.

A limit is reached when the triangular sweep output waveform exceeds the slow rate limit of the LM3900 ( $0.5V/\mu s$ ). Note that the output of the Schmitt circuit has to move up only one  $V_{BE}$  to bring the clamp transistor,  $Q_1$ , ON, and therefore output slew rate of this circuit is not a limit.

To improve the temperature stability of the VCO, a PNP emitter follower can be used to give approximate compensation for the  $V_{BE}$ 's at the inputs to the amplifier (see Figure 52). Finally to improve the mark to space ratio accuracy over temperature and at low control voltages, an additional amplifier can be added such that both reference currents are applied to

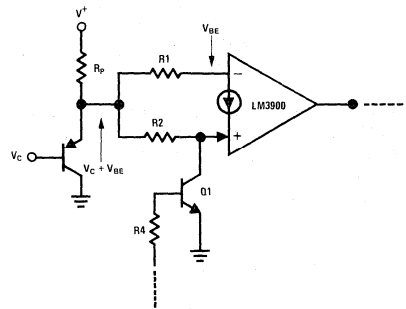


FIGURE 52. Reducing Temperature Drift

the same type of (inverting) inputs of the LM3900. The circuit to accomplish this is shown within dotted lines in Figure 53.

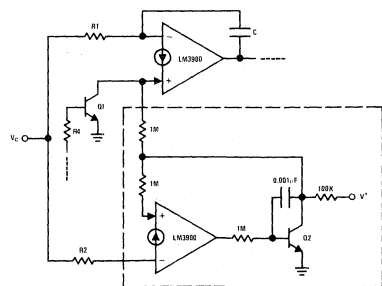


FIGURE 53. Improving Mark/Space Ratio

## 8.2 Phase Comparator

A basic phase comparator is shown in Figure 54. This circuit provides a pulse-width modulated output voltage waveform,  $V_{O1}$ , which must be filtered to provide a DC output voltage (this filter can be the same as the one needed in the PL<sup>2</sup>). The resistor  $R_2$  is made smaller than  $R_1$  so the (+) input serves to inhibit the (-) input

signal. The center of the dynamic range is indicated by the waveforms shown on the figure ( $90^\circ$  phase difference between  $f_{IN}$  and  $f_{VCO}$ ).

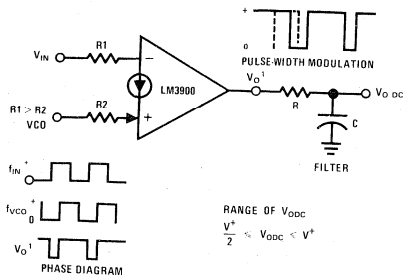


FIGURE 54. Phase Comparator

The filtered DC output voltage will center at  $3V^+/4$  and can range from  $V^+/2$  to  $V^+$  as the phase error ranges from 0 degrees to 180 degrees.

### 8.3 A Complete Phase-locked Loop

A phase-locked loop can be realized with three of the amplifiers as shown in Figure 55. This has a center frequency of approximately 3 kHz.

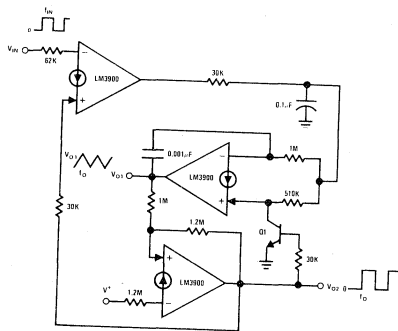


FIGURE 55. A Phase-locked Loop

To increase the lock range, DC gain can be added at the input to the VCO by using the fourth amplifier of the LM3900. If the gain is inverting, the limited DC dynamic range out of the phase detector can be increased to improve the frequency lock range. With inverting gain, the input to the VCO could go to zero volts. This will cause the output of the VCO to go high ( $V^+$ ) and will latch if applied to the (+) input of the phase comparator. Therefore apply the VCO signal to the (-) input of the phase comparator or add the common-mode biasing resistors of Figure 51.

## 8.4 Conclusions

One LM3900 package (4 amplifiers) can provide all of the operations necessary to make a phase-locked loop. In addition, a VCO is a generally useful component for other system applications.

## 9.0 DESIGNING DIGITAL AND SWITCHING CIRCUITS

The amplifiers of the LM3900 can be overdriven and used to provide a large number of low speed digital and switching circuit applications for control systems which operate off of single power supply voltages larger than the standard  $+5 V_{DC}$  digital limit. The large voltage swing and slower speed are both advantages for most industrial control systems. Each amplifier of the LM3900 can be thought of as "a super transistor" with a  $\beta$  of 1,000,000 (25 nA input current and 25 mA output current) and with a non-inverting input feature. In addition, the active pull-up and pull-down which exists at the output will supply larger currents than the simple resistor pull-ups which are used in digital logic gates. Finally, the low input currents allow timing circuits which minimize the capacitor values as large impedance levels can be used with the LM3900.

### 9.1 An "OR" GATE

An OR gate can be realized by the circuit shown in Figure 56. A resistor (150 k $\Omega$ ) from  $V^+$  to the (-) input keeps the output of the amplifier in a low voltage saturated state for all inputs A, B, and C at 0V. If any one of the input signals were to go high ( $\cong V^+$ ) the current flow through the 75 k $\Omega$  input resistor will cause the amplifier to switch to the positive output saturation state ( $V_O \cong V^+$ ). The current loss through the other input resistors (which have an input in the low voltage state) represents an insignificant amount of the total input current which is provided by the, at least one, high voltage input. More than three inputs can be OR'ed if desired.

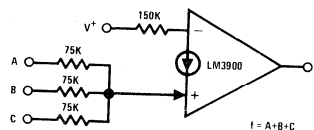


FIGURE 56. An "OR" Gate

The "fan-out" or logical drive capability is large (50 gates if each gate input has a 75 k $\Omega$  resistor) due to the 10 mA output current capability of the LM3900. A NOR gate can be obtained by interchanging the inputs to the LM3900.

### 9.2 An "AND" Gate

A three input AND gate is shown in Figure 57. This gate requires all three inputs to be high in order to have sufficient current entering the (+) input to cause the output of the amplifier to switch high. The addition of  $R_2$  causes a smaller current to enter the (+) input when only two of the inputs are high. (A two input AND gate would not require a resistor as  $R_2$ ). More than

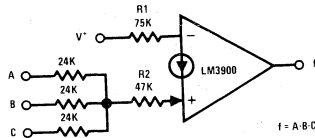


FIGURE 57. An "AND" Gate

three inputs becomes difficult with this resistor summing approach as the (+) input is too close to having the necessary current to switch just prior to the last input going high. For a larger fan-in an input diode network (similar to DTL) is recommended as shown in Figure 58. Interchange the inputs for a NAND gate.

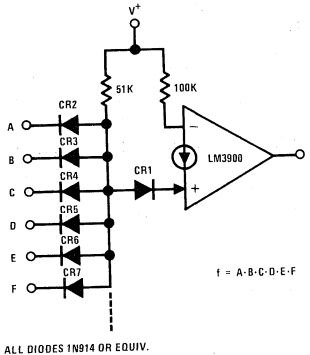


FIGURE 58. A Large Fan-in "AND" Gate

### 9.3 A Bi-stable Multivibrator

A bi-stable multivibrator (an asynchronous RS flip-flop) can be realized as shown in Figure 59. Positive feedback is provided by resistor  $R_4$  which causes the latching. A positive pulse at

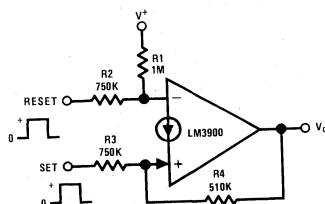


FIGURE 59. A Bi-stable Multivibrator

the "set" input causes the output to go high and a "reset" positive pulse will return the output to essentially  $0V_{DC}$

### 9.4 Trigger Flip Flops

Trigger flip flops are useful to divide an input frequency as each input pulse will cause the output of a trigger flip flop to change state. Again, due to the absence of a clocking signal input, this is for an asynchronous logic application. A circuit which uses only one amplifier is shown in Figure 60. Steering of the differentiated positive input trigger is provided by the diode CR2. For a low output voltage state,

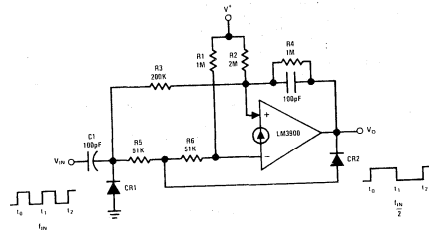


FIGURE 60. A Trigger Flip Flop

CR2 shunts the trigger away from the (-) input and resistor  $R_3$  couples this positive input trigger to the (+) input terminal. This causes the output to switch high. The high voltage output state now keeps CR2 OFF and the smaller value of  $(R_5 + R_6)$  compared with  $R_3$  causes a larger positive input trigger to be coupled to the (-) input which causes the output to switch to the low voltage state.

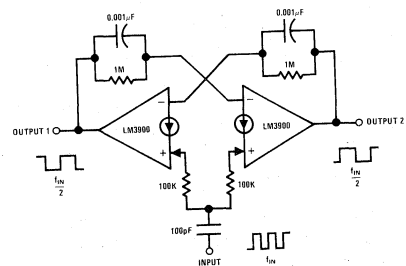


FIGURE 61. A Two-amplifier Trigger Flip Flop

A second trigger flip flop can be made which consists of two amplifiers and also provides a complementary output. This connection is shown in Figure 61.

### 9.5 Monostable Multivibrators (One-shots)

Monostable multivibrators can be made using one or two of the amplifiers of the LM3900. In addition, the output can be designed to be

either high or low in the quiescent state. Further, to increase the usefulness, a one-shot can be designed which triggers at a particular DC input voltage level to serve the dual role of providing first a comparator and then a pulse generator.

### 9.5.1 A Two-amplifier One-shot

A circuit for a two-amplifier one-shot is shown in Figure 62. As the resistor,  $R_2$ , from  $V^+$  to the (-) input is smaller than  $R_5$  (from  $V^+$  to the (+) input), amplifier 2 will be biased to a low-voltage output in the quiescent state. As a

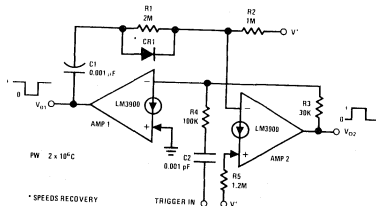


FIGURE 62. A One-shot Multivibrator

result, no current is supplied to the (-) input of amplifier 1 (via  $R_3$ ) which causes the output of this amplifier to be in the high voltage state. Capacitor  $C_1$  therefore has essentially the full  $V^+$  supply voltage across it ( $V^+ - 2V_{BE}$ ). Now when a differentiated trigger (due to  $C_2$ ) causes amplifier 1 to be driven ON (output voltage drops to essentially zero volts) this negative transient is coupled (via  $C_1$ ) to the (-) input of amplifier 2 which causes the output of this amplifier to be driven high (to positive saturation). This condition remains while  $C_1$  discharges via ( $R_1$ ) from approximately  $V^+$  to approximately  $V^+/2$ . This time interval is the pulse width (PW). After  $C_1$  no longer diverts sufficient current of  $R_2$  away from the (-) input of amplifier 2 (i.e.,  $C_1$  is discharged to approximately  $V^+/2$  V) the stable DC state is restored—amplifier 2 output low and amplifier 1 output high.

This circuit can be rapidly re-triggered due to the action of the diode,  $CR_1$ . This re-charges  $C_1$  as amplifier 1 drives full output current capability (approximately 10 mA) through  $C_1$ ,  $CR_1$  and into the saturated (-) input of amplifier 2 to ground. The only time limit is the 10 mA available from amplifier 1 and the value of  $C_1$ . If a rapid reset is not required,  $CR_1$  can be omitted.

### 9.5.2 A Combination One-shot/Comparator Circuit

In many applications a pulse is required if a DC input signal exceeds a predetermined

value. This exists in free-running oscillators where after a particular output level has been reached a reset pulse must be generated to recycle the oscillator. This double function is provided with the circuit of Figure 63. The

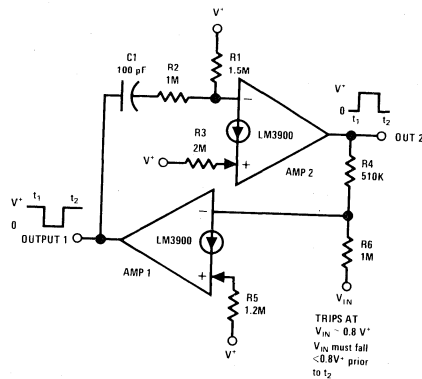


FIGURE 63. A One-shot Multivibrator with an Input Comparator

resistors  $R_5$  and  $R_6$  of amplifier 1 provide the inputs to a comparator and, as shown, an input signal,  $V_{IN}$ , is compared with the supply voltage,  $V^+$ . The output voltage of amplifier 1 is normally in a high voltage state and will fall and initiate the generation of the output pulse when  $V_{IN}$  is  $R_6/R_5 V^+$  or approximately 80% of  $V^+$ . To keep  $V_{IN}$  from disturbing the pulse generation it is required that  $V_{IN}$  fall to less than the trip voltage prior to the termination of the output pulse. This is the case when this circuit is used to generate a reset pulse and therefore this causes no problems.

### 9.5.3 A One-amplifier One-shot (Positive Pulse)

A one-shot circuit can be realized using only one amplifier as shown in Figure 64.

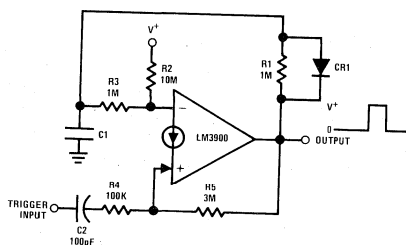


FIGURE 64. A One-amplifier One-shot (Positive Output)

The resistor  $R_2$  keeps the output in the low voltage state. A differentiated positive trigger causes the output to switch to the high voltage state and resistor  $R_5$  latches this state. The

capacitor,  $C_1$ , charges from essentially ground to approximately  $V^+/4$  where the circuit latches back to the quiescent state. The diode,  $CR_1$ , is used to allow a rapid re-triggering.

### 9.5.4 A One-amplifier One-shot (Negative Pulse)

A one-amplifier one-shot multivibrator which has a quiescent state with the output high and which falls to zero volts for the pulse duration is shown in Figure 65.

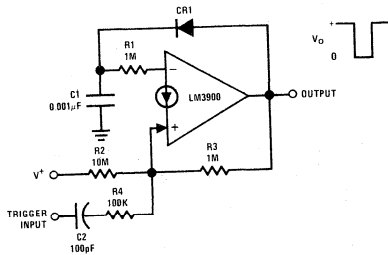


FIGURE 65. A One-amplifier One-shot (Negative Output)

The sum of the currents through  $R_2$  and  $R_3$  keeps the (-) input at essentially ground. This causes  $V_O$  to be in the high voltage state. A differentiated negative trigger waveform causes the output to switch to the low voltage state. The large voltage across  $C_1$  now provides input current via  $R_1$  to keep the output low until  $C_1$  is discharged to approximately  $V^+/10$ . At this time the output switches to the stable high voltage state.

If the  $R_4$   $C_2$  network were moved to the (-) input terminal, the circuit will trigger on a differentiated positive trigger waveform.

## 9.6 Comparators

The voltage comparator is a function required for most system operations and can easily be performed by the LM3900. Both an inverting and a non-inverting comparator can be obtained.

### 9.6.1 A Comparator for Positive Input Voltages

The circuit in Figure 66 is an inverting comparator. To insure proper operation, the reference

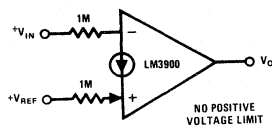


FIGURE 66. An Inverting Voltage Comparator

voltage must be larger than  $V_{BE}$ , but there is no upper limit as long as the input resistor is large enough to guarantee that the input current will not exceed  $200\mu A$ .

### 9.6.2 A Comparator for Negative Input Voltages

Adding a common-mode biasing network to the comparator in Figure 66 makes it possible to compare voltages between zero and one volt as well as the comparison of rather large negative voltages, Figure 67. When working with negative voltages, the current supplied by the common-mode network must be large enough to satisfy both the current drain demands of the input voltages and the bias current requirement of the amplifier.

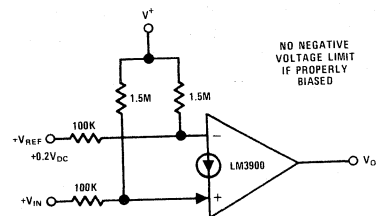


FIGURE 67. A Non-inverting Low-voltage Comparator

### 9.6.3 A Power Comparator

When used in conjunction with an external transistor, this power comparator will drive loads which require more current than the IC amplifier is capable of supplying. Figure 68 shows a non-inverting comparator which is capable of driving a 12V, 40 mA panel lamp.

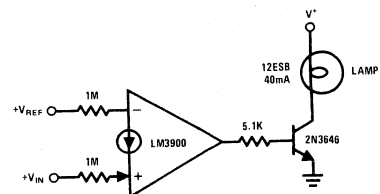


FIGURE 68. A Non-inverting Power Comparator

### 9.6.4 A More Precise Comparator

A more precise comparator can be designed by using a second amplifier such that the input voltages of the same type of inputs are compared. The (-) input voltages of two amplifiers are naturally more closely matched initially and track well with temperature changes. The comparator of Figure 69 uses this concept.

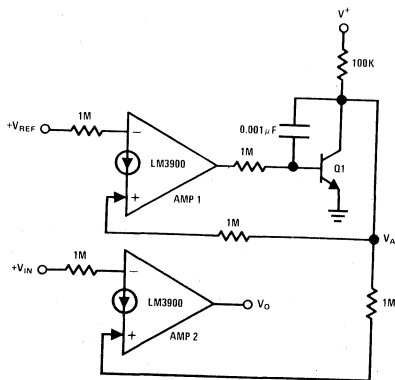


FIGURE 69. A More Precise Comparator

The current established by  $V_{REF}$  at the inverting input of amplifier 1 will cause transistor  $Q_1$  to adjust the value of  $V_A$  to supply this current. This value of  $V_A$  will cause an equal current to flow into the non-inverting input of amplifier 2. This current corresponds more exactly to the reference current of amplifier 1.

A differential input stage can also be added to the LM3900 (see section 10.16) and the resulting circuit can provide a precision comparator circuit.

### 9.7 Schmitt-Triggers

Hysteresis may be designed into comparators which use the LM3900 as shown in Figure 70.

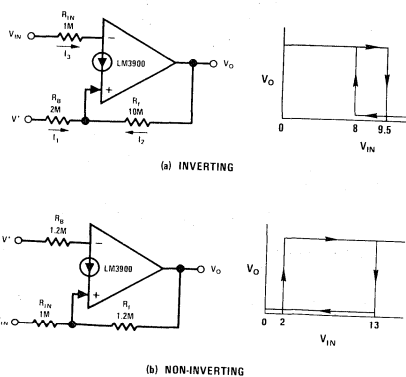


FIGURE 70. Schmitt-Triggers

The lower switch point for the inverting Schmitt-Trigger is determined by the amount of current flowing into the positive input with the output voltage low. When the input current,  $I_3$ , drops below the level required by the

current mirror, the output will switch to the high limit. With  $V_O$  high, the current demanded by the mirror is increased by a fixed amount,  $I_2$ . As a result, the  $I_3$  required to switch the output increases this same amount. Therefore, the switch points are determined by selecting resistors which will establish the required currents at the desired input voltages. Reference current ( $I_1$ ) and feedback current ( $I_2$ ) are set by the following equation.

$$I_1 = \frac{V^+ - \phi}{R_B}$$

$$I_2 = \frac{V_{O \text{ MAX}} - \phi}{R_F}$$

By adjusting the values of  $R_B$ ,  $R_F$ , and  $R_{IN}$ , the switching values of  $V_{IN}$  may be set to any levels desired.

The non-inverting Schmitt-Trigger works in the same way except that the input voltage is applied to the (+) input. The range of  $V_{IN}$  may be very large when compared with the operating voltage of the amplifier.

## 10.0 SOME SPECIAL CIRCUIT APPLICATIONS

This section contains various special circuits which did not fit the order of things or which are one-of-a-kind type of applications.

### 10.1 Current Sources and Sinks

The amplifiers of the LM3900 can be used in feedback loops which regulate the current in external PNP transistors to provide current sources or in external NPN transistors to provide current sinks. These can be multiple sources or single sources which are fixed in value or made voltage variable.

#### 10.1.1 A Fixed Current Source

A multiple fixed current source is provided by the circuit of Figure 71. A reference voltage ( $1 V_{DC}$ ) is established across resistor  $R_3$  by the resistive divider ( $R_3$  and  $R_4$ ). Negative feedback is used to cause the voltage drop across  $R_1$  to also be  $1 V_{DC}$ . This controls the emitter current of transistor  $Q_1$  and if we neglect the small current diverted into the (-) input via the 1M input resistor ( $13.5 \mu A$ ) and the base current of  $Q_1$  and  $Q_2$  (an additional 2% loss if the  $\beta$  of these transistors is 100), essentially this same current is available out of the collector of  $Q_1$ .



Larger input resistors can be used to reduce current loss and a Darlington connection can be used to reduce errors due to the  $\beta$  of  $Q_1$ .

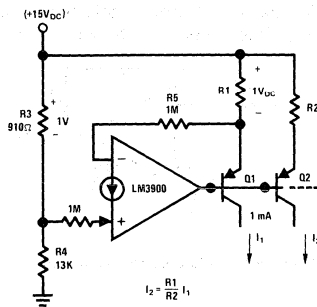


FIGURE 71. Fixed Current Sources

The resistor,  $R_2$ , can be used to scale the collector current of  $Q_2$  either above or below the 1 mA reference value.

### 10.1.2 A Voltage Variable Current Source

A voltage variable current source is shown in Figure 72. The transconductance is  $-(1/R_2)$  as the voltage gain from the input terminal to the emitter of  $Q_1$  is -1. For a  $V_{IN} = 0$  VDC the output current is essentially zero mA DC. The resistors  $R_1$  and  $R_6$  guarantee that the amplifier can turn OFF transistor  $Q_1$ .


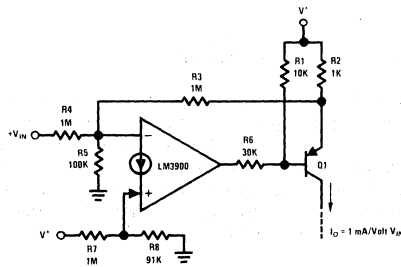



FIGURE 72. A Voltage Controlled Current Source
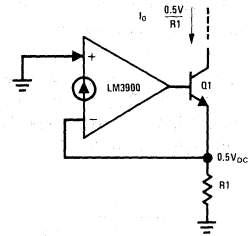
### 10.1.3 A Fixed Current Sink

Two current sinks are shown in Figure 73. The circuit of Figure 73(a) requires only one resistor and supplies an output current which is directly proportional to this R value. A negative temperature coefficient will result due to the 0.5 VDC reference being the base-emitter junction voltage of the (-) input transistor. If this temperature coefficient is objectionable, the circuit of Figure 73(b) can be employed.



(a) A SIMPLE CURRENT SINK

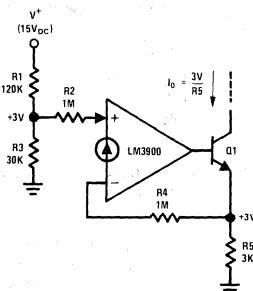

(b) REDUCING TEMPERATURE DRIFT OF  $I_2$

FIGURE 73. Fixed Current Sinks

### 10.1.4 A Voltage Variable Current Sink

A voltage variable current sink is shown in Figure 74. The output current is 1 mA per volt of  $V_{IN}$  (as  $R_5 = 1$  k $\Omega$  and the gain is +1). This circuit provides approximately 0 mA output current for  $V_{IN} = 0$  VDC.

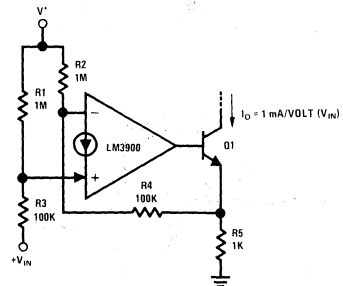


FIGURE 74. A Voltage Controlled Current Sink

## 10.2 Operation From $\pm 15$ VDC Power Supplies

If the ground pin (no. 7) is returned to a negative voltage and some changes are made in the biasing circuits, the LM3900 can be operated from  $\pm 15$  VDC power supplies.

### 10.2.1 An AC Amplifier Operating with $\pm 15$ V<sub>DC</sub> Power Supplies

An AC coupled amplifier is shown in Figure 75. The biasing resistor,  $R_B$ , is now returned to ground and both inputs bias at one  $V_{BE}$  above the  $-V_{EE}$  voltage (approximately  $-15$  V<sub>DC</sub>).

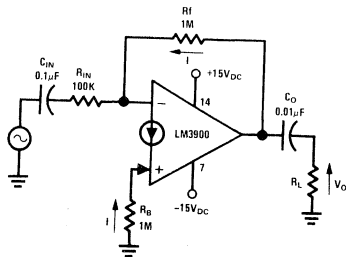


FIGURE 75. An AC Amplifier Operating with  $\pm 15$  V<sub>DC</sub>

With  $R_f = R_B$ ,  $V_O$  will bias at approximately 0 V<sub>DC</sub> to allow a maximum output voltage swing. As pin 7 is common to all four of the amplifiers which are in the same package, the other amplifiers are also biased for operation off of  $\pm 15$  V<sub>DC</sub>.

### 10.2.2 A DC Amplifier Operating with $\pm 15$ V<sub>DC</sub> Power Supplies

Biasing a DC amplifier is more difficult and requires that the  $\pm$  power supplies be complementary tracking (i.e.,  $|+V_{CC}| = |-V_{EE}|$ ). The operation of this biasing can be easier understood if we start by first considering the amplifier without including the feedback resistors, as shown in Figure 76. If  $R_1 = R_2 = R_3 + R_4 = 1$  M $\Omega$  and  $|+V_{CC}| = |-V_{EE}|$ , then the current,

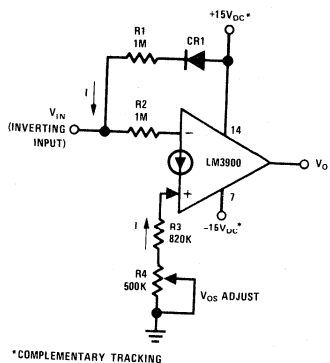


FIGURE 76. DC Biasing for  $\pm 15$  V<sub>DC</sub> Operation

$I$ , will bias  $V_{IN}$  at zero volts DC (resistor  $R_4$  can be used to adjust this). The diode,  $CR_1$ , has

been added for temperature compensation of this biasing. Now, if we include these biasing resistors, we have a DC amplifier with the input biased at approximately zero volts. If feedback resistors are added around this biased amplifier we get the schematic shown in Figure 77.

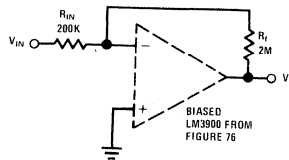


FIGURE 77. A DC Amplifier Operating with  $\pm 15$  V<sub>DC</sub>

This is a standard inverting DC amplifier connection. The (+) input is "effectively" at ground and the biasing shown in Figure 76 is used to take care of DC levels at the inputs.

## 10.3 Tachometers

Many pulse averaging tachometers can be built using the LM3900. Inputs can be voltage pulses, current pulses or the differentiated transitions of squarewaves. The DC output voltage can be made to increase with increasing input frequency, can be made proportional to twice the input frequency (frequency doubling for reduced output ripple), and can also be made proportional to either the sum or the difference between two input frequencies. Due to the small bias current and the high gain of the LM3900, the transfer function is linear between the saturation states of the amplifier.

### 10.3.1 A Basic Tachometer

If an RC averaging network is added from the output to the (-) input, the basic tachometer of Figure 78 results. Current pulse inputs will provide the desired transfer function shown on the figure. Each input current pulse causes a small change in the output voltage. Neglecting the effects of  $R$  we have

$$\Delta V_O \cong \frac{I \Delta t}{C}$$

The inclusion of  $R$  gives a discharge path so the output voltage does not continue to integrate, but rather provides the time dependency which is necessary to average the input pulses. If an additional signal source is simply placed in parallel with the one shown, the output becomes proportional to the sum of these input frequencies. If this additional source were applied to the (-) input, the output voltage would be proportional to the difference between these input frequencies. Voltage pulses can be converted to current pulses by using an input resistor. A series isolating diode should be used if

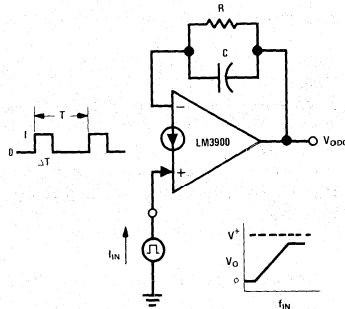


FIGURE 78. A Basic Tachometer

a signal is applied to the (-) input to prevent loading during the low voltage state of this input signal.

### 10.3.2 Extending $V_{OUT}$ (Minimum) to Ground

The output voltage of the circuit of Figure 78 does not go to ground level but has a minimum value which is equal to the  $V_{BE}$  of the (-) input ( $0.5 V_{DC}$ ). If it is desired that the output voltage go exactly to ground, the circuit of Figure 79 can be used. Now with  $V_{IN} = 0 V_{DC}$ ,  $V_O = 0V_{DC}$  due to the addition of the common-mode biasing resistors ( $180 k\Omega$ ). The diode,

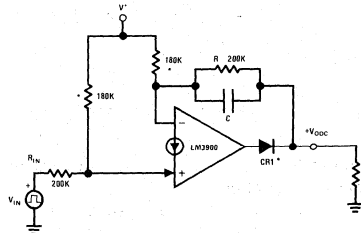


FIGURE 79. Adding Biasing to Provide  $V_O = 0 V_{DC}$

$CR_1$ , allows the output to go below  $V_{CE SAT}$  of the output, if desired (a load is required to provide a DC path for the biasing current flow via the R of the averaging network).

### 10.3.3 A Frequency Doubling Tachometer

To reduce the ripple on the DC output voltage, the circuit of Figure 80 can be used to effectively double the input frequency. Input pulses are not required, a squarewave is all that is needed. The operation of the circuit is to average the charge and discharge transient currents of the input capacitor,  $C_{IN}$ . The resistor,  $R_{IN}$ , is used to convert the voltage pulses to current pulses and to limit the surge currents (to approximately  $200 \mu A$  peak—or less if operating at high temperatures).

When the input voltage goes high, the charging current of  $C_{IN}$ ,  $I_{CHG}$  enters the (+) input, is mirrored about ground and is drawn from the RC averaging network into the (-) input terminal. When the input voltage goes back to ground, the discharge current of  $C_{IN}$ ,  $I_{DISCHARGE}$  will also be drawn from the RC averaging network via the now conducting diode,  $CR_1$ . This full wave action causes two current pulses to be drawn through the RC averaging network for each cycle of the input frequency.

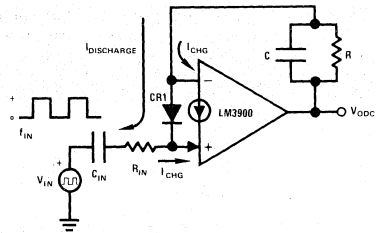


FIGURE 80. A Frequency Doubling Tachometer

### 10.4 A Squaring Amplifier

A squaring amplifier which incorporates symmetrical hysteresis above and below the zero output state (for noise immunity) is often needed to amplify the low level signals which are provided by variable reluctance transducers. In addition, a high frequency roll-off (low pass characteristic) is desirable both to reduce the natural voltage buildup at high frequencies and to also filter high frequency input noise disturbances. A simple circuit which accomplishes this function is shown in Figure 81. The input

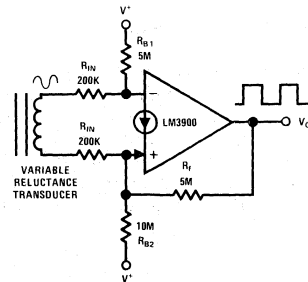


FIGURE 81. A Squaring Amplifier with Hysteresis

voltage is converted to input currents by using the input resistors,  $R_{IN}$ . Common-mode biasing is provided by  $R_{B1}$  and  $R_{B2}$ . Finally positive feedback (hysteresis) is provided by  $R_f$ . The large source resistance,  $R_{IN}$ , provides a low pass filter due to the "Miller-effect" input capacitance of the amplifier (approximately  $0.002 \mu F$ ). The amount of hysteresis and the symmetry about the zero volt input are controlled by the positive feedback resistor,  $R_f$ , and  $R_{B1}$  and  $R_{B2}$ .

With the values shown in Figure 81 the trip voltages are approximately  $\pm 150$  mV centered about the zero output voltage state of the transducer (at low frequencies where the low pass filter is not attenuating the input signal).

### 10.5 A Differentiator

An input differentiating capacitor can cause the input of the LM3900 to swing below ground and actuate the input clamp circuit. Again, common-mode biasing can be used to prevent this negative swing at the input terminals of the LM3900. The schematic of a differentiator circuit is shown in Figure 82. Common-mode

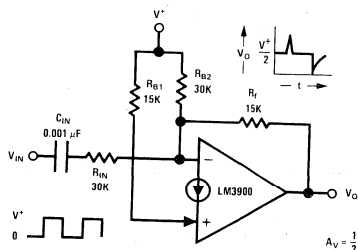


FIGURE 82. A Differentiator Circuit

biasing is provided by  $R_{B1}$  and  $R_{B2}$ . The feedback resistor,  $R_f$ , is one-half the value of  $R_{IN}$  so the gain is  $1/2$ . The output voltage will bias at  $V^+/2$  which thereby allows both a positive and a negative swing above and below this bias point. The resistor,  $R_{IN}$ , keeps the negative swing isolated from the (-) input terminal and therefore both inputs remain biased at  $+V_{BE}$ .

### 10.6 A Difference Integrator

A difference integrator is the basis of many of the sweep circuits which can be realized using the LM3900 operating on only a single power supply voltage. This circuit can also be used to provide the time integral of the difference between two input waveforms. The schematic of the difference integrator is shown in Figure 83.

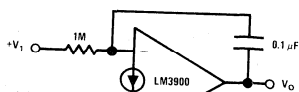


FIGURE 83. A Difference Integrator

This is a useful component for DC feedback loops as both the comparison to a reference and the integration take place in one amplifier.

## 10.7 A Low Drift Sample and Hold Circuit

In sample and hold applications a very low input biasing current is required. This is usually achieved by using a FET transistor or a special low input current IC op amp. The existence of many matched amplifiers in the same package allows the LM3900 to provide some interesting low "equivalent" input biasing current applications.

### 10.7.1 Reducing the "Effective" Input Biasing Current

One amplifier can be used to bias one or more additional amplifiers as shown in Figure 84.

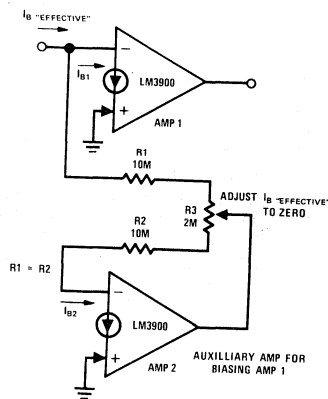


FIGURE 84. Reducing  $I_B$  "Effective" to Zero

The input terminal of Amp. 1 will only need to supply the signal current if the DC biasing current,  $I_{B1}$ , is accurately supplied via  $R_1$ . The adjustment,  $R_3$ , allows a zeroing of " $I_B$  effective" but simply omitting  $R_3$  and letting  $R_1 = R_2$  (and relying on amplifier symmetry) can cause  $I_B$  "effective" to be less than  $I_B/10$  (3 nA). This is useful in circuit applications such as sample and hold, where small values of  $I_B$  "effective" are desirable.

### 10.7.2 A Low Drift Ramp and Hold Circuit

The input current reduction technique of the previous section allows a relatively simple ramp and hold circuit to be built which can be ramped up or down or allowed to remain at any desired output DC level in a "hold" mode. This is shown in Figure 85. If both inputs are at  $0 V_{DC}$  the circuit is in a hold mode. Raising either input will cause the DC output voltage to ramp either up or down depending on which one goes positive. The slope is a function of the magnitude of the input voltage and additional inputs can be placed in parallel, if desired, to increase the input control variables.

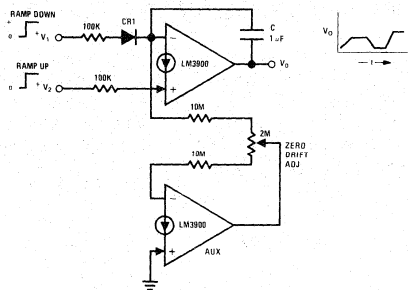


FIGURE 85. A Low-drift Ramp and Hold Circuit

### 10.7.3 Sample-and Compare with New $+V_{IN}$

An example of using the circuit of the previous section is shown in Figure 86 where clamping transistors,  $Q_1$  and  $Q_2$ , put the circuit in a hold mode when they are driven ON. When OFF the output voltage of Amp. 1 can ramp either up or down as needed to guarantee that the output voltage which is applied to Amp. 3. Resistor  $R_1$  provides a fixed "down" ramp current which is balanced or controlled via the comparator, Amp. 3, and the resistor  $R_4$ . When  $Q_1$  and  $Q_2$  are OFF a feedback loop guarantees that  $V_{O1}$  (from Amp. 1) is equal to  $+V_{IN}$  (to Amp. 3). Amplifier 2 is used to supply the input biasing current to Amp. 1.

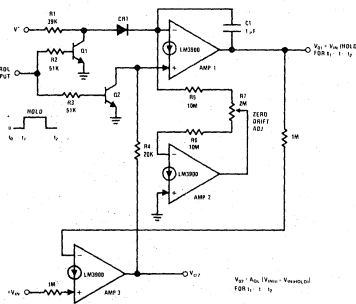


FIGURE 86. Sample-and Hold and Compare with New  $+V_{IN}$

The stored voltage appears at the output,  $V_{O1}$  of Amp. 1, and as Amp. 3 is active, a continued comparison is made between  $V_{O1}$  and  $V_{IN}$  and the output of Amp. 3 fully switches based on this comparison. A second loop could force  $V_{IN}$  to be maintained at the stored value ( $V_{O1}$ ) by making use of  $V_{O2}$  as an error signal for this second loop. Therefore, a control system could be manually controlled to bring it to a particular operating condition; then, by exercising the hold control, the system would maintain this operating condition due to the analog memory provided by  $V_{O1}$ .

### 10.8 Audio Mixer or Channel Selector

The multiple amplifiers of the LM3900 can be used for audio mixing (many amplifiers simultaneously providing signals which are added to generate a composite output signal) or for channel selection (only one channel enabled at a time). Three amplifiers are shown being summed into a fourth amplifier in Figure 87.

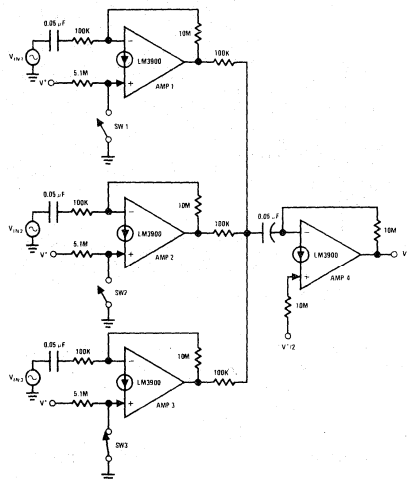


FIGURE 87. Audio Mixing or Selection

If a power amplifier were available, all four amplifiers could feed the single input of the power amplifier. For audio mixing all amplifiers are simultaneously active. Particular amplifiers can be gated OFF by making use of DC control signals which are applied to the (+) inputs to provide a channel select feature. As shown on Figure 87, Amp. 3 is active (as sw 3 is closed) and Amps. 1 and 2 are driven to positive output voltage saturation by the 5.1M which is applied to the (+) inputs. The DC output voltage bias level of the active amplifier is approximately  $0.8 V_{DC}$  and could be raised if larger signal levels were to be accommodated. Frequency shaping networks can be added either to the individual amplifiers or to the common amplifier, as desired. Switching transients may need to be filtered at the DC control points if the output amplifier is active during the switching intervals.

### 10.9 A Low Frequency Mixer

The diode which exists at the (+) input can be used for non-linear signal processing. An example of this is a mixer which allows two input frequencies to produce a sum and difference frequency (in addition to other high frequency

components). Using the amplifier of the LM3900, gain and filtering can also be accomplished with the same circuit in addition to the high input impedance and low output impedance advantages. The schematic of Figure 88 shows a mixer with a gain of 10 and a low pass single pole filter (1M and 150 pF feedback elements) with a corner frequency of 1 kHz. With

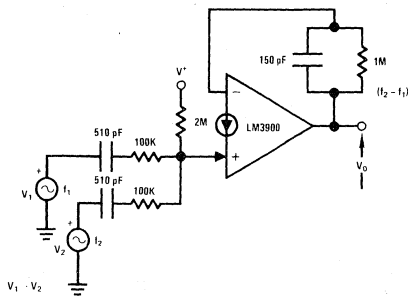


FIGURE 88. A Low Frequency Mixer

one signal larger in amplitude, to serve as the local oscillator input ( $V_1$ ), the transconductance of the input diode is gated at this rate ( $f_1$ ). A smaller signal ( $V_2$ ) can now be added at the second input and the difference frequency is filtered from the composite resulting waveform and is made available at the output. Relatively high frequencies can be applied at the inputs as long as the desired difference frequency is within the bandwidth capabilities of the amplifier and the RC low pass filter.

### 10.10 A Peak Detector

A peak detector is often used to rapidly charge a capacitor to the peak value of an input waveform. The voltage drop across the rectifying diode is placed within the feedback loop of an op amp to prevent voltage losses and temperature drifts in the output voltage. The LM3900 can be used as a peak detector as shown in Figure 89. The feedback resistor,  $R_f$ , is kept

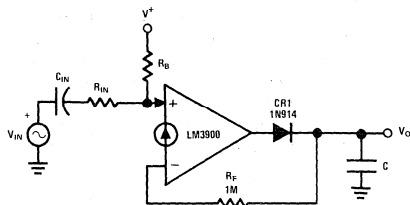


FIGURE 89. A Peak Detector

small (1 M $\Omega$ ) so that the 30 nA base current will cause only a +30 mV error in  $V_O$ . This

feedback resistor is constantly loading C in addition to the current drawn by the circuitry which samples  $V_O$ . These loading effects must be considered when selecting a value for C.

The biasing resistor,  $R_B$ , allows a minimum DC voltage to exist across the capacitor and the input resistor,  $R_{IN}$ , can be selected to provide gain to the input signal.

## 10.11 Power Circuits

The amplifier of the LM3900 will source a maximum current of approximately 10 mA and will sink maximum currents of approximately 80 mA (if overdriven at the (-) input). If the output is driven to a saturated state to reduce device dissipation, some interesting power circuits can be realized. These maximum values of current are typical values for the unit operating at 25°C and therefore have to be de-rated for reliable operation. For fully switched operation, amplifiers can be paralleled to increase current capability.

### 10.11.1 Lamp and/or Relay Drivers ( $\leq 30$ mA)

Low power lamps and relays (as reed relays) can be directly controlled by making use of the larger value of sink current than source current. A schematic is shown in Figure 90 where the input resistor, R, is selected such that  $V_{IN}$  supplies at least 0.1 mA of input current.

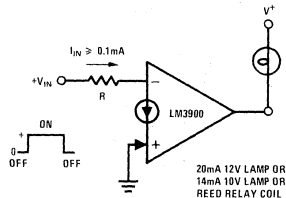


FIGURE 90. Sinking 20 to 30 mA Loads

### 10.11.2 Lamp and/or Relay Drivers ( $\leq 300$ mA)

To increase the power capability, an external transistor can be added as shown in Figure 91. The resistors  $R_1$  and  $R_2$  hold  $Q_1$  OFF when the output of the LM3900 is high. The resistor,  $R_2$ , limits the base drive when  $Q_1$  goes ON. It is required that pin 14 tie to the same power supply as the emitter of  $Q_1$  to guarantee that  $Q_1$  can be held OFF. If an inductive load is used, such as a relay coil, a backswing diode should be added to prevent large inductive voltage kicks during the switching interval, ON to OFF.

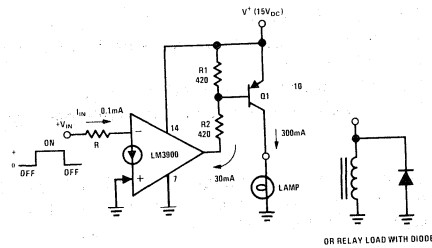


FIGURE 91. Boosting to 300 mA Loads

### 10.11.3 Positive Feedback Oscillators

If the LM3900 is biased into the active region and a resonant circuit is connected from the output to the (+) input, a positive feedback oscillator results. A driver for a piezoelectric transducer (a warning type of noise maker) is shown in Figure 92. The resistors  $R_1$  and  $R_2$  bias the output voltage at  $V^+/2$  and keep the amplifier active. Large currents can be entered into the (+) input and negative currents (or currents out of this terminal) are provided by the epi-substrate diode of the IC fabrication.

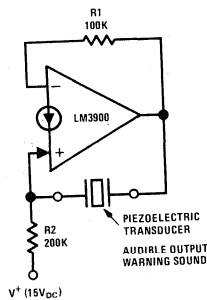


FIGURE 92. Positive Feedback Power Oscillators

When one of the amplifiers is operated in this large negative input current mode, the other amplifiers will be disturbed due to interaction. Multiple sounds may be generated as a result of using two or more transducers in various combinations, but this has not been investigated. Other two-terminal RC, RLC or piezoelectric resonators can be connected in this circuit to produce an oscillator.

### 10.12 High Voltage Operation

The amplifiers of the LM3900 can drive an external high voltage NPN transistor to provide a larger output voltage swing (as for an electrostatic CRT deflection system) or to operate off of an existing high voltage power supply (as the +98 V<sub>DC</sub> rectified line). Examples of both type of circuits are presented in this section.

### 10.12.1 A High Voltage Inverting Amplifier

An inverting amplifier with an output voltage swing from essentially 0 V<sub>DC</sub> to +300 V<sub>DC</sub> is shown in Figure 93. The transistor,  $Q_1$ , must be a high breakdown device as it will have the full HV supply across it. The biasing resistor  $R_3$  is used to center the transfer characteristic and the gain is the ratio of  $R_2$  to  $R_1$ . The load resistor,  $R_L$ , can be increased, if desired, to reduce the HV current drain.

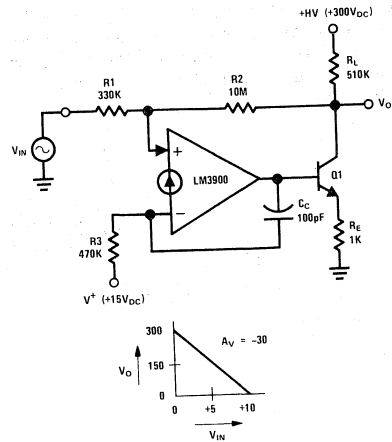


FIGURE 93. A High Voltage Inverting Amplifier

### 10.12.2 A High Voltage Non-inverting Amplifier

A high voltage non-inverting amplifier is shown in Figure 94. Common-mode biasing resistors

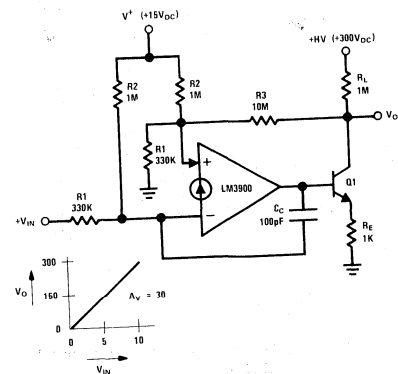


FIGURE 94. A High Voltage Non-inverting Amplifier

( $R_2$ ) are used to allow  $V_{IN}$  to go to 0 V<sub>DC</sub>. The output voltage,  $V_O$ , will not actually go to zero due to  $R_E$ , but should go to approximately

0.3  $V_{DC}$ . Again, the gain is 30 and a range of the input voltage of from 0 to +10  $V_{DC}$  will cause the output voltage to range from approximately 0 to +300  $V_{DC}$ .

### 10.12.3 A Line Operated Audio Amplifier

An audio amplifier which operates off a +98  $V_{DC}$  power supply (the rectified line voltage) is often used in consumer products. The external high voltage transistor,  $Q_1$  of Figure 95, is biased and controlled by the LM3900. The magnitude of the DC biasing voltage which appears across the emitter resistor of  $Q_1$  is controlled by the resistor which is placed from the (-) input to ground.

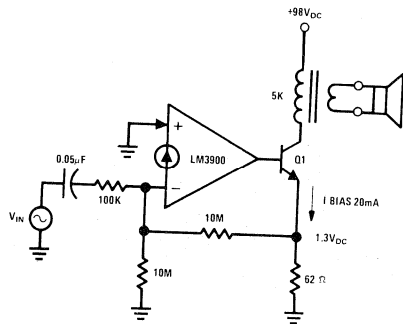


FIGURE 95. A Line Operated Audio Amplifier

### 10.13 A Dual-channel Class-A Driver for Auto Radios

A germanium power transistor is widely used in automotive class A audio amplifiers. As shown in Figure 96, two amplifiers can be cascaded

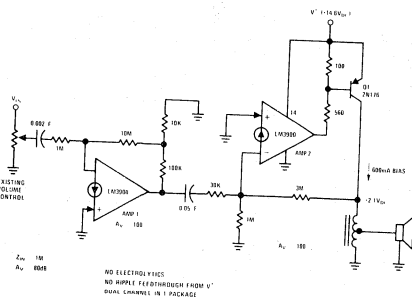


FIGURE 96. A Dual-channel IC Driver for Class A Car Radios

to bias and to control the 2N176 power transistor. This circuit has many advantages over the standard discrete circuit which is used as:

- 1.) No electrolytic capacitors are used.
- 2.) The ripple on the power supply line is rejected.

- 3.) The input impedance is high ( $1 M\Omega$ ).
- 4.) A large closed loop gain is easily achieved (80 dB).
- 5.) The slow start-up delay is eliminated.
- 6.) Two channels are available in one package.

Again, the pin 14 voltage must be at least as high as the power supply used at the emitter of  $Q_1$  to guarantee an OFF control for  $Q_1$ .

### 10.14 Temperature Sensing

The LM3900 can be used to monitor the junction temperature of the monolithic chip as shown in Figure 97(a). Amp. 1 will generate an output voltage which can be designed to undergo a large negative temperature change by design of  $R_1$  and  $R_2$ . The second amplifier compares this temperature dependent voltage with the power supply voltage and goes high at a designed maximum  $T_j$  of the IC.


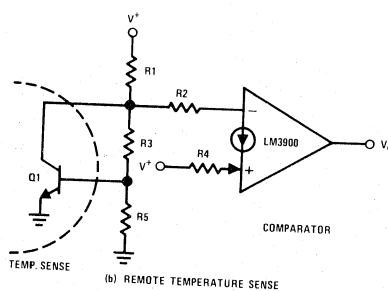


FIGURE 97. Temperature Sensing

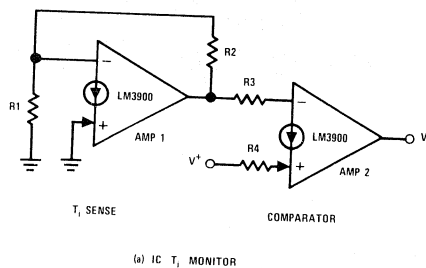For remote sensing, an NPN transistor,  $Q_1$  of Figure 97(b), is connected as an  $N V_{BE}$  generator (with  $R_3$  and  $R_5$ ) and is biased via  $R_1$  from the power supply voltage,  $V^+$ . The LM3900 again compares this temperature dependent voltage with the supply voltage and can be designed to have  $V_O$  go high at a maximum temperature of the remote temperature sensor,  $Q_1$ .



### 10.15 A "Programmable Unijunction"

If a diode is added to the Schmitt-trigger, a "programmable unijunction" function can be obtained as shown in Figure 98. For a low input voltage, the output voltage of the LM3900 is high and CR1 is OFF. When the input voltage rises to the high trip voltage, the output falls to essentially 0V and CR1 goes ON to discharge the input capacitor, C. The low trip voltage

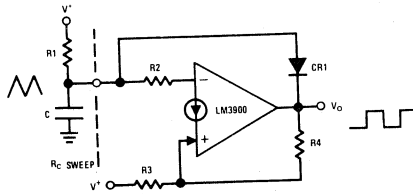


FIGURE 98. A "Programmable Unijunction"

must be larger than approximately 1V to guarantee that the forward drop of CR1 added to the output voltage of the LM3900 will be less than the low trip voltage. The discharge current can be increased by using smaller values for  $R_2$  to provide pull down currents larger than the 1.3 mA bias current source. The trip voltages of the Schmitt-Trigger are designed as shown in section 9.7.

### 10.16 Adding a Differential Input Stage

A differential amplifier can be added to the input of the LM3900 as shown in Figure 99.

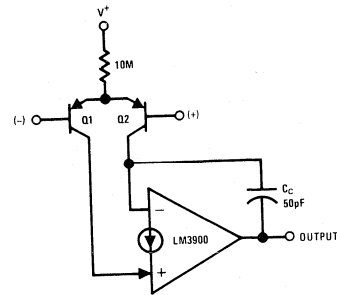


FIGURE 99. Adding a Differential Input Stage

This will increase the gain and reduce the offset voltage. Frequency compensation can be added as shown. The  $BV_{EBO}$  limit of the input transistors must not be exceeded during a large differential input condition, or diodes and input limiting resistors should be added to restrict the input voltage which is applied to the bases of  $Q_1$  and  $Q_2$  to  $\pm V_D$ .

The input common-mode voltage range does not go exactly to ground as a few tenths of a volt are needed to guarantee that  $Q_1$  or  $Q_2$  will not saturate and cause a phase change (and a resulting latch-up). The input currents will be small, but could be reduced further, if desired, by using FETS for  $Q_1$  and  $Q_2$ . This circuit can also be operated off of  $\pm 15 V_{DC}$  supplies.



# LM139/LM239/LM339 — A Quad of Independently Functioning Comparators

National Semiconductor  
Application Note 74  
R. T. Smathers  
T. M. Frederiksen  
W. M. Howard  
January 1973



## INTRODUCTION

The LM139/LM239/LM339 family of devices is a monolithic quad of independently functioning comparators designed to meet the needs for a medium speed, TTL compatible comparator for industrial applications. Since no antisaturation clamps are used on the output such as a Baker clamp or other active circuitry, the output leakage current in the OFF state is typically 0.5 nA. This makes the device ideal for system applications where it is desired to switch a node to ground while leaving it totally unaffected in the OFF state.

Other features include single supply, low voltage operation with an input common mode range from ground up to approximately one volt below  $V_{CC}$ . The output is an uncommitted collector so it may be used with a pull-up resistor and a separate output supply to give switching levels from any voltage up to 36V down to a  $V_{CE\text{SAT}}$  above ground (approx. 100 mV), sinking currents up to 15 mA. In addition it may be used as a single pole switch to ground, leaving the switched node unaffected while in the OFF state. Power dissipation with all four comparators in the OFF state is typically 4 mW from a single 5V supply (1 mW/comparator).

## CIRCUIT DESCRIPTION

Figure 1 shows the basic input stage of one of the four comparators of the LM139. Transistors  $Q_1$

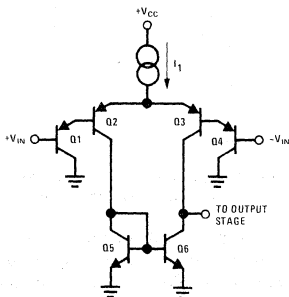


FIGURE 1. Basic LM139 Input Stage

through  $Q_4$  make up a PNP Darlington differential input stage with  $Q_5$  and  $Q_6$  serving to give single-ended output from differential input with no loss in gain. Any differential input at  $Q_1$  and  $Q_4$  will be amplified causing  $Q_6$  to switch OFF or ON depending on input signal polarity. It can easily

be seen that operation with an input common mode voltage of ground is possible. With both inputs at ground potential, the emitters of  $Q_1$  and  $Q_4$  will be at one  $V_{BE}$  above ground and the emitters of  $Q_2$  and  $Q_3$  at  $2 V_{BE}$ . For switching action the base of  $Q_5$  and  $Q_6$  need only go to one  $V_{BE}$  above ground and since  $Q_2$  and  $Q_3$  can operate with zero volts collector to base, enough voltage is present at a zero volt common mode input to insure comparator action. The bases should not be taken more than several hundred millivolts below ground, however, to prevent forward biasing a substrate diode which would stop all comparator action and possibly damage the device. If very large input currents were provided.

Figure 2 shows the comparator with the output stage added. Additional voltage gain is taken

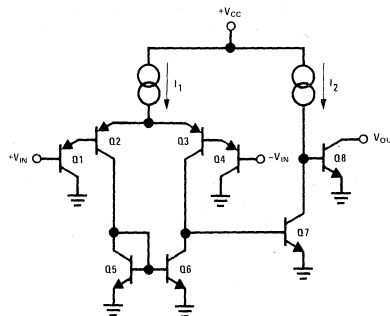


FIGURE 2. Basic LM139 Comparator

through  $Q_7$  and  $Q_8$  with the collector of  $Q_8$  left open to offer a wide variety of possible applications. The addition of a large pull-up resistor from the collector of  $Q_8$  to either  $+V_{CC}$  or any other supply up to 36V both increases the LM139 gain and makes possible output switching levels to match practically any application. Several outputs may be tied together to provide an ORing function or the pull-up resistor may be omitted entirely with the comparator then serving as a SPST switch to ground.

Output transistor  $Q_8$  will sink up to 15 mA before the output ON voltage rises above several hundred millivolts. The output current sink capability may be boosted by the addition of a discrete transistor at the output.

The complete circuit for one comparator of the LM139 is shown in Figure 3. Current sources  $I_3$

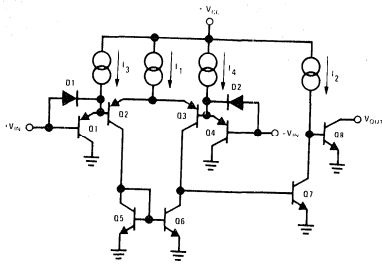


FIGURE 3. Complete LM139 Comparator Circuit

and  $I_4$  are added to help charge any parasitic capacitance at the emitters of  $Q_1$  and  $Q_4$  to improve the slew rate of the input stage. Diodes  $D_1$  and  $D_2$  are added to speed up the voltage swing at the emitters of  $Q_1$  and  $Q_2$  for large input voltage swings.

Biasing for current sources  $I_1$  through  $I_4$  is shown in Figure 4. When power is first applied to the circuit, current flows through the JFET  $Q_{13}$  to bias up diode  $D_5$ . This biases transistor  $Q_{12}$  which turns ON transistors  $Q_9$  and  $Q_{10}$  by allowing a path to ground for their base and collector currents.

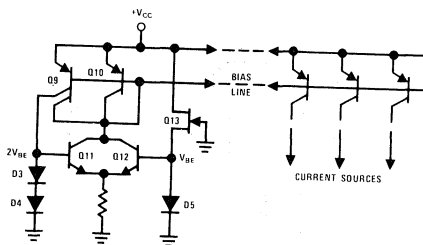


FIGURE 4. Current Source Biasing Circuit

Current from the left hand collector of  $Q_9$  flows through diodes  $D_3$  and  $D_4$  bringing up the base of  $Q_{11}$  to  $2 V_{BE}$  above ground and the emitters of  $Q_{11}$  and  $Q_{12}$  to one  $V_{BE}$ .  $Q_{12}$  will then turn OFF because its base emitter voltage goes to zero. This is the desired action because  $Q_9$  and  $Q_{10}$  are biased ON through  $Q_{11}$ ,  $D_3$  and  $D_4$  so  $Q_{12}$  is no longer needed. The "bias line" is now sitting at a  $V_{BE}$  below  $+V_{CC}$  which is the voltage needed to bias the remaining current sources in the LM139 which will have a constant bias regardless of  $+V_{CC}$  fluctuations. The upper input common mode voltage is  $V_{CC}$  minus the saturation voltage of the current sources (approximately 100 mV) minus the  $2 V_{BE}$  of the input devices  $Q_1$  and  $Q_2$  (or  $Q_3$  and  $Q_4$ ).

## COMPARATOR CIRCUITS

Figure 5 shows a basic comparator circuit for converting low level analog signals to a high level digital output. The output pull-up resistor should be chosen high enough so as to avoid excessive power dissipation yet low enough to supply enough drive to switch whatever load circuitry is used on the comparator output. Resistors  $R_1$  and  $R_2$  are used to set the input threshold trip voltage ( $V_{REF}$ ) at any value desired within the input common mode range of the comparator.

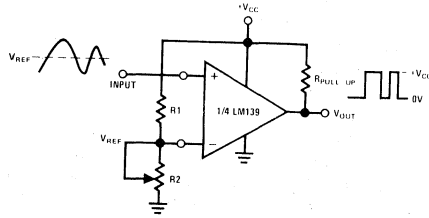


FIGURE 5. Basic Comparator Circuit

## Comparators with Hysteresis

The circuit shown in Figure 5 suffers from one basic drawback in that if the input signal is a slowly varying low level signal, the comparator may be forced to stay within its linear region between the output high and low states for an undesirable length of time. If this happens, it runs the risk of oscillating since it is basically an uncompensated, high gain op amp. To prevent this, a small amount of positive feedback or hysteresis is added around the comparator. Figure 6 shows a

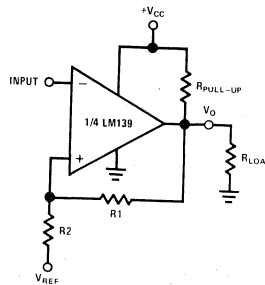


FIGURE 6. Comparator with Positive Feedback to Improve Switching Time

comparator with a small amount of positive feedback. In order to insure proper comparator action, the components should be chosen as follows:

$$R_{PULL-UP} < R_{LOAD} \text{ and}$$

$$R_1 > R_{PULL-UP}$$

This will insure that the comparator will always switch fully up to  $+V_{CC}$  and not be pulled down by the load or feedback. The amount of feedback is chosen arbitrarily to insure proper switching with the particular type of input signal used. If the

output swing is 5V, for example, and it is desired to feedback 1% or 50 mV, then  $R_1 \approx 100 R_2$ . To describe circuit operation, assume that the inverting input goes above the reference input ( $V_{IN} > V_{REF}$ ). This will drive the output,  $V_O$ , towards ground which in turn pulls  $V_{REF}$  down through  $R_1$ . Since  $V_{REF}$  is actually the non-inverting input to the comparator, it too will drive the output towards ground insuring the fastest possible switching time regardless of how slow the input moves. If the input then travels down to  $V_{REF}$ , the same procedure will occur only in the opposite direction insuring that the output will be driven hard towards  $+V_{CC}$ .

Putting hysteresis in the feedback loop of the comparator has far more use, however, than simply as an oscillation suppressor. It can be made to function as a Schmitt trigger with presettable trigger points. A typical circuit is shown in Figure 7. Again, the hysteresis is achieved by shifting the reference voltage at the positive input when the output voltage  $V_O$  changes state. This network

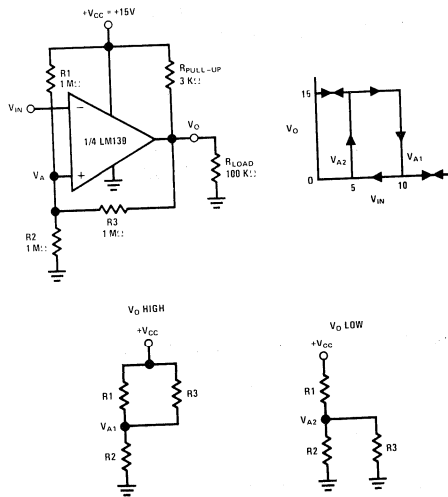


FIGURE 7. Inverting Comparator with Hysteresis

requires only three resistors and is referenced to the positive supply  $+V_{CC}$  of the comparator. This can be modeled as a resistive divider,  $R_1$  and  $R_2$ , between  $+V_{CC}$  and ground with the third resistor,  $R_3$ , alternately connected to  $+V_{CC}$  or ground, paralleling either  $R_1$  or  $R_2$ . To analyze this circuit, assume that the input voltage,  $V_{IN}$ , at the inverting input is less than  $V_A$ . With  $V_{IN} \leq V_A$  the output will be high ( $V_O = +V_{CC}$ ). The upper input trip voltage,  $V_{A1}$ , is defined by:

$$V_{A1} = \frac{+V_{CC} R_2}{(R_1 \parallel R_3) + R_2}$$

or

$$V_{A1} = \frac{+V_{CC} R_2 (R_1 + R_3)}{R_1 R_2 + R_1 R_3 + R_2 R_3} \quad (1)$$

When the input voltage  $V_{IN}$ , rises above the reference voltage ( $V_{IN} > V_{A1}$ ), voltage,  $V_O$ , will go low ( $V_O = \text{GND}$ ). The lower input trip voltage,  $V_{A2}$ , is now defined by:

$$V_{A2} = \frac{+V_{CC} R_2 \parallel R_3}{R_1 + R_2 \parallel R_3}$$

or

$$V_{A2} = \frac{+V_{CC} R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} \quad (2)$$

When the input voltage,  $V_{IN}$ , decreases to  $V_{A2}$  or lower, the output will again switch high. The total hysteresis,  $\Delta V_A$ , provided by this network is defined by:

$$\Delta V_A = V_{A1} - V_{A2}$$

or, subtracting equation 2 from equation 1

$$\Delta V_A = \frac{+V_{CC} R_1 R_2}{R_1 R_2 + R_1 R_3 + R_2 R_3} \quad (3)$$

To insure that  $V_O$  will swing between  $+V_{CC}$  and ground, choose:

$$R_{\text{PULL-UP}} < R_{\text{LOAD}} \quad \text{and} \quad (4)$$

$$R_3 > R_{\text{PULL-UP}} \quad (5)$$

Heavier loading on  $R_{\text{PULL-UP}}$  (i.e. smaller values of  $R_3$  or  $R_{\text{LOAD}}$ ) simply reduces the value of the maximum output voltage thereby reducing the amount of hysteresis by lowering the value of  $V_{A1}$ . For simplicity, we have assumed in the above equations that  $V_O$  high switches all the way up to  $+V_{CC}$ .

To find the resistor values needed for a given set of trip points, we first divide equation (3) by equation (2). This gives us the ratio:

$$\frac{\Delta V_A}{V_{A2}} = \frac{1 + \frac{R_1}{R_3} + \frac{R_1}{R_2}}{1 + \frac{R_3}{R_2} + \frac{R_3}{R_1}} \quad (6)$$

If we let  $R_1 = n R_3$ , equation (6) becomes:

$$\frac{\Delta V_A}{V_{A2}} = n \quad (7)$$

We can then obtain an expression for  $R_2$  from equation (1) which gives

$$R_2 = \frac{R_1 \parallel R_3}{\frac{+V_{CC}}{V_{A1}} - 1} \quad (8)$$

The following design example is offered:

Given:  $V^+ = +15V$   
 $R_{LOAD} = 100\text{ k}\Omega$   
 $V_{A1} = +10V$   
 $V_{A2} = +5V$

To find:  $R_1, R_2, R_3, R_{PULL-UP}$

Solution:

From equation (4)  $R_{PULL-UP} < R_{LOAD}$

$$R_{PULL-UP} < 100\text{ k}\Omega$$

so let

$$R_{PULL-UP} = 3\text{ k}\Omega$$

From equation (5)  $R_3 > R_{LOAD}$

$$R_3 > 100\text{ k}\Omega$$

so let

$$R_3 = 1\text{ M}\Omega$$

$$\text{From equation (7) } n = \frac{\Delta V_A}{V_{A2}} = \frac{10-5}{5} = 1$$

and since

$$R_1 = nR_3$$

this gives

$$R_1 = 1R_3 = 1\text{ M}\Omega$$

$$\text{From equation (8) } R_2 = \frac{500\text{ k}\Omega}{\frac{15}{10} - 1} = 1\text{ M}\Omega$$

These are the values shown in Figure 7.

The circuit shown in Figure 8 is a non-inverting comparator with hysteresis which is obtained with only two resistors,  $R_1$  and  $R_2$ . In contrast to the first method, however, this circuit requires a separate reference voltage at the negative input. The trip voltage,  $V_A$ , at the positive input is shifted about  $V_{REF}$  as  $V_O$  changes between  $+V_{CC}$  and ground.

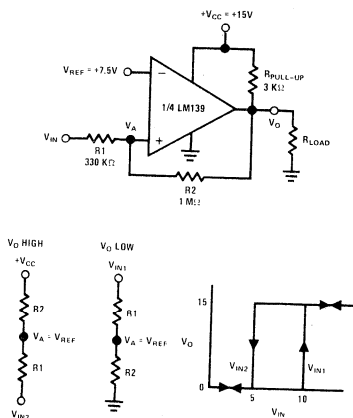


FIGURE 8. Non-Inverting Comparator with Hysteresis

Again for analysis, assume that the input voltage,  $V_{IN}$ , is low so that the output,  $V_O$ , is also low

( $V_O = \text{GND}$ ). For the output to switch,  $V_{IN}$  must rise up to  $V_{IN1}$  where  $V_{IN1}$  is given by:

$$V_{IN1} = \frac{V_{REF}(R_1 + R_2)}{R_2} \quad (9)$$

As soon as  $V_O$  switches to  $+V_{CC}$ ,  $V_A$  will step to a value greater than  $V_{REF}$  which is given by:

$$V_A = V_{IN} + \frac{(V_{CC} - V_{IN1})R_1}{R_1 + R_2} \quad (10)$$

To make the comparator switch back to its low state ( $V_O = \text{GND}$ )  $V_{IN}$  must go below  $V_{REF}$  before  $V_A$  will again equal  $V_{REF}$ . This lower trip point is now given by:

$$V_{IN2} = \frac{V_{REF}(R_1 + R_2) - V_{CC}R_1}{R_2} \quad (11)$$

The hysteresis for this circuit,  $\Delta V_{IN}$ , is the difference between  $V_{IN1}$  and  $V_{IN2}$  and is given by:

$$\Delta V_{IN} = V_{IN1} - V_{IN2} =$$

$$\frac{V_{REF}(R_1 + R_2)}{R_2} - \frac{V_{REF}(R_1 + R_2) - V_{CC}R_1}{R_2}$$

or

$$\Delta V_{IN} = \frac{V_{CC}R_1}{R_2} \quad (12)$$

As a design example consider the following:

Given:  $R_{LOAD} = 100\text{ k}\Omega$   
 $V_{IN1} = 10V$   
 $V_{IN2} = 5V$   
 $+V_{CC} = 15V$

To find:  $V_{REF}, R_1, R_2$  and  $R_3$

Solution:

Again choose  $R_{PULL-UP} < R_{LOAD}$  to minimize loading, so let

$$R_{PULL-UP} = 3\text{ k}\Omega$$

$$\text{From equation (12) } \frac{R_1}{R_2} = \frac{\Delta V_{IN}}{V_{CC}}$$

$$\frac{R_1}{R_2} = \frac{10-5}{15} = \frac{1}{3}$$

$$R_1 = \frac{R_2}{3}$$

$$\text{From equation (9) } V_{REF} = \frac{10}{1 + \frac{R_1}{R_2}}$$

$$V_{REF} = \frac{V_{IN}}{1 + \frac{1}{3}} = 7.5V$$

To minimize output loading choose

$$R_2 > R_{PULL-UP}$$

or

$$R_2 > 3 \text{ k}\Omega$$

so let

$$R_2 = 1 \text{ M}\Omega$$

The value of  $R_1$  is now obtained from equation (12)

$$R_1 = \frac{R_2}{3}$$

$$R_1 = \frac{1 \text{ M}\Omega}{3} \cong 330 \text{ k}\Omega$$

These are the values shown in Figure 8.

### Limit Comparator with Lamp Driver

The limit comparator shown in Figure 9 provides a range of input voltages between which the output devices of both LM139 comparators will be OFF.

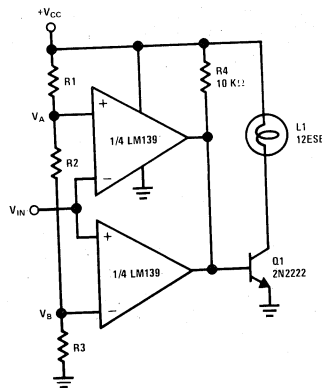


FIGURE 9. Limit Comparator with Lamp Driver

This will allow base current for  $Q_1$  to flow through pull-up resistor  $R_4$ , turning ON  $Q_1$  which lights the lamp. If the input voltage,  $V_{IN}$ , changes to a value greater than  $V_A$  or less than  $V_B$ , one of the comparators will switch ON, shorting the base of  $Q_1$  to ground, causing the lamp to go OFF. If a PNP transistor is substituted for  $Q_1$  (with emitter tied to  $+V_{CC}$ ) the lamp will light when the input is above  $V_A$  or below  $V_B$ .  $V_A$  and  $V_B$  are arbitrarily set by varying resistors  $R_1$ ,  $R_2$  and  $R_3$ .

### Zero Crossing Detector

The LM139 can be used to symmetrically square up a sine wave centered around zero volts by incorporating a small amount of positive feedback to improve switching times and centering the input threshold at ground (see Figure 10). Voltage divider  $R_4$  and  $R_5$  establishes a reference voltage,  $V_1$ , at the positive input. By making the series resistance,  $R_1$  plus  $R_2$  equal to  $R_5$ , the switching condition,  $V_1 = V_2$ , will be satisfied when  $V_{IN} = 0$ . The positive feedback resistor,  $R_6$ , is

made very large with respect to  $R_5$  ( $R_6 = 2000 R_5$ ). The resultant hysteresis established by this network is very small ( $\Delta V_1 < 10 \text{ mV}$ ) but it is sufficient to insure rapid output voltage transitions. Diode  $D_1$  is used to insure that

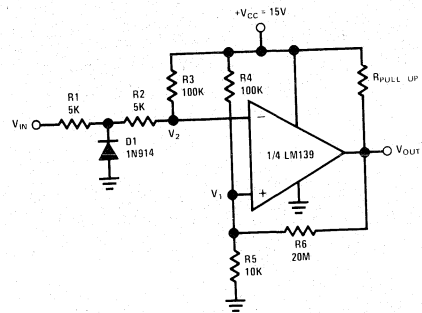


FIGURE 10. Zero Crossing Detector

the inverting input terminal of the comparator never goes below approximately  $-100 \text{ mV}$ . As the input terminal goes negative,  $D_1$  will forward bias, clamping the node between  $R_1$  and  $R_2$  to approximately  $-700 \text{ mV}$ . This sets up a voltage divider with  $R_2$  and  $R_3$  preventing  $V_2$  from going below ground. The maximum negative input overdrive is limited by the current handling ability of  $D_1$ .

### Comparing the Magnitude of Voltages of Opposite Polarity

The comparator circuit shown in Figure 11 compares the magnitude of two voltages,  $V_{IN1}$  and

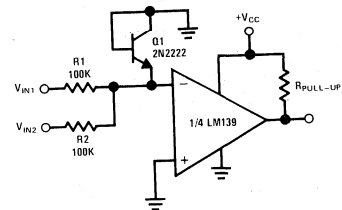


FIGURE 11. Comparing the Magnitude of Voltages of Opposite Polarity

$V_{IN2}$  which have opposite polarities. The resultant input voltage at the minus input terminal to the comparator,  $V_A$ , is a function of the voltage divider from  $V_{IN1}$  and  $V_{IN2}$  and the values of  $R_1$  and  $R_2$ . Diode connected transistor  $Q_1$  provides protection for the minus input terminal by clamping it at several hundred millivolts below ground. A 2N2222 was chosen over a 1N914 diode because of its lower diode voltage. If desired, a small amount of hysteresis may be added using the techniques described previously. Correct magnitude comparison can be seen as follows: Let  $V_{IN1}$  be the input for the positive polarity input voltage and  $V_{IN2}$  the input for the negative polarity. If the magnitude of  $V_{IN1}$  is greater than that

of  $V_{IN2}$  the output will go low ( $V_{OUT} = GND$ ). If the magnitude of  $V_{IN1}$  is less than that of  $V_{IN2}$ , however, the output will go high ( $V_{OUT} = V_{CC}$ ).

### Magnetic Transducer Amplifier

A circuit that will detect the zero crossings in the output of a magnetic transducer is shown in Figure 12. Resistor divider,  $R_1$  and  $R_2$ , biases the positive input at  $+V_{CC}/2$ , which is well within the common mode operating range. The minus input is biased through the magnetic transducer. This

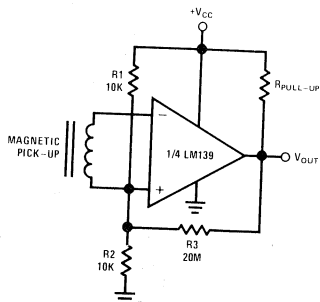


FIGURE 12. Magnetic Transducer Amplifier

allows large signal swings to be handled without exceeding the input voltage limits. A symmetrical square wave output is insured through the positive feedback resistor  $R_3$ . Resistors  $R_1$  and  $R_2$  can be used to set the DC bias voltage at the positive input at any desired voltage within the input common mode voltage range of the comparator.

### OSCILLATORS USING THE LM139

The LM139 lends itself well to oscillator applications for frequencies below several megacycles. Figure 13 shows a symmetrical square wave generator using a minimum of components. The output

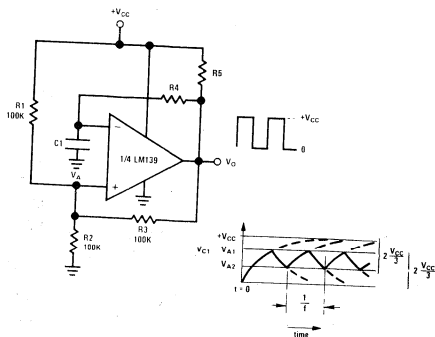


FIGURE 13. Square Wave Generator

frequency is set by the RC time constant of  $R_4$  and  $C_1$  and the total hysteresis of the loop is set by  $R_1$ ,  $R_2$  and  $R_3$ . The maximum frequency is limited only by the large signal propagation delay

of the comparator in addition to any capacitive loading at the output which would degrade the output slew rate.

To analyze this circuit assume that the output is initially high. For this to be true, the voltage at the negative input must be less than the voltage at the positive input. Therefore, capacitor  $C_1$  is discharged. the voltage at the positive input,  $V_{A1}$ , will then be given by:

$$V_{A1} = \frac{+V_{CC} R_2}{R_2 + (R_1 \parallel R_3)} \quad (13)$$

where if  $R_1 = R_2 = R_3$

$$\text{then } V_{A1} = \frac{2 V_{CC}}{3} \quad (14)$$

Capacitor  $C_1$  will charge up through  $R_4$  so that when it has charged up to a value equal to  $V_{A1}$ , the comparator output will switch. With the output  $V_O = GND$ , the value of  $V_A$  is reduced by the hysteresis network to a value given by:

$$V_{A2} = \frac{+V_{CC}}{3} \quad (15)$$

using the same resistor values as before. Capacitor  $C_1$  must now discharge through  $R_4$  towards ground. The output will return to its high state ( $V_O = +V_{CC}$ ) when the voltage across the capacitor has discharged to a value equal to  $V_{A2}$ . For the circuit shown, the period for one cycle of oscillation will be twice the time it takes for a single RC circuit to charge up to one half of its final value. The period can be calculated from:

$$V_1 = V_{MAX} e^{-t_1/RC} \quad (16)$$

where

$$V_{MAX} = \frac{2 V_{CC}}{3} \quad (17)$$

and

$$V_1 = \frac{V_{MAX}}{2} = \frac{V_{CC}}{3} \quad (18)$$

One period will be given by:

$$\frac{1}{\text{freq.}} = 2t_1 \quad (19)$$

or calculating the exponential gives

$$\frac{1}{\text{freq.}} = 2 (0.694) R_4 C_1 \quad (20)$$

Resistors  $R_3$  and  $R_4$  must be at least 10 times larger than  $R_5$  to insure that  $V_O$  will go all the way up to  $+V_{CC}$  in the high state. The frequency stability of this circuit should strictly be a function of the external components.



## Pulse Generator with Variable Duty Cycle

The basic square wave generator of Figure 13 can be modified to obtain an adjustable duty cycle pulse generator, as shown in Figure 14, by providing a separate charge and discharge path for capacitor  $C_1$ . One path, through  $R_4$  and  $D_1$  will charge the capacitor and set the pulse width ( $t_1$ ). The other path,  $R_5$  and  $D_2$ , will discharge the capacitor and set the time between pulses ( $t_2$ ). By varying resistor  $R_5$ , the time between pulses of the generator can be changed without changing the pulse width. Similarly, by varying  $R_4$ , the pulse width will be altered without affecting the time between pulses. Both controls will change the frequency of the generator, however. With the values

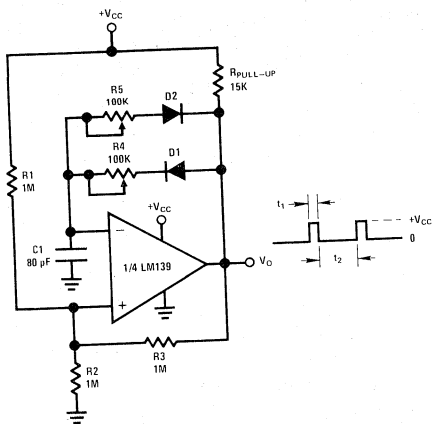


FIGURE 14. Pulse Generator with Variable Duty Cycle

given in Figure 14, the pulse width and time between pulses can be found from:

$$V_1 = V_{MAX} (1 - e^{-t_1/R_4 C_1}) \text{ risetime} \quad (21a)$$

$$V_1 = V_{MAX} e^{-t_2/R_5 C_1} \text{ falltime} \quad (21b)$$

where

$$V_{MAX} = \frac{2 V_{CC}}{3} \quad (22)$$

and

$$V_1 = \frac{V_{MAX}}{2} = \frac{V_{CC}}{3} \quad (23)$$

which gives

$$\frac{1}{2} = e^{-t_1/R_4 C_1} \quad (24)$$

$t_2$  is then given by:

$$\frac{1}{2} = e^{-t_2/R_5 C_1} \quad (25)$$

These terms will have a slight error due to the fact that  $V_{MAX}$  is not exactly equal to  $2/3 V_{CC}$  but is actually reduced by the diode drop to:

$$V_{MAX} = \frac{2}{3} (V_{CC} - V_{BE}) \quad (26)$$

therefore

$$\frac{1}{2(1 - V_{BE})} = e^{-t_1/R_4 C_1} \quad (27)$$

and

$$\frac{1}{2(1 - V_{BE})} = e^{-t_2/R_5 C_1} \quad (28)$$

## Crystal Controlled Oscillator

A simple yet very stable oscillator can be obtained by using a quartz crystal resonator as the feedback element. Figure 15 gives a typical circuit diagram

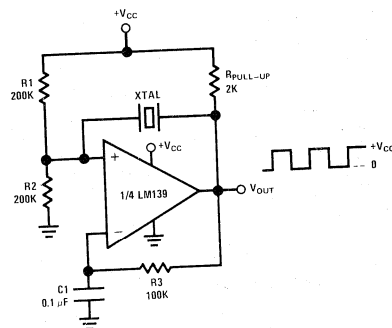


FIGURE 15. Crystal Controlled Oscillator

of this. This value of  $R_1$  and  $R_2$  are equal so that the comparator will switch symmetrically about  $+V_{CC}/2$ . The RC time constant of  $R_3$  and  $C_1$  is set to be several times greater than the period of the oscillating frequency, insuring a 50% duty cycle by maintaining a DC voltage at the inverting input equal to the absolute average of the output waveform.

When specifying the crystal, be sure to order series resonant along with the desired temperature coefficient and load capacitance to be used.

## MOS Clock Driver

The LM139 can be used to provide the oscillator and clock delay timing for a two phase MOS clock driver (see Figure 16). The oscillator is a standard comparator square wave generator similar to the one shown in Figure 13. Two other comparators

of the LM139 are used to establish the desired phasing between the two outputs to the clock driver. A more detailed explanation of the delay circuit is given in the section under "Digital and Switching Circuits."

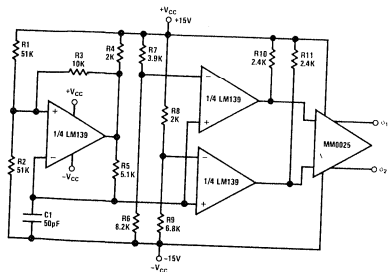


FIGURE 16. MOS Clock Driver

### Wide Range VCO

A simple yet very stable voltage controlled oscillator using a minimum of external components can be realized using three comparators of the LM139. The schematic is shown in Figure 17a. Comparator 1 is used closed loop as an integrator (for further discussion of closed loop operation see section on Operational Amplifiers) with comparator 2 used as a triangle to square wave converter and comparator 3 as the switch driving the integrator. To analyze the circuit, assume that comparator 2 is its high state ( $V_{SQ} = +V_{CC}$ ) which drives comparator 3 to its high state also. The out-

put device of comparator 3 will be OFF which prevents any current from flowing through  $R_2$  to ground. With a control voltage,  $V_C$ , at the input to comparator 1, a current  $I_1$  will flow through  $R_1$  and begin discharging capacitor  $C_1$ , at a linear rate. This discharge current is given by:

$$I_1 = \frac{V_C}{2 R_1} \quad (29)$$

and the discharge time is given by:

$$I_1 = C_1 \frac{\Delta V}{\Delta t} \quad (30)$$

$\Delta V$  will be the maximum peak change in the voltage across capacitor  $C_1$  which will be set by the switch points of comparator 2. These trip points can be changed by simply altering the ratio of  $R_F$  to  $R_S$ , thereby increasing or decreasing the amount of hysteresis around comparator 2. With  $R_F = 100 \text{ k}\Omega$  and  $R_S = 5 \text{ k}\Omega$ , the amount of hysteresis is approximately  $\pm 5\%$  which will give switch points of  $+V_{CC}/2 \pm 750 \text{ mV}$  from a 30V supply. (See "Comparators with Hysteresis").

As capacitor  $C_1$  discharges, the output voltage of comparator 1 will decrease until it reaches the lower trip point of comparator 2, which will then force the output of comparator 2 to go to its low state ( $V_{SQ} = \text{GND}$ ).

This in turn causes comparator 3 to go to its low state where its output device will be in saturation. A current  $I_2$  can now flow through resistor  $R_2$  to

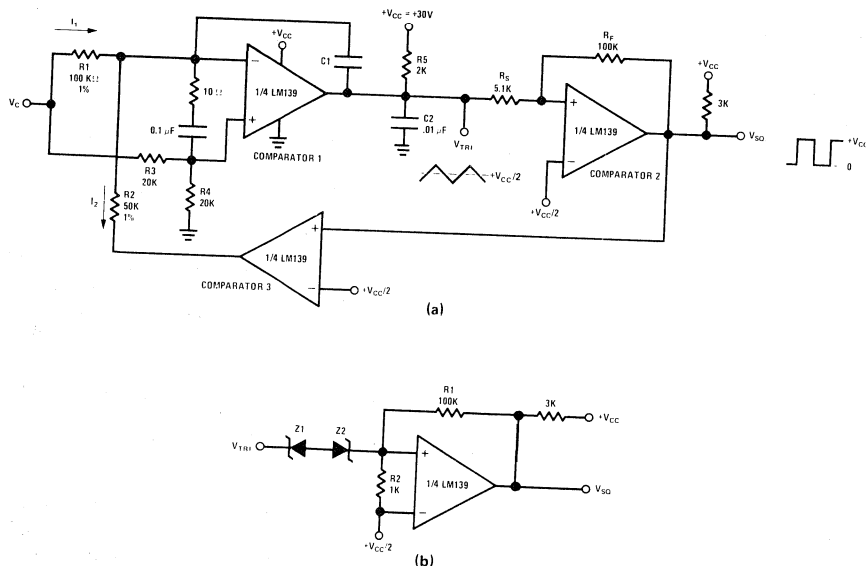


FIGURE 17. Voltage Controlled Oscillator

ground. If the value of  $R_2$  is chosen as  $R_1/2$  a current equal to the capacitor discharge current can be made to flow out of  $C_1$  charging it at the same rate as it was discharged. By making  $R_2 = R_1/2$ , current  $I_2$  will equal twice  $I_1$ . This is the control circuitry which guarantees a constant 50% duty cycle oscillation independent of frequency or temperature. As capacitor  $C_1$  charges, the output of comparator 1 will ramp up until it trips comparator 2 to its high state ( $V_{SQ} = +V_{CC}$ ) and the cycle will repeat.

The circuit shown in Figure 17a uses a +30V supply and gives a triangle wave of 1.5V peak-to-peak. With a timing capacitor,  $C_1$  equal to 500 pF, a frequency range from approximately 115 kHz down to approximately 670 Hz was obtained with a control voltage ranging from 50V down to 250 mV. By reducing the hysteresis around comparator 2 down to  $\pm 150$  mV ( $R_F = 100$  k $\Omega$ ,  $R_S = 1$  k $\Omega$ ) and reducing the compensating capacitor  $C_2$  down to .001  $\mu$ F, frequencies up to 1 MHz ( $f_o \leq 1$  Hz) the timing capacitor,  $C_1$ , should be increased up to approximately 1  $\mu$ F to insure that the charging currents,  $I_1$  and  $I_2$ , are much larger than the input bias currents of comparator 1.

Figure 17b shows another interesting approach to provide the hysteresis for comparator 2. Two identical Zener diodes,  $Z_1$  and  $Z_2$ , are used to set the trip points of comparator 2. When the triangle wave is less than the value required to Zener one of the diodes, the resistive network,  $R_1$  and  $R_2$ , provides enough feedback to keep the comparator in its proper state, (the input would otherwise be floating). The advantage of this circuit is that the trip points of comparator 2 will be completely independent of supply voltage fluctuations. The disadvantage is that Zeners with less than one volt breakdown voltage are not obtainable. This limits the maximum upper frequency obtainable because of the larger amplitude of the triangle wave. If a regulated supply is available, Figure 17a is preferable simply because of less parts count and lower cost.

Both circuits provide good control over at least two decades in frequency with a temperature coefficient largely dependent on the TC of the external timing resistors and capacitors. Remember that good circuit layout is essential along with the .01 $\mu$ F compensation capacitor at the output of comparator 1 and the series 10 $\Omega$ , resistor and 0.1 $\mu$ F capacitor between its inputs, for proper operation. Comparator 1 is a high gain amplifier used closed loop as an integrator so long leads and loose layout should be avoided.

#### DIGITAL AND SWITCHING CIRCUITS

The LM139 lends itself well to low speed (<1 MHz) high level logic circuits. They have the advantage of operating with high signal levels, giving high noise immunity, which is highly desirable for industrial applications. The output signal level

can be selected by setting the  $V_{CC}$  to which the pull-up resistor is connected to any desired level.

#### AND/NAND Gates

A three input AND gate is shown in Figure 18. Operation of this gate is as follows: resistor divider  $R_1$  and  $R_2$  establishes a reference voltage at the inverting input to the comparator. The non-inverting input is the sum of the voltages at the inputs divided by the voltage dividers comprised of  $R_3$ ,  $R_4$ ,  $R_5$  and  $R_6$ . The output will go high only

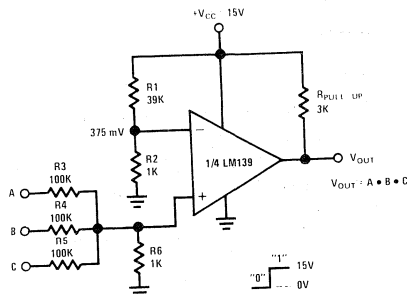


FIGURE 18. Three Input AND Gate

when all three inputs are high, causing the voltage at the non-inverting input to go above that at inverting input. The circuit values shown work for a "0" equal to ground and a "1" equal +15V. The resistor values can be altered if different logic levels are desired. If more inputs are required, diodes are recommended to improve the voltage margin when all but one of the inputs are the "1" state. This circuit with increased fan-in is shown in Figure 19.

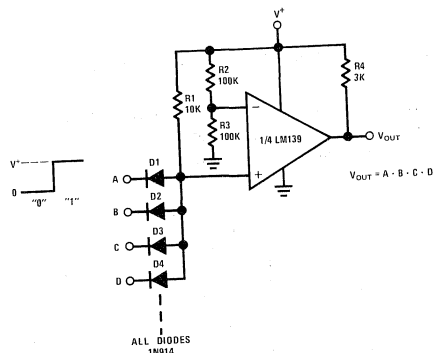


FIGURE 19. AND Gate with Large Fan-In

To convert these AND gates to NAND gates simply interchange the inverting and non-inverting inputs to the comparator. Hysteresis can be added to speed up output transitions if low speed input signals are used.

## OR/NOR Gates

The three input OR gate (positive logic) shown in Figure 20 is achieved from the basic AND gate

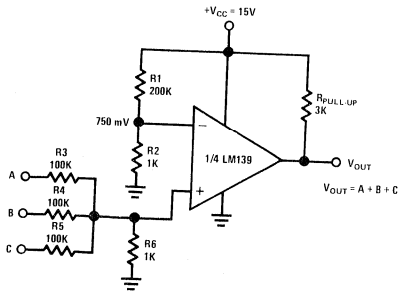


FIGURE 20. Three Input OR Gate

simply by increasing  $R_1$  thereby reducing the reference voltage. A logic "1" at any of the inputs will produce a logic "1" at the output. Again a NOR gate may be implemented by simply reversing the comparator inputs. Resistor  $R_6$  may be added for the OR or NOR function at the expense of noise immunity if so desired.

## Output Strobing

The output of the LM139 may be disabled by adding a clamp transistor as shown in Figure 21. A

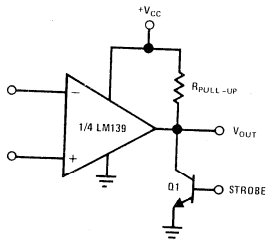


FIGURE 21. Output Strobing Using a Discrete Transistor

stroke control voltage at the base of  $Q_1$  will clamp the comparator output to ground, making it immune to any input changes.

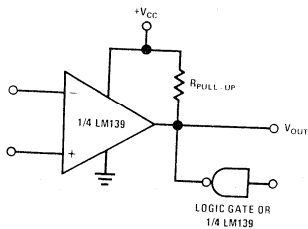


FIGURE 22. Output Strobing with TTL Gate

If the LM139 is being used in a digital system the output may be strobed using any other type of

gate having an uncommitted collector output (such as National's DM5401/DM7401). In addition another comparator of the LM139 could also be used for output strobing, replacing  $Q_1$  in Figure 21, if desired. (See Figure 22.)

## One Shot Multivibrators

A simple one shot multivibrator can be realized using one comparator of the LM139 as shown in Figure 23. The output pulse width is set by the

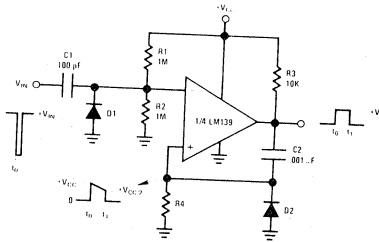


FIGURE 23. One Shot Multivibrator

values of  $C_2$  and  $R_4$  (with  $R_4 > 10 R_3$  to avoid loading the output). The magnitude of the input trigger pulse required is determined by the resistive divider  $R_1$  and  $R_2$ . Temperature stability can be achieved by balancing the temperature coefficients of  $R_4$  and  $C_2$  or by using components with very low TC. In addition, the TC of resistors  $R_1$  and  $R_2$  should be matched so as to maintain a fixed reference voltage of  $+V_{CC}/2$ . Diode  $D_2$  provides a rapid discharge path for capacitor  $C_2$  to reset the one shot at the end of its pulse. It also prevents the non-inverting input from being driven below ground. The output pulse width is relatively independent of the magnitude of the supply voltage and will change less than 2% for a five volt change in  $+V_{CC}$ .

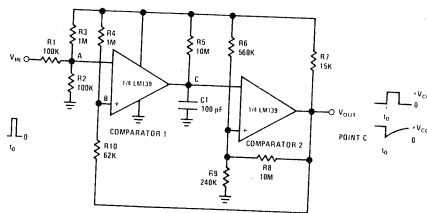


FIGURE 24. Multivibrator with Input Lock-Out

The one shot multivibrator shown in Figure 24 has several characteristics which make it superior to that shown in Figure 23. First, the pulse width is independent of the magnitude of the power supply voltage because the charging voltage and the intercept voltage are a fixed percentage of  $+V_{CC}$ . In addition this one-shot is capable of 99% duty cycle and exhibits input trigger lock-out to insure that the circuit will not re-trigger before the output pulse has been completed. The trigger level is the

voltage required at the input to raise the voltage at point A higher than the voltage at point B, and is set by the resistive divider  $R_4$  and  $R_{10}$  and the network  $R_1$ ,  $R_2$  and  $R_3$ . When the multivibrator has been triggered, the output of comparator 2 is high causing the reference voltage at the non-inverting input of comparator 1 to go to  $+V_{CC}$ . This prevents any additional input pulses from disturbing the circuit until the output pulse has been completed.

The value of the timing capacitor,  $C_1$ , must be kept small enough to allow comparator 1 to completely discharge  $C_1$  before the feedback signal from comparator 2 (through  $R_{10}$ ) switches comparator 1 OFF and allows  $C_1$  to start an exponential charge. Proper circuit action depends on rapidly discharging  $C_1$  to a value set by  $R_6$  and  $R_9$  at which time comparator 2 latches comparator 1 OFF. Prior to the establishment of this OFF state,  $C_1$  will have been completely discharged by comparator 1 in the ON state. The time delay, which sets the output pulse width, results from  $C_1$  recharging to the reference voltage set by  $R_6$  and  $R_9$ . When the voltage across  $C_1$  charges beyond this reference, the output pulse returns to ground and the input is again reset to accept a trigger.

#### Bistable Multivibrator

Figure 25 is the circuit of one comparator of the LM139 used as a bistable multivibrator. A reference voltage is provided at the inverting input by a voltage divider comprised of  $R_2$  and  $R_3$ . A pulse

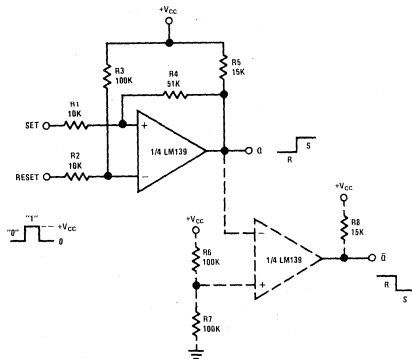


FIGURE 25. Bistable Multivibrator

applied to the SET terminal will switch the output high. Resistor divider network  $R_1$ ,  $R_4$ , and  $R_5$  now clamps the non-inverting input to a voltage greater than the reference voltage. A pulse now applied to the RESET input will pull the output low. If both  $Q$  and  $\bar{Q}$  outputs are needed, another comparator can be added as shown dashed in Figure 25.

Figure 26 shows the output saturation voltage of the LM139 comparator versus the amount of current being passed to ground. The end point of

1 mV at zero current along with an  $R_{SAT}$  of  $60\Omega$  shows why the LM139 so easily adapts itself to oscillator and digital switching circuits by allowing the DC output voltage to go practically to ground while in the ON state.

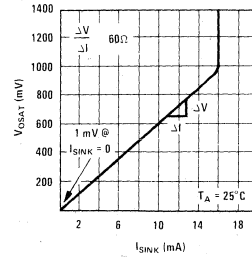


FIGURE 26. Typical Output Saturation Characteristics

#### Time Delay Generator

The final circuit to be presented under "Digital and Switching Circuits" is a time delay generator (or sequence generator) as shown in Figure 27.

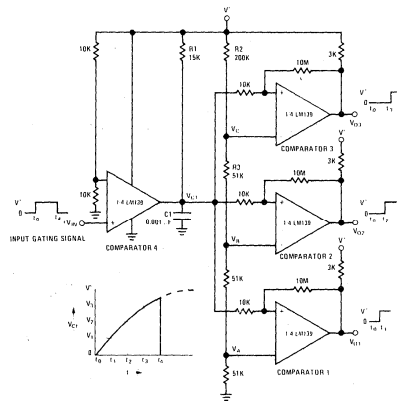


FIGURE 27. Time Delay Generator

This timer will provide output signals at prescribed time intervals from a time reference  $t_0$  and will automatically reset when the input signal returns to ground. For circuit evaluation, first consider the quiescent state ( $V_{IN} = 0$ ) where the output of comparator 4 is ON which keeps the voltage across  $C_1$  at zero volts. This keeps the outputs of comparators 1, 2 and 3 in their ON state ( $V_{OUT} = GND$ ). When an input signal is applied, comparator 4 turns OFF allowing  $C_1$  to charge at an exponential rate through  $R_1$ . As this voltage rises past the preset trip points  $V_A$ ,  $V_B$  and  $V_C$  of comparators 1, 2 and 3 respectively, the output voltage of each of these comparators will switch to the high state ( $V_{OUT} = +V_{CC}$ ). A small amount of

hysteresis has been provided to insure fast switching for the case where the  $R_C$  time constant has been chosen large to give long delay times. It is not necessary that all comparator outputs be low in the quiescent state. Several or all may be reversed as desired simply by reversing the inverting and non-inverting input connections. Hysteresis again is optional.

### LOW FREQUENCY OPERATIONAL AMPLIFIERS

The LM139 comparator can be used as an operational amplifier in DC and very low frequency AC applications ( $\leq 100$  Hz). An interesting combination is to use one of the comparators as an op amp to provide a DC reference voltage for the other three comparators in the same package.

Another useful application of an LM139 has the interesting feature that the input common mode voltage range includes ground even though the amplifier is biased from a single supply and ground. These op amps are also low power drain devices and will not drive large load currents unless current boosted with an external NPN transistor. The largest application limitation comes from a relatively slow slew rate which restricts the power bandwidth and the output voltage response time.

The LM139, like other comparators, is not internally frequency compensated and does not have internal provisions for compensation by external components. Therefore, compensation must be applied at either the inputs or output of the device. Figure 28 shows an output compensation

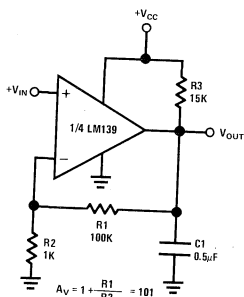


FIGURE 28. Non-Inverting Amplifier

scheme which utilizes the output collector pull-up resistor working with a single compensation capacitor to form a dominant pole. The feedback network,  $R_1$  and  $R_2$  sets the closed loop gain at  $1 + R_1/R_2$  or 101 (40 dB). Figure 29 shows the output swing limitations versus frequency. The output current capability of this amplifier is limited by the relatively large pull-up resistor (15 k $\Omega$ ) so the output is shown boosted with an external NPN transistor in Figure 30. The frequency response is greatly extended by the use of the new compensa-

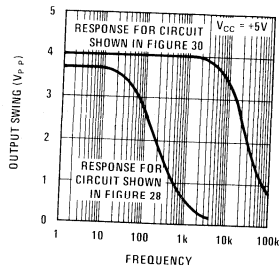


FIGURE 29. Large Signal Frequency Response

tion scheme also shown in Figure 30. The DC level shift due to the  $V_{BE}$  of  $Q_1$  allows the output

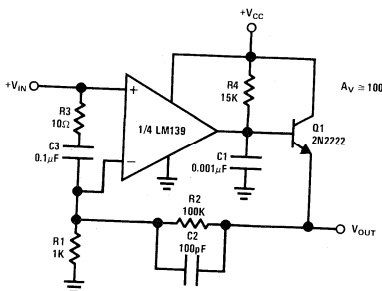


FIGURE 30. Improved Operational Amplifier

voltage to swing from ground to approximately one volt less than  $+V_{CC}$ . A voltage offset adjustment can be added as shown in Figure 31.

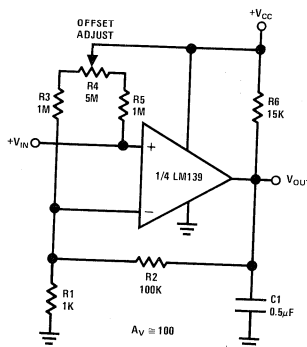


FIGURE 31. Input Offset Null Adjustment

### Dual Supply Operation

The applications presented here have been shown biased typically between  $+V_{CC}$  and ground for simplicity. The LM139, however, works equally well from dual (plus and minus) supplies commonly used with most industry standard op amps and comparators, with some applications actually requiring fewer parts than the single supply equivalent.

The zero crossing detector shown in Figure 10 can be implemented with fewer parts as shown in Figure 32. Hysteresis has been added to insure fast transitions if used with slowly moving input signals. It may be omitted if not needed, bringing the total parts count down to one pull-up resistor.

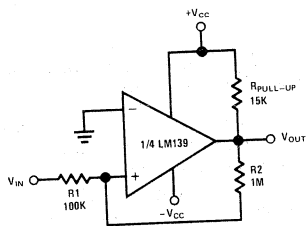


FIGURE 32. Zero Crossing Detector Using Dual Supplies

The MOS clock driver shown in Figure 16 uses dual supplies to properly drive the MM0025 clock driver.

The square wave generator shown in Figure 13 can be used with dual supplies giving an output that swings symmetrically above and below ground (see Figure 33). Operation is identical to the single supply oscillator with the only change being in the lower trip point.

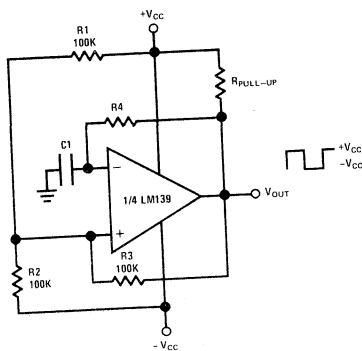


FIGURE 33. Squarewave Generator Using Dual Supplies

Figure 34 shows an LM139 connected as an op amp using dual supplies. Biasing is actually simpler if full output swing at low gain settings is required by biasing the inverting input from ground rather than from a resistive divider to some voltage between +VCC and ground.

All the applications shown will work equally well biased with dual supplies. If the total voltage across the device is increased from that shown, the output pull-up resistor should be increased to prevent the output transistor from being pulled out of

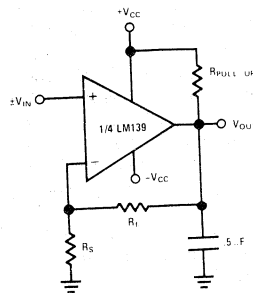


FIGURE 34. Non-Inverting Amplifier Using Dual Supplies

saturation by drawing excessive current, thereby preventing the output low state from going all the way to -VCC.

## MISCELLANEOUS APPLICATIONS

The following is a collection of various applications intended primarily to further show the wide versatility that the LM139 quad comparator has to offer. No new modes of operation are presented here so all of the previous formulas and circuit descriptions will hold true. It is hoped that all of the circuits presented in this application note will suggest to the user a few of the many areas in which the LM139 can be utilized.

### Remote Temperature Sensor/Alarm

The circuit shown in Figure 35 shows a temperature over-range limit sensor. The 2N930 is a National process 07 silicon NPN transistor connected to produce a voltage reference equal to a multiple of its base emitter voltage along with a temperature coefficient equal to a multiple of 2.2 mV/°C. That multiple is determined by the ratio of R<sub>1</sub> to R<sub>2</sub>. The theory of operation is as follows: with transistor Q<sub>1</sub> biased up, its base to emitter voltage will appear across resistor R<sub>1</sub>. Assuming a reasonably high beta ( $\beta \geq 100$ ) the base current can be neglected so that the current that flows through resistor R<sub>1</sub> must also be flowing through R<sub>2</sub>. The voltage drop across resistor R<sub>2</sub> will be given by:

$$I_{R1} = I_{R2}$$

and

$$V_{R1} = V_{be} = I_{R1} R_1$$

so

$$V_{R2} = I_{R2} R_2 = I_{R1} R_2 = V_{be} \frac{R_2}{R_1} \quad (31)$$

As stated previously this base-emitter voltage is strongly temperature dependent, minus 2.2 mV/°C for a silicon transistor. This temperature coefficient is also multiplied by the resistor ratio R<sub>1</sub>/R<sub>2</sub>.

This provides a highly linear, variable temperature coefficient reference which is ideal for use as a temperature sensor over a temperature range from approximately  $-65^{\circ}\text{C}$  to  $+150^{\circ}\text{C}$ . When this temperature sensor is connected as shown in Figure 35 it can be used to indicate an alarm condition of either too high or too low a temperature excursion. Resistors  $R_3$  and  $R_4$  set the trip point reference voltage,  $V_B$ , with switching occurring when  $V_A = V_B$ . Resistor  $R_5$  is used to bias up  $Q_1$  at some low value of current simply to keep quiescent power dissipation to a minimum. An  $I_Q$  near  $10\mu\text{A}$  is acceptable.

Using one LM139, four separate sense points are available. The outputs of the four comparators can be used to indicate four separate alarm conditions or the outputs can be OR'ed together to indicate an alarm condition at any one of the sensors. For the circuit shown the output will go HIGH when the temperature of the sensor goes above the preset level. This could easily be inverted by simply reversing the input leads. For operation over a narrow temperature range, the resistor ratio

$R_2/R_1$  should be large to make the alarm more sensitive to temperature variations. To vary the trip points a potentiometer can be substituted for  $R_3$  and  $R_4$ . By the addition of a single feedback resistor to the non-inverting input to provide a slight amount of hysteresis, the sensor could function as a thermostat. For driving loads greater than 15 mA, an output current booster transistor could be used.

#### Four Independently Variable, Temperature Compensated, Reference Supplies

The circuit shown in Figure 36 provides four independently variable voltages that could be used for low current supplies for powering additional equipment or for generating the reference voltages needed in some of the previous comparator applications. If the proper Zener diode is chosen, these four voltages will have a near zero temperature coefficient. For industry standard Zeners, this will be somewhere between 5.0 and 5.4V at a Zener current of approximately 10 mA. An alternative solution is offered to reduce this 50 mW quiescent

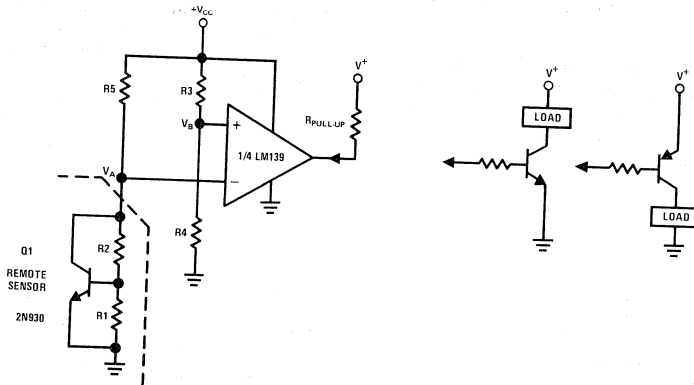


FIGURE 35. Temperature Alarm

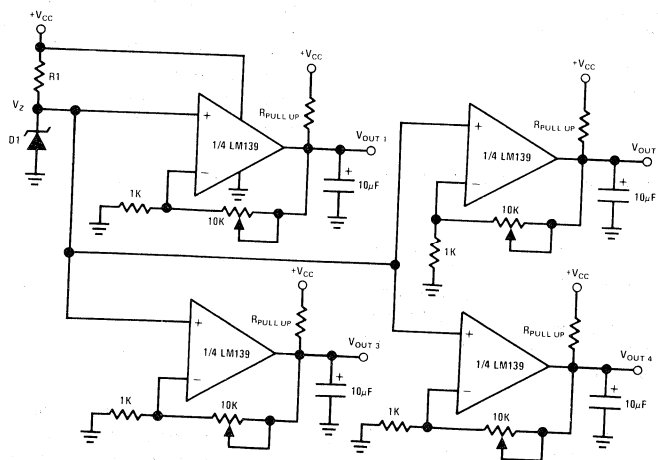


FIGURE 36. Four Variable Reference Supplies



power drain. Experimental data has shown that any of National's process 21 transistors which have been selected for low reverse beta ( $\beta_R < .25$ ) can be used quite satisfactorily as a zero T.C. Zener. When connected as shown in Figure 37, the T.C.

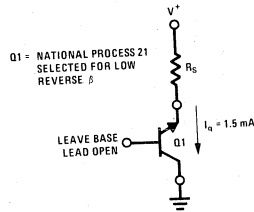


FIGURE 37. Zero T.C. Zener

of the base-emitter Zener voltage is exactly cancelled by the T.C. of the forward biased base-collector junction if biased at 1.5 mA. The diode can be properly biased from any supply by adjusting  $R_5$  to set  $I_q$  equal to 1.5 mA. The outputs of any of the reference supplies can be current boosted by using the circuit shown in Figure 30.

### Digital Tape Reader

Two circuits are presented here — a tape reader for both magnetic tape and punched paper tape. The circuit shown in Figure 38, the magnetic tape

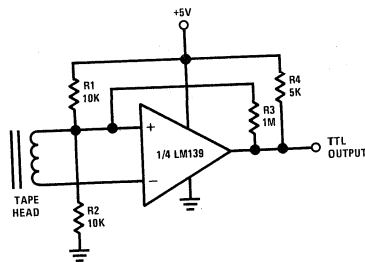


FIGURE 38. Magnetic Tape Reader with TTL Output

reader, is the same as Figure 12 with a few resistor values changed. With a 5V supply, to make the output TTL compatible, and a 1M $\Omega$  feedback resistor,  $\pm 5$  mV of hysteresis is provided to insure fast switching and higher noise immunity. Using one LM139, four tape channels can be read simultaneously.

The paper tape reader shown in Figure 39 is essentially the same circuit as Figure 38 with the only change being in the type of transducer used. A photo-diode is now used to sense the presence or absence of light passing through holes in the tape. Again a 1M $\Omega$  feedback resistor gives  $\pm 5$  mV of hysteresis to insure rapid switching and noise immunity.

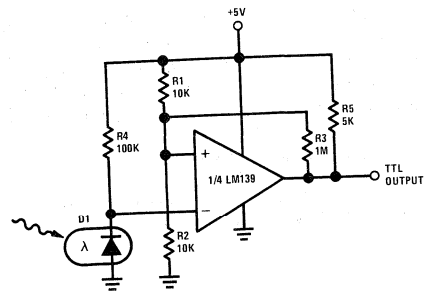


FIGURE 39. Paper Tape Reader With TTL Output

### Pulse Width Modulator

Figure 40 shows the circuit for a simple pulse width modulator circuit. It is essentially the same as that shown in Figure 13 with the addition of an input control voltage.

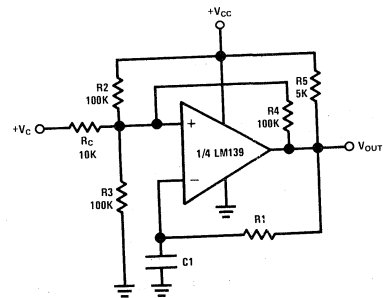


FIGURE 40. Pulse Width Modulator

voltage equal to  $+V_{CC}/2$ , operation is basically the same as that described previously. If the input control voltage is moved above or below  $+V_{CC}/2$ , however, the duty cycle of the output square wave will be altered. This is because the addition of the control voltage at the input has now altered the trip points. These trip points can be found if the circuit is simplified as in Figure 41. Equations 13 through 20 are still applicable if the effect of  $R_C$  is added, with equations 17 through 20 being altered for the condition where  $V_C \neq +V_{CC}/2$ .

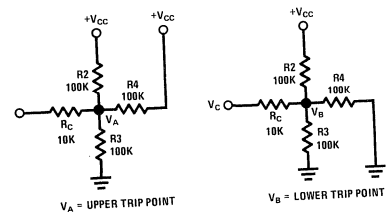


FIGURE 41. Simplified Circuit For Calculating Trip Points of Figure 40.

Pulse width sensitivity to input voltage variations will be increased by reducing the value of  $R_C$  from 10 k $\Omega$  and alternately, sensitivity will be

reduced by increasing the value of  $R_C$ . The values of  $R_1$  and  $C_1$  can be varied to produce any desired center frequency from less than one hertz to the maximum frequency of the LM139 which will be limited by  $+V_{CC}$  and the output slew rate.

### Positive and Negative Peak Detectors

Figures 42 and 43 show the schematics for simple positive or negative peak detectors. Basically the

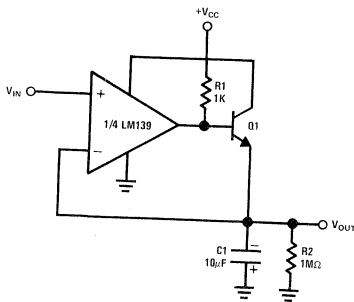


FIGURE 42. Positive Peak Detector

LM139 is operated closed loop as a unity gain follower with a large holding capacitor from the output to ground. For the positive peak detector a low impedance current source is needed so an additional transistor is added to the output. When the output of the comparator goes high, current is passed through  $Q_1$  to charge up  $C_1$ . The only discharge path will be the  $1M\Omega$  resistor shunting  $C_1$  and any load that is connected to  $V_{OUT}$ . The decay time can be altered simply by changing the  $1M\Omega$  resistor higher or lower as desired. The output should be used through a high impedance

follower to avoid loading the output of the peak detector.

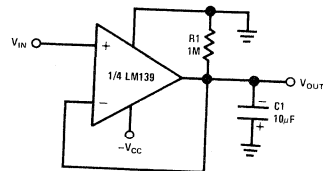


FIGURE 43. Negative Peak Detector

For the negative peak detector, a low impedance current sink is required and the output transistor of the LM139 works quite well for this. Again the only discharge path will be the  $1M\Omega$  resistor and any load impedance used. Decay time is changed by varying the  $1M\Omega$  resistor.

### Conclusion

The LM139 is an extremely versatile comparator package offering reasonably high speed while operating at power levels in the low mW region. By offering four independent comparators in one package, many logic and other functions can now be performed at substantial savings in circuit complexity, parts count, overall physical dimensions, and power consumption.

For limited temperature range applications, the LM239 or LM339 may be used in place of the LM139.

It is hoped that this application note will provide the user with a guide for using the LM139 and also offer some new application ideas.

# Applications for a High Speed FET Input Op Amp

National Semiconductor  
Application Note 75  
Barry Siegel  
December 1972



## INTRODUCTION

The principal limitations in speed and bandwidth in IC FET input op amps have been reduced by over an order of magnitude with the introduction of the LH0062/LH0062C. Internal compensation assures unity gain stability with bandwidths in excess of 15 MHz. Voltage follower slew rate is typically 75V/ $\mu$ s and is guaranteed in excess of 50V/ $\mu$ s. Furthermore, external components may be used to extend the slew rate to 120V/ $\mu$ s and settling times under 1 $\mu$ s. The LH0062H (TO-5) is pin compatible with LM101, LM741 and LH0022. A summary of the LH0062's performance characteristics is given in Table 1.

PARAMETER (T <sub>A</sub> = 25°C)	MIN	TYP	MAX	UNITS
Input Offset Voltage		2.0	5.0	mV
Input Bias Current			20	pA
Voltage Gain	50	100		V/mV
Slew Rate	50	75		V/ $\mu$ s
Bandwidth		15		MHz

TABLE 1. Summary of LH0062 Characteristics

## CIRCUIT DESCRIPTION

The LH0062 is basically a two stage amplifier (Figure 1) consisting of a N channel junction FET input stage (Q<sub>1</sub> and Q<sub>2</sub>) and a PNP output stage (Q<sub>4</sub> and Q<sub>5</sub>). Q<sub>1</sub> and Q<sub>2</sub> are a well matched

interdigitated monolithic pair that provide high common mode rejection and input offset voltage tracking usually associated only with bipolar designs. The current mirror (Q<sub>6</sub> and Q<sub>7</sub>) converts to single ended operation in addition to providing active high impedance load for Q<sub>4</sub> and Q<sub>5</sub> thus providing high gain. Q<sub>3</sub> and D<sub>1</sub> provides a temperature compensated current source for the input stage and Q<sub>8</sub>, Q<sub>9</sub>, D<sub>2</sub> and D<sub>3</sub> form a class AB

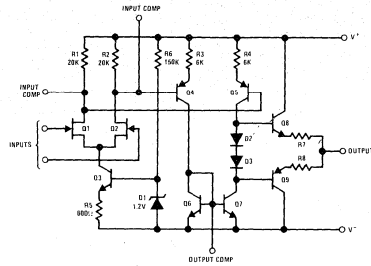


FIGURE 1. Simplified LH0062 Circuit Schematic

output buffer. Detailed schematic is illustrated in Figure 2. Note that the FET inputs are protected by 5V zener diodes and input current under transient conditions should be limited by inserting a 1k ohm or larger resistor in series with one of the inputs.

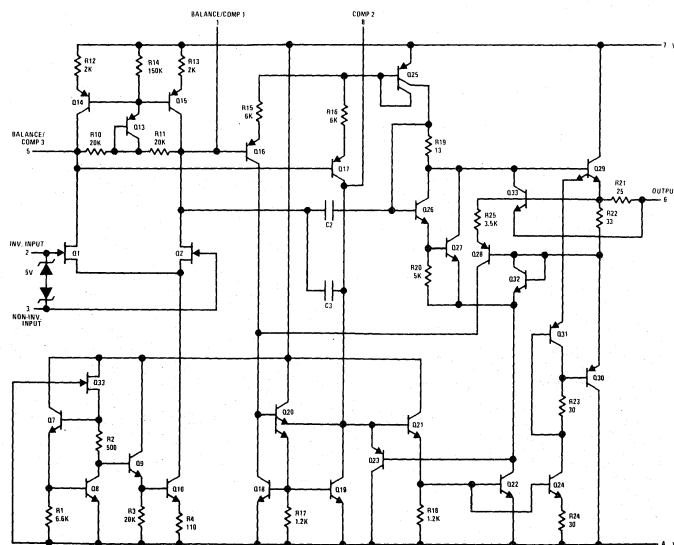


FIGURE 2. Complete LH0062 Schematic

## COMPENSATION CONSIDERATIONS

As noted earlier, the LH0062 is internally compensated for unity gain stability. However, a few precautions are advised. Like most wide band amplifiers, the LH0062 is sensitive to power supply inductance, and decoupling the supplies with 0.1 $\mu$ F ceramic disc capacitors within an inch or two of the device will prevent spurious oscillations and save a fair amount of grief. The device is capable


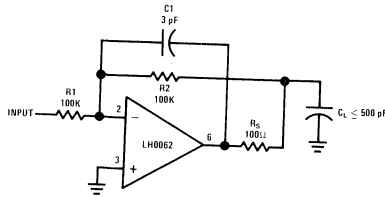


FIGURE 3. Isolating a Capacitive Load up to 500 pF

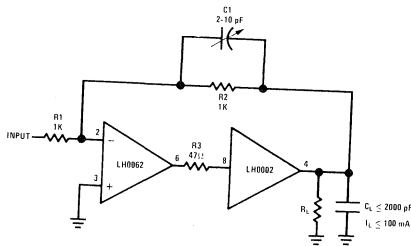of driving 50 to 100 pF loads; for larger loads, an isolation resistor,  $R_3$  as shown in Figure 3 is recommended. Alternatively, a current buffer such as the LH0002 or LH0033 may be used for loads in excess of 500 pF with no degradation in slew rate as shown in Figure 4.



Note: In the examples above, a small capacitor,  $C_1$ , is used to cancel the effects of stray capacitance at the input.

FIGURE 4. Driving Capacitances in Excess of 500 pF and Loads

The LH0062 may be feed-forward compensated in inverting mode applications as shown in Figure 5. This boosts slew rate to over 120V/ $\mu$ s and bandwidth to over 30 MHz. When full bandwidth is

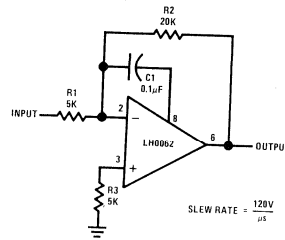


FIGURE 5. Feed Forward Compensation

not required, the device may be over-compensated as shown in Figure 6 to reduce bandwidth to 5 MHz. This technique improves phase margin and reduces susceptibility to spurious oscillations in applications where speed is less critical.

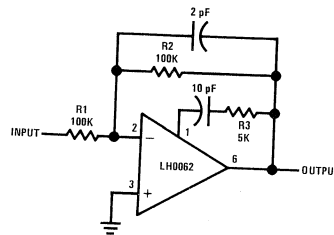


FIGURE 6. Overcompensation

Minimum settling time of less than 1 $\mu$ s to 0.1% for a 20V input step is obtained as illustrated in Figure 7. A small tweak capacitor,  $C_1$  is recommended to cancel stray board layout capacitance,  $C_s$ . Once best value of trimmer capacitor  $C_1$  is determined for a particular layout, it may be replaced with a fixed value.

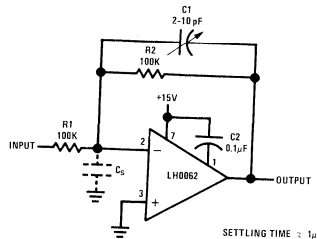


FIGURE 7. Compensation for Minimum Settling Time

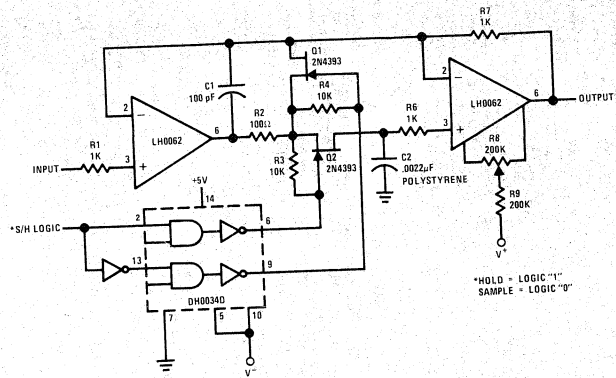


FIGURE 8. High Speed Sample & Hold

## APPLICATIONS

The circuit of Figure 8 is a high speed sample and hold with sample acquisition time of  $10\mu\text{s}$  for 0.1% accuracy and aperture time of approximately 25 ns. Resistor,  $R_6$ , is used to limit input current during power on and off transients. Although the inputs of the LHD062 are protected by back-to-back diodes excessive input current could damage the device. Resistor  $R_9$  and the pot,  $R_8$ , allow null of the output offset with negligible effect on offset drift.

The peak detector of Figure 9 will acquire a +10V peak signal in under  $4\mu\text{s}$  with droop rates under 20 mV/sec. Reversing the polarity of diodes  $D_1$  and  $D_2$  will allow peak detecting negative signals. Any ultra-low leakage diode may be substituted for the 2N930 collector-base junction.

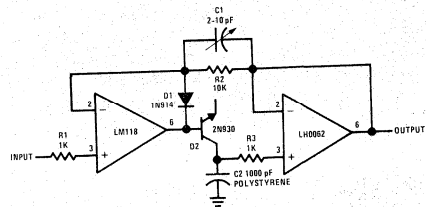


FIGURE 9. High Speed Peak Detector

The circuit of Figure 10 is a programmable integrator with a range in period from  $1\mu\text{s}$  to 1 ms. For best results  $C_1$  through  $C_4$  should be low leakage construction such as polycarbonate or polystyrene. A simple method of implementing the offset adjustment is to momentarily insert a 100k ohm resistor between pins 2 and 6 of the LHD062. With the switches of the AH5009 off, the output may be set to zero with  $R_2$ .

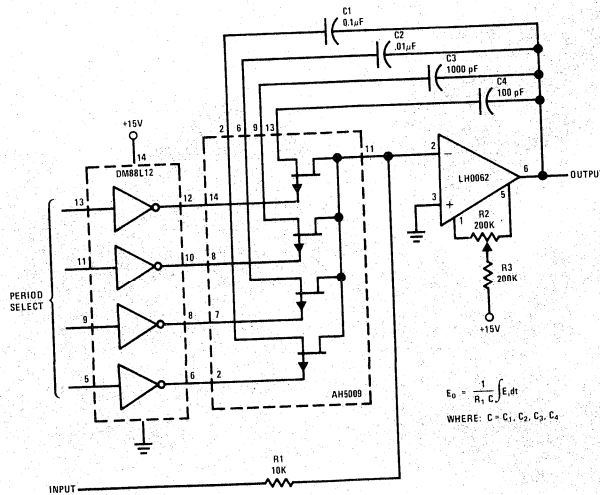


FIGURE 10. Programmable Integrator

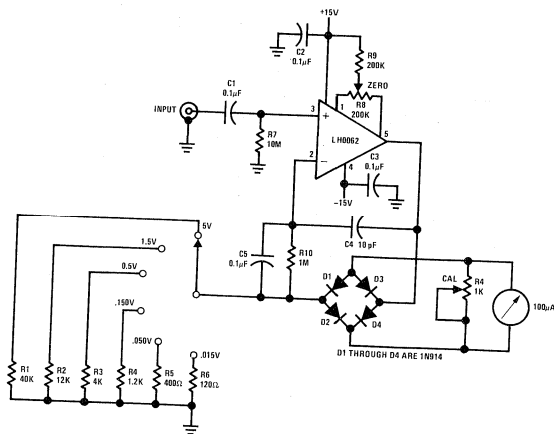


FIGURE 11. Wide Band AC Voltmeter

The circuit of Figure 11 is a wide band AC voltmeter capable of measuring AC signals as low as 15 mV at frequencies from 100 Hz to 500 kHz. Full scale sensitivity may be changed by altering the values  $R_1$  through  $R_6$  ( $R \cong V_{IN}/100\mu A$ ).

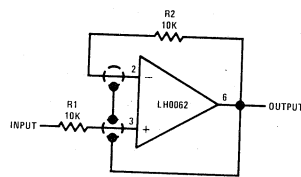


FIGURE 12. Guard/Bootstrap for Unity Gain

### HEAT SINKING, GUARDING, AND BOOTSTRAPPING

The LH0062 is specified for operation without an external heat sink. However, standby power is typically 240 mW causing a junction rise of approximately 60°C. A clip-on heat sink can reduce internal heating hence reduce input bias current from 20 pA at 25°C ambient to 2 or 3 pA.

Guarding input leads is recommended in stringent applications. An excellent discussion on guarding is given in AN-63 and the techniques discussed are directly applicable to the LH0062. Another benefit of guarding is reduced input capacitance. By bootstrapping the inputs, as shown in Figure 12, the apparent input capacitance is reduced to fractions of a pico-farad.

Furthermore, the case of the LH0062 is electrically isolated, and the output may be tied to case in order to eliminate stray capacitance introduced by the header.

### REFERENCES

1. R. K. Underwood, "New Design Techniques for FET Op Amps," National Semiconductor AN-63, March 1972.
2. R. C. Dobkin, "LM118 Op Amp Slews 70V/ $\mu$ s," National Semiconductor LB-17, September 1971.

## IC Preamplifier Challenges Choppers on Drift

National Semiconductor  
Application Note 79  
Robert C. Dobkin  
February 1973



Since the introduction of monolithic IC amplifiers there has been a continual improvement in DC accuracy. Bias currents have been decreased by 5 orders of magnitude over the past 5 years. Low offset voltage drift is also necessary in a high accuracy circuits. This is evidenced by the popularity of low drift amplifier types as well as the requests for selected low-drift op amps. However, until now the chopper stabilized amplifier offered the lowest drift. A new monolithic IC preamplifier designed for use with general purpose op amps improves DC accuracy to where the drift is lower than many chopper stabilized amplifiers.

### INTRODUCTION

Chopper amplifiers have long been known to offer the lowest possible DC drift. They are not without problems, however. Most chopper amps can be used only as inverting amplifiers, limiting their applications. Chopping can introduce noise and spikes into the signal. Mechanical choppers need replacement as well as being shock sensitive. Further, chopper amplifiers are designed to operate over a limited power supply, limited temperature range.

Previous low-drift op amps do not provide optimum performance either. Selected devices may only meet their specified voltage drift under restrictive conditions. For example, if a 741 device is selected without offset nulling, the addition of an offset null pot can drastically change the drift. Low drift op amps designed for offset balancing have another problem. The resistor network used in the null circuit is designed to null the drift when the offset voltage is nulled. The mechanism to achieve nulled drift depends on the difference in temperature coefficient between the internal resistors and the external null pot. Since the internal resistors have a non-linear temperature coefficient and may vary device to device as well as between manufacturers, it can only approximately null offset drift. The problem gets worse if the external null pot has a TC other than zero.

A new IC preamplifier is now available which can give drifts as low as  $0.2\mu\text{V}/^\circ\text{C}$ . It is used with conventional op amps and eliminates the problems associated with older devices. As well as improving the DC input characteristics of the op amp, loop-gain is increased when an LM121 is used. This further improves overall accuracy since DC gain error is decreased.


The LM121 preamp is designed to give zero drift when the offset voltage is nulled to zero. The operating current of the LM121 is programmable

by the value of the null network resistors. The drift is independent of the value of the nulling network so it can be used over a wide range of operating currents while retaining low drift. The operating current can be chosen to optimize bias current, gain, speed, or noise while still retaining the low drift. Further, since the drift is independent of the match between external and internal resistors when the offset is nulled, lower and more predictable drifts can be expected in actual use. The input is fully differential, overcoming many of the problems with single ended chopper-amps. The device also has enough common mode rejection ratio to allow the low drift to be fully utilized.
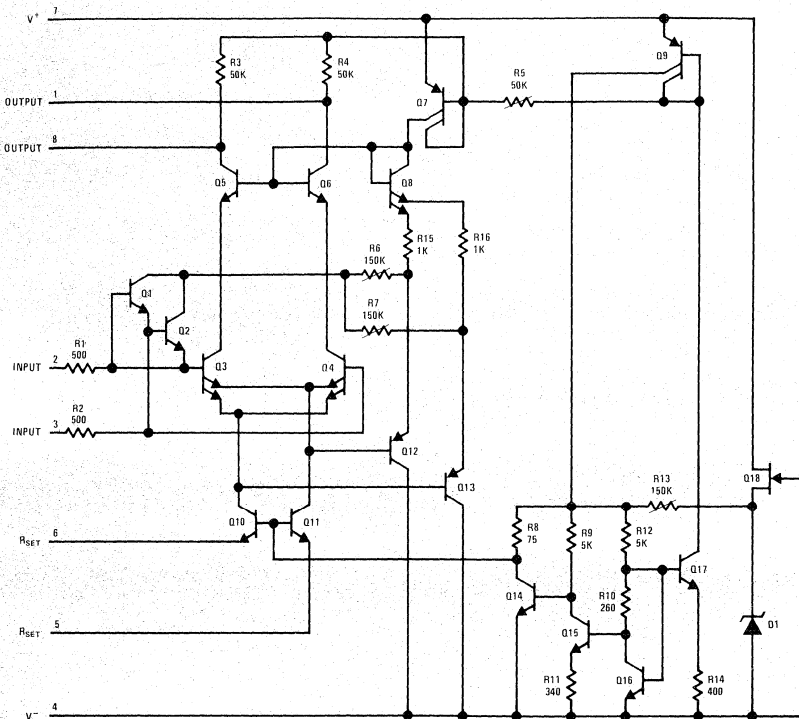
### CIRCUIT DESCRIPTION

The LM121 is a well matched differential amplifier utilizing super-gain transistors as the input devices. A schematic is shown in Figure 1. The input signal is applied to the bases of  $Q_3$  and  $Q_4$  through protection resistors  $R_1$  and  $R_2$ .  $Q_3$  and  $Q_4$  have two emitters to allow offset balancing which will be explained later. The operating current for the differential amplifier is supplied by current sources  $Q_{10}$  and  $Q_{11}$ . The operating current is externally programmed by resistors connected from the emitters of  $Q_{10}$  and  $Q_{11}$  to the negative supply. Input transistors  $Q_3$  and  $Q_4$  are cascoded by transistors  $Q_5$  and  $Q_6$  to keep the collector base voltage on the input stage equal to zero. This eliminates leakage at high operating temperatures and keeps the common mode input voltage from appearing across the low breakdown super-gain input transistors. Additionally, the cascode improves the common mode rejection of the differential amplifier.  $Q_1$  and  $Q_2$  protect the input against large differential voltages.

The output signal is developed across resistive loads  $R_3$  and  $R_4$ . The total collector current of the input is then applied to the base of a fixed gain PNP,  $Q_7$ . The collector current of  $Q_7$  sets the operating current of  $Q_8$ ,  $Q_{12}$ , and  $Q_{13}$ . These transistors are used to set the operating voltage of the cascode,  $Q_5$  and  $Q_6$ . By operating the cascode biasing transistors at the same operating current as the input stage, it is possible to keep collector base voltage at zero; and therefore, collector-base leakage remains low over a wide current range. Further, this minimizes the effects of  $V_{BE}$  variations and finite transistor current gain. At high operating currents the collector base voltage of the input stage is increased by about 100 mV due to the drop across  $R_{15}$  and  $R_{16}$ . This prevents the input transistors from saturating under worst case conditions of high current and high operating temperature.



\*PIN CONNECTIONS SHOWN ON DIAGRAM AND TYPICAL APPLICATIONS ARE FOR TO-5 PACKAGE.

FIGURE 1. Schematic Diagram of the LM121

The rest of the devices comprise the turn-on and regulator circuitry. Transistors Q<sub>14</sub>, Q<sub>15</sub>, and Q<sub>16</sub> form a 1.2V regulator for the bases of the input stage current source. By fixing the bases of the current sources at 1.2V, their output current changes proportional to absolute temperature. This compensates for the temperature sensitivity of the input stage transconductance. Temperature compensating the transconductance makes the pre-amp more useful in some applications such as an instrumentation amplifier and minimizes bandwidth variations with temperature. The regulator is started by Q<sub>18</sub> and its operating current is supplied by Q<sub>17</sub> and Q<sub>9</sub>. Figure 2 shows the LM121 chip.

#### Offset Balancing

The LM121 was designed to operate with an offset balancing network connected to the current source transistors. The method of balancing the offset also minimizes the drift of the preamp. Unlike earlier devices such as the LM725, the LM121 depends only upon the highly predictable emitter base voltages of transistors to achieve low drift. Devices like the LM725 depend on the match between internal resistor temperature coefficient and the external null pot as well as the input stage transistors characteristics for drift compensation.

The input stage of the LM121 is actually two differential amplifiers connected in parallel, each having a fixed offset. The offset is due to different

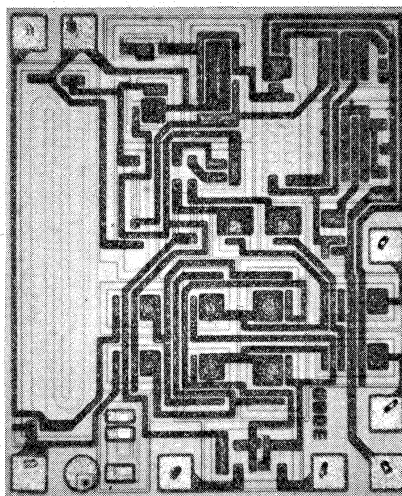


FIGURE 2. LM121 Chip



areas for the transistor emitters. The offset for each pair is given by:

$$\Delta V_{BE} = \frac{kT}{q} \ln \frac{A_1}{A_2}$$

where  $k$  is Boltzmann's constant  $T$  is absolute temperature,  $q$  is the charge on an electron, and  $A_1$  and  $A_2$  are emitter areas. Because of the offset, each pair has a fixed drift. When the pairs are connected in parallel, if they match, the offsets and drift cancel. However, since matching is not perfect, the emitters of the pairs are not connected in parallel, but connected to independent current sources to allow offset balancing. The offset and drift effect of each pair is proportional to its operating current, so varying the ratio of the current from current sources will vary both the offset and drift. When the offset is nulled to zero, the drift is nulled to below  $1\mu\text{V}/^\circ\text{C}$ .

The offset balancing method used in the LM121 has several advantages over conventional balancing schemes. Firstly, as mentioned earlier, it theoretically zeros the drift and offset simultaneously. Secondly, since the maximum balancing range is fixed by transistor areas, the effect of null network variations on offset voltage is minimized. Resistor shifts of one percent only cause a  $30\mu\text{V}$  shift in offset voltage on the LM121, while a one percent shift in collector resistors on a standard diff amp causes a  $300\mu\text{V}$  offset change. Finally, it allows the value of the null network to set the operating current.

### Achieving Low Drift

A very low drift amplifier poses some uncommon application and testing problems. Many sources of error can cause the apparent circuit drift to be much higher than would be predicted. In many cases, the low drift of the op amp is completely swamped by external effects while the amplifier is blamed for the high drift.

Thermocouple effects caused by temperature gradient across dissimilar metals are perhaps the worst offenders. Whenever dissimilar metals are joined, a thermocouple results. The voltage generated by the thermocouple is proportional to the temperature difference between the junction and the measurement end of the metal. This voltage can range between essentially zero and hundred of microvolts per degree, depending on the metals used. In any system using integrated circuits a minimum of three metals are found: copper, solder, and kovar (lead material of the IC).

Nominally, most parts of a circuit are at the same temperature. However, a small temperature gradient can exist across even a few inches — and this is a big problem with low level signals. Only a few degrees gradient can cause hundreds of microvolts of error. The two places this shows up,


generally are the package-to printed circuit board interface and temperature gradients across resistors. Keeping package leads short and the two input leads close together help greatly.

For example, a very low drift amplifier was constructed and the output monitored over a 1 minute period. During the 1 minute it appeared to have input referred offset variations of  $\pm 5\mu\text{V}$ . Shielding the circuit from air currents reduced this to  $\pm 0.5\mu\text{V}$ . The  $10\mu\text{V}$  error was due to thermal gradients across the circuit from air currents.

Resistor choice as well as physical placement is important for minimizing thermocouple effects. Carbon, oxide film and some metal film resistors can cause large thermocouple errors. Wirewound resistors of evenohm or managanin are best since they only generate about  $2\mu\text{V}/^\circ\text{C}$  referenced to copper. Of course, keeping the resistor ends at the same temperature is important. Generally, shielding a low drift stage electrically and thermally will yield good results.

Resistors can cause other errors besides gradient generated voltage. If the gain setting resistors do not track with temperature a gain error will result. For example a gain of 1000 amplifier with a constant 10 mV input will have a 10V output. If the resistors mistrack by 0.5% over the operating temperature range, the error at the output is 50 mV. Referred to input, this is a  $50\mu\text{V}$  error. Most precision resistors use different material for different ranges of resistor values. It is not unexpected that resistors differing by a factor of 1000, do not track perfectly with temperature. For best results insure that the gain fixing resistors are of the same material or have tracking temperature coefficients.

Testing low drift amplifiers is also difficult. Standard drift testing techniques such as heating the device in an oven and having the leads available through a connector, thermoprobe, or the soldering iron method — do not work. Thermal gradients cause much greater errors than the amplifier drift. Coupling microvolt signals through connectors is especially bad since the temperature difference across the connector can be  $50^\circ\text{C}$  or more. The device under test along with the gain setting resistor should be isothermal. The circuit in Figure 3 will yield good results if well constructed.

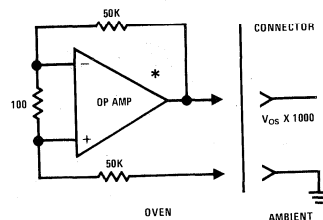

\*OP AMP SHOWN IN FIGURE 9.

FIGURE 3. Drift Measurement Circuit

## Performance

It is somewhat difficult to specify the performance of the LM121 since it is programmable over a wide range of operating currents. Changing the operating current varies gain, bias current, and offset current — three critical parameters in a high accuracy system. However, offset voltage and drift are virtually independent of the operating current.

Typical performance at an operating current of  $20\mu\text{A}$  is shown in Table I. Figures 4 and 5 show how the bias current, offset current, and gain change as a function of programming current. Drift is guaranteed at  $1\mu\text{V}/^\circ\text{C}$  independent of the operating current.

TABLE I. Typical Performance at an Operating Current of  $10\mu\text{A}$  Per Side

Offset Voltage	Nullled
Bias Current	7 nA
Offset Current	0.5 nA
Offset Voltage Drift	$0.3\mu\text{V}/^\circ\text{C}$
Common Mode Rejection Ratio	125 dB
Supply Voltage Rejection Ratio	125 dB
Common Mode Range	$\pm 13\text{V}$
Gain	20V/V
Supply Current	0.5 mA

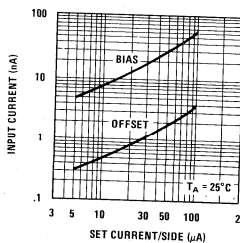


FIGURE 4. Bias and Offset Current vs Set Current

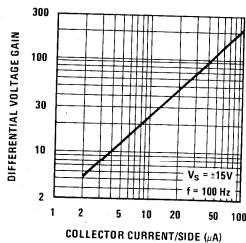


FIGURE 5. Gain vs Set Current

Over a temperature range of  $-55^\circ\text{C}$  to  $+125^\circ\text{C}$  the LM121 has less than  $1\mu\text{V}/^\circ\text{C}$  offset voltage drift when nullled. It is important that the offset voltage is accurately nullled to achieve this low drift. The drift is directly related to the offset

voltage with  $3.8\mu\text{V}/^\circ\text{C}$  drift resulting from every millivolt of offset. For example, if the offset is nullled to  $100\mu\text{V}$ , about  $0.4\mu\text{V}/^\circ\text{C}$  will result — or twice the typically expected drift. This drift is quite predictable and could even be used to cancel the drift elsewhere in a system. Figure 6 shows drift as a function of offset voltage. For critical applications selected devices can achieve  $0.2\mu\text{V}/^\circ\text{C}$ .

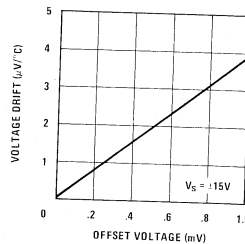


FIGURE 6. Drift vs Offset Voltage

Figures 7 and 8 show the bias current, offset current, and gain variation over a  $-55^\circ\text{C}$  to  $+125^\circ\text{C}$  temperature range. These performance characteristics do not tell the whole story. Since the LM121

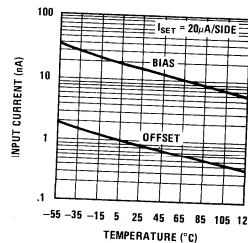


FIGURE 7. Bias and Offset Current vs Temperature

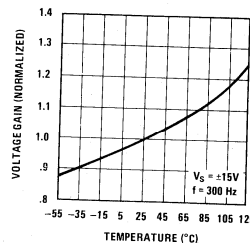


FIGURE 8. Gain vs Temperature for the LM121

is used with an operational amplifier, the op amp characteristics must be considered for over-all amplifier performance.

## Op Amp Effects

The LM121 is nominally used with a standard type of operational amplifier. The op amp functions as the second and ensuing stages of the amplifying system. When the LM121 is connected to an op amp, the two devices may be treated (and used) just as a single op amp. The inputs of the combination are the inputs of the LM121 and the output is from the op amp. Feedback, as with any op amp, is applied back to the inputs. Figure 9 shows the general configuration of an amplifier using the LM121.

The offset voltage and drift of the op amp used have an effect on overall performance and must be considered. (The bias and offset currents of today's op amp are low enough to be ignored.) Although the exact effects of the op amp stage are difficult and tedious to calculate, a few approximations will show the sources of drift.

Op amp drift is perhaps the most important source of error. Drift of the op amp is directly reduced by the gain of the LM121. The drift referred to the input is given by:

$$\text{input drift} = \frac{\text{op amp drift}}{\text{LM121 gain}} + \text{LM121 drift.}$$

If the op amp has a drift of  $10\mu\text{V}/^\circ\text{C}$  and the LM121 is operated at a gain of  $A_V = 50$ , there will be a  $0.2\mu\text{V}/^\circ\text{C}$  component of the total drift due to the op amp. It is therefore important that the LM121 be operated at relatively high gain to minimize the effects of op amp drift. Lower gains for the LM121 will give proportionately less reduction in op amp drift. Of course, a moderately low drift op amp such as the LM108A eases the problem.

Op amp offset voltage also has an effect on total drift. For purpose of analysis assume the LM121 to be perfect with no offset or drift of its own. Then any offset seen when the LM121 is connected to an op amp is due to the op amp alone. The offset is equal to:

$$\text{offset voltage} = \frac{\text{op amp offset}}{\text{LM121 gain}}$$

or the offset is reduced by the gain of the LM121. For example, with a gain of 50 for the LM121, 2 mV of offset on the op amp appears as  $40\mu\text{V}$  of offset at the LM121 input. Unlike offset due to a mismatch in the LM121, this  $40\mu\text{V}$  of offset does not cause any drift. However, when the system is nulled so the offset at the input of the LM121 is zero,  $40\mu\text{V}$  of imbalance has been inserted into the LM121. The imbalance caused by nulling the

offset induced by the op amp will cause a drift of about  $0.14\mu\text{V}/^\circ\text{C}$ . With the system nulled the drift due to op amp will cause a drift of about  $0.15\mu\text{V}/^\circ\text{C}$ . With the system nulled the drift due to op amp offset can be expressed as:

$$\text{drift } (\mu\text{V}/^\circ\text{C}) = \frac{\text{op amp offset (mV)}}{\text{LM121 gain}} (3.6\mu\text{V}/^\circ\text{C}).$$

In actual operation, drift due to op amp offsets will usually be better than predicted. This is because offset voltage and drift are not independent. With the LM121 there is a strong, predictable, correlation between offset and drift. Also, there is a correlation with op amps, but it is not as strong. The drift of the op amp tends to cancel the drift induced in the LM121 when the system is nulled.

In the previous example the drift due to the op amp offset was  $0.15\mu\text{V}/^\circ\text{C}$ . If the op amp has a drift of  $3.6\mu\text{V}/^\circ\text{C}$  per millivolt of offset (like the LM121) it will have a drift of  $7.2\mu\text{V}/^\circ\text{C}$ . This drift is reduced by the gain of the LM121 ( $A_V = 50$ ) to  $0.14\mu\text{V}/^\circ\text{C}$ . This  $0.14\mu\text{V}/^\circ\text{C}$  will cancel the  $0.14\mu\text{V}/^\circ\text{C}$  drift due to balancing the LM121. Since op amps do not always have a strong correlation between offset and drift, the cancellation of drifts is not total. Once again, high gain for the LM121 and a low offset op amp helps achieve low drifts.

## Frequency Compensation

The additional gain of the LM121 preamplifier when used with an operational amplifier usually necessitates additional frequency compensation. This is because the additional gain introduced by the LM121 must be rolled-off before the phase shift through the LM121 and op amp reaches  $180^\circ$ . The additional compensation depends on the gain of the LM121 as well as the closed loop gain of the system. Two frequency compensation techniques are shown here that will operate with any op amp that is unity gain stable.

When the closed loop gain of the op amp with the LM121 is less than the gain of the LM121 alone, more compensation is needed. The worst case situation is when there is 100% feedback — such as a voltage follower or integrator — and the gain of the LM121 is high. When high closed loop gains are used — for example  $A_V = 1000$  — and only an additional gain of 100 is inserted by the LM121, the frequency compensation of the op amp will usually suffice.

The basic circuit of the LM121 in Figure 9 shows two compensation capacitors connected to the op amp (disregarding the 30 pF frequency compensation for the op amp alone). The capacitor from pin

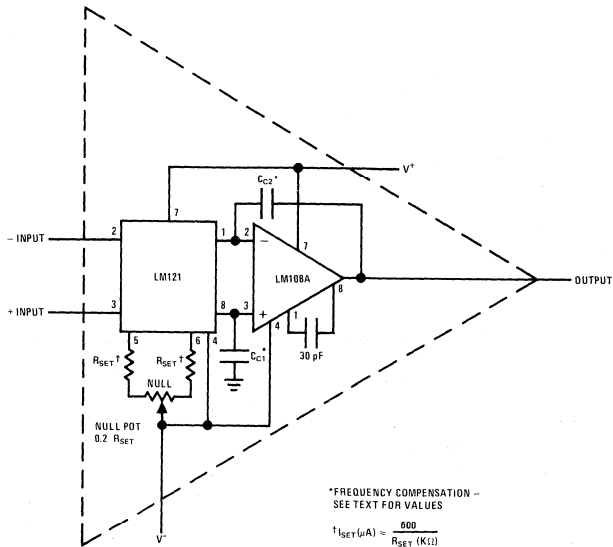


FIGURE 9. General Purpose Amplifier Using the LM121

6 to pin 2 around the op amp acts as an integrating capacitor to roll off the gain. Since the output of the LM121 is differential, a second capacitor is needed to roll off pin 3 of the op amp. These capacitors are  $C_{C1}$  and  $C_{C2}$  in Figure 9.

With capacitors equal, the circuit retains good AC power supply rejection. The approximate value of the compensation capacitors is given by:

$$C_C = \frac{8}{10^6 A_{CL} R_{SET}} \text{ farads}$$

where  $R_{SET}$  is the current set resistor from each current source and where  $A_{CL}$  is closed loop gain. Table II shows typical capacitor values.

An alternate compensation scheme was developed for applications requiring more predictable and smoother roll off. This is useful where the amplifier's gain is changed over a wide range. In this case  $C_{C1}$  is made large and connected to  $V^+$  rather than ground. The output of the LM121 is rendered single ended by a  $0.01\mu F$  bypass capacitor to  $V^+$ . Overall frequency compensation then is achieved by an integrating capacitor around the op amp:

$$\text{Bandwidth at unity gain} \cong \frac{12}{2\pi R_{SET} C}$$

$$\text{for } 0.5 \text{ MHz bandwidth } C = \frac{4}{10^6 R_{SET}}$$

TABLE II. Typical compensation capacitors for various operating currents and closed loop gains. Values given apply to LM101A, LM108, and LM741 type amplifiers.

CLOSED LOOP GAIN	CURRENT SET RESISTOR				
	120 k $\Omega$	60 k $\Omega$	30 k $\Omega$	12 k $\Omega$	6 k $\Omega$
$A_V = 1$	68 pF	130 pF	270 pF	680 pF	1300 pF
$A_V = 5$	15 pF	27 pF	50 pF	130 pF	270 pF
$A_V = 10$	10 pF	15 pF	27 pF	68 pF	130 pF
$A_V = 50$	1 pF	3 pF	5 pF	15 pF	27 pF
$A_V = 100$		1 pF	3 pF	5 pF	10 pF
$A_V = 500$			1 pF	1 pF	3 pF
$A_V = 1000$					

For use with higher frequency op amps such as the LM118 the bandwidth may be increased to about 2 MHz. If closed loop gain is greater than unity "C" may be decreased to:

$$C = \frac{4}{10^6 A_{CL} R_{SET}}$$

### Applications

No attempt will be made to include precision op amp applications as they are well covered in other literature. The previous sections detail frequency compensation and drift problems encountered in using very low drift op amps. The circuit shown in Figure 9 will yield good results in almost any op amp application. However, it is important to choose the operating current properly. From the curves given it is relatively easy to see the effects of current changes. High currents increase gain and reduce op amp effects on drift. Bias and offset current also increase at high current. When the operating source resistance is relatively high, errors due to high bias and offset current can swamp offset voltage drift errors. Therefore, with high source impedances it may be advantageous to operate at lower currents.

Another important consideration is output common mode voltage. This is the voltage between the outputs of the LM121 and the positive power supply. Firstly, the output common mode voltage must be within the operating common mode range of the output op amp. At currents above 10 $\mu$ A there is no problems with the LM108, LM101, and LM741 type devices. Higher currents are needed for devices with more limited common mode range, such as the LM118. As the operating current is increased, the positive common mode limit for the LM121 is decreased. This is because there is more voltage drop across the internal 50k load resistors. The output common mode voltage and positive common mode limits are about equal and given by:

$$\text{Output common mode voltage} \approx V^+ - 0.6V^+ \frac{0.65 \times 50k\Omega}{R_{SET}}$$

$$\text{positive common mode limit}$$

If it is necessary to increase the common mode output voltage (or limit), external resistors can be connected in parallel with the internal 50k $\Omega$  resistors. This should only be done at high operating currents (80 $\mu$ A) since it reduces gain and diverts part of the input stage current from the internal biasing circuitry. A reasonable value for external resistors is 50k $\Omega$ .

The external resistors should be of high quality and low drift, such as wirewound resistors, since they will affect drift if they do not track well with temperature. A 20ppm/ $^{\circ}$ C difference in external resistor temperature coefficient will introduce an additional 0.3 $\mu$ V/ $^{\circ}$ C drift.

An unusually simple gain of 1000 instrumentation amplifier can be made using the LM121. The amplifier has a floating, full differential, high impedance input. Linearity is better than 1%, depending upon input signal level with maximum error at maximum input. Gain stability, as shown in Figure 10, is about  $\pm$ 2% over a  $-55^{\circ}$ C to  $+125^{\circ}$ C temperature range. Finally, the amplifier has very low drift and high CMRR.

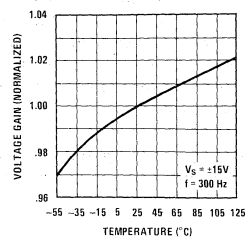


FIGURE 10. Instrumentation Amplifier Gain vs Temperature

Figure 11 shows a schematic of the instrumentation amplifier. The LM121 is used as the input stage and operated open-loop. It converts an input voltage to a differential output current at pins 1 and 8 to drive an op amp. The op amp acts as a current to voltage converter and has a single-ended output.

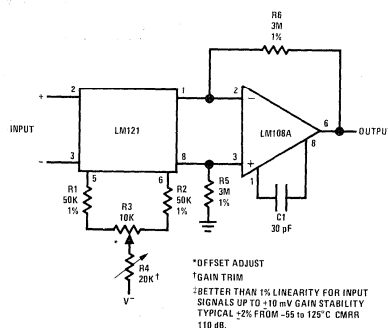


FIGURE 11. Gain of 1000 Instrumentation Amplifier

Resistors R<sub>1</sub> and R<sub>2</sub> with null pot R<sub>3</sub> set the operating current of the LM121 and provide offset adjustment. R<sub>4</sub> is a fine trim to set the gain at 1000. There is very little interaction between the gain and null pots.

This instrumentation amplifier is limited to a maximum input signal of  $\pm$ 10 mV for good linearity. At high signal levels the transfer characteristic of the LM121 become rapidly non-linear, as with any differential amplifier. Therefore, it is most useful as a high gain amplifier.

Since feedback is not applied around the LM121, CMRR is not dependent on resistor matching. This eliminates the need for precisely matched resistors as with conventional instrumentation amplifiers. Although the linearity and gain stability are not as good as conventional schemes, this amplifier will find wide application where low drift and high CMRR are necessary.

A precision reference using a standard cell is shown in Figure 12. The low drift and low input current of the LM121A allow the reference amplifier to buffer the standard cell with high accuracy. Typical long term drift for the LM121 operating at constant temperature is less than  $2\mu\text{V}$  per 1000 hours.

To minimize temperature gradient errors, this circuit should be shielded from air currents. Good

single-point wiring should also be used. When power is not applied, it is necessary to disconnect the standard cell from the input of the LM121 or it will discharge through the internal protection diodes.

## CONCLUSIONS

A new preamplifier for operational amplifiers has been described. It can achieve voltage drifts as low as many chopper amplifiers without the problems associated with chopping. Operating current is programmable over a wide range so the input characteristics can be optimized for the particular application. Further, using a preamp and a conventional op amp allows more flexibility than a single low-drift op amp.

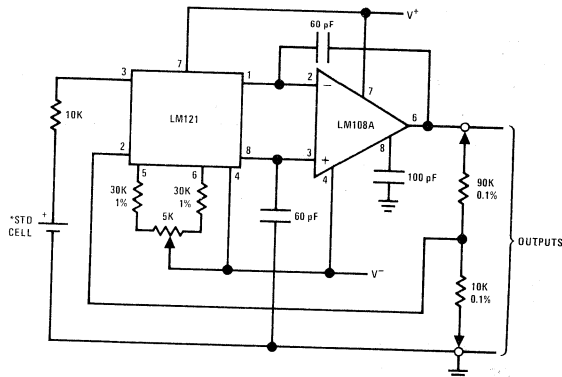


FIGURE 12. 10V Reference

# LM1800 (LM1310, LM1310E\*) Phase Locked Loop FM Stereo Demodulator

National Semiconductor  
Application Note 81  
T. D. Isbell  
D. S. Mishler  
June 1973



## INTRODUCTION

The LM1800 is a phase locked loop FM stereo demodulator built on a single monolithic die. In addition to separating left (L) and right (R) signal information from the detected IF output, the LM1800 features automatic stereo/monaural switching, 45 dB power supply rejection, and a 100 mA stereo indicator lamp driver. Particularly attractive is the low external part count and total elimination of coils. A single inexpensive potentiometer performs all tuning. The resulting FM stereo system delivers high fidelity sound while still meeting the cost requirements of inexpensive stereo receivers.

Figures 1 and 2 outline the role played by the LM1800 in the FM stereo receiver. The frequency domain plot shows that the composite input waveform contains L+R information in the audio band and L-R information suppressed carrier modulated on 38 kHz. A 19 kHz pilot tone, locked to the 38 kHz subcarrier at the transmitter, is also included. SCA information occupies a higher band but is of no importance in the consumer FM receiver.

The block diagram of the LM1800 shows the composite input signal applied to the audio frequency amplifier, which acts as a unity gain buffer to the decoder section. A second amplified signal is capacitively coupled to two phase detectors — one in the phase locked loop and the other in the

stereo switching circuitry. In the phase locked loop, the output of the 76 kHz voltage controlled oscillator (VCO) is frequency divided twice (to 38 then 19 kHz), forming the other input to the loop phase detector. The output of the loop phase detector adjusts the VCO to precisely 76 kHz. The 38 kHz output of the first frequency divider becomes the regenerated subcarrier which demodulates L-R information in the decoder section. The amplified composite and an "in phase" 19 kHz signal, generated in the phase locked loop, drive the "in phase" phase detector. When the loop is locked, the DC output voltage of this phase detector measures pilot amplitude. For pilot signals sufficiently strong to enable good stereo reception the trigger latches, applying regenerated subcarrier to the decoder and powering the stereo indicator lamp. Hysteresis, built into the trigger, protects against erratic stereo/monaural switching and the attendant lamp flicker.

In the monaural mode (electronic switch open) the decoder outputs duplicate the composite input signal except that the de-emphasis capacitors (from pins 3 and 6 to ground) roll off with the load resistors at 2 kHz. In the stereo mode (electronic switch closed), the decoder demodulates the L-R information, matrixes it with the L+R information, then delivers buffered separated L and R signals to output pins 4 and 5 respectively.

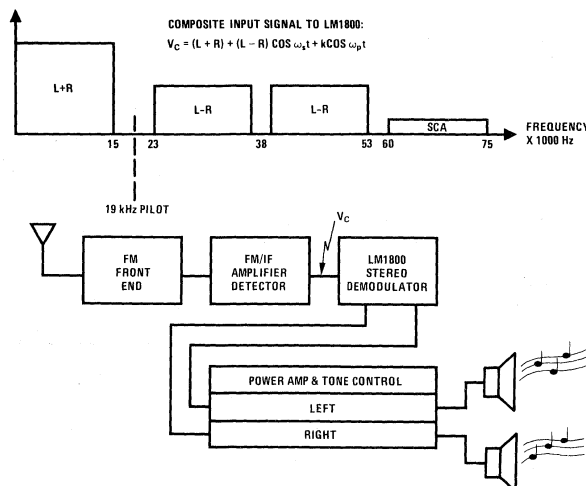


FIGURE 1. FM Receiver Block Diagram and Frequency Spectrum of LM1800 Input Signal

\*The information contained in this application note also generally applies to LM1310, LM1310E.

### CIRCUIT DESCRIPTION

The complex circuit schematic of Figure 13 is more easily understood by reducing it to four subsections:

- Regulator and Audio Amplifier
- Phase Locked Loop
- Stereo/Monaural Switching Circuitry
- Decoder and Output Section

### Regulator and Audio Amplifier

Transmission of power supply ripple and noise has plagued users of integrated FM stereo demodulators in the past. The introduction of a voltage regulator on the chip, along with improvements in the decoder output circuitry, provides excellent supply rejection, eliminating the need for costly supply filtering. Figure 3 shows an equivalent schematic of the 5.8V regulator.  $Z_2$  holds the voltage across

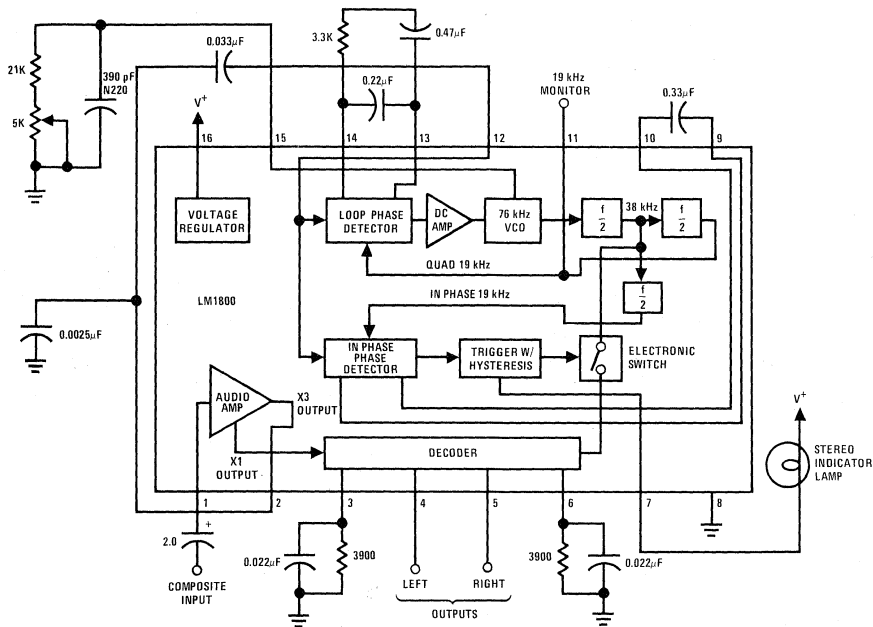


FIGURE 2. LM1800 Block Diagram

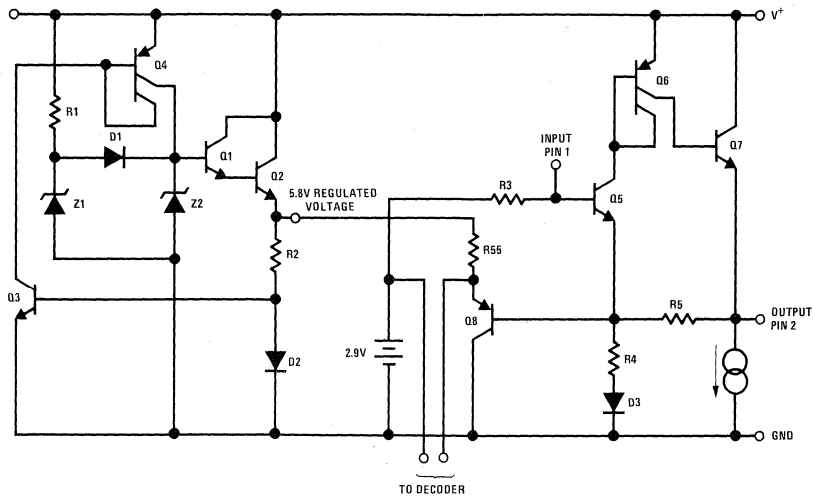


FIGURE 3. Regulator and Audio Amplifier



$R_2$  constant, thereby establishing a constant current through  $D_2$ ,  $Q_3$  and  $Q_4$ . The current through  $Z_2$  then depends on the voltage drop across  $Z_2$  and not on the supply line.  $R_1$ ,  $Z_1$  and  $D_1$  assure startup after which the voltage across  $D_1$  drops to zero, disconnecting  $R_1$  from the remainder of the regulator circuitry.

The audio amp is biased internally by 2.9V through  $R_3$  to the base of  $Q_5$ . Since the emitter current of  $Q_5$  is much less than that of  $Q_7$  and the base current of  $Q_8$  is also negligible, current through  $R_4$  approximately equals that through  $R_5$ . The DC quiescent voltage at the output pin becomes:

$$V_{P2} = V_{E5} + (V_{E5} - 0.7) R_5/R_4 = 5.4 \text{ volts}$$

and gain to a dynamic input is:

$$A_{\text{pin } 1 - \text{pin } 2} = 1 + R_5/R_4 = 3.0$$

A second signal path of unity gain exists through  $Q_5$  and  $Q_8$ . The potential at  $Q_8$ 's emitter is also approximately 2.9V, providing conveniently biased drive to the decoder section.  $R_3$  sets the input resistance at typically 45 k $\Omega$ .

#### Phase Locked Loop

A phase locked loop is a feedback system comprised of a phase detector, a low pass filter, and an error amplifier in the forward transmission path while a voltage controlled oscillator provides the feedback element. Figure 4 illustrates a simplified loop. Without an input signal the error voltage drops to zero. The VCO then oscillates at some free running frequency,  $f_0$ . As an input signal is introduced, the phase detector compares the phase (and frequency, since frequency is the time derivative of phase) of the input signal with that of the VCO, generating an error voltage related to the frequency difference. The error signal is filtered

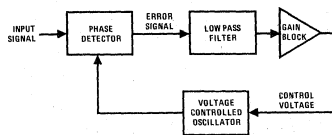


FIGURE 4. Basic Phase Locked Loop Block Diagram

and amplified before it is applied to the control input of the VCO. The control voltage forces the VCO frequency to move in the direction that reduces the frequency difference between the input signal and  $f_0$ . For free running frequencies sufficiently close to the incoming signal, the nature of loop feedback causes the VCO to synchronize to exactly the incoming frequency. Some finite phase difference exists between the two signals. This phase difference is necessary to generate the corrective error voltage for the VCO.

The LM1800 operates on precisely this principle except that the VCO free runs at approximately four times the frequency of the incoming pilot. Two frequency dividers provide a signal at the phase detector input sufficiently close in frequency to the 19 kHz pilot tone to accomplish lock. The loop provides sufficient gain to keep the phase error small, and the frequency dividers generate accurate 50% duty cycle waveforms, both necessary requirements for good stereo demodulation.

#### VCO

Consider the voltage controlled oscillator scheme outlined in Figure 5. At turn-on the non-inverting input rises rapidly to 1.2V as set by the resistor divider ( $R_{13}/R_{15}$ ), while the external capacitor holds the inverting input low. The output quickly rises to 5.8V and begins charging the capacitor through  $R_{11}$ . The output simultaneously lifts the non-inverting input rapidly to 4.7V. When the voltage across the capacitor also reaches 4.7V, the output drops low, reverse biasing the diodes while the capacitor begins discharging through the potentiometer. With the output low, the non-inverting input is again resistively set at 1.2V until the capacitor discharges and the cycle repeats. The capacitor voltage decays about twenty times slower than it charges, resulting in a repetition rate dominated by the external RC time constant.

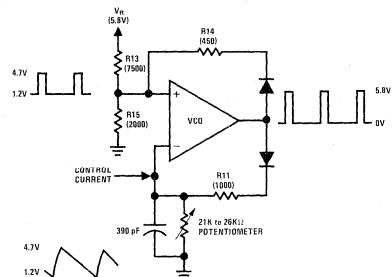


FIGURE 5. Equivalent Circuit of VCO

When the VCO is in its high state, the output is clamped at the regulated voltage. This causes the temperature coefficient of the trip points to be dependent on only the regulated voltage, resulting in an oscillation frequency quite independent of temperature.

Figure 6 details the frequency dividers used to transform the short duty cycle 76 kHz waveform into precisely 50% duty cycle 38 and 19 kHz waveforms. To understand their operation, first consider  $Q_{24}/Q_{25}$  saturated while  $Q_{23}/Q_{26}$  are in cutoff. As the trigger goes low the collector voltage for  $Q_{25}/Q_{26}$  collapses and conduction in them ceases. Since  $Q_{23}/Q_{24}$  are bistable by themselves,  $Q_{24}$  remains saturated and  $Q_{23}$  cutoff. With the trigger in this low state, the base of  $Q_{24}$  sits at one base-emitter voltage (0.7V) while the base of  $Q_{23}$  is at the saturation voltage of  $Q_{24}$

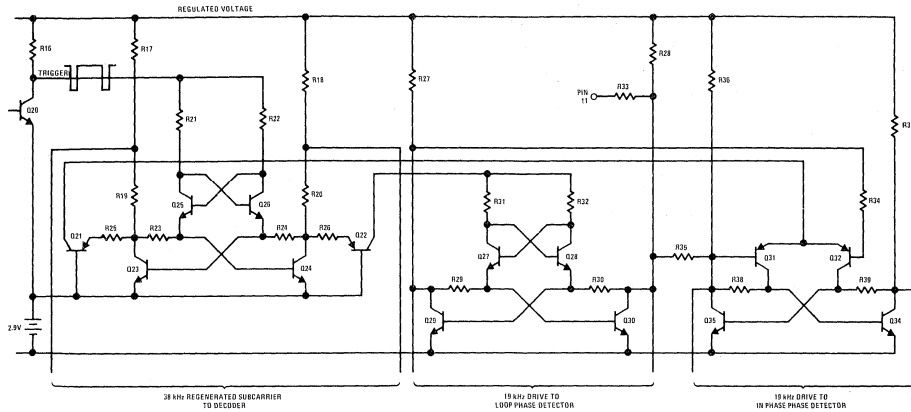


FIGURE 6. Frequency Dividers

(0.2V). On the rising edge of the trigger pulse,  $Q_{26}$  conducts before  $Q_{25}$  because of the different voltages on their emitters.  $Q_{26}$  saturates and drives enough current through  $R_{24}$  to saturate  $Q_{23}$  while  $Q_{24}$  goes to cutoff. Thus  $Q_{23}/Q_{24}$  change state on every rising edge of a trigger pulse, dividing the repetition rate of the trigger signal by two. The other two frequency dividers function similarly except that the third one is slaved in quadrature

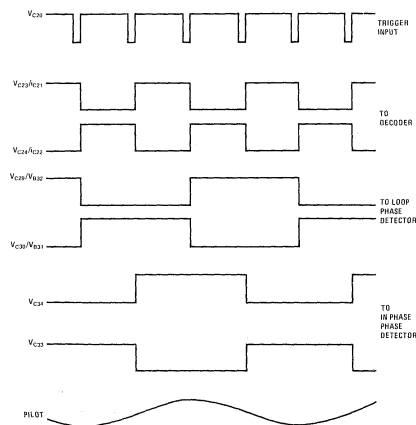


FIGURE 7. Frequency Divider Waveforms

with the second. Figure 7 shows the waveforms throughout the divider string.

#### Loop Phase Detector

The loop phase detector is shown equivalently in Figure 8. Consider the loop phase detector where the toggle is driven in quadrature with the pilot.

The waveforms show that zero volts DC appears across the capacitor. Any deviation from this quadrature relationship produces a voltage, which

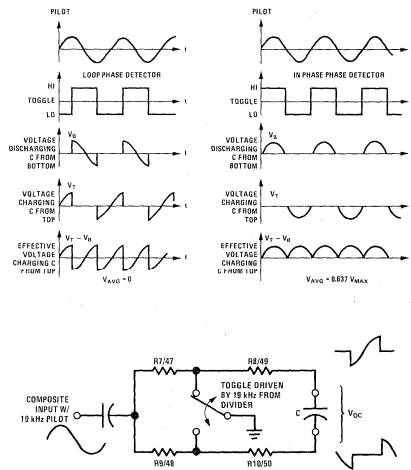


FIGURE 8. Phase Detector Performance

is a function of phase difference, across the capacitor. A second condition results when the toggle is driven in phase with the pilot. In this case the DC voltage across the capacitor measures pilot tone amplitude and is used to drive the stereo-monaural switching circuitry.

The DC amplifier in the phase locked loop is standard differential with push-pull output, maintaining excellent temperature stability in the loop.

#### Stereo/Monaural Switching Circuitry

Composite inputs sufficiently large for good quality stereo switch the LM1800 into the stereo mode

via the circuitry of Figure 9. The differential pair Q<sub>47</sub>/Q<sub>48</sub> is driven by the DC output of the "in phase" phase detector. When the phase locked loop is locked, this differential input voltage to Q<sub>47</sub>/Q<sub>48</sub> is proportional to pilot amplitude (as explained in previous section and Figure 8). The emitter area of Q<sub>47</sub> is five times larger than that of Q<sub>48</sub>, building in 40 mV offset voltage. Until the base of Q<sub>48</sub> is 40 mV higher than the base of Q<sub>47</sub>, collector current in Q<sub>47</sub> is larger than collector current in Q<sub>48</sub>. Transistor design of Q<sub>49</sub> constrains its beta to unity. So long as I<sub>C47</sub> is larger than I<sub>C48</sub>, Q<sub>49</sub> remains in saturation (holding Q<sub>50</sub> in cutoff). When the 40 mV offset voltage is overcome in Q<sub>47</sub>/Q<sub>48</sub>, Q<sub>49</sub> comes out of saturation and Q<sub>50</sub> enters conduction. Q<sub>50</sub>, Q<sub>51</sub>, D<sub>5</sub>, and R<sub>51</sub> form a positive feedback loop which regenerates when Q<sub>50</sub> is allowed to conduct. R<sub>51</sub> is chosen to halt the regeneration process at I<sub>C51</sub> = 30 μA. The latched loop current drives the lamp driver Darlington (Q<sub>54</sub>/Q<sub>55</sub>) as well as Q<sub>57</sub> (via Q<sub>52</sub> and Q<sub>53</sub>). The signal to the decoder switches from common to differential mode 38 kHz and stereo demodulation begins. Should the input composite waveform decrease by 6 dB, the differential voltage back at Q<sub>47</sub>/Q<sub>48</sub> reduces to 20 mV. Under this condition the current flowing from Q<sub>49</sub> into Q<sub>51</sub> (as Q<sub>49</sub> returns toward saturation) is sufficient to unlatch the loop, prohibiting drive to both Q<sub>57</sub> and Q<sub>54</sub>/Q<sub>55</sub>. The signal driving the decoder returns to common mode 38 kHz and monaural reception resumes. R<sub>52</sub> and Q<sub>56</sub> limit cold lamp surge currents to about 250 mA.

### Decoder and Output Section

The basic decoder section shown in Figure 10 has been used previously in the LM1304, LM1305, LM1307, LM1307E series, and is well described in reference 2. In an effort to transform the rigor into intuition, consider first Q<sub>43</sub>, Q<sub>44</sub>, and the emitter matrix resistors (R<sub>44</sub>, R<sub>45</sub>, R<sub>46</sub>). Under small signal conditions the emitter of Q<sub>43</sub> remains at a constant voltage while the emitter of Q<sub>44</sub> tracks the composite input waveform applied to its base. Analysis of the simplified circuit shown in Figure 11 produces the current waveforms through R<sub>44</sub> and R<sub>45</sub>. These currents are not equal and opposite as in a standard multiplier because R<sub>46</sub> in no way approximates a current source. Rather, the currents through R<sub>44</sub> and R<sub>45</sub> can be shown to be related by a constant:

$$K = I_{R44}/I_{R45} = R_{46}/(R_{45} + R_{46})$$

For NPN transistors operating in their active regions, collector current approximately equals emitter current, then:

$$I_{C43} = KI_{C44}$$

Since the upper quad transistors (Q<sub>39</sub>, Q<sub>40</sub>, Q<sub>41</sub>, Q<sub>42</sub>) operate as antiphase switches, the base current resulting through Q<sub>38</sub> becomes the sum of I<sub>C44</sub> gated by Q<sub>42</sub> and I<sub>C43</sub> gated by Q<sub>40</sub>. These upper quad transistors alternately pass or block the currents flowing in Q<sub>43</sub> and Q<sub>44</sub>. This gating

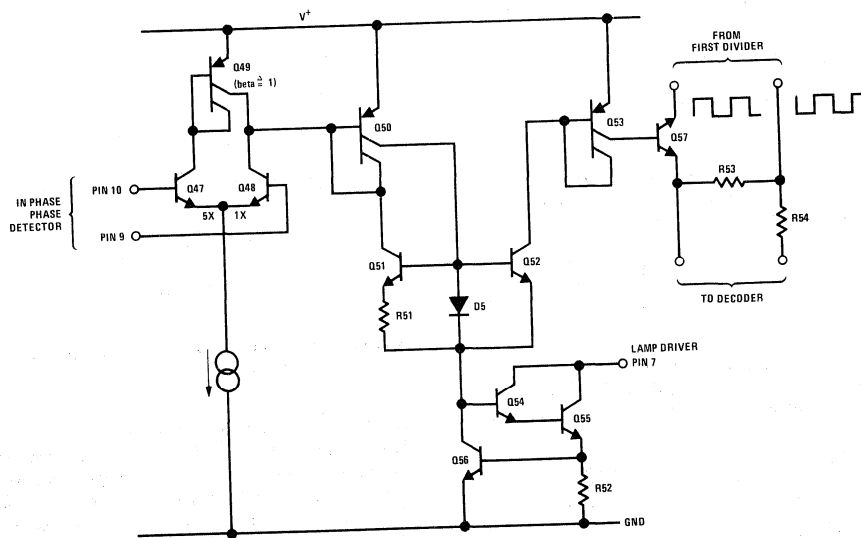


FIGURE 9. Stereo/Monaural Switch

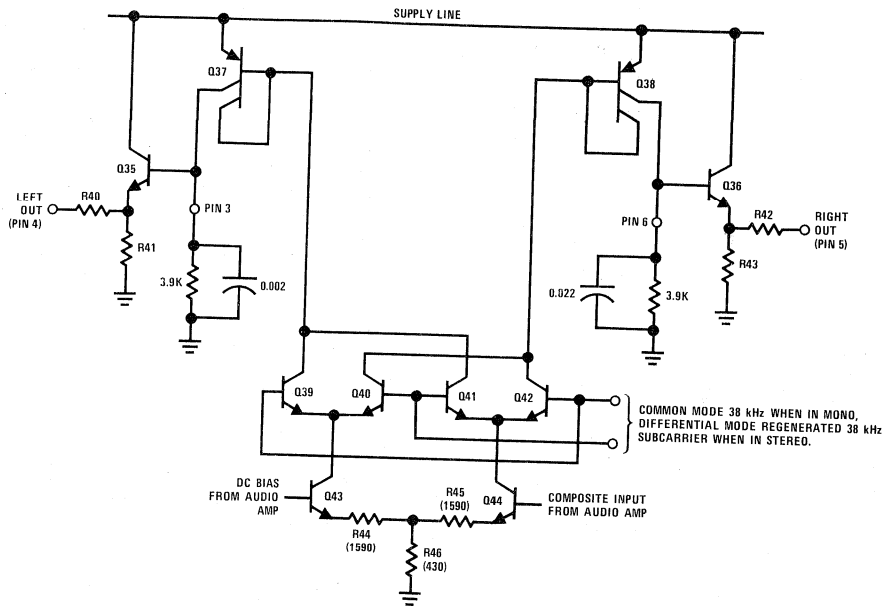


FIGURE 10. Decoder and Output Section

action is represented mathematically in Figure 12. Applying the gating function to the currents in  $Q_{43}$  and  $Q_{44}$ :

$$I_{B38} = V_C \left[ \frac{1}{2} - \frac{2}{\pi} \cos \omega_s t \right] - K V_C \left[ \frac{1}{2} + \frac{1}{\pi} \cos \omega_s t \right]$$

where  $V_C$  = composite input signal

and  $\omega_s$  = subcarrier (38 kHz)

Substituting the expression for  $V_C$  (given in Figure 1), carrying out the algebra, and retaining only the low frequency terms gives:

$$I_{B38} = L \left[ 0.5 - 0.5K - \frac{K+1}{\pi} \right] + R \left[ 0.5 - 0.5K + \frac{K+1}{\pi} \right]$$

Equating the coefficient of the left (L) term to zero, yields a value for K of 0.22. Thus designing the matrix resistors,  $R_{44}$ ,  $R_{45}$ ,  $R_{46}$  to give this


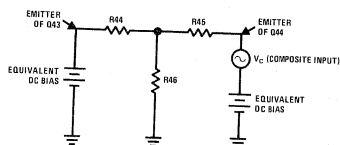


FIGURE 11. Equivalent Circuit for Decoder Matrix

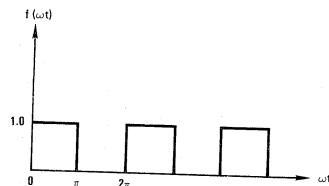value for K cancels all left information from the  $Q_{38}$  current. The base current of  $Q_{38}$  then is proportional to the right (R) separated signal.



$$f(\omega t) = \frac{1}{2} + \frac{2}{\pi} \sum_{n=1}^{\infty} \frac{1}{n} \cos n\omega t$$

$$= \frac{1}{2} + \frac{2}{\pi} \cos \omega t + \dots$$

FIGURE 12. Fourier Analysis of Decoder Switching Waveform

Similar analysis can be performed to show that the base current of  $Q_{37}$  contains only left (L) separated signal. Amplification and level shifting of these base currents occurs in fixed beta transistors  $Q_{37}$  and  $Q_{38}$ , and the resultant currents drive external grounded loads at pins 3 and 6. Since the collector currents of  $Q_{37}$  and  $Q_{38}$  depend only on their respective base currents, supply ripple and noise are rejected from the output pins.  $Q_{35}$  and  $Q_{36}$  serve as output buffers with  $R_{40}$  and  $R_{42}$  setting the output resistance at typically  $1300\Omega$ .

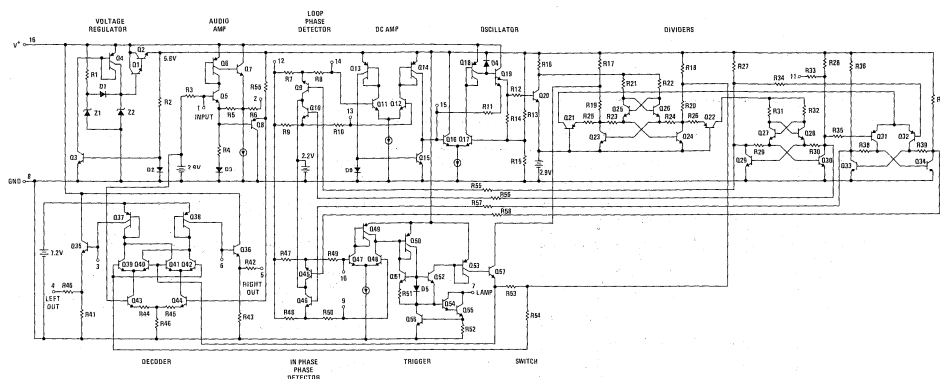


FIGURE 13. LM1800 Equivalent Schematic

In the monaural mode the upper quad transistors are driven by a common mode signal which causes all four transistors to conduct equally. This passes the composite input directly to the outputs where the de-emphasis capacitors serve to roll off the higher frequency unwanted information. Further, the LM1800 offers improved distortion over earlier integrated demodulators. As the signal driving the base of  $Q_{44}$  increases in amplitude, the AC currents through  $Q_{43}$  and  $Q_{44}$  become a significant percentage of the DC bias currents. In this manner the transconductance of  $Q_{43}$  and  $Q_{44}$  is modulated by the incoming signal resulting in second harmonic distortion. To reduce this effect, the base bias potentials of  $Q_{43}$  and  $Q_{44}$  is modulated by the incoming signal resulting in second harmonic distortion. To reduce this effect, the base bias potentials of  $Q_{43}$  and  $Q_{44}$  is modulated by the incoming signal resulting in second harmonic distortion. To reduce this effect, the base bias potentials of  $Q_{43}$  and  $Q_{44}$  is modulated by the incoming signal resulting in second harmonic distortion.

### CIRCUIT PERFORMANCE

The circuit in Figure 14 illustrates the simplicity of designing an FM stereo demodulation system using the LM1800.  $R_3$  and  $C_3$  establish an adequate loop capture range and a low frequency well damped natural loop resonance.  $C_3$  has the effect of shunting phase jitter, a dominant cause of high frequency channel separation problems. Recall that the 38 kHz subcarrier regenerates by phase locking the output of a 19 kHz divider to the pilot tone. Time delays through the divider result in the 38 kHz waveform leading the transmitted subcarrier. Addition of capacitor  $C_9$  ( $0.0025\mu\text{F}$ ) at pin 9 introduces a lag at the input to the phase lock loop, compensating for these frequency divider delays. The output resistance of the audio amplifier is designed at  $500\Omega$  to facilitate this connection.

Table I and Figures 15 through 27 detail typical performance resulting from this basic hookup. The excellent supply rejection characteristics shown,

coupled with the fact that supply current drain is nearly independent of supply voltage, somewhat simplifies receiver power supply requirements. The low drain current, even for a 24V supply, results in cooler circuit operation and increased reliability. Figure 22 shows that increasing the size of input coupling capacitor  $C_6$  improves low frequency channel separation by reducing the phase shift of the lower frequency components in the composite waveform.

Figure 27 illustrates an interesting characteristic of the LM1800: channel separation increases as the VCO is detuned in either direction. The separation peaks change in size for different signal frequencies and change in position (% detuning) for changing composite amplitudes. If the VCO free running frequency is set at precisely 19 kHz, separation remains constant over a wide range of composite amplitude levels, signal frequencies, temperature changes, and component drifts. The 19 kHz monitor available to the customer at pin 11 can be fed into a frequency counter for accurate adjustment of the VCO free running frequency. If a frequency counter is not available, the VCO can be adjusted by utilizing the fact that capture range is symmetrical about the incoming pilot:

- (a) rotate frequency adjust pot full CCW
- (b) insert weak composite input signal
- (c) rotate pot CW until stereo lamp comes on, note position of pot ( $R_x$ )
- (d) remove composite and rotate pot full CW
- (e) reinsert weak composite input signal
- (f) rotate pot CCW until stereo lamp comes on again, note position of pot ( $R_y$ )
- (g) set pot midway between  $R_x$  and  $R_y$ .

Figure 28 is included for the user who is willing to sacrifice some performance, particularly channel separation at high input levels and low frequencies to eliminate two external capacitors and reduce the electrolytic input coupling cap size.

On either circuit, some improvement in channel separation can be attained by altering the VCO

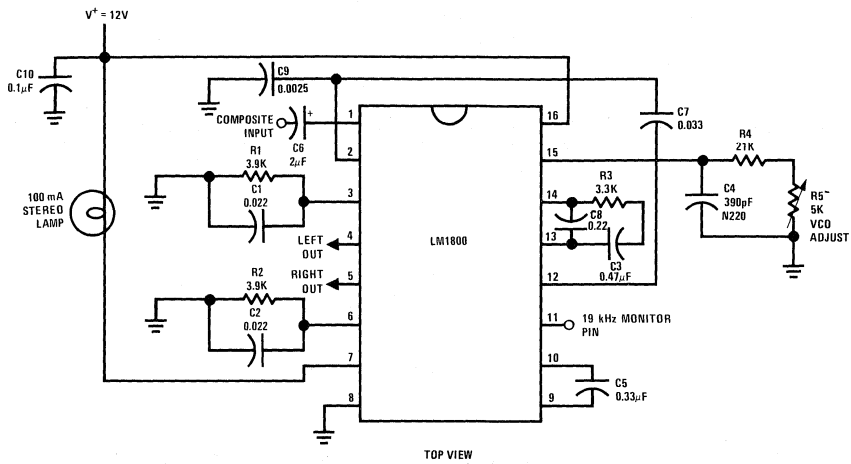



FIGURE 14. Typical Application Circuit

TABLE 1.


PARAMETERS	CONDITIONS	TYP	UNITS
Supply Current	Lamp "OFF"	21	mA
Lamp Driver Saturation Voltage	100 mA Lamp Current	1.3	V
Lamp Driver Leakage Current		1	nA
Pilot Level for Lamp "ON"	Pin 11 Adjusted for 19 kHz $\pm 10$ Hz	16	mV
Pilot Level for Lamp "OFF"	Pin 11 Adjusted for 19 kHz $\pm 10$ Hz	8	mV
Stereo Lamp Hysteresis		6	dB
Stereo Channel Separation	100 Hz (Note 1)	40	dB
	1000 Hz (Note 1)	45	dB
	10000 Hz (Note 1)	45	dB
Monaural Channel Unbalance	200 mVrms, 1000 Hz Input	0.3	dB
Recovered Audio	200 mVrms, 400 Hz Input	190	mVrms
Total Harmonic Distortion	500 mVrms, 1000 Hz Monaural Input	0.5	%
Capture Range	25 mV of 19 kHz pilot	$\pm 4$	% of $f_0$
Supply Ripple Rejection	600 mVrms, 200 Hz Ripple	45	dB
Dynamic Input Resistance		45	k $\Omega$
Dynamic Output Resistance		1300	$\Omega$
SCA Rejection	200 mVrms Composite at 67 kHz	50	dB
Ultrasonic Frequency Rejection	Combined 19 and 38 kHz	33	dB

**Note 1:** The stereo input signal is made by summing 123 mVrms left or right modulated signal with 25 mVrms of 19 kHz pilot tone, measuring all voltages with an average responding meter calibrated in rms, the resulting waveform is about 800 mVp-p. VCO adjusted to 19kHz  $\pm 10$ Hz.


**FIGURE 15. Supply Drain**

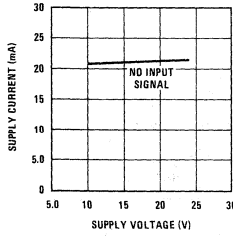


**FIGURE 16. Total Harmonic Distortion**

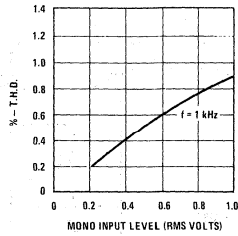


**FIGURE 17. Supply Ripple Rejection**

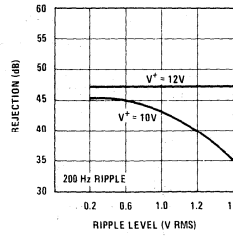


**FIGURE 18. Supply Ripple Rejection**

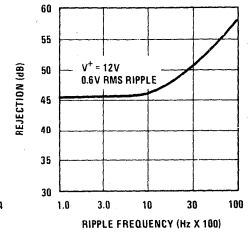


**FIGURE 19. VCO Temperature Stability**

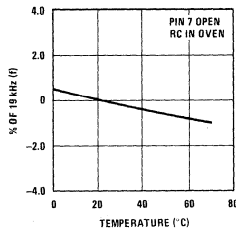


**FIGURE 20. VCO Supply Sensitivity**

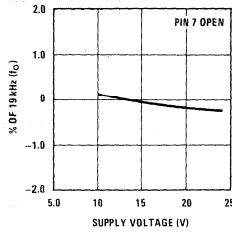


**FIGURE 21. Pilot Level For Lamp On**

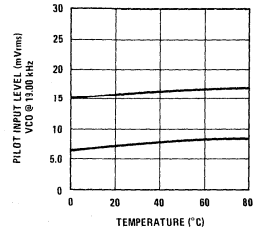


**FIGURE 22. Channel Separation**

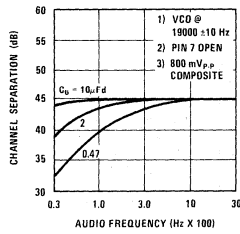


**FIGURE 23. Channel Separation**

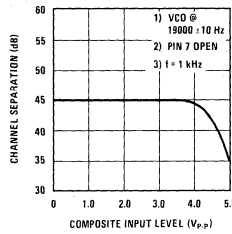


**FIGURE 24. Output Frequency Spectrum**

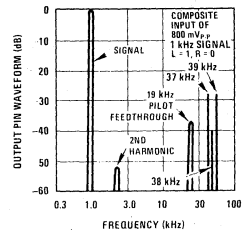


**FIGURE 25. Capture Range**

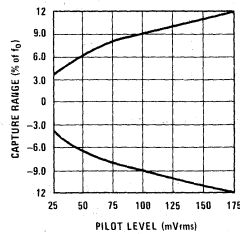

**FIGURE 26. Lamp Driver Characteristics**

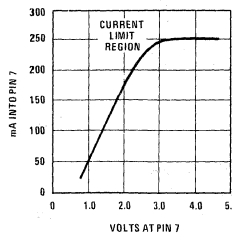

**FIGURE 27. Channel Separation and VCO Tuning**

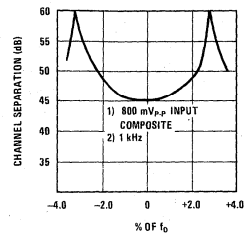

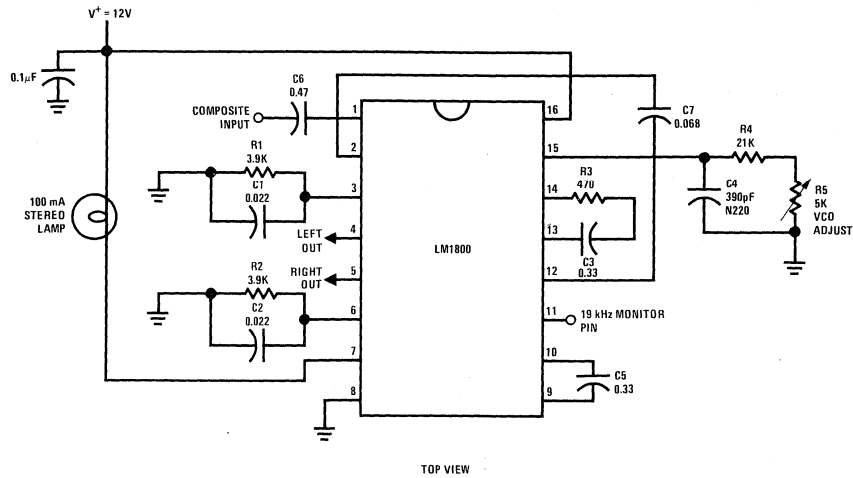


FIGURE 28. Minimum Parts Count Application Circuit

slightly. The loop gain can be shown to decrease for a decrease in VCO resistance ( $R_4 + R_5$  in Figure 14). Maintaining a constant RC product, while increasing the capacity from 390 pF to 510 pF narrows the capture range by about 25%. Although the resulting system has slightly improved channel separation, it is more sensitive to VCO tuning.

When the circuits so far described are connected in an actual FM receiver, channel separation often suffers due to imperfect frequency response of the IF stage. The input lead network of Figure 29

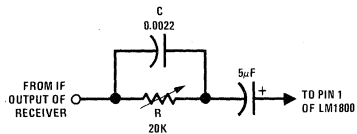


FIGURE 29. Compensation for Receiver IF Roll-off

can be used to compensate for roll off in the IF and will restore high quality stereo sound. Should a receiver designer prefer a stereo/monaural switching point different than those programmed into the LM1800 (pilot: 16 mVrms on, 8.0 mVrms off typical), the circuit of Figure 30 provides the desired flexibility.

The user who wants slightly increased voltage gain through the demodulator can increase the size of the load resistors ( $R_1$  and  $R_2$  of Figure 14 or 28), being sure to correspondingly change the de-emphasis capacitors ( $C_1$  and  $C_2$ ). Loads as high as 5600Ω may be used (gain of 1.4). Performance of the LM1800 is virtually independent of the supply voltage used (from 10 to 24V) due to the on chip regulator.

Although the circuit diagrams show a 100 mA indicator lamp, the user may desire an LED. This presents no problem for the LM1800 so long as a resistor is connected in series to limit current to a safe value for the LED. The lamp or LED can be powered from any source (up to 24V), and need not necessarily be driven from the same supply as the LM1800.


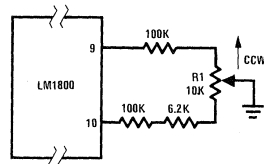




FIGURE 30. Stereo/Monaural Switch Point Adjustment

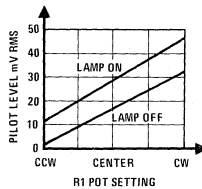Utilization of the phase locked loop principle enables the LM1800 to demodulate FM stereo signals without the use of troublesome and expensive coils. The numerous features available on the demodulator make it extremely attractive in a variety of home and automotive receivers. Indeed the LM1800 represents a new generation in integrated stereo FM demodulators.



## REFERENCES

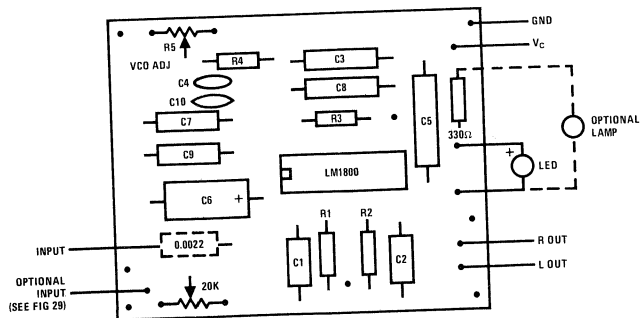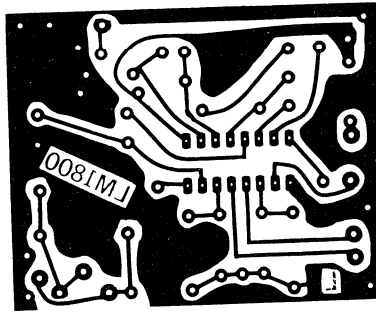1. Blaser, L. and Cocke, W., "The  $\mu A758$ , A Phase Locked Loop FM Stereo Multiplex Decoder." Fairchild Application Note 319, June 1972.
2. Hector Gasquet, "A Monolithic Integrated FM Stereo Decoder System." Motorola Application Note AN-432A.
3. Michael J. Gay, "A Monolithic Phase-Lock-Loop Stereo Decoder." IEEE Transactions on Broadcast and TV Receivers, Vol. BTR-17, No. 3, August 1971.
4. Thomas B. Mills, "The Phase Locked Loop IC as a Communication System Building Block." National Semiconductor Application Note AN-46, June 1971.
5. "Phase Locked Loops Applications Book," Signetics Corporation, 1972.





# LM125, LM126 Precision Dual Tracking Regulators

National Semiconductor  
Application Note 82  
Todd Smathers  
Nello Sevastopoulos  
May 1974  
Revised August 1980



## INTRODUCTION

The LM125 and LM126 family of devices are precision, dual, tracking, monolithic voltage regulators. Each provides separate positive and negative regulated outputs, thus simplifying dual power supply designs. Operation requires few or no external components depending on the application. Internal settings provide fixed output voltages: the LM125 at  $\pm 15V$  and the LM126 at  $\pm 12V$ .

Each regulator is protected from excessive internal power dissipation by a thermal shutdown circuit which turns off the regulator whenever the chip reaches a preset maximum temperature. Other features include both internal and external current limit sensing for device protection while operating with or without external current boost. For applications requiring more current than the internal current limit will allow, boosted operation is possible with the addition of a one NPN pass transistor per regulator. External resistors sense load current for controlling the limiting circuitry. Internal frequency compensation is provided on both positive and negative regulators. The internal voltage reference pin is brought out to facilitate noise filtering when desired.

## CIRCUIT DESCRIPTION

Figure 1 shows a block diagram of the basic dual tracking regulator. A voltage reference establishes a fixed dc level, independent of supply or temperature variations, at the non-inverting input to the negative regulator Error Amplifier. The Error Amplifier drives the Output Control Circuit which includes the high current output transistors, current limiting, and thermal shutdown circuitry.

The negative regulator output voltage is established by comparing the Voltage Reference against a fraction of the output as set by  $R_A$  and  $R_B$ .

To achieve the desired tracking action of the positive regulator, a voltage established between the positive and negative regulator outputs by resistors  $R_C$  and  $R_D$  is compared to ground by the positive regulator Error Amplifier. This insures

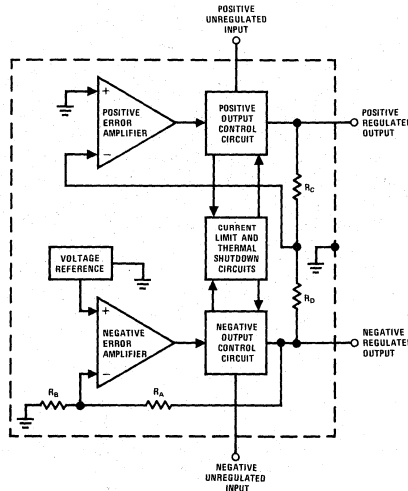


FIGURE 1. Block Diagram for the Basic Dual Tracking Regulator

that the positive regulator output voltage will always equal the negative regulator output voltage multiplied by the ratio of  $R_C$  to  $R_D$ . This ratio is unity for the LM125 ( $V_O = \pm 15V$ ), and LM126 ( $V_O = \pm 12V$ ). The positive regulator Output Control Circuit is essentially the same as that in the negative regulator.

The current limit and thermal shutdown circuitry sense the output load current and die temperature

respectively and switch off all output drive capability upon reaching their predetermined limits.

Figure 2 gives a more detailed picture of the negative regulator circuitry. The temperature compensated reference voltage appears at the non-inverting input of the differential amplifier, Q19 and Q20, while an error signal proportional

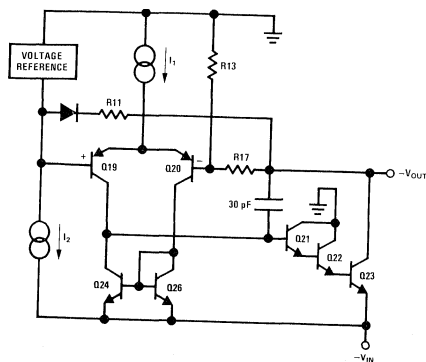


FIGURE 2. Simplified Negative Regulator

to any change in output voltage is applied to the other input. This error signal is amplified by the differential amplifier, Q19 and Q20, and by the triple Darlington Q21, Q22, Q23 to produce a current change through R13 and R17 which brings the output voltage back to its original value. Loop gain is high, typically 88 dB at low output currents, so a 30 pF compensating capacitor is used to guarantee stability. Since  $-V_{OUT}$  is the output of a high gain feedback amplifier, high supply rejection is ensured.

Figure 3 shows the basic positive regulator. This is actually an inverting operational amplifier.

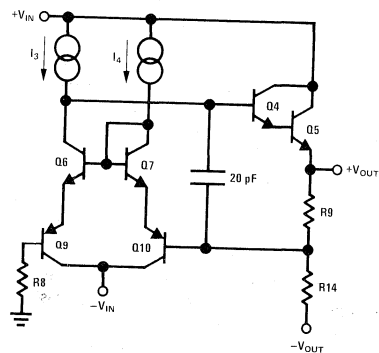


FIGURE 3. Simplified Positive Regulator

The negative regulated voltage ( $-V_{OUT}$ ) is applied to the current summing input through R14 while the output ( $+V_{OUT}$ ) is fed-back via R9. Then

$+V_{OUT}$  is simply  $-(R9/R14)(-V_{OUT})$ . Any change in the positive regulator output will create an error signal at the base of Q10 which will be amplified and sent to the voltage follower, Q4 and Q5, forcing the output voltage to track the input voltage. Here the loop gain is on the order of 66 dB so a compensating capacitor of approximately 20 pF is used to ensure amplifier stability.

The circuitry used for regulator start up, biasing, temperature sensing, and thermal shutdown is shown in Figure 4. The field effect transistor Q28, is initially ON allowing the negative input voltage to force current through zener diode Q34. When enough current flows to fully establish the zener voltage, transistor Q29, Q30 and Q31 turn on and bias up all current sources. The zener voltage also decreases the gate to source voltage of the FET, pinching it off to a lower current value to reduce quiescent power dissipation.

The thermal sensing and shutdown circuitry is comprised of Q34, Q29, Q35, Q32, Q37, Q38, R27, R29, R30, R31, and R33. The voltage divider made up of R29 and R30 provides a relatively fixed bias voltage  $V_1$  at the bases of Q35 and Q36, holding them in the OFF state. When the chip temperature increases to a maximum permissible level, the base to emitter voltage of Q35 and/or Q36 will have decreased sufficiently so that  $V_1$  is now high enough to turn them ON. This causes a voltage drop across R27 sufficient to turn on Q32 which switches Q37 and Q38 to a conducting state shunting all output drive current to  $-V_{IN}$ . The regulator output voltages are then clamped to zero. Transistors Q35 and Q36 are located on the chip near the regulator output devices so they will see the maximum temperatures reached on the chip, ensuring that neither regulator will ever see more than this preset maximum temperature. The collectors of Q35 and Q36 are tied together so that if either regulator reaches the thermal shutdown temperature, both regulators will shutdown. This ensures that the device can never be destroyed because of excessive internal power dissipation in either regulator.

Figure 5 shows the current limiting circuitry used in the positive regulator; the negative regulator current limiter is identical. The internal current limiter is comprised of Q8 and R5; the external current limiter is comprised of Q11 and an external resistor  $R_{CL}$ . Both operate in a similar manner. As the output current through Q5 increases, the voltage drop across resistor R5 eventually turns ON Q8 and shunts all base drive away from the output devices, Q4 and Q5. The maximum load current available with this circuit is approximately 250 mA at  $T_j = 25^\circ\text{C}$  (see Figure 9).

The external current limiting circuit works in a similar manner. Here the output current is sensed across the external resistor  $R_{CL}$ . When the voltage

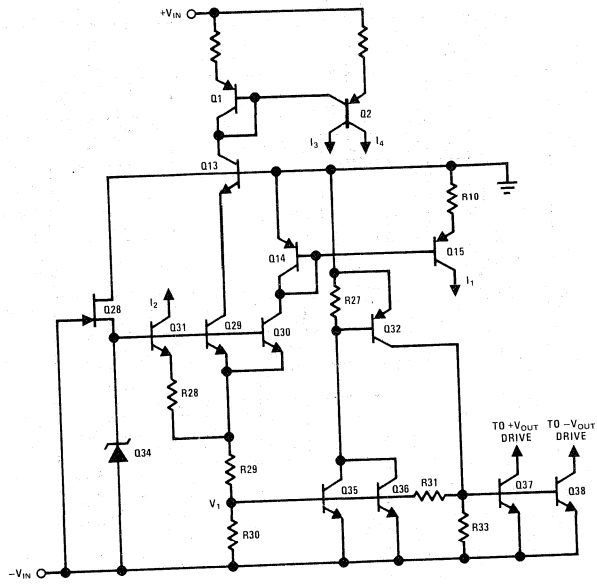


FIGURE 4. Start-up, Biasing and Thermal Shutdown Circuitry

drop across  $R_{CL}$  is sufficient to turn ON transistor Q11, the output drive current is switched away from the output devices Q4 and Q5. This externally set current limit is particularly valuable when used with an external current boosting pass transistor where the current limit could be set to protect that transistor from excessive power dissipation.

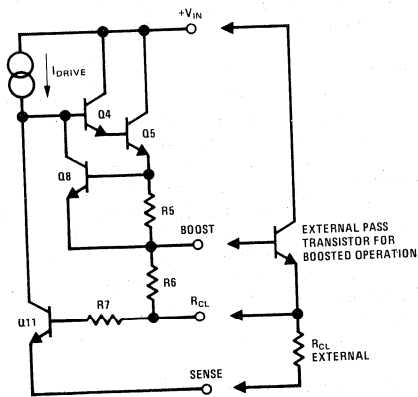


FIGURE 5. Positive Regulator Current Limiting Circuitry

The constant voltage reference circuit is shown in Figure 6. Zener diode  $Z_1$  has a positive temperature coefficient of known value.  $V_{BE}$  of Q18 (negative temperature coefficient) is multiplied by the ratio

of R18 and R19 and added to the positive TC of  $Z_1$  to produce a near zero TC voltage reference. Current source  $I_2$  is used only during start-up.


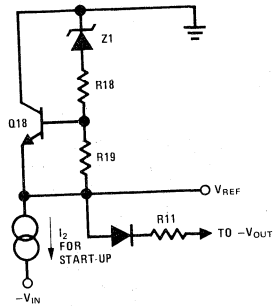


FIGURE 6. Voltage Reference Circuitry

Figure 7 shows the complete schematic of the LM125, LM126 family of dual regulators. Diodes Q12 and Q17 protect the output transistors, plus any external pass devices used, from breakdown in the event the positive and negative regulated outputs become shorted. Transistors Q6 and Q7 offer full differential voltage gain with the convenience of single ended output. Transistors Q13 and Q33 insure that operation with  $\pm 30V$  input is possible. Q24 and Q26 in the negative regulator amplifier provide single ended output from a differential input with no loss in gain.

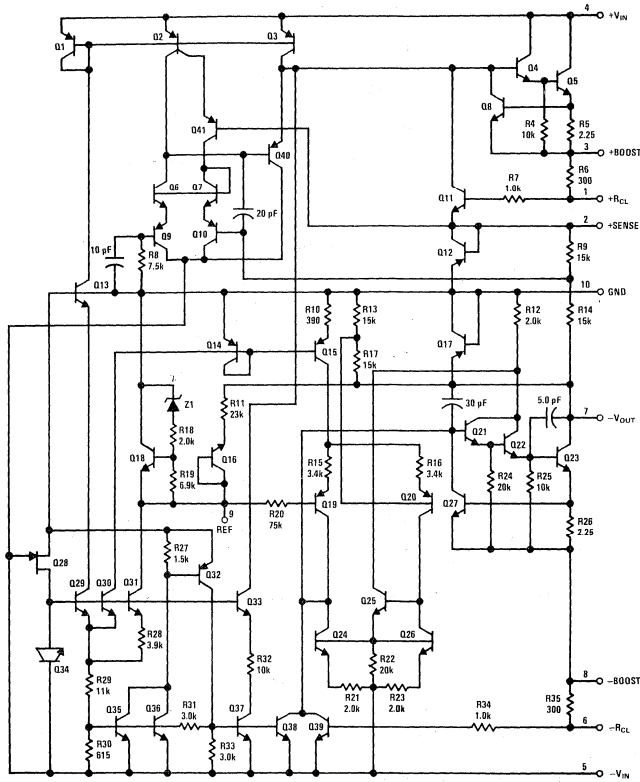


NOTE: PIN NUMBERS APPLY TO METAL CAN PACKAGE ONLY.

FIGURE 7. LM125, LM126
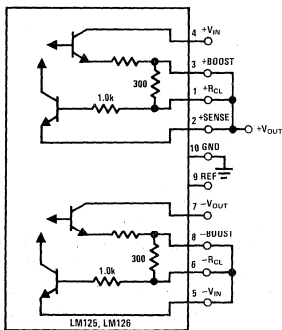
## APPLICATIONS

The basic dual regulator is shown connected in Figure 8. The only connections required other than plus and minus inputs, outputs, and ground



NOTE: PIN NUMBERS FOR METAL CAN PACKAGE ONLY.

FIGURE 8. Basic Dual Regulator

are to complete the output current paths from +R<sub>CL</sub> to +V<sub>OUT</sub> and from -R<sub>CL</sub> to -V<sub>IN</sub>. These may be a direct shorts if the internal preset current

limit is desired, or resistors may be used to set the maximum current at some level less than the internal current limit. The internal 300Ω resistors from pins 3 to 1 and pins 8 to 6 should be shorted as shown when no external pass transistors are used. To improve line ripple rejection and transient response, filter capacitors may be added to the inputs, outputs, or both, depending on the unregulated input available. If a very low noise output voltage is desired, a capacitor may be connected from the reference voltage pin to ground. Thus shunting noise generated by the reference zener. Figure 9 shows the internal current limiting characteristics for the basic regulator circuit of Figure 8.

## HIGH CURRENT REGULATOR

For applications requiring more supply current than can be delivered by the basic regulator, an external NPN pass transistor may be added to each regulator. This will increase the maximum output current by a factor of the external transistor beta. The circuit for current boosted operation is shown in Figure 10.

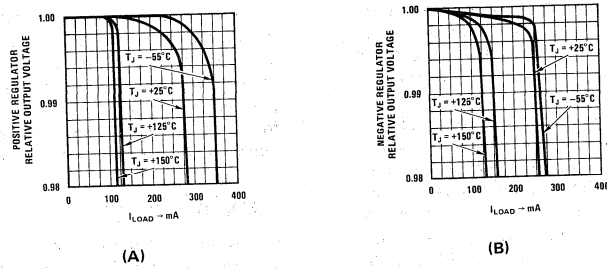


FIGURE 9. Internal Current Limiting Characteristics

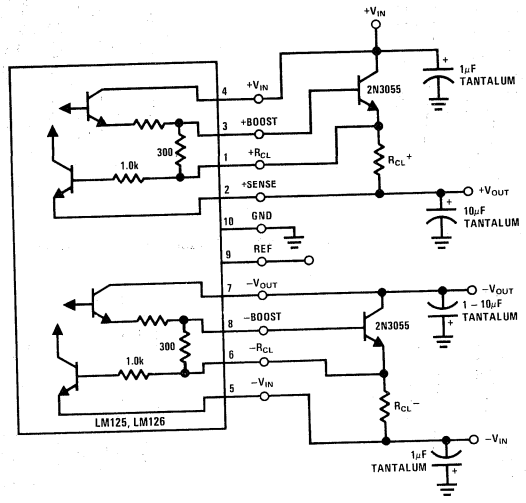


FIGURE 10. Boosted High Current Regulator

In the boosted mode, current limiting is often a necessary requirement to insure that the external pass device is not overheated or destroyed. Experience shows this to be the usual cause of IC regulator failure. If the regulator output is grounded the pass device may fail and short, destroying the regulator. To limit the maximum output current, a series resistor ( $R_{CL}$  in Figure 10) is used to sense load current. The regulator will current limit when the voltage drop across  $R_{CL}$  equals the current limit sense voltage found in Figure 11. Figure 12 shows the external current limiting characteristics unboosted and Figure 13 shows the external current limiting characteristics in the boosted mode.

To ensure circuit stability at high currents in this configuration, it may be necessary to bypass each input with low inductance, tantalum capacitors to prevent forming resonant circuits with long input leads. A  $C \geq 1\mu F$  is recommended. The same problem can also occur at the regulator

output where a  $C \geq 10\mu F$  tantalum will ensure stability and increase ripple rejection.

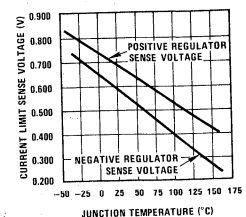


FIGURE 11. Current Limit Sense Voltage for a 0.1% Change in Regulated Output Voltage

The 2N3055 pass device is low in cost and maintains a reasonably high beta at collector currents up to several amps. The devices 2N3055 may be of either planar or alloy junction construction. The planar devices, have a high  $f_T$  providing more stable operation due to low phase shift. The

alloy devices, with  $f_T$  typically less than 1.0 MHz, may require additional compensation to guarantee stability. The simplest of compensation for the slower devices is to use output filter capacitor values greater than  $50\mu\text{F}$  (tantalum). An alternative is to use an RC filter to create a leading phase response to cancel some of the phase lag of the devices. The stability problem with slower pass transistors, if it occurs at all, is usually seen only on the negative regulator. This is because the positive regulator output stage is a conventional Darlington while the negative output stage contains three devices in a modified triple

Darlington connection giving slightly more internal phase shift. Additional compensation may be added to the negative regulator by connecting a small capacitor in the 100 pF range from the negative boost terminal to the internal reference. Since the positive regulator uses the negative regulator output for a reference, this also offers some additional indirect compensation to the positive regulator.

### 7 AMP REGULATOR

In Figure 14 the single external pass transistor has been replaced by a conventional Darlington pair

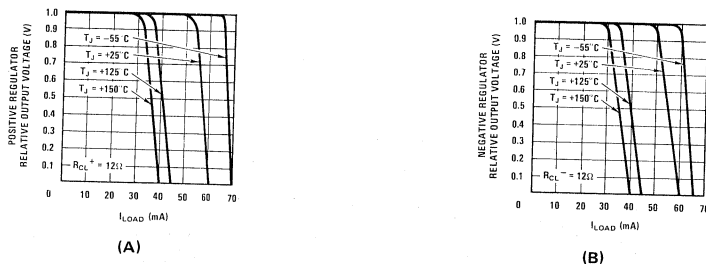


FIGURE 12. External Current Limiting Characteristics- Unboosted

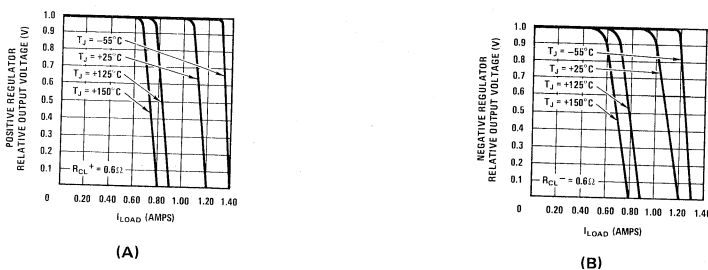


FIGURE 13. External Current Limiting Characteristics- Boosted

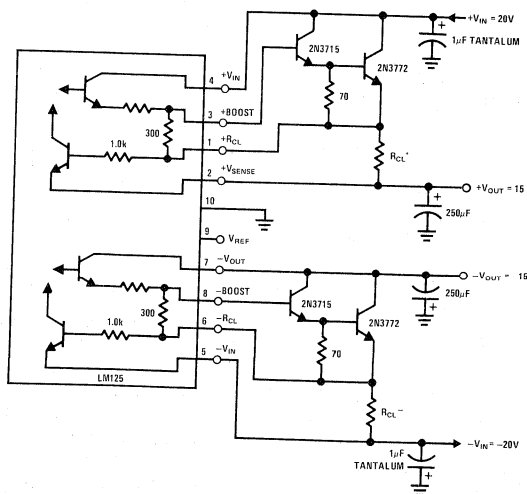


FIGURE 14. High Current Regulator Using a Darlington Pair for Pass Elements



using a 2N3715 and a 2N3772. With this configuration the output current can reach values to 10A with very good stability. The external Darlington stage increases the minimum input-output voltage differential to 4.5V. When current limit protection resistor is used, as in Figure 14, the maximum output current is limited by power dissipation of the 2N3772 (150W at 25°C). During normal operation this is  $(V_{IN}-V_{OUT}) I_{OUT}$  (W), but it increases to  $V_{IN} I_{SC}$  (W) under short circuit conditions. The short circuit output current is then:

$$I_{SC} = \frac{P_{MAX} (T_C = 25^\circ C)}{V_{IN}}$$

$$= \frac{150W}{20V (min)} = 7.5A \text{ max.}$$

$I_L$  could be increased to 10A or more only if  $I_{SC} < I_L$ . A foldback current limit circuit will accomplish this. The typical load regulation is 40 mV from no load to a full load. ( $T_J = 25^\circ C$ , pulsed load with 20 ms  $t_{ON}$  and 250 ms  $t_{OFF}$ .)

#### FOLDBACK CURRENT LIMITING

In many regulator applications, the normal operation power dissipation in the pass device can easily be multiplied by a factor of ten or more when the output is shorted. This may destroy the pass device, and possibly the regulator, unless the heat sink is oversized to handle this fault condition. A foldback current limiting circuit reduces short circuit output current to a fraction of the full load output current thus avoiding the

need for larger heat sink. Figure 15 shows a foldback current limiting circuit on both positive and negative regulators.

The foldback current limiting, a fraction of the output voltage must be used to oppose the voltage across the current limit sense resistor. Current limiting does not occur until the voltage across the sense resistor is higher than this opposing voltage by the amount shown in Figure 11. When the output is grounded, the opposing voltage is no longer present so current limiting occurs at a lower level. This is accomplished in Figure 15 by using a programmable current source to give a constant voltage drop across R5 for the negative regulator, and by a simple resistor divider for the positive regulator. The reason for the difference between the two is that the negative regulator current limiting circuit is located between the output pass transistor and the unregulated input while the positive regulator current limiter is between the output pass transistor and the regulated output.

The operation of the positive foldback circuit is similar to that described in NSC application note AN-23. A voltage divider R1 and R2 from  $V_E$  to ground creates a fixed voltage drop across R1 opposite in polarity to the drop across  $R_{CL}^+$ . When the load current increases to the point where the drop across  $R_{CL}^+$  is equal to the drop across R1 plus the current limit sense voltage given in Figure 11, the positive regulator will begin to current limit. As the positive output begins to drop, the voltage across R1 will also decrease so that it now requires less load current to produce the current limit sense voltage. With

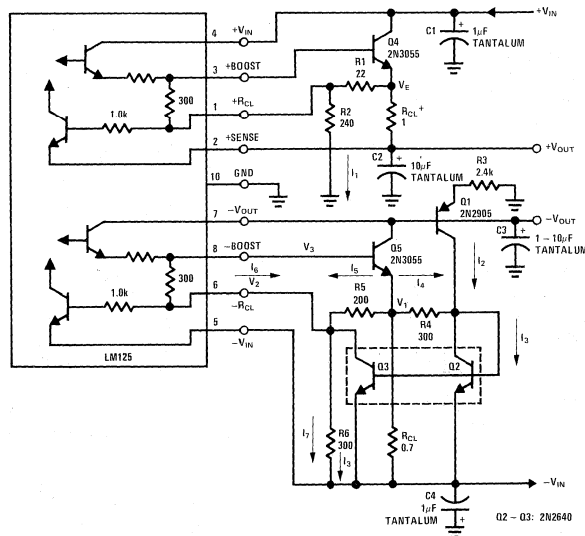


FIGURE 15. Foldback Current Limiting Circuit

the regulator output fully shorted to ground (+V<sub>OUT</sub> = 0) the current limit will be set by the value of +R<sub>CL</sub> alone.

$$\text{If } \frac{I_{FB}}{I_{SC}} \leq 5$$

then the following equations can be used for calculating the positive regulator foldback current limiting resistors.

$$R_{CL}^+ = \frac{V_{SENSE}}{I_{SC}} \quad (1)$$

where V<sub>SENSE</sub> is from Figure 11.

At the maximum load current foldback point:

$$V_{RCL}^+ = I_{FB} R_{CL}^+ \quad (2)$$

$$V_{R1} = V_{RCL}^+ - V_{SENSE} \quad (3)$$

$$V_{R1} = I_{FB} R_{CL}^+ - V_{SENSE} \quad (4)$$

Then

$$R1 = \frac{V_{R1}}{I_1} \quad (5)$$

and

$$R2 = \frac{+V_{OUT} + V_{SENSE}}{I_1} \quad (6)$$

The only point of caution is to ensure that the total current (I<sub>1</sub>) through R2 is much greater than the current contribution from the internal 300Ω resistor. This can be checked by:

$$\frac{I_{FB} R_{CL}^+}{300} \ll I_1 \quad (7)$$

Note: The current from the internal 300Ω resistor is V<sub>3-1</sub>/300Ω, but V<sub>3-1</sub> = V<sub>BE</sub> + V<sub>RCL</sub> - V<sub>SENSE</sub><sup>+</sup> assuming V<sub>BE</sub> ≈ V<sub>SENSE</sub><sup>+</sup> at the foldback point, V<sub>3-1</sub> ≈ V<sub>RCL</sub><sup>+</sup> = I<sub>FB</sub> R<sub>CL</sub><sup>+</sup>.

Design example: 2 amp regulator LM125 positive foldback current limiting (see Figure 15).

Given:

$$I_{FOLDBACK} = 2.0A$$

$$I_{SHORT-CIRCUIT} = 500 \text{ mA}$$

V<sub>SENSE</sub> (See Figure 11)

$$+V_{IN} = 25V$$

$$+V_{OUT} = 15V$$

$$\beta_{PASS \text{ DEVICE}} = 70$$

$$\theta_{JA} = 150^\circ C/W$$

$$T_A = 50^\circ C$$

With a beta of 70 in the pass device and a maximum output current of 2.0A the regulator must deliver:

$$\frac{2A}{\beta} = \frac{2A}{70} = 29 \text{ mA}$$

The LM125 power dissipation will be calculated ignoring any negative output current for this example.

$$\begin{aligned} P_{LM125} &= (V_{IN} - V_{OUT}) I_{OUT} \\ &= (25 - 15) 29 \text{ mA} \\ &= 290 \text{ mW} \end{aligned}$$

$$T_{RISE} @ \theta_{JA} = 150^\circ C/W = 150^\circ C \times 0.29 = 44^\circ C$$

$$T_J = T_A + T_{RISE} = 50^\circ C + 44^\circ C = 94^\circ C$$

From Figure 11:

$$V_{SENSE} @ (T_J = 94^\circ C) = 520 \text{ mV}$$

From equation (1)

$$R_{CL}^+ = \frac{V_{SENSE}}{I_{SC}} = \frac{520 \text{ mV}}{500 \text{ mA}} \cong 1\Omega$$

From equation (2)

$$V_{RCL}^+ = I_{FB} R_{CL}^+ = 2A \cdot 1\Omega = 2V$$

From equation (3)

$$V_{R1} = V_{RCL}^+ - V_{SENSE}$$

$$V_{R1} = 2V - 520 \text{ mV} = 1.480V$$

A value for I<sub>1</sub> can now be found from equation (7)

$$\frac{I_{FB} R_{CL}^+}{300} = \frac{2A \cdot 1\Omega}{300\Omega} = 6.6 \text{ mA}$$

So set I<sub>1</sub> = 10 × 6.6 mA = 66 mA

From equations (5) and (6)

$$R1 = \frac{V_{R1}}{I_1} = \frac{1.480V}{66 \text{ mA}} \cong 22\Omega$$

$$R2 = \frac{+V_{OUT} + V_{SENSE}}{I_1} = \frac{15 + 0.520}{66 \text{ mA}} \cong 240\Omega$$

The foldback limiting characteristics are shown in Figure 16 for the values calculated above at various operating temperatures.

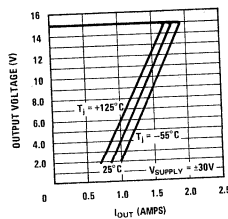


FIGURE 16. Positive Regulator Foldback Current Limiting Characteristics

The negative regulator foldback current limiting works essentially the same way as the positive side. Q1 forces a constant current,  $I_2$ , determined by  $-V_{OUT}$  and R3, through Q2. Transistors Q2 and Q3 are matched so a current identical to  $I_3$  will flow through Q3. With the output short-circuited ( $-V_{OUT} = 0$ ), Q1 will be OFF, setting  $I_2 = 0$ . The load current will be limited when  $V_1$  increases sufficiently due to load current to make  $V_2$  higher than  $-V_{IN}$  by the current limit sense voltage.

The short circuit current is:

$$I_{SC} \cong \frac{V_{SENSE}}{R_{CL}^-} \quad (8)$$

For calculating the maximum full load current with the output still in regulation, current  $I_2$

$$I_2 = \frac{V_{OUT} - V_{BEQ1}}{R3} \quad (9)$$

At the point of maximum load current,  $I_{FB}$ , where the regulator should start folding back:

$$V_1 = -V_{IN} + I_{FB} R_{CL}^- \quad (10)$$

and

$$V_2 = -V_{IN} + V_{SENSE} \quad (11)$$

The current through Q2 (and Q3) will have increased from  $I_2$  by the amount of  $I_4$  due

to the voltage  $V_1$  increasing above its no-load quiescent value. Since the voltage across Q2 is simply the diode drop of a base-emitter junction:

$$I_4 = \frac{[V_1 - (-V_{IN})] - V_{BE}}{R4}$$

Substituting in equation (10) gives:

$$\begin{aligned} I_4 &= \frac{I_{FB} R_{CL}^- - V_{BE}}{R4} \\ &= \frac{I_{FB} R_{CL}^- - V_{BE}}{300\Omega} \end{aligned} \quad (12)$$

The current through Q2 is now

$$I_3 = I_2 + I_4 \quad (13)$$

and the current through Q3 is:

$$I_3 = I_5 + I_6 - I_7 \quad (14)$$

The drop across R5 is found from:

$$V_1 - V_2 = (-V_{IN} + I_{FB} R_{CL}^-) - [V_{SENSE} + (-V_{IN})];$$

simplifying,

$$V_1 - V_2 = I_{FB} R_{CL}^- - V_{SENSE} \quad (15)$$

Since  $V_{SENSE}$  is the base to emitter voltage drop of the internal limiter transistor, the  $V_{SENSE}$  in equation (15) very nearly equals the  $V_{BE}$  in equation (12). Therefore the drop across R5 approximately equals the drop across R4. The current through R5,  $I_5$ , can now be determined as:

$$I_5 = \frac{I_{FB} R_{CL}^- - V_{SENSE}}{R5} \quad (16)$$

Summing the currents through Q3 is now possible assuming the base-emitter drop of the 2N3055 pass device can be given by  $V_{BE} \approx V_{SENSE}$ :

$$I_6 = \frac{V_3 - V_2}{300} \quad (17)$$

where  $V_3 = V_1 + V_{BE} \approx V_1 + V_{SENSE}$

$$I_6 = \frac{V_1 + V_{SENSE} - V_2}{300}$$

Substituting in equation (15)

$$I_6 = \frac{I_{FB} R_{CL}^-}{300} \quad (18)$$

$$I_7 = \frac{V_2 - (-V_{IN})}{R6} = \frac{V_{SENSE}}{R6}$$

Equating equation (13) with equation (14) and inserting resistor values shown in Figure 15,

$$I_2 + I_4 = I_5 + I_6 - I_7$$

$$I_2 + \frac{I_{FB} R_{CL}^- - V_{SENSE}}{300} = \quad (19)$$

$$I_5 + \frac{I_{FB} R_{CL}^- - V_{SENSE}}{300}$$

Canceling, we find:

$$I_2 = I_5 \quad (20)$$

This is the key to the negative foldback circuit. Current source Q1 forces current  $I_2$  to flow through resistor R5. The voltage drop across R5 opposes the normal current limit sense voltage so that the regulator will not current limit until the drop across  $R_{CL}^-$  due to load current, equals the controlled drop across R5 plus  $V_{SENSE}$  (given in Figure 11). This can be written as:

$$I_{FB} = \frac{V_{SENSE} + I_2 R_5}{R_{CL}^-} \quad (21)$$

$$I_{FB} = \frac{V_{SENSE} + 200 I_2}{R_{CL}^-}$$

A design example is now offered:

Given:

$$I_{FOLDBACK} = 2.5A$$

$$I_{SHORT-CIRCUIT} = 750 \text{ mA}$$

$$V_{SENSE} \text{ (See Figure 11)}$$

$$-V_{IN} = 25V$$

$$-V_{OUT} = -15V$$

$$\beta_{PASS DEVICE} = 90$$

$$\theta_{JA} = 150^\circ C/W$$

$$T_A = 25^\circ C$$

The same calculations are used here to figure  $V_{SENSE}$  as with the positive regulator foldback example maximum regulator output current is calculated from:

$$I_{OUT} = \frac{2.5 A}{90} = 28 \text{ mA}$$

$$P_{LM125} = (V_{IN} - V_O) I_{OUT}$$

$$= 10V \times 28 \text{ mA}$$

$$= 280 \text{ mW}$$

$$T_{RISE} = 150^\circ C/W \times 0.28W = 42^\circ C$$

$$T_J = T_A + T_{RISE} = 25^\circ C + 42^\circ C = 67^\circ C$$

From Figure 11:

$$V_{SENSE} = 500 \text{ mV}$$

From equation (8):

$$R_{CL}^- = \frac{500 \text{ mV}}{750 \text{ mA}} = 0.68\Omega$$

From equation (21):

$$I_2 = \frac{I_{FB} R_{CL}^- - V_{SENSE}}{200\Omega} = 6.0 \text{ mA}$$

From equation (9):

$$R_3 = \frac{V_{OUT} - V_{BEQ1}}{I_2}$$

$$R_3 \approx \frac{14.3}{6.0 \text{ mA}} = 2.4k$$

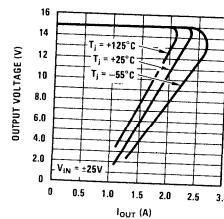


FIGURE 17. Negative Regulator Foldback Current Limiting Characteristics

Figure 16 and 17 show the measured foldback characteristics for the values derived in the design examples. The value of  $R_5$  is set low so that the magnitude of  $I_5$  for foldback is greater than  $I_4$  through  $I_6$ . This reduces the foldback point sensitivity to the TC of the internal  $300\Omega$  resistor and any mismatch in the TC of Q2, Q3 or the pass device.

$R_6$  can be computed from equation (18):

$$R_6 = \frac{V_{SENSE}^-}{I_7} = \frac{V_{SENSE}^-}{I_5 + I_6 - I_3}$$

combining (13) and (20).

$$R6 = \frac{V_{SENSE}^-}{I_6 - I_4} = \frac{V_{SENSE}^-}{I_{FB} R_{CL} \left( \frac{1}{300} - \frac{1}{R4} \right) + \frac{V_{BE}}{R4}} \quad (22)$$

Setting  $V_{BE} \approx V_{SENSE}^-$  and  $R4 = 300$  to match the internal  $300\Omega$  (22) becomes:

$$R6 = R4$$

Also setting  $\frac{I_4}{I_5} = \frac{2}{3} \rightarrow R5 = 200$

### A 10 AMP REGULATOR

Figure 18 illustrates the complete schematic of a 10A regulator with foldback current limiting. The design approach is similar to that of the 2A regulator. However, in this design, the current contribution from the internal  $300\Omega$  resistor is greater due to the  $2V_{BE}$  drop across the Darlington pair. Expression (7) becomes:

$$\frac{I_{FB} R_{CL} + V_{BE}}{300} \ll I_1; \quad (23)$$

and, for the negative regulator, expression (22) becomes:

$$R6 = \frac{V_{SENSE}^-}{I_{FB} R_{CL} \left[ \frac{1}{300} - \frac{1}{R4} \right] + V_{BE} \left[ \frac{1}{300} + \frac{1}{R4} \right]} \quad (24)$$

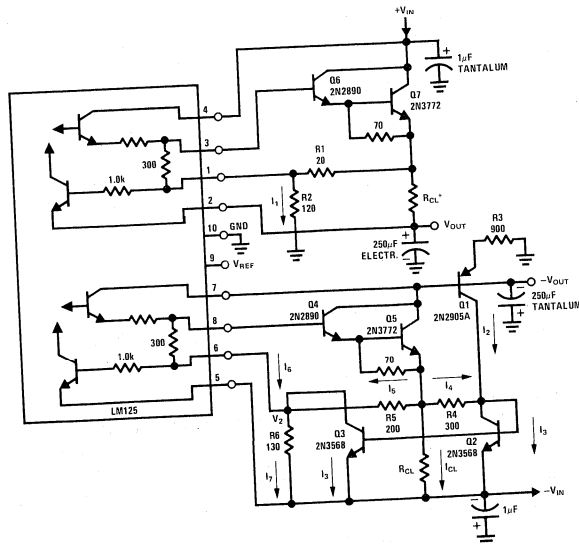


FIGURE 18. 10A Regulator with Foldback Current Limiting

The disagreement between the theoretical and experimental values for the negative regulator is not alarming. In fact  $R_{CL}$  was based on equation (8), which is correct if for zero  $V_{OUT}$ ,  $I_5$  is zero as well. This implies:

$$V_{SENSE} \text{ (at SC)} = \frac{V_{BEQ4} + V_{BEQ5}}{2} \text{ (at SC)}$$

which is a first order approximation.

Figure 19 illustrates the power dissipation in the external power transistor for both sides. Maximum power dissipation occurs between full load and short circuit so the heat sink for the 2N3772 must be designed accordingly, remembering that

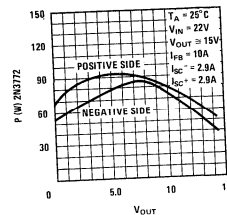


FIGURE 19. Power Dissipation in the External Pass Transistor (Q5, Q7)

the 2N3772 must be derated according to  $0.86W/^{\circ}C$  above  $25^{\circ}C$ . This corresponds to a thermal resistance junction to case of  $1.17^{\circ}C/W$ .

### Example

Positive Side	Theoretical Value	Experimental Results
$I_{FB} = 10 \text{ A}$	$I_{125} = 13 \text{ mA}$	$I_{FB} = 9.8 \text{ A}$
$I_{SC} = 2.5 \text{ A}$	$P_{LM125} = 150 \text{ mW}$	$I_{SC} = 2.9 \text{ A}$
$V_{IN} = 22 \text{ V}$	$R_{CL}^+ = 0.26 \Omega$	$R_{CL}^+ = 0.26 \Omega$
$V_{OUT} = 15 \text{ V}$	$R1 = 21 \Omega$	R1: adjusted to $20 \Omega$
$\beta = \beta1 \beta2 = 15 \times 50 = 750 \text{ min}$	$R2 = 130 \Omega$	R2: adjusted to $120 \Omega$
$T_A = 25^\circ \text{C}$	$V_{SENSE}^+ = 650 \text{ mV}$	

Negative Side	Theoretical Value	Experimental Results
$I_{FB} = 10 \text{ A}$	$R_{CL}^- = 0.22 \Omega$	$I_{FB} = 10 \text{ A}$
$I_{SC} = 2.5 \text{ A}$	$R4 = 300 \Omega$	$I_{SC} = 2.9 \text{ A}$
$V_{IN} = 22 \text{ V}$	$R5 = 200 \Omega$	$R_{CL}^-$ : adjusted to $0.3 \Omega$
$V_{OUT} = 15 \text{ V}$	$R6 = 150 \Omega$	R6: adjusted to $130 \Omega$
$\beta = 800$	$R3 = 1.6 \text{ k}\Omega$	R3: adjusted to $900 \Omega$
$T_A = 25^\circ$	$V_{SENSE}^- = 550 \text{ mV}$	
$\frac{I_4}{I_5} = \frac{2}{3}$		

Note: For this example, in designing each side, the power dissipation of the opposite side has not been taken into the account.

### POSITIVE CURRENT DEPENDENT SIMULTANEOUS CURRENT LIMITING

The LM125, LM126 uses the negative output as a reference for the positive regulator. As a consequence, whenever the negative output current limits, the positive output follows tracks to within 200 – 800 mV of ground. If, however, the positive regulator should current limit the negative output will remain in full regulation. This imbalance in output voltages could be a problem in some supply applications.

As a solution to this problem, a simultaneous limiting scheme, dependent on the positive regulator output current, is presented in Figure 20. The output current causes an I-R drop across R1 which brings transistor Q1 into conduction. As the positive load current increases  $I_1$  increases until the voltage drop across R2 equals the negative current limit sense voltage. The negative regulator will then current limit, and positive side will closely follow the negative output down to a level of 700 – 800 mV. For  $V_{OUT}^+$  to drop the final 700 – 800 mV with small output current change,  $R_{CL}^+$  should be adjusted so that the positive current limit is slightly larger than the simultaneous limiting. Figure 21 illustrates the simultaneous current limiting of both sides.

The following design equations may be used:

$$R1 I_{CL}^+ = R3 I_1 + V_{BEQ1} \quad (25)$$

$$I_1 = \frac{V_{SENSE}^-}{R2} \quad (26)$$

Combining (25) and (26),

$$I_{CL}^+ = \frac{\frac{R3}{R2} V_{SENSE}^- + V_{BEQ1}}{R1} \quad (27)$$

with

$$R_{CL}^+ = \frac{V_{SENSE}^+}{1.1 I_{CL}^+} \quad (28)$$

The negative current limit (independent of  $I_{CL}^+$ ) can be set at any desired level.

$$I_{CL}^- = \frac{V_{SENSE}^- + V_{DIODE}}{R_{CL}^-} \quad (29)$$

Transistor Q2 turns off the negative pass transistor during simultaneous current limiting.

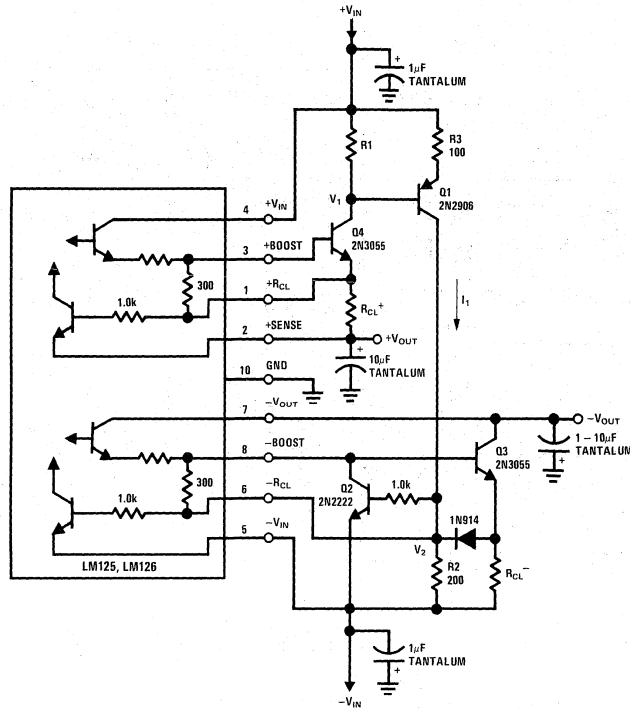


FIGURE 20. Positive Current Dependent Simultaneous Current Limiting

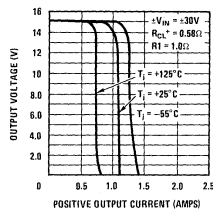


FIGURE 21. Positive Current Dependent Simultaneous Shutdown

### ELECTRONIC SHUTDOWN

In some regulated supply applications it is desirable to shutdown the regulated outputs ( $\pm V_O = 0$ ) without having to shutdown the unregulated inputs (which may be powering additional equipment). Various shutdown methods may be used. The simplest is to insert a relay, a saturated bipolar device, or some other type switch in series with either the regulator inputs or outputs. The switch must be able to open and close under maximum load current which, may be several amps.

As an alternate solution, the internal reference voltage of the regulator may be shorted to ground.

This will force the positive and negative outputs to approximately +700 mV and +300 mV respectively. Both outputs are fully active so the full output current can still be supplied into a low impedance load. If this is unacceptable, another solution must be found.

The circuit in Figure 22 provides complete electronic shutdown of both regulators. The shutdown control signal is TTL compatible but by adjusting R8 and R9 the regulator may be shutdown at any desired level above  $2 V_{BE}$ , calculated as follows:

$$V_T \approx \left[ \frac{R8}{R3\beta Q4} + \frac{R9}{R3} \right] V_{BE} + 2 V_{BE} \quad (30)$$

Positive and negative shutdown operations are similar. When a shutdown signal  $V_T$  is applied, Q4 draws current through R3 and D2 establishing a voltage  $V_R$  which starts the current sources Q1 and Q2. Assuming that Q1 and Q2 are matched, and making  $R1 = R2 = R3$ , the currents  $I_1, I_2, I_3$  are equal and both sides of the regulator shutdown simultaneously.

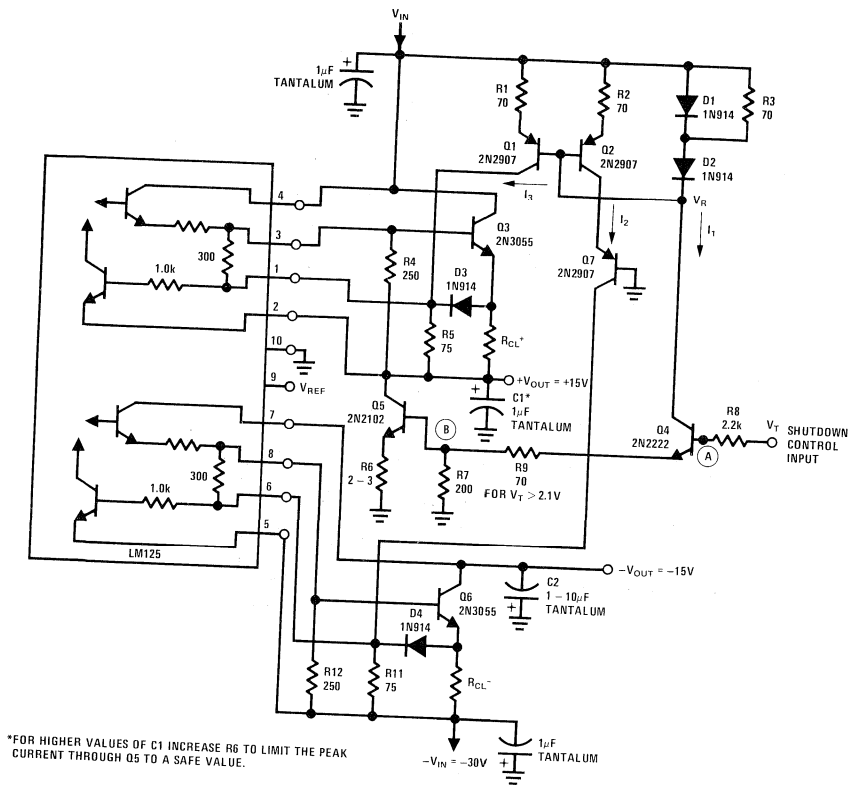


FIGURE 22. Electronic Shutdown for the Boosted Regulator

The current  $I_3$  creates a drop across  $R_5$ , which equals or exceeds the limit sense voltage of the positive regulator, causing it to shutdown. Since  $I_3$  has no path to ground except through the load, a fixed load is provided by  $Q_5$ , which is turned on by the variable current source  $Q_4$ .  $C_1$  also discharges through  $Q_5$  and current limiting resistor  $R_6$ . Resistor  $R_4$  prevents  $Q_3$  turn on during shutdown, which could otherwise occur due to the drop across  $R_5$  plus the internal  $300\Omega$  resistor. Diode  $D_3$  prevents  $I_3$  from being shunted through  $R_{CL-}$ .

$C_2$  discharges through the load.  $Q_7$  shares the total supply voltage with  $Q_2$ , thus limiting power dissipation of  $Q_2$ . Another power dissipation problem may occur when the design is done for  $V_T = 2.0V$  for example, and  $V_T$  is increased above the preset threshold value.  $I_1$  is increased and  $Q_4$  has to dissipate  $(V_{IN} - 3V_{BE} - V_T) I_1$  (W). The simplest solution is to increase  $R_8$ . If this is insufficient, a set of diodes may be added between nodes A and B to clamp  $I_1$  to a reasonable value. This is illustrated in Figure 23:

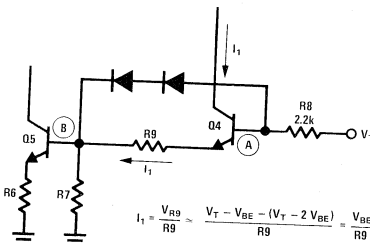


FIGURE 23.

So  $I_1$  is made independent of  $V_T$  and by setting a minimum value of  $10\text{ mA}$  ( $R_9 = 70\Omega$ ). The regulator will shutdown at any desired level above  $3V_{BE}$ , without overheating transistor  $Q_4$ . Also using



Figure 23 the diode D1 in Figure 22 may be omitted. The shutdown characteristics of Figure 22 are shown in Figure 24.

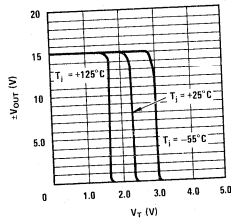


FIGURE 24. Electronic Shutdown Characteristics

The normal current limiting current is set by equation (31)

$$I_{CL} = \frac{V_{SENSE} + V_{DIODE}}{R_{CL}} \quad (31)$$

The same approach is used with the unboosted regulator shown in Figure 25. In this case the voltage sense resistor is the internal 300Ω one. Since output capacitors are no longer required Q3 is just used as a current sink and its emitter load has been removed.

### POWER DISSIPATION

The power dissipation of the LM125 is:

$$P_d = (V_{IN}^+ - V_{OUT}^+) I_{OUT}^+ + (V_{IN}^- - V_{OUT}^-) I_{OUT}^- + V_{IN}^+ I_S^+ + V_{IN}^- I_S^-$$

where  $I_S$  is the standby current.

Ex: ±1A regulator using 2N3055 pass transistors. Assuming a  $\beta = 100$ , and ±25V supply,

$$P_d = 400 \text{ mW.}$$

The temperature rise for the TO-5 package will be:

$$T_{RISE} = 0.4 \times 150^\circ\text{C/W} = 60^\circ\text{C}$$

Therefore the maximum ambient temperature is  $T_{A\text{MAX}} = T_{J\text{MAX}} - T_{RISE} = 90^\circ\text{C}$ . If the device is to operate at  $T_A$  above  $90^\circ\text{C}$  then the TO-5 package must have a heat sink.  $T_{RISE}$  in this case will be:

$$T_{RISE} = P_d (\theta_{J-C} + \theta_{C-S} + \theta_{S-A}).$$

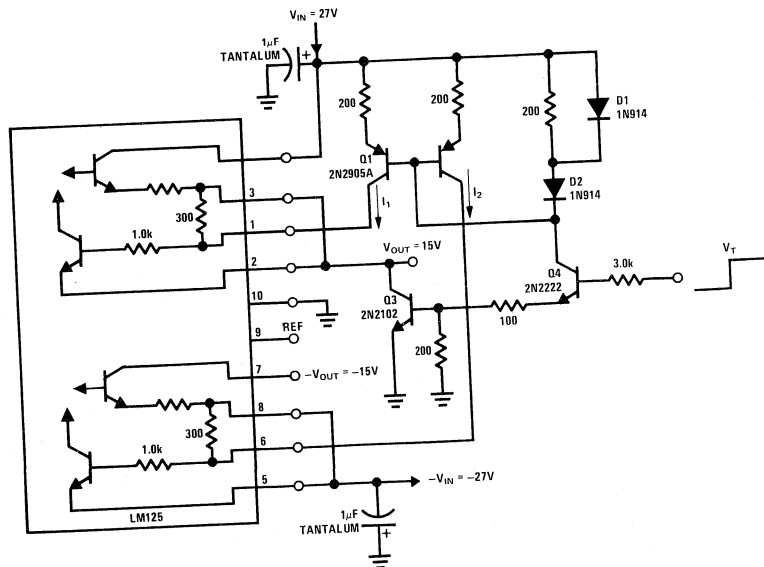


FIGURE 25. Electronic Shutdown for the Basic Regulator



# Comparing the High Speed Comparators

National Semiconductor  
Application Note 87  
Interface  
Development Group  
June 1973



## INTRODUCTION

Several integrated circuit voltage comparators exist which were designed with high speed and complementary TTL outputs as the main objectives. The more common applications for these devices are high speed analog to digital (A to D) converters, tape and disk-file read channels, fast zero-crossing detectors, and high speed differential line receivers. This note compares the National Semiconductor devices to similar devices from other manufacturers.

The product philosophy at National was to create pin-for-pin replacement circuits that could be considered as second-sources to the other comparators, while simultaneously containing the improvements necessary to make a more optimum device

for the intended usage. Optimized parameters include speed, input accuracy and impedance, supply voltage range, fanout, and reliability. The LM160/LM260/LM360 are replacement devices for the  $\mu$ A760, while the LM161/LM261/LM361 replace the SE/NE529. Tables I and II compare the critical parameters of the National commercial range devices to their respective counterparts.

## SPEED

Throughout the universe the subject of speed must be approached with caution; the same holds true here. Speed (propagation delay time) is a function

TABLE I. LM360/ $\mu$ A760C Comparison  $0^\circ \leq T_A \leq +70^\circ\text{C}$ ,  $V^+ = +5.0\text{V}$ ,  $V^- = -5.0\text{V}$

PARAMETER	LM360	$\mu$ A760C	UNITS
Input Offset Voltage	5.0	6.0	mV max
Input Offset Current	3.0	7.5	$\mu$ A max
Input Bias Current	20	60	$\mu$ A max
Input Capacitance	4.0	8.0	pF typ
Input Impedance	17	5.0	k $\Omega$ typ @ 1 MHz 25 $^\circ$ C
Differential Voltage Range	$\pm 5.0$	$\pm 5.0$	V typ
Common Mode Voltage Range	$\pm 4.0$	$\pm 4.0$	V typ
Gain	3.0	3.0	V/mV typ 25 $^\circ$
Fanout	4.0	2.0	74 Series TTL Loads
Propagation Delays:			
(1) 30 mV <sub>p-p</sub> 10 MHz Sinewave in	25	30	ns max 25 $^\circ$
(2) 2.0 V <sub>p-p</sub> 10 MHz Sinewave in	20	25	ns max 25 $^\circ$
(3) 100 mV Step + 5.0 mV Overdrive	14	22	ns typ 25 $^\circ$

TABLE II. LM261/NE529 Comparison  $0^\circ \leq T_A \leq +70^\circ\text{C}$ ,  $V^+ = +10\text{V}$ ,  $V^- = -10\text{V}$ ,  $V_{CC} = +5.0\text{V}$

PARAMETER	LM261	NE529	UNITS
Input Offset Voltage	3.0	10	mV max
Input Offset Current	3.0	15	$\mu$ A max
Input Bias Current	20	50	$\mu$ A max
Input Impedance	17	5.0	k $\Omega$ typ @ 1 MHz 25 $^\circ$ C
Differential Voltage Range	$\pm 5.0$	$\pm 5.0$	V typ
Common Mode Voltage Range	$\pm 6.0$	$\pm 6.0$	V typ
Gain	3.0	4.0	V/mV typ 25 $^\circ$
Fanout	4.0	6.0	74 Series TTL Loads
Propagation Delay - 50 mV Overdrive	20	22	ns max 25 $^\circ$

of the measurement technique. The earlier "standard" of using a 100 mV input step with 5.0 mV overdrive has given way to seemingly endless variations. To be meaningful, speed comparisons must be made with identical conditions. It is for this reason that the speed conditions specified for the National parts are the same as those of the parts replaced.

Probably the most impressive speed characteristic of the six National parts is the fact that propagation delay is essentially independent of input overdrive (Figure 1); a highly desirable characteristic in A to D applications. Their delay typically

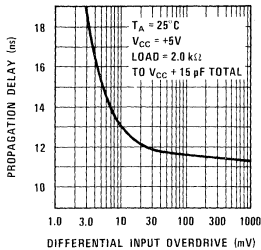


FIGURE 1. Delay vs Overdrive

varies only 3 ns for overdrive variations of 5.0 mV to 500 mV, whereas the other parts have a corresponding delay variation of two to one. As can be seen in Tables I and II, the National parts have an improved maximum delay specification. Further, the 20 ns maximum delay is meaningful since it is specified with a representative load: a 2.0 k $\Omega$  resistor to +5.0V and 15 pF total load capacitance. Figure 2 shows typical delay variation with temperature.

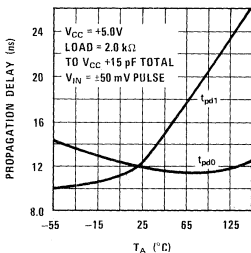


FIGURE 2. Delay vs Temperature

### INPUT PARAMETERS

The A to D, level detector, and line receiver applications of these devices require good input accuracy and impedance. In all these cases the

differential input voltage is relatively large, resulting in a complete switch of input bias current as the input signal traverses the reference voltage level. This effect can give rise to reduced gain and threshold inaccuracy, dependent on input source impedances and comparator input bias currents. Tables I and II show that the National parts have a substantially lower maximum bias current to ease this problem. This was done without resorting to Darlington input stages whose price is higher offset voltages and longer delay times. The lower bias currents also raise input resistance in the threshold region. Lower input capacitance and higher input resistance result in higher input impedance at high frequencies.

Even with low source impedances, input accuracy is still dependent on offset voltage. Since none of the devices under discussion has internal offset null capability, ultimate accuracy was improved by designing and specifying lower maximum offset voltage drift with temperature.

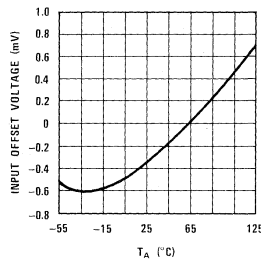


FIGURE 3. Offset Temperature Coefficient

### OTHER PERFORMANCE AREAS

In the case of the LM160/LM260/LM360, fanout was doubled over the previous device. For the LM161/LM261/LM361, operating supply voltage range was extended to  $\pm 15V$  op amp supplies

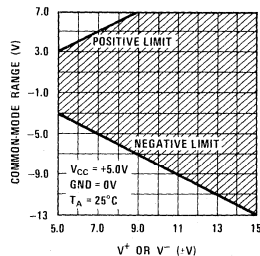


FIGURE 4. LM161 Common Mode Range

which are often readily available where such a comparator is used. Figure 4 reveals the common mode range of the latter device.

The performance improvements previously mentioned were a result of circuit design (Figures 5 and 6) and device processing. Schottky clamping, which can give rise to reliability problems, was not used. Gold doping, which results in processing dependent speeds and low transistor beta, was not used. Instead a non-gold-doped process with high breakdown voltage, high beta, and high  $f_T$  ( $\approx 1.5$  GHz)

was selected which produced remarkably consistent performance independent of normal process variation. The higher breakdown voltage allows the LM161/LM261/LM361 to operate on  $\pm 15V$  supplies and results in lower transistor capacitance; higher beta provides lower input bias currents; and higher  $f_T$  helps reduce propagation time.

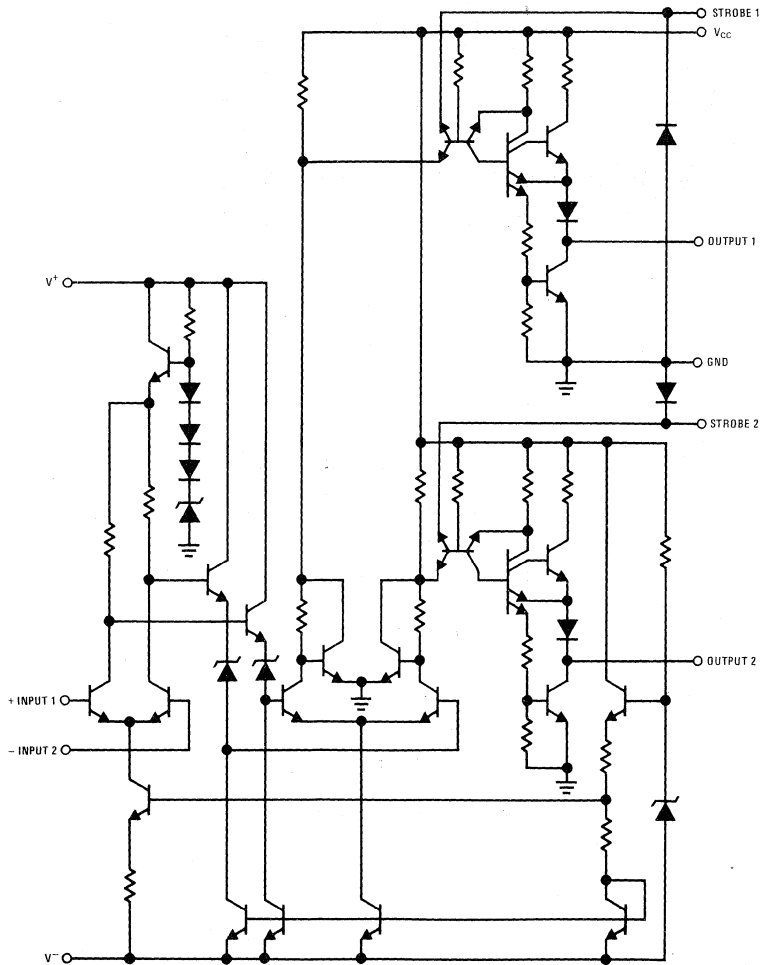


FIGURE 5. LM161 Schematic Diagram

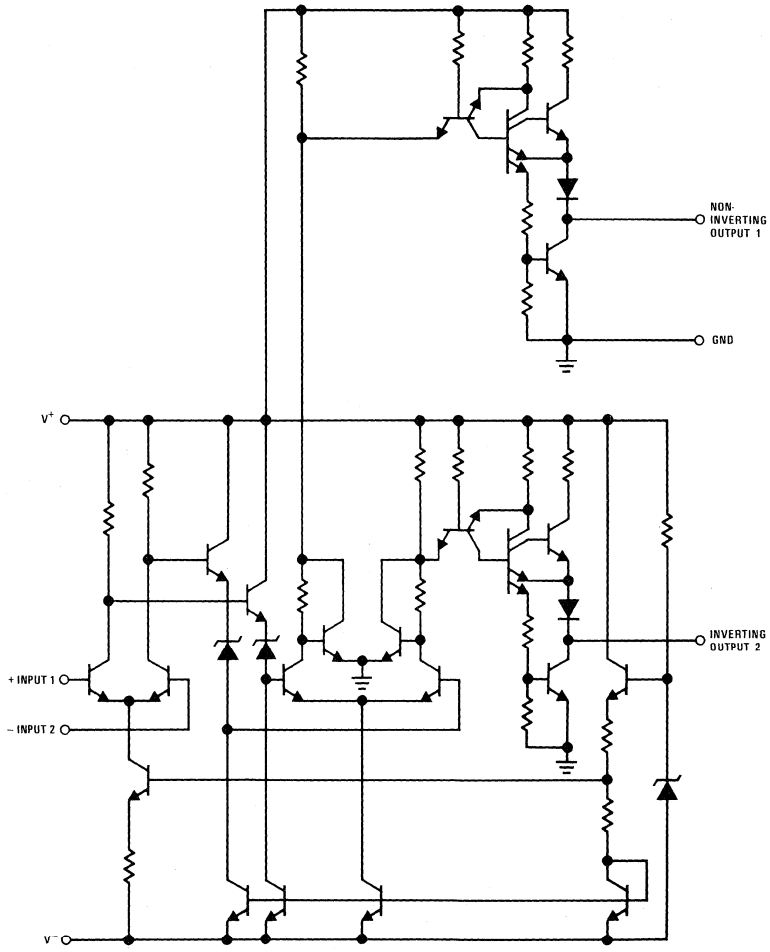


FIGURE 6. LM160 Schematic Diagram

**APPLICATIONS**

Typical applications have been mentioned previously. The LM160 and LM161 may be combined as in Figure 7 to create a fast, accurate peak detector for use in tape and disk-file read channels. A 3-bit A to D converter with 21 ns typical conversion time is shown in Figure 8. Although

primarily intended for interfacing to TTL logic, direct connection may be made to ECL logic from the LM161 by the technique shown in Figure 9. When used this way the common mode range is shifted from that of the TTL configuration. Finally level detectors or line receivers may be implemented with hysteresis in the transfer characteristic as seen in Figure 10.

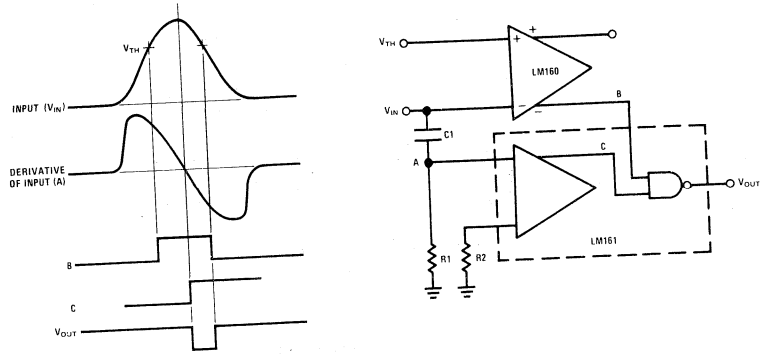


FIGURE 7. Peak Detector

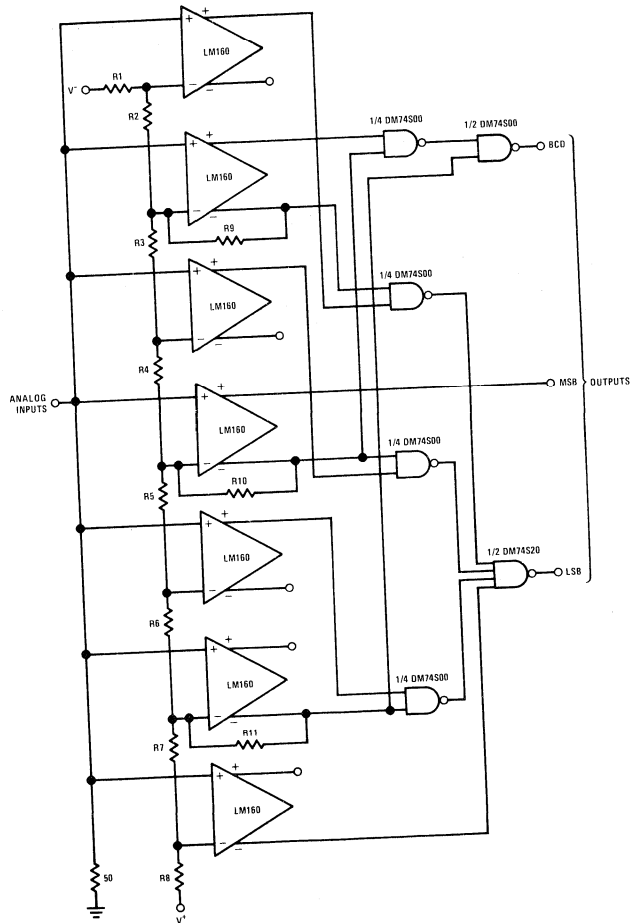


FIGURE 8. High Speed 3-bit A to D Converter


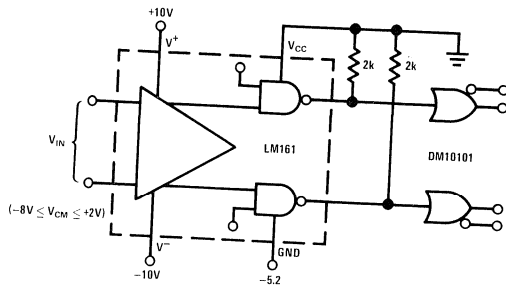


FIGURE 9. Direct Interfacing to ECL

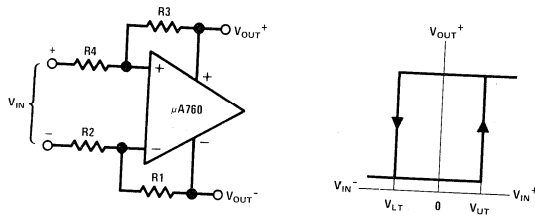

$$V_{UT} = V_{OH} \left( \frac{R2}{R1} \right) - V_{OL} \left( \frac{R4}{R3} \right)$$

$$V_{LT} = V_{OL} \left( \frac{R2}{R1} \right) - V_{OH} \left( \frac{R4}{R3} \right)$$

FIGURE 10. Level Detector with Hysteresis



# CMOS Linear Applications

National Semiconductor  
Application Note 88  
Gene Taatjes  
July 1973



PNP and NPN bipolar transistors have been used for many years in "complementary" type of amplifier circuits. Now, with the arrival of CMOS technology, complementary P-channel/N-channel MOS transistors are available in monolithic form. The MM74C04 incorporates a P-channel MOS transistor and an N-channel MOS transistor connected in complementary fashion to function as an inverter.

Due to the symmetry of the P- and N-channel transistors, negative feedback around the complementary pair will cause the pair to self bias itself to approximately 1/2 of the supply voltage. Figure 1 shows an idealized voltage transfer characteristic curve of the CMOS inverter connected with negative feedback. Under these conditions the inverter is biased for operation about the midpoint in the linear segment on the steep transition of the voltage transfer characteristic as shown in Figure 1.

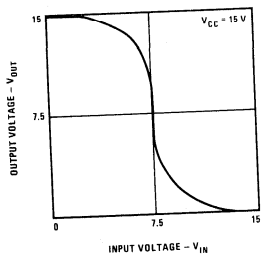


FIGURE 1. Idealized Voltage Transfer Characteristics of an MM74C04 Inverter.

Under AC conditions, a positive going input will cause the output to swing negative and a negative going input will have an inverse effect. Figure 2 shows 1/6 of a MM74C04 inverter package connected as an AC amplifier.

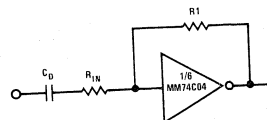


FIGURE 2. A 74CMOS Inverter Biased for Linear Mode Operation.

The power supply current is constant during dynamic operation since the inverter is biased for Class A operation. When the input signal swings near the supply, the output signal will become distorted because the P-N channel devices are driven into the non-linear regions of their transfer characteristics. If the input signal approaches the supply voltages, the P- or N-channel transistors become saturated and supply current is reduced to essentially zero and the device behaves like the classical digital inverter.

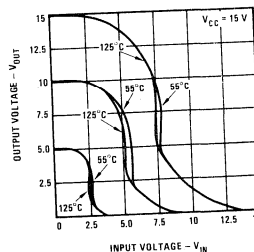


FIGURE 3. Voltage Transfer Characteristics for an Inverter Connected as a Linear Amplifier.

Figure 3 shows typical voltage characteristics of each inverter at several values of the  $V_{CC}$ . The shape of these transfer curves are relatively constant with temperature. Temperature affects for the self biased inverter with supply voltage is shown in Figure 4. When the amplifier is operating at 3 volts, the supply current changes drastically as a function of supply voltage because the MOS transistors are operating in the proximity of their gate-source threshold voltages.

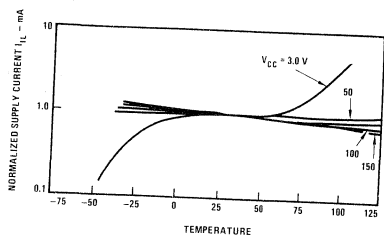


FIGURE 4. Normalized Amplifier Supply Current Versus Ambient Temperature Characteristics.

Figure 5 shows typical curves of voltage gain as a function of operating frequency for various supply voltages.

Output voltages can swing within millivolts of the supplies with either a single or dual supply.

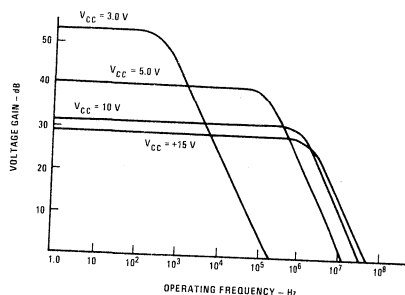


FIGURE 5. Typical Voltage Gain Versus Frequency Characteristics for Amplifier Shown in Figure 2.

## APPLICATIONS

### Cascading Amplifiers for Higher Gain.

By cascading the basic amplifier block shown in Figure 2 a high gain amplifier can be achieved. The gain will be multiplied by the number of stages used. If more than one inverter is used inside the feedback loop (as in Figure 6) a higher open loop gain is achieved which results in more accurate closed loop gains.

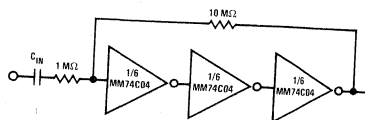


FIGURE 6. Three CMOS Inverters Used as an X10 AC Amplifier.

### Post Amplifier for Op Amps.

A standard operational amplifier used with a CMOS inverter for a Post Amplifier has several advantages. The operational amplifier essentially sees no load condition since the input impedance to the inverter is very high. Secondly, the CMOS inverters will swing to within millivolts of either supply. This gives the designer the advantage of operating the operational amplifier under no load conditions yet having the full supply swing capability on the output. Shown in Figure 7 is the LM4250 micropower Op Amp used with a 74C04 inverter for increased output capability while maintaining the low power advantage of both devices.

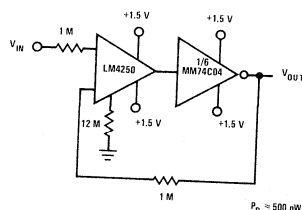


FIGURE 7. MM74C04 Inverter Used as a Post Amplifier for a Battery Operated Op Amp.

The MM74C04 can also be used with single supply amplifier such as the LM324. With the circuit shown in Figure 8, the open loop gain is approximately 160 dB. The LM324 has 4 amplifiers in a package and the MM74C04 has 6 amplifiers per package.

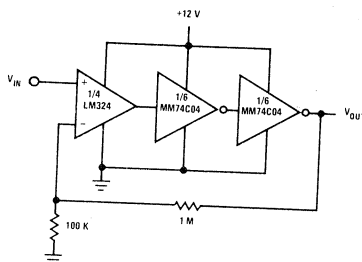


FIGURE 8. Single Supply Amplifier Using a CMOS Cascade Post Amplifier with the LM324.

CMOS inverters can be paralleled for increased power to drive higher current loads. Loads of 5.0 mA per inverter can be expected under AC conditions.

Other 74C devices can be used to provide greater complementary current outputs. The MM74C00 NAND Gate will provide approximately 10 mA

from the  $V_{CC}$  supply while the MM74C02 will supply approximately 10 mA from the negative supply. Shown in Figure 9 is an operational amplifier using a CMOS power post amplifier to provide greater than 40 mA complementary currents.

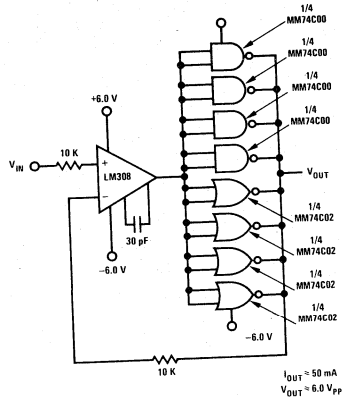


FIGURE 9. MM74C00 and MM74C02 Used as a Post Amplifier to Provide Increased Current Drive.


#### Other Applications.

Shown in Figure 10 is a variety of applications utilizing CMOS devices. Shown is a linear phase shift oscillator and an integrator which use the CMOS devices in the linear mode as well as a few circuit ideas for clocks and one shots.

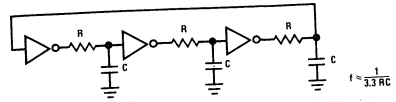
#### Conclusion

Careful study of CMOS characteristics show that CMOS devices used in a system design can be used for linear building blocks as well as digital blocks.


Utilization of these new devices will decrease package count and reduce supply requirements. The circuit designer now can do both digital and linear designs with the same type of device.




Phase Shift Oscillator Using MM74C04

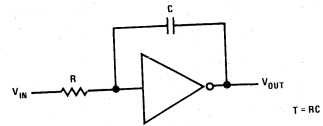


Integrator Using Any Inverting CMOS Gate

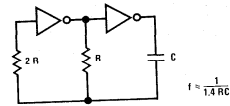

Square Wave Oscillator

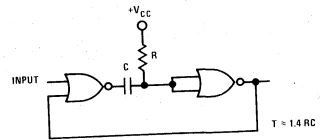

One Shot

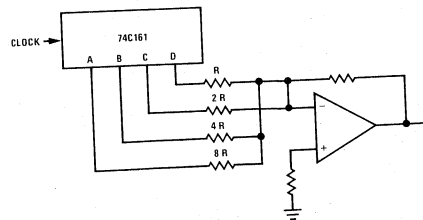

Staircase Generator

FIGURE 10. Variety of Circuit Ideas Using CMOS Devices.



# Versatile Timer Operates from Microseconds to Hours

National Semiconductor  
Application Note 97  
Carl Nelson  
December 1973



## INTRODUCTION

Timing functions, until recently, have been somewhat neglected by integrated circuit manufacturers. The primary reason was the extremely wide range of input and output signals currently incorporated in discrete designs. In addition, power supply voltages varied over a ten to one range and timing periods were as short as microseconds and as long as hours.

The LM122 timer has been designed to operate over a very wide range of input/output signal levels, supply voltages, and timing periods. It will replace most discrete designs with improved performance and reliability. This new timer overcomes many of the problems incurred in discrete or early IC designs.

First, it locks out trigger signals during the timing period to guarantee a precise output regardless of trigger level — while maintaining the ability to be retrigged almost immediately following the end of the timing pulse. (Duty cycles up to 99.9% can be achieved). Secondly, the timing period is free from jitter caused by supply fluctuations because

the timing components are driven from an internal regulated source. Supply voltage for the timer can vary from 4.5V to 40V even during the timing period! An additional feature is the  $\pm 40V$  excursion allowed on the trigger input and the 40V/50 mA drive capability of the output transistor. These two specifications allow the LM122 to interface directly to present designs without level shift or power boosting problems. Finally, the LM122 will generate stable timing periods from several microseconds to hours—a useful range of eight decades. Worst case guarantees on comparator bias current and threshold level allow the user to easily select timing components for maximum accuracy.

## CIRCUIT DESCRIPTION

The LM122 circuitry can be divided into five separate sections: output stage, bias network, voltage regulator, comparator, and logic. These sections are grouped on the schematic in Figure 1 to simplify understanding of the timer.

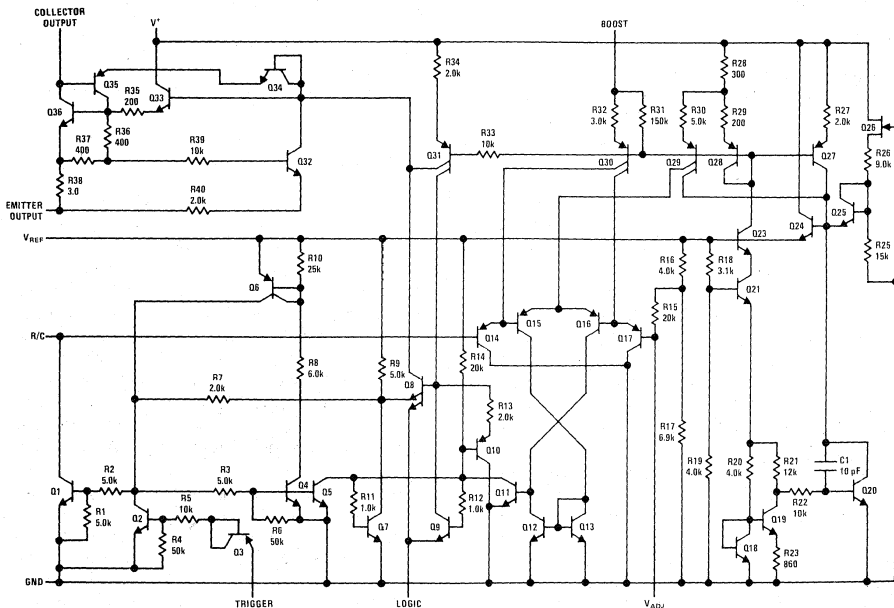


FIGURE 1. Schematic Diagram

The floating transistor output stage of the LM122 consists of Q32 through Q36. Q36 is the actual output transistor and is driven by emitter follower, Q33. Q34 and Q35 are antisaturation clamps to reduce stored charge in Q36 and to limit current through Q33. Q32 acts as a current limiter with the limit set at about 120 mA.

The regulator built into the LM122 is a  $V_{BE}/\Delta V_{BE}^*$  type with a typical output voltage of 3.15V at up to 5.0 mA load current. Q18 and Q19 generate a 100 $\mu$ A current through Q19 which has a positive temperature coefficient of 0.33%/°C. This generates 1.2V and +4 mV/°C TC across R21. When added to the base emitter diode voltages of Q20 and Q21, a 2.4V, zero TC reference is established at the base of Q21. R18 and R19 form a divider to raise the regulated voltage to 3.15V. (This particular voltage was chosen because it can be operated off a single 5.0V supply and because one RC time constant is exactly 2.0V out of 3.15V.) Q23 buffers Q21 from supply fluctuations and sets up the currents for the bias section of the timer. Q20 is a single stage of voltage gain for the regulator. It is buffered by the series pass transistor, Q24. Q25, Q26, R25, and R26 are included for starting purposes and do not affect operation once current is flowing in the regulator section.

The function of the comparator is to cause an output change of state when the timing capacitor has charged to one RC time constant. Q11 through Q17 perform this function. Q14, Q15, Q16, and Q17 are a Darlington differential stage driving an active load formed by Q12 and Q13. Q11 is a second stage operating as a common emitter amplifier with R14 as its load resistor. For long timing intervals, the Darlington is run with no bleed current from Q30. Operating current for Q15 and Q16 is about 5 $\mu$ A per side. The specially processed lateral PNP's have  $h_{FE}$ 's of about 200, so operating current for Q14 and Q17 is typically 25 nA. At these current levels, the substrate PNP's have  $h_{FE}$ 's of 80, giving comparator input currents of 300 pA! One side of the comparator is tied to a divider (R16 and R17) which is set at 63.2% of the reference voltage — one RC time constant. The other side is connected to the external timing resistor and capacitor.

The logic section of the LM122 performs four functions: first, it provides a latching action to make the circuitry immune to retriggering during the timing interval; second, it simulates the action of an exclusive OR gate to generate a logic reverse function; additionally, it translates the low level output from the comparator to the high level swing needed to drive the floating transistor output; and finally, it drives the discharge transistor to reset the timing capacitor. Q2 and Q3 make up the TTL compatible trigger input to the logic section. Q3 is a lateral PNP with 60V reverse emitter-base breakdown voltage, allowing negative inputs as high as -40V without harm to the chip. R5 is an epitaxial resistor which pinches off at

30V and has a breakdown of 80V. This allows positive input voltages of up to 40V on the trigger terminal even when operating the timer from a supply voltage of only 5.0V. Typical current drawn by the trigger terminal is 40 $\mu$ A at 2.0V and 600 $\mu$ A at 40V. Q4 and Q6 form a latch which self-limits at about 400 $\mu$ A and can be turned off by Q2. Q5 and Q7 interface the latch to the comparator so that the comparator can fire the latch at the end of the timing period. Q8, Q9, and Q10 perform the level shifting required to drive the output transistor and double as an exclusive OR gate, with the emitters of Q8 and Q9 as one input and the collectors of Q5 and Q11 as the second input. Grounding the Q8 and Q9 emitters reverses the effect of a signal appearing at the collector of Q11.

Biasing for the various circuits in the timer is generated by a string of PNP current sources consisting of Q27 through Q31. Current levels are established by the constant current source, Q23, driving diode connected Q28. The current from Q23 is 400 $\mu$ A, setting the drop across the emitter resistor, R28 plus R29, at 200 mV. Q29 delivers 10 $\mu$ A to the comparator and Q31 supplies a total of 100 $\mu$ A to the output transistor and logic circuitry. Part of Q29's collector is returned to Q27 to avoid having to use a large value resistor for R30. Q30 is completely off when using the timer for long timing periods. Shorting the boost terminal to  $V^+$  adds about 5 $\mu$ A bleed current at the emitters of Q14 and Q17. This extra current is needed to slew the emitters of the comparator for timing periods less than 1 ms.

## DESCRIPTION OF PIN FUNCTIONS

One of the main features of the LM122 is its great versatility. Since this device is unique, a description of the functions and limitations of each pin is in order. This will make it much easier to follow the discussion of the various applications presented in this note.

$V^+$  is the positive supply terminal of the LM122. When using a single supply, this terminal may be driven by any voltage between 4.5V and 40V. The effect of supply variations on timing period is less than 0.005%/V, so supplies with high ripple content may be used without causing pulse width changes. Supply bypassing on  $V^+$  is not generally needed but may be necessary when driving highly reactive loads. Quiescent current drawn from the  $V^+$  terminal is typically 2.5 mA, independent of the supply voltage. Of course, additional current will be drawn if the reference is externally loaded.

The  $V_{REF}$  pin is the output of a 3.15V series regulator referenced to the ground pin. Up to 5.0 mA can be drawn from this pin for driving external networks. In most applications the timing resistor is tied to  $V_{REF}$ , but it need not be in situations where a more linear charging current is required. The regulated voltage is very useful in

\*See AN-42, "On Card Regulator for Logic Circuits"

applications where the LM122 is not used as a timer; such as switching regulators, variable reference comparators, and temperature controllers. Typical temperature drift of the reference is less than  $0.01\%/^{\circ}\text{C}$ .

The trigger terminal is used to start timing. Threshold is typically 1.6V at  $+25^{\circ}\text{C}$  and has a temperature dependence of  $-5.0\text{ mV}/^{\circ}\text{C}$ . Current drawn from the trigger source is typically  $20\mu\text{A}$  at threshold, rising to  $600\mu\text{A}$  at 30V, then leveling off due to FET action of the series resistor, R5. For negative input trigger voltages, the only current drawn is leakage in the nA region.

If the trigger terminal is held high as the timing period ends, the output pulse will appear normally, but the timing capacitor will not be discharged. This is a necessary circuit action to prevent repetitive cycles when the trigger is held high. After the timing period, the capacitor is discharged when the trigger decreases below the threshold, without affecting the output.

The R/C pin is tied to the uncommitted side of the comparator and to the collector of the capacitor discharge transistor. Timing ends when the voltage on this pin reaches 2.0V (1 RC time constant referenced to the 3.15V regulator). The internal discharge transistor turns on only if the trigger voltage has dropped below threshold. In comparator or regulator applications of the timer, the trigger is held permanently high and the R/C pin acts just like the input to an ordinary comparator. The maximum voltages which can be applied to this pin are +5.5V and  $-0.7\text{V}$ . Input current to the R/C pin is typically 300 pA when the voltage is negative with respect to the  $V_{\text{ADJ}}$  terminal. For higher voltages, the current drops to leakage levels. In the boosted mode, input current is 30 nA. Gain of the comparator is very high, 200,000 or more depending on the state of the logic reverse pin and the connection of the output transistor.

The ground pin of the LM122 need not necessarily be tied to system ground. It can be connected to any positive or negative voltage as long as the supply is negative with respect to the  $V^{+}$  terminal. Level shifting may be necessary for the input trigger if the trigger voltage is referred to system ground. This can be done by capacitive coupling or by actual resistive or active level shifting. One point must be kept in mind; the emitter output must not be held above the ground terminal with a low source impedance. This could occur, for instance, if the emitter were grounded when the ground pin of the LM122 was tied to a negative supply.

The terminal labeled  $V_{\text{ADJ}}$  is tied to one side of the comparator and to a voltage divider between  $V_{\text{REF}}$  and ground. The divider voltage is set at 63.2% of  $V_{\text{REF}}$  with respect to ground—exactly one RC time constant. The impedance of the divider is increased to about 30k with a series resistor to present a minimum load on external

signals tied to  $V_{\text{ADJ}}$ . This resistor is a pinched type with a typical variation in absolute value of  $\pm 100\%$  and a TC of  $0.7\%/^{\circ}\text{C}$ . For this reason, external signals (typically a pot between  $V_{\text{REF}}$  and ground) connected to  $V_{\text{ADJ}}$  should have a source resistance as low as possible. For small changes in  $V_{\text{ADJ}}$ , up to several k $\Omega$  is all right, but for large variations 250 $\Omega$  or less should be maintained. This can be accomplished with a 1.0k pot, since the maximum impedance from the wiper is 250 $\Omega$ . If a voltage is forced on  $V_{\text{ADJ}}$  from a hard source, voltage should be limited to  $-0.5$ , and  $+5.0\text{V}$ , or current limited to  $\pm 1.0\text{ mA}$ . This includes capacitively coupled signals because even small values of capacitors contain enough energy to degrade the input stage if the capacitor is driven with a large, fast slewing signal. The  $V_{\text{ADJ}}$  pin may be used to abort the timing cycle. Grounding this pin during the timing period causes the timer to react just as if the capacitor voltage had reached its normal RC trigger point; the capacitor discharges and the output changes state. An exception to this occurs if the trigger pin is held high when the  $V_{\text{ADJ}}$  pin is grounded. In this case, the output changes state, but the capacitor does not discharge. If the trigger drops while  $V_{\text{ADJ}}$  is being held low, discharge will occur immediately and the cycle will be over. If the trigger is still high when  $V_{\text{ADJ}}$  is released, the output may or may not change state, depending the voltage across the timing capacitor. For voltages below 2.0V during the timing capacitor, the output will change state immediately, then once more as the voltage rises past 2.0V. For voltages above 2.0V, no change will occur in the output.

In noisy environments or in comparator-type applications, a bypass capacitor on the  $V_{\text{ADJ}}$  terminal may be needed to eliminate spurious outputs because it is high impedance point. The size of the cap will depend on the frequency and energy content of the noise. A  $0.1\mu\text{F}$  will generally suffice for spike suppression, but several  $\mu\text{F}$  may be used if the timer is subjected to high level 60 Hz EMI.

The emitter and the collector outputs of the timer can be treated just as if they were an ordinary transistor with 40V minimum collector-emitter breakdown voltage. Normally, the emitter is tied to the ground pin and the signal is taken from the collector, or the collector is tied to  $V^{+}$  and the signal is taken from the emitter. Variations on these basic connections are possible. The collector can be tied to any positive voltage up to 40V when the signal is taken from the emitter. However, the emitter will not be pulled higher than the supply voltage on the  $V^{+}$  pin. Connecting the collector to a voltage less than the  $V^{+}$  voltage is allowed. The emitter should not be connected to a hard source other than that to which the ground pin is tied. The transistor has built-in current limiting with a typical knee current of 120 mA. Temporary short circuits are allowed; even with collector-emitter voltages up to 40V. The power time product, however, must not exceed 15 watt-seconds

for power levels above the maximum rating of the package. A short to 30V, for instance, can not be held for more than 4 seconds. These levels are based on a 40°C maximum initial chip temperature. When driving inductive loads, always use a clamp diode to protect the transistor from inductive kick-back.

A boost pin is provided on the LM122 to increase the speed of the internal comparator. The comparator is normally operated at low current levels for lowest possible input current. For short time intervals where low input current is not needed, comparator operating current can be increased several orders of magnitude for fast operation. Shorting the boost terminal to  $V^+$  increases the emitter current of the vertical PNP drivers in the differential stage from 25 nA to 5.0µA.

With the timer in the unboosted state, timing periods are accurate down to about 1 ms. In the boosted mode, loss of accuracy due to comparator speed is only about 800 ns, so timing periods of several microseconds can be used.

The "Logic" pin is used to reverse the signal appearing at the output transistor. An open or "high" condition on the logic pin programs the output transistor to be "off" during the timing period and "on" all other times. Grounding the logic pin reverses the sequence to make the transistor "on" during the timing period. Threshold for the logic is typically 150 mV with 150µA flowing out of the terminal. If an active drive to the logic pin is desired, a saturated transistor drive is recommended, either with a discrete transistor or the open collector output of integrated logic. A maximum  $V_{SAT}$  of 75 mV at 200µA is required. A typical example of active drive to the logic pin is the pulse width discriminator shown in Figure 16.

## CALCULATING WORST CASE TIMING ERROR

Timing errors for the LM122 come from the following sources:

1. Timing ratio error
2. Capacitor saturation voltage
3. Internal switching delays
4. Comparator bias current
5. External resistor and capacitor tolerance
6. Capacitor and board leakage

In general, errors 1 and 5 are the most significant, so they will be treated first.

For most applications, the major contribution to timing error from the LM122 itself is variation in timing ratio, which is the ratio of the comparator threshold voltage (typically 2.0V) to the voltage at the  $V_{REF}$  pin. A 1% error in this ratio results in a 1.8% initial timing error. Timing ratio error comes from variations in the internal divider ratio and from offset voltage in the comparator. The

LM122 is specified to have a timing ratio from 0.626 to 0.638 at +25°C, giving a ±1.8% worst case contribution to initial timing period error. Over temperature, the worst case figures doubles to ±3.6%. If the initial error is trimmed out externally however, timing error drift due to timing ratio will generally be less than ±0.5% over temperature.

Adding all the contributions to timing error from the LM122 itself will usually give a figure in the 2% to 3% range at +25°C. External timing components ( $R_t$  and  $C_t$ ) will normally contribute much more error than this unless selected components are used. ±5% tolerance on  $R_t$  and  $C_t$  will increase the worst case error to 12% to 13%. By trimming out initial component errors, an exact initial timing period can be obtained, but temperature drift then becomes the limiting factor. For most applications, the contributions to timing period drift due to the LM122 itself will be in the 0.005%/°C to 0.02%/°C range.

If accurate timing over temperature is required, low drift components must be used for  $R_t$  and  $C_t$ . Capacitors are available with temperature coefficients of 100 to 200 ppm/°C. Resistors, at least in the lower ranges, are available with TC's much better than this. Above 1 MΩ, however, care must be used in the selection of a low TC resistor. Units are available up to 100 MΩ with less than 100 ppm/°C drift.

Capacitor saturation voltage is the voltage still remaining on the timing capacitor after it has been reset to as near ground as the internal discharge transistor can drive it. For timing resistors 1 MΩ or greater, this remaining voltage is typically 2.5 mV. For smaller timing resistors, the capacitor saturation voltage can be calculated by the following formula:

$$V_C \approx 2.5 \text{ mV} + \frac{(V_{REF}) * (80\Omega)}{R_t}$$

\* $V_{REF}$  = 3.15V

The effect of  $V_C$  on timing period is linear at 0.03%/mV. Temperature dependence of  $V_C$  is typically +0.2%/°C for  $R_t \leq 300\text{k}\Omega$ , rising to 0.4%/°C for  $R_t = 10 \text{ k}\Omega$ . This gives a typical temperature coefficient of timing error *due to*  $V_C$  of (0.002) (2.5 mV) (0.03%/mV) = 0.0015%/°C for  $R_t \geq 1 \text{ M}\Omega$  and (0.004) (24 mV) (0.03%/mV)  $\approx$  0.003%/°C for  $R_t = 10 \text{ k}\Omega$ . Since most applications can use timing resistors in the range of 100 kΩ and up, error *from capacitor saturation voltage* rarely exceeds 0.15% initially, with ±0.05% variation over the full temperature range.

Internal switching delays cause errors which tend to be a fixed time rather than a percentage of the timing period. In the boosted mode this delay is typically 800 ns, and with the boost off; the delay is about 25µs. These times can be added



directly to the calculated timing period for worst case analysis. For timing periods longer than 25 ms, the 25 $\mu$ s delay gives an error of 0.1% or less. In the range of 1 or 25 ms, error due to delays is 0.1% or less for the boosted mode, rising to a maximum of 4.0% in the unboosted mode. At  $\tau = 10\mu$ s, delay is the major contribution to timing error ( $\approx 8\%$ ).

Comparator bias current contributes a negligible timing error for all but very long time timing periods. Error can be calculated with a simple formula:

$$\text{Error (\%)} = -50 \cdot R_t \cdot I_b \quad (\text{Note sign})$$

$I_b$  = Comparator Bias Current

$R_t$  = Timing Resistor

For  $R_t = 100 \text{ M}\Omega$  and  $I_b = 0.3 \text{ nA}$  (typical) a 1.5% reduction in timing period is incurred. For worst case calculations at +25°C, an  $I_b$  of 1 nA maximum is specified in the unboosted mode and 100 nA in the boosted mode. At temperatures below +25°C, these numbers still hold. At +125°C,  $I_b$  increases due to leakage to a maximum of  $\pm 5 \text{ nA}$  unboosted. For worst case calculations below +125°C, the leakage error (5 nA) can be assumed to halve for each 10°C drop below +125°C. At +95°C for instance, the leakage component of  $I_b$  would be (5 nA/8)  $\approx 0.6 \text{ nA}$  for a total  $I_b$  of 1.6 nA worst case. For the commercial LM322 and LM3905, worst case  $I_b$  is 2 nA at +75°C, and for the LM2905  $I_b$  is 2 nA maximum at +85°C. For temperatures between -25°C and +85°C, the TC of  $I_b$  is typically 5 pA/°C in the unboosted mode and 100 pA/°C in the boosted mode. For a 100 M $\Omega$   $R_t$ , this 5 pA/°C contributes -0.025%/°C to timing period drift.

$$\text{Error (\%/°C)} = (-50)(\Delta I_b/\Delta T)(R_t)$$

For worst case calculations a  $\Delta I_b/\Delta T$  (-25  $\leq T_A \leq$  +85°C) of 12 pA/°C may be used for the LM122/LM222 and 20 pA/°C for the LM322 and LM2905/LM3905.

External leakage paths may cause timing errors for large values of  $R_t$  and high board temperatures. Connections made to the R/C pin should be kept free of dust, moisture, and soldering flux if long time intervals are to be kept accurate. All package types have the R/C pin located between  $V_{REF}$  and the ground pin to minimize these leakages.

## DESIGN HINTS

### Eliminating Timing Cycle Upon Initial Application of Power

The LM122 will start a timing cycle automatically (with no trigger input) when  $V^+$  is first turned on. If this characteristic is undesirable, it can be defeated by tying the timing capacitor to  $V_{REF}$  instead of ground as shown in Figure 2. This connection does not affect operation of the timer in any other way. If an electrolytic timing capacitor is used, be sure the negative end is tied to the R/C pin and the positive end to  $V_{REF}$ . A 1.0 k $\Omega$

resistor should be included in series with the timing capacitor to limit the surge current load on  $V_{REF}$  when the capacitor is discharged.

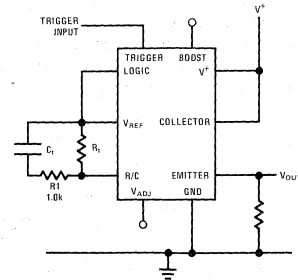


FIGURE 2. Eliminating Initial Timing Cycle

### Using Electrolytic Timing Capacitors

Electrolytic capacitors are not usually recommended for timing because of their unstable capacitance and high leakage. For long timing periods (> 10 seconds) at moderate temperatures (0°C to 50°C) however, an electrolytic may be attractive because of its low cost per microfarad. Solid tantalum capacitors such as the Kemet\* C series T310 (molded epoxy) or T110 (hermetic) are recommended. These units have long term stabilities of 2% to 3% and a temperature coefficient of +0.2%/°C. Selected units are available for timing use with very low leakage.

### Reset Time

The timing capacitor used with the LM122 is reset with an internal transistor which has a collector offset voltage of 2.5 mV @ 1 $\mu$ A with approximately 80 $\Omega$  of collector resistance. The time required to reset this capacitor determines the minimum time between timing pulses. An approximate formula for reset time is:

$$\text{Reset Time} = (80 \Omega) (C_t^\dagger) (5)$$


$^\dagger C_t$  = External timing capacitor.

### NOISY ENVIRONMENTS


The LM122 is relatively insensitive to noise on supply lines and to radiated energy. In *extremely* noisy environments however, it may be necessary to configure the LM122 differently, both to eliminate false triggering and to prevent premature end of a timing period. The circuit "a" shown in Figure 3 has been set up for maximum noise rejection. C1 bypasses the  $V_{ADJ}$  pin because of the relatively high impedance ( $\approx 30 \text{ k}\Omega$ ) of this point. Negative spikes on the  $V_{ADJ}$  pin will cause premature end of the timing period. C2 bypasses the supply for rejection of fast transients. R1 sets up the trigger pin to a "normally high" condition. This prevents extremely high electromagnetic fields from triggering the internal flip-flop during a timing period. The input trigger signal is capacitively coupled through C3. Triggering occurs on the *negative* edge of the trigger pulse as shown in the waveform sketch next to Figure 21.

\*Manufactured by Union Carbide

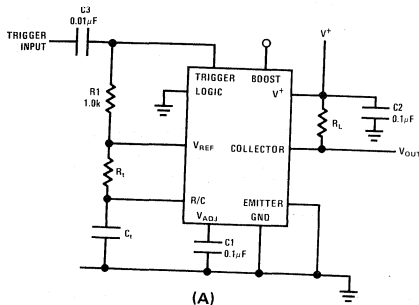If the output voltage from the LM122 can be set up to go "high" during the timing cycle, the alternate connection shown in "b" can be used. Here, the trigger is held high by D2 during the timing period. When the output goes low after the timing period is over, the circuit may be retriggered immediately via D1. R1 and C3 suppress unwanted spikes at the trigger input.



(A)

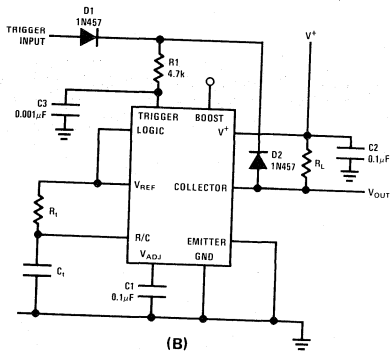

(B)

FIGURE 3. Maximum Noise Immunity

### ABORTING A TIMING CYCLE (Figure 4)

The LM122 does not have an input specifically allocated to a stop-timing function. If such a function is desired, it may be accomplished several ways:

- Ground  $V_{ADJ}$
- Raise R/C more positive than  $V_{ADJ}$
- Wire "OR" the output

Grounding  $V_{ADJ}$  will end the timing cycle just as if the timing capacitor had reached its normal discharge point. A new timing cycle can be started by the trigger terminal as soon as the ground is released. A switching transistor is best for driving  $V_{ADJ}$  to as near ground as possible. Worst case sink current is about  $300\mu A$ .

A timing cycle may be also ended by a positive pulse to a resistor ( $R \leq R_L/100$ ) in series with the timing capacitor. The pulse amplitude must be

at least equal to  $V_{ADJ}$  (2.0V), but should not exceed 5.0V. When the timing capacitor discharges, a negative spike of up to 2.0V will occur across the resistor, so some caution must be used if the drive pulse is used for other circuitry.

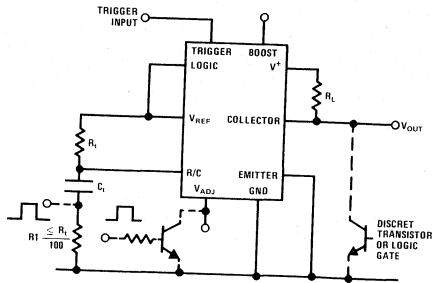


FIGURE 4. Cycle Interrupt

The output of the timer can be wire ORed with a discrete transistor or an open collector logic gate output. This allows overriding of the timer output, but does not cause the timer to be reset until its normal cycle time has elapsed.

### Using the LM122 as a Comparator

A built-in reference and zero volt common mode limit make the LM122 very useful as a comparator. Threshold may be adjusted from zero to three volts by driving the  $V_{ADJ}$  terminal with a divider tied to  $V_{REF}$ . Stability of the reference voltage is typically  $\pm 1\%$  over a temperature range of  $-55^\circ C$  to  $+125^\circ C$ . Offset voltage drift in the comparator is typically  $25\mu V/^\circ C$  in the boosted mode and  $50\mu V/^\circ C$  unboosted. A resistor can be inserted in series with the input to allow overdrives up to  $\pm 50V$  as shown in Figure 5. There is actually no limit on input voltage as long as current is limited to  $\pm 1$  mA. The resistor shown contributes


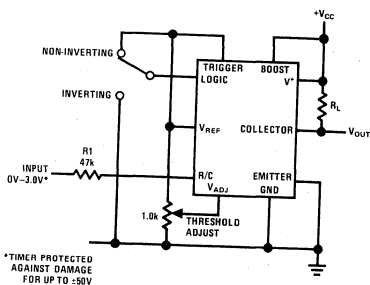


FIGURE 5. Comparator With 0 Volts to 3.0 Volts Threshold

a worst case of 5 mV to initial offset. In the unboosted mode, the error drops to 0.25 mV maximum. The capability of operating off a single 5V supply should make this comparator very useful.
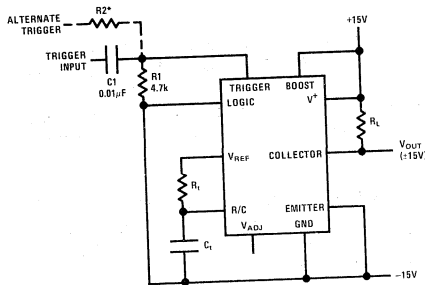
## Using Dual Supplies

The LM122 can be operated off dual supplies as shown in Figure 6. The only limitation is that the emitter terminal cannot be tied to ground, it must either drive a load referred to  $V^-$  or be actually tied to  $V^-$  as shown. Although capacitive coupling is shown for the trigger input (to allow 5V triggering), a resistor can be substituted for C1. R2 must be chosen to give proper level shifting between the trigger signal and the trigger pin of the timer. Worst case "lo" on the trigger pin (with respect to  $V^-$ ) is 0.8V, and worst case "high" is 2.5V. R2 may be calculated from the divider equation with R1 to give these levels.




\*SELECT FOR PROPER LEVEL SHIFT  
EMITTER TERMINAL OR EMITTER LOAD MUST BE TIED TO GND PIN OF TIMER.

FIGURE 6. Operating Off Dual Supplies
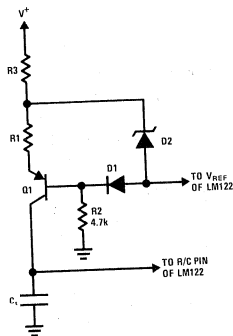
## LINEARIZING THE CHARGING SWEEP

In some applications (such as a linear pulse width modulator) it may be desirable to have the timing capacitor charge from a constant current source. A simple way to accomplish this is shown in the accompanying sketch.



Q1 converts the current through R1 to a current source independent of the voltage across  $C_t$ . R2, R3, D1, and D2 are added to make the current through R1 independent of supply variations and temperature changes. (D2 is a low TC type) D2 and R3 can be omitted if the  $V^+$  supply is stable and D1 and R2 can be omitted also if temperature stability is not critical. With D1 and R2 omitted, the current through R1 will change about 0.015%/°C with a 15V supply and 0.1%/°C with a 5.0V supply.

## APPLICATIONS

### Basic Timers

Figure 7 is a basic timer using the collector output.  $R_t$  and  $C_t$  set the time interval with  $R_L$  as the load. During the timing interval the output may be

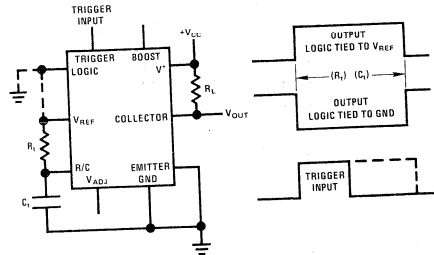


FIGURE 7. Basic Timer-Collector Output and Timing Chart

either high or low depending on the connection of the logic pin. Timing waveforms are shown in the sketch alongside Figure 7.

Figure 8 is again a basic timer, but with the output taken from the emitter of the output transistor. As with the collector output, either a high or low condition may be obtained during the timing period.

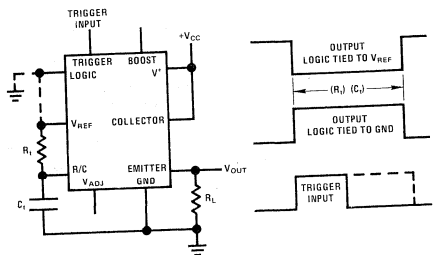


FIGURE 8. Basic Timer-Emitter Output and Timing Chart

Figure 9 shows the timer interfacing 5V logic to a high voltage relay. Although the  $V^+$  terminal could be tied to the +28V supply, this would be

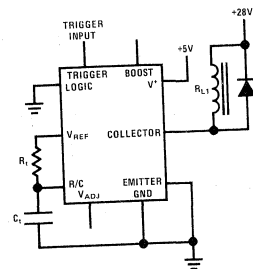


FIGURE 9. 5 Volt Logic Supply Driving 28 Volt Relay

an unnecessary waste of power in the IC. In any case, the threshold for the trigger is 1.6V regardless of where  $V^+$  is tied.

Figure 10 indicates the ability of the timer to interface to digital logic when operating off a high supply voltage.  $V_{OUT}$  swings between +5V and ground with a minimum fanout of 5 for medium speed TTL.

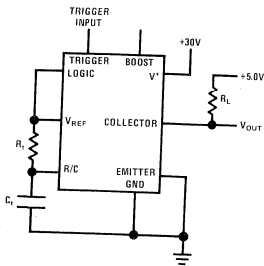


FIGURE 10. 30 Volt Supply Interfacing to 5 Volt Logic

Figure 11 is an application where the LM122 is used to simulate a thermal delay relay which

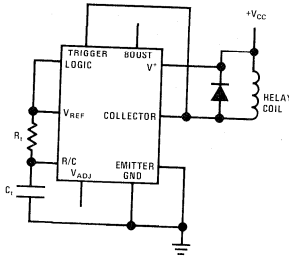


FIGURE 11. Time Out on Power Up (Relay Energized  $R_t C_t$  Seconds After  $V_{CC}$  is Applied)

prevents power from being applied to other circuitry until the supply has been on for some time. The relay remains de-energized for  $R_t C_t$

seconds after  $V_{CC}$  is applied, then closes and stays energized until  $V_{CC}$  is turned off. Figure 12 is a similar circuit except that the relay is energized


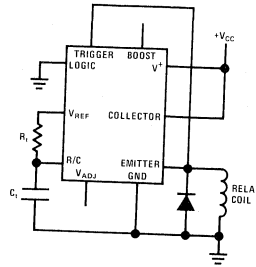


FIGURE 12. Time Out on Power Up (Relay Energized Until  $R_t C_t$  Seconds After  $V_{CC}$  is Applied)

as soon as  $V_{CC}$  is applied.  $R_t C_t$  seconds later, the relay is de-energized and stays off until the  $V_{CC}$  supply is recycled.

Figure 13 is a more advanced application of the LM122 as a proportioning temperature controller with optical isolation and synchronized zero crossing features. The timing function is not used. Instead the trigger terminal is held high and the LM122 is used as a high gain comparator with a built in reference. R1 is a thermistor with a  $-4\%/^{\circ}\text{C}$  temperature coefficient used as the sensor. R2 is used to set the temperature to be controlled by R1. R3 through R8 set up the proportioning action. R3 raises the impedance of the R1/R2 divider so that R5 sees a relatively constant impedance independent of the set point temperature. R6 and R8 reduce the  $V_{ADJ}$  impedance so that internal variations in divider impedance do not affect proportioning action. R5 and R7 set

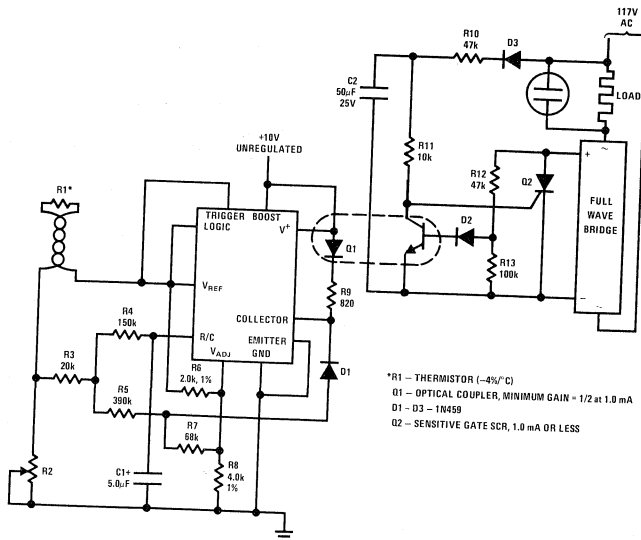

\*R1 - THERMISTOR ( $-4\%/^{\circ}\text{C}$ )  
 O1 - OPTICAL COUPLER, MINIMUM GAIN = 1/2 at 1.0 mA  
 D1 - D3 - 1N459  
 O2 - SENSITIVE GATE SCR, 1.0 mA OR LESS

FIGURE 13. Proportioning Temperature Controller with Synchronized Zero-Crossing

the actual width of the proportioning band and can be scaled as necessary to alter the width of the band. Larger resistors make the band narrower. The values shown give approximately a 1°C band. R4 and C1 determine the proportioning frequency which is about 1 Hz with the values shown. C1 or R4 can change to alter frequency, but R4 should be between 50k and 500k, and C1 must be a low leakage type to prevent temperature shifts. D1 prevents supply voltage fluctuations from affecting set point or proportioning band. Any unregulated supply between 6V and 15V is satisfactory.

Q1 is an optical isolator with a minimum gain of 0.5. With the values shown for R9, R10, and R11, Q1 is over-driven by at least 3 to 1 to insure deep saturation for reliable turn off of the SCR. Q2 must be a sensitive gate device with a worst case gate firing current of 0.5 mA. R12, R13, and D2 implement the synchronized zero-crossing feature by preventing Q1 from turning off after the voltage across Q2 has climbed above 2.5V. D3, R10, and C2 provide a source of semifiltered dc current for SCR gate drive. D3 and Q2 must have a minimum breakdown of 200V.

Figure 14 shows the LM122 connected as a one hour timer with manual controls for start, reset, and cycle end. S1 starts timing, but has no effect after timing has started. S2 is a center off switch which can either end the cycle prematurely with

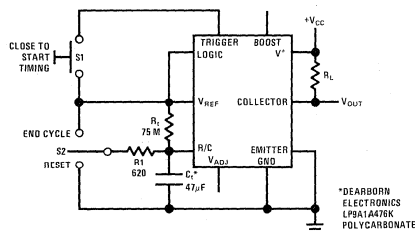


FIGURE 14. One Hour Timer With Reset and Manual Cycle End

the appropriate change in output state and discharging of  $C_t$ , or cause  $C_t$  to be reset to 0V without a change in output. In the latter case, a new timing period starts as soon as S2 is released. The average charging current through  $R_t$  is about 30 nA, so some attention must be paid to parts layout to prevent stray leakage paths. The suggested timing capacitor has a typical self time constant of 300 hours and a guaranteed minimum of 25 hours at +25°C. Other capacitor types may be used if sufficient data is available on their leakage characteristics.

Figure 15 is another application where the LM122 does not use its timing function. A switching regulator is made using the internal reference and comparator to drive a PNP switch transistor. Features of this circuit include a 5.5V minimum input voltage at 1A output current, low part count, and good efficiency (> 75%) for input

voltages to 10V. Line and load regulation are less than 0.5% and output ripple at the switching frequency is only 30 mV. Q1 is an inexpensive plastic device which does not need a heatsink for ambient temperature up to 50°C. D1 should be a fast switching diode. Output voltage can be adjusted between 1V and 30V by choosing proper values for R2, R3, R4, and R5. For outputs less than 2V, a divider with 250Ω Thevinin resistance must be connected between  $V_{REF}$  and ground with its tap point tied to  $V_{ADJ}$ .

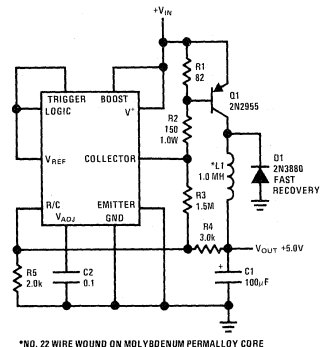


FIGURE 15. 5 Volt Switching Regulator With 1.0 Amp Output and 5.5 Volt Minimum Input

By driving the logic terminal of the LM122 simultaneously to the trigger input, a simple, accurate pulse width detector can be made (Figure 16).

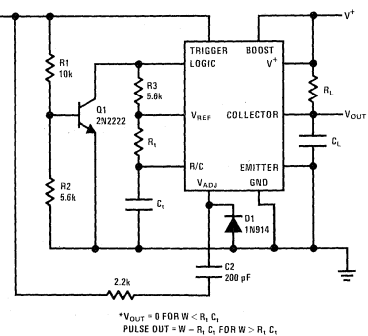


FIGURE 16. Pulse Width Detector

In this application the logic terminal is normally held high by R3. When a trigger pulse is received, Q1 is turned on, driving the logic terminal to ground. The result of triggering the timer and reversing the logic at the same time is that the output does not change from its initial low condition. The only time the output will change states is when the trigger input stays high longer than one time period set by  $R_t$  and  $C_t$ . The output pulse width is equal to the input trigger width minus  $R_t \cdot C_t$ . C2 insures no output pulse for short (< RC) trigger pulses by prematurely resetting the timing capacitor when the trigger pulse drops.

$C_L$  filters the narrow spikes which would occur at the output due to interval delays during switching.

The LM122 can be used as a two terminal time delay switch if an "on" voltage drop of 2V to 3V can be tolerated. In Figure 17, the timer is used to drive a relay "on"  $R_t C_t$  seconds after application of power. "off" current of the switch is 4 mA maximum, and "on" current can be as high as 50 mA.

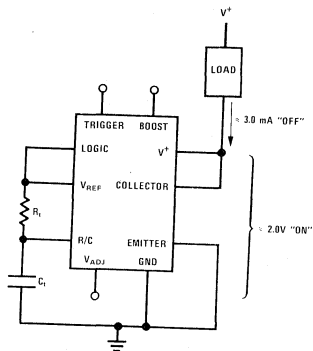


FIGURE 17. Two-Terminal Time Delay Switch

An accurate frequency to voltage converter can be made with the LM122 by averaging output pulses with a simple one pole filter as shown in Figure 18. Pulse width is adjusted with R2 to

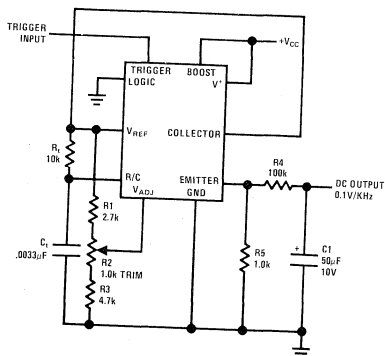


FIGURE 18. Frequency to Voltage Converter (Tachometer) Output Independent of Supply Voltage

provide initial calibration at 10 kHz. The collector of the output transistor is tied to  $V_{REF}$ , giving constant amplitude pulses equal to  $V_{REF}$  at the emitter output. R4 and C1 filter the pulses to give a dc output equal to,  $(R_t)(C_t)(V_{REF})(f)$ . Linearity is about 0.2% for a 0V to 1V output. If better linearity is desired R5 can be tied to the summing node of an op amp which has the filter in the feedback path. If a low output impedance is desired, a unity gain buffer such as the LM110 can be tied to the output. An analog meter can be driven directly by placing it in series with R5 to ground. A series RC network across the meter to provide damping will improve response at very low frequencies.

In some applications it is desirable to reduce supply drain to zero between timing cycles. In Figure 19 this is accomplished by using an external PNP as a latch to drive the  $V^+$  pin of the timer.

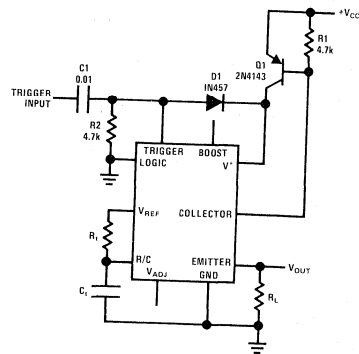


FIGURE 19. Zero Power Dissipation Between Timing Intervals

Between timing periods Q1 is off and no supply current is drawn. When a trigger pulse of 5V minimum amplitude is received, the LM122 output transistor and Q1 latch for the duration of the timing period. D1 prevents coupling back into the trigger signal from the dc load created by the trigger input. If the trigger input is a short pulse, C1 and R2 may be eliminated.  $R_L$  must have a minimum value of  $(V_{CC})/(2.5 \text{ mA})$ .

The LM122 can be made into a self-starting oscillator by feeding the output back to the trigger input through a capacitor as shown in Figure 20. Operating frequency is  $1/(R_t C_t)$ . The

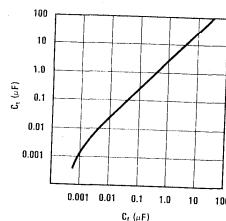
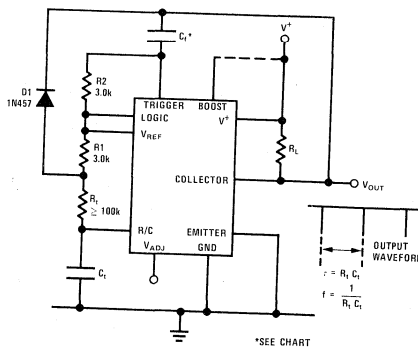


FIGURE 20. Oscillator

output is a narrow negative pulse whose width is approximately  $2R_2 C_f$ . For optimum frequency

stability,  $C_f$  should be as small as possible. The minimum value is determined by the time required to discharge  $C_t$  through the internal discharge transistor. A conservative value for  $C_f$  can be chosen from the graph included with Figure 20. For frequencies below 1 kHz, the frequency error introduced by  $C_f$  is a few tenths of one percent or less for  $R_t > 500k$ .

Although the LM122 is triggered by a positive going trigger signal, a differentiator tied to a normally "high" trigger will result in negative edge triggering. In Figure 21, R1 serves the dual

purpose of holding the trigger pin normally high and differentiating the input trigger pulse coupled through C1. The timing diagram included with Figure 21 shows that triggering actually occurs a short time after the negative going trigger, while positive going triggers have no effect. The delay time between a negative trigger signal and actual starts of timing is approximately  $0.5$  to  $1.5 R_1 C_1$  depending on the trigger amplitude, or about  $2.5$  to  $7.5\mu s$  with the values shown. This time will have to be increased for  $C_t$  larger than  $0.01\mu F$  because  $C_t$  is charged to  $V_{REF}$  whenever the trigger pin is kept high and must reset itself during the short time that the trigger pin voltage is low. A conservative value for C1 is:

$$C_1 \geq \frac{C_t}{10}$$

The LM122 can be connected as a chain of timers quite easily with no interface required. In Figure 22A and 22B, two possible connections are shown. In both cases, the output of the timer is low during the timing period so that the positive going signal at the end of timing period can trigger the next timer. There is no limitation on the timing period of one timer with respect to any other timer before or after it, because the trigger input to any timer can be high or low when that timer ends its timing period.

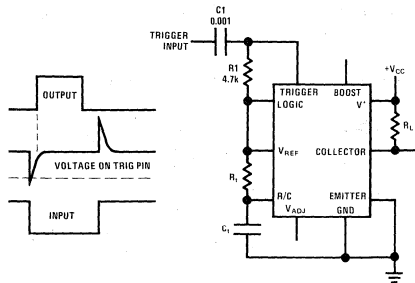


FIGURE 21. Timer Triggered by Negative Edge of Input Pulse


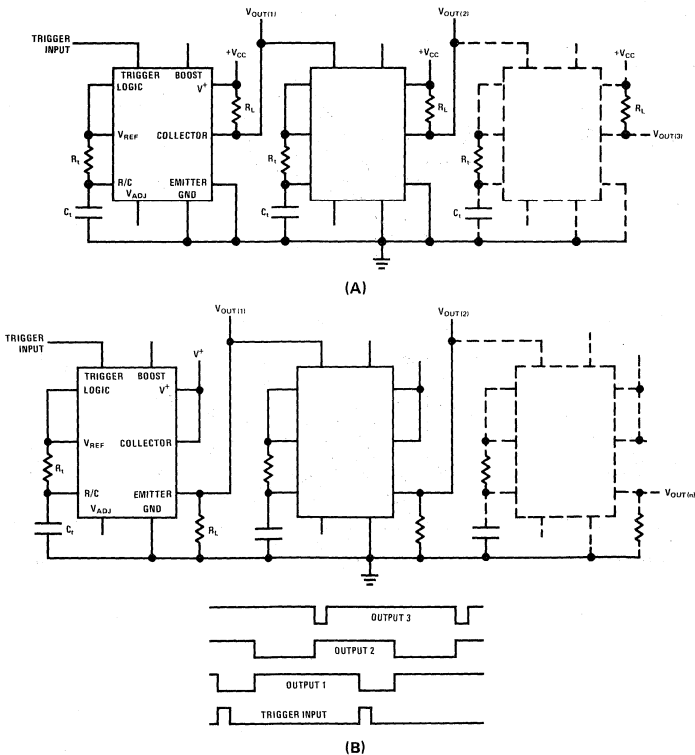



FIGURE 22. Chain of Timers

# typical performance characteristics


Comparator Bias Current

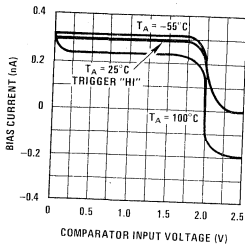


Comparator Bias Current

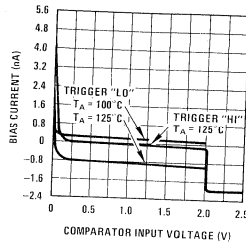


Comparator Bias Current

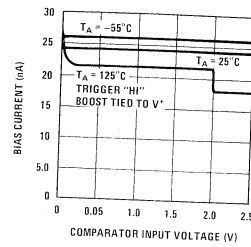


Supply Current

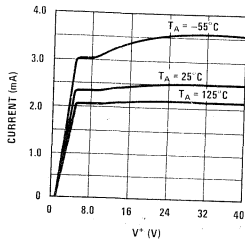


Trigger Input Characteristics

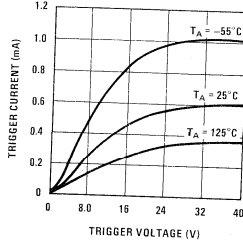


Trigger Threshold

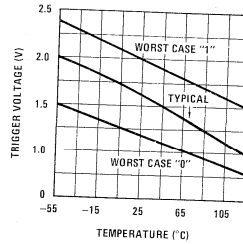

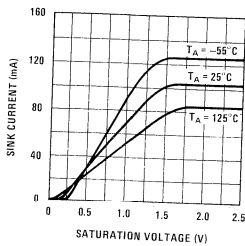
Collector Output Saturation Characteristics at High Current



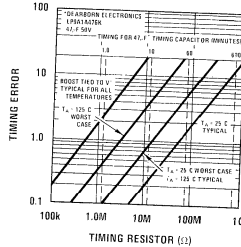
Timing Error Due to Comparator Bias Current




Reference Regulation

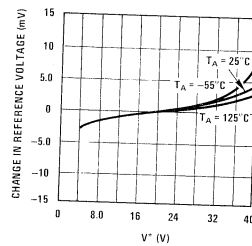


Reference Regulation

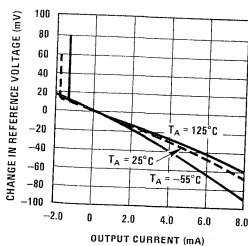

Suggested Timing Components

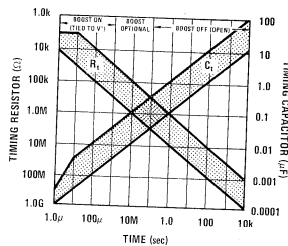

Short Output Pulse

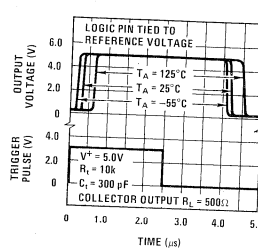



# LM340 Series Three Terminal Positive Regulators

National Semiconductor  
 Application Note 103  
 Nello Sevastopoulos  
 George Cleveland  
 Jim Sherwin  
 March 1974  
 Revised August 1980



## INTRODUCTION

The LM340-XX are three terminal 1.0A positive voltage regulators, with preset output voltages of 5.0V or 15V. The LM340 regulators are complete 3-terminal regulators requiring no external components for normal operation. However, by adding a few parts, one may improve the transient response, provide for a variable output voltage, or increase the output current. Included on the chip are all of the functional blocks required of a high stability voltage regulator; these appear in Figure 1.

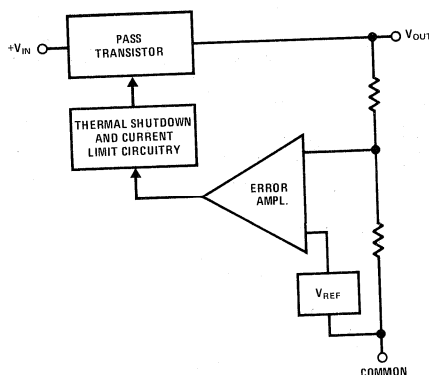


FIGURE 1. Functional Block of the LM340

The error amplifier is internally compensated; the voltage reference is especially designed for low noise and high predictability; and, as the pass element is included, the regulator contains fixed current limiting and thermal protection. The LM340 is available in either metal can TO-3 or plastic TO-220 package.

## 1. CIRCUIT DESIGN

### Voltage Reference

Usually IC voltage regulators use temperature-compensated zeners as references. Such zeners exhibit  $BV > 6.0V$  which sets the minimum supply

voltage somewhat above 6.0V. Additionally they tend to be noisy, thus a large bypass capacitor is required.

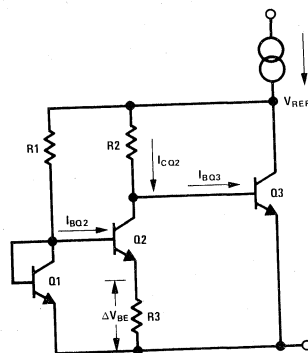


FIGURE 2. Simplified Volt Reference

Figure 2 illustrates a simplified reference using the predictable temperature, voltage, and current relationship of emitter-base junctions.

Assuming  $J_{Q1} > J_{Q2}$ ,  $I_{CQ2} \gg I_{BQ2} = I_{BQ3}$ , Area (emitter Q1) = Area (emitter Q2),

$$\text{and } V_{BEQ1} = V_{BEQ3}, \text{ then} \quad (1-1)$$

$$V_{REF} \approx \left( \frac{kT}{q} \ln \frac{R2}{R1} \right) \frac{R2}{R3} + V_{BEQ3} \quad (1-2)$$

### Simplified LM340

In Figure 3 the voltage reference includes R1 - R3 and Q1 - Q5. Q3 also acts as an error amplifier and Q6 as a buffer between Q3 and the current source. If the output drops, this drop is fed back, through R4, R5, Q4, Q5, to the base of Q3. Q7 then conducts more current re-establishing the output given by:

$$V_{OUT} = V_{REF} \frac{R4 + R5}{R4}$$

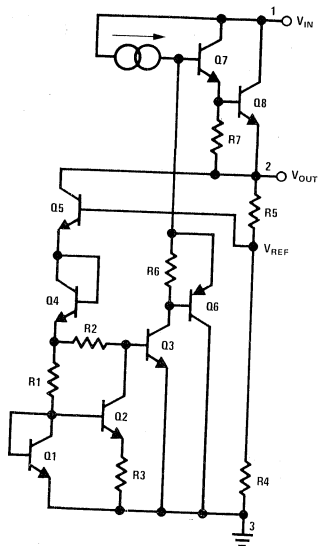


FIGURE 3. LM340 Simplified

### Complete Circuit of the LM340 (Figure 4)

Here  $(J_{Q2}, J_{Q3}) > (J_{Q4}, J_{Q5})$  and a positive TC  $\Delta V_{BE}$  appears across R6. This is amplified by 17,  $(R6/R6 = 17)$  and is temperature compensated by the  $V_{BE}$  of Q6, Q7, Q8 to develop the reference voltage. R17 is changed to get the various fixed output voltages.

### Short Circuit Protection

A)  $V_{IN} - V_{OUT} < 6.0V$ : There is no current through D2 and the maximum output current will be given by:

$$I_{OUT MAX} = \frac{V_{BEQ14}}{R16} \approx 2.2A \quad (T_j = 25^\circ C) \quad (1-4)$$

B)  $V_{IN} - V_{OUT} > 6.0V$ : To keep Q16 operating within its maximum power rating the output current limit must decrease as  $V_{IN} - V_{OUT}$  increases. Here D2 conducts and the drop across R16 is less than  $V_{BE}$  to turn on Q14. In this case  $I_{OUT}$  maximum is:

$$I_{OUT MAX} = \frac{1}{R16} \left( V_{BEQ14} - \frac{[(V_{IN} - V_{OUT}) - V_{ZD2} - V_{BEQ14}]}{R13} R14 \right) \quad (1-5)$$

$$= 0.077 [37.2 - (V_{IN} - V_{OUT})] \quad (A)$$

at  $T_j = 25^\circ C$

### Thermal Shut Down

In Figure 4 the  $V_{BE}$  of Q13 is clamped to 0.4V. When the die temperature reaches approximately  $+175^\circ C$  the  $V_{BE}$  to turn on Q13 is 0.4V. When Q13 turns on it removes all base drive from Q15

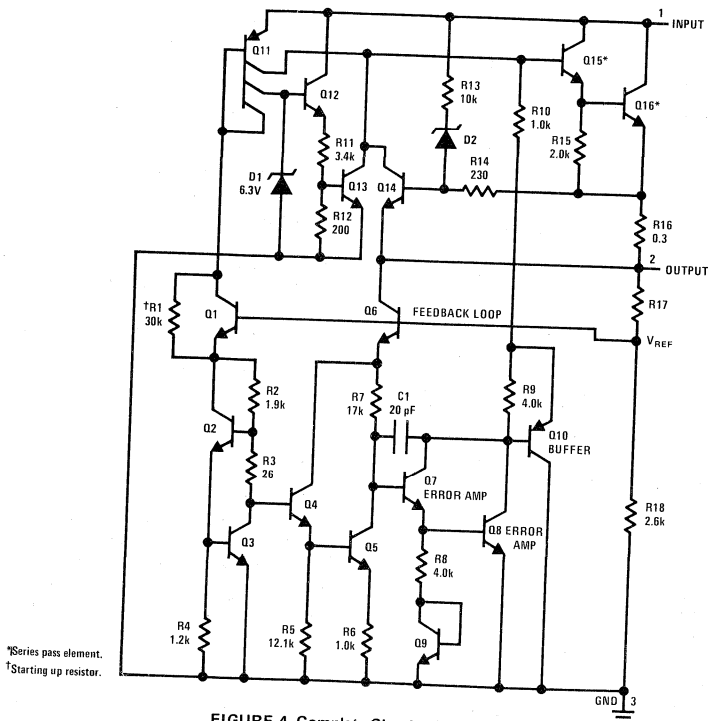


FIGURE 4. Complete Circuit of the LM340

\*Series pass element.  
†Starting up resistor.

which turns off the regulator thus preventing a further increase in die temperature.

### Power Dissipation

The maximum power dissipation of the LM340 is given by:

$$P_{D\text{MAX}} = (V_{IN\text{MAX}} - V_{OUT}) I_{OUT\text{MAX}} + V_{IN\text{MAX}} I_Q \quad (1-6)$$

The maximum junction temperature (assuming that there is no thermal protection) is given by:

$$T_{JM} = \frac{36 - 13 I_{OUT\text{MAX}} - (V_{IN} - V_{OUT})}{0.0855} + 25^\circ\text{C} \quad (1-7)$$

Example:

$V_{IN\text{MAX}} = 23\text{V}$ ,  $I_{OUT\text{MAX}} = 1.0\text{A}$ , LM340T-15.

Equation (1-7) yields:  $T_{JM} = 200^\circ\text{C}$ . So the  $T_J$  max of  $150^\circ\text{C}$  specified in the data sheet should be the limiting temperature.

From (1-6)  $P_D \cong 8.1\text{W}$ . The thermal resistance of the heat sink can be estimated from:


$$\theta_{s-a} = \frac{T_{J\text{MAX}} - T_A}{P_D} - (\theta_{j-c} + \theta_{c-s}) \quad (1-8)$$

The thermal resistance  $\theta_{j-c}$  (junction to case) of the TO-220 package is  $6^\circ\text{C/W}$ , and assuming a  $\theta_{c-s}$  (case to heat sink) of 0.4, equation (1-8) yields:

$$\theta_{s-a} = 8.4^\circ\text{C/W}$$
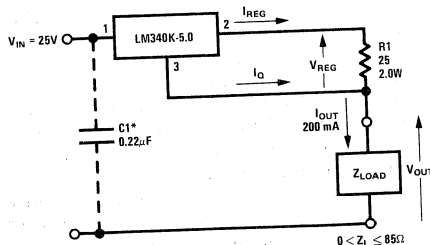
## 2. CURRENT SOURCE

The circuit shown on Figure 5 provides a constant output current (equal to  $V_{OUT}/R1$  or 200 mA)



\*Required if regulator is located far from power supply filter.

FIGURE 5. Current Source

for a variable load impedance of 0 to  $85\Omega$ . Using the following definitions and the notation shown on Figure 5,  $Z_{OUT}$  and  $I_{OUT}$  are:

$Q_{CC}/V$  = Quiescent current change per volt of input/output (pin 1 to pin 2) voltage change of the LM340

$L_r/V$  = Line regulation per volt: the change in the LM340 output voltage per volt of input/output voltage change at a given  $I_{OUT}$ .

$$\Delta I_{OUT} = (Q_{CC}/V) \Delta V_{OUT} + \frac{L_r/V}{R1} \Delta V_{OUT} \quad (2-1)$$

$$Z_{OUT} = \frac{\Delta V_{OUT}}{\Delta I_{OUT}} \quad (2-2)$$

$$Z_{OUT} = \frac{\Delta V_{OUT}}{(Q_{CC}/V) \Delta V_{OUT} + \frac{(L_r/V)}{R1} \Delta V_{OUT}} \quad (2-3)$$

$$Z_{OUT} = \frac{1}{(Q_{CC}/V) + \frac{(L_r/V)}{R1}} \quad (2-4)$$

The LM340-5.0 data sheet lists maximum quiescent current change of 1.0 mA for a 7.0V to 25V change in input voltage; and a line regulation (interpolated for  $I_{OUT} = 200\text{mA}$ ) of 35 mV maximum for a 7.0V to 25V change in input voltage:

$$Q_{CC}/V = \frac{1.0\text{mA}}{15\text{V}} = 55\ \mu\text{A/V} \quad (2-5)$$

$$L_r/V = \frac{35\text{mV}}{18\text{V}} \cong 2\ \text{mV/V} \quad (2-6)$$

The worst case change in the 200 mA output current for a 1.0V change in output or input voltage using equation 2-1 is:

$$\frac{\Delta I_{OUT}}{1.0\text{V}} = 55\ \mu\text{A} + \frac{2\text{mV}}{25\Omega} = 135\ \mu\text{A} \quad (2-7)$$

and the output impedance for a 0 to  $85\Omega$  change in  $Z_L$  using equation 2-4 is:

$$Z_{OUT} = \frac{1}{55\ \mu\text{A} + \frac{2\text{mV}}{25\Omega}} = 7.4\ \text{k}\Omega \quad (2-8)$$

Typical measured values of  $Z_{OUT}$  varied from 10 –  $12.3\ \text{k}\Omega$ , or 81 –  $100\ \mu\text{A/V}$  change input or output (approximately 0.05%/V).

## 3. HIGH CURRENT REGULATOR WITH SHORT CIRCUIT CURRENT LIMIT

The 15V regulator circuit of Figure 6 includes an external boost transistor to increase output current capability to 5.0A. Unlike the normal boosting methods, it maintains the LM340's ability to provide short circuit current limiting and thermal shut-down without use of additional active components. The extension of these safety features to the external pass transistor Q1 is based on a current sharing scheme using R1, R2, and D1. Assuming

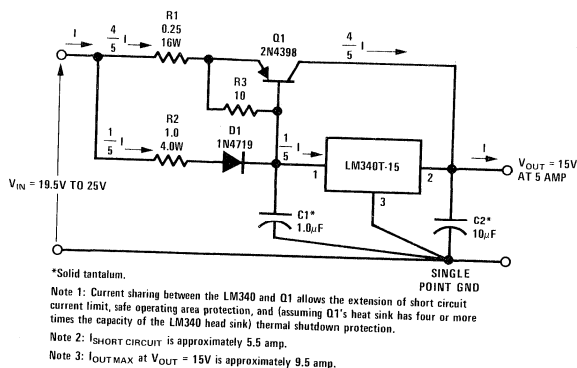


FIGURE 6. 15V 5.0A Regulator with Short Circuit Current Limit

the base-to-emitter voltage of Q1 and the voltage drop across D1 are equal, the voltage drops across R1 and R2 are equal. The currents through R1 and R2 will then be inversely proportional to their resistances. For the example shown on Figure 6, resistor R1 will have four times the current flow of R2. For reasonable values of Q1 beta, the current through R1 is approximately equal to the collector current of Q1; and the current through R2 is equal to the current flowing through the LM340. Therefore, under overload or short circuit conditions the protection circuitry of the LM340 will limit its own output current and, because of the R1/R2 current sharing scheme, the output current of Q1 as well. Thermal overload protection also extends Q1 when its heat sink has four or more times the capacity of the LM340 heat sink. This follows from the fact that both devices have approximately the same input/output voltage and share the load current in a ratio of four to one.

The circuit shown on Figure 6 normally operates at up to 5.0A of output current. This means up to 1.0A of current flows through the LM340 and up to 4.0A flows through Q1. For short term overload conditions the curve of Figure 7 shows the maximum instantaneous output current versus temperature for the boosted regulator. This curve reflects the approximately 2.0A current limit of the LM340 causing an 8.0A current limit in the pass

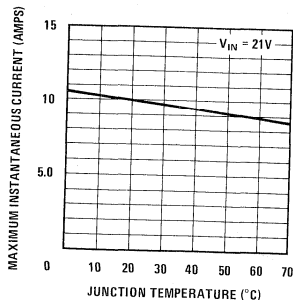


FIGURE 7. Maximum Instantaneous Current vs Junction Temperature

transistor, or 10A, total. Under continuous short circuit conditions the LM340 will heat up and limit to a steady total state short circuit current of 4.0A to 6.0A as shown in Figure 8. This curve was taken using a Wakefield 680-75 heat sink (approximately 7.5°C/W) at a 25°C ambient temperature.

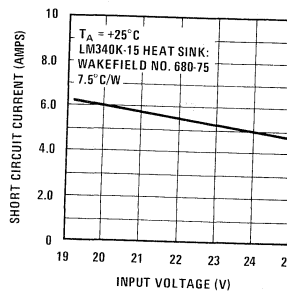


FIGURE 8. Continuous Short Circuit Current vs Input Voltage

For optimum current sharing over temperature between the LM340 and Q1, the diode D1 should be physically located close to the pass transistor on the heat sink in such a manner as to keep it at the same temperature as that of Q1. If the LM340 and Q1 are mounted on the same heat sink the LM340 should be electrically isolated from the heat sink since its case (pin 3) is at ground potential and the case of Q1 (its collector) is at the output potential of the regulator. Capacitors C1 and C2 are required to prevent oscillations and improve the output impedance respectively. Resistor R3 provides a path to unload excessive base charge from the base of Q1 when the regulator goes suddenly from full load to no load. The single point ground system shown on Figure 6 allows the sense pins (2 and 3) of the LM340 to monitor the voltage directly at the load rather than at some point along a (possibly) resistive ground return line carrying up to 5.0A of load current. Figure 9 shows the typical variation of load regulation versus load current for the boosted regulator. The insertion of the external pass transistor increases the input/output differential voltage from 2.0V to approximately 4.5V. For an

output current less than 5.0A, the R2/R1 ratio can be set lower than 4:1. Therefore, a less expensive PNP transistor may be used.

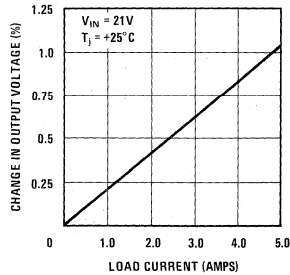


FIGURE 9. Load Regulation

#### 4. 5.0V, 5.0A VOLTAGE REGULATOR FOR TTL

The high current 5.0V regulator for TTL shown in Figure 10 uses a relatively inexpensive NPN pass transistor with a lower power PNP device to replace the single, higher cost, power PNP shown in Figure 6. This circuit provides a 5.0V output at up to 5.0A of load current with a typical load regulation of 1.8% from no load to full load. The peak instantaneous output current observed was 10.4A at a 25°C junction temperature (pulsed load with a 1.0 ms ON and a 200 ms OFF period) and 8.4A for a continuous short circuit. The typical line regulation is 0.02% of input voltage change ( $I_{OUT} = 0$ ).

One can easily add an overload indicator using the National's new NSL5027 LED. This is shown with dotted lines in Figure 10. With this configuration R2 is not only a current sharing resistor but also an overload sensor. R5 will determine the current through the LED; the diode D2 has been added to match the drop across D1. Once the load current exceeds 5.0A (1.0A through the LM340 assuming perfect current sharing and  $V_{D1} = V_{D2}$ ) Q3 turns ON and the overload indicator lights up.

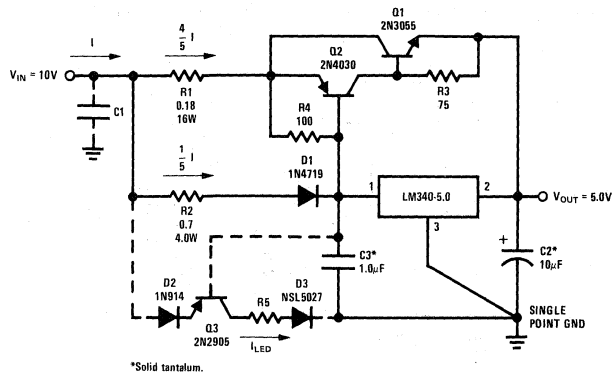


FIGURE 10. 5.0V, 5.0A Regulator for TTL (with short circuit, thermal shutdown protection, and overload indicator)

Example:

$$I_{OVERLOAD} = 5.0A$$

$$I_{LED} = 40 \text{ mA (light intensity of 16 mcd)}$$

$$V_{LED} = 1.75, R5 \approx \frac{V_{IN} - 2.65}{I_{LED}} \quad (4-1)$$

#### 5. ADJUSTABLE OUTPUT VOLTAGE REGULATOR FOR INTERMEDIATE OUTPUT VOLTAGES

The addition of two resistors to an LM340 circuit allows a non-standard output voltage while maintaining the limiting features built into IC. The example shown in Figure 11 provides a 10V output using an LM340K-5.0 by raising the reference (pin number 3) of the regulator by 5.0V.

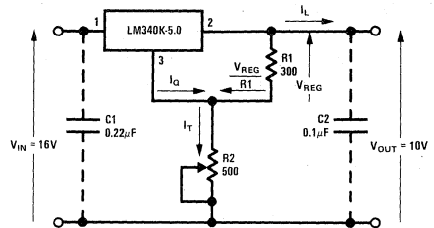


FIGURE 11. 10V Regulator

The 5.0V pedestal results from the sum of regulator quiescent current  $I_Q$  and a current equal to  $V_{REG}/R1$ , flowing through potentiometer R2 to ground. R2 is made adjustable to compensate for differences in  $I_Q$  and  $V_{REG}$  output. The circuit is practical because the change in  $I_Q$  due to line voltage and load current changes is quite small.

The line regulation for the boosted regulator is the sum of the LM340 line regulation, its effects on the current through R2, and the effects of

$\Delta I_Q$  in response to input voltage changes. The change in output voltage is:

$$\Delta V_{OUT} = (L_r/V) \Delta V_{IN} + \frac{(L_r/V) \Delta V_{IN} R_2}{R_1} + (Q_{CC}/V) \Delta V_{IN} R_2 \quad (5-1)$$

giving a total line regulation of:

$$\frac{\Delta V_{OUT}}{\Delta V_{IN}} = (L_r/V) \left(1 + \frac{R_2}{R_1}\right) + (Q_{CC}/V) R_2 \quad (5-2)$$

The LM340-5.0 data sheet lists  $\Delta V_{OUT} < 50$  mV and  $\Delta I_Q < 1.0$  mA for  $\Delta V_{IN} = 18$  V at  $I_{OUT} = 500$  mA. This is:

$$L_r/V = \frac{50 \text{ mV}}{18 \text{ V}} \approx 3 \text{ mV/V} \quad (5-3)$$

$$Q_{CC}/V = \frac{1.0 \text{ mA}}{18 \text{ V}} = 55 \text{ } \mu\text{A/V} \quad (5-4)$$

The worst case at line regulation for the circuit of Figure 11 calculated by equation 5-2,  $I_{OUT} = 500$  mA and  $R_2 = 310 \Omega$  is:

$$\frac{\Delta V_{OUT}}{1.0 \text{ V}} = 3 \text{ mV/V} \left(1 + \frac{310 \Omega}{300 \Omega}\right) + (55 \text{ } \mu\text{A/V}) 310 \Omega \quad (5-5)$$

$$\frac{\Delta V_{OUT}}{1.0 \text{ V}} = 6 \text{ mV/V} + 17 \text{ mV/V} = 23 \text{ mV/V} \quad (5-6)$$

This represents a worst case line regulation value of 0.23%/V.

The load regulation is the sum of the LM340 voltage regulation, its effect on the current through  $R_2$ , and the effect of  $\Delta I_Q$  in response to changes in load current. Using the following definitions and the notation shown on Figure 11  $\Delta V_{OUT}$  is:

$Z_{OUT}$  = Regulator output impedance: the change in output voltage per amp of load current change.

$Z_{340}$  = LM340 output impedance

$Q_{CC}/A$  = Quiescent current change per amp of load current change

$$\Delta V_{OUT} = (Z_{340}) \Delta I_L + \frac{(Z_{340}) \Delta I_L R_2}{R_1} + (Q_{CC}/A) \Delta I_L R_2 \quad (5-7)$$

and the total output impedance is:

$$Z_{OUT} = \frac{\Delta V_{OUT}}{\Delta I_L} = Z_{340} \left(1 + \frac{R_2}{R_1}\right) + (Q_{CC}/A) R_2 \quad (5-8)$$

The LM340-5.0 data sheet gives a maximum load regulation  $L_r = 50$  mV and  $\Delta I_Q = 1.0$  mA for a 1.0A load change.

$$Z_{340} = \frac{50 \text{ mV}}{1.0 \text{ A}} = 0.05 \Omega \quad (5-9)$$

$$Q_{CC}/A = \frac{1 \text{ mA}}{1.0 \text{ A}} = 100 \text{ } \mu\text{A/A} \quad (5-10)$$

This gives a worst case dc output impedance (ac output impedance being a function of C2) for the 10V regulator using equation 5-8 of:


$$Z_{OUT} = 0.05 \Omega \left(1 + \frac{310 \Omega}{300 \Omega}\right) + (100 \text{ } \mu\text{A/A}) 310 \Omega \quad (5-11)$$

$$Z_{OUT} = 0.10 \Omega + 0.031 \Omega = 0.13 \Omega$$

or a worst case change of approximately 1.5% for a 1.0A load change. Typical measured values are about one-third of the worst case value.
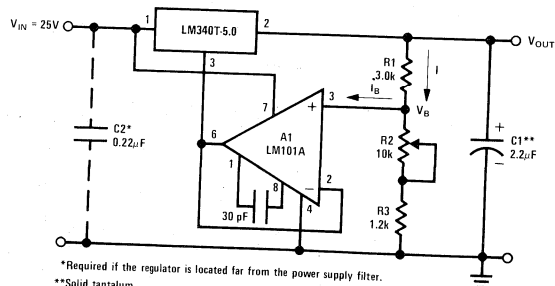
## 6. VARIABLE OUTPUT REGULATOR

In Figure 12 the ground terminal of the regulator is "lifted" by an amount equal to the voltage applied to the non-inverting input of the operational amplifier LM101A. The output voltage of the



\*Required if the regulator is located far from the power supply filter.  
\*\*Solid tantalum.

FIGURE 12. Variable Output Regulator

regulator is therefore raised to a level set by the value of the resistive divider R1, R2, R3 and limited by the input voltage. With the resistor values shown in Figure 12, the output voltage is variable from 7.0V to 23V and the maximum output current (pulsed load) varies from 1.2A to 2.0A ( $T_J = 25^\circ\text{C}$ ) as shown in Figure 13.

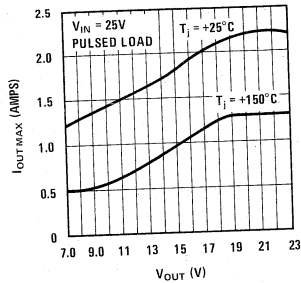


FIGURE 13. Maximum Output Current

Since the LM101A is operated with a single supply (the negative supply pin is grounded). The common mode voltage  $V_B$  must be at least at a  $2.0 V_{BE} + V_{SAT}$  above ground. R3 has been added to insure this when  $R2 = 0$ . Furthermore the bias current  $I_B$  of the operational amplifier should be negligible compared to the current flowing through the resistive divider.

Example:

$$V_{IN} = 25V$$

$$V_{OUTMIN} = 5 + V_B, (R2 = 0),$$

$$V_B = R3 (I - I_B) = 2.0V$$

$$R1 = 2.5 R3$$

$$V_{OUTMAX} = V_{IN} - \text{dropout volt.}$$

$$(R2 = R2_{MAX})$$

$$R2_{MAX} = 3.3 R1$$

So setting R3, the values of R1 and R2 can be determined.

If the LM324 is used instead of the LM101A, R3 can be omitted since its common mode voltage range includes the ground, and then the output will be adjustable from 5 to a certain upper value defined by the parameters of the system.

The circuit exhibits the short-circuit protection and thermal shutdown properties of the LM340 over the full output range.

The load regulation can be predicted as:

$$\Delta V_{OUT} = \frac{R1 + R2 + R3}{R1} \Delta V_{340} \quad (6-1)$$

where  $\Delta V_{340}$  is the load regulation of the device given in the data sheet. To insure that the regulator will start up under full load a reverse biased small signal germanium diode, 1N91, can be added between pins 2 and 3.

## 7. VARIABLE OUTPUT REGULATOR 0.5V - 29V

When a negative supply is available an approach equivalent to that outlined in section 6 may be used to lower the minimum output voltage of the regulator below the nominal voltage that of the LM340 regulator device. In Figure 14 the voltage  $V_G$  at the ground pin of the regulator is determined by the drop across R1 and the gain of the amplifier. The current I may be determined by the following relation:

$$I = \frac{V_{340}}{R1} \frac{R2 R5 - R3 R4}{R4 (R2 + R3)} + \frac{V_{IN}^-}{R1} \quad (7-1)$$

$$\text{or if } R2 + R3 = R4 + R5 = R$$

$$I = \frac{V_{340} R2}{R1 R4} + \frac{1}{R1} (V_{IN}^- - V_{340}) \quad (7-2)$$

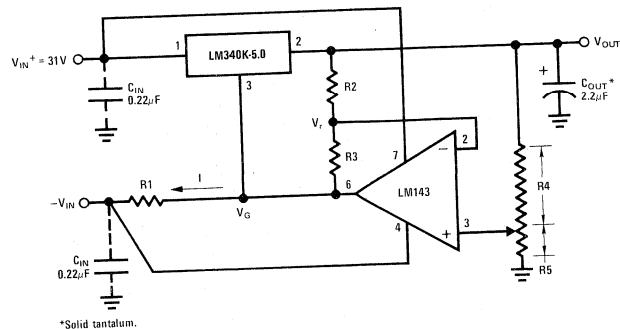


FIGURE 14. Variable Output Voltage 0.5V - 30V

considering that the output is given by:

$$V_{OUT} = V_G + V_{340} \quad (7-3)$$

and

$$V_G = R1 I - V_{IN}^- \quad (7-4)$$

combining 7-2, 7-3, 7-4 an expression for the output voltage is:

$$V_{OUT} = V_{340} \frac{R2}{R4} \quad (7-5)$$

Notice that the output voltage is inversely proportional to R4 so the output voltage may be adjusted very accurately for low values. A minimum output of 0.5V has been set. This implies that

$$\frac{R2}{R4} = 0.1 \quad \frac{R3}{R4} = 0.9 \quad \frac{R3}{R2} = 9 \quad (7-6)$$

An absolute zero output voltage will require  $R4 = \infty$  or  $R2 = 0$ , neither being practical in this circuit. The maximum output voltage as shown in Figure 14 is 30V if the high voltage operational amplifier LM143 is used. If only low values of  $V_{OUT}$  are sought, then an LM101 may be used. R1 can be computed from:

$$R1 = \frac{V_{IN}^-}{I_{Q340}} \quad (7-7)$$

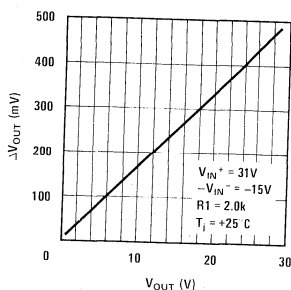


FIGURE 15. Typical Load Regulation for a 0.5V - 30V Regulator ( $\Delta I_{OUT} = 1.0A$ )

Figure 15 illustrates the load regulation as a function of the output voltage.


## 8. DUAL POWER SUPPLY

The plus and minus regulators shown in Figure 16 will exhibit line and load regulations consistent with their specifications as individual regulators. In fact, operation will be entirely normal until the problem of common loads occurs. A 30Ω load from the +15V output to the -15V output (representing a 0.5A starting load for the LM340K-15 if the LM320K-15 is already started) would allow start up of the LM340 in most cases. To insure LM340 startup over the full temperature range into a worst case 1.0A current sink load the germanium power "diode" D1 has been added to the circuit. Since the forward voltage drop of the germanium diode D1 is less than that of the silicon substrate diode of the LM340 the external diode will take any fault current and allow the LM340 to start up even into a negative voltage load. D1 and silicon diode D2 also protect the regulator outputs from inadvertent shorts between outputs and to ground. For shorts between outputs the voltage difference between either input and the opposite regulator output should not exceed the maximum rating of the device.

The example shown in Figure 16 is a symmetrical ±15V supply for linear circuits. The same principle applies to non-symmetrical supplies such as a +5.0V and -12V regulator for applications such as registers.
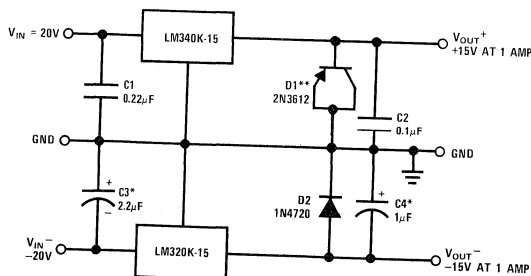
## 9. TRACKING DUAL REGULATORS

In Figure 17, a fraction of the negative output voltage "lifts" the ground pins of the negative LM320K-15 voltage regulator and the LM340K-15 through a voltage follower and an inverter respectively. The dual operational amplifier LM1558 is used for this application and since its supply voltage may go as high as ±22V the regulator outputs may be set between 5.0V and 20V. Because of the tighter output tolerance and the better drift of the LM320, the positive regulator



\*Solid tantalum.  
\*\*Germanium diode (using a PNP germanium transistor with the collector shorted to the emitter).  
Note: C1 and C2 required if regulators are located far from power supply filter.

FIGURE 16. Dual Power Supply



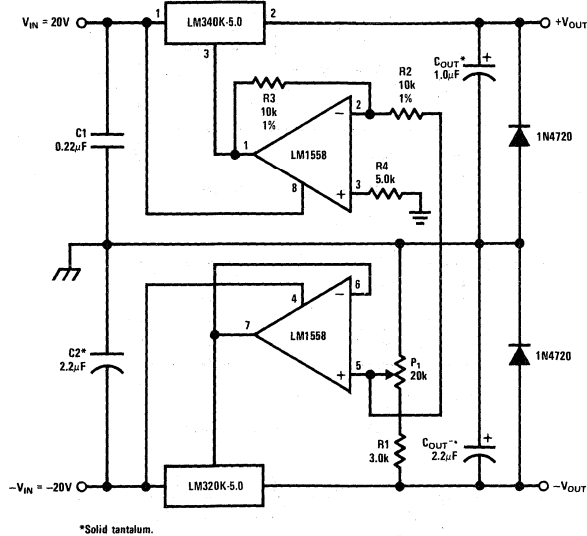


FIGURE 17. Tracking Dual Supply  $\pm 5.0V - \pm 18V$

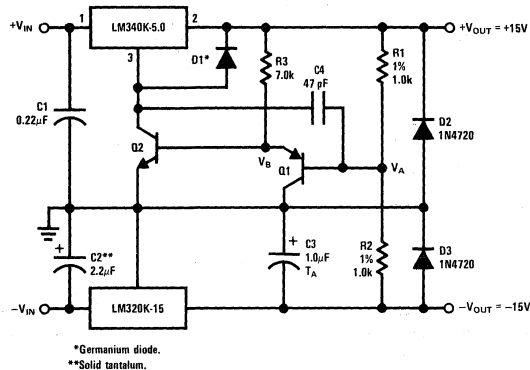


FIGURE 18. Tracking Dual Supply  $\pm 15V$

is made to track the negative. The best tracking action is achieved by matching the gain of both operational amplifiers, that is, the resistors R2 and R3 must be matched as closely as possible.

Indeed, with R2 and R3 matched to better than 1%, the LM340 tracks the LM320 within 40 – 50 mV over the entire output range. The typical load regulation at  $V_{OUT} = \pm 15V$  for the positive regulator is 40 mV from a 0 to 1.0A pulsed load and 80 mV for the negative.

Figure 18 illustrates  $\pm 15V$  tracking regulator, where again the positive regulator tracks the negative. Under steady state conditions  $V_A$  is at a virtual ground and  $V_B$  at a  $V_{BE}$  above ground. Q2 then conducts the quiescent current of the LM340. If  $-V_{OUT}$  becomes more negative the collector base junction of Q1 is forward biased thus lowering  $V_B$  and raising the collector voltage of Q2. As

a result  $+V_{OUT}$  rises and the voltage  $V_A$  again reaches ground potential.

Assuming Q1 and Q2 to be perfectly matched, the tracking action remains unchanged over the full operating temperature range.

With R1 and R2 matched to 1%, the positive regulator tracks the negative within 100 mV (less than 1%). The capacitor C4 has been added to improve stability. Typical load regulations for the positive and negative sides from a 0 to 1.0A pulsed load ( $t_{ON} = 1.0$  ms,  $t_{OFF} = 200$  ms) are 10 mV and 45 mV respectively.

## 10. HIGH INPUT VOLTAGE

The input voltage of the LM340 must be kept within the limits specified in the data sheet. If

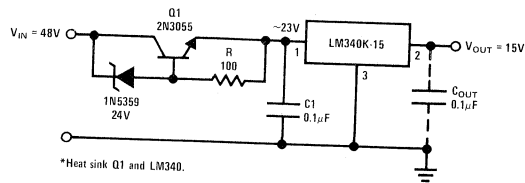


FIGURE 19. High Input Voltage

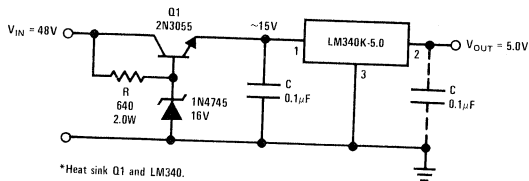


FIGURE 20. High Input Voltage

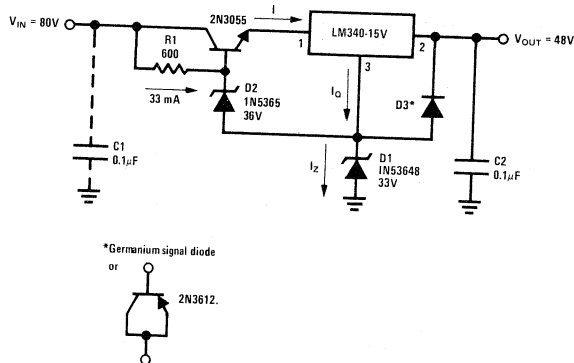


FIGURE 21. High Voltage Regulator

the device is operated above the absolute maximum input voltage rating, two failure modes may occur. With the output shorted to ground, the series pass transistor Q16 (see Figure 4) will go to avalanche breakdown; or, even with the output not grounded, the transistor Q1 may fail since it is operated with a collector-emitter voltage approximately 4.0V below the input.

If the only available supply runs at a voltage higher than the maximum specified, one of the simplest ways to protect the regulator is to connect a zener diode in series with the input of the device to level shift the input voltage. The drawback to this approach is obvious. The zener must dissipate  $(V_{SUPPLY} - V_{INMAX} \text{ LM340}) \cdot (I_{OUTMAX})$  which may be several watts. Another way to overcome the over voltage problem is illustrated in Figure 19 where an inexpensive, NPN-zener-resistor, combination may be considered as an equivalent to the power zener. The typical load regulation of this circuit is 40 mV from 0 to 1.0A pulsed load ( $T_j = 25^\circ\text{C}$ ) and the line regulation is 2.0 mV for 1.0V variation in the input voltage ( $I_{OUT} = 0$ ). A similar alternate approach is shown in Figure 20.

With an optional output capacitor the measured noise of the circuit was 700µVp-p.

## 11. HIGH VOLTAGE REGULATOR

In previous sections the principle of "lifting the ground terminal" of the LM340, using a resistor divider or an operational amplifier, has been illustrated. One can also raise the output voltage by using a zener diode connected to the ground pin as illustrated in the Figure 21 to obtain an output level increased by the breakdown voltage of the zener. Since the input voltage of the regulator has been allowed to go as high as 80V a level shifting transistor-zener (D2)-resistor combination has been added to keep the voltage across the LM340 under permissible values. The disadvantage of the system is the increased output noise and output voltage drift due to the added diodes.

Indeed it can be seen that, from no load to full load conditions, the  $\Delta I_Z$  will be approximately the current through R1 ( $\approx 35 \text{ mA}$ ) and therefore the degraded regulation caused by D1 will be  $V_Z$  (at  $35 \text{ mA} + I_Q$ ) -  $V_Z$  (at  $I_Q$ ).

The measured load regulation was 60 mV for  $\Delta I_{OUT}$  of 5.0 mA to 1.0A (pulsed load), and the line regulation is 0.01%/V of input voltage change ( $I_{OUT} = 500$  mA) and the typical output noise 2.0 mVp-p ( $C2 = 0.1\mu F$ ). The value of R1 is calculated as:

$$R1 \approx \beta \left[ \frac{V_{IN} - (V_{Z1} + V_{Z2})}{I_{full\ load}} \right] \quad (11-1)$$

## 12. ELECTRONIC SHUTDOWN

Figure 22 shows a practical method of shutting down the LM340 under the control of a TTL or DTL logic gate. The pass transistor Q1 operates either as a saturated transistor or as an open switch. With the logic input high (2.4V specified minimum for TTL logic) transistor Q2 turns on and pulls 50 mA down through R2. This provides sufficient base drive to maintain Q1 in saturation during the

ON condition of the switch. When the logic input is low (0.4V specified maximum for TTL logic) Q2 is held off, as is Q1; and the switch is in the OFF condition. The observed turn-on time was 7.0 $\mu s$  for resistive loads from 15 $\Omega$  to infinity and the turn-off time varied from approximately 3.0 $\mu s$  for a 15 $\Omega$  load to 3.0 ms for a no-load condition. Turn-off time is controlled primarily by the time constant of  $R_{LOAD}$  and C1.

## 13. VARIABLE HIGH VOLTAGE REGULATOR WITH OVERVOLTAGE SHUTDOWN

A high voltage variable-output regulator may be constructed using the LM340 after the idea illustrated in section 7 and drawn in Figure 23. The principal inconvenience is that the voltage across the regulator must be limited to maximum rating of the device, the higher the applied input voltage the higher must be lifted the ground pin of the LM340. Therefore the range of the variable


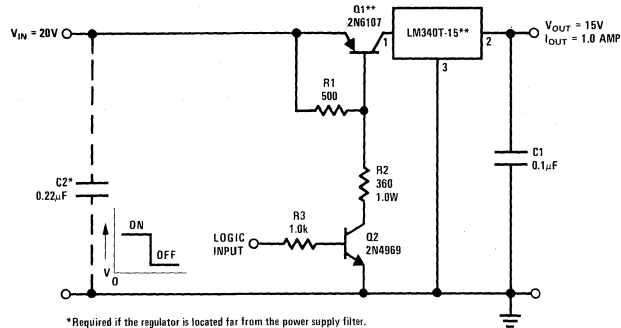


FIGURE 22. Electronic Shutdown Circuit

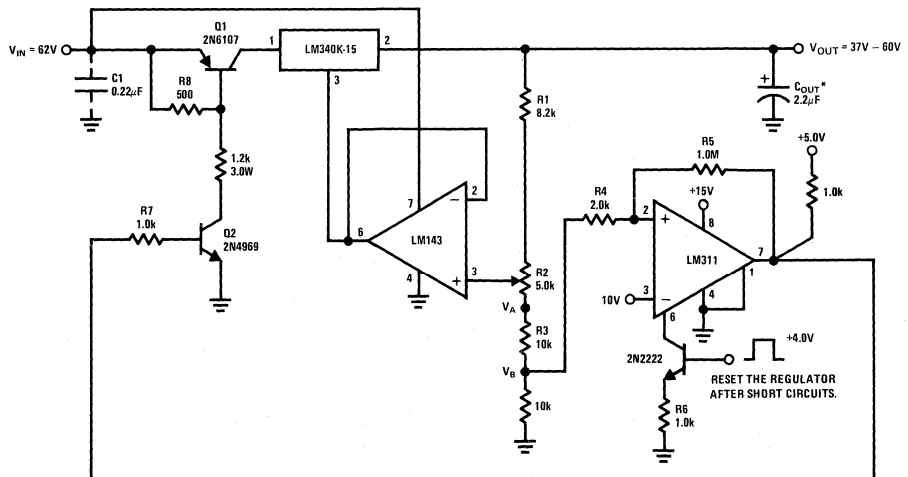

\*Solid tantalum.

FIGURE 23. Variable High Voltage Regulator with Shortcircuit and Overvoltage Protection

output is limited by the supply voltage limit of the operational amplifier and the maximum voltage allowed across the regulator. An estimation of this range is given by:

$$V_{OUTMAX} - V_{OUTMIN} = V_{SUPPLYMAX340} - V_{NOMINAL340} - 2.0V \quad (13-1)$$

Examples:

$$\begin{aligned} \text{LM340-15: } V_{OUTMAX} - V_{OUTMIN} \\ = 35 - 15 - 2 = 18V \end{aligned}$$

Figure 23 illustrates the above considerations. Even though the LM340 is by itself short circuit protected, when the output drops, also  $V_A$  drops and the voltage difference across the device increases. If it exceeds 35V the pass transistor internal to the regulator will breakdown, as explained in section 11. To remedy this, an over-

voltage shutdown is included in the circuit. When the output drops the comparator switches low, pulls down the base of Q2 thus opening the switch Q1, and shutting down the LM340. Once the short circuit has been removed the LM311 must be activated through the strobe to switch high and close Q1, which will start the regulator again. The additional voltages required to operate the comparator may be taken from the 62V since the LM311 has a certain ripple rejection and the reference voltage (pin 3) may have a superimposed small ac signal. The typical load regulation can be computed from equation 6-1.

#### BIBLIOGRAPHY

1. AN-42: *"IC Provides on Card Regulation for Logic Circuits."*
2. Carl T. Nelson: *"Power distribution and regulation can be simple, cheap and rugged."* EDN, February 20, 1973.

# Noise Specs Confusing?

National Semiconductor  
 Application Note 104  
 Jim Sherwin  
 May 1974



It's really all very simple—once you understand it. Then, here's the inside story on noise for those of us who haven't been designing low noise amplifiers for ten years.

You hear all sorts of terms like signal-to-noise ratio, noise figure, noise factor, noise voltage, noise current, noise power, noise spectral density, noise per root Hertz, broadband noise, spot noise, shot noise, flicker noise, excess noise, 1/F noise, fluctuation noise, thermal noise, white noise, pink noise, popcorn noise, bipolar spike noise, low noise, no noise, and loud noise. No wonder not everyone understands noise specifications.

In a case like noise, it is probably best to sort it all out from the beginning. So, in the beginning, there was noise; and then there was signal. The whole idea is to have the noise very small compared to the signal; or, conversely, we desire a high signal-to-noise ratio S/N. Now it happens that S/N is related to noise figure NF, noise factor F, noise power, noise voltage  $\bar{e}_n$ , and noise current  $\bar{i}_n$ . To simplify matters, it also happens that any noisy channel or amplifier can be completely specified for noise in terms of two noise generators  $\bar{e}_n$  and  $\bar{i}_n$  as shown in Figure 1.

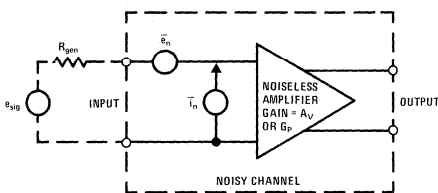


FIGURE 1. Noise Characterization of Amplifier

All we really need to understand are NF,  $\bar{e}_n$ , and  $\bar{i}_n$ . So here is a rundown on these three.

**NOISE VOLTAGE,  $\bar{e}_n$ ,** or more properly, EQUIVALENT SHORT-CIRCUIT INPUT RMS NOISE VOLTAGE is simply that noise voltage which would appear to originate at the input of the noiseless amplifier if the input terminals were shorted. It is expressed in nanovolts per root Hertz  $nV/\sqrt{Hz}$  at a specified frequency, or in microvolts in a given frequency band. It is determined or measured by shorting the input terminals, measuring the output rms noise, dividing by amplifier gain, and referencing to the input. Hence the term, equivalent noise voltage. An output bandpass filter of known characteristic is used in measurements, and the measured

value is divided by the square root of the bandwidth  $\sqrt{B}$  if data is to be expressed per unit bandwidth or per root Hertz. The level of  $\bar{e}_n$  is not constant over the frequency band; typically it increases at lower frequencies as shown in Figure 2. This increase is 1/f NOISE.

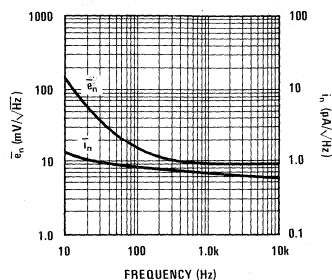


FIGURE 2. Noise Voltage and Current for an Op Amp

**NOISE CURRENT,  $\bar{i}_n$ ,** or more properly, EQUIVALENT OPEN-CIRCUIT RMS NOISE CURRENT is that noise which occurs apparently at the input of the noiseless amplifier due only to noise currents. It is expressed in picoamps per root Hertz  $pA/\sqrt{Hz}$  at a specified frequency or in nanoamps in a given frequency band. It is measured by shunting a capacitor or resistor across the input terminals such that the noise current will give rise to an additional noise voltage which is  $\bar{i}_n \times R_{in}$  (or  $X_{cin}$ ). The output is measured, divided by amplifier gain, referenced to input, and that contribution known to be due to  $\bar{e}_n$  and resistor noise is appropriately subtracted from the total measured noise. If a capacitor is used at the input, there is only  $\bar{e}_n$  and  $\bar{i}_n \times X_{cin}$ . The  $\bar{i}_n$  is measured with a bandpass filter and converted to  $pA/\sqrt{Hz}$  if appropriate; typically it increases at lower frequencies for op amps and bipolar transistors, but increases at higher frequencies for field-effect transistors.

**NOISE FIGURE, NF** is the logarithm of the ratio of input signal-to-noise and output signal-to-noise.

$$NF = 10 \log \frac{(S/N)_{in}}{(S/N)_{out}} \quad (1)$$

where: S and N are power or (voltage)<sup>2</sup> levels

This is measured by determining the S/N at the input with no amplifier present, and then dividing by the measured S/N at the output with signal source present.

The values of  $R_{gen}$  and any  $X_{gen}$  as well as frequency must be known to properly express NF in meaningful terms. This is because the amplifier  $\bar{i}_n \times Z_{gen}$  as well as  $R_{gen}$  itself produces input noise. The signal source in Figure 1 contains some noise. However  $e_{sig}$  is generally considered to be noise free and input noise is present as the THERMAL NOISE of the resistive component of the signal generator impedance  $R_{gen}$ . This thermal noise is WHITE in nature as it contains constant NOISE POWER DENSITY per unit bandwidth. It is easily seen from Equation 2 that the  $\overline{e_n^2}$  has the units  $V^2/Hz$  and that ( $\bar{e}_n$ ) has the units  $V/\sqrt{Hz}$

$$\overline{e_n^2} = 4kTRB \quad (2)$$

where: T is temperature in °K  
 R is resistor value in ohms  
 B is bandwidth in Hz  
 k is Boltzman's constant

### Relation Between $\bar{e}_n$ , $\bar{i}_n$ , $\mu F$

Now we can examine the relationship between  $\bar{e}_n$  and  $\bar{i}_n$  at the amplifier input. When the signal source is connected, the  $\bar{e}_n$  appears in series with the  $e_{sig}$  and  $\bar{e}_R$ . The  $\bar{i}_n$  flows through  $R_{gen}$  thus producing another noise voltage of value  $\bar{i}_n \times R_{gen}$ . This noise voltage is clearly dependent upon the value of  $R_{gen}$ . All of these noise voltages add at the input in rms fashion; that is, as the square root of the sum of the squares. Thus, neglecting possible correlation between  $\bar{e}_n$  and  $\bar{i}_n$ , the total input noise is

$$\overline{e_N^2} = \overline{e_n^2} + \overline{e_R^2} + \overline{i_n^2} R_{gen}^2 \quad (3)$$

Further examination of the NF equation shows the relationship of  $\bar{e}_N$ ,  $\bar{i}_n$ , and NF.

$$\begin{aligned} NF &= 10 \log \frac{S_{in} \times N_{out}}{S_{out} \times N_{in}} \\ &= 10 \log \frac{S_{in} G_p \overline{e_N^2}}{S_{in} G_p \overline{e_R^2}} \end{aligned}$$

where:  $G_p$  = power gain

$$\begin{aligned} &= 10 \log \frac{\overline{e_N^2}}{\overline{e_R^2}} \\ &= 10 \log \frac{\overline{e_n^2} + \overline{e_R^2} + \overline{i_n^2} R_{gen}^2}{\overline{e_R^2}} \\ NF &= 10 \log \left( 1 + \frac{\overline{e_n^2} + \overline{i_n^2} R_{gen}^2}{\overline{e_R^2}} \right) \quad (4) \end{aligned}$$

Thus, for small  $R_{gen}$ , noise voltage dominates; and for large  $R_{gen}$ , noise current becomes important. A clear advantage accrues to FET input amplifiers, especially at high values of  $R_{gen}$ , as the FET is essentially zero  $\bar{i}_n$ . Note, that for an NF value to have meaning, it must be accompanied by a value for  $R_{gen}$  as well as frequency.

### Calculating Total Noise, $\bar{e}_N$

We can generate a plot of  $\bar{e}_N$  for various values of  $R_{gen}$  if noise voltage and current are known vs frequency. Such a graph is shown in Figure 3 drawn from Figure 2. To make this plot, the thermal noise  $\bar{e}_R$  of the input resistance must be calculated from Equation 2 or taken from the graph of Figure 4. Remember that each term in Equation 3 must be squared prior to addition, so the data from Figure 4 and from Figure 2 is squared. A sample of this calculation follows.

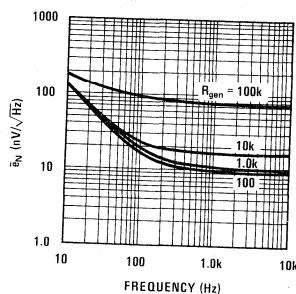


FIGURE 3. Total Noise for the Op Amp of Figure 2.

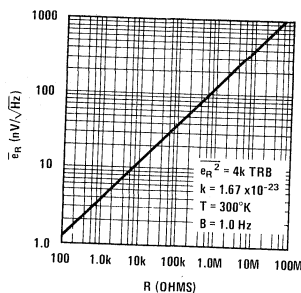


FIGURE 4. Thermal Noise of Resistor

Example 1: Determine total equivalent input noise per unit bandwidth for an amplifier operating at 1 kHz from a source resistance of 10 kohms. Use the data from Figures 2 and 4.

1. Read  $\bar{e}_R$  from Figure 4 at 10 kohm; the value is  $12 \text{ nV}/\sqrt{\text{Hz}}$ .
2. Read  $\bar{e}_n$  from Figure 2 at 1 kHz; the value is  $9.5 \text{ nV}/\sqrt{\text{Hz}}$ .
3. Read  $\bar{i}_n$  from Figure 2 at 1 kHz; the value is  $0.68 \text{ pA}/\sqrt{\text{Hz}}$ . Multiply by 10 kohm to obtain  $6.8 \text{ nV}/\sqrt{\text{Hz}}$ .

4. Square each term individually, and enter into Equation 3.

$$\begin{aligned}\bar{e}_N &= \sqrt{e_n^2 + e_R^2 + i_n^2 R_{gen}^2} \\ &= \sqrt{9.5^2 + 12^2 + 6.8^2} = \sqrt{279} \\ \bar{e}_N &= 16.7 \text{ nV}/\sqrt{\text{Hz}}\end{aligned}$$

This is total rms noise at the input in one Hertz bandwidth at 1 kHz. If total noise in a given bandwidth is desired, one must integrate the noise over a bandwidth as specified. This is most easily done in a noise measurement set-up, but may be approximated as follows.

1. If the frequency range of interest is in the flat band; i.e., between 1 kHz and 10 kHz in Figure 2, it is simply a matter of multiplying  $\bar{e}_N$  by the square root of the bandwidth. Then, in the 1 kHz-10 kHz band, total noise is

$$\begin{aligned}\bar{e}_N &= 16.7 \sqrt{9000} \\ &= 1.59 \mu\text{V}\end{aligned}$$

2. If the frequency band of interest is not in the flat band of Figure 2, one must break the band into sections, calculating average noise in each section, squaring, multiplying by section bandwidth, summing all sections, and finally taking square root of the sum as follows:

$$\bar{e}_N = \sqrt{e_R^2 B + \sum_1^i (e_n^2 + i_n^2 R_{gen}^2) B_i} \quad (5)$$

where:  $i$  is the total number of sub-blocks.

For most purposes a sub-block may be one or two octaves. Example 2 details such a calculation.

Example 2: Determine the rms noise level in the frequency band 50 Hz to 10 kHz for the amplifier of Figure 2 operating from  $R_{gen} = 2\text{k}$ .

TABLE I. Noise Calculations for Example 2

B (Hz)	$\Delta f$ (Hz)	$\bar{e}_n^2$ (nV/Hz)	+ $i_n^2 R_{gen}^2$	SUM x $\Delta f$	= (nV <sup>2</sup> )
50-100	50	(20) <sup>2</sup> = 400	(8.7 x 2.0k) <sup>2</sup> = 302	702 x 50	35,000
100-300	200	(13) <sup>2</sup> = 169	(8 x 2.0k) <sup>2</sup> = 256	425 x 200	85,000
300-1000	700	(10) <sup>2</sup> = 100	(7 x 2.0k) <sup>2</sup> = 196	296 x 700	207,000
1.0k-10k	9000	(9) <sup>2</sup> = 81	(6 x 2.0k) <sup>2</sup> = 144	225 x 9000	2,020,000
50-10,000	9950	$\bar{e}_R^2 = (5.3)^2 = 28$		28 x 9950	279,000
Total $\bar{e}_N = \sqrt{2,626,000} = 1620 \text{ nV} = 1.62 \mu\text{V}$					

\*The units are as follows:  $(20 \text{ nV}/\sqrt{\text{Hz}})^2 = 400 \text{ (nV)}^2/\text{Hz}$   
 $(8.7 \mu\text{A}/\sqrt{\text{Hz}} \times 2.0\text{kohms})^2 = (17.4 \text{ nA}/\sqrt{\text{Hz}})^2 = 302 \text{ (nV)}^2/\text{Hz}$   
 Sum =  $702 \text{ (nV)}^2/\text{Hz} \times 50 \text{ Hz} = 35,000 \text{ (nV)}^2$

1. Read  $\bar{e}_R$  from Figure 4 at 2k, square the value, and multiply by the entire bandwidth. Easiest way is to construct a table as shown below.
2. Read the median value of  $\bar{e}_n$  in a relatively small frequency band, say 50 Hz-100 Hz, from Figure 2, square it and enter into the table.
3. Read the median value of  $i_n$  in the 50 Hz-100 Hz band from Figure 2, multiply by  $R_{gen} = 2\text{k}$ , square the result and enter in the table.
4. Sum the squared results from steps 2 and 3, multiply the sum by  $\Delta f = 100-50 = 50 \text{ Hz}$ , and enter in the table.
5. Repeat steps 2-4 for band sections of 100 Hz-300 Hz, 300 Hz-1000 Hz and 1 kHz-10 kHz. Enter results in the table.
6. Sum all entries in the last column, and finally take the square root of this sum for the total rms noise in the 50 Hz-10,000 Hz band.
7. Total  $\bar{e}_N$  is 1.62  $\mu\text{V}$  in the 50 Hz-10,000 Hz band.

#### Calculating S/N and NF

Signal-to-noise ratio can be easily calculated from known signal levels once total rms noise in the band is determined. Example 3 shows this rather simple calculation from Equation 6 for the data of Example 2.

$$S/N = 20 \log \frac{e_{sig}}{\bar{e}_N} \quad (6)$$

Example 3: Determine S/N for an rms  $e_{sig} = 4 \text{ mV}$  at the input to the amplifier operated in Example 2.

1. RMS signal is  $e_{sig} = 4 \text{ mV}$
2. RMS noise from Example 2 is 1.62  $\mu\text{V}$
3. Calculate S/N from Equation 6

$$\begin{aligned}S/N &= 20 \log \frac{4 \text{ mV}}{1.62 \mu\text{V}} \\ &= 20 \log (2.47 \times 10^3) \\ &= 20 (\log 10^3 + \log 2.47) \\ &= 20 (3 + 0.393) \\ S/N &= 68 \text{ dB}\end{aligned}$$

It is also possible to plot NF vs frequency at various  $R_{gen}$  for any given plot of  $\bar{e}_n$  and  $\bar{i}_n$ . However there is no specific all-purpose conversion plot relating NF,  $\bar{e}_n$ ,  $\bar{i}_n$ ,  $R_{gen}$  and  $f$ . If either  $\bar{e}_n$  or  $\bar{i}_n$  is neglected, a reference chart can be constructed. Figure 5 is such a plot when only  $\bar{e}_n$  is considered. It is useful for most op amps when  $R_{gen}$  is less than about 200 ohms and for FETs at any  $R_{gen}$  (because there is no significant  $\bar{i}_n$  for FETs), however actual NF for op amps with  $R_{gen} > 200$  ohms is higher than indicated on the chart.

The graph of Figure 5 can be used to find spot NF if  $\bar{e}_n$  and  $R_{gen}$  are known, or to find  $\bar{e}_n$  if NF and  $R_{gen}$  are known. It can also be used to find max  $R_{gen}$  allowed for a given max NF when  $\bar{e}_n$  is known. In any case, values are only valid if  $\bar{i}_n$  is negligible and at the specific frequency of interest for NF and  $\bar{e}_n$ , and for 1 Hz bandwidth. If bandwidth increases, the plot is valid so long as  $\bar{e}_n$  is multiplied by  $\sqrt{B}$ .

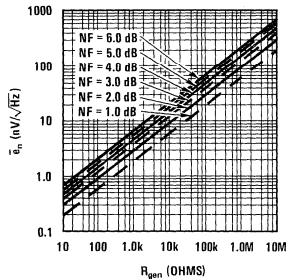


FIGURE 5. Spot NF vs  $R_{gen}$  when Considering Only  $\bar{e}_n$  and  $\bar{e}_R$  (not valid when  $\bar{i}_n R_{gen}$  is significant)

### The Noise Figure Myth

Noise figure is easy to calculate because the signal level need not be specified (note that  $e_{sig}$  drops out of Equation 4). Because NF is so easy to handle in calculations, many designers tend to lose sight of the fact that signal-to-noise ratio  $(S/N)_{out}$  is what is important in the final analysis, be it an audio, video, or digital data system. One can, in fact, choose a high  $R_{gen}$  to reduce NF to near zero if  $\bar{i}_n$  is very small. In this case  $\bar{e}_R$  is the major source of noise, overshadowing  $\bar{e}_n$  completely. The result is very low NF, but very low S/N as well because of very high noise. Don't be fooled into believing that low NF means low noise *per se!*

Another term is worth considering, that is optimum source resistance  $R_{OPT}$ . This is a value of  $R_{gen}$  which produces the lowest NF in a given system. It is calculated as

$$R_{OPT} = \frac{\bar{e}_n}{\bar{i}_n} \quad (7)$$

This has been arrived at by differentiating Equation 4 with respect to  $R_{gen}$  and equating it to zero (see Appendix). *Note that this does not mean lowest noise.*

For example, using Figure 2 to calculate  $R_{OPT}$  at say 600 Hz,

$$R_{OPT} = \frac{10 \text{ nV}}{0.7 \text{ pA}} = 14 \text{ kohms}$$

Then note in Figure 3, that  $\bar{e}_N$  is in the neighborhood of 20 nV/ $\sqrt{\text{Hz}}$  for  $R_{gen}$  of 14k. While  $\bar{e}_N = 10 \text{ nV}/\sqrt{\text{Hz}}$  for  $R_{gen} = 0\text{-}100$  ohms. STOP! Do not pass GO. Do not be fooled. Using  $R_{gen} = R_{OPT}$  does not guarantee lowest noise UNLESS  $e_{sig}^2 = kR_{gen}$  as in the case of transformer coupling. When  $e_{sig}^2 > kR_{gen}$ , as is the case where signal level is proportional to  $R_{gen}$  ( $e_{sig} = kR_{gen}$ ), it makes sense to use the highest practical value of  $R_{gen}$ . When  $e_{sig}^2 < kR_{gen}$ , it makes sense to use a value of  $R_{gen} < R_{OPT}$ . These conclusions are verified in the Appendix.

This all means that it does not make sense to tamper with the  $R_{gen}$  of existing signal sources in an attempt to make  $R_{gen} = R_{OPT}$ . Especially, do not add series resistance to a source for this purpose. It does make sense to adjust  $R_{gen}$  in transformer coupled circuits by manipulating turns ratio or to design  $R_{gen}$  of a magnetic pick-up to operate with pre-amps where  $R_{OPT}$  is known. It does make sense to increase the design resistance of signal sources to match or exceed  $R_{OPT}$  so long as the signal voltage increases with  $R_{gen}$  in at least the ratio  $e_{sig}^2 \propto R_{gen}$ . It does not necessarily make sense to select an amplifier with  $R_{OPT}$  to match  $R_{gen}$  because one amplifier operating at  $R_{gen} = R_{OPT}$  may produce lower S/N than another (quieter) amplifier operating with  $R_{gen} \neq R_{OPT}$ .

With some amplifiers it is possible to adjust  $R_{OPT}$  over a limited range by adjusting the first stage operating current (the National LM121 and LM381 for example). With these, one might increase operating current, varying  $R_{OPT}$ , to find a condition of minimum S/N. Increasing input stage current decreases  $R_{OPT}$  as  $\bar{e}_n$  is decreased and  $\bar{i}_n$  is simultaneously increased.

Let us consider one additional case of a fairly complex nature just as a practical example which will point up some factors often overlooked.

Example 4: Determine the S/N *apparent to the ear* of the amplifier of Figure 2 operating over 50-12, 800 Hz when driven by a phonograph cartridge exhibiting  $R_{gen} = 1350\Omega$ ,  $L_{gen} = 0.5\text{H}$ , and average  $e_{sig} = 4.0 \text{ mVrms}$ . The cartridge is to be loaded by 47k as in Figure 6. This is equivalent to using a Shure V15, Type 3 for average level recorded music.

1. Choose sectional bandwidths of 1 octave each, these are listed in the following table.
2. Read  $\bar{e}_n$  from Figure 2 as average for each octave and enter in the table.
3. Read  $\bar{i}_n$  from Figure 2 as average for each octave and enter in the table.
4. Read  $\bar{e}_R$  for the  $R_{gen} = 1350\Omega$  from Figure 4 and enter in the table.



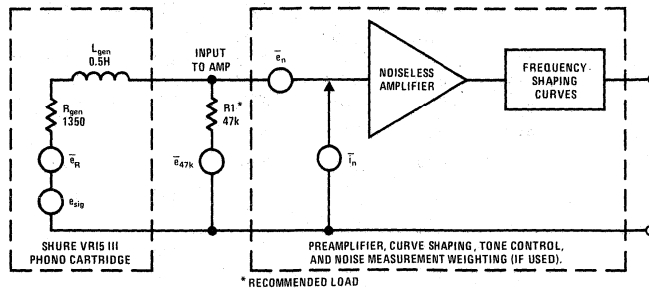


FIGURE 6. Phono Preamp Noise Sources

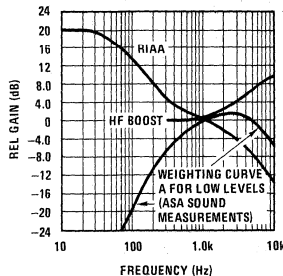


FIGURE 7. Relative Gain for RIAA, ASA Weighting A, and H-F Boost Curves

5. Determine the values of  $Z_{gen}$  at the midpoint of each octave and enter in the table.
6. Determine the amount of  $\bar{e}_R$  which reaches the amplifier input; this is

$$\bar{e}_R \frac{R1}{R1 + Z_{gen}}$$

7. Read the noise contribution  $\bar{e}_{47k}$  of  $R1 = 47k$  from Figure 4.
8. Determine the amount of  $\bar{e}_{47k}$  which reaches the amplifier input; this is

$$\bar{e}_{47k} \frac{Z_{gen}}{R1 + Z_{gen}}$$

9. Determine the effective noise contributed by  $\bar{i}_n$  flowing through the parallel combination of  $R1$  and  $Z_{gen}$ . This is

$$\bar{i}_n \frac{Z_{gen}R1}{Z_{gen} + R1}$$

10. Square all noise voltage values resulting from steps 2, 6, 8 and 9; and sum the squares.
11. Determine the relative gain at the midpoint of each octave from the RIAA playback response curve of Figure 7.
12. Determine the relative gain at these same midpoints from the A weighted response curve of Figure 7 for sound level meters (this roughly accounts for variations in human hearing).
13. Assume a tone control high frequency boost of 10 dB at 10 kHz from Figure 7. Again determine relative response of octave midpoints.
14. Multiply all relative gain values of steps 11-13 and square the result.
15. Multiply the sum of the squared values from step 10 by the resultant relative gain of step 14 and by the bandwidth in each octave.
16. Sum all the values resultant from step 15, and find the square root of the sum. This is the total audible rms noise apparent in the band.
17. Divide  $e_{sig} = 4$  mV by the total noise to find  $S/N = 69.5$  dB.

## Steps for Example

1	Frequency Band (Hz)	50-100	100-200	200-400	400-800	800-1600	1.6-3.2k	3.2-6.4k	6.4-12.8k
	Bandwidth, B (Hz)	50	100	200	400	800	1600	3200	6400
	Bandcenter, f (Hz)	75	150	300	600	1200	2400	4800	9600
5	$Z_{gen}$ at f (ohms)	1355	1425	1665	2400	4220	8100	16k	32k
	$Z_{gen}$ R1 (ohms)	1300	1360	1600	2270	3900	6900	11.9k	19k
	$Z_{gen}/(R1 + Z_{gen})$	0.028	0.030	0.034	0.485	0.082	0.145	0.255	0.400
	$R1/(R1 + Z_{gen})$	0.97	0.97	0.97	0.95	0.92	0.86	0.74	0.60
11	RIAA Gain, $A_{RIAA}$	5.6	3.1	2.0	1.4	1	0.7	0.45	0.316
12	Corr for Hearing, $A_A$	0.08	0.18	0.45	0.80	1	1.26	1	0.5
13	H-F Boost, $A_{boost}$	1	1	1	1	1.12	1.46	2.3	3.1
14	Product of Gains, $A$	0.45	0.55	0.9	1.12	1.12	1.28	1.03	0.49
	$A^2$	0.204	0.304	0.81	1.26	1.26	1.65	1.06	0.241
4	$\bar{e}_R$ (nV/ $\sqrt{Hz}$ )	4.5	4.5	4.5	4.5	4.5	4.5	4.5	4.5
7	$\bar{e}_{47k}$ (nV/ $\sqrt{Hz}$ )	29	29	29	29	29	29	29	29
3	$\bar{i}_n$ (pA/ $\sqrt{Hz}$ )	0.85	0.80	0.77	0.72	0.65	0.62	0.60	0.60
2	$\bar{e}_n$ (nV/ $\sqrt{Hz}$ )	19	14	11	10	9.5	9	9	9
9	$\bar{e}_1 = \bar{i}_n (Z_{gen} R1)$	1.1	1.09	1.23	1.63	2.55	4.3	7.1	11.4
6	$\bar{e}_2 = \bar{e}_R R1/(R1 + Z_{gen})$	4.35	4.35	4.35	4.25	4.15	3.86	3.33	2.7
8	$\bar{e}_3 = \bar{e}_{47k} Z_{gen}/(R1 + Z_{gen})$	0.81	0.87	0.98	1.4	2.4	4.2	7.4	11.6
10	$\bar{e}_n^2$	360	195	121	100	90	81	81	81
	$\bar{e}_1^2$ (from $\bar{i}_n$ )	1.21	1.2	1.5	2.65	6.5	18.5	50	150
	$\bar{e}_2^2$ (from $\bar{e}_R$ )	19	19	19	18	17	15	11	7.2
	$\bar{e}_3^2$ (from $\bar{e}_{47k}$ )	0.65	0.76	0.96	2	5.8	18	55	135
	$\Sigma \bar{e}_n^2$ (nV <sup>2</sup> /Hz)	381	216	142	122	120	133	147	373
15	$BA^2$ (Hz)	10.2	30.4	162	504	1010	2640	3400	1550
	$BA^2 \Sigma \bar{e}_n^2$ (nV <sup>2</sup> )	3880	6550	23000	61500	121000	350000	670000	580000
16	$\Sigma (\bar{e}_{n1}^2 + \bar{e}_{n1}^2 + \bar{e}_{n2}^2 + \bar{e}_{n3}^2) B_1 A_1^2 = 1,815,930$ nV <sup>2</sup>								
	$\bar{e}_N = \sqrt{\Sigma} = 1.35\mu V$								
17	$S/N = 20 \log (4.0 \text{ mV}/1.35\mu V) = 69.5$ dB								

Note the significant contributions of  $\bar{i}_n$  and the 47k resistor, especially at high frequencies. Note also that there will be a difference between calculated noise and that noise measured on broadband meters because of the A curve employed in the example. If it were not for the A curve attenuation at low frequencies, the  $\bar{e}_n$  would add a very important contribution below 200 Hz. This would be due to the RIAA boost at low frequency. As it stands, 97% of the 1.35 $\mu$ V would occur in the 800-12.8 kHz band alone, principally because of the high frequency boost and the A measurement curve. If the measurement were made without either the high frequency boost or the A curve, the  $\bar{e}_n$  would be 1.25 $\mu$ V. In this case, 76% of the total noise would arise in the 50 Hz-400 Hz band alone. If the A curve were used, but the high-frequency boost were deleted,  $\bar{e}_n$  would be 0.91 $\mu$ V; and 94% would arise in the 800-12, 800 Hz band alone.

The three different methods of measuring would only produce a difference of +3.5 dB in overall S/N, however the prime sources of the largest part of the noise and the frequency character of the noise can vary greatly with the test or measurement conditions. It is, then, quite important to know the method of measurement in order

to know which individual noise sources in Figure 6 must be reduced in order to significantly improve S/N.

## CONCLUSIONS

The main points in selecting low noise preamplifiers are:

1. Don't pad the signal source; live with the existing  $R_{gen}$ .
2. Select on the basis of low values of  $\bar{e}_n$  and especially  $\bar{i}_n$  if  $R_{gen}$  is over about a thousand ohms.
3. Don't select on the basis of NF or  $R_{OPT}$  in most cases. NF specs are all right so long as you know precisely how to use them and so long as they are valid over the frequency band for the  $R_{gen}$  or  $Z_{gen}$  with which you must work.
4. Be sure to (root) sum all the noise sources  $\bar{e}_n$ ,  $\bar{i}_n$  and  $\bar{e}_R$  in your system over appropriate bandwidth.
5. The higher frequencies are often the most important unless there is low frequency boost or high frequency attenuation in the system.
6. Don't forget the filtering effect of the human ear in audio systems. Know the eventual frequency emphasis or filtering to be employed.

## APPENDIX I

Derivation of  $R_{OPT}$ :

$$NF = 10 \log \frac{\overline{e_R^2} + \overline{e_n^2} + \overline{i_n^2} R_{gen}^2}{\overline{e_R^2}}$$

$$10 \log \left( 1 + \frac{\overline{e_n^2} + \overline{i_n^2} R_{gen}^2}{\overline{e_R^2}} \right)$$

$$\frac{\partial NF}{\partial R} = \frac{0.435}{(4kTRB)^2} \frac{4kTRB(2R\overline{i_n^2}) - (\overline{e_n^2} + \overline{i_n^2} R^2)4kTB}{1 + (\overline{e_n^2} + \overline{i_n^2} R^2)/4kTRB}$$

where:  $R = R_{gen}$

Set this = 0, and

$$4kTRB(2R\overline{i_n^2}) = 4kTB(\overline{e_n^2} + \overline{i_n^2} R^2)$$

$$2\overline{i_n^2} R^2 = \overline{e_n^2} + \overline{i_n^2} R^2$$

$$\overline{i_n^2} R^2 = \overline{e_n^2}$$

$$R^2 = \overline{e_n^2} / \overline{i_n^2}$$

$$R_{OPT} = \frac{\overline{e_n}}{\overline{i_n}}$$

## APPENDIX II

Selecting  $R_{gen}$  for highest S/N.

$$S/N = \frac{e_{sig}^2}{B(\overline{e_R^2} + \overline{e_n^2} + \overline{i_n^2} R^2)}$$

For S/N to increase with R,

$$\frac{\partial S/N}{\partial R} > 0$$

$$\frac{\partial S/N}{\partial R} = \frac{2e_{sig}(\partial e_{sig}/\partial R)(\overline{e_R^2} + \overline{e_n^2} + \overline{i_n^2} R^2) - e_{sig}^2(4kT + 2\overline{i_n^2} R)}{B(\overline{e_R^2} + \overline{e_n^2} + \overline{i_n^2} R^2)^2}$$

APPENDIX II (Con't)

If we set  $> 0$ , then

$$2 (\partial e_{\text{sig}}/\partial R) (\overline{e_R^2} + \overline{e_n^2} + \overline{i_n^2} R^2) > e_{\text{sig}} (4kT + 2\overline{i_n^2} R)$$

For  $e_{\text{sig}} = k_1 \sqrt{R}$ ,  $\partial e_{\text{sig}}/\partial R = \frac{k_1}{2\sqrt{R}}$

$$(2k_1/2\sqrt{R}) (\overline{e_R^2} + \overline{e_n^2} + \overline{i_n^2} R^2) > k_1 \sqrt{R} (4kT + 2\overline{i_n^2} R)$$

$$\overline{e_R^2} + \overline{e_n^2} + \overline{i_n^2} R^2 > 4kTR + 2\overline{i_n^2} R^2$$

$$\overline{e_n^2} > \overline{i_n^2} R^2$$

$$R < \overline{e_n}/\overline{i_n}$$

Therefore S/N increases with  $R_{\text{gen}}$  so long as  $R_{\text{gen}} \leq R_{\text{OPT}}$

For  $e_{\text{sig}} = k_1 R$ ,  $\partial e_{\text{sig}}/\partial R = k_1$

$$2k_1 (\overline{e_R^2} + \overline{e_n^2} + \overline{i_n^2} R^2) > k_1 R (4kT + 2\overline{i_n^2} R)$$

$$2\overline{e_R^2} + 2\overline{e_n^2} + 2\overline{i_n^2} R^2 > 4kTR + 2\overline{i_n^2} R^2$$

$$\overline{e_R^2} + 2\overline{e_n^2} > 0$$

Then S/N increases with  $R_{\text{gen}}$  for any amplifier.

For any  $e_{\text{sig}} < k_1 \sqrt{R}$ , an optimum  $R_{\text{gen}}$  may be determined. Take, for example,  $e_{\text{sig}} = k_1 R^{0.4}$ ,  $\partial e_{\text{sig}}/\partial R = 0.4k_1 R^{-0.6}$

$$(0.8k_1/R^{0.6})(\overline{e_R^2} + \overline{e_n^2} + \overline{i_n^2} R^2) > k_1 R^{0.4} (4kT + 2\overline{i_n^2} R)$$

$$0.8 \overline{e_R^2} + 0.8 \overline{e_n^2} + 0.8 \overline{i_n^2} R^2 > 4kTR + 2 \overline{i_n^2} R^2$$

$$0.8 \overline{e_n^2} > 0.2 \overline{e_R^2} + 1.2 \overline{i_n^2} R^2$$

Then S/N increases with  $R_{\text{gen}}$  until

$$0.25 \overline{e_R^2} + 1.5 \overline{i_n^2} R^2 = \overline{e_n^2}$$

## Fast IC Power Transistor with Thermal Protection

National Semiconductor  
Application Note 110  
Robert C. Dobkin  
May 1974



### INTRODUCTION

Overload protection is perhaps most necessary in power circuitry. This is shown by recent trends in power transistor technology. Safe-area, voltage and current handling capability have been increased to limits far in excess of package power dissipation. In RF transistors, devices are now available and able to withstand badly mismatched loads without destruction. However, for anyone working with power transistors, they are still easily destroyed.

Since power circuitry, in many cases, drives other low level circuitry—such as a voltage regulator—protection is doubly important. Overloads that cause power transistor failure can result in the destruction of the entire circuit. This is because the common failure mode for power transistors is a short from collector to emitter—applying full voltage to the load. In the case of a voltage regulator, the raw supply voltage would be applied to the low level circuitry.

A new monolithic power transistor provides virtually absolute protection against any type of overload. Included on the chip are current limiting, safe area protection and thermal limiting. Current limiting controls the peak current through the chip to a safe level below the fusing current of the aluminum metallization. At high collector to emitter voltage the safe area limiting reduces the peak current to further protect the power transistor. If, under prolonged overload, power dissipation causes chip temperature to rise toward destructive levels, thermal limiting turns off the device keeping the devices at a safe temperature. The inclusion of thermal limiting, a feature not easily available in discrete circuitry makes this device especially attractive in applications where normal protective schemes are ineffective.

The device's high gain and fast response further reduce requirements of surrounding circuitry. As well as being used in linear applications, the IC can interface transistor-transistor logic or complementary-MOS logic to power loads without external devices. In fact, the input-current requirement of 3 microamperes is small enough for one CMOS gate to drive over 400 LM195's.

Besides high dc current gain, the IC has low input capacitance so it can be easily driven from high impedance sources—even at high frequencies. In a standard TO-3 power package, the monolithic structure ties the emitter, rather than the collector, to the case effectively bootstrapping the base-to-package capacitance. Additionally, connecting the emitter to the package is especially convenient for grounded emitter circuits.

The device is fully protected against any overload condition when it is used below the maximum voltage rating. The current-limiting circuitry restricts the power dissipation to 35 watts, 1.8 amperes are available at collector-to-emitter voltage of 17V decreasing to about 0.8

amperes at 40V. In reality, however, like standard transistors, power dissipation in actual use is limited by the size of the external heat sink.

Switching time is fast also. At 40V 25 Ohm load can be switched on or off in a relatively fast 500 ns. The internal planar double diffused monolithic transistors have an  $f_T$  of 200 MHz to 400 MHz. The limiting factor on overall speed is the protective and biasing circuitry around the output transistors. An important performance point is that no more than the normal 3 $\mu$ A base current is needed for fast switching.

To the designer, the LM195 acts like an ordinary power transistor, and its operation is almost identical to that of a standard power device. However, it provides almost absolute protection against any type of overload. And, since it is manufactured with standard seven-mask IC technology, the device is producible in large quantities at reasonable cost.

### CIRCUIT DESIGN

Besides the protective features, the monolithic power transistor should function as closely to a discrete transistor as possible. Of course, due to the circuitry on the chip, there will be some differences.

Figure 1 shows a simplified schematic of the power transistor. A power NPN Darlington is driven by an input PNP. The PNP and output NPN's are biased by internal current source  $I_1$ . The composite three transistors yield a total current gain in excess of  $10^6$  making it easy to drive the power transistors from high impedance sources. Unlike normal power transistors, the base current is negative, flowing out of the PNP. However, in most cases this is not a problem.

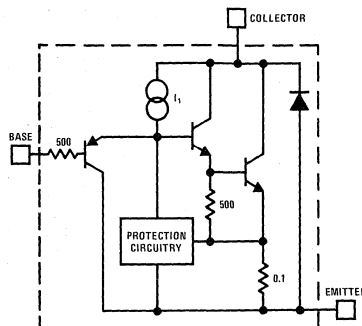


FIGURE 1. Simplified Circuit of the LM195

The input PNP transistor is made with standard IC processing and has a reverse base-emitter breakdown voltage in excess of 40V. This allows the power transistor to be driven from a stiff voltage source without damage due to excessive base current. At input voltages in excess of about 1V the input PNP becomes reverse biased and no current is drawn from the base lead. In fact it is possible for the base of the monolithic transistor to be driven with up to 40V even though the collector to emitter voltage is low. Further, the input PNP isolates the base drive from the protective circuitry insuring that even with high base drive the device will be protected. When the device is turned off current  $I_1$  is shunted from the base of the NPN transistor by the PNP and appears at the emitter terminal. This sets the minimum load current to about 2 mA, not a severe restriction for a power transistor. Because of the PNP and  $I_1$ , the power transistor turns "on" rather than "off" if the base is opened; however, most power circuits already include a base-emitter resistor to absorb leakage currents in present power transistors.

A schematic of the LM195 is shown in *Figure 2*. The circuitry is biased by four current sources comprised of Q4, Q7, Q8 and Q9. The operating current is set by Q5 and Q6 and is relatively independent of supply voltage. FET Q1 and R2 insure reliable starting of the bias circuitry while D1 clamps the output of the FET limiting the starting current at high supply voltage.

The output transistors Q19 and Q20 are driven from input PNP Q14. Current limiting independent of temperature changes is provided by Q21, Q16, and Q15. At high collector to emitter voltages the current limit decreases due to the voltage across R21 from D3, D4 and R20. The double emitter structure used on Q21 allows the power limiting to more closely approximate

constant power curve rather than a straight line decrease in output current as input voltage increases.

Transistor Q13 thermally limits the device by removing the base drive at high temperature. The actual temperature sensing is done by Q11 and Q12 with Q10 regulating the voltage across the sensors so thermal limit temperature remains independent of supply. As temperature increases, the collector current of Q11 increases while the  $V_{BE}$  of Q12 decreases. At about 170°C the Q12 turns on Q13 removing the base drive from the output transistors. Finally, C1, Q2 and Q3 boost operating currents during switching to obtain faster response time and Q17 and Q18 compensate for  $h_{fe}$  variations in the power devices.

### PERFORMANCE

The new power transistor is packaged in a standard TO-3 transistor package making it compatible with standard power transistors. An added advantage of the monolithic structure is that the emitter is tied to the case rather than the collector. This allows the device to be connected directly to ground in collector output applications.

A photomicrograph of the LM195 is shown in *Figure 3*. More than half of the die area is needed for the output power transistor (Q20). Actually, the power transistor is many individual small transistors connected in parallel with a common collector. Partitioning the power device into small discrete areas improves power handling over a single large device. Firstly, the power device has ten base sections spread across the chip. Between the base diffusion are N+ collector contacts. Each section has its own emitter ballasting resistor to insure current sharing between sections. One of these resistors is used to sense the output current for current limiting.

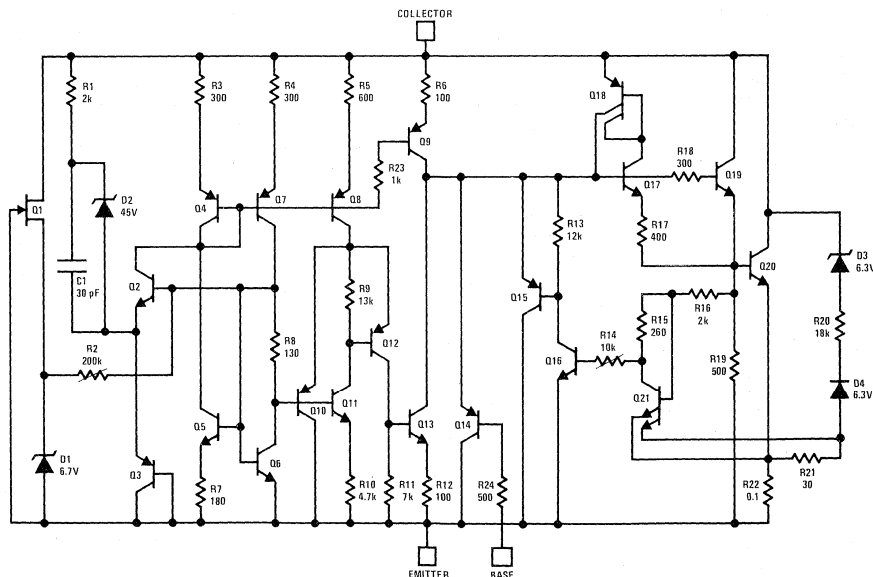


FIGURE 2. Schematic Diagram of the LM195

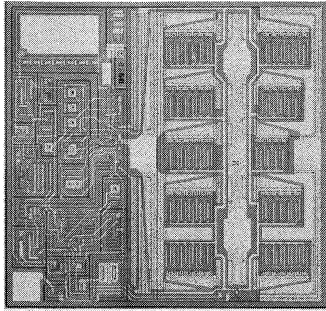


FIGURE 3. LM195 Chip

TABLE I. Typical Performance

Collector to Emitter Voltage	42V
Base to Emitter Voltage (max.)	42V
Peak Collector Current (internally limited)	1.8 amps
Reverse Base Emitter Voltage	20V
Base to Emitter Voltage ( $I_C = 1.0$ amp)	0.9V
Base Current	$3\mu A$
Saturation Voltage	2V
Switching Time (turn on or turn off)	500 ns
Power Dissipation (internally limited)	35 watts
Thermal Limit Temperature	$165^\circ C$
Maximum Operating Temperature	$150^\circ C$
Thermal Resistance (Junction to Case)	$2.3^\circ C/W$

A detail of one of the base sections is shown in *Figure 4*. An interdigitated structure is used with alternating base contacts and emitter stripes. Integrated into each emitter is an individual emitter ballasting resistor to insure equal current sharing between emitters in each section. Aluminum metalization runs the length of the emitter stripe to prevent lateral voltage drop from debiasing a section of the stripe at high operating currents. All current in the stripe flows out through the small ballasting resistor where it is summed with the currents from the

other stripes in the section. The partitioning in conjunction with the emitter resistor gives a power transistor with large safe-area and good power handling capability.

## APPLICATIONS

With the full protection and high gain offered by this monolithic power transistor, circuit design is considerably simplified. The inclusion of thermal limiting, not normally available in discrete design allows the use of smaller heat sinks than with conventional protection circuitry. Further, circuits where protection of the power device is difficult—if not impossible—now cause no problems.

For example, with only current limiting, the power transistor heat sink must be designed to dissipate worst case overload power dissipation at maximum ambient temperature. When the power transistor is thermally limited, only normal power need be dissipated by the heat sink. During overload, the device is allowed to heat up and thermally limit, drastically reducing the size of the heat sink needed.

Switching circuits such as lamp drivers, solenoid drivers or switching regulators do not dissipate much power during normal operation and usually no heat sink is necessary. However, during overload, the full supply voltage times the maximum output current must be dissipated. Without a large heat sink standard power transistors are quickly destroyed.

Using this new device is easier than standard power transistors but a few precautions should be observed. About the only way the device can be destroyed is excessive collector to emitter voltage or improper power supply polarity. Sometimes when used as an emitter follower, low level high frequency oscillations can occur. These are easily cured inserting a 5k-10k resistor in series with the base lead. The resistor will eliminate the oscillation without effecting speed or performance. Good power supply bypassing should also be used since this is a high frequency device.

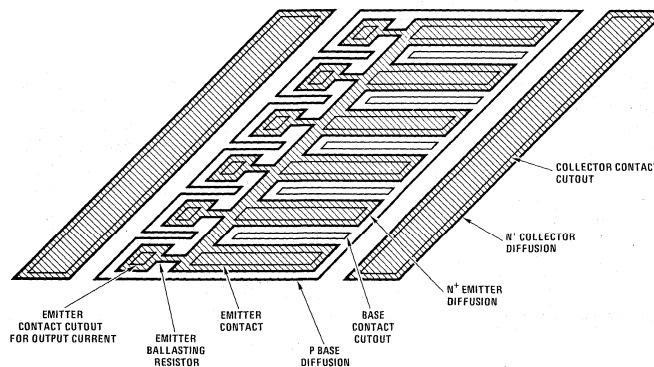


FIGURE 4. Detailed Structure of one Section of the Power Transistor

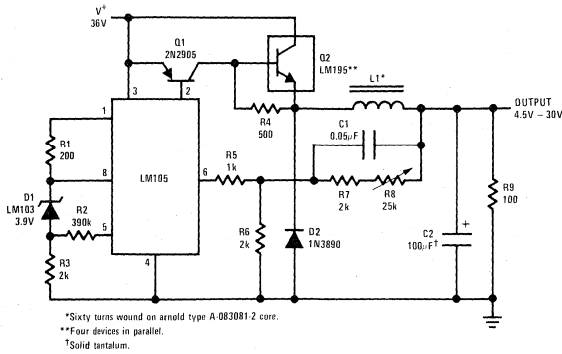


FIGURE 5. 6 Amp Variable Output Switching Regulator

Figure 5 shows a 6 amp, variable output switching regulator for general purpose applications. An LM105 positive regulator is used as the amplifier-reference for the switching regulator. Positive feedback to induce switching is obtained from the LM105 at pin 1 through an LM103 diode. The positive feedback is applied to the internal amplifier at pin 5 and is independent of supply voltage. This forces the LM105 to drive the pass devices either "on" or "off," rather than linearly controlling their conduction. Negative feedback, delayed by L1 and the output capacitor, C2, causes the regulator to switch with the duty cycle automatically adjusting to provide a constant output. Four LM195's are used in parallel to obtain a 6 amp output since each device can only supply about 2 amps. Note that no ballasting resistors are needed for current sharing. When Q1 turns "on" all bases are pulled up to  $V^+$  and no base current flows in the LM195 transistors since the input PNP's are reverse biased.

A two terminal current/power limiter is shown in Figure 6. The base and collector are shorted—turning the power transistor on. If the load current exceeds 2 amps, the device current limits protecting the load. If the overload remains on, the device will thermal limit, further protecting itself and the load. In normal operation, only 2V appear across the device so high efficiency is realized and no heat sink is needed. Another method of protection would be to place the monolithic power transistor on a common heat sink with the devices to be protected. Overheating will then cause the LM195 to thermal limit protecting the rest of the circuitry.

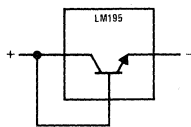


FIGURE 6. Two Terminal Current Limiter

The low base current make this power device suitable for many unique applications. Figure 7 shows a time delay

circuit. Upon application of power or S1 closing, the load is energized. Capacitor C1 slowly charges toward  $V^-$  through R1. When the voltage across R1 decreases below about 0.8 volts the load is de-energized. Long delays can be obtained with small capacitor values since a high resistance can be used.

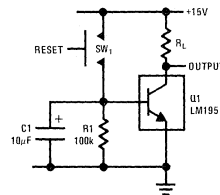


FIGURE 7. Time Delay Circuit

Figure 8 and 9 show how the LM195 can be used with standard IC's to make positive or negative voltage regulators. Since the current gain of the LM195 is so high, both regulators have better than 2 mV load regulation. They are both fully overload protected and will operate with only 2V input-to-output voltage differential.

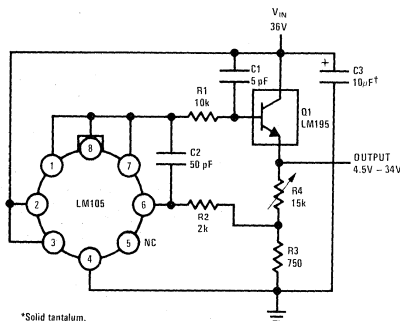


FIGURE 8. 1 Amp Positive Voltage Regulator



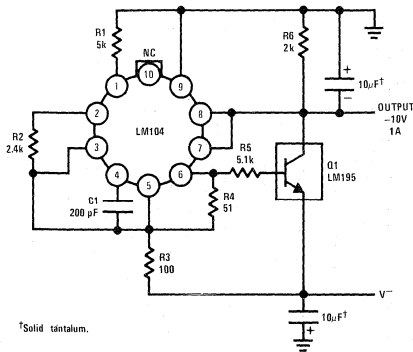


FIGURE 9. 1 Amp Negative Regulator

An optically isolated power transistor is shown in *Figure 10*. D1 and D2 are almost any standard optical isolator. With no drive, R1 absorbs the base current of Q1 holding it off. When power is applied to the LED, D2 allows current to flow from the collector to base. Less than 20µA from the diode is needed to turn the LM195 fully on.

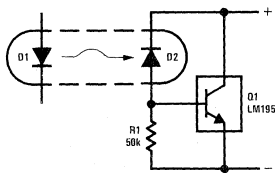


FIGURE 10. Optically Isolated Power Transistor

An alternate connection for better ac response is to return the cathode of D2 to separate positive supply rather than the collector of Q1, as shown in *Figure 11*, eliminating the added collector to base capacitance of the diode. With this circuit a 40V 1 amp load can be switched in 500 ns. Of course, any photosensitive diode can be used instead of the opto-isolator to make a light activated switch.

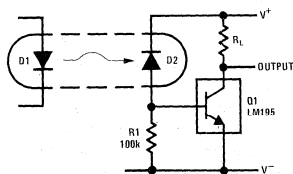


FIGURE 11. Fast Optically Isolated Switch

A power lamp flasher is shown in *Figure 12*. It is designed to flash a 12V bulb at about a once-per-second rate. The reverse base current of Q2 provides biasing for Q1 eliminating the need for a resistor. Typically, a cold bulb can draw 8 times its normal operating current.

Since the LM195 is current limited, high peak currents to the bulb are not experienced during turn-on. This prolongs bulb life as well as easing the load on the power supply.


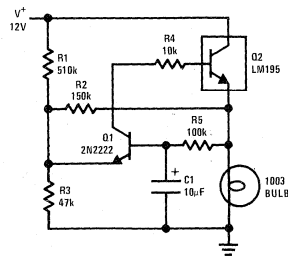


FIGURE 12. 1 Amp Lamp Flasher

Since no PNP equivalent of this device is available, it is advantageous to use the LM195 in a quasi-complementary configuration to simulate a power PNP. *Figure 13* shows a quasi PNP made with an LM195. A low current PNP is used to drive the LM195 as the power output device. Resistor R1 protects against overdrive destroying the PNP and, in conjunction with C1, frequency compensates the loop against oscillations. Resistor R2 sets the operating current for the PNP and limits the collector current.

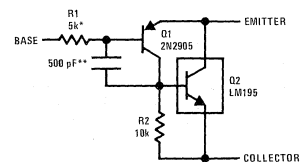

\*Protects against excessive base drive.  
\*\*Needed for stability.

FIGURE 13. PNP Configuration for LM195

*Figure 14* shows a power op amp with a quasi-complementary power output stage. Q1 and Q2 form the equivalent of a power PNP. The circuit is simply an op amp with a power output stage. As shown, the circuit is stable for almost any load. Better bandwidth can be obtained by decreasing C1 to 15 pF (to obtain 150 kHz full output response), but capacitive loads can cause oscillation. If due to layout, the quasi-complementary loop oscillates, collector to base capacitance on Q1 will stabilize it. A simpler power op amp for up to 300 Hz operation is shown in *Figure 15*.

One of the more difficult circuit types to protect is a current regulator. Since the current is already fixed, normal protection doesn't work. Circuits to limit the voltage across the current regulator may allow excessive current to flow through the load. About the only protection method that protects both the regulator and the driven circuit is thermal limiting.

A 100 mA, two terminal regulator is shown in *Figure 16*. The circuit has low temperature coefficient and operates

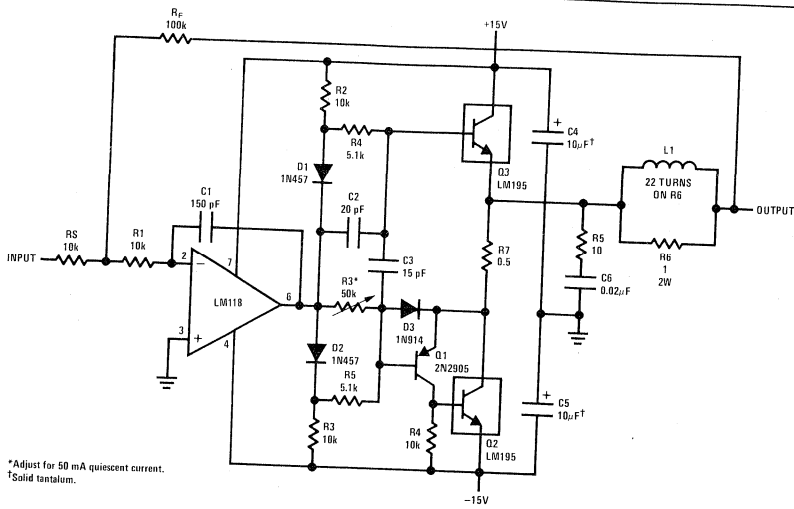


FIGURE 14. Power Op Amp

\*Adjust for 50 mA quiescent current.  
 †Solid tantalum.

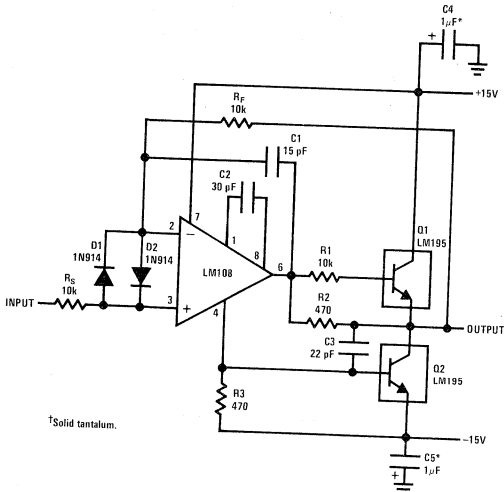


FIGURE 15. 1 Amp Voltage Follower

†Solid tantalum.

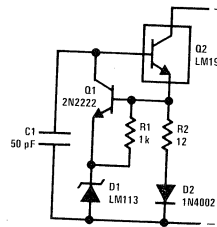


FIGURE 16. Two Terminal 100 mA Current Regulator

down to 3V. Once again, the reverse base current of the LM195 to bias the operating circuitry.

A 2N2222 is used to control the voltage across a current sensing resistor, R2 and diode D1, and therefore the current through it. The voltage across the sense network is the  $V_{BE}$  of the 2N2222 plus 1.2V from the LM113. In the sense network R2 sets the current while D1 compensates for the  $V_{BE}$  of the transistor. Resistor R1 sets the current through the LM113 to 0.6 mA.

## CONCLUSIONS

A new IC power transistor has been developed that significantly improves power circuitry reliability. The device is virtually impossible to destroy through abuse. Further it has high gain and fast response. It is manufactured with standard seven mask IC technology making it produceable in large quantities at reasonable prices. Finally, in addition to the protection features, it has high gain simplifying surrounding circuitry.

# Wide Range Function Generator

National Semiconductor  
Application Note 115  
Robert C. Dobkin  
July 1974



The sine, square, triangle function generator has proven to be exceptionally useful. Various IC circuits have been published for generating square and triangle waveforms in an attempt to duplicate the general purpose function generator. However, these simple circuits are usually limited to about 10 kHz and have no sine wave output. The function generator shown here provides all three waveforms and operates from below 10 Hz to 1 MHz with usable output to about 2 MHz.


## DESIGN

As with most function generators, an integrator-comparator generates the square and triangle waveforms with a shaping circuit forming the triangle wave into a sine wave.

Obtaining six decades of operating with a single control plus 2 MHz operation requires some unusual circuit

design techniques as well as good high frequency IC's. The triangle wave is generated by switching current-source transistors to alternately charge and discharge the timing capacitor. This generates a linear tri-wave without the use of an op amp integrator. A FET voltage follower buffers the tri-wave and drives the comparator, output amplifier and sine converter.

A precision dual comparator is used to set the peak-to-peak amplitude of the tri-wave. It is necessary to accurately control the tri-wave since the sine converter requires close amplitude control to produce a low distortion output. An accurate divider across the 5V supply regulators sets the threshold at the inputs of the LM319 comparators. The tri-wave is applied to the other comparator inputs through another divider—R8, R9, R10 and C2. The comparator switches when the amplitude of the tri-wave is  $\pm 2.5V$ . Capacitor C2 compensates for delays in the comparator at high frequencies.

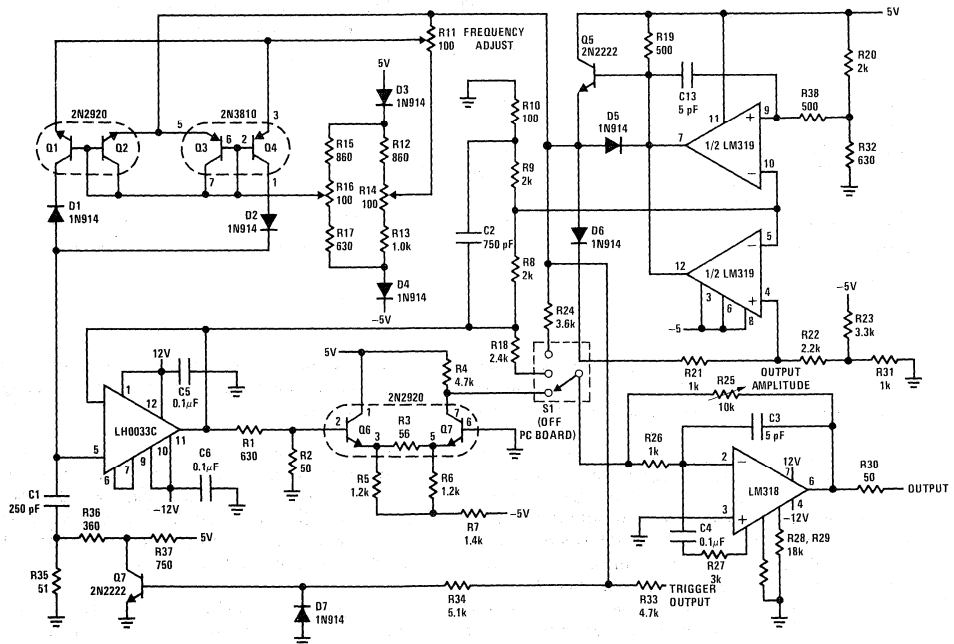

Function Generator Schematic

## PARTS LIST

R1	630Ω	1%		C1	250 pF	
R2	50Ω	1%		C2	750 pF	
R3	56Ω	5%		C3	5 pF	
R4	4.7k	5%		C4	0.1μF	
R5	1.2k	1%		C5	0.1μF	
R6	1.2k	1%		C6	0.1μF	
R7	1.4k	1%		C7	500μF	25V
R8	2k	5%		C8	500μF	25V
R9	2k	5%		C9	4.7μF	Solid Tantalum
R10	100Ω	5%		C10	4.7μF	Solid Tantalum
R11	100Ω potentiometer			C11	4.7μF	Solid Tantalum
R12	860Ω	5%		C12	4.7μF	Solid Tantalum
R13	1k	5%		C13	5 pF	
R14	100Ω PC mount trimpot					
R15	860Ω	5%				
R16	100Ω PC mount trimpot			Q1-Q2	2N2920	Dual NPN
R17	630Ω	5%		Q3-Q4	2N3810	Dual PNP
R18	2.4k	5%		Q5	2N2222	
R19	500Ω	5%		Q6-Q7	2N2920	Dual NPN
R20	2k	5%		Q8	2N2222	
R21	1k	5%				
R22	2.2k	5%		D1-D7	1N914	
R23	3.3k	5%				
R24	3.6k	5%		1-Varo VE27	Full Wave Bridge	
R25	10k potentiometer			1-LM318H	Operational Amplifier	
R26	1k	5%		1-LM319N	Dual Comparator	
R27	3k	5%		1-LH0033C	Fast Buffer	
R28	18k	5%		1-LM340K	12V Positive Voltage Regulator	
R29	18k	5%		1-LM320K	-12V Negative Voltage Regulator	
R30	50Ω	5%		1-LM309H	5V Positive Voltage Regulator	
R31	1k	5%		1-LM320H	-5V Negative Voltage Regulator	
R32	630Ω	5%				
R33	4.7k	5%		T1	= Triad F90X	
R34	5.1k	5%				
R35	51Ω	5%		S <sub>1</sub>	-3 Position ST Switch	
R36	360Ω	5%		S <sub>2</sub>	-SPST Switch	
R37	750Ω	5%				
R38	500Ω	5%				
						1/4 Amp Fuse and Holder—PC Board, Mounting Hardware, etc.

A square wave output from the comparator is obtained at the emitter of Q5 and is used to drive both the current switches and output amplifier. The current switches—Q1, Q2, Q3, Q4—provide a 5 nA to 5 mA current to timing capacitor, C1. The exponential relationship between emitter-base voltage and collector current allows a six decade current range to be obtained with a single potentiometer. The maximum output current is set by the current through R15 or R17 (depending on polarity) and appears when the arm of the frequency control, R11, ties all four emitters together. As R11 is rotated, a voltage is developed between the emitters of Q1-Q4 and Q2-Q3. This voltage decreases the emitter base voltage of Q1 and Q4 decreasing their operating current. About 380 mV is developed across R11 and corresponds to over a 10<sup>6</sup> reduction in charging current.

Converting the tri-wave to a sine wave also uses the non-linear relationship between emitter-base voltage and collector current of a transistor pair.

Transistors Q6 and Q7 form a differential amplifier with emitter degeneration. The tri-wave is attenuated by R1 and R2 to about 450 mV and applied to one half of the pair—Q6. This drives the transistors non-linearly producing a sine wave output current at the collector of Q7 to drive the output amplifier.

The output amp, an LM318, uses feedforward compensation to maximize bandwidth and slew rate. It is used for adjustable scaling of all three waveforms to ±10V. Even with the feedforward, there is not quite enough bandwidth for good reproduction of the triangle or

square wave at frequencies over 1 MHz. Therefore, if the higher frequencies are of major interest, a faster output amplifier is necessary.


### CONSTRUCTION AND SET UP

It is important to observe good construction practices for proper operation. All four power supplies should be bypassed with  $4.7\mu\text{F}$  solid tantalum capacitors on the circuit board. Since the circuit operates at relatively high frequencies, short leads and a compact layout is a good idea. The wiring to the function selector switch should be made with shielded wire to minimize spikes from the fast square wave. At low frequencies, charging currents to the timing capacitor are quite low, so 60 Hz pickup can modulate the operating frequency. Shielding the current sources and C1 from the power transformer is in order.


All transistors used to set the timing currents must track with temperature changes. Of course, the individual pairs will track but the NPN pair must also track the PNP pair as well. There are many small heat sinks for transistors which can be used to thermally couple Q1, Q2, to Q3, Q4. Temperature differences between the pair will cause the symmetry to change.

Set up is not difficult either. Firstly, R11 is set for a 1 MHz output. Then R16 is used to adjust the output symmetry. Secondly, R11 is set to provide a 10 Hz output and the symmetry is again adjusted by R14.

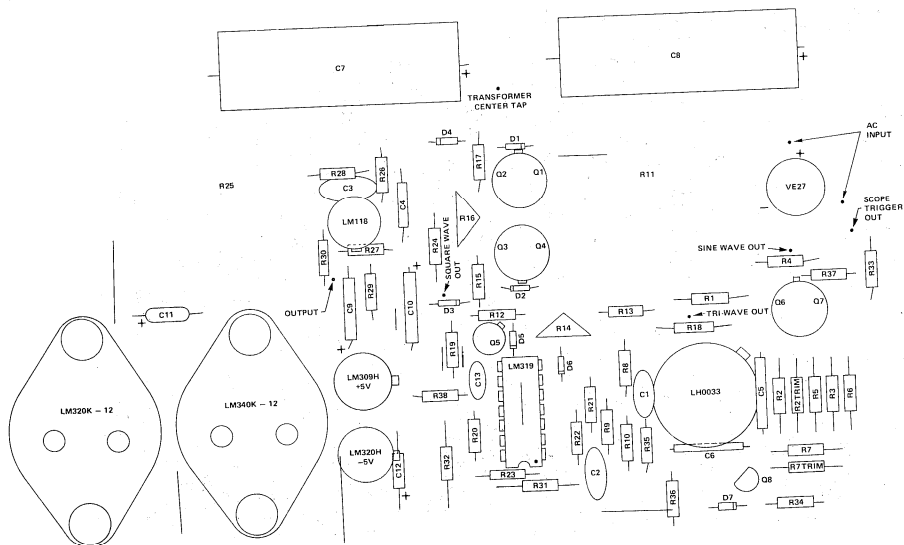
Other possible adjustments that may be necessary are in the sine converter. R7 can be trimmed if the sine output (from the LM318) has a dc offset. Also, it may be necessary to adjust R2 to minimize distortion. (It should be mentioned that there can be considerable distortion if the symmetry of the tri-wave is not 50%.)



Component Location, Top View

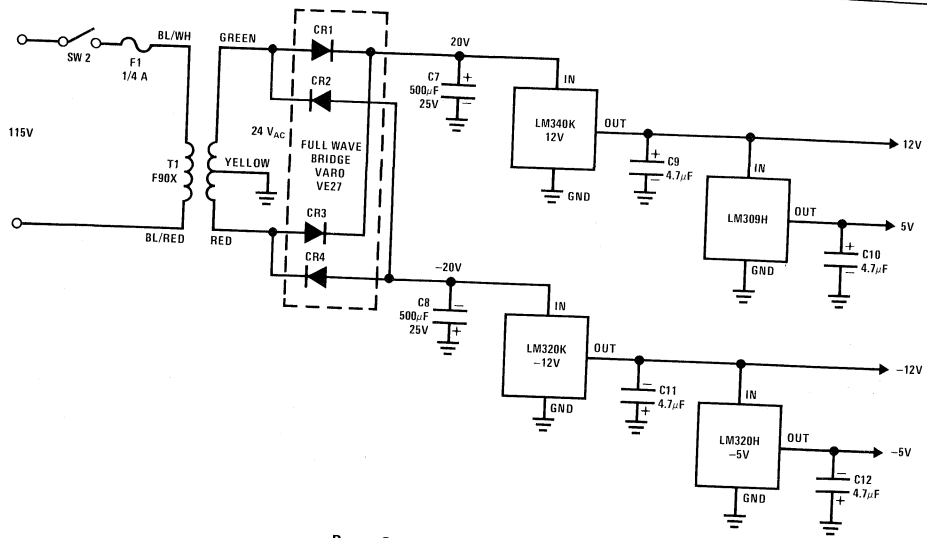

Power Supply Section Schematic

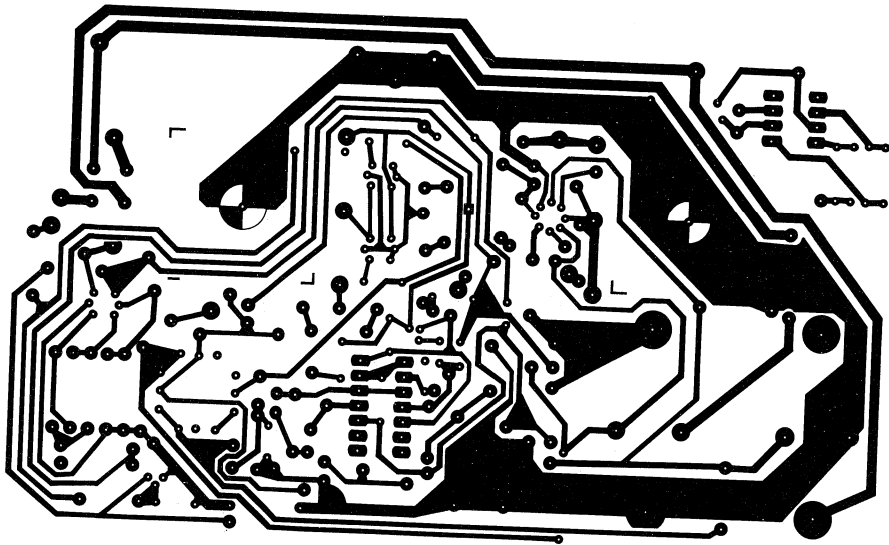

Circuit Board Layout  
 (This PC layout must be enlarged approximately 120% in order to be usable.)

# Use the LM158/LM258/ LM358 Dual, Single Supply Op Amp

National Semiconductor  
Application Note 116  
Jim Sherwin  
May 1974  
Revised August 1980



AN-116 Use the LM158/LM258/LM358 Dual, Single Supply Op Amp

## INTRODUCTION

Use the LM158/LM258/LM358 dual op amp with a single supply in place of the MC1458/MC1558/MC1558C with split supply and reap the profits in terms of:

- Input and output voltage range down to the negative (ground) rail
- Single supply operation
- Lower standby power dissipation
- Higher output voltage swing
- Lower input offset current
- Generally similar performance otherwise.

The main advantage, of course, is that you can eliminate the negative supply in many applications and still retain equivalent op amp performance. Additionally, and in some cases more importantly, the input and output levels are permitted to swing down to ground (negative rail) potential. Table I shows the relative performance of the two in terms of guaranteed and/or typical specifications.

In many applications the LM158/LM258/LM358 can also be used directly in place of LM1558 for split supply operation.

## SINGLE SUPPLY OPERATION

The LM1458/LM1558 or similar op amps exhibit several important limitations when operated from a single positive (or negative) supply. Chief among these is that input and output signal swing is severely limited for a given supply as shown in *Figure 1*. For linear operation, the input voltage must not reach within 3 volts of ground or of the supply, and output range is similarly limited to within 3–5 volts of ground or supply. This means that operation with a +12V supply could be limited as low as 2 Vp-p output swing. The LM358 however, allows a 10.5 Vp-p output swing for the same 12V supply. Admittedly these are worst case specification limits, but they serve to illustrate the problem.

TABLE I. Comparison of Dual Op Amps LM1458 and LM358

CHARACTERISTIC	LM1458	LM358
$V_{IO}$	6 mV Max	7 mV Max
CM $V_i$	24 Vp-p*	0 – 28.5V*
$I_{IO}$	200 nA	50 nA
$I_{OB}$	500 nA	–500 nA
CMRR	60 dB Min @ 100 Hz 90 dB Typ	85 dB Typ @ DC
$\bar{e}_n$ @ 1 kHz, $R_{GEN}$ 10 k $\Omega$	45 nV/ $\sqrt{Hz}$ Typ	40 nV/ $\sqrt{Hz}$ Typ**
$Z_{IN}$	200 M $\Omega$ Typ	Typ 100 M $\Omega$
$A_{VOL}$	20k Min 100k Typ	100k Typ
$f_c$	1.1 MHz Typ	1 MHz Typ**
$P_{BW}$	14 kHz Typ	11 kHz Typ**
$dV_o/dt$	0.8V/ $\mu$ s Typ	0.5V/ $\mu$ s Typ**
$V_o$ @ $R_L = 10k/2k$	24/20 Vp-p*	28.5 Vp-p
$I_{sc}$	20 mA Typ	Source 20 mA Min (40 Typ) Sink 10 mA Min (20 Typ)
PSRR @ DC	37 dB Min 90 dB Typ	100 dB Typ
$I_D$ ( $R_L = \infty$ )	8 mA Max	2 mA Max

‡ From laboratory measurement

\* Based on  $V_S = 30V$  on LM358 only, or  $V_S = \pm 15V$

\*\* From data sheet typical curves

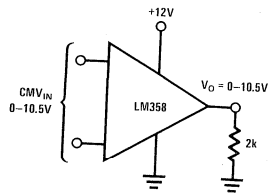
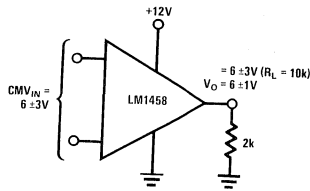


FIGURE 1. Worst Case Signal Levels with +12V Supply

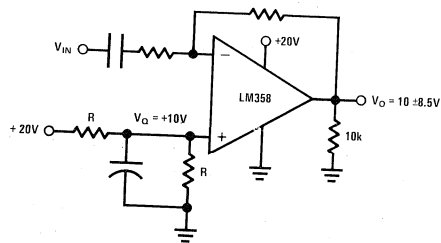
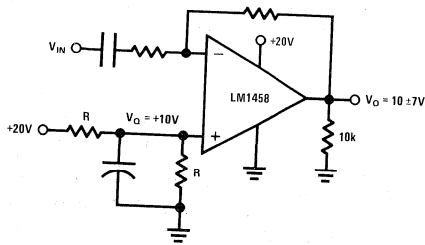


FIGURE 2. Operating with AC Signals

## AC GAIN

For ac signals the input can be capacitor coupled. The input common mode and quiescent output voltages are fixed at one-half the supply voltage by a resistive divider at the non-inverting input as shown in Figure 2. This quiescent output could be set at a lower voltage to minimize power dissipation in the LM358, if desired, so long as  $V_Q \geq V_{IN}$  pk. For the LM1458 the quiescent output must be higher,  $V_Q \geq 3V + V_{IN}$  pk thus, for small signals, power dissipation is much greater with the LM1458. Example: Required  $V_O = V_Q \pm 1V$  pk into 2k,  $V_{SUPPLY}$  = as required. Find quiescent dissipation in load and amplifier for LM1458 and LM358.

### LM358

$$V_Q = +1V$$

$$V_{SUPPLY} = +3.5V$$

$$P_{LOAD} = \frac{E_L^2}{R_L} = \frac{1}{2k} = 0.5 \text{ mW}$$

$$P_D = V_{SIS} \cdot (V_S - V_Q) I_L$$

$$= 3.5V \times 0.7 \text{ mA} + (3.5 - 1) \frac{1V}{2k}$$

$$P_D = 2.45 + 1.25 = 3.7 \text{ mW}$$

$$P_{TOTAL} = 3.7 + 0.5 = 4.2 \text{ mW}$$

\*From typical characteristics

### LM1458

$$V_Q = 4V$$

$$V_{SUPPLY} = 8V$$

$$P_{LOAD} = \frac{4^2}{2k} = 8 \text{ mW}$$

$$P_D = P_D^* + (V_S - V_Q) I_L$$

$$= 22 \text{ mW} + (8 - 4) \frac{4V}{2k}$$

$$P_D = 22 + 8 = 30 \text{ mW}$$

$$P_{TOTAL} = 30 + 8 = 38 \text{ mW}$$

\*From typical characteristics

The LM1458 requires over twice the supply voltage and nearly 10 times the supply power of the LM358 in this application.

## INVERTING DC GAIN

Connections and biasing for dc inverting gain are essentially the same as for the ac coupled case. Note, of course, that the output cannot swing negative when operated from a single positive supply. Figure 3 shows the connections and signal limitations.

## NON-INVERTING DC GAIN

The non-inverting gain connection does not require the  $V_Q$  biasing as before; the inverting input can be returned to ground in the usual manner for gains greater than unity, (see Figure 4). A tremendous advantage of the LM358 in this connection is that input signals and output may extend all the way to ground; therefore dc signals in the low-millivolt range can be handled. The LM1458 still requires that  $V_{IN} = 3-17V$ . Therefore maximum gain is limited to  $A_V = (V_O - 3)/3$ , or  $A_{V \text{ max}} = 5.4$  for a 20V supply.

There is no similar limitation for the LM358.



### ZERO T.C. INPUT BIAS CURRENT

An interesting and unusual characteristic is that  $I_{IN}$  has a zero temperature coefficient. This means that matched resistance is not required at the input, allowing omission of one resistor per op amp from the circuit in most cases.

### BALANCED SUPPLY OPERATION

The LM358 will operate satisfactorily in balanced supply operation so long as a load is maintained from output to the negative supply.

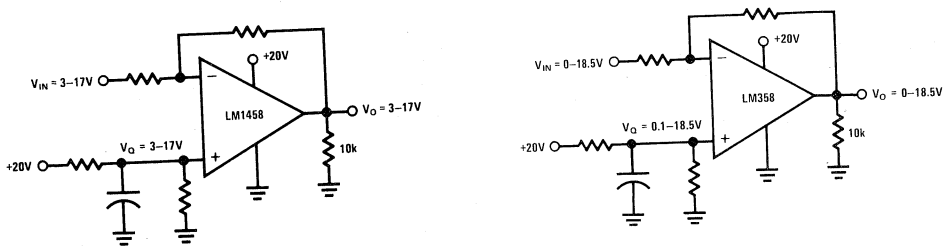


FIGURE 3. Typical DC Coupled Inverting Gain

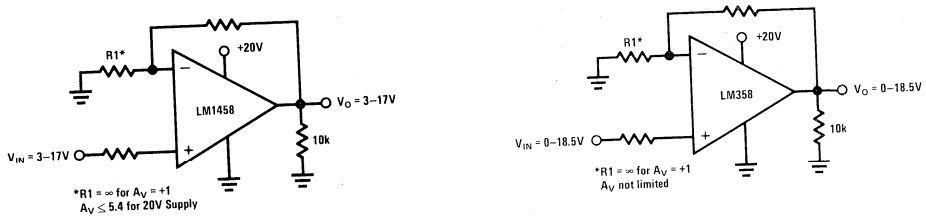


FIGURE 4. Typical DC Coupled Non-Inverting Gain

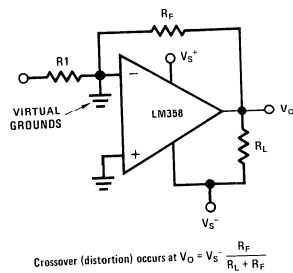


FIGURE 5. Split Supply Operation of LM358

The output load to negative supply forces the amplifier to source some minimum current at all times, thus eliminating crossover distortion. Crossover distortion without this load would be more severe than that expected with the normal op amp. Since the single supply design took notice of this normal load connection to ground, a class AB output stage was not included. Where ground referenced feedback resistors are used as in *Figure 5*, the required load to the negative supply depends upon the peak negative output signal level desired without exhibiting crossover distortion.  $R_L$  to the negative rail should be chosen small enough that the voltage divider formed by  $R_F$  and  $R_L$  will permit  $V_o$  to swing negative to the desired point according to the equation

$$R_L = R_F \frac{V_S^- - V_o}{V_o}$$

$R_L$  could also be returned to the positive supply with the advantage that  $V_o$  max would never exceed ( $V_S^+ - 1.5V$ ). Then with  $\pm 15V$  supplies  $R_{L \text{ MIN}}$  would be  $0.12 R_F$ . The disadvantage would be that the LM358 can source twice as much current as it can sink, therefore  $R_L$  to negative supply can be one-half the value of  $R_L$  to positive supply.

The need for single or split supply is based on system requirements which may be other than op amp oriented. However if the only need for balanced supplies is to simplify the biasing of op amps, there are many systems which can find a cost effective benefit in operating LM358's from single supplies rather than standard op amps from balanced supplies. Of the usual op amp circuits, Table II shows those few which have limited function with single supply operation. Most are based on the premise that to operate from a single supply, a reference  $V_o$  at about one-half the supply be available for bias or (zero) signal reference. The basic circuits are those listed in AN-20.

TABLE II. Conventional Op Amp Circuits Suitable for Single Supply Operation

APPLICATION	LIMITATIONS
AC Coupled amp <sup>‡</sup>	$V_o^*$
Inverting amp	$V_o$
Non-inverting amp	OK*
Unity gain buffer	OK
Summing amp	$V_o$
Difference amp	$V_o$
Differentiator	$V_o$
Integrator	$V_o$
LP Filter	$V_o$
I-V Connector	$V_o$
PE Cell Amp	OK
I Source	$I_{O \text{ MIN}} = \frac{1.5}{R1}$
I sink	OK
Volt Ref	OK
FW Rectifier	$V_o$ or modified circuit
Sine wave osc	$V_o$
Triangle generator	$V_o$
Threshold detector	OK
Tracking, regulator PS	Not practical
Programmable PS	OK
Peak Detector	OK to $V_{IN} = 0$

<sup>‡</sup>See AN20 for conventional circuits

\* $V_o$  denotes need for a reference voltage, usually at about  $\frac{V_S}{2}$

OK means no reference voltage required

# LM377, LM378 and LM379 Dual Two, Four and Six Watt Power Amplifiers

National Semiconductor  
Application Note 125  
Jim Sherwin  
January 1975



## INTRODUCTION

The LM377, LM378 and LM379 are two-channel power amplifiers capable of delivering 2, 4, and 6 watts respectively into 8 or 16Ω loads. They feature on-chip frequency compensation, output current limiting, thermal shut-down protection, fast turn-on and turn-off without "pops" or pulses of active gain, an output which is self-entering at  $V_{CC}/2$ , and a 5 to 20 MHz gain-bandwidth product. Applications include stereo or multi-channel audio power output for phono, tape or radio use over a supply range of 10 to 35V, as well as servo amplifier, power oscillator and various instrument system circuits. Normal supply is single-ended, however, split supplies may be used without difficulty or degradation in power supply rejection.

## CIRCUIT DESCRIPTION

The simplified schematic of *Figure 1* shows the important design features of the amplifier. The differential input stage made up of Q1–Q4 uses a double (split) collector PNP Darlington pair having several advantages. The high base-emitter breakdown of the lateral PNP transistor is about 60V which affords significant input over-voltage protection. The double collector allows operation at high emitter current to achieve good first stage  $f_t$  and minimum phase shift while simultaneously operating at low transconductance to allow internal compensation with a physically small capacitor C1. (Unity gain bandwidth of an amplifier with pole-splitting compensation occurs where the first stage transconductance equals  $\omega C1$ .)

Further decrease of transconductance is provided by degeneration caused by resistors at Q2 and Q3 emitters which also allow better large signal slew rate. The second collector provides bias current to the input emitter follower for increased frequency response and slew rate. Full differential input stage gain is provided by the "turnaround" differential to single-ended current source loads Q5 and Q6. The input common-mode voltage does not extend below about 0.5V above ground as might otherwise be expected from initial examination of the input circuit. This is because Q7 is actually preceded by an emitter follower transistor not shown in the simplified circuit.

The second stage Q7 operates common-emitter with a current source load for high gain. Pole splitting compensation is provided by C1 to achieve unity gain bandwidth of about 10 MHz. Internal compensation is sufficient with closed-loop gain down to about  $A_V = 25$ .

The output stage is a complementary common-collector class AB composite. The upper, or current sourcing section, is a Darlington emitter follower Q12 and Q13. The lower, or current sinking section is a composite PNP made up of Q14, Q15, and Q9. Normally, this type of PNP composite has low  $f_t$  and excessive delay caused by the lateral PNP transistor Q9. The usual result is poor unity gain bandwidth and probable oscillation on the negative half of the output waveform. The traditional fix has been to add an external series

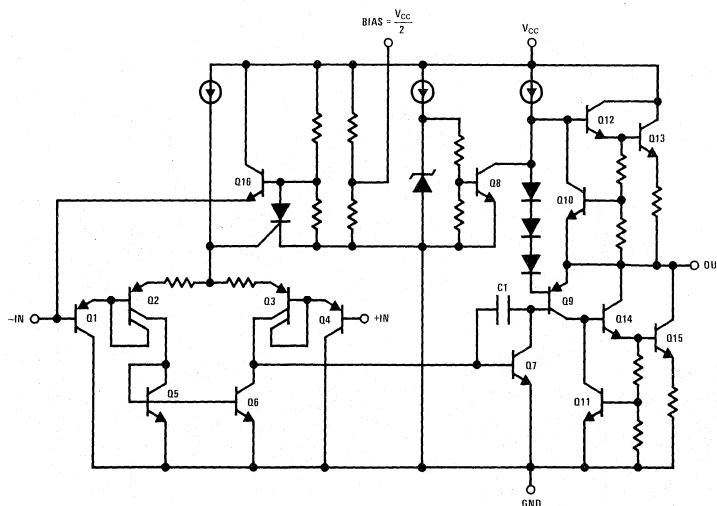


FIGURE 1. Simplified Schematic Diagram

RC network from output to ground to reduce loop gain of the composite PNP and so prevent the oscillation. In the LM377 series amplifiers, Q9 is made a field-aided lateral PNP to overcome these performance limitations and so reduce external parts count. There is no need for the external RC network, no oscillation is present on the negative half cycle, and bandwidth is better with this output stage. Q10 and Q11 provide output current limiting at about 1.3A, and there is internal thermal limiting protection at 150°C junction temperature. The output may be ac shorted without problem; and, although not guaranteed performance, dc shorts to ground are acceptable. A dc short to supply is destructive due to the thermal protection circuit which pulls the output to ground.

To achieve a stable dc operating point, it is desirable to close the feedback loop with unity dc gain. To achieve this simultaneously with a high ac gain normally requires a fairly large bypass capacitor, C1, in *Figure 2*.

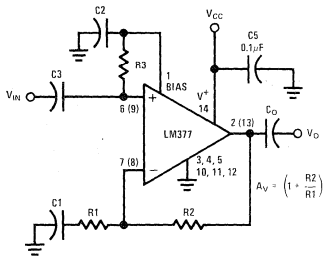


FIGURE 2. Non-Inverting Amplifier Connection

Establishing the initial charge on this capacitor results in a turn-on delay. An additional capacitor, C2, is normally required to supply a ripple-free reference

to set the dc operating point. To achieve good supply rejection  $X_{C2}$  is normally made much smaller than a series resistor from the bias divider circuit ( $R_S$  in *Figure 3*). Where a supply rejection of 40 dB is required with 40 dB closed-loop gain, 80 dB ripple attenuation is required of  $R_S C2$ . The turn-on time can be calculated as follows:

$$PSRR = \frac{R_S - jX_{C2}}{X_{C2}} \approx \frac{R_S}{X_{C2}} = \omega RC = \omega T$$

$$T = \frac{PSRR}{\omega} = \frac{80 \text{ dB}}{2\pi \cdot 120 \text{ Hz}} = \frac{10^4}{754} = 13.3 \text{ sec}$$

$$t_{ON} \approx \frac{T}{3} = 4.5 \text{ seconds to small signal operation}$$

$$t_{ON} \approx 3T = 40 \text{ seconds to full output voltage swing}$$

The 3T delay might normally be considered excessive! The LM377 series amplifiers incorporate active turn-on circuitry to eliminate the long turn-on time. This circuitry appeared in *Figure 1* as Q16 and an accompanying SCR; it is repeated and elaborated in *Figure 3*. In operation, the turn-on circuitry charges the external capacitors, bringing output and input levels to  $V_{CC}/2$ , and then disconnects itself leaving only the  $V_{CC}/2$  divider  $R_B/R_B$  in the circuit.

The turn-on circuit operation is as follows. When power is applied, approximately  $V_{CC}/2$  appears at the base of Q16, rapidly charging C1 and C2 via a low emitter-follower output impedance and series resistors of 3k and 1k. This causes the emitters of the differential input pair to rise to  $V_{CC}/2$ , bringing the differential amp Q3 and Q4 into balance. This, in turn, drives Q3 into conduction. Transistors Q2 and Q3 form an SCR latch which then triggers and clamps the base of Q16 to

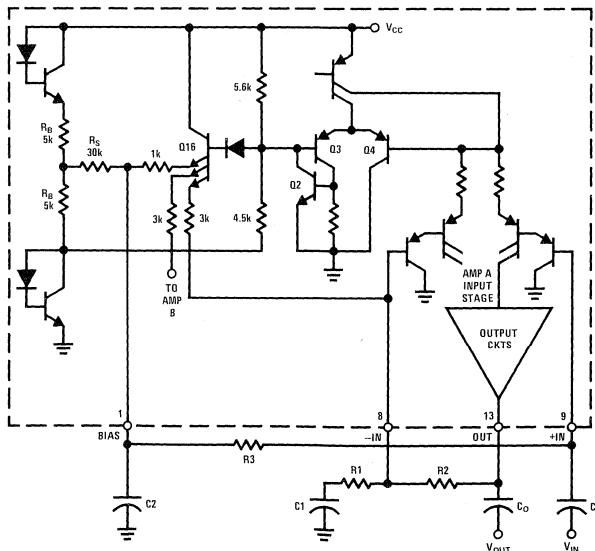


FIGURE 3. Internal Turn-On Circuitry

ground, thus disabling the charging circuit. Once the capacitors are charged, the internal voltage divider  $R_B/R_B$  maintains the operating point at  $V_{CC}/2$ . Using  $C2 = 250\mu F$ , the  $t_{ON} = 3T \approx 0.3$  seconds and PSRR  $\approx 75$  dB at 120 Hz due to the 30k resistor  $R_S$ . Using  $C2 = 1000\mu F$ , PSRR would be 86 dB. The internal turn-on circuit prevents the usual "pop" from the speaker at turn-on. The turn-off period is also pop-free as there is no series of pulses of active gain often seen in other similar amplifiers.

Note that the base of Q4 is tied to the emitters of only one of the two input circuits. Should only one amplifier be in use, it is important that it be that with input at pins 8 and 9.

### EXTERNAL BIASING CONNECTION

The internal biasing is complete for the inverting gain connection of *Figure 4* except for the external C2 which provides power supply rejection. The bias terminal 1 may be connected directly to C2 and the non-inverting input terminals 6 and 9. Normal gain-set feedback connections to the inverting inputs plus input and output coupling capacitors complete the circuitry. The output will Q up to  $V_{CC}/2$  in a fraction of one second.

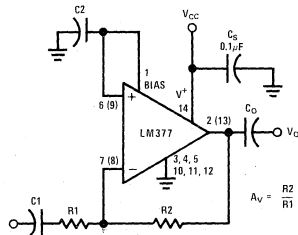



FIGURE 4. Inverting Amplifier Connection

The non-inverting circuit of *Figure 2* is only slightly more complex, requiring the input return resistor R3 from input to the bias terminal and additional input capacitor C3. C1 must remain in the circuit at the same or larger value than in *Figure 4*.

### AUDIO AMPLIFIER APPLICATIONS
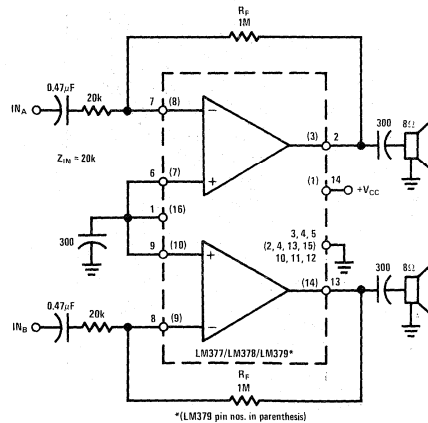
#### 2/4/6 Watt Stereo Amplifier

The obvious and primary intended application is as an audio frequency power amplifier for stereo or quadraphonic music systems. The amplifier may be operated in either the non-inverting or the inverting modes of *Figures 2 and 4*. The inverting circuit has the lowest parts count so is most economical when driven by relatively low-impedance circuitry. *Figure 5* shows the total parts count for such a stereo amplifier. The feedback resistor value of 1 meg in *Figure 5* is about the largest practical value due to an input bias current max of approximately  $1/2\mu A$  (100 nA typ). This will cause a  $-0.1$  to  $0.5V$  shift in dc output level, thus limiting peak negative signal



\*(LM378 pin nos. in parenthesis)

	LM377	LM377/LM378	LM379
$P_D =$	2W/CH	3W/CH	4W/CH
$v_s =$	80 mV max	96 mV max	113 mV max
$A_v =$	50	50	50
$V_{CC} =$	18V	24V	28V

FIGURE 5. Inverting Stereo Amplifier

swing. This output voltage shift can be corrected by the addition of series resistors (equal to the  $R_F$  in value) in the + input lines. However, when this is done, a potential exists for high frequency instability due to capacitive coupling of the output signal to the + input. Bypass capacitors could be added at + inputs to prevent such instability, but this increases the parts count equal to that of the non-inverting circuit of *Figure 6* which has a superior input impedance. For applications utilizing high impedance tone and volume controls, the non-inverting connection will most surely be used.


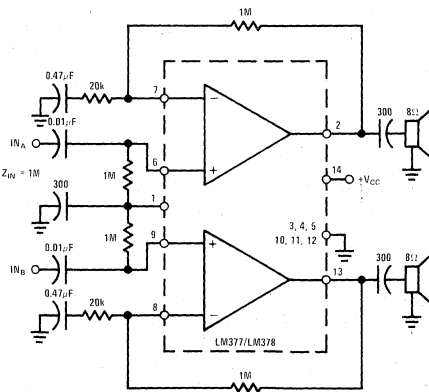


FIGURE 6. Non-Inverting Stereo Amplifier

The prime limitations on output power of the LM377 and LM378 will be the type of heat sink employed, supply voltage, and load resistance. Reference to the data sheet curves will indicate the most efficient supply voltages to use for specific power output levels with 8 or  $16\Omega$  loads. The pertinent curves are reproduced in *Figures 7 through 10*. For other conditions  $P_D = V_{CC}^2 / 20 R_L$ . At high power out, efficiency exceeds 50%

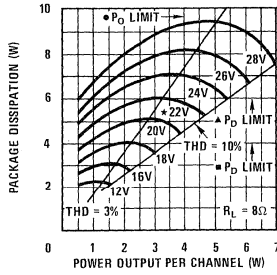

- Approx.  $P_D$  limit acc't. 0.7A rms internal current limit at oper. die temp.
- ▲  $P_D$  limit for LM377/LM378 on PC board w/Staver V7-1 heat sink.
- $P_D$  limit for LM377/LM378 on PC board (2.5 sq. in. Cu).
- Safe limit for LM377.

FIGURE 7. Device Dissipation for 8Ω Load


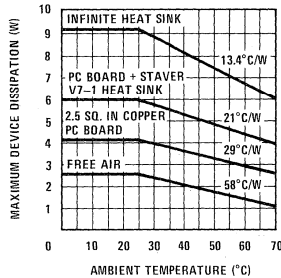


FIGURE 9. LM377/LM378 Power Derating

and dissipation drops below output power. A dual 2W amplifier must then dissipate about 4.0W with an 18V supply or 4.9W with a 20V supply when  $R_L = 8\Omega$ . Normally, one would choose the 18V supply for lower dissipation; however, the 20V supply allows reduced distortion levels or considerably higher powers. A dual 4W amplifier will dissipate about 8W with a 26V supply. This is above the dissipation limit for an LM378 with normal heat sink. Accordingly, a fairly efficient heat sink must be employed in order to allow full 8W continuous output from the LM378 (Figure 9). The recommended heat sinks are listed in Table 1 with measured power output levels at  $V_S = 18$  to 29V for LM377 and LM378 (observe voltage limits on LM377) with 8 or 16Ω load.
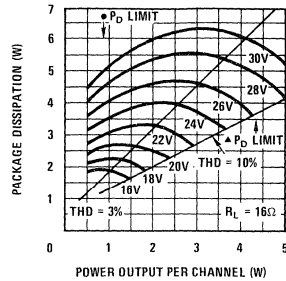
#### POWER OUTPUT PER CHANNEL (BOTH CHANNELS DRIVEN) BEFORE CLIPPING

Power dissipation vs power output/channel (both channels driven) is indicated in Figures 7 and 8 for load resistances of 8 and 16Ω.



- $P_D$  limit LM377/LM378 on PC board w/Staver V7-1.
- ▲  $P_D$  limit LM377/LM378 on PC board.

FIGURE 8. Device Dissipation for 16Ω Load

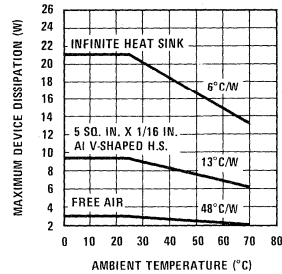


FIGURE 10. LM379 Power Derating

Limiting points to keep in mind, noted on Figures 7 and 8, are 4W package dissipation limit for LM377/LM378 when soldered to PC board with 2.5 sq. in. copper, 6W limit when a Staver V7-1 heat sink is added, and internal current limit at about 1.5A peak at 25°C die temperature reducing to about 1A peak at operating die temperature. This results in an approximate  $P_O = 4W$ /channel limit for  $R_L = 8\Omega$ . The onset of clipping occurs just to left of the THD = 3% line in Figures 7 and 8.

The overall result is that the LM377 and LM378 with practical heat sinks, are limited to operation below package dissipation of 6W and below  $P_O = 4W$ /channel when  $R_L = 8\Omega$ . Thus maximum  $P_O = 3W$ /channel before clipping or 4W/channel at about 6% THD with either device at  $V_{CC} = 22V$ . With a 16Ω load the LM378 can deliver 4W/channel with 3–4% THD when  $V_{CC} = 29$ –30V. The LM379 is limited to  $P_O = 4$ –5W/channel before clipping at  $V_{CC} = 26$ –28V,  $R_L = 8\Omega$ , or 4W/channel at  $V_{CC} = 30V$ ,  $R_L = 16\Omega$ .  $P_O = 6W$  occurs at 8–10% THD with  $V_{CC} = 28$ –30V and  $R_L = 8\Omega$ .

TABLE 1. Continuous Power Out (Both Channels)

HEAT SINK	LM377 $R_L = 8\Omega$			LM378 $R_L = 16\Omega$		
	$V_S = 18V$	$V_S = 20V$	$V_S = 22V$	$V_S = 24V$	$V_S = 26V$	$V_S = 29V$
PC Board, 40°C/W	2.2W	0.8W	0.3W	2.2W	1W	0.3W
PC Board and Staver V7-1, 12°C/W	2.2W	2.7W	3.1W	2.2W	2.5W	3.3W

Note that the  $P_O = 6W$  rating on LM379 is at 10% THD where peak current is similar to that at  $P_O = 4W$ ,  $V_{CC} = 26V$ ,  $R_L = 8\Omega$ .

What really exists then are power out before clipping of 2W/channel at  $V_{CC} = 18V$  with PC board mounting, 3W/channel at  $V_{CC} = 22V$  with maximum practical heat sinking on either LM377 or LM378, and 4W/channel at  $V_{CC} \geq 26V$  for LM379.

Device dissipation vs ambient temperature with several heat sink types is indicated in Figures 9 and 10 for convenience of matching heat sink capacity to the circuit needs. In those cases where heat sink capacity is inadequate for device dissipation requirements, the internal thermal limit circuitry will automatically limit device dissipation on signal peaks. The result is similar to peak clipping in its effect and causes severe distortion. The device can provide momentary peak power output in excess of the maximum heat sink limited steady-state levels for a second or so depending upon the margin between maximum steady-state level and the actual average power level prior to the peak demand. Once in thermal limiting, clipping occurs on each positive and/or negative half cycle of a steady waveform.

In the majority of audio amplifier applications, the heat sinking can be considerably smaller due to the approximately 30 dB ratio between rms and peak power levels in music and speech. If we assume willingness to accept clipping at peak levels 20 dB above average level, then average power levels will be 0.2–0.3W/channel in LM377 and LM378. Heat sink requirements are thus significantly reduced as these peak levels occur less than 10% of time periods of several seconds duration. Thus the circuit does not go into thermal overload even though the heat sink is designed for 3W dissipation (LM377 operating at 0.3W/channel,  $V_{CC} = 18V$ ).

### STABILIZATION

The LM377 series amplifiers are internally stabilized so external compensation capacitors are not required. The high Gain x BW provides a bandwidth greater than 50 kHz as seen in Figure 11. These amplifiers are,

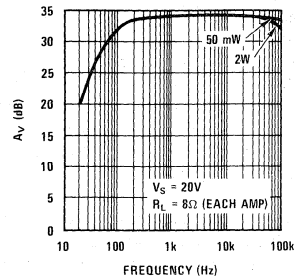


FIGURE 11. Frequency Response of the Stereo Amp of Figure 5

however, not intended for closed loop gain below 25. The typical Bode plot of Figure 12 shows a phase margin of  $70^\circ$  for gain of 5.6 (15 dB) which is stable. At unity gain the phase margin is less than  $30^\circ$  or marginally stable. This margin may vary considerably from device to device due to variation in Gain x BW.

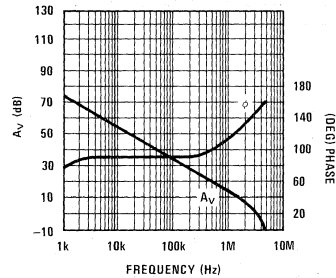


FIGURE 12. Open Loop Bode Plot (Approximately Worst Case)

As with any amplifier of high Gain x BW, careful circuit layout is important to insure unconditional stability. Specifically, coupling to the non-inverting inputs from output and feedback elements should be minimized. The supply should also be bypassed with an 0.05–0.1  $\mu F$  ceramic or 0.47  $\mu F$  mylar capacitor within 2 inches of the IC terminals. One layout which accomplishes this is illustrated in Figure 13. The signal circuits are symmetrically arranged on either side of the IC package.

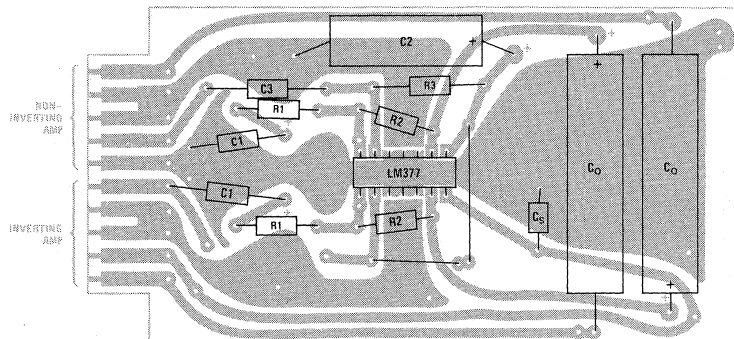


FIGURE 13. Parts Layout for LM377/LM378 Dual Amplifier

Operation may be either inverting or non-inverting, therefore, one side is shown connected each way. Normally both sides would be connected in the same sense. The PC board art-work is shown in *Figure 14*. The edge connector could, of course, be omitted and wire connections made to appropriate contacts at either end. This layout is satisfactory for gain as low as 10. Below  $A_V = 10$ , instability may occur.

Ground and power connections must be adequate to handle the 1 to 2A peak supply and load currents. Ground loops can be especially troublesome because of these high currents. The load return line should be connected directly to the ground pins of the package on one side and/or the input and feedback ground lines should be connected directly to the ground pins (possibly on the other side of the package). Note that the layout in *Figure 14* has a connection at center of the card edge connector for signal ground and two separate, flanking, terminals for the load and power grounds. The signal ground should not be connected so as to intercept any output signal voltage drop due to resistance between IC ground and load ground.

#### 10–12 Watt Channel Boosted Amplifier

Where more power output is desired, the simple booster circuit of *Figure 15* allows power output of 10W/channel

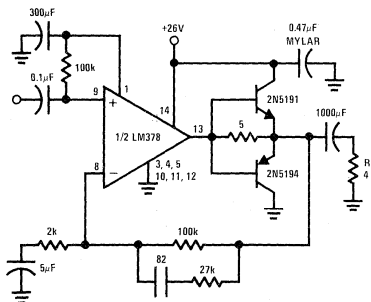


FIGURE 15. 10 Watt Power Amplifier

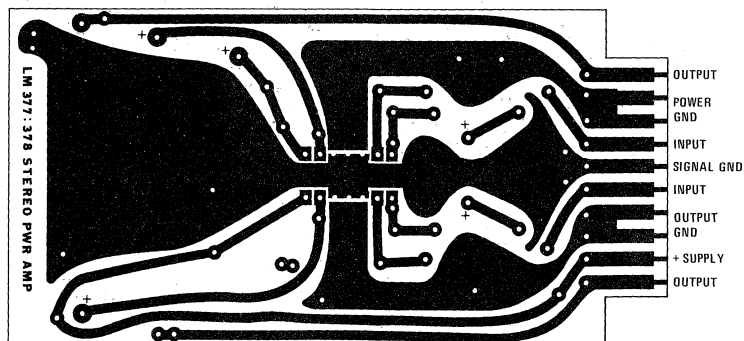


FIGURE 14. PC Board for LM377/LM378 Dual Amplifier

when driven from the LM378. The circuit is exceptionally simple, and the output exhibits lower levels of crossover distortion than does the LM378 alone. This is due to the inclusion of the booster transistors within the feedback loop. At signal levels below 20 mW, the LM378 supplies the load directly through the 5Ω resistor to about 100 mA peak current. Above this level, the booster transistors are biased ON by the load current through the same 5Ω resistor.

The response of the 10W boosted amplifier is indicated in *Figure 16* for power levels below clipping. Distortion

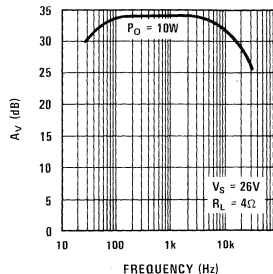


FIGURE 16. 10 Watt Boosted Amplifier, Frequency Response

is below 2% from about 50 Hz to 30 Hz. Fifteen watts rms power is available at 10% distortion; however, this represents extreme clipping. Although the LM378 delivers little power, its heat sink must be adequate for about 3W package dissipation. The output transistors must also have an adequate heat sink.

The circuit of *Figure 17* achieves about 12W/channel output prior to clipping. Power output is increased because there is no power loss due to effective series resistance and capacitive reactance of the output coupling capacitor required in the single supply circuit. At power up to 10W/channel, the output is extremely clean, containing less than 0.2% THD midband at 10W. The bandwidth is also improved due to absence of the output coupling capacitor. The frequency response and distortion are plotted in *Figures 18 and 19* for low and high power levels. Note that the input coupling capacitor is still required, even though the input may be ground



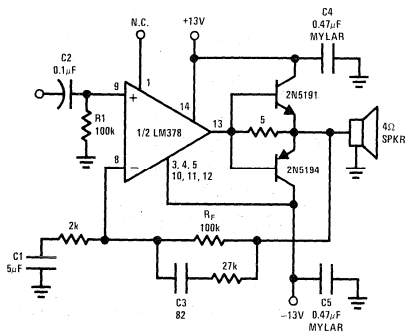


FIGURE 17. 12 Watt Low-Distortion Power Amplifier

referenced, in order to isolate and balance the dc input offset due to input bias current. The feedback coupling capacitor, C1, maintains dc loop gain at unity to insure zero dc output voltage and zero dc load current. Capacitors C1 and C2 both contribute to decreasing gain at low frequencies. Either or both may be increased for better low frequency bandwidth. C3 and the 27k resistor provide increased high frequency feedback for improved high frequency distortion characteristics. C4 and C5 are low inductance mylar capacitors connected within 2 inches of the IC terminals to ensure high frequency stability. R1 and R<sub>f</sub> are made equal to maintain V<sub>OUT DC</sub> = 0. The output should be within 10 to 20 mV of zero volts dc. The internal bias is unused; pin 1

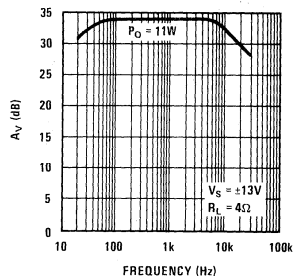


FIGURE 18. Response for Amplifier of Figure 17

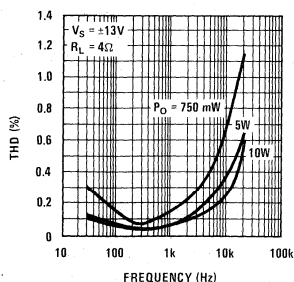


FIGURE 19. Distortion for Amplifier of Figure 17

should be open circuit. When experimenting with this circuit, use the amplifier connected to terminals 8, 9 and 13. If using only the amplifier on terminals 6, 7 and 2, connect terminals 8 and 9 to ground (split supply) to cause the internal bias circuits to disconnect.

### Bridge Amplifier

The LM377 series amplifiers are equally useful in the bridge configuration to drive floating loads, which may be loudspeakers, servo motors or whatever. Double the power output can be obtained in this connection, and output coupling capacitors are not required. Load impedance may be either 8 or 16Ω in the bridge circuit of Figure 20. Response of this circuit is 20 Hz

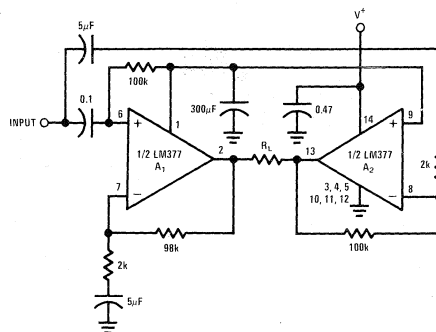


FIGURE 20. 4-Watt Bridge Amplifier

to 160 kHz as shown in Figure 21 and distortion is 0.1% midband at 4W rising to 0.5% at 10 kHz and 50 mW output Figure 22. The higher distortion at low power is due to a small amount of crossover notch distortion which becomes more apparent at low powers and high frequencies. The circuit of Figure 23 is similar except for higher input impedance. In Figure 23, the signal drive for the inverting amplifier is derived from the feedback voltage of the non-inverting amplifier. Resistors R1 and R3 are the input and feedback resistors for A<sub>2</sub>, whereas R1 and R2 are the feedback network for A<sub>1</sub>. So far as A<sub>1</sub> is concerned, R2 sees a virtual ground at the (-) input to A<sub>2</sub>; therefore, the gain of A<sub>1</sub> is (1 + R2/R1). So far as A<sub>2</sub> is concerned, its input signal is the voltage appearing at the (-) input to A<sub>1</sub>. This equals that at the (+) input to A<sub>1</sub>. The driving point impedance at the (-) input to A<sub>1</sub> is very low even though R2 is 100k. A<sub>1</sub> can be considered a unity gain amplifier with internal R = R2 = 100k and R<sub>L</sub> = R1 = 2k. Then the effective output resistance of the unity gain amplifier is:

$$R_{OUT} = \frac{R_{INTERNAL}}{A_{OL}/A_{\beta}} = \frac{100k}{600/1} = 167\Omega$$

Layout is critical if output oscillation is to be avoided. Even with careful layout, capacitors C1 and C2 may be required to prevent oscillation. With the values shown, the amplifier will drive a 16Ω load to 4W with less than 0.2% distortion midband, rising to 1% at 20 kHz (Figure 24). Frequency response is 27 Hz to 60 kHz as shown in Figure 25. The low frequency roll off is due to the double poles C3 R3 and C4 R1.

### Power Oscillator

One half of an LM377 may be connected as an oscillator to deliver up to 2W to a load. Figure 26 shows a Wein bridge type of oscillator with FET amplitude stabilization in the negative feedback path. The circuit employs

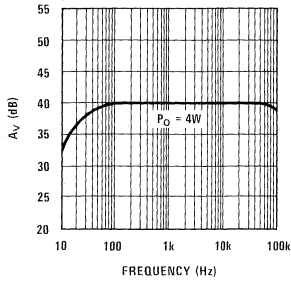


FIGURE 21. Frequency Response, Bridge Amp of Figure 20

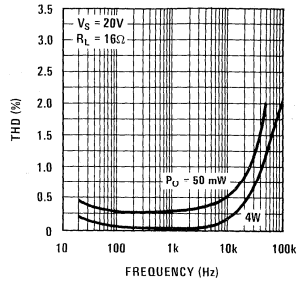


FIGURE 22. Distortion for Bridge Amp of Figure 20

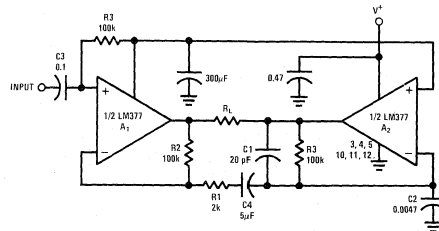


FIGURE 23. 4-Watt Bridge Amplifier with High Input Impedance

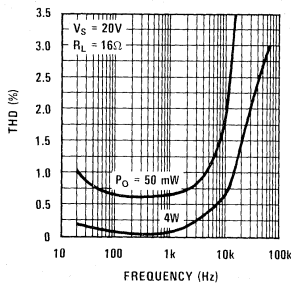


FIGURE 24. Distortion for Bridge Amp of Figure 23

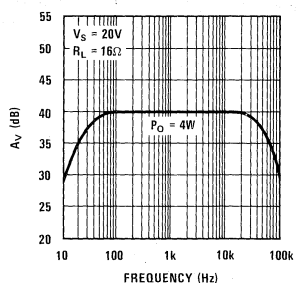


FIGURE 25. Frequency Response, Bridge Amp of Figure 23

internal biasing and operates from a single supply. C3 and C6 allow unity gain dc feedback and isolate the bias from ground. Total harmonic distortion is under 1% to 10 kHz, and could possibly be improved with careful adjustment of R5. The FET acts as the variable element in the feedback attenuator R4 to R6. Minimum negative feedback gain is set by the resistors R4 to R6, while the FET shunts R6 to increase gain in the absence of adequate output signal. The peak detector D2 and C8 senses output level to apply control bias to the FET. Zener diode D1 sets the output level although adjustment could be made if R9 were a potentiometer with R8 connected to the slider. Maximum output level with the values shown is 5.3V rms at 60 Hz. C7 and the attenuator R7 and R8 couple 1/2 the signal of the FET drain to the gate for improved FET linearity and low distortion. The amplitude control loop could be replaced by an incandescent lamp in non-critical circuits (Figure 27) although dc offset will suffer by a factor of about 3 (dc gain of the oscillator). R10 matches R3 for improved dc stability; and the network R11, C9 increases high frequency gain for improved stability. Without this RC, oscillation may occur on the negative half cycle of output waveform. A

low inductance capacitor, C5, located directly at the supply leads on the package is important to maintain stability and prevent high frequency oscillation on negative half cycle of the output waveform. C5 may be 0.1μF ceramic, or 0.47μF mylar. Layout is important; especially take care to avoid ground loops as discussed in the section on amplifiers. If high frequency instability still occurs, add the R12, C10 network to the output.

Figure 27 shows the use of the LM377 to drive a small 60 Hz two phase servo motor up to 3W per phase. Applications such as a constant (or selectable) speed phonograph turntable drive are adequately met by this circuit. A split supply is used to simplify the circuit, reduce parts count, and eliminate several large bypass capacitors. An incandescent lamp is used in a simple amplitude stabilization loop. Input dc is minimized by balancing dc resistance at + and - amplifier inputs (R1 = R3 and R6 = R8). High frequency stability is assured by increasing closed-loop gain from approximately 3 at 60 Hz to about 30 above 40 kHz with the network consisting of R3, R4 and C3. The interstage

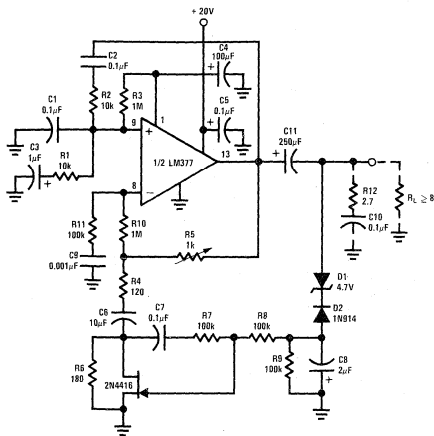


FIGURE 26. Wein Bridge Power Oscillator



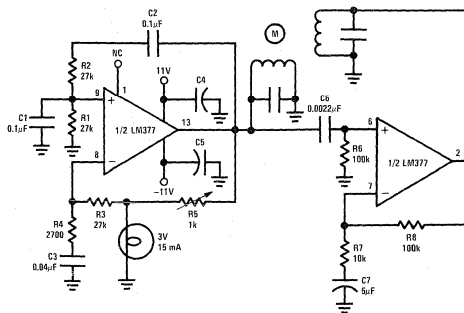



FIGURE 27. Two-Phase Motor Drive

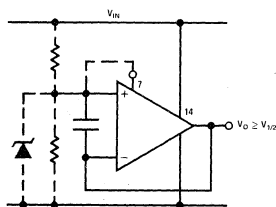

Supply Regulator

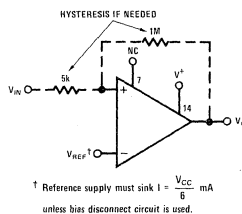

Power Comparator

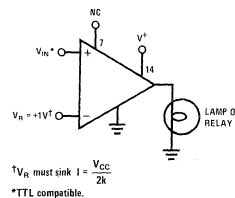

Lamp or Relay Driver

FIGURE 28. Miscellaneous Applications

coupling C6 R6 network shifts phase by 85° at 60 Hz to provide the necessary two phase motor drive signal. The gain of the phase shift network is purposely low so that the buffer amplifier will operate at a gain of 10 for adequate high frequency stability. As in other circuits, the importance of supply bypassing, careful layout, and prevention of output ground loops is to be stressed. The motor windings are tuned to 60 Hz with shunt capacitors. This circuit will drive 8Ω loads to 3W each.

### MISCELLANEOUS APPLICATIONS

A number of non-audio applications come to mind, such as a dual power supply regulator, power comparator, and relay or lamp driver as shown in Figure 28. The degree of practicality of any of these will be limited by the special characteristics of the LM377/LM378/LM379 chip. Limitations are a higher than usual input-offset voltage and temperature drift (not troublesome in the intended capacitor coupled applications). As the devices are not unity-gain stable, a shunt capacitor across the inputs is needed in low gain applications such as the supply regulator. The output saturation voltage is 2 to 3V, thus internal power dissipation is non-negligible in relay or lamp driver applications.

As a lamp driver, the LM377 is limited to those applications where its dissipation is outweighed by the advantage of the internal current limiting. The real advantage of this current limiting is that the lamp driver cannot be destroyed by a shorted lamp if the lamp common terminal is ground (the LM377 will not survive an output short to supply).

In any of these applications, recall that the internal turn-on circuit will supply current out the (-) input until inputs are raised to  $V_{CC}/2$ .

### COMPLETE SYSTEMS

The LM377 to LM379 dual power amplifiers are useful in table or console radios, phonographs, tape players, intercoms, or any low to medium power music systems. Several examples of complete audio systems are described. One is a 2-channel audio system for radio, phono, and tape playback. The other is rear channel amplifier pair for extracting "ambience" information from stereo signals and amplifying for 4-channel sound.

Figures 29 to 30 describe the complete electronic section of a 2-channel sound system with inputs for AM

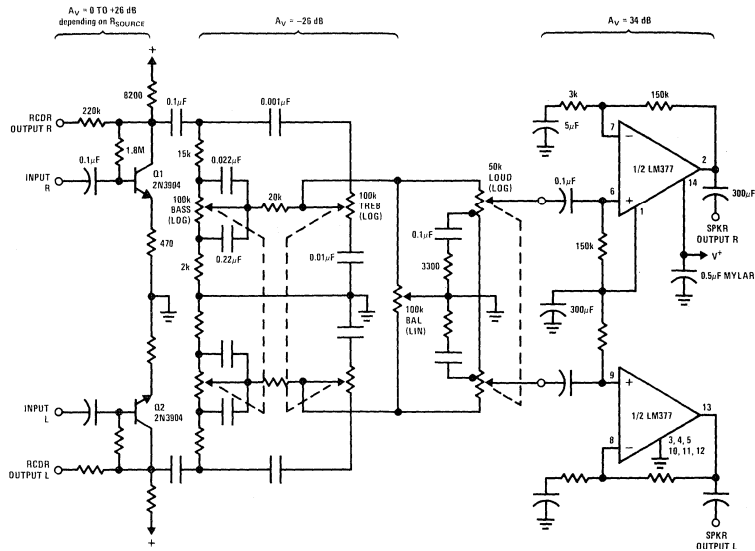


FIGURE 29. Two-Channel Power Amplifier and Control Circuits

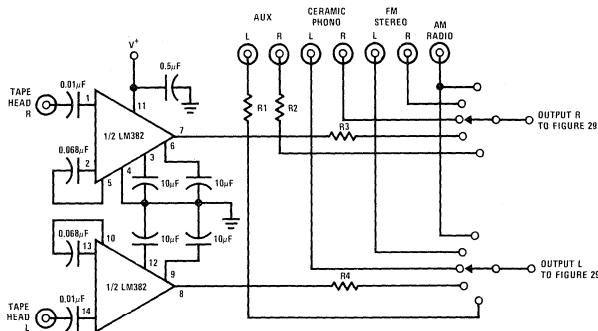


FIGURE 30. Two-Channel Tape-Playback Amplifier and Signal Switching

radio, stereo FM radio, phono, and tape playback. Figure 29 combines the power amplifier pair with loudness, balance, and tone controls. The tone controls allow boost or cut of bass and/or treble. Transistors Q1 and Q2 act as input line amplifiers with the triple function of (1) presenting a high input impedance to the inputs, especially ceramic phono; (2) providing an amplified output signal to a tape recorder; and (3) providing gain to make up for the loss in the tone controls. Feedback tone controls of the Baxandall type employing transistor gain could be used; but then, with the same transistor count, the first two listed functions of Q1 Q2 would be lost. It is believed that this circuit represents the lowest parts count for the complete system. Figure 30 is the additional circuitry for input switching and tape playback amplifiers. The LM382 with capacitors as shown provides for NAB tape playback compensation. For further information on the LM382 or the similar LM381 and LM387, refer to the data sheets.

Figure 31 shows the relationship between signal source impedance and gain or input impedance for the amplifier stage Q1 Q2. Stage gain may be set at a desired value by

choice of either the source impedance or insertion of resistors in series with the inputs (as R1 to R4 in Figure 30). Gain is variable from  $-15$  to  $+24$  dB by choice of series R from 0 to 10 meg. Gain required for  $e_{IN} = 100$  to 200 mV (approximate value of recovered audio from FM stereo or AM radio) is about 18 to 21 dB overall for 2W into an  $8\Omega$  speaker at 1 kHz or 21 to 24 dB for 4W.

The rear channel "ambience" circuit of Figures 32 and 33 can be added to an existing stereo system to extract a difference signal (R - L or L - R) which, when combined with some direct signal (R or L), adds some fullness, or "concert hall realism" to reproduction of recorded music. Very little power is required at the rear channels, hence an LM377 will suffice for most "ambience" applications. The inputs are merely connected to the existing speaker output terminals of a stereo set, and two more speakers are connected to the ambience circuit outputs. Note that the rear speakers should be connected in opposite phase to those of the front speakers, as indicated by the  $+/-$  signs on the diagram of Figure 32.

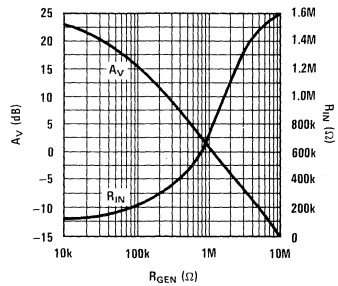


FIGURE 31.  $A_V$  and  $R_{IN}$  for Input Stage of Figure 28.

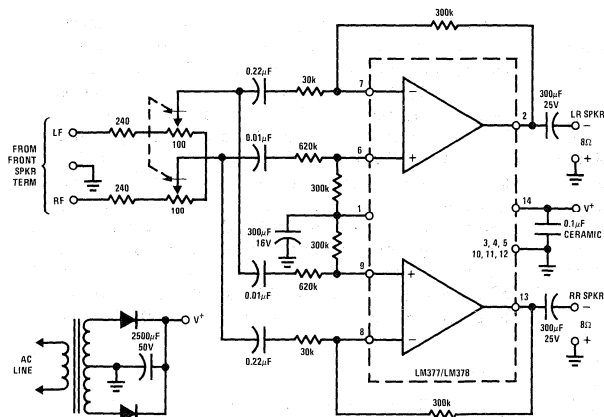


FIGURE 32. Rear Speaker Ambience (4-Channel) Amplifier

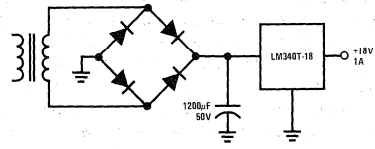


FIGURE 33. Alternate Power Supply for Ambience Circuit

APPENDIX: INTERPRETATION OF  $P_O$  vs  $P_D$  CURVES

The angled straight lines on the curves of *Figures A-1* and *A-2* indicate the loci of operating points where clipping occurs. When THD = 3%, the output waveform has noticeable clipping. The THD = 10% line is an operating area of severe clipping. Clipping begins just to the left of the THD = 3% line so this discussion deals only with operation up to, but not quite at, the 3% line.

The three circles on *Figure A-1* are the data sheet spec limits for LM377/LM378/LM379; that is, 2, 4 and 6W/channel with 20, 24 and 28V supplies respectively.

Observe that the 2W point is well to the left of the THD = 3% line, or well under clipping. The 4 and 6W points march progressively further toward the THD = 10% line, or deeper into clipping. Also note the dissipation limits in *Figure A-3* for LM377/LM378 on PC board and on PC board with addition of Staver V7-1 heat sink are 4.1 and 6W respectively. These represent the limits for commonly available heat sinks for the DIP package. No doubt a special heat sink fabricated "just-so" could extend the 6W limit to 6 1/2 or 7W, but we'll stop at 6W. Data have been added to *Figure A-4* showing LM379

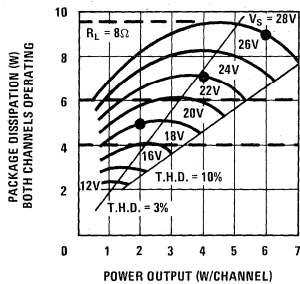


FIGURE A-1. Power Dissipation vs Power Output

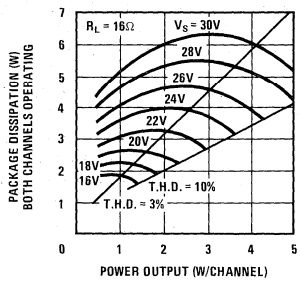


FIGURE A-2. Power Dissipation vs Power Output

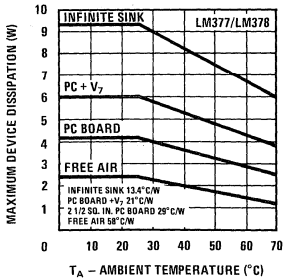


FIGURE A-3. Maximum Dissipation vs Ambient Temperature

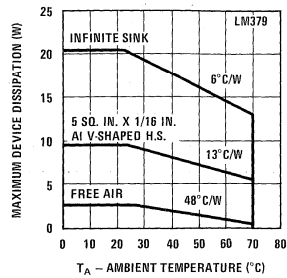


FIGURE A-4. Maximum Dissipation vs Ambient Temperature

dissipation with a simple small heat sink. This heat sink is 5 square inches of 1/16" aluminum in a modified V shape which is clamped to the sink side of the LM379.

These practical limits are transferred to *Figure A-1* as horizontal dashed lines across the  $P_O$  vs  $P_D$  curves at 4.1, 6 and 9.6W. We see that the reference points, 2W at 20V and 4W at 24V, are above the practical  $P_D$  limits for PC board alone and for PC board with Staver V7-1 heat sink. The third point, 6W at 28V is OK so far. What this means is that, in bench testing, the LM377 must have better than PC mounting to meet data sheet specified operation; and the LM378 will likely not meet data sheet specified operation with any practical heat sink. The LM377 will meet specs with the PC board plus Staver heat sink. The LM378 will meet specs with a 7W heat sink, but not with normally available heat sinks. The LM379 will meet specs with the 5 square inch sink described above. What may be most important, however, is performance short of clipping. For that reason, the remainder of this section will deal only with rms power at levels below clipping.

Returning to *Figure A-1*, it appears that the LM377 or LM378 with only PC board heat sinking will be able to deliver 2.2W/channel into 8Ω with an 18V supply. But, if the supply is raised to 20V, the  $P_D$  limit is exceeded at 1W. With PC board plus a Staver heat sink, the LM377/LM378 will deliver 3.2W/channel with 22V supply, yet raising the supply to 24V limits us to  $P_O = 1.9W$ /channel.

So why use a LM378 if the supply limit is 22V? The reason is that few supplies are regulated in the consumer world. This means that if the supply is 22V under full load, the no-signal supply may rise 10% or more; and the variations in line voltage may add another 10% for a total supply maximum of at least 26.5V. Therefore the LM377 is only recommended for full-load operating supplies of less than 20V. But remember, it can deliver over 2W/channel with an 18V supply on a PC board, or 2 1/2W/channel with 20V supply and Staver heat sink. The LM378 will provide 3.2W/channel with 22V supply and PC board plus Staver heat sinking. With poorly regulated supplies over 20V or with 16Ω load, the LM378 is the obvious choice as higher supply voltages are required to obtain high powers with 16Ω loads. Although no greater power is available than with 8Ω loads.

There is no reasonable  $P_D$  limit on the LM379 as we can dissipate nearly 20W with adequate practical heat sinking and 9.6W with minimal sink. Then  $V_{CC}$  is the limit, say 30V. That would put us off the graph on *Figure A-1* at about 5.5W/channel or at 3W/channel with 16Ω load. Even at 8Ω and 30V, package dissipation is only 11W, or 9.6W with 28V. The kicker is in the data sheet electrical characteristics under current limit; 1.5A typ when  $T_{TAB} = 25^\circ C$ . The tab is above  $25^\circ C$  when package dissipation is 9–11W. Still, this is a realistic test for high speed machine testing. In actual use, the current limit moves down to maybe 1.25A or even less. What does this mean? Consider an 8Ω load in power equation, and that 1–1.25A pk is 0.7–0.88A rms.

$$\begin{aligned}
 P &= I^2 R \\
 &= (0.7)^2 8 = (0.5) 8 \quad \text{or} \quad = (0.88)^2 8 = (0.77) 8 \\
 &= 4W \qquad \qquad \qquad = 6.2W
 \end{aligned}$$

Now we have the actual limits at  $P_{O(MAX)} = 4\text{--}6.2W$  at 8Ω or 8W at 16Ω. Trouble is we are limited to 5W at 28V, 8Ω or 5.5W at 30V, 8Ω and 4W at 16Ω by a 30V operating limit. Current limits could run higher than data sheet typicals; many do, in fact. Then we can get more than 4W/channel as a limit. Since this is a typical spec, there is no guarantee either way.

Note with interest that an LM377 with Staver V7-1 heat sink will deliver 3.2W/channel with 22V supply (but hold it close to 22V or use a LM378) and the LM379 will deliver 5W/channel with a 28V supply. The LM379 is the practical choice because it is easier and probably cheaper to heat sink, and there is more  $P_D$  headroom to allow for variations in supply voltage (very important). Also, the better the heat sink on the LM379, the lower the tab temperature, and the higher the operating current limit.

Beyond the limits discussed, the temperature or current limits operate, the peaks are clipped, the waveform remains at peak value for a longer portion of the input cycle, the rms  $P_O$  increases,  $P_D$  decreases, and rms power approaches peak power.

Here is a summary of the performance the customer may encounter.

TABLE A-1. Max  $P_O$  Before Clipping (8Ω Load)

Heat Sink =	PC BOARD (29°C/W)			PC BOARD + V7-1 (21°C/W)				13°C/W SINK		
$V_{CC}$ =	16	18	19	18	20	22	23	26	28	30
$P_O/CH$ =	1.5	2.2	1.4	2.2	2.5	3.2	1.9	4.3	5.0	5.5
	----- LM377 -----									
	----- LM378 -----									
	----- LM379 -----									

# LM143 Monolithic High Voltage Operational Amplifier Applications

National Semiconductor  
Application Note 127  
Sam Ochi  
John Flink  
April 1976



## INTRODUCTION

The LM143 is a general purpose, high voltage operational amplifier featuring  $\pm 40V$  maximum supply voltage operation, output swing to  $\pm 37V$ ,  $\pm 38V$  input common-mode range, input overvoltage protection up to  $\pm 40V$  and slew rate greater than  $2V/\mu s^*$ . Offset null capability plus low input bias and offset currents (8 nA and 1 nA respectively) minimize errors in both high and low source impedance applications. Due to isothermal symmetry of the chip layout, gain is constant for loads  $\geq 2 k\Omega$  at output levels to  $\pm 37V$ . Because of these features, the LM143 offers advantages not found in other general purpose op amps. The LM143 may, in fact, be used as an improved performance, plug-in replacement for the LM741 in most applications.

This paper describes the operation of the LM143 and presents applications which take advantage of its unique, high voltage capabilities. Obviously, other applications exist where the low input current and high slew rate of the LM143 are useful. (See AN-29 on the LM108). Application tips are included in the appendix to guide the user toward reliable, trouble-free operation.

## CIRCUIT DESCRIPTION

A simplified schematic of the LM143, shown in *Figure 1*, illustrates the basic circuit operation. The super- $\beta$  input transistors<sup>(1)</sup>, Q1 and Q2, are used as emitter followers to achieve low input bias currents. Although these devices exhibit  $\beta = 2000-5000$ , they inherently have a low collector-base breakdown voltage of about 4V. Therefore, active voltage clamps Q3 and Q4 protect Q1 and Q2 under all input conditions including common-

mode and differential overvoltage. Other NPNs in the circuit are representative of those found in standard IC op amps, ( $\beta \approx 200$ ,  $LV_{CEO} = 50-70V$ ).

The input stage differential amplifier Q7 and Q8 with large base width exhibit  $LV_{CEO} = 90V$  to  $110V$  and high  $BV_{EBO}$  so readily withstand input overvoltages. The total input stage collector current ( $I_1 = 80\mu A$ ) is made higher than in most op amps to improve slew rate. Emitter degeneration resistors, R10 and R11, reduce transconductance<sup>(2)</sup> to limit small signal bandwidth at 1 MHz for a phase margin of  $75^\circ$ . Q16 and Q17 function as active collector loads for Q7 and Q8 and provide differential to single-ended current conversion with full differential gain.

One of the highest breakdown voltages available in standard planar NPN processing is the collector-base,  $BV_{CBO}$  which is typically 90V to 120V. To make use of this high voltage capability in the active region, the second stage consists of a cascode (common emitter—common base pair) connection of Q21 and Q23. The internal voltage bias  $V_{B1}$ , shunts avalanche-induced leakage current away from the base of Q21, avoiding  $\beta$  multiplication as found in the  $LV_{CEO}$  mode. Q23 and emitter follower Q22 are internally biased at a low voltage so the  $BV_{CEO}$  mode is impossible. Frequency compensation is achieved with an internal, high voltage capacitor,  $C_C$ .

\*An externally compensated version of the LM143, the LM144, offers even higher slew rate in most applications. The LM144 is pin-for-pin compatible with the LM101A.

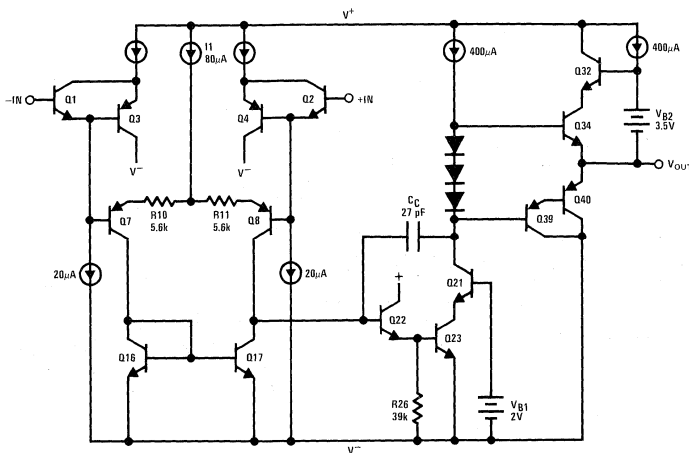


FIGURE 1. LM143 Simplified Schematic

The second stage drives a complementary class AB output stage. A cascode connection of Q32 and Q34 is again employed for high breakdown voltage. The associated voltage bias,  $V_{B2}$ , is internally derived. A Darlington PNP pair, Q39 and Q40 with  $BV_{CEO} = 100V$ , provides the active pull-down.

### HIGH VOLTAGE APPLICATIONS

The following applications make use of the high voltage capabilities of the LM143. As with most general purpose op amps, the power supplies should be adequately bypassed to ground with  $0.1\mu F$  capacitors.

#### 130 Vp-p Drive to a Floating Load

A circuit diagram using two LM143's to drive up to 130V peak-to-peak is given in Figure 2.

A non-inverting voltage amplifier, with a gain of  $A_V = 1 + (R_2/R_1)$ , is followed by a unity gain inverter. The load is applied across the outputs of A1 and A2. Therefore,  $V_{OUT} = V_1 - V_2 = V_1 - (-V_1) = 2V_1$ . If  $V_1 = 65$  Vp-p, then  $2V_1 = 130$  Vp-p.

The above circuit was breadboarded and the results are as follows:

- i) Maximum output voltage: 138 Vp-p unclipped into  $10\text{ k}\Omega$  load
- ii) Slew rate:  $6V/\mu s$

#### $\pm 34V$ Common-Mode Range Instrumentation Amplifier

An instrumentation amplifier with  $\pm 34V$  common-mode range, high input impedance and a gain of X1000 is shown in Figure 3.

For a differential input signal,  $V_{IN}$ , A1 and A2 act as non-inverting amplifiers of gain  $A_{V1} = 1 + (2R_1/R_2)$ , where  $R_1 = R_3$ . However, the gain is unity for common-

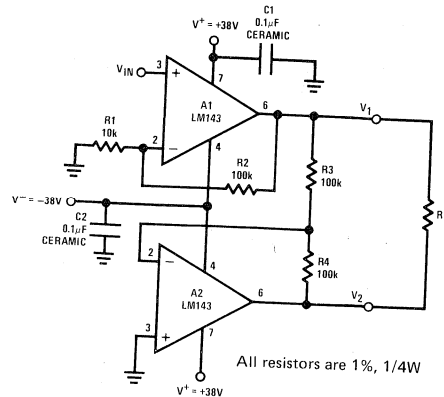


FIGURE 2. 130V Drive Across a Floating Load

mode signals since voltages  $V_1$  and  $V_2$  are in phase, and no current flow is developed through  $R_1$ ,  $R_2$  and  $R_3$ . The second stage is simply an op amp connected as a simple differential amplifier of gain,  $A_{V2} = (R_5/R_4)$ , where  $R_5 = R_7$  and  $R_4 = R_6$ . The total gain of the instrumentation amplifier is

$$A_V = \left(1 + \frac{2R_1}{R_2}\right) \left(\frac{R_5}{R_4}\right) = \left(1 + \frac{2 \times 100k}{22.22k}\right) \left(\frac{1.0M}{10k}\right) = 1000$$

$R_7$  may be adjusted to take up the resistance tolerances of  $R_4$ ,  $R_5$  and  $R_6$  for best common-mode rejection (CMR). Also,  $R_2$  may be made adjustable to vary the gain of the instrumentation amplifier without degrading the CMR.

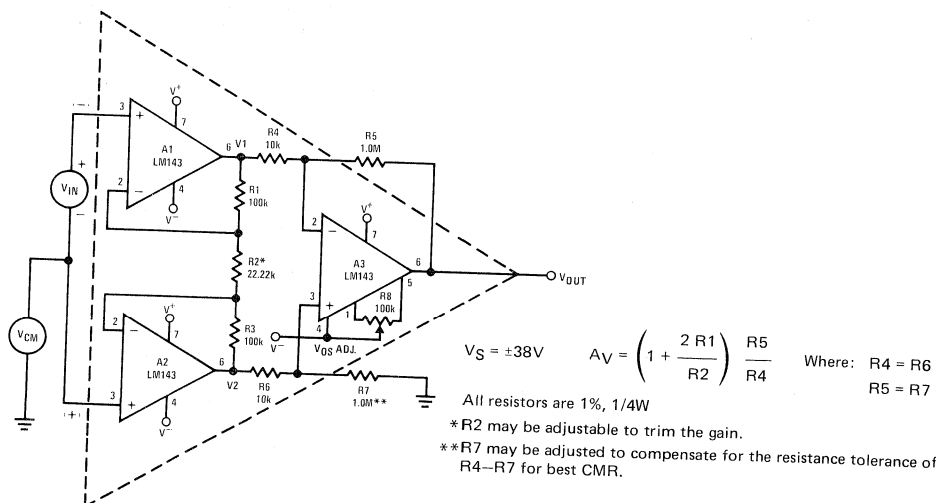


FIGURE 3. Wide Common-Mode Range Instrumentation Amplifier



Laboratory evaluation of this circuit revealed noise and CMR data as follows:

- i) Frequency response with 10k load and  $A_V = 1000$ :  
-3.0 dB at 8.9 kHz
- ii) CMR measurements (common-mode signal of  $\pm 34$  Vp-p) in *Figure 4*
- iii) Noise measurements in *Figure 5*

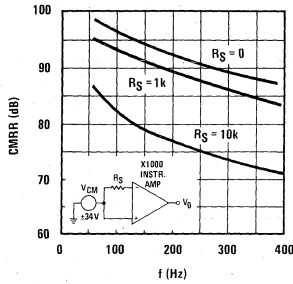


FIGURE 4. Common-Mode Rejection Measurements


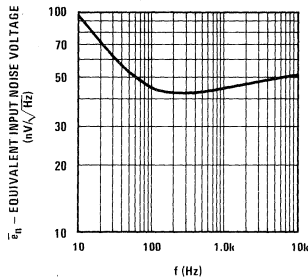


FIGURE 5. Noise Measurements
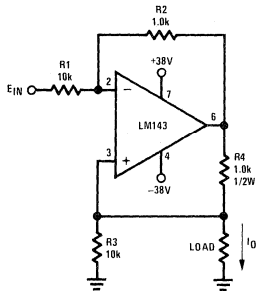
### High Compliance Current Source

A current source with a compliance of  $\pm 28$ V is shown in *Figure 6*.



All resistors 1% metal film, 1/4W unless otherwise specified.

FIGURE 6. High-Compliance Current Source

The non-inverting input of the op amp senses the current through R4 to establish an output current,  $I_O$  proportional to the input voltage. The expression for  $I_O$  is

$$I_O = - \frac{E_{IN} R_2}{R_1 R_4} = - \frac{0.1 \text{ mA}}{V} E_{IN}$$

R3 keeps the circuit stable under any value of load resistance. Measured circuit performance is as follows:

$$I_{O \text{ MAX}} = \pm 3.5 \text{ mA at } E_{IN} = \pm 35 \text{ V}$$

$$R_{O \text{ UT}} = 2 \text{ M}\Omega \text{ at } I_{O \text{ UT}} = \pm 2.0 \text{ mA}$$

### CURRENT BOOSTED APPLICATIONS

Because of the high voltage capability of the LM143, some thought must be given for the selection of the minimum load resistance. At an ambient temperature of 25°C, the LM143 can dissipate 680 mW. Worst case dissipation arises when the load resistance  $R_L$  is connected to one supply and  $V_O = 0$ . Then the amplifier sources  $I_O = (38\text{V}/R_L)$  with 38V internal voltage drop. During this condition,


$$P_{\text{MAX}} = 680 \text{ mW} = \frac{E_L^2}{R_L} = \frac{(38\text{V})^2}{R_L}$$

$$\text{or } R_L = \frac{1444\text{V}^2}{680 \text{ mW}} \approx 2.1 \text{ k}\Omega$$

Hence, load resistances less than 2k will cause excessive power dissipation.
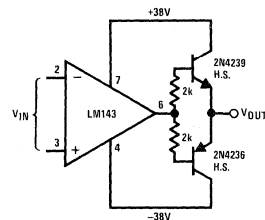
### Simple Power Boost Circuit

For loads less than 2 k $\Omega$ , a power boost circuit should be added. The simple booster shown in *Figure 7* has the advantage of minimal parts count, but crossover distortion is noticeable and there is no short circuit protection; hence, either the LM143 or the boost transistors may fail under short circuit conditions.



Heat sink is a Thermalloy No. 2230-5 or equivalent.


All resistors are 10%, 1W.

FIGURE 7. Simple Power Boost Circuit
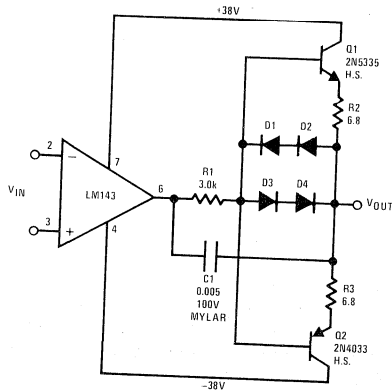
### 100 mA Current Boost Circuit

With the addition of 4 diodes, a resistor and a capacitor, the booster circuit can be short circuit protected at 100 mA as shown in *Figure 8*.

R1 protects the LM143 by limiting the maximum drive current to  $(38V/3.0k) \cong 12.5$  mA, thereby keeping



Heat sink is a Thermalloy No. 2230-5 or equivalent.

All diodes are 1N914.

All resistors are 1/2W, 10%.

FIGURE 8. 100 mA Current Boost Circuit

safely within the device dissipation limit of 680 mW. D1–D4 in conjunction with R2 and R3 protect the output transistors Q1 and Q2 by shunting the output drive current if the voltage drop across R2 or R3 exceeds 0.7V.


Breadboard Data:

- i) Frequency Response: Limited by LM143 frequency response and slew rate.
- ii) Step response for unity gain, voltage follower configuration: Less than 10% overshoot for 1.0V step with 0.01 $\mu$ F capacitive load, 50% overshoot with 0.47 $\mu$ F capacitive load. The circuit is unconditionally stable for capacitive loads.
- iii) Output Voltage:  $\pm 33$  Vp-p into 400 $\Omega$  load
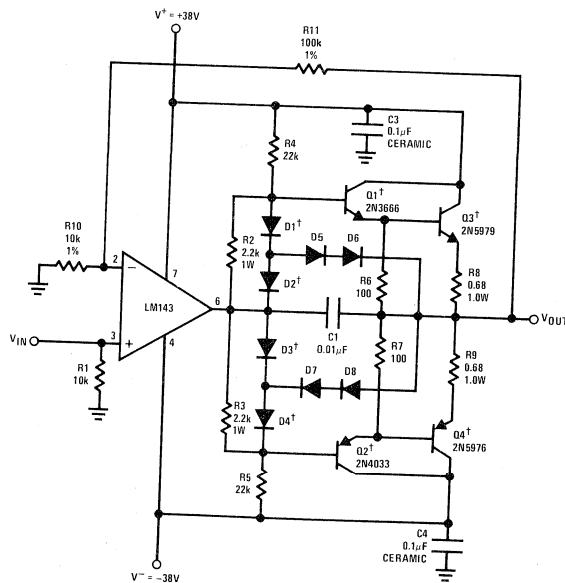
### 1.0 Amp Class AB Current Booster

If crossover distortion is objectionable and currents of up to 1.0A are needed, the circuit in *Figure 9* should be used.

The output of the LM143 drives a class AB complementary output stage. The quiescent current for the output stage is set by the current flow through R4, R5 and diodes D1–D4. The diodes D1–D4 are on a common heat sink with the output transistors Q3 and Q4 so that the voltage drops across the diodes and base-



†Put on common heat sink, Thermalloy 6006B or equivalent.

All diodes are 1N3193.

All resistors are 10%, 1/4W except as noted.

FIGURE 9. 1 Amp Class AB Current Booster with Short Circuit Protection

emitter junctions of the output transistors will track with temperature. Normally, R4 and R5 supply the current drive for the output Darlington's, Q1, Q3 and Q2, Q4, but if additional drive is needed, the LM143 supplies the remainder through R2 and R3. For short circuited load, the drive current is bypassed around the output transistors through D1, D5 and D6 during the positive half cycle and through D4, D7 and D8 during the negative half cycle. Drive current bypassing, or output current limiting, occurs whenever R8 or R9 sees more than one diode drop ( $\cong 0.7V$ ). An expression for the maximum output current is

$$I_{MAX} \cong \frac{0.7V}{0.68\Omega}$$

$$I_{MAX} \cong 1.0A.$$

Capacitor C1 stabilizes the circuit under most feedback and load conditions and C3 and C4 bypass the power supply. Measured performance is as follows:

- i) Maximum output voltage with  $R_L = 40\Omega$ : +29.6V, -28V with  $V_S = \pm 38$  VDC.
- ii) Harmonic distortion measurements of Figure 10 were measured with a closed loop gain of 10.


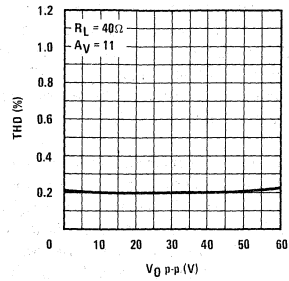


FIGURE 10. Harmonic Distortion Measurements
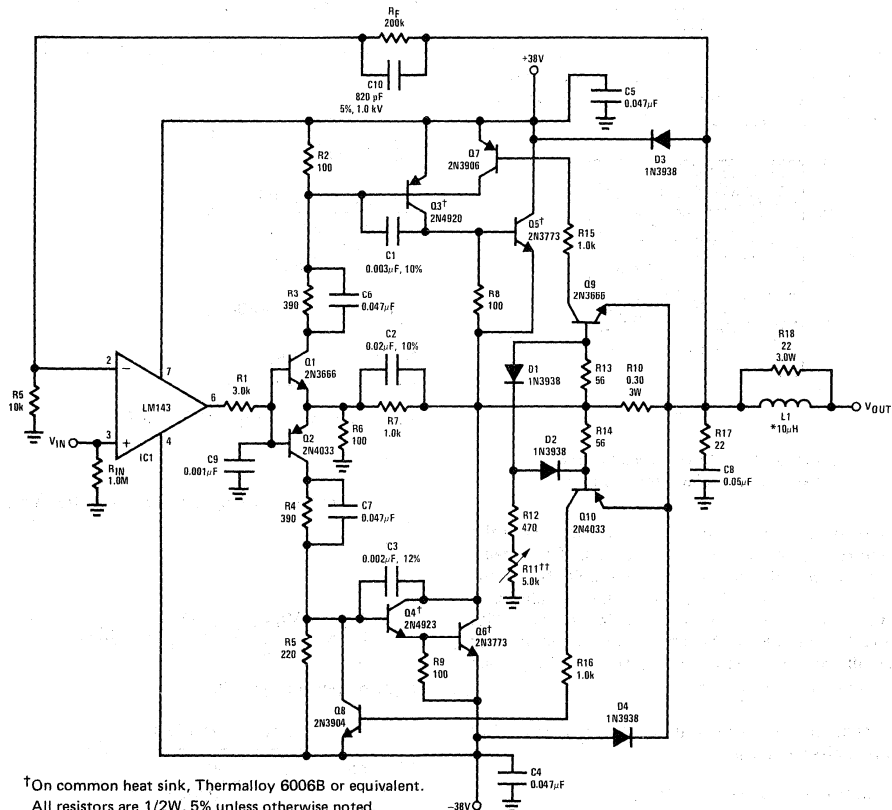
### Very High Current Booster with High Compliance

If very high peak drive current is required in addition to a capability for the output swing to within 4.0V of the supplies under full load, the circuit in Figure 11 should be used.



† On common heat sink, Thermalloy 6006B or equivalent.  
 All resistors are 1/2W, 5% unless otherwise noted.  
 All capacitors are 20%, 100V, ceramic disc unless otherwise noted.

†† Output current limit adjust.

FIGURE 11. Very High Current Booster with High Compliance

Excluding the LM143, the current booster has three stages. The first stage is made up of Q1 and Q2 which level shifts and boosts the current output of the LM143 to about 100 mA. Q3 and Q4 further boost the output of Q1 and Q2 to about 1.0A. Q5 and Q6 then have adequate drive to source and sink at least 10A. There is no quiescent current path when the output voltage is zero since Q1 and Q2 are biased off.

The short circuit protection circuit is made up of Q7 and Q9 on the positive side and Q8 and Q10 on the negative side. Q9 or Q10 turns on as soon as  $V_{BE} \cong 0.7V$  appears across R10 when the output terminal is shorted to ground. Then Q7 or Q8 bypass the drive to the output devices, Q5 and Q6. Since R10 is  $0.3\Omega$ , current limiting under short circuited output occurs at 2.3A and is relatively independent of the current limit adjustment resistor, R11. An expression for the maximum output current,  $I_{OUT MAX}$ , with  $V_{OUT}$  and R11 as variables is

$$|I_{OUT MAX}| \cong \frac{(|V_{OUT}| - V_{D1})R13}{R11 + R12 + R13} + V_{BE9}$$

$$\cong \frac{(|V_{OUT}| - 0.7)56\Omega}{R11 + 526\Omega} + 0.7V$$

$$\cong \frac{0.3\Omega}{0.3\Omega}$$

The equation is valid for both output polarities. The plot in Figure 12 superimposes the above equation on the maximum operating area curve for the 2N3773 and illustrates the safe area protection feature.

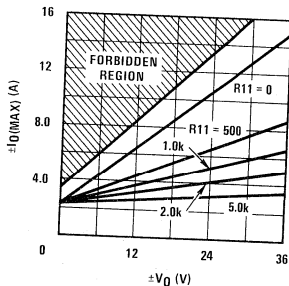


FIGURE 12. Maximum Output Current as a Function of R11 and  $V_{OUT}$

The diodes, D1 and D2, are in the circuit to keep the base-emitter junctions of Q9 and Q10 from being reversed biased during the opposite polarity output voltage swings. C1, C2, C3, C6, C7 and C9 are judiciously inserted in the circuit to prevent oscillation. R17, R18, C8 and L1 are used in the circuit to maintain stability under all load conditions. Diodes D3 and D4 provide protection for inductive loads.

All measurements taken with a  $4\Omega$  load and  $\pm 38V$  supplies unless otherwise stated:

- i) Maximum power out: 144 Wrms
- ii) Frequency response:
  - a)  $-3.0$  dB at 10 kHz at full power
  - b)  $-3.0$  dB at 11.5 kHz at 10 Vp-p out

- iii) Maximum output voltage:  $\pm 34V$
- iv) Maximum capacitive load:  $10\mu F$  with 10% overshoot for a small signal step response
- v) DC deadband:  $20\mu V$
- vi) Quiescent current: 12.7 mA (positive supply), 2.1 mA (negative supply)
- vii) Input impedance:  $1 M\Omega$
- viii) Voltage gain: 21

## HIGH POWER APPLICATIONS

### 90 Wrms Audio Power Amplifier

A circuit diagram of an audio power amplifier which is capable of 90 Wrms into a  $4\Omega$  speaker or 70 Wrms into an  $8\Omega$  speaker is given in Figure 13. The circuit features safe area, short circuit and overload protection, harmonic distortion less than 0.1% at 1.0 kHz, and an all NPN output stage.

The output of the LM143 drives a quasi-complementary output stage made up of Q1, Q2, Q3 and Q4. This quasi-complementary circuit, which makes possible an all NPN output, was chosen over the complementary output circuit due to the lack of low cost high voltage power PNP transistors.

Safe area current limiting occurs whenever the output current is

$$|I_{OUT MAX}| = \frac{(|V_{OUT}| - V_{D3})R11}{R11 + R13} + V_{BE5}$$

$$\frac{0.3\Omega}{R12}$$

where  $R11 = R15 = 330\Omega$ ,

$R13 = R14 = 3.9k$ ,

$R12 = R16 = 0.25\Omega$  and

$V_{BE5} \cong V_{BE6} \cong V_{D3} \cong V_{D4} \cong 0.7V$ .


If the output is shorted, the above equation simplifies to

$$I_{OUT MAX} = \frac{V_{BE5}}{R12} \cong \frac{0.7V}{0.25\Omega} = 2.8A$$

If the output voltage is 30V,

$$I_{OUT MAX} = \frac{(30V - 0.7V) 330}{4.23k} + 0.7V$$
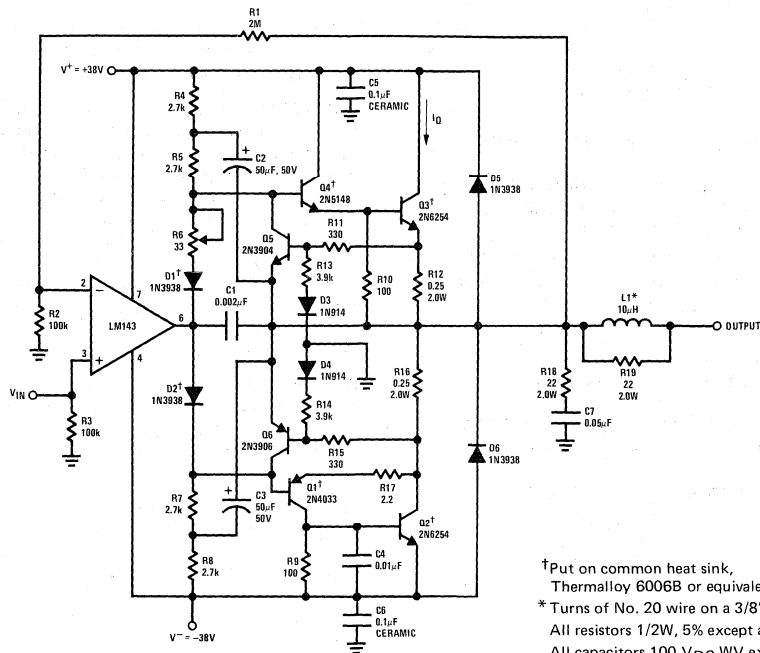
$$\cong \frac{0.25\Omega}{0.25\Omega} = 12A$$



†Put on common heat sink, Thermalloy 6006B or equivalent.  
 \* Turns of No. 20 wire on a 3/8" form.  
 All resistors 1/2W, 5% except as noted.  
 All capacitors 100 V<sub>DC</sub> WV except as noted.

FIGURE 13. 90W Audio Power Amplifier

The maximum output current,  $I_{O(MAX)}$ , versus  $V_O$  is plotted in Figure 14. D4 and D3 are in the circuit to keep Q5 off during the negative half of the output voltage cycle and Q6 off during the positive half cycle.

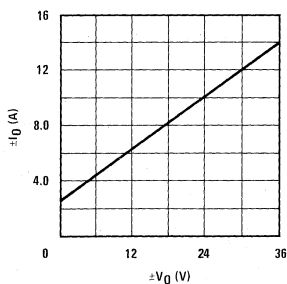


FIGURE 14. Output Current Limiting as a Function of Output Voltage

The output stage is biased into class AB operation by using the resistor string R4, R5, R7 and R8 to set the voltage drops across R6, D1 and D2, which then determine the quiescent current through the output transistors. These diodes are thermally coupled to the output devices to track their base-emitter junction voltages with temperature. Low distortion at low power levels is achieved by adjusting R6 to set the quiescent current through Q3 and Q2 to about 100 mA. Figure 15 shows a plot of distortion at 50 mW versus quiescent current.

C2 and C3 are connected between the output and the R4, R5 and R7, R8 junctions to provide a "bootstrapped" drive potential for the output stage during output voltage swings near the power supply potentials. The absolute magnitudes of the voltages at these junctions exceed the power supply voltages during the high output swings so that adequate current drives to Q4 and Q1 are available. C1 and C4 are used for compensating the output stage. C5 and C6 are used for power supply bypassing. R18, C7, R19 and L1 are included in the circuit to keep the amplifier stable under all load conditions. D5 and D6 provide protection for inductive loads.

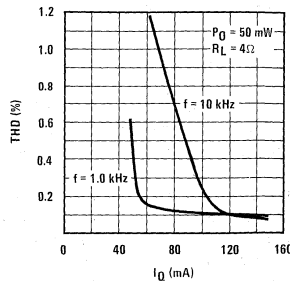


FIGURE 15. Quiescent Current vs Distortion

The input impedance of the audio amplifier is simply the value of R3. To keep the output offset voltages to a minimum,  $R3 \cong R1 \parallel R2$ . The voltage gain is

$$A_V = 1 + \frac{R1}{R2} = 1 + \frac{2.0M}{100k} = 21$$

The following data was taken with  $V_S = \pm 38V$ :

- i) Maximum power output before visible clipping:
  - a) 90 Wrms at 1.0 kHz into 4Ω load
  - b) 70 Wrms at 1.0 kHz into 8Ω load
- ii) Distortion measurement: distortion versus frequency and power is plotted in *Figures 16 and 17*.
- iii) Maximum capacitive load: 20μF
- iv) Output noise, 10 Hz to 20 kHz: 100μVrms
- v) Frequency response:
  - a) Small signal (1.0 Vrms into 4.0Ω): -3.0 dB at 40 kHz
  - b) Power (90W into 4Ω): -3.0 dB at 29 kHz
  - c) Power (70W into 8Ω): -3.0 dB at 30 kHz

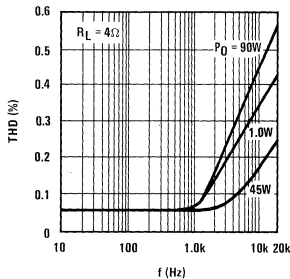


FIGURE 16. Distortion vs Frequency,  $R_L = 4\Omega$ .

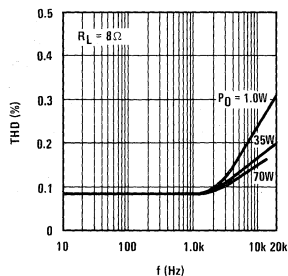


FIGURE 17. Distortion vs Frequency,  $R_L = 8\Omega$ .

## POWER SUPPLY CIRCUITS

The ability of the LM143 to withstand up to 80V can be exploited fully in the design of regulated power supplies. The circuits to be described use a zener reference voltage, an IC voltage amplifier, and a discrete power transistor pass element. If care is taken to keep the voltage drop across the pass element within 40V, standard three terminal voltage regulators such as the LM340, LM120, etc. may be used as pass elements and significantly decrease parts count and circuit complexity. Circuits using this approach are given in the LM340 application note (see AN-103).

## A Tracking ±65V Supply with 500 mA Output

A tracking power supply circuit can be made by modifying the circuit for the 130 Vp-p driver circuit. The modified circuit is given in *Figure 18*.

A 2N4275 is used as a stable zener voltage reference of about 6.5V. Its output is amplified from one to about 10 times by the circuitry associated with IC1. The output of IC1 is applied through R10 to the Darlington connected transistors, Q2 and Q3. The feedback resistor, R5, one end of which is connected to the  $V^+$  output node, is made variable so that the  $V^+$  output voltage will vary from 6.5V to about +65V. The  $V^+$  output is applied to a unity gain inverting power amplifier to generate the  $V^-$  output voltage. The output circuit of the unity gain inverter uses a composite PNP, Q4 and Q5, to provide the current boost.

Since the input terminals of A2 are at ground potential, the positive supply lead cannot be grounded; instead, it is connected to the output of a 4.7V zener diode, D8, to keep within the input common-mode range.

C1, C3 and C4 are used for decreasing the power supply noise. C2 is used in bypassing most of the noise generated by the reference voltage and C5 and C6 are used to reduce the voltage output noise. Short circuit protection is provided by D1, D2, D3, R10 and R14 on the positive side and by D4, D5, R11 and R15 on the negative side. The short circuit protection circuit is the same as the one used in the 1.0A current booster circuit.

The short circuit current is given by

$$I_{MAX} \cong \frac{V_{BE}}{R14} \cong \frac{V_{BE}}{R15}$$


$$\cong \frac{0.7}{0.56} = 1.25A$$

where  $V_{BE}$  = voltage drop across a diode.
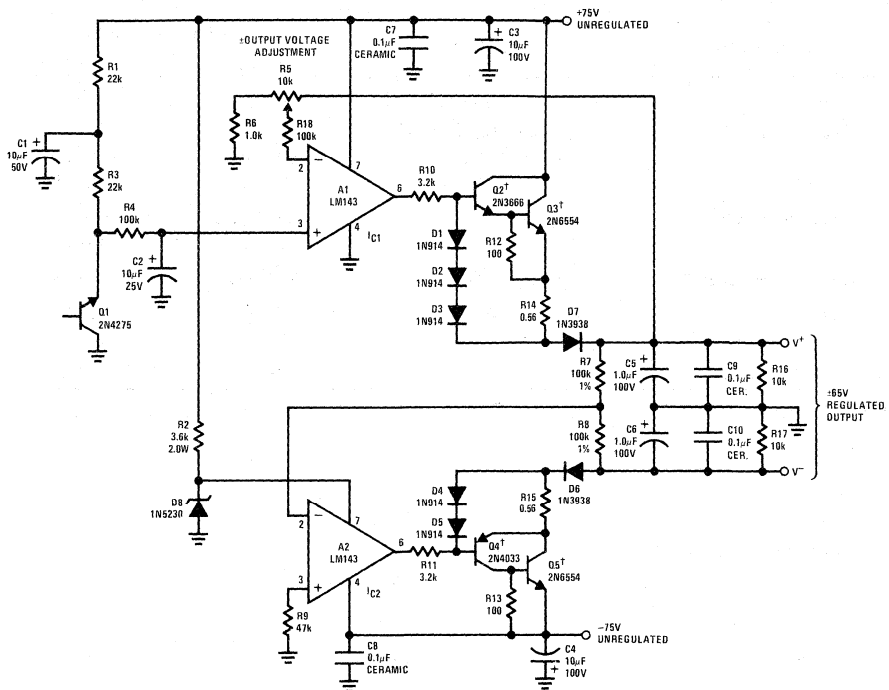
## +65V, 1.0A Power Supply with Continuously Variable Output Current and Voltage


If a continuously variable output current as well as output voltage supply is needed, a power supply circuit given in *Figure 19* will do the job. It has an output range from 7.1V to 65V with an adjustable output current range of 0 to 1.0A.

Basically, the power supply circuit is a non-ideal voltage source in series with a non-ideal current source. A reference voltage of approximately 6.5V is obtained by zenering the base-emitter junction of the 2N4275. The positive temperature coefficient of the zenering voltage is compensated by the negative temperature coefficient of the forward biased base-collector junction. The output of the voltage reference goes to the variable gain power amplifier made up of IC2, Q6, Q7 and their associated components and to a reference current source made up of Q2, D1 and components around them. The variable gain power amplifier multiplies the reference voltage from one to ten times due to the variable feedback resistor, R17. Since the maximum current output of IC2 is at most 20 mA, the Darlington connected Q6 and Q7 are used to boost the available output current to 500 mA.



†Put on common heat sink, Thermalloy 6006B or equivalent.  
 All resistors are 1/2W, 5%, except as noted.

FIGURE 18. Tracking 65V, 1A Power Supply with Short Circuit Protection

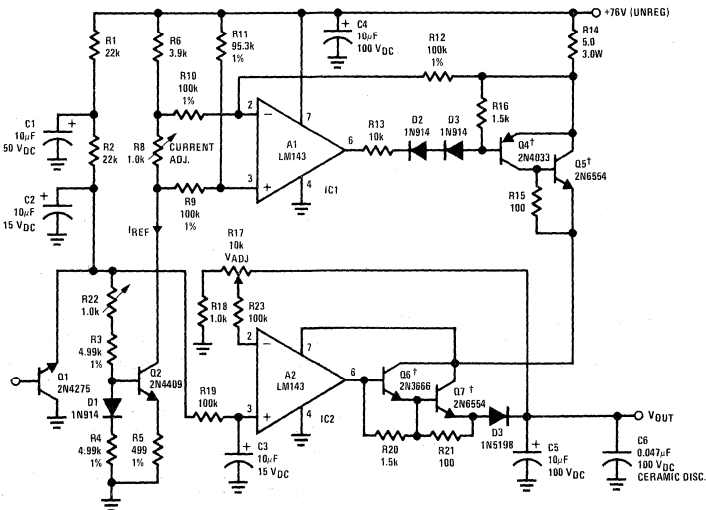

†Put on common heat sink, Thermalloy 6006B or equivalent.  
 All resistors 1/2W, 10% unless otherwise noted.  
 All capacitors 20%.

FIGURE 19. 1A, 65V Power Supply with Variable Current Limit

### Breadboard Data for the Tracking 65V Power Supply

$V_{IN} = \pm 75V$ ,  $I_{OUT} = \pm 500\text{ mA}$ ,  $T_j = 25^\circ\text{C}$ ,  $T_A = 25^\circ\text{C}$ ,  $V_{OUT} = \pm 40V$ , unless otherwise specified.

PARAMETER	CONDITIONS	MEASURED DATA	
		+V <sub>OUT</sub>	-V <sub>OUT</sub>
Load Regulation	$0 \leq I_{OUT} \leq 500\text{ mA}$	0.5 mV	1.0 mV
Line Regulation	$ \pm 50V  \leq V_{IN} \leq  \pm 80V $ $I_{OUT} = \pm 100\text{ mA}$ $I_{OUT} = \pm 500\text{ mA}$	175 mV	176 mV
		169 mV	173 mV
Quiescent Current	$I_{OUT} = 0$	Pos. Supply	Neg. Supply
		28.22 mA	6.55 mA
Output Noise Voltage*	$10\text{ Hz} \leq f \leq 100\text{ kHz}$	0.125 mV	0.135 mV
Ripple Rejection	$I_{OUT} = \pm 20\text{ mA}$ , $f = 120\text{ Hz}$	-72.5 dB	-63.4 dB
Output Voltage Drift*		3.38 mV/ $^\circ\text{C}$	3.43 mV/ $^\circ\text{C}$

\*The output noise and drift are due primarily to the zener reference.

### Measured Performance of the 1A, 65V Power Supply

$V_{IN} = +76V$ ,  $I_{OUT} = 500\text{ mA}$ ,  $T_j = 25^\circ\text{C}$ ,  $V_{OUT} = +40V$  unless otherwise specified

PARAMETER	CONDITIONS	MEASURED DATA
Load Regulation	$0 \leq I_{OUT} \leq 500\text{ mA}$ (Pulsed Load)	5.0 mV
Line Regulation	$46V \leq V_{IN} \leq 76V$ $I_{OUT} = 100\text{ mA}$ $I_{OUT} = 500\text{ mA}$ (dc Loads)	297 mV
		286 mV
Maximum Output Voltage	dc Load	68.6V
Quiescent Current		21.4 mA
Output Noise Voltage*	$10\text{ Hz} \leq f \leq 100\text{ kHz}$	0.280 mV
Ripple Rejection	$I_{OUT} = 20\text{ mA}$ $f = 120\text{ Hz}$ $\Delta V_S = 3.0\text{ Vp-p}$ $\Delta V_O = 6.0\text{ mVp-p}$	66.6 dB
Loads are Pulsed Loads	200 $\mu\text{s}$ Pulse Every 200 ms	

\*The output noise is due primarily to zener reference.

The power current source is an op amp used as a differential amplifier which senses the voltage drop across R8 and maintains this same voltage across R14. Hence, the maximum output current is

$$I_{OUT} = \frac{R8}{R14} \times I_{REF} \leq \frac{1.0\text{k}}{5.0\Omega} \times 5.0\text{ mA} = 1.0\text{A.}$$

Since the output load under most conditions will not demand what the power current source can deliver, Q4 and Q5 will remain in saturation during normal operation. When Q4 and Q5 are pulled out of saturation,

the output load voltage will drop until the load current just equals what is available from the power current source. Because the positive supply terminal of IC2 is tied to the collectors of Q4 and Q5, IC2 will supply just enough current drive to Q6 and Q7 to keep itself on. Hence, a current limiting resistor is unnecessary for IC2. A 10k current limiting resistor, R13, is present since the total unregulated power supply voltage is available for IC1. R6 is used to stay within the input common-mode voltage range of IC1.

$I_{REF}$  is derived from the 6.5V reference source, Q1, by using Q2 in a current source configuration. R22 is made adjustable so that  $I_{REF}$  can be set for 5.0 mA.



## CONCLUSION

The LM143 is a high performance operational amplifier suited for applications requiring supply voltages up to  $\pm 40V$ . The LM143 is especially useful in power supply circuits where the unregulated voltages are as high as  $\pm 40V$  and in amplifier circuits where output voltages greater than  $\pm 30V$  peak are needed. The LM143 is internally compensated and is pin-for-pin compatible with the LM741. Compared with the LM741, the LM143 exhibits an order of magnitude lower input bias currents, better than five times the slew rate and twice the output voltage swing.

## APPENDIX

Toward the goal of trouble-free applications, this appendix details some of the more subtle features of the LM143 and reviews application hints pertinent both to op amps in general and the LM143 in particular. The complete schematic of the LM143 is shown in Figure 20.

The circuit starts drawing supply current, at supply voltages of  $\pm 4V$ , when current is provided to a 7.5V

zener diode D5 by the collector FET Q41. The gate-channel junction of Q41 exhibits 100V breakdown as source and drain are lightly doped NPN collector and substrate material. The collector current of Q18 biases current sources Q25 through Q30 and sets the supply current at nearly zero TC.

Q19 furnishes a bias voltage, 5V above the negative supply, for the collectors of Q15, Q20 and Q22. The low impedance 2V reference ( $V_{B1}$  in Figure 1) for the base of Q21 appears at the emitter of Q20 and has the correct TC to insure that Q23 never saturates. Should this occur, the low resistance of Q23 would cause premature  $V_{CE0}$  breakdown of Q21.

The input transistors, Q1 and Q2, are biased by Q13 and Q14 which have a breakdown voltage essentially equal to  $BV_{CBO}$  by virtue of the high emitter impedance, R18 and R19, relative to the low dynamic impedance of D4. In a similar way, Q18 and Q19 stand off essentially the full supply voltage. These devices have a high output impedance caused by series feedback and so hold the supply current nearly constant to prevent excessive power dissipation at high supply voltages.

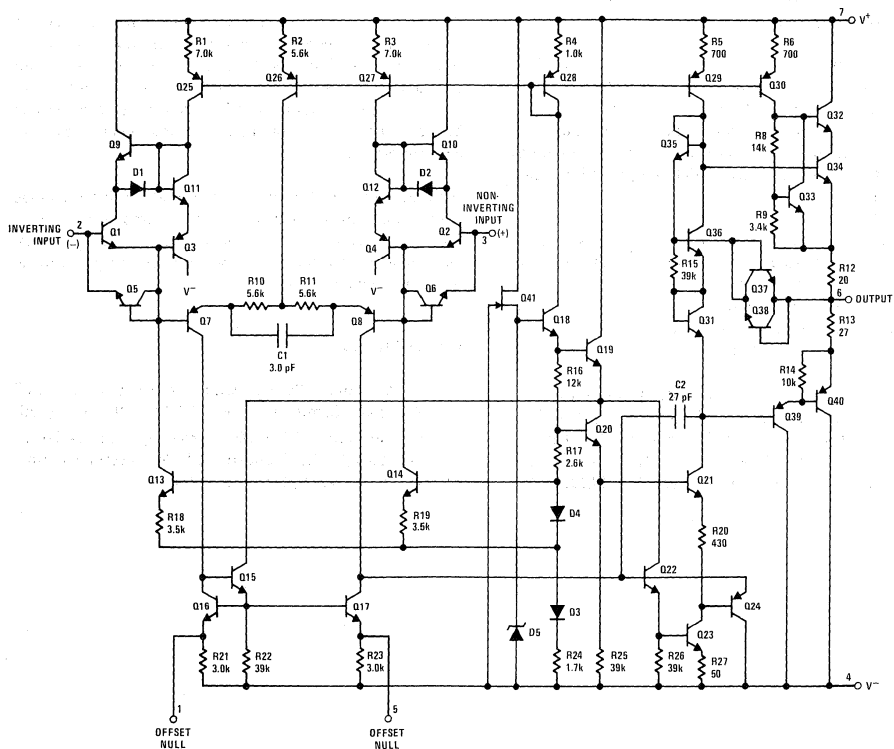


FIGURE 20. Complete Schematic of the LM143

While the simple voltage clamping scheme, Q3 and Q4 in *Figure 1*, is adequate, it is prone to oscillation when built with high  $\beta$  PNPs. The more elaborate scheme of *Figure 20* prevents instability. This clamping method is similar to that used in the LM108, but allows large differential inputs to exist with complete input over-voltage protection. Q9 and Q10, which withstand the high input common-mode voltage, have a  $BVCBO$ -type breakdown due to the low impedance diodes seen from the base leads and the high impedance of Q1 and Q2 (enhanced by 100% series feedback) in the emitter leads. Input overvoltage protection also holds up under high-level transient input voltages.

With a large negative-going step input, as could occur in the unity-gain voltage follower configuration, diode-connected Q6 turns "ON," protecting the emitter-base junction of Q2 from zener breakdown and subsequent long-term  $\beta$  degradation. At the same time, stray capacitance at the collector of Q2 is discharged by D2 through Q4 and Q12. This holds Q10 in a true  $BVCBO$  mode (emitter open-circuited) and clamps the voltage across Q2 to  $3 V_{BE}$ .

With a large positive-going step input, stray capacitance at the collectors of Q2 and Q12 is charged by the forward-biased collector junction of Q2. As before, with D2 conducting, Q10 is again in the  $BVCBO$  breakdown mode. Since the inverting input can be subject to the same transients, Q1 is afforded the same protection.

Distributed capacitance associated with R10 and R11, together with the collector-base capacitance of Q26, cause a high frequency transmission pole (the "tail" pole<sup>(2)</sup>) which can degrade phase margin. This is avoided by adding a small lead capacitor, C1, which provides an alternative low-impedance signal path, thus bypassing the tail pole.

The offset null resistors, R21 and R23, are made larger than that strictly necessary to null the offset voltage. This reduces the transconductance of Q17 and, therefore, the noise gain of the active loads into R10 and R11. By this simple expedient, broadband input noise voltage is substantially reduced.

The voltage reference for the output stage ( $V_{B2}$  in *Figure 1*) is realized by actively simulating a 4-diode stack. The voltage across Q33, given by  $(1 + R8/R9) V_{BE}$ , is about 3.5V. Biased at  $400\mu A$  from Q30, the circuit presents a low impedance, less than  $50\Omega$ , to the

base of Q32. Since the TC of the reference is negative, Q34 is designed to always remain out of saturation under worst-case conditions of high temperature and high output current. This avoids potential destructive breakdown of Q32.

Current limiting for Q32 and Q34 is provided by diode-connected Q37 and resistor R12. When the voltage drop across R12 turns on Q37, it removes base drive from Q34. In a similar fashion, current limiting in the negative direction is initiated when the voltage drop across R13 causes Q38 to conduct. This current is limited in Q21 by R20 to about 1 mA. When this occurs, base drive is removed from Q39.

Although output short circuits to ground or either supply can be sustained indefinitely at supply voltages lower than  $\pm 22V$ , short circuits should be of limited duration when operating at higher supply voltages. Units can be destroyed by any combination of high ambient temperature, high supply voltages, and high power dissipation which results in excessive die temperature. This is also true when driving low impedance or reactive loads or loads that can revert to low impedance; for example, the LM143 can drive most general purpose op amps outside of their maximum input voltage range, causing heavy current to flow and possibly destroying both devices.

Precautions should be taken to insure that the power supplies never become reversed in polarity—even under transient conditions. With reverse voltage, the IC will conduct excessive current, fusing the internal aluminum interconnects. As with all IC op amps, voltage reversal between the power supplies will almost always result in a destroyed unit.

Finally, caution should be exercised in high voltage applications as electrical shock hazards are present. Since the negative supply is connected to the case, users may inadvertently contact voltages equal to those across the power supplies.

## REFERENCES

1. R. J. Widlar, "Super Gain Transistors for ICs," National Semiconductor TP-11, March 1969.
2. J. E. Solomon, "The Monolithic Op Amp: A Tutorial Study," IEEE Journal of Solid-State Circuits, Vol. SC-9, No. 6, December 1974.

# A Linear Multiple Gain Controlled Amplifier

National Semiconductor  
Application Note 129  
Jim Sherwin  
August 1975



## INTRODUCTION

A linear control function over three decades of gain can be achieved with a FET in the feedback path of a non-inverting amplifier. Besides the ultimate simplicity of the circuit, multiple tracking gain control circuits can be constructed with dual op amps and monolithic dual FET's or quad op amps and monolithic quad FET's. Such circuits could even be integrated with ion-implanted FET's on single or multiple monolithic op amp chips. The gain control range may be designed for less than 2 to 1 or higher than 1000:1, but input voltage levels are limited by acceptable levels of distortion. Bandwidth is dependent on maximum gain and unity gain bandwidth of the op amp used. The gain control circuit is especially suitable for volume expansion applications.

## GAIN CONTROL WITH FETS

The FET has long been used as a voltage controlled resistor (VCR), often as the shunt arm in the series-shunt attenuator of *Figure 1*. Advantages of the FET as a VCR are that:

1. The control signal is almost perfectly isolated from the controlled signal path, and
2. The resistance can be made to vary over an almost infinite max/min ratio.

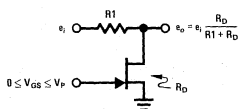


FIGURE 1. Voltage Controlled FET Attenuator

Disadvantages are that:

1. The FET behaves as a linear resistance only for small values of source-drain voltage  $V_{DS}$ ,
2. Non-linearity (of resistance) increases as the control voltage  $V_{GS}$  approaches cut-off voltage  $V_P$  when the resistance is maximum,
3. The relationship of resistance  $r_d$  to  $V_{GS}$  is reciprocal rather than direct linear,
4. VCR multiples with matched resistance characteristics over their full control range have been extremely difficult to obtain at any kind of reasonable price, and
5. Production spread in  $V_P$  requires separate bias set and gain set on each circuit.

Examination of the FET drain characteristics in *Figure 2* will reveal the essential non-linearity of  $r_d$  at high signal levels, especially as  $V_{GS}$  approaches  $V_P$ . This non-linear region must be avoided in order to achieve tolerable distortion levels. One obvious way is to limit  $V_{DS}$  to small values when  $r_d$  is high as suggested by *Figures 2c and 2d*, another is to utilize FET's with high  $V_P$  as suggested by reference to *Figures 2b and 2d*.

The reciprocal relationship of  $r_d$  and  $V_{GS}$  is an advantage, as it is precisely that which allows the linear control of gain in the circuit to be described. The availability of matched monolithic dual FET's such as the NSC 2N3958 (watch out for the matched pairs as their resistance match close to  $V_P$  may not be as good as that of the monolithic versions) make available low cost duals with very closely matched resistance characteristics over the full control range. There are even some monolithic quads available (such as the AM9709 series). The final problem of the production range of  $V_P$  can be much improved with ion-implant diffusion techniques whereby lot variation in  $V_P$  may be held to within a few tenths of one volt.

The gain control circuit is that of an ordinary non-inverting op amp with feedback. The usual circuit is modified in *Figure 3a* to include a FET as controlled resistor. The gain function is normal except that  $r_d$  replaces  $R2$  in the usual form.

$$A_V = 1 + \frac{R1}{r_d} \quad (1)$$

Now  $r_d$  can be equated to a control voltage  $V_C$  as follows:

$$r_d = r_o \frac{V_P}{V_P - V_{GS}} \quad (2)$$

Where:

$$r_o = r_d \Big|_{V_{GS} = 0}$$

$$r_d = r_o \frac{V_P}{V_C} \quad (3)$$

Where:

$$V_C = V_P - V_{GS}$$

The gain function is thus seen to be linear with  $V_C$ .

$$A_V = 1 + \frac{R1}{r_o} \frac{V_C}{V_P} \quad (4)$$

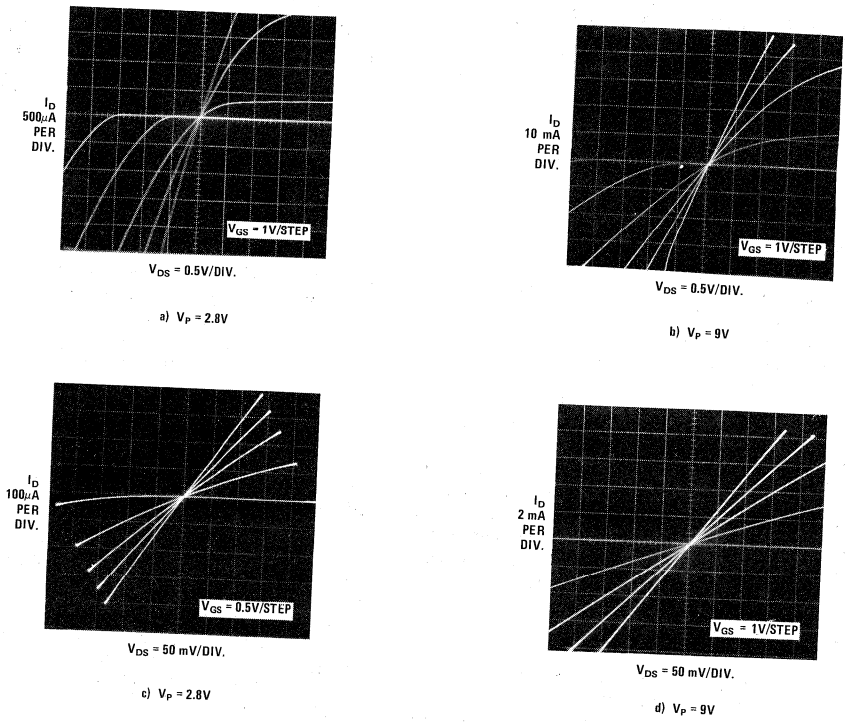


FIGURE 2. AC Output Characteristics of FET

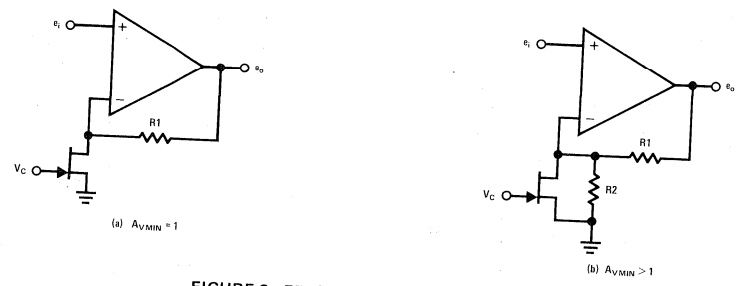


FIGURE 3. FET/Op Amp Gain Control Circuit

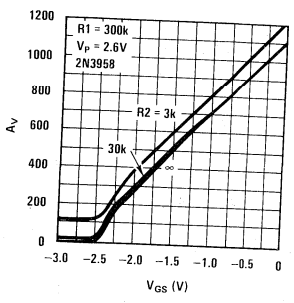


FIGURE 4. Gain vs Control Voltage For Short Channel FET

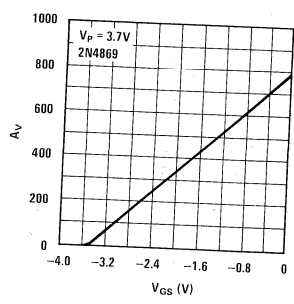


FIGURE 5. Gain vs Control Voltage For Long Channel FET

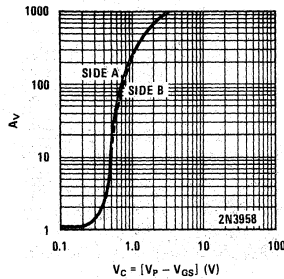


FIGURE 6. Control-Gain Match For Dual FET

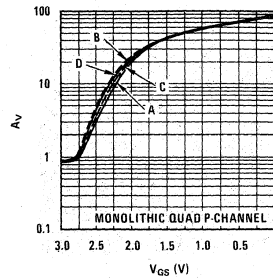


FIGURE 7. Monolithic Quad Gain Control Tracking

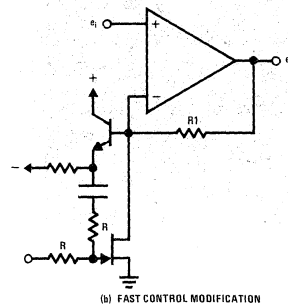
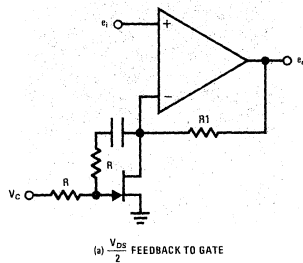


FIGURE 8. Circuit to Reduce Distortion

At  $V_C = 0$ , the gain reduces to unity; and at  $V_C = V_P$ , the gain increases to  $1 + R1/r_o$  which may be as high as 1000 or so. If it is desired to limit the minimum gain to some value greater than unity, another resistor  $R2$  may be added as in *Figure 3b*. Then the gain equation becomes:

$$A_V = 1 + \frac{R1}{R2 r_o (V_P/V_C)} \frac{R2 + r_o (V_P/V_C)}{R2 + r_o (V_P/V_C)}$$

$$= 1 + \frac{R1 [R2 + r_o (V_P/V_C)]}{R2 r_o (V_P/V_C)}$$

$$A_V = 1 + \frac{R1}{R2} + \frac{R1 V_C}{r_o V_P} \quad (5)$$

In either case, the gain function is linear with  $V_C$ .


The circuits of *Figure 3* do indeed show a linear gain versus control voltage as plotted in *Figure 4* for several values of minimum gain. There is some non-linearity near minimum gain which appears in all curves. This is certainly due to a non-ideal characteristic of the FET caused by finite contact and bulk resistance at source and drain. *Figure 5* shows a similar control curve for a FET with longer channel in which the controlled channel resistance is a greater part of the total resistance than that of the short channel device of *Figure 4*. For those applications requiring a more precisely linear control of gain, the long channel devices will be preferable.

Several variable-gain circuits can be made to track when monolithic multiple FET's are used as the control elements with matched feedback resistors. A monolithic FET dual (NSC 2N3958) used in two identical control circuits shows remarkable tracking over the entire control range, even when  $V_{GS}$  is near  $V_P$  where variations would be expected to be most apparent. The plots appear in *Figure 6*. Similar performance for a quad gain control using a monolithic P-channel quad FET (AM97C09 or AM97Q09) is shown in *Figure 7*.

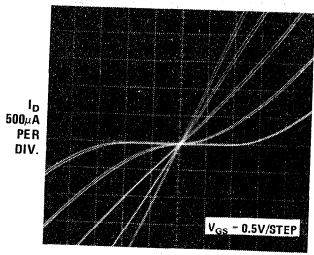
#### DISTORTION

Reference to *Figure 2* will show that the FET acts as a linear resistance only for relatively small values of drain-source voltage, in either polarity. This is particularly apparent for positive  $V_{DS}$  (for N-channel FET) and  $V_{GS}$  approaching  $V_P$ . The difference between *Figures 2c* and *2d* indicates that the maximum allowed applied signal will be greater for high  $V_P$  as compared with low  $V_P$ .


It is possible to improve the linearity characteristics somewhat by applying a part of the  $V_{DS}$  in series with the control voltage applied as  $V_{GS}$ . The circuit to accomplish this is that shown in *Figure 8*. It happens that about half of  $V_{DS}$  applied to the gate provides the greatest improvement for small signals. The addition of two resistors and one capacitor as in *Figure 8a* is all that is required. The capacitor simply blocks the control voltage from the FET drain and the op amp input. *Figure 8b* shows the addition of an emitter follower to




$V_{DS} = 0.5V/DIV.$   
a)  $V_P = 2.8V$

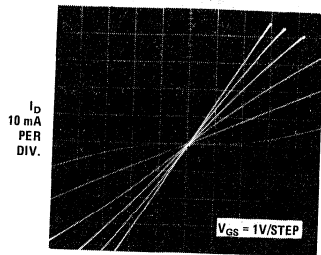

$V_{DS} = 0.5V/DIV.$   
b)  $V_P = 9V$

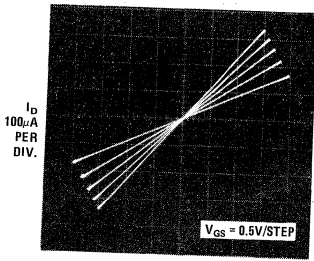

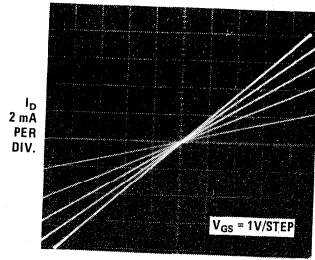$V_{DS} = 50 mV/DIV.$   
c)  $V_P = 2.8V$



$V_{DS} = 50 mV/DIV.$   
d)  $V_P = 9V$

FIGURE 9. AC Output Characteristics of FET with Feedback Linearization

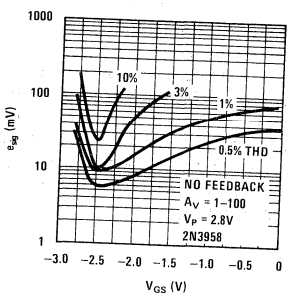


FIGURE 10. Distortion With  $V_P = 2.8V$

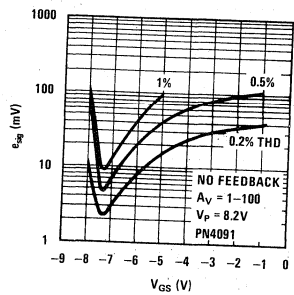


FIGURE 11. Distortion With  $V_P = 8.2V$

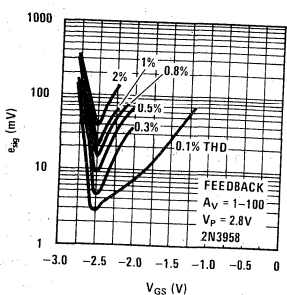


FIGURE 12. Distortion With  $V_P = 2.8V$ , With Linearization

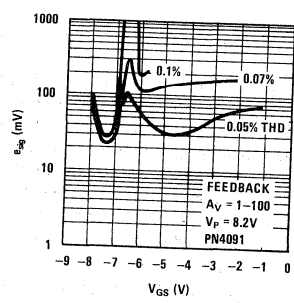


FIGURE 13. Distortion With  $V_P = 8.2V$ , Linearized

prevent abrupt changes in  $V_C$  from coupling to the op amp. Figure 9 shows the improved linearity of the drain characteristics as compared to Figure 2. The improvement is also seen in the distortion versus input signal plots of Figures 10–13. Note particularly that the distortion at any value of  $V_C$  is primarily a function of input signal (which equals the feedback signal applied to the FET drain at the inverting input). Some modification is made to this direct relationship if an R2 is shunted across the FET as in Figure 3b. Measured distortion at low signal level is the result of noise rather than of signal distortion. Maximum gain is limited to about 100 in these plots so as to avoid the region of lower S/N. The noise is that of the op amp input stage and the signal source resistance plus the contribution of the FET which is essentially the thermal noise of  $r_d$ .

### BANDWIDTH AND CONTROL TIME CONSTANT

The circuit bandwidth is the closed loop bandwidth of the op amp used at the (instantaneous) set gain. The gain control time constant is that of the input circuit to the FET (dependent on the value of R in Figure 8) limited by the slew rate of the op amp. The FET itself reacts practically instantly, producing a step change in feedback ratio. Control time constant is thus a few microseconds at most.

### APPLICATIONS

Three obvious applications present themselves; they are:

1. Remote or multichannel gain control
2. Volume expansion
3. Volume compression/limiting

To this short list might be added a number of others, including applications in noise reduction and quad sound techniques.

The gain-controlled amplifier of Figure 14 has a gain range of 1–1000, a maximum output level of 8.5 Vrms, and a bandwidth of better than 20 kHz at maximum gain. The FET used has high  $V_P$  for maximum freedom from distortion. Figures 15 and 16 show the gain function and constant distortion contour lines. Note that the gain control curve is non-linear near unity gain because the PN4091 is a short channel FET. Distortion

is quite low except as limited by maximum output voltage. Note that the maximum  $e_{in}$  is restricted by output saturation. The LM318 is used in the example only to achieve wideband response at maximum gain. The amplifier input voltage must be restricted to about 8 mVrms at maximum gain when the S/N will be about 60 dB over a 10 kHz bandwidth.

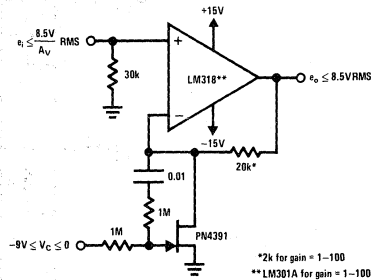


FIGURE 14. Amplifier With Gain Range = 1–1000

A more practical circuit might employ a gain range of 1–100. Then the amplifier could be a LM301A and still achieve a 10 kHz bandpass at maximum gain. The input signal could, accordingly, be increased to 80 mVrms for a S/N of 80 dB. This performance can be extended to dual and quad control circuits with tracking gain functions, but watch the bandwidth as required at maximum gain. Any of the several dual op amps could be used with the 2N3958 (monolithic dual from NSC), or the LM324 quad op amp can be used in limited gain times bandwidth applications with a quad monolithic FET. Figure 17 shows all details of an ac coupled tracking quad gain control with 40 dB range. Gain varies over 1–100 range, bandwidth is 10 kHz minimum, S/N is better than 70 dB with 4.3 Vrms maximum output. Figure 7 shows the gain curve and matching characteristics.

Noise considerations could be important in this method of gain control, as the signal is amplified rather than attenuated. To realize the function of a 40 dB variable attenuator, it is necessary to install a fixed attenuator at the amplifier input and perhaps also at the output. This will reduce the minimum signal level to millivolts, thus a low noise amplifier is desirable. The LM381 dual low-noise ac coupled amplifier could be used in a 40 dB

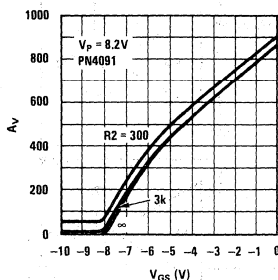


FIGURE 15. Gain For Circuit of Figure 14

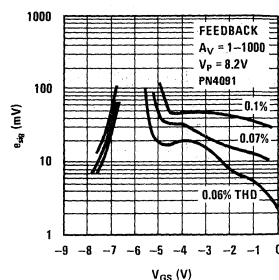


FIGURE 16. Distortion For Circuit of Figure 14

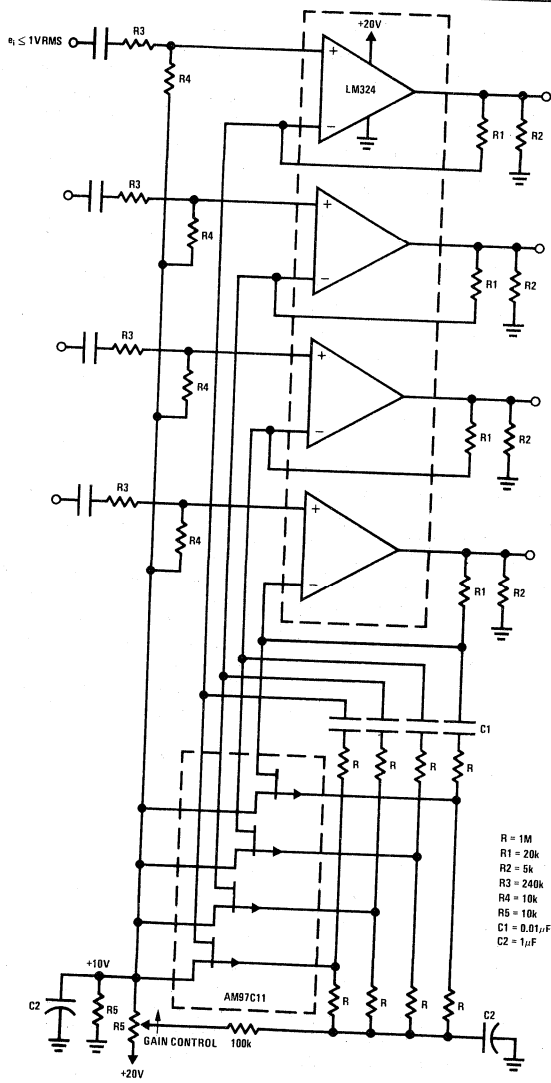


FIGURE 17. Quad Gain Control

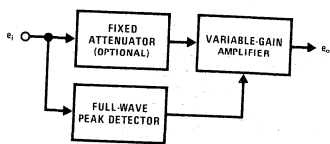


FIGURE 18. Volume Expander/Compressor Block Diagram

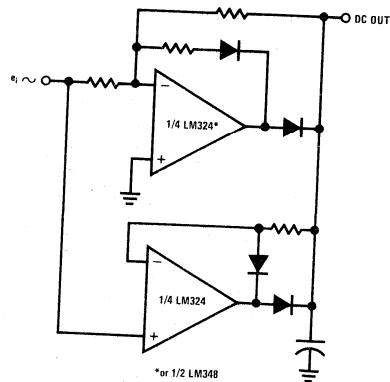


FIGURE 19. Full Wave Linear Precision Peak Detector



audio attenuator to realize S/N about 100 dB or in a 60 dB attenuator to realize 80 dB S/N. Improvements in S/N can be made by reducing system bandwidth in fixed or low frequency operation. Minimum noise is also achieved by using the minimum practical amplifier source resistance. Values as low as 1 k $\Omega$  are advantageous.

The effect of temperature will be to change the gain according to the temperature sensitivity of the FET. This effect can be reduced by using a silicon resistor for the feedback resistor, R1. If the FET were to be integrated onto the op amp chip, an attempt should be made to include R1 on the chip as well.

The application to a volume expander circuit is of interest as the control is linear, the required control range is only about 1:4, and the input signal is small for the low gain condition when distortion would otherwise be most apparent. The elements of a volume expander are indicated in Figure 18. The gain controlled amplifier need only exhibit a 12 dB variation in gain, being lowest for small signals. The slope of gain versus control should be linear, more specifically the slope of (log) gain in dB versus (log) signal in dB should be linear. A practical range is 12 dB gain change over a 30 dB input signal range. The peak detector should be linear down to very small signals, exhibit a fast attack or charge time of a millisecond or less, a discharge time constant of about 2 seconds, and operate on the first

half cycle (full-wave detector). The detector should, therefore, be a full-wave precision linear peak detector with low internal impedance; the requirements can be met with the circuit of Figure 19.

The expander circuit shown in Figure 20 will perform as desired. The gain control function is plotted in Figure 21; distortion is below 0.1% at all levels. Resistors R3 and R4 are added in order to modify the linear control curve to the desired log curve. Note that the input signal is attenuated prior to amplification in order to reduce distortion and maintain an overall gain of approximately 0 dB at midrange of expansion. The noise with the LM124 over a 20 kHz bandwidth is, of course, a function of signal; but the maximum signal to noise ratio is 80 dB. The circuit could be adapted to stereo or quad sound as in Figures 22-23. Questions for individual design concern the method of control. Whether to expand all channels together, and whether to derive the control signals individually from each channel, a summation from 2 to 4 channels, or from a single channel (assuming that high level from any channel indicates high levels from all channels). Note that the FET is biased OFF (minimum gain) for low signals, and increasing signals progressively bias the FET ON (maximum gain).

The volume compression circuit is a logical mate to the expander. The only difference would be that the FET is initially biased ON (maximum gain) for low signals, and

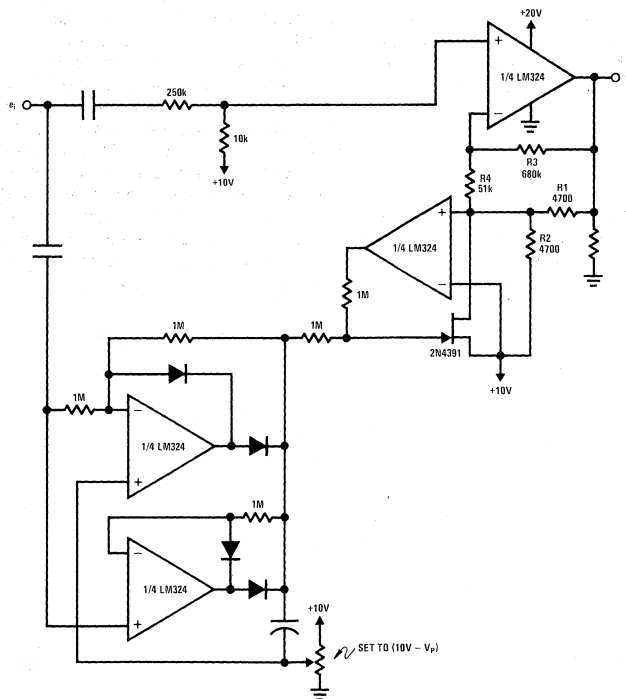


FIGURE 20. Volume Expander Circuit

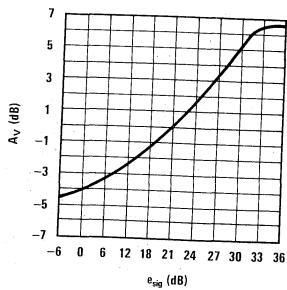


FIGURE 21. Expander Gain Characteristic

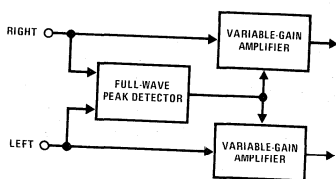


FIGURE 22. Stereo Expander Block

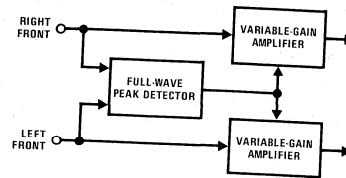


FIGURE 23. Four-Channel Expander Block

increasing signals progressively bias the FET OFF (minimum gain). A disadvantage is that the circuit produces greatest distortion in the low gain condition when signals are highest. Maximum S/N is degraded by 24 dB over that of the expander, minimum S/N is the same.

## CONCLUSION

The combination of FET and op amp provides a linear dc (voltage) control of gain over a range to 60 dB. As the circuit realizes positive gain, rather than being a controlled attenuator, the input signal is limited. Input

signal is further limited to several hundred millivolts by the non-linearity of the FET (which sees the full input signal). Because input signals will generally be in the 10–300 mV range, noise performance of the selected op amp will be important. Even so, S/N of 60–100 dB is obtainable with standard amplifiers. Tracking pair or quad gain-control amplifiers are realizable with existing monolithic dual or quad FET's, and the combination of FET and op amp lends itself to simple integration. The circuit is well-suited to remote and multiple linear gain control and to volume expander/compressors. The volume expander is especially interesting as the signal level and gain conditions result in extremely low distortion and more than adequate signal-to-noise ratio.

# The Monolithic Temperature Transducer — A New Interfacing Concept

National Semiconductor  
Application Note 132  
Peter Lefferts  
December 1974



AN-132 The Monolithic Temperature Transducer — A New Interfacing Concept

## INTRODUCTION

The percentage of analog and analog/digital signal handling done by monolithic integrated circuits is ever increasing. However, until now almost all input signals were voltages generated by often complex and expensive transducers needing special input wiring to the integrated circuit.

Now with the ability of an IC to *directly* sense absolute temperature, and provide a linear, buffered electrical output, the situation has greatly changed. A number of physical parameters can now be sensed directly by the National LX5600 monolithic transducer with a resulting saving in hardware, wiring, and therefore cost.

For example, using temperature sensing as an "interface"; position, air velocity, liquid presence, and conductivity can be measured or controlled. Rate of temperature change can be sensed to improve the performance of on-off temperature controllers. The monolithic transducer allows a much simplified servo for improving surface or moving-surface temperature measurements. The purpose of this note is to illustrate the possibility and practicality of a number of these sensing techniques.

As background for the rest of this note, the block diagram and operation of the thermometer will be briefly described. Also methods of powering the LX5600 will be outlined, and a special integrated power transistor ideal for isolating the thermometer from heavy or variable loads will be presented.

## TRANSDUCER DESIGN

Figure 1 illustrates how the 3 separate functions of the thermometer IC are arranged so that only 4 external

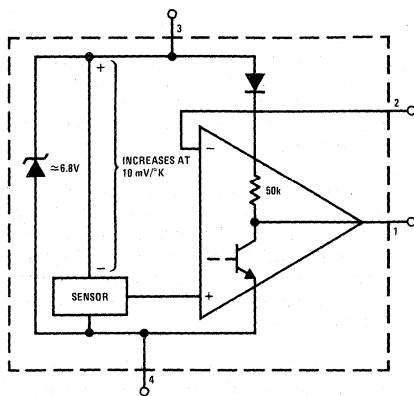


FIGURE 1. Block Diagram

connections are needed. The zener and its amplifier form a shunt regulator with a typical impedance of  $3\Omega$ . The reference is quite stable with temperature so that a potentiometer across pins 3 and 4 can be used to set up a Centigrade or Fahrenheit zero calibration. This would be used when the thermometer is applied in its linear mode, such as with pins 1 and 2 shorted together so that the op amp forms a unity gain follower.

Similarly a pot across 3 and 4 with the wiper to pin 2 determines a temperature set-point since the op amp can be operated "open loop," which will cause the output at pin 1 to swing about 30V for a  $0.2^\circ\text{C}$  (or Kelvin) change at the sensor around the set point.

The sensor section, with its associated amplifier, generates a negative going signal of  $10\text{ mV}/^\circ\text{K}$ . For instance, at  $0^\circ\text{C}$  this signal would be  $-2.73\text{V}$  (with respect to pin 3) and appear at the plus terminal of the internal operational amplifier. The actual sensor principle is somewhat more sophisticated than a resistance or diode-drop change with temperature. It uses the difference in  $V_{be}$  between matched transistors which involves operating two transistors at greatly differing collector currents but with their bases in parallel. If this collector current ratio is controlled there will be a very predictable difference of emitter voltage. Further, this voltage varies with temperature in a known and reproducible manner. This voltage change is less dependent on processing variations than any of the other known semiconductor effects. Further details on these effects can be found in the reference. (1)

The internal op amp provides a consistent, very light loading of the sensor output. Having a feedback terminal available, gains from unity up to 100 or so are feedback controllable, or an open-loop gain of several thousand is available. PNP input transistors allow the op amp to function as a comparator over a large range of inputs. Internal compensation is provided. Output is a collector with a 50k load (pull-up) resistor provided, that is, however diode decoupled for output voltages higher than the pin 3 supply voltage. A complete schematic of the transducer is provided in the appendix.

## POWERING THE TRANSDUCER

Successful application of the LX5600 starts with providing power in the optimum way. Since the device senses its own temperature, it follows that minimum internal power dissipation is desirable. With no output load, the internal electronics (op amp, etc.) typically need about  $1/2\text{ mA}$  to operate correctly. If the zener shunt regulator is to operate also,  $1\text{ mA}$  is recommended. Let us examine the four powering methods of Figure 2 with regard to zener operation and temperature rise. Still air operation, a 6.8V zener, and  $0.17^\circ\text{C}/\text{mW}$  temperature rise for a TO-5 package are assumed for the following discussion.

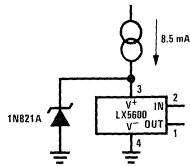


FIGURE 2a. Constant Voltage Mode

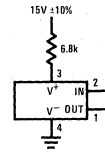


FIGURE 2b. Dropping Resistor Method

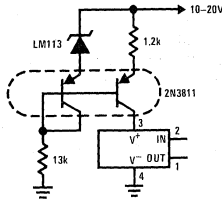


FIGURE 2c. Precision Current Source

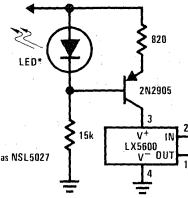


FIGURE 2d. Low Cost Current Source

FIGURE 2. Powering the Monolithic Transducer

Figure 2a illustrates minimum device dissipation by sacrificing use of the internal reference. A typical unit would self-heat only about  $0.5^{\circ}\text{C}$  and would vary only about  $0.1^{\circ}\text{C}$  over supply and temperature variations. This connection is particularly useful for accurate air temperature measurements and is very suitable for differential measurements where a second transducer can supply the reference.

The simplest method is Figure 2b using only a resistor. With the supply variations shown, the reference typically varies less than 1 mV. The temperature rise is only about  $1.25^{\circ}\text{C}$  with plus or minus about a quarter degree for supply variations. With a modestly-regulated supply, the resistor powering method obviously becomes very good. However, if one considers an aging automotive battery with a loaded output of only 11V available, a 3.9k resistor would be needed to insure 1 mA of current. Then the same battery being heavily charged ( $15\text{ V}_{\text{DC}}$ ) would supply twice the current to the thermometer with an increase of self-heating of about  $1.2^{\circ}\text{C}$ .

One of the applications to follow involves reading outside air temperature. Since most people are accustomed to reading temperature in  $^{\circ}\text{F}$ , the over  $2^{\circ}\text{F}$  error of the above example will be noticeable. The two constant current supplies to be described solve this problem. Total change in self-heating becomes well less than  $0.1^{\circ}\text{F}$  over a  $100^{\circ}\text{C}$  temperature range and a 2:1 supply voltage range. Further, the internal reference is properly powered, with current changes causing less than 1 mV change in  $V_z$ .

The reference current source of Figure 2c uses the precision 1.22V reference diode which changes only about 1% over the entire  $-55^{\circ}\text{C}$  to  $+125^{\circ}\text{C}$  temperature range. A diode-connected transistor, temperature compensates the constant current transistor so almost exactly the reference voltage appears also across the emitter resistor, stabilizing the current.

The source of Figure 2c is probably of greater cost and precision than is needed in this application. The Figure 2d current source is much less expensive and yet reasonably stable. With only about a volt needed between power input and collector output, it is much superior

to the usual zener referenced current source requiring 5 to 6V of such loss.

A little used characteristic of light emitting diodes is employed in stabilizing this current source. At the low currents used, the LED has a typical drop of 1.5 to 1.7V, or about 0.8 to 1V more than the junction drop of a small transistor. Thus, when paired as shown in Figure 2d the remaining voltage appears across the transistor's emitter resistor. Further this voltage is temperature stable since the LED's junction temperature coefficient is just about the same as a transistor's base-emitter junction coefficient. In both cases this is about  $-2\text{ mV}/^{\circ}\text{C}$ . Preliminary tests indicate that adjustments of the temperature coefficient can be made by changing the ratios of transistor to LED current, and that once a stable combination is found similar parts (same part number and same process) should reproduce the stability obtained within 1 or 2%, over the  $-55^{\circ}\text{C}$  to  $100^{\circ}\text{C}$  range. Doubling LED current only results in approximately 40 mV increased junction drop, so a 2:1 supply change will only result in a 5% further current change.

#### OPTIMUM LOAD ISOLATION

The need to minimize power dissipation has already been emphasized. In fact the previous heat rise figures were based on zero load on the thermometer's output transistor. Certain of the applications to be presented involve driving of lamps, solenoids, or heaters. Much would be lost in simplicity if the thermometer had to drive a buffer amplifier followed by two or more cascaded power transistors.

To solve this problem the LM195/LM395 monolithic power transistor is used. An ampere of load current may be handled requiring only a few microamperes drive from the monolithic thermometer. Under this condition, power dissipation due to the thermometer's output signal can be as little as 1% of the total device dissipation, and thus be negligible in causing temperature error.

The block diagram of Figure 3 shows how this very high gain is achieved. Integrated on the same chip as the power transistor is an NPN emitter follower driver which is driven by another PNP emitter follower. The

emitter-base drops of these two drivers are in the opposite direction, and tend to substantially cancel. Remaining is the emitter-base drop of the power transistor so input signals seem to see a power transistor of normal input voltage but abnormal current gain resulting from the three transistor cascade. Further, the input resistor and integrated PNP transistor allow +40V and -20V overdrives to the base without damage.

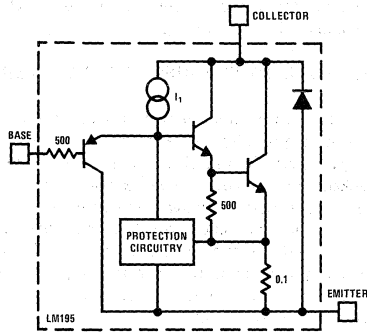


FIGURE 3. Simplified Circuit of the LM195

Reliability under adverse environments is enhanced by other protective circuitry that has been integrated in with this transistor. Collector current is limited to 2 amperes by sensing drop across the 0.1Ω emitter resistor internally. Junction temperature is limited by turning off the output transistor at 170°C junction temperature, using an internal temperature sensor. Thus the LM195 is extremely difficult to destroy except by exceeding collector voltage from a low impedance supply. (2)

#### APPLICATIONS AREAS

Applications areas will be covered in two sections. First, in the obvious area of temperature sensing and control, several uses with different types of output signals will be illustrated. Then some other sensing functions will be covered. All circuits shown have been breadboarded and are functional, but have not been given field testing at this time.

When a 15V supply is shown, the circuit is assumed a lab or instrumentation application. When a supply varying from 11V to 15V is shown, it is intended that this represent a 12V automotive battery or similar unregulated supply. The circuit has then been tested over a range of 10V to 16V, without significant degradation of performance.

#### TELEMETRY INTERFACE

Various pieces of mobile test equipment such as instrumentation recorders or telemetry subcarrier VCOs operate best with a calibrated 0 to +5V input. In some cases a low output impedance is also helpful. The LX5600, for certain design reasons, indicates increasing temperature by a negative going voltage with respect to the positive supply pin. Thus the thermometer's output must be inverted, level shifted, and given an extra voltage gain of 4 to provide the illustrated output.

Figure 4 provides the methods of doing this. Q1 supplies the thermometer with a constant current as previously described. The output transistor, Q2, provides the inverting function and requires very little base drive, holding down transducer dissipation. The entire system now requires dc feedback around it to stabilize gain (and thus the full scale calibration) and to eliminate supply and base-emitter voltage variations from the output. Feedback to pin 2 of the transducer is shown (by Figure 1) to be the "minus" input to an operational amplifier within the transducer. Thus the output signal needs to be reinverted by the LM201A operational amplifier.

The system has an open loop gain of 5,000 to 10,000, so the attenuation of the output signal that is fed back negatively determines closed loop gain. The reinverting op amp actually has an attenuation of 0.27. The 250Ω pot in the output divider is thus the full-scale adjust and trims the attenuation to 0.25, or a gain of 4. Pin 3 of the transducer provides the voltage reference for the zero adjust divider. At the calibration point of 0°C, the LM201A output must be at a nominal 2.73V below pin 3 of the transducer. Since voltages at both ends of the 30k, 110k network are known at 0°C, it is easy to predict the voltage adjustment at pin 3 of the LM201A required to fulfill this condition.

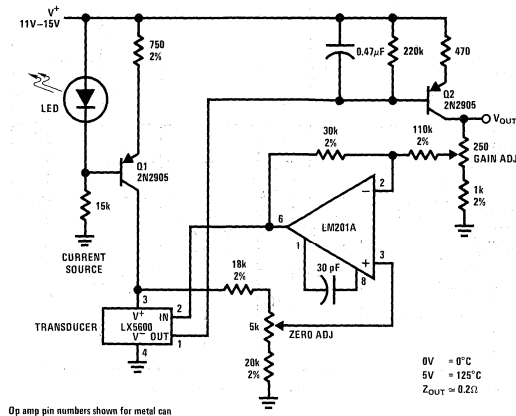


FIGURE 4. Telemetry Interface

The 0.47 $\mu$ F capacitor loading the transducer's output is required for stability against oscillations. The system has a very long feedback loop (3 different amplifiers), thus it is extremely easy for the total phase shifts to become 180° at a relatively low frequency. The large capacitor lowers overall gain to less than one at a frequency much less than this. There is no adverse effect on performance since temperature is such a slow moving parameter.

By design, the full-scale adjust has no effect when V<sub>OUT</sub> is at zero. This means that if zero is calibrated first, and full-scale second, the controls are non-interacting. Calibrating to 4V out, at boiling water temperature may be convenient. The unit we calibrated exhibited a 0.1% independent linearity up to 100°C, and less than 2 mV output change (1/20°C) with a 4V supply change. One little trick is needed for exact zero calibration. Due to loading by the op amp network, a temporary bias of about 0.1 mA is needed at the full-scale pot wiper to read a true zero out. The minus current can be temporarily provided by a 100k resistor and 9V "transistor battery." Obviously, other calibrating points can be chosen, and other ranges can be obtained by changing the different resistor networks.

A few precautions may be needed. For maximum accuracy three of the ground points should be common, or brought to the same point with separate wires. These points are the bottoms of the two dividers, and pin 4 of the thermometer. The others are less critical. If long wires, or a noisy supply is anticipated the V<sup>+</sup> pin (pin 7) of the LM201A should be bypassed. Since the V<sup>-</sup> pin of the op amp is at ground, resistor networks for other

ranges must be such that none of the input or outputs have to go closer than 2V to ground (3V under coldest conditions).

For the purposes of this and other circuits discussed, resistors are all 1/2 watt unless noted, and have the following characteristics. One percent resistors should be high stability metal film or wire wound types (e.g., 50 ppm/°C). Resistors marked 2% can be lower cost medium stability types such as tin oxide. Others can be standard 5% carbon types.

### TEMPERATURE TO FREQUENCY CONVERTER

For test data transmission, or to interface conveniently with existing digital displays, a proportional frequency signal may be desirable. In trying to determine the lowest cost package for an automotive exterior temperature indicator, a novel system evolved. It was obvious that a simple circuit in the same protective enclosure as the transducer would minimize cost and wiring. If the single positive supply wire could be made to carry the output signal frequency, it would represent an irreducible minimum cost to hook up.

The above aim was achieved using only the transducer, a very low cost IC (array), a few external parts, and a single supply/output wire. During the short negative output pulses on the supply wire, an internal 22 $\mu$ F capacitor keeps the converter electronics running. Pulse repetition rate is directly proportional to absolute temperature. Again, a LED/transistor constant-current source provides an ideal, modulateable supply from a varying voltage source.

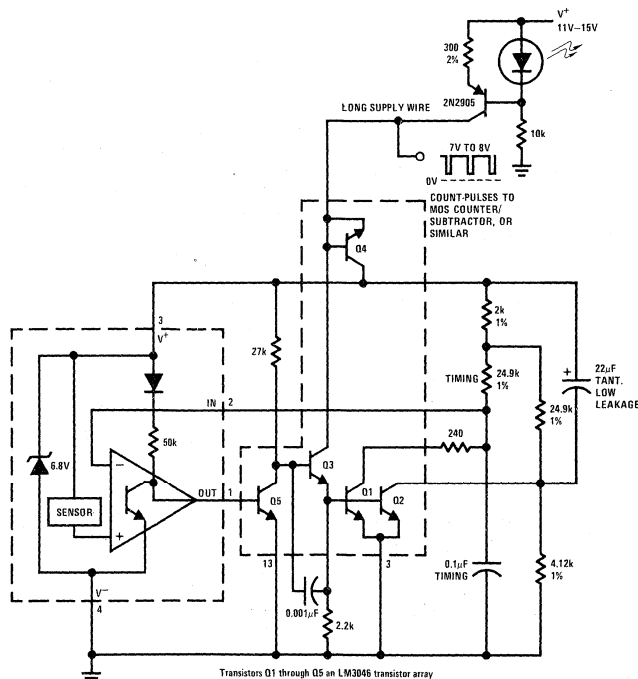


FIGURE 5. Temperature to Frequency Converter

The type of oscillator is similar to a number of "timer" circuits. A capacitor ramps up to a reference voltage, and trips a comparator. The comparator immediately lowers the reference to another fixed point and starts the ramp down. Upon reaching the lower reference the conditions are reversed.

In the converter, there are three slight differences. For one, the run-down of the ramp is made very fast, and contributes negligibly to the timing. Secondly, the upper reference the ramp charges to, moves negatively in linear proportion to temperature. Finally, the lower reference is controlled to be a fixed voltage below the upper at all times. This controls the generated sawtooth to a fixed amplitude at all times. However, since the upper comparison limit moves down with increased temperature, the whole dc level of the sawtooth moves down, increasing voltage across the charging resistor linearly with temperature.

Following are the detailed functions of the various components. The op amp inside the transducer is operated open-loop as a comparator. The 0.1 $\mu$ F timing capacitor is connected directly to the minus input of this amplifier and causes its output to switch "low" when capacitor charge reaches temperature sensor voltage. Transistor Q5 inverts and speeds up the op amp switch transition, and drives the base of Q3. This transistor's collector puts the negative pulse on the supply line, while its emitter drives the bases of Q1 and Q2. As a result, Q1 starts discharging the timing capacitor, and Q2 switches the bottom of the 22 $\mu$ F filter/coupler capacitor to ground.

This is an important step as it determines exactly how far the timing capacitor discharges. It can be seen that due to the large filter capacitor, voltage at the transducer's pin 3 is immediately lowered by the amount of voltage that had appeared across the 4.12k resistor. The sensor and op amp "plus" input follow this drop exactly. Therefore the new comparison point (toward which the timing capacitor is discharging) is lower by exactly the voltage drop of the 4.12k resistor. This voltage sets sawtooth amplitude to about 1V, with the upper and lower limits following temperature as described.

The voltage across a capacitor is predicted by current x time, divided by the capacitance. Since frequency has the units 1/t then:

$$f = \frac{1}{CV} \quad (1)$$

In other words, frequency will be linear with current change; with a fixed capacitance and a constant voltage change across the capacitance. There are some second order effects due to the slight change of the RC curve as charging percentage varies from about 30% cold to 20% hot. This was measured as less than 2°F out of a range from -68°F to +127°F. It is believed a compensation can be arranged for this small effect.

The remaining transistor, Q4 of the array, is connected so its collector becomes a decoupling diode. When the supply is modulated with the large negative output pulse, the charge on the critical filter/coupling capacitor is not substantially disturbed during the 10 $\mu$ s or so discharge time.

There is a simple, but interesting advantage to the single-package concept for the T/F Converter. Since it shares the same thermal environment with the sensor, linear changes with temperature of the oscillator components can be calibrated out as part of the entire system's frequency change with temperature. This somewhat relaxes the requirement for premium components.

## PROBE WITH SERVO'D SHIELD

When only part of a sensor can touch a surface to be measured, it has difficulty reaching the actual surface temperature. This is due to radiative and convective as well as normal conductive effects from all parts not touching the surface. Errors may be 10 or even 20% of the amount by which the surface is hotter than ambient. A very large improvement can be obtained if the sensor is surrounded loosely on all but one side by a thermal shield. The shield should be actively driven to within a degree of the surface temperature.

It sounds like going in circles, (i.e., knowing the surface temperature in order to measure it). However, the system is made to work by having the shield *track* the actual surface temperature sensor. If the coupling between surface and sensor is just a little better than sensor to shield, the whole system converges on an accurate final reading. This explains why there is *insulation* between sensor and shield, while the servo control sensor is soldered directly to the heater transistor.

Figure 6 provides the mechanical details of the system. The LM195 power transistor is both the main power amplifier and heater, being capable of about 23W of heating as shown. Internal current and thermal limit make this a safe and practical mode of operation, and places a great deal of heat in a small area. The system is also surprisingly fast, with the application of heat electrically being sensed within 1/2 second by the servo sensor. The servo sensor is closer to the heat generating silicon die than any of the rest of the system.

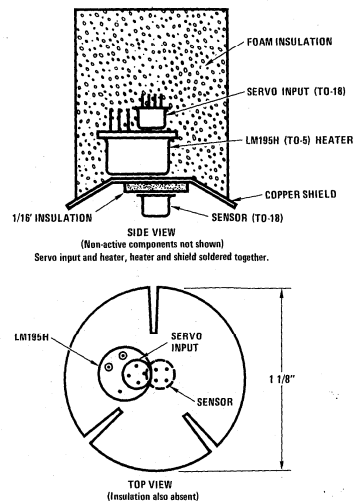


FIGURE 6. Servo'd Shield

Circuitry available inside the LX5700 sensors makes the Servo'd Shield Schematic, Figure 7, extremely simple. The close tracking of sensors after adjustment, simply allows the output of the surface sensor to become the setpoint signal for the servo input sensor. The 27 k $\Omega$  and 3 M $\Omega$  resistors set the servo's op amp gain to about 100. This is needed because the LM195H decreases in required base drive as it heats up, thus appearing to add positive feedback, increasing gain of the system. The 100k/56k divider provides a helpful level shift and absorbs bias current generated by the integrated power transistor.

The 100 $\mu$ F capacitor compensates for an interesting thermal characteristic of the system. Especially at lower temperatures, the power transistor heats at least an order of magnitude faster than it cools. The LX5700 op amp can sink much more current than it sources, so the capacitor establishes a slow turn-on, fast turn-off base signal to the LM195. This compensates the system to prevent large heating overshoots.

Several of the other components need explaining. The diode in series with the sensor ground leg allows the internal zener to be non-conducting, so that pin 3 can be adjusted up or down the 40 to 80 mV necessary to cause the two thermometers to track. A DVM with two digits to the right of the decimal will read directly in  $^{\circ}$ C by moving the point right two places. The meter can be zeroed at 0 $^{\circ}$ C by the 1k trimmer. The heavy filter at the "Lo" or minus input to the DVM is needed because many meters with "floating" input are not well isolated, and inject noise back into the sensing system. The negative going thermometer output at the minus DVM terminal enables the temperature displayed to have the correct sign.

As a cautionary note, the 2-wire ground system as shown is needed to reject feedback caused by initial large heating current surges drawn by the LM195H. Passive components shown as in the probe can be in the foam insulation (on standoffs or a miniature board) but

would be better placed above the insulation to avoid heating them to probe temperatures also.

## THE ANTICIPATING CONTROLLER

If the conditions are right, and the hardware available, the anticipating controller can be executed rather simply. Normally 2 amplifiers and about 3 different kinds of feedback are required to make a controller stable and accurate under varying load conditions. This is due to the unavoidable delay between application of heat and a usable sensor output. The anticipating controller adds a selected amount of phase leading signal to the normal amplified output from the temperature sensor. This, at least partially, compensates for the sensing lags.

In the system shown, heater/sensor delays up to about a minute can be compensated for. A simple electronic system can be constructed because of the high sensor output obtainable (100 mV/ $^{\circ}$ C) and the very low bias currents required by the LM216 op amp. This allows use of the 100 M $\Omega$  feedback resistor and thus very high differentiator (or anticipating) gain without significant errors. In a test using a heated plate with about a 30 second lag from ideal response, addition of the anticipating signal decreased thermal oscillations from 3 $^{\circ}$  to one or two tenths of a degree.

The LX5700 amplifies its normal 10 mV/ $^{\circ}$ C by about 10 due to the feedback network for its internal op amp. The feedback resistor is the 100k pot and the other gain setting resistance is the series combination of the 5.6k resistor and the setpoint pot resistance at the wiper. The dc gain of the LM216 op amp is set by the 10 M $\Omega$  and 100 M $\Omega$  resistors at another factor of 10, yielding 1V/ $^{\circ}$ C. Differentiator gain is set by the same 100 M $\Omega$  resistance and the 2 $\mu$ F capacitor. A temperature change of 1/20 $^{\circ}$ /second would result in a 1V output if the 100k pot were set to maximum differentiator gain. The 33k resistor in series with the differentiating capacitor, and the 0.001 $\mu$ F feedback capacitor serve to limit high frequency gain and reduce the effects of noise and

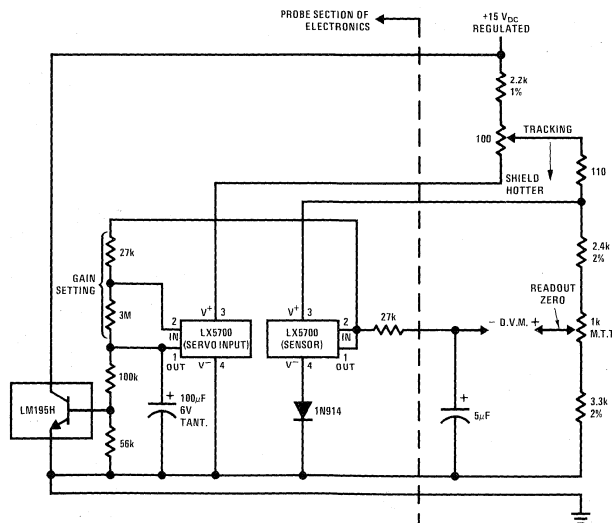


FIGURE 7. Servo'd Shield Schematic



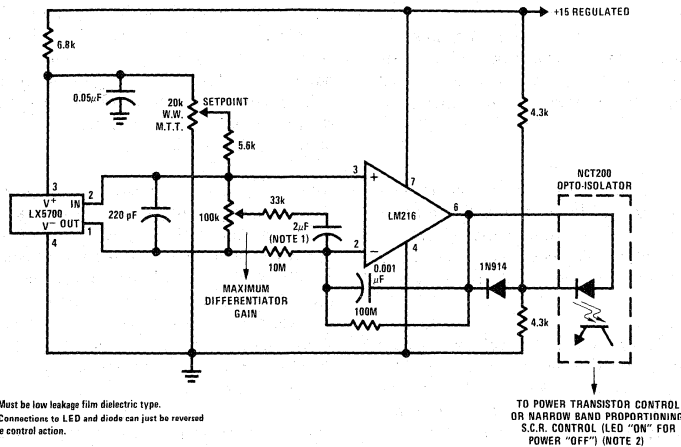


FIGURE 8. Anticipating Controller

pickup which can otherwise be greatly emphasized in a differentiator.

The output circuit energizes the opto-isolator when the op amp output swings somewhat above the supply centertap set by the two 4.3k resistors. Depending on divider value, current gain of the coupler, and sensitivity of its load, almost arbitrarily small changes of temperature or *rate* of temperature change may control heating or cooling. In some cases gain will have to purposely be reduced to get a stable control point.

### OTHER SENSING FUNCTIONS

Temperature is easy, but what about temperature difference? Monolithic transducers are very good at sensing this because of their close tracking and the capability of delivering from tens of millivolts to many volts of output for each °C of temperature difference. Any physical process that generates a small temperature gradient to ambient or a reference can be sensed by a pair of transducers. This potentially involves chemical processes, friction, compression of gasses, radiation, evaporation, and a whole raft of heat generating or absorbing phenomena. Three rather simple such applications will be illustrated.

#### Liquid or Moving Air Detection

Figure 9 shows a basic 2 sensor configuration for performing a number of differential temperature functions. As noted, one sensor is heated considerably by internal dissipation, and the other is biased slightly lower at supply voltage pin 3 so that if the "hot" sensor lost half its excess heat, its output (operating essentially open loop) will switch to a "high" state. This of course turns on the power transistor. The feedback network consisting of a 1M resistor and 680Ω resistor provides slightly less than 1/2°C hysteresis or snap action which prevents partial outputs or oscillation near the setpoint.

Adjustments are not too critical due to the large temperature differences that are created. Cooling of the sensing unit by an electrically non-conducting liquid (such as oil) is about 16°C. Still liquid was used

for the measurement. Air at about 400 FPM (a little under 5 mph) provides about 10°C cooling.

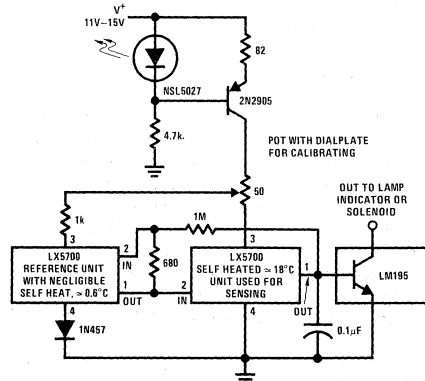


FIGURE 9. Liquid or Moving Air Detection

For either application the adjustment is fairly simple. With the sensing transducer in the "hot" condition (still-air, or out of liquid for 2 minutes) find the pot setting that just turns the power output off. Then with the sensing transducer in the cool condition (in liquid or moving air) for 30 seconds, find the setting that just turns the output on. Since these two settings "overlap," a final setting between these two will provide stable operation. If it is noted that response in the heating direction is markedly slower, displacing the adjustment toward the "cool" setting (referring to the pot dialplate) can partially compensate for this.

If the detector is used as a failsafe sensor in a system cooled by a fan, the sensor's self-heating delay gives time for said cooling fan to come up to speed without requiring a special delay or override for system start-up. Speed of response can have good or bad effects on the over-all system. The sensors are essentially slow enough so that momentary air blockage or liquid splashing won't give erroneous signals. In liquid sensing, drops

adhering to the sensing transducer can slow it down by 2 or 3 to 1. A "drip point" such as 3/8" long piece of #28 bare wire soldered to the lowest part of the case helps. Insulating supports, or lead insulation, within 1/2" of the sensing LX5700 slows it down considerably.

### Wind Velocity

Actual "air speed" has more effect on gasoline mileage than road speed at above 40 mph. Further there is great interest by sailboat racers as to wind velocity or air speed. Again, a differential between a heated and unheated transducer can be used in this sensing job.

Briefly, the setpoint input (pin 2) of the transducer that is to sense velocity, is biased so that its voltage is always equivalent to a number of degrees above ambient. This voltage is obtained by adding a small dc level to the output of an ambient sensing transducer. The output of the velocity transducing LX5700 is used to control its own heating; holding it the specified number of degrees above ambient. The current to do this is measured, and is obviously a measure of the amount of heating required. As wind velocity rises, so does this current as the transducer "servo's" its temperature to a constant amount above ambient.

In *Figure 10* this amount of heating is set by the wiper voltage of the 20k pot into the 100k/4.12k divider. The bottom of this divider is driven by the LX5600 air temperature reference, connected in unity gain mode. The output of the velocity sensor drives the base of Q1. If this sensor cools, Q1 base goes positive, reducing its emitter current and collector current. The current drawn by the 620Ω collector load doesn't change significantly however. The current now *not* supplied by Q1 is drawn instead through D2, through the meter, and eventually through the reference zener of the velocity sensor. This of course heats the sensor, closing the feedback loop.

The system is made electrically stable by the 0.1 compensating capacitor and the fact that Q1 exhibits practically no collector voltage gain. Q2 is not normally conducting, but it and the divider on its base provide a

clamp voltage for the Q1 collector. This prevents a "latchup" mode that occurs if Q1 happens to draw a transient current pulse. The "zero velocity current" adjustment allows this heating current needed at zero velocity to bypass the meter. To avoid a low velocity discontinuity, it is probably best to "zero" the meter at about 1% of full scale.

Sensor Arrangement as shown in *Figure 11*, minimizes the sensitivity of the system to vertical components of wind, and limits the exposed part of the sensor to a controlled area (no lead effects, etc.) which has uniform nondirectionality in the horizontal plane. The breadboard used Balsa wood due to its good insulation qualities *and* very low thermal mass. In the field consideration should be given to prevention of water absorption. No thermal air velocity system will give correct data in rain or dense fog.

The current vs airspeed curve shows the typical decreasing sensitivity with increasing velocity, but a good calibration curve has not been obtained at this time through lack of instrumentation. Response speed is decidedly slower than that of thermocouple types, but in some cases this may be an advantage, such as in determining average airspeed on a gusty day.

### Position Sensing

This may be the most novel or, on the other hand, strangest of the applications shown. Under certain conditions however, the very considerable position "integration" due to the thermal mass of the sensor may make this system quite practical, and much less expensive than electronic filtering. As shown in *Figures 12 and 13* the essence of the system is a small sliding *heater* acting as a position transmitter. The receiver is a brass tube which allows the total heater output to be transmitted out toward the ends. The temperature reached at each end is proportional to heater position.

Logically, with the heater in the center, both ends reach the same temperature. With the heater at one end, that end is about 50°C warmer than ambient, and

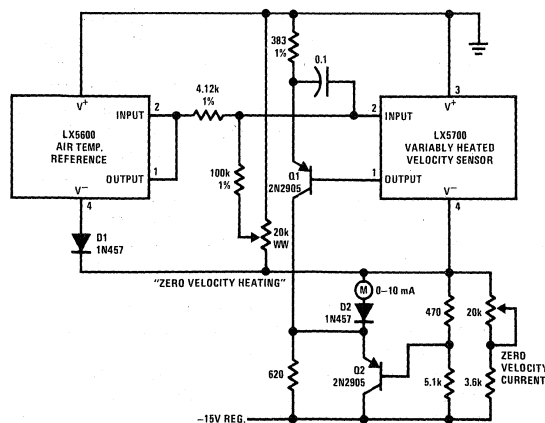


FIGURE 10. Air Velocity Meter

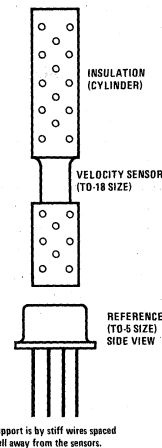


FIGURE 11. Sensor Arrangement

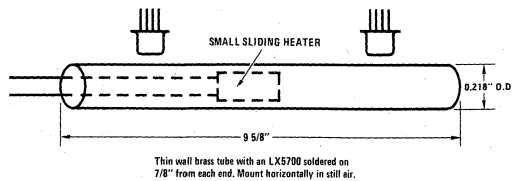


FIGURE 12. Position Sensor Tube

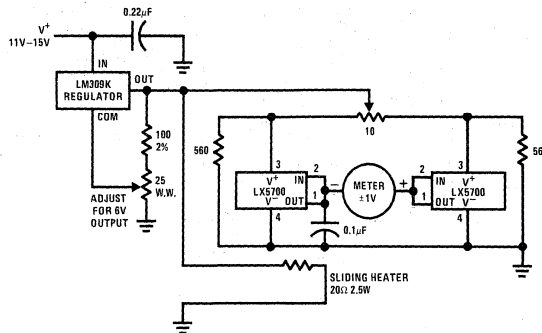


FIGURE 13. Position Sensor Schematic

the other end is near ambient. As the heater moves toward one end, one thermometer becomes more sensitive, and the other less. The differential effects tend to cancel, and the first breadboard unit had a temperature difference linearity within 4% relative to measured position. The heater must stay *between* the sensors to achieve this, with the extra length of tube at the ends helping to linearize the system.

The electrical system powers the sensors at minimum dissipation, and regulates heater power to keep position "gain" constant. The pot simply allows an electrical zero of the two thermometers and meter, which can be done with the heater off. The meter can be a 2 polarity DVM with 600 mV to 1V full scale, or a zero centered mechanical meter with similar deflection either side of zero.

The system takes 2 to 3 minutes to reach 98% of final reading. This may make it a very good position *averaging* system in cases where there is high amplitude vibration. Average truck spring deflection could be read while it is rolling along a rough road for instance. The system will have less wear problems than a sliding position pot and be less expensive than a Linear Variable Transformer system. It may also be useful in a position servo system that needs very heavy filtering.

#### SUMMARY AND CONCLUSIONS

Since the monolithic temperature transducer is a relatively new and unique device, this has been primarily an applications paper attempting to broaden the base of practical Integrated Circuit usage. Some general techniques were explained and seven specific systems

have been described in construction and performance. Hopefully these concepts will remain after the details are forgotten.


First, there are many considerably different schemes for temperature control or measurement based on the versatility of a transducer that has both amplifying and regulating capability in the same package. This three circuits in one package availability allows consideration of systems that formerly would have been too expensive or complex.

Secondly, the ease of accurately sensing small temperature *differences* leads to sensors for other than just temperature sensing. Sensing liquids, air velocity, and mechanical position have been demonstrated, and other possibilities include rate-of-rise sensors for fire detection, RMS regulators, and humidity gauges. It will be interesting to see what others turn up that we have missed.


#### REFERENCES

- (1) Robert C. Dobkin, *1.2 Volt Reference*, National Semiconductor Corporation Application Note 56, December 1971.
- (2) Robert C. Dobkin, *Fast IC Power Transistor with Thermal Protection*, National Semiconductor Corporation Application Note 110, May 1974.
- (3) *Transducers, Pressure & Temperature*, National Semiconductor Corporation catalog and handbook, August 1974.

APPENDIX SCHEMATICS

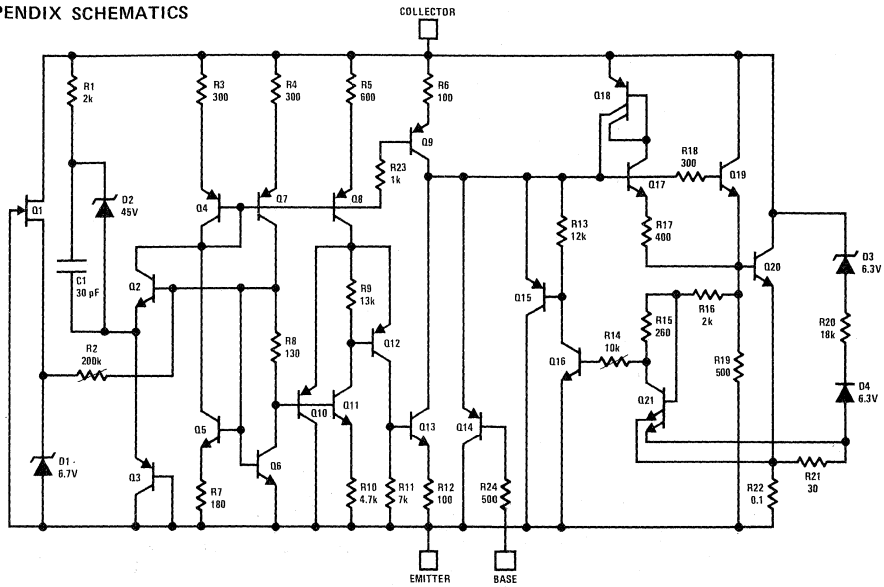

Schematic Diagram of the LM195

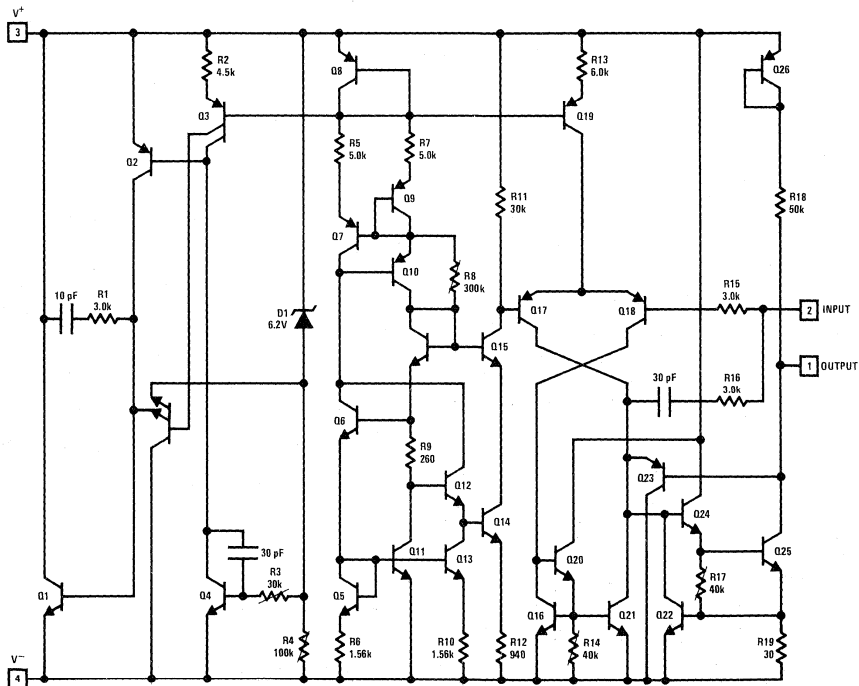

Schematic Diagram of the LX5600/LX5700

# FM Remote Speaker System

National Semiconductor  
Application Note 146  
Jim Sherwin  
Nello Sevastopoulos  
Tim Regan  
June 1975



## INTRODUCTION

A high quality, noise free, wireless FM transmitter/receiver may be made using the LM566 VCO and LM565 PLL Detector. The LM566 VCO is used to convert the program material into FM format, which is then transformer coupled to standard power lines. At the receiver end the material is detected from the power lines and demodulated by the LM565.

The important difference between this carrier system and others is its excellent quality and freedom from noise. Whereas the ordinary wireless intercom uses an AM carrier and exhibits a poor signal-to-noise ratio (S/N), the system described here uses an FM carrier for inherent freedom from noise and a PLL detection system for additional noise rejection.

The complete system is suitable for high-quality transmission of speech or music, and will operate from any AC outlet anywhere on a one-acre homesite. Frequency response is 20-20,000 Hz and THD is under 1/2% for speech and music program material.

Transmission distance along a power line is at least adequate to include all outlets in and around a suburban home and yard. Whereas many carrier systems operate satisfactorily only when transmitter and receiver are plugged into the same side of the 120-240V power service line, this system operates equally well with the receiver on either side of the line.

The transmitter is plugged into the AC line at a radio or stereo system source. The signal for the transmitter is ideally taken from the MONITOR or TAPE OUT connectors provided on component system Hi-fi receivers. If these outputs are not available, the signal could be taken from the main or extra speaker terminals, although the remote volume would then be under control of the local gain control. The carrier system receiver need only

be plugged into the AC line at the remote listening location. The design includes a 2.5W power amplifier to drive a speaker directly.

## TRANSMITTER

Two input terminals are provided so that both LEFT and RIGHT signals of a stereo set may be combined for mono transmission to a single remote speaker if desired.

The input signal level is adjustable by  $R_1$  to prevent over-modulation of the carrier. Adding  $C_2$  across each input resistor  $R_7$  and  $R_8$  improves the frequency response to 20 kHz as shown in *Figure 5*. Although casual listening does not demand such performance, it could be desired in some circumstances.

The VCO free-running frequency, or carrier frequency  $f_c$ , determined by  $R_4$  and  $C_4$  is set at 200 kHz which is high enough to be effectively coupled to the AC line. VCO sensitivity under the selected bias conditions with  $V_s = 12V$  is about  $\pm 0.66 f_c/V$ . For minimum distortion, the deviation should be limited to  $\pm 10\%$ ; thus maximum input at pin #5 of the VCO is  $\pm 0.15V$  peak. A reduction due to the summing network brings the required input to about 0.2V rms for  $\pm 10\%$  modulation of  $f_c$ , based on nominal output levels from stereo receivers. Input potentiometer  $R_1$  is provided to set the required level. The output at pin #3 of the LM566, being a frequency modulated square wave of approximately 6V pk-pk amplitude, is amplified by a single transistor  $Q_1$  and coupled to the AC line via the tuned transformer  $T_1$ . Because  $T_1$  is tuned to  $f_c$ , it appears as a high impedance collector load, so  $Q_1$  need not have additional current limiting. The collector signal may be as much as 40-50V pk-pk. Coupling capacitor  $C_8$  isolates the transformer from the line at 60 Hz.

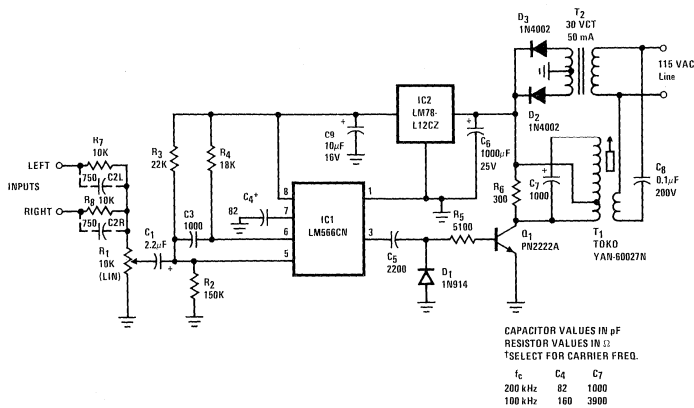


FIGURE 1. Carrier System Transmitter

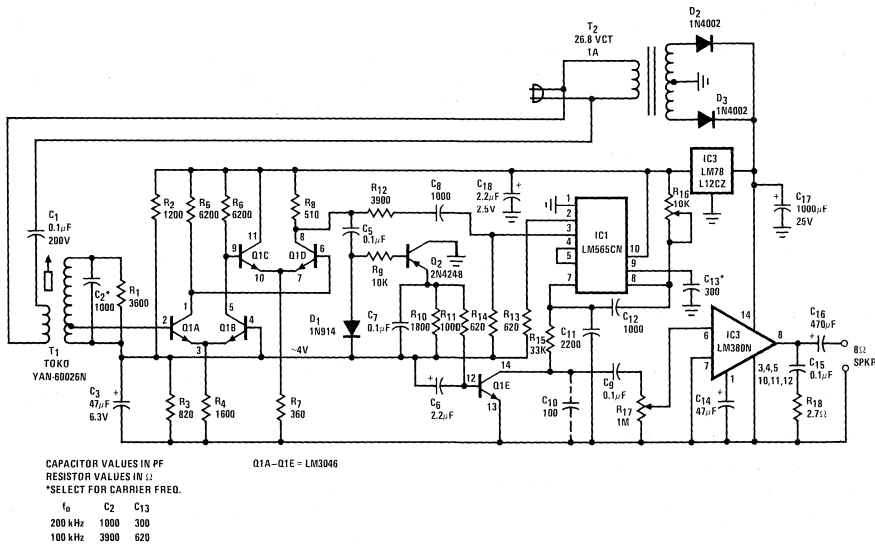


FIGURE 2. Carrier System Receiver

A voltage regulator provides necessary supply rejection for the PLL. The power transformer is sized for peak secondary voltage somewhat below the regulator breakdown voltage spec (35V) with a 125V line.

### RECEIVER

The receiver amplifies, limits, and demodulates the received FM signal in the presence of line transient interference sometimes as high as several hundred volts peak. In addition, it provides audio mute in the absence of carrier and 2.5W output to a speaker.

The carrier signal is capacitively coupled from the line to the tuned transformer  $T_1$ . Loaded Q of the secondary tank  $T_1C_2$  is decreased by shunt resistor  $R_1$  to enable

acceptance of the  $\pm 10\%$  modulated carrier, and to prevent excessive tank circuit ringing on noise spikes. The secondary of  $T_1$  is tapped to match the base input impedance of  $Q_{1A}$ . Recovered carrier at the secondary of  $T_1$  may be anywhere from 0.2 to 45V p-p; the base of  $Q_{1A}$  may see pk-to-pk signal levels of from 12mV to 2.6V.

$Q_{1A}$ - $Q_{1D}$  operates as a two-stage limiter amplifier whose output is a symmetrical square wave of about 7V pk-pk with rise and fall times of 100 ns.

The output of the limiting amplifier is applied directly to the mute peak detector, but is reduced to 1V pk-pk for driving the PLL detector.

The PLL detector operates as a narrow band tracking filter which tracks the input signal and provides a low-distortion demodulated audio output with high S/N. The oscillator within the PLL is set to free-run or near the carrier frequency of 200 kHz. The free-run frequency is  $f_o \approx 1/(3.7 R_{16}C_{13})$ . Since the PLL will lock to a carrier near its free-run frequency, an adjustment of  $R_{16}$  is not strictly necessary;  $R_{16}$  could be fixed at 4700 or 5100 $\Omega$ . Actually, the PLL with the indicated value of  $C_{11}$  can lock on a carrier within about  $\pm 40$  kHz of its center frequency. However, rejection of impulse noise in difficult circumstances can be maximized by carefully adjusting  $f_o$  to the carrier frequency  $f_c$ . Adding  $C_{10} = 100$  pF will reduce the carrier level fed to the power amplifier. Even though the listener cannot hear the carrier, the audio amplifier could overload due to carrier signal power.

A mute circuit is included to quiet the receiver in the absence of a carrier. Otherwise, when the transmitter is turned OFF, an excessive noise level would result as the PLL attempts to lock on noise. The mute detector consists of a voltage doubling peak detector  $D_1Q_2C_7$ . The peak detector shunts the 1-2 mA bias away from  $Q_{1E}$  without loading the limiter amplifier. When no carrier is present, the +4V line biases  $Q_{1E}$  ON via  $R_{10}$  and  $R_{11}$ ; and the audio signal is shorted to ground. When a carrier is present, the 7V square wave from the limiter amplifier is peak detected, and the resultant negative output is

integrated by  $R_9C_7$ , averaged by  $R_{10}$  across  $C_7$ , and further integrated by  $R_{11}C_6$ . The resultant output of about -4V subtracts from the +4V bias supply, thus depriving  $Q_{1E}$  of base current. Peak detector integration and averaging prevents noise spikes from deactivating the mute in the absence of a carrier when the limiter amplifier output is a series of narrow 7V spikes.

The LM380 supplies 2.5W of audio power to an 8 ohm load. Although this is adequate for casual listening in the kitchen or garage, for hi-fi listening, a larger amplifier may be desired.

### CONSTRUCTION

PC board layout and stuffing diagrams are shown in *Figures 3 & 4*. After the receiver board has been loaded and checked, the power transformer is mounted to the foil side of the board with a piece of fish-paper or electrical insulating cloth between board and transformer. Insulating washers of 1/16-1/4 inch thickness can be used to advantage in holding the transformer away from the foil. The board is laid out so that the volume control potentiometer may be mounted on either side of the board depending on the desired mounting to a panel.

The line coupling coils are available in production quantities from TOKO AMERICA INC, 5520 West Touhy, Skokie, IL.

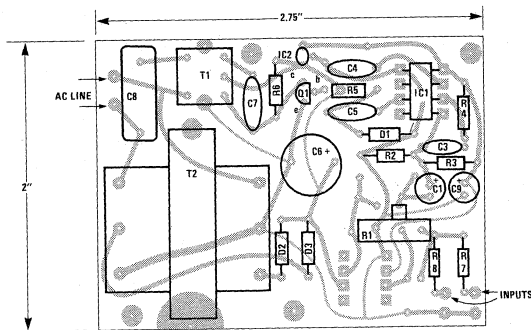


FIGURE 3. Carrier System Transmitter PC Layout and Loading Diagram (Not Full Scale)

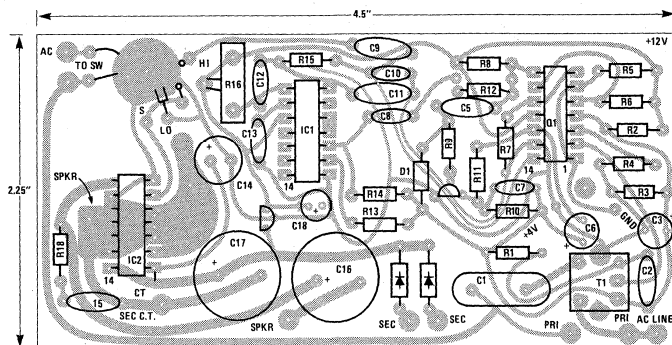


FIGURE 4. Carrier System Receiver PC Layout and Loading Diagram (Not Full Scale)

## ADJUSTMENT

Adjustments are few and extremely simple. Transmitter carrier frequency  $f_c$  is fixed near 200 kHz by  $R_4$  and  $C_4$ ; the exact frequency is unimportant.  $T_1$  for both transmitter and receiver are tuned for maximum coupling to and from the AC line. Plug in both receiver and transmitter; no carrier modulation is necessary. Insure that both units are operative. Observe or measure with an AC VTVM the waveform at  $T_1$  secondary in the receiver. Tune  $T_1$  of the transmitter for maximum observed signal amplitude. Then tune  $T_1$  of the receiver for a further maximum. Repeat on the transmitter, then the receiver. Tuning is now complete for the line coupling transformers and should not have to be repeated for either. If the receiver is located some distance from the transmitter in use, or on the opposite side of the 110-220V service line, a re-adjustment of the receiver  $T_1$  may be made to maximize rejection of SCR dimmer noise. The receiver PLL free-running frequency is adjusted by  $R_{16}$ . Set  $R_{16}$  near the center of its range. Rotate slowly in either direction until the PLL loses lock (evidenced by a sharp increase in noise and a distorted output). Note the position and then repeat, rotating in the other direction. Note the new position and then center  $R_{16}$  between the two noted positions. A fine adjustment may be made for minimum noise with an SCR dimmer in operation. The final adjustment is for modulation amplitude at the transmitter. Connect the audio signal to the transmitter input and adjust the input potentiometer  $R_1$  for a signal maximum of about 0.1V rms at the input to the LM566. Adjustment is now complete for both transmitter and receiver and need not be repeated.

## A STEREO SYSTEM

If full stereo or the two rear channels of a quadraphonic system are to be transmitted, both transmitter and receiver must be duplicated with differing carriers. Omit  $R_8$  and include  $R_7$  &  $C_2$  on the transmitter if desired. Carriers could be set to 100 and 200 kHz for the two channels. Actually, they need only be set a distance of 40 kHz apart.

## PERFORMANCE

Overall S/N is about 65 dB. Distortion is below about 1/4% at low frequencies, and in actual program material it should not exceed 1/2% as very little signal power occurs in music above about 1 kHz.

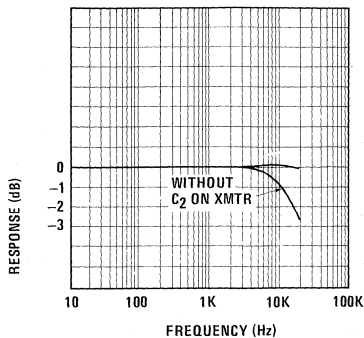


FIGURE 5. Overall System Performance  
Transmitter Input to Input of Receiver Power Amplifier

The 2.5W audio amplifier provides an adequate sound level for casual listening. The LM380 has a fixed gain of 50. Therefore for a 2.5W max output, the input must be 89 mV. This is slightly less than the  $\pm 10\%$  deviation level so we are within design requirements. Average program level would run a good 10 dB below this level at 28 mV input.

Noise rejection is more than adequate to suppress line noise due to fluorescent lamps and normal line transients. Appliance motors on the same side of the 110-220V line may produce some noise. Even SCR dimmers produce only a background of impulse noise depending upon the relative location of receiver and SCR. Otherwise, performance is noise-free anywhere in the home. Satisfactory operation was observed in a factory building so long as transmitter and receiver were connected to the same phase of the three-phase service line.

## APPLICATIONS

Additional applications other than home music systems are possible. Intercoms are one possibility, with a separate transmitter and receiver located at each station. A microphone can serve as the source material and the system can act as a monitor for a nursery room. Background music may be added to existing buildings without the expense of running new wiring.



# Low Cost IC Stereo Receiver

National Semiconductor  
Application Note 147  
Dennis Bohn  
Jim Sherwin  
June 1975



## INTRODUCTION

The recent availability of a broad line of truly high-performance consumer integrated circuits makes it possible to construct a high quality, low noise, low distortion and low cost AM/FM/Stereo receiver. Design emphasis is placed on a high level of performance, minimum factory adjustments and low parts count. As such, the receiver has immediate applications to table-top, high-fidelity, automotive and communications markets.

Provisions are included for the addition of a ceramic phono unit as well as a tapehead amplifier allowing inclusion of eight-track or cassette transport systems. Complete tone control circuitry is provided offering both boost and cut of Bass and Treble frequencies. Left and right channel Balance, and system Volume complete the manual front-panel controls.

Panel meters are employed in the FM system for both signal strength and center tuning, allowing for easy and accurate tuning. A directly driven LED offers immediate indication of FM stereo reception.

The complete design requires just five IC's, restricting the use of discrete active elements to the preassembled FM front-end and the single transistor tone control design.

## FM and FM STEREO

A preassembled front-end was selected as the cost-effective approach to minimum parts count and minimum factory adjustments. This model features an FET input stage providing excellent distortion performance. High selectivity is obtained thru the use of two cascaded ceramic filters yielding an approximate 6-pole response with less than 12 dB insertion loss.

The LM3089 FM IF System does all the major functions necessary for FM processing, including a three stage amplifier/limiter and balanced product detector, as well as an audio preamplifier. A single quadrature coil was used for ease of alignment; yielding recovered audio with THD less than 0.5%, however a double coil may be used to diminish THD to 0.1% if required. Carrier level detectors provide delayed AGC, SIGNAL strength meter drive, and adjustable interstation mute control R<sub>11</sub>. The internal AFC amplifier was used to drive the TUNING meter, giving a visual indication of center tuning.

FM stereo demodulation is accomplished by the use of the LM1800 phase locked loop, thereby eliminating the need for external coils. Only two adjustments are necessary: R<sub>14</sub>, which sets the 19 kHz oscillator, and R<sub>17</sub>,

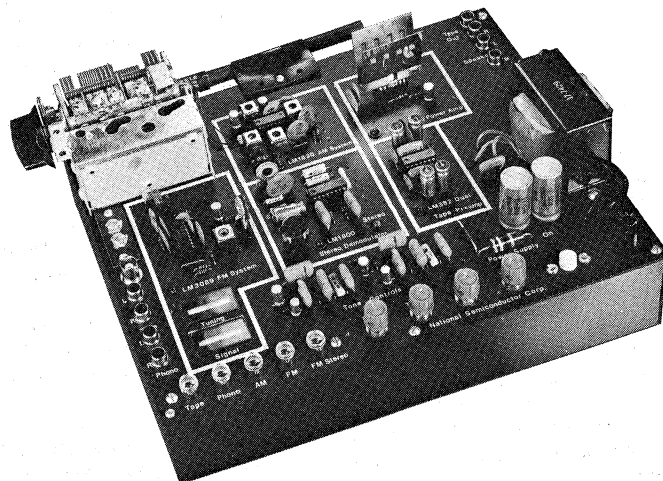


FIGURE 1. IC Receiver

which corrects for excess phase shift thru the IF stages, and yields maximum channel separation. Automatic stereo/monaural switching is built-in, and may be used in lieu of mechanical switching if desired. The open collector lamp driver is used to light a LED whenever a stereo station is encountered. (Further details available from application note AN-81.)

## AM

The AM function of the receiver is done completely with the LM1820 AM radio system. While designed for 3 section tuned superheterodyne applications, the LM1820 may be used with the less expensive 2 section tuned designs by omitting the RF stage and redefining its function as 2ND IF stage (see linear brief LB-29). As shown, the LM1820 provides the necessary converter/oscillator, IF, and AGC detector functions, while the external diode  $D_1$  does the audio demodulation,  $D_1$  is slightly forward biased thru  $R_2$  for improved distortion performance. In addition its resistance is used in conjunction with  $C_9$  to form the first stage of the required low pass filter; the second stage consists of  $R_3$  and  $C_{10}$ .

## TAPE

The LM382 dual preamplifier was selected for its minimum parts count and low noise capability. With a guaranteed maximum equivalent input noise voltage of  $1.2\mu\text{Vrms}$  (10 kHz BW), it easily amplifies the low level tape signals while retaining excellent S/N ratio ( $\sim 64$  dB below 2 mV input level). An ion-implanted resistor matrix is supplied on the chip for self-biasing the output to half-supply, and provides the resistors necessary to create the NAB equalization curve; requiring only four external capacitors per channel to complete the amplifier. For production models this preamplifier would normally be mounted directly on the tape player to minimize hum and noise pick-up.

## TONE CONTROLS

A single transistor tone control circuit was designed as the optimum cost/performance trade-off. The transistor is configured in a shunt-shunt feedback design, allowing gain variations between input functions. This is necessary to prevent sudden changes in output level when different inputs are selected. With a shunt feedback design the gain is easily controlled by choice of source impedance per *Figure 5*.

Approximately 20 dB of boost or cut of Bass and/or Treble frequencies is possible with the network shown. The turnover frequencies are approximately 500 Hz and 1600 Hz for bass and treble, respectively. The insertion loss of approximately 27 dB is made up by the gain of the transistor tone control amplifier. Balance and Volume controls are included as shown. Loudness control may

be included by using a tapped Volume pot and the associated bass boost RC network if desired. More elaborate tone controls such as Baxandall feedback are possible, but at a premium in cost.

## POWER AMPLIFIER

The stereo power section, consisting of the LM378 dual audio amplifier, delivers 3W/channel with total harmonic distortion (THD) less than 1%, and 4W/channel with THD less than 10%, operating from split supply voltages of  $\pm 11\text{V}$ . Split supplies were chosen to facilitate a minimum parts count design. This approach allows direct coupling of the amplifier to the speakers since the output DC level is zero volts (offset voltage will be less than 25 mV), thereby eliminating the need of large coupling capacitors and their associated degradation of power, distortion and cost. Since the input bias voltages are zero volts, the need for bias resistors and the bias-pin supply bypassing capacitor are also eliminated. Input capacitors are omitted and bias current for the positive input is obtained directly thru the Volume pots since the tone control circuitry has been designed such that there is no DC potential applied.

It is important to apply proper supply voltages and adequate heatsinking in using the LM378 (see application note AN-125). Note that while the standby and low output power operating points of the power supply are  $\pm 15\text{V}$ , the maximum power out point causes the supply to sag to  $\pm 11\text{V}$  therefore reducing package power dissipation to acceptable levels. Socketable heatsinking is possible using a Staver V7-5 heatsink soldered directly to the center three pins on both sides of the LM378.

## POWER SUPPLY

The worst case ripple rejection of 45 dB for the IC's used allows for a simple unregulated power supply, however the discrete front-end and tone control amplifiers require some regulation to preserve the IC performance. A single zener diode  $Z_1$  was selected to create a +12V supply for this function. The split supplies required for the power amplifier are derived from a conventional full-wave bridge rectifier operating off of the center-tapped secondary of the line transformer.

## REFERENCES

1. Isbell, T.D. and Mishler, D.S., "LM1800 Phase Locked Loop FM Stereo Demodulator." National Semiconductor Application Note AN-81, June 1973.
2. Papanicolaou, E.S. and Mortensen, H.H., "Low-Cost AM-Radio System Using LM1820 And LM386." National Semiconductor Linear Brief LB-29, May 1975.
3. Sherwin, J., "LM377, LM378 And LM379 Dual Two, Four, And Six Watt Power Amplifiers." National Semiconductor Application Note AN-125, January 1975.

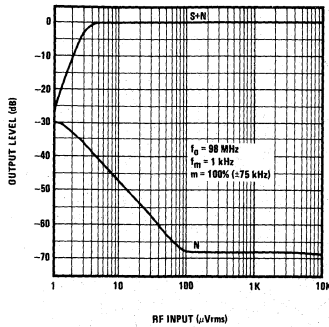


FIGURE 2. FM Sensitivity

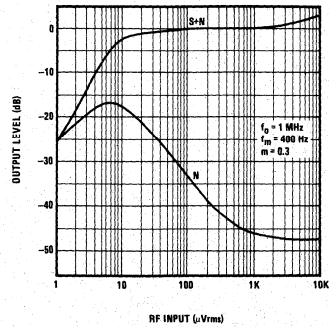


FIGURE 3. AM Sensitivity

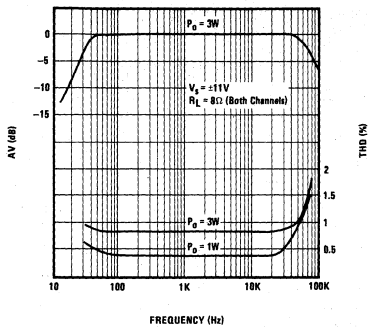


FIGURE 4. Power Amplifier Frequency Response and Total Harmonic Distortion

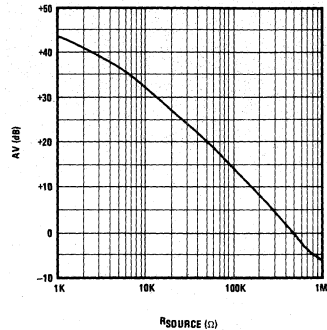


FIGURE 5.  $A_V$  vs.  $R_{SOURCE}$  for Tone Control Preamp Stage.

## SPECIFICATIONS

### FM-MONO

Sensitivity:  $2.5\mu V$  for 30 dB quieting  
 Harmonic Distortion: 0.3%  
 Hum & Noise: -65 dB  
 Frequency Response: 50-15 kHz  $\pm 3$  dB

### FM-STEREO

Channel Separation: 45 dB  
 Harmonic Distortion: 0.4%

### AM

Sensitivity:  $20\mu V$  for 20 dB S+N/N  
 Harmonic Distortion: 2%  
 Hum & Noise: -45 dB

### TAPE

Frequency Response: NAB equalized  $\pm 2$  dB  
 Harmonic Distortion: 0.3%  
 Hum & Noise: -64 dB below 2 mV input level

### AMPLIFIER

Power Output: 3W RMS, per channel into 8 ohms  
 at less than 1% THD from 40-30 kHz  
 Frequency Response: 35-55 kHz  $\pm 3$  dB

## VENDOR DEVICES

FM Tuner: Waller 32SN2F1-30  
 Coils: T3: AM Osc. Toko RWO-6A6255  
 T4: IF, 455 kHz Toko RRC-3A6426N  
 T5: IF, 455 kHz Toko RRC-3A6427A  
 T6: IF, 455 kHz Toko RZC-1A6425A  
 T7: Quadrature, 10.7 MHz -  
 Toko TKXC-33733BS  
 Ceramic Filters: 10.7 MHz Toko CFS-30AE-10  
 Selector Switch: IEE/Schadow Type F-4U with  
 FA201 Mech. Reflecting Indicators  
 Meters: TUNING: #11226, SIGNAL: #11222  
 Mercer Electronics  
 Heatsink: Staver V7-5

## VENDOR LOCATIONS

Waller Corp., Crystal Lake, Ill. (815) 459-6510  
 Toko (America), Inc., New York, N.Y.  
 (212) 736-0245  
 IEE/Schadow Corp., Eden Prairie, Minn.  
 (612) 944-1820  
 Mercer Electronics (Simpson Electric Co.),  
 Elgin, Ill. (312) 379-1130  
 Staver Co., Bay Shore, N.Y. (516) 666-8000



# The Low Noise JFET— The Noise Problem Solver

National Semiconductor  
Application Note 151  
John Maxwell  
January 1976



The most versatile low noise active device available to the designer today is the Junction Field-Effect Transistor (JFET). JFETs are virtually free of the problems which have plagued bipolar transistors—limited bandwidth, popcorn noise, a complex design procedure to optimize noise performance. In addition, JFETs offer low distortion and very high dynamic range.

Most designers think of JFETs for very high source impedances. However, modern devices offer the designer performance improvements over bipolar transistors in NF for all but lowest impedance (<500Ω) sources and even then may provide improved performance if popcorn noise, bandwidth or circuit component noise is a consideration (see Figure 1).

Therefore, the purpose of this article is to review low noise design procedures and indicate the simplicity of designing high performance low noise amplifiers with low cost JFETs.

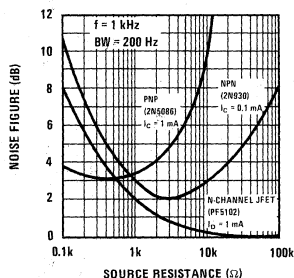


FIGURE 1. Bipolar and JFET Transistor Noise Comparison


## REVIEW OF BASICS

Before guidelines are established for designing low noise JFET amplifiers, a method of noise characterization must be chosen. Designers are confronted with a multitude of different noise parameters such as Noise Figure (NF), noise voltage and current densities, noise temperature, noise resistance, etc. Designers are primarily concerned with signal to noise (S/N) ratios preferring noise voltage, ( $e_n$ ) and current ( $i_n$ ) density.

Noise generally manifests itself in three forms: thermal noise, shot noise and flicker or "1/f" noise. Thermal noise arises from thermal agitation of electrons in a conductor and is given by Nyquist's relation:

$$\overline{V_R^2} = 4k TR \Delta f \quad (1)$$

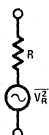- $\overline{V_R^2}$  = mean square noise voltage
- k = Boltzmann constant  
( $1.38 \times 10^{-23}$  VAS/°K)
- T = Absolute temperature (°K)
- R = Resistance in ohms
- $\Delta f$  = Noise bandwidth (Hz)



The noise of a resistor may be represented as a spectral density ( $V^2/Hz$ ) or more commonly in  $\mu V/\sqrt{Hz}$  or  $nV/\sqrt{Hz}$  and is given by:

$$e_{nR} = (\overline{V_R^2}/\Delta f)^{1/2} \quad (2)$$

It is sometimes more convenient to represent thermal noise as noise current instead of a noise voltage. One needs only to consider the Norton equivalent yielding a noise current density.

$$i_{nR} = \frac{e_{nR}}{R} = \left(\frac{4kT}{R}\right)^{1/2} \quad (3)$$

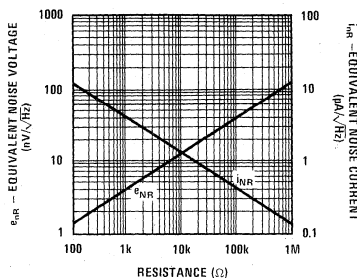


FIGURE 2. Thermal Noise Voltage and Current Densities vs. Resistance.

The second basic form of noise, shot noise, is due to the randomness of current flow (discrete charge particles) in semiconductor P-N junctions.

$$\overline{i^2} = 2q I_{DC} \Delta f \quad (4)$$

- $\overline{i^2}$  = Mean square noise current
- q = Charge of an electron ( $1.6 \times 10^{-19}$  AS)
- $I_{DC}$  = dc current flowing through the junction (A)
- $\Delta f$  = Noise bandwidth (Hz)

As with thermal noise, shot noise may be represented as a current density ( $A^2/Hz$ ) or  $pA/\sqrt{Hz}$ .

$$i_n = (\overline{i^2}/\Delta f)^{1/2} \quad (5)$$

It should be noted that both thermal noise and shot noise are "white" noise sources, i.e., frequency independent.

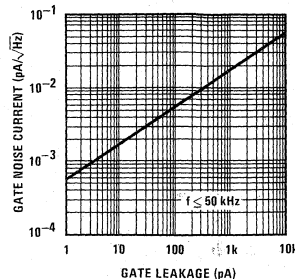


FIGURE 3. Current Noise vs. Gate Leakage Current

The third basic noise source confronting designers is flicker or "1/f" noise whose density is roughly inversely proportional to frequency starting at about 1 kHz in both JFETs and bipolar transistors and increasing as frequency is decreased. Through careful processing, flicker noise in JFETs has been reduced to levels nearly insignificant to the designer. Flicker noise in JFETs is primarily a noise voltage and is source independent. Flicker noise in bipolar transistors is a function of base and leakage currents increasing with increased source impedance or operating currents.

A simple noise model of a JFET or any amplifying device may be constructed using a thermal and shot noise source which would adequately describe its noise performance allowing signal to noise ratios to be calculated directly.

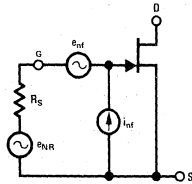


FIGURE 4. Simple JFET Noise Model

The input noise per unit bandwidth at some frequency may be calculated from the mean square sum of the noise sources (assuming the JFET noise sources are uncorrelated or independent of one another).

$$e_{nt}^2 = e_{nR}^2 + e_{nf}^2 + i_{nf}^2 R_s^2 \quad (6)$$

The total noise in the same bandwidth  $\Delta f$ , where the noise sources are independent of frequency, is simply:

$$V_{NOISE} = (e_{nt}^2 \Delta f)^{1/2} \quad (7)$$

Practically, noise sources are not frequency independent except resistor noise with no dc bias. The total input noise for the nonideal case may be calculated by breaking the spectrum up into several small bands and calculating the noise in each band where the noise sources are nearly frequency independent. The total input noise would then be the RMS sum of the noise in each of the bands  $N_1 \dots N_n$ .

$$V_{NOISE} = (V_{N1}^2 + V_{N2}^2 + \dots + V_{Nn}^2)^{1/2} \quad (8)$$

## THE DESIGN PROCESS

The final circuit configuration and suitable JFET will be determined by the external circuit constraints.

- 1) Minimum signal to noise ratio (maximum amplifier noise)
- 2) Type and magnitude of source impedance (resistive or reactive)
- 3) Amplifier input impedance requirements
- 4) Bandwidth and maximum frequency of interest
- 5) Maximum operating temperature

- 6) Stage gain
- 7) Power supply voltage and current limitations
- 8) Circuit configuration, single or dual device

The design procedure is dependent on the type of source and each case must be considered separately. Resistive sources will be considered first because they are the least restrictive for the preamplifier.

## Resistive Sources

Preamplifiers for resistive sources are typically voltage amplifiers requiring a fixed input resistance and capacitance consistent with the maximum frequency of interest and source resistance. In most cases a resistor of the desired value connected between the gate and ground will satisfy the input resistance requirement leaving the maximum input capacitance as the major concern.

The maximum amplifier input capacitance is a function of the JFET source resistor, input resistance, source capacitance and maximum frequency. The maximum allowable input capacitance will be used in eliminating unsuitable JFET geometrics and optimizing the circuit configuration. Sometimes the JFET geometry (or type) with the lowest noise may also have an input capacitance that makes it unsuitable. The JFET input capacitance should be considered before noise in high source resistance, wideband amplifier designs.

$$C_{in} \cong C_{rs} \left( 1 + \frac{gm R_D}{1 + gm R_s} \right) + \frac{C_{gs}^*}{1 + gm R_s} \quad (9)$$

$$*C_{gs} = C_{is} - C_{rs}$$

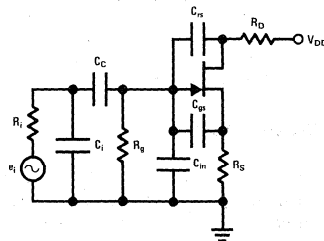


FIGURE 5. A Typical Resistive Source JFET Amplifier

If low input capacitance is required, a cascode configuration minimizes input capacitance and still allows high gain within a device type. The cascode configuration can also be used to reduce the voltage across a device, reducing device heating (for high current operation) and gate leakage currents when source impedances are very high.

Once the basic circuit configuration has been decided upon or dictated by gain, bandwidth and power supply limitations, the final JFET selection will be on noise. Redrawing the amplifier in Figure 4 with all of the noise sources, the total amplifier noise per unit bandwidth can be found.

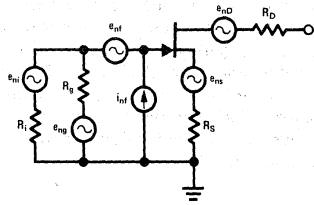


FIGURE 6. A Typical Resistive Source JFET Amplifier with Noise Sources

$$e_{nt} = \left[ e_{nig}^2 + e_{nf}^2 + e_{ns}^2 + \frac{e_{nD}^2}{A_v^2} + i_n^2 (R_i/R_g)^2 \right]^{1/2} \quad (10)$$

- where:  $e_{nig}^2$  = The noise of the parallel connection of  $R_i$  and  $R_g$   
 $e_{nf}^2$  = The noise voltage of the JFET  
 $e_{ns}^2$  = The noise of the source resistor  $R_s$   
 $\frac{e_{nD}^2}{A_v^2}$  = The noise at the drain (thermal noise of the load plus the second stage noise)  
 $i_n^2 (R_i/R_g)^2$  = The current noise contribution of the JFET

When the amplifier is operated at room temperature and moderate drain voltages, the current noise term is usually negligible with source resistances as high as  $10 \text{ M}\Omega$ . Depending on the voltage gain of the stage, the drain circuit noise may be negligible, simplifying the input noise expression.

$$e_{nt} = (e_{nig}^2 + e_{nf}^2 + e_{ns}^2)^{1/2} \quad (11)$$

The final JFET selection will be based on the noise requirements from the maximum allowable noise  $V_{MAX}$ .

$$V_{MAX} = (e_{nf}^2 + e_{ns}^2)^{1/2} \quad (12)$$

Depending on  $V_{MAX}$  and  $e_{nf}^2$  the source resistor may have to be bypassed to ground to eliminate noise of the bias resistor.

#### Capacitive Sources

Preamplifiers for capacitive sources are primarily current amplifiers requiring very high input resistance and controlled input capacitance to match the source capacitance.

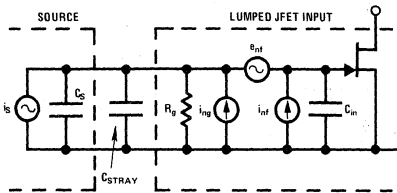


FIGURE 7. JFET Preamplifier with a Capacitive Source

The source capacitance should equal the sum of the preamplifier input capacitance and the stray capacitance for maximum frequency response and power transfer

from the signal source. Assuming the gate resistor,  $R_g$ , is so large as to not load the capacitive source, the input noise voltage is:

$$e_{nt} \cong \left[ e_{nf}^2 + (i_{nf}^2 + i_{ng}^2) \left( \frac{R_g^2}{(1 + \omega^2 R_g^2 C^2)} \right) \right]^{1/2} \quad (13)$$

where  $C = C_s + C_{in}$

with an input signal of

$$e_s \cong i_s \left( \frac{R_g^2}{1 + \omega^2 R_g^2 C^2} \right)^{1/2} \quad (14)$$

When the source and input capacitance are matched, the final JFET geometry will be selected on two criteria: the noise voltage,  $e_n$ , and the current noise from the gate leakage,  $I_{G(ON)}$ , to optimize the signal to noise ratio. As in the resistive source case, the circuit configuration and JFET selection is an iterative process using all of the external circuit constraints and device parameters and limitations.

#### Inductive Sources

Amplifiers designed for inductive sources (including transformers) require fixed input resistances (as in the resistive source case) and controlled input capacitance (as in the capacitive source case). The input noise per unit bandwidth will rise with increasing frequency to a maximum value at resonance of the inductive source and the input capacitance or when the shunt resistance of the inductor is larger than the input resistance of the amplifier.

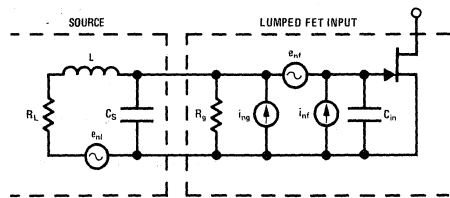


FIGURE 8. JFET Amplifier with an Inductive Source

The inductive source amplifier is the most difficult to analyze due to the complex input impedance. The input noise per unit bandwidth is given by:

$$e_{nt}^2 = e_{nf}^2 + (i_{nf}^2) (|Z_{in}|^2) + 4 kT (\text{Re} (Z_{in})) \quad (15)$$

where  $Z = X_{CIN} // R_g$

and  $Z_{in} = Z // (Z_L + R_L)$

Usually the current noise of the JFET is negligible, simplifying the expression a little, but not much. The optimization process for inductive sources is very complex and it will require the spectrum to be broken up into several small bands to arrive at a final design. Generally, a JFET with a minimum noise voltage will be the proper choice.

Transformers may be used with JFET amplifiers to minimize noise with very low source impedances. Transformers have both drawbacks and advantages and both must be examined before a transformer design is chosen. Poor frequency response, susceptibility to mechanical and magnetic pickup and thermal noise head the list of disadvantages to be weighed against two very important advantages. First, the noise voltage is transformed by the turns ratio  $N$ ; second, the resistance is transformed by  $N^2$ . These can be used to advantage by matching very low values of source resistance to a relatively noisy amplifier and still maintaining a good signal to noise ratio, i.e., the total noise at the source assuming an ideal transformer is

$$e_{nt}^2 = e_{nRs}^2 + \frac{e_{nAmp}^2}{N^2} \quad (16)$$


### SUMMARY

Low noise amplifier design concepts have been introduced for the three basic types of sources. Basic parameters ( $C_{in}$ ,  $e_n$ ,  $gm$ ) were discussed that affect both circuit configuration and JFET type. There is no universal low noise JFET or circuit configuration that solves all problems. Each low noise amplifier design is different and must be considered within its own framework of performance requirements.


### REFERENCES

- A. Van der Ziel, "Noise," Prentice-Hall, 1954.  
 Richard S.C. Cobbold, "Theory and Applications of Field-Effect Transistors," John Wiley & Sons, 1970.  
 C.D. Motchenbacher and F.C. Fitchen, "Low Noise Electronic Design," John Wiley & Sons, 1973.
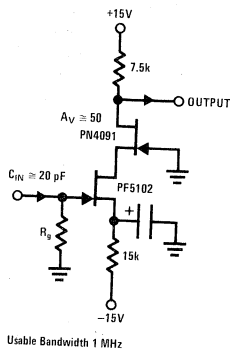
### SOME PRACTICAL LOW NOISE JFET INPUT CIRCUITS



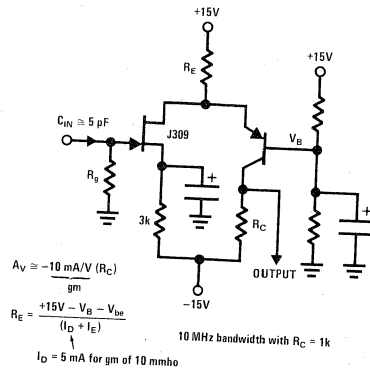a) Wide Band, Low Input Capacitance, Very Low Noise Preamplifier



b) Low Noise, Very Low Input Capacitance Video Amplifier



APPENDIX A

Important National JFET Process Parameter Guide

Test Conditions  $V_{DS} = 15V$ ,  $I_D = 1 \text{ mA}$  ( $V_{GS} = 0V$ )\*

PROCESS	$e_n @ 10 \text{ Hz}$ ( $nV/\sqrt{\text{Hz}}$ )	$e_n @ 1 \text{ kHz}$ ( $nV/\sqrt{\text{Hz}}$ )	$e_n @ 100 \text{ kHz}$ ( $nV/\sqrt{\text{Hz}}$ )	$g_{fs}$ (mmho)	$I_{G(ON)}$ ( $\mu A$ )	$C_{GD}$ (pF)	$C_{GS}$ (pF)
50	15	5	2.5	3	5V 2 $\mu A$ 10V 10 $\mu A$ 15V 1 nA	0.7	2.5
51	5	3	1.3	7	30	3	9
55	10	4	2.5	2.4	5	2	4
92	10	4	1.5	4.5	10V 20 $\mu A$ 15V 1 nA	2	4
83	10	5	2.5	2	5	1	2.5
84*	50	15	9	0.2	0.1	0.01	2
94	10	5	2.5	2	1-2	0.01	4
95	10	4	2.5	1.5	15	3.5	15
96	5	3	1.3	7	30	3	9
93	15	7	2	3.5	10V 20 $\mu A$ 15V 1 nA	1	3.2

National JFET Process Low Noise Amplifier Guide

PROCESS	50	51	55	92	83	84	93	94	95	96
Low Noise Application	Single JFET				Dual JFET					
Resistive Ultra-Low $e_n < 5 \text{ nV}/\sqrt{\text{Hz}}$ @ 10 Hz		X								X
Resistive Low Freq < 20 kHz		X	X		X			X	X	X
Resistive Wideband < 10 MHz	X	X		X	X		X	X	X	X
Resistive Wide Band > 10 MHz	X			X			X			
Resistive Very High $R_S > 10 \text{ M}\Omega$	X					X		X		
Capacitive Low C < 10 pF	X		X	X	X	X	X	X		
Capacitive High C > 20 pF		X	X						X	X
Inductive	X	X	X	X	X	X	X	X	X	X

## APPENDIX B

### NOISE PARAMETER CONVERSION

#### Noise Figure (NF) to an Effective $e_n$

It is more convenient to present noise data for bipolar transistors in the form of contours of constant noise figure at a fixed frequency or plots of noise figure versus frequency at a fixed source resistance due to large values of noise current ( $i_n$ ). Noise figure must be converted to an effective noise voltage ( $e_{nE}$ ) for comparisons to be made between a BJT and a JFET or for signal to noise ratio calculations.

By definition:

$$NF = 10 \log \frac{\text{Total Output Noise Power}}{\text{Output Noise Power of the Source}} \quad (B1)$$

From equations 1 and 2, one finds the source noise power to be

$$\text{Source Noise Power} = \frac{e_{nR}^2 \Delta f}{R_S} \quad (B2)$$

for some source resistance  $R_S$ .

Referring to *Figure 4*, the total output noise power at the input of the amplifier would be:

$$\text{Total Output Noise Power} = \frac{e_{nR}^2 \Delta f}{R_S} + \frac{e_{nf}^2 \Delta f}{R_S} + i_{nf}^2 R_S^2 \Delta f \quad (B3)$$

The noise figure (NF) can now be expressed in terms of the noise source generators,  $e_{nR}$ ,  $e_{nf}$  and  $i_{nf}$  allowing an expression to convert noise figure (NF) to an effective noise voltage ( $e_{nE}$ ).

$$NF = 10 \log \left( 1 + \frac{e_{nf}^2 + i_{nf}^2 R_S^2}{e_{nR}^2} \right) \quad (B4)$$

yielding

$$e_{nf}^2 + i_{nf}^2 R_S^2 = e_{nE}^2 = (10^{NF/10} - 1) e_{nR}^2 \quad (B5)$$

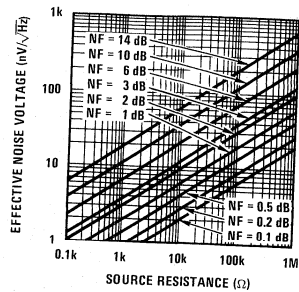


FIGURE B1. Effective Noise Voltage ( $e_{nE}$ ) vs Noise Figure and Source Resistance ( $R_S$ )

#### Noise Resistance

The effective noise voltage density ( $e_n$ ) and noise current density ( $i_n$ ) are found directly by referring to *Figure 1*, and reading the values for the corresponding resistances.

$$e_{nR} = (4 KTR)^{1/2} \quad (1)$$

$$i_{nR} = \left( \frac{4 KT}{R} \right)^{1/2} \quad (3)$$

## APPENDIX C

### JFET Current Noise

At low frequencies the current noise and voltage noise sources are uncorrelated in JFETs with the current noise being pure shot noise due to gate leakage currents. As frequency is increased, the current noise also increases starting at frequencies as low as 50 kHz in some high capacitance device types.

It has been suggested and experimentally verified that the noise current at high frequencies is due to increased gate input conductance.

$$i_n^2 = 4 KT [Re(Y_{11})]^{-1} \quad (C1)$$

$Re(Y_{11})$  is available on high frequency JFET data sheet as the real portion of the common source input admittance parameters. In effect the channel noise is coupling to the gate circuit through the source-gate and drain gate capacitances. Hence low capacitance devices exhibit lower values of noise current at high frequencies than do high capacitance devices.

# Constant Current LED

National Semiconductor  
Application Note 153  
Peter Lefferts  
October 1975



## INTRODUCTION

The NSL4944 is a simple two-lead device normally used as an AC or DC indicator, yet can also be used as a rectifier and constant current source at the same time in associated circuitry. A number of such applications will be illustrated. Further, most of the regulating circuitry is not in series with the LED. This allows the complete regulated LED to operate at only about 300 mV more than a standard red LED. Thus the NSL4944 operates on half the voltage needed by previously available regulated or resistor LEDs. The device is rated for a maximum of 18 V forward and reverse.

These characteristics provide several advantages. Unloaded TTL gates provide enough voltage, in either high or low states, to directly drive the universal indicator. Size and weight can be saved in instruments with a number of indicator lights by reducing the size of filter capacitors or voltage regulators. The NSL4944 can operate on unfiltered DC or at somewhat reduced intensity on 3 to 12 VAC rms. Since the IC within the regulated LED blocks reverse voltage, the device can be used as a low voltage rectifier or polarity indicator.

## DESIGN FEATURES

The LED and its current source, as illustrated in Figure 1, both fit within a standard LED package. The typical operating voltages shown allow the device to operate with lower supplies and take up less room than an LED and component dropping resistor.

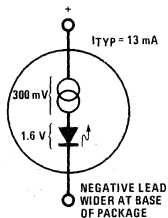


FIGURE 1. Equivalent Circuit

Figure 2 shows how some of the operating features of the NSL4944 are achieved. The rectifying characteristic occurs because the only input to the device passes through the IC's PNP emitters. These have a high reverse voltage in standard linear processing. The voltage reference and comparison amplifier operate from the same low voltage that the LED does. The big PNP transistor which passes both  $I_{LED}$  and  $I_{REF}$  can be operated almost in saturation since the comparison amplifier can pull the PNP base down to only one volt from common.

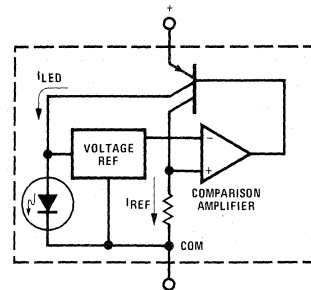


FIGURE 2. Simplified Schematic

## INDICATOR POWERING

The following figures contain some of the innumerable ways of providing power to the NSL4944.

Power and parts count is minimized by powering the indicator from a low voltage transformer winding as shown in Figure 3. This method, however, provides only

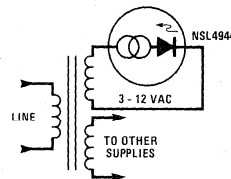


FIGURE 3. AC Power

half intensity light, but the apparent visual decrease is not as great. Some flicker occurs if the observer moves his head rapidly. The supply of Figure 4 will provide up to 87% of maximum light output. The bulk of a filter capacitor is still not needed, and at 12 VAC in, flicker will be almost imperceptible since the LED "off" periods will be less than a millisecond. In both situations, the indicator may be switched a number of ways, including bipolar transistors, since only DC can pass through the indicator.

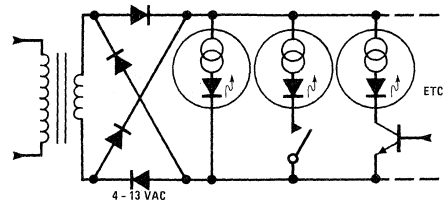


FIGURE 4. Unfiltered DC Power

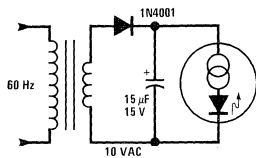


FIGURE 5. Minimizing DC Filtering

As shown in Figure 5, full intensity and zero possible flicker are achieved by minimal DC filtering. The small capacitor shown operates with 10 V p-p ripple and only about 8 V average DC, while the constant current drain characteristics of the NSL4944 allow only a few percent change in light intensity. If a system or instrument with a regulated supply has a number of LED indicators, regulator size and dissipation can be minimized by powering the regulated LEDs from the unregulated voltage.

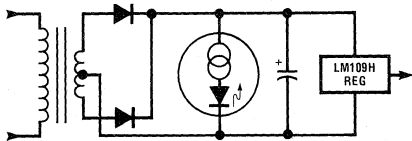


FIGURE 6. Unregulated DC

### LOGIC APPLICATIONS

The low operating voltage and constant current characteristics make the regulated LED an ideal status indicator for digital circuitry. An interesting fact to keep in mind is that full regulator current is not needed to light the LED. If, for example, only 8 mA is available (from a voltage of 1.6 to 1.9 V) the LED will light at a somewhat reduced intensity. The regulator will be switched full on instead of current limiting . . . but in such a situation it doesn't matter.

Any circuit capable of supplying 10 to 20 mA and a voltage swing of at least 1 V can switch the NSL4944 from an off to an on state. Within 25°C of room temperature, an input voltage of 1.3 V will produce little or no light, and 2.3 V will produce 70% to 90% of full output. However, with a small signal change, the pre-existing biases must be correct. The output swing of a

TTL stage goes much closer to ground than to the 5 V supply. Therefore, Figure 7-C requires a 3.5 V supply for the indicators to have complete on-off switching.

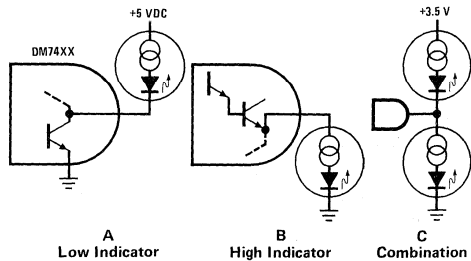


FIGURE 7. TTL Indicators

### CIRCUIT APPLICATIONS

In many circuits or small instruments the need for a constant current source or current limiter arises. FETs can generally only be used as low current sources, so for 10 mA or more, construction of a current source requires 3, 4, or more parts. If an indicator or pilot light is also needed, the regulated LED may be a very economical source of the needed constant current.

The examples below illustrate all three characteristics of the NSL4944. It is a combined rectifier, constant current source, and pilot light.

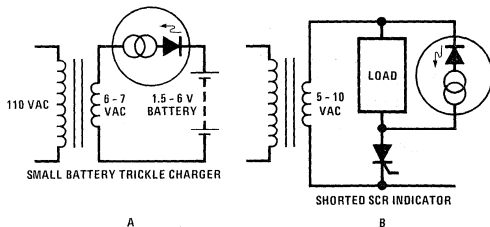


FIGURE 8.

Constant currents have a number of circuit or equipment design uses. Some of these have been combined for illustration in Figure 9. A number of LEDs can "share" a single constant current LED. Further, any of the ordinary LEDs can be turned on and off by a shunting switch without affecting operation of any of the others.

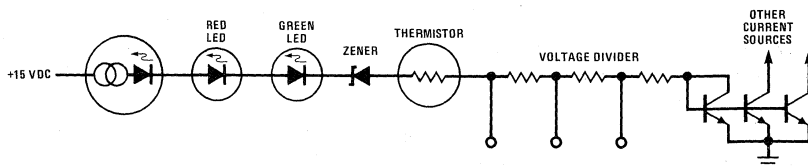


FIGURE 9. Uses for Constant Current

In equipment with unregulated supplies, or supplies having some unfiltered ripple, the 20,000  $\Omega$  impedance of the NSL4944 current source will be helpful. Supply ripple and variation passed on to Zener diodes, thermistors, and low value voltage divider bias sources will be greatly reduced. The sensitivity of low value thermistors to temperature changes will be increased. If practical, the regulated LED should be put in the same, or similar temperature environment as the thermistor used for temperature measurement. Otherwise a 20 to 40 degree temperature change at the LED would lead to an apparent one degree change sensed at the thermistor. Multiple current sources find use in some audio amplifier designs, and in power op-amp modules.

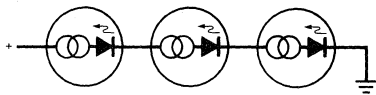


FIGURE 10. Series NSL4944s

There are some characteristics of series regulated LEDs, and current sources in general, that should be kept in mind. All the LEDs will light properly, and the string will run at the current of the least current source. This lowest value source will absorb most of the supply voltage, with the other LEDs having only the starting voltage of about 2 V across them. Thus the maximum forward voltage increases only slightly as more devices are added. In the example above it would be 22 V. However, due to non-linear reverse current characteristics, maximum reverse voltages can be added.

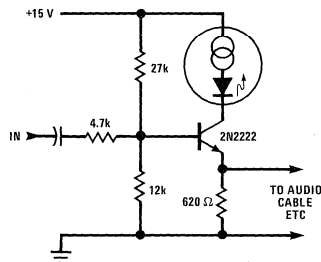


FIGURE 11. Current Limiting and Short Protection

A current source can also be a current limiter. Figure 11 shows an NSL4944 put in the collector of an emitter follower such as might be used in a pre-amp or mike mixer cable driver.

Normally voltage across the LED is only 2 V, allowing almost full supply-to-supply swing of the emitter follower output. In comparison a limiting resistor would either greatly increase output impedance, or severely limit output swing. However, if the output cable is accidentally shorted, only a little more than the rated current of the LED will flow. Output transistor dissipation actually decreases under emitter short conditions.

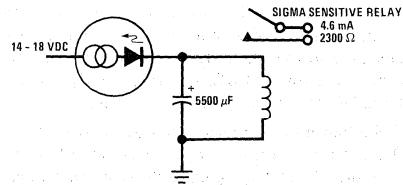


FIGURE 12. Six Second Time Delay

Logically, a constant current source is helpful in designing time delay circuits. If the circuit of Figure 12 were built with a resistor, the timing period would only be half the amount shown, and timing would vary over 50% with the supply variations shown.

Instead, the current regulated LED is still drawing within 10% of full current when the relay reaches its 11 V pull-in voltage. The 14 to 18 V supply variation will produce only about a 3% timing variation, a considerable improvement. Variations due to temperature and electrolytic capacitor tolerances will remain, however.

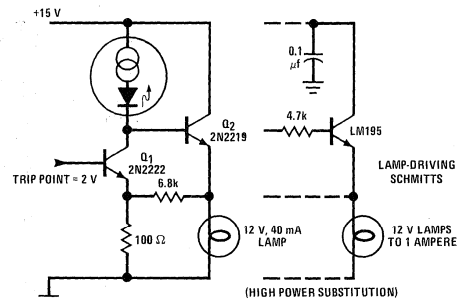


FIGURE 13. Use as Active Load

The lamp-driver Schmitt of Figure 13 illustrates a still further use of the NSL4944's constant current source. Substituting a current source for the collector resistor increases the useful voltage gain of  $Q_1$ . Further, almost full base current remains available to  $Q_2$ , even when supplying 12 V output, which would not be possible using a resistor. When the lamp and  $Q_2$  are off, most of the LED current flows in the 100  $\Omega$  resistor, thus determining the circuit's switching or trip point of 2 V.

With  $Q_1$  saturated,  $Q_2$  still provides a volt to the bulb, contributing some preheating and reducing the bulb's starting current surge. On,  $Q_2$  provides the bulb with 12 V due to the minimum voltage drop in the constant current LED. The 6.8k feedback resistor sets hysteresis at a measured 50 mV at the input. This can be varied without having to change the rest of the circuit. 10k provides almost "0" hysteresis (undesirable and unstable) while 2k sets a hysteresis of 0.5 V.


## CONCLUSION

A number of applications have been examined for a highly improved two-lead LED/IC. Its indicating capabilities, high reverse voltage, and wide constant current range may make it the most useful of the two-lead, hence simple to use, IC devices. To begin with, it can be lit from AC, unfiltered DC, and very poorly filtered or regulated DC with a savings in parts or size.

The NSL4944 may be driven from the 1 to 1.5 V swing of TTL circuitry, to the 15 to 18 V swing of Linear and MOS circuits. Its rectifying capabilities allow it to act as

a small battery charger or reverse voltage monitor for power supplies, batteries, or low voltage SCRs. For all these, and the following functions, the LED "on" indication is in addition to the constant current circuit function performed. The device's constant current can power other LEDs, Zeners, thermistors, or other current or voltage sources. It has been shown that the current regulated LED can be a current limiter, a timing element, or an active load while simplifying and improving circuit performance.

## PHYSICAL DIMENSIONS

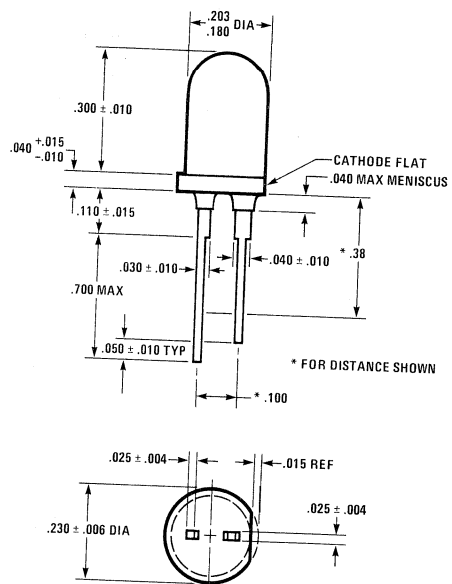

### NOTE:

1.  $\pm .015$  TOLERANCE ON ALL DIMENSIONS UNLESS OTHERWISE SPECIFIED.

# 1.3V IC Flasher, Oscillator, Trigger or Alarm

National Semiconductor  
Application Note 154  
Peter Lefferts  
December 1975



AN-154 1.3V IC Flasher, Oscillator, Trigger or Alarm

## INTRODUCTION

Most linear integrated circuits are designed to operate with power supplies of 4.5 to 40 V. Practically no battery/portable equipment is provided with indicator lights due to unacceptable power drain. Even LEDs (solid state lamps) won't light from a 1.5 V battery, and drain the common 9 V radio battery in a few hours.

The LM3909 changes all this. Obtaining long life from a single 1.5 V cell, it opens a whole new area of applications for linear integrated circuits. Sufficient voltage for flashing a light emitting diode is generated with cell voltage down to 1.1 V. In such low duty cycle applications batteries will last for months to years of continuous operation. Such flasher circuits then become practical for marking location of flashlights, emergency equipment, and boat mooring floats in the dark.

The LM3909 is simple in design, easy to use, and includes extra resistors to minimize external circuitry and the size of the completed flasher or oscillator.

## CIRCUIT OPERATION

The circuit below in figure A is the LM3909 connected as the simplest type of oscillator. Ignoring the capacitor for a moment, and assuming 1.5 V on pin 5, current will flow in the 3k and 6k timing resistors through the emitter of Q<sub>1</sub>. This current will be amplified by about 3 by Q<sub>2</sub> and passed to the base of Q<sub>3</sub>. Q<sub>3</sub> will then conduct, pulling down on the base of Q<sub>4</sub> and hence the base of Q<sub>1</sub>. This is a negative feedback since it will reduce timing resistor current and current to the power transistor's base until a balance is reached. This will occur with the collector of Q<sub>3</sub> at about 0.5 V, the base of Q<sub>4</sub> at about 1 V, and a very small voltage from pin 8 to ground. The difference between these two voltages is the base-emitter drop of Q<sub>1</sub> and 2/3 the base-emitter drop of Q<sub>4</sub> as set by the high resistance divider from its base to emitter.

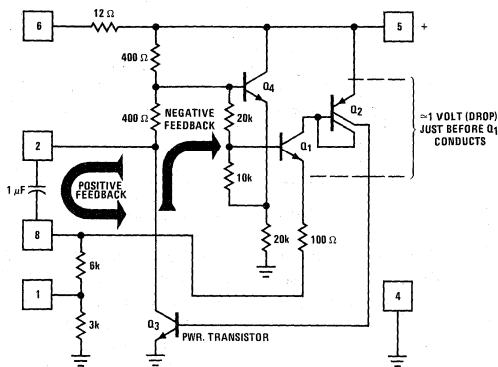


FIGURE A.

Note that negative feedback *voltage* is attenuated by at least 2 due to the divider of two 400 Ω resistors. Now considering the capacitor, its positive feedback is initially unity. Therefore the DC bias condition and the temporary excess positive feedback conditions are met and the circuit must oscillate.

The waveform at pin 8 of the above oscillator is shown below. The waveform at pin 2, the power transistor collector, is almost a rectangle. It extends from a saturation voltage of 0.1 V or less to within about 0.1 V of the supply voltage. The "on" period of course coincides with the negative pulses at pin 8. Other circuit voltages can easily be inferred from these two waveforms.

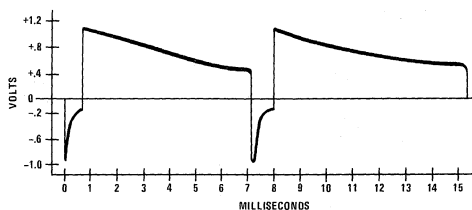


FIGURE B.

The simplicity of LED and incandescent pilot lamp flashers is illustrated below. In the LED flasher, the LM3909 uses the single capacitor for both timing and voltage boosting.

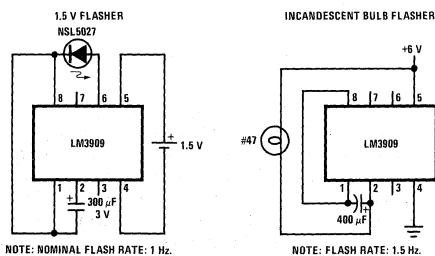


FIGURE 1. Two Simple Flashers

The LM3909, although designed as a LED flasher, is ideal for other applications such as high current, trigger pulse for SCRs and "Triacs." The frequency of oscillation adjusts from under 1 Hz to hundreds of kHz. Waveshape can be set from pulses a few μs wide to approximately a square wave. Thus the LM3909 can perform as a sound effects generator, an audible alarm, or audible continuity checker. Finally it can be a radio (detector/amplifier), low power one-way intercom, two-way telegraph set, or part of a "mini-strobe" light flashing up to 7 times per second.

Operating with only a 1.5 V battery as a supply gives the LM3909 several rather unique characteristics. First, *no* known connection can cause immediate destruction of the IC. Its internal feedback loop insures self-starting of properly loaded oscillator circuits. Experimenters can safely explore the possibilities of the LM3909 as an AC amplifier, one-shot, latch circuit, resistance limit detector, multi-tone oscillator, heat detector, or high frequency oscillator.

With the accent on the practical, a brief circuit description will be given followed by circuits in the following application areas:

- Flasher & Indicator Applications
- Audio & Oscillator Applications
- Trigger & Other Applications

For those who want to modify or design their own circuits using the LM3909, application hints will be covered near the end of this note.

### CIRCUIT DESCRIPTION

The circuit of figure 2 again shows the typical 1.5 V LED flasher, but with the internal circuitry of the IC illustrated.

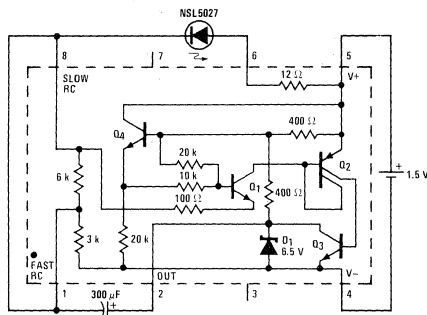


FIGURE 2. Circuit Operation

The flasher achieves minimum power usage in two ways. Operated as above, the LED receives current only about 1% of the time. The rest of the time, all transistors but  $Q_4$  are off. The 20k resistor from  $Q_4$ 's emitter to supply-common draws only about 50  $\mu$ A. The 300  $\mu$ F capacitor is charged through the two 400  $\Omega$  resistors connected to pin 5 and through the 3k resistor connected to pin 4 of the circuit.

Transistors  $Q_1$  through  $Q_3$  remain off until the capacitor becomes charged to about 1 V. This voltage is determined by the junction drop of  $Q_4$ , its base-emitter voltage divider, and the junction drop of  $Q_1$ . When voltage at pin 1 becomes a volt more negative than that at pin 5 (the supply positive terminal)  $Q_1$  begins to conduct. This then turns on  $Q_2$  and  $Q_3$ .

The LM3909 then supplies a pulse of high current to the LED. Current amplification of  $Q_2$  and  $Q_3$  is between 200 and 1000.  $Q_3$  can handle over 100 mA and rapidly pulls pin 2 close to supply common (pin 4). Since the capacitor is charged, its other terminal at pin 1 goes

below the supply common. The voltage at the LED is then higher than battery voltage, and the 12  $\Omega$  resistor between pins 5 and 6 limits the LED current.

Many of the other oscillator circuits work in a similar fashion. If voltage boost is not needed (with or without current limiting) loads can be hooked between pins 2 and 6 or pins 2 and 5.

### APPLICATIONS: Flasher & Indicator

Differing uses and supply voltages will require adjustment of flashing rates. Often it is convenient to leave the capacitor the same value to minimize its size, or to fix the pulse energy to the LED. First, the internal RC resistors can be used to obtain 3k, 6k, or 9k by hooking to or shorting the appropriate pins. Further adjustment methods are shown in the two parts of figure 3 below.

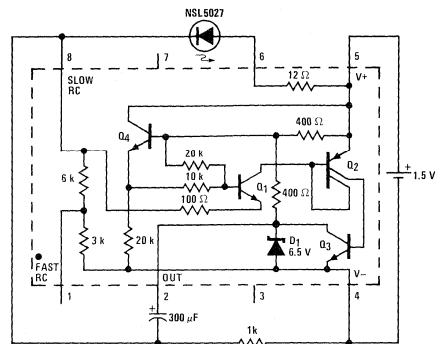


FIGURE 3a. Fast Blinker

In figure 3a, it can be seen that the internal RC resistors are shunted by an external 1k between pins 8 and 4. This will give a little over 3 times the flashing rate of the typical 1.5 V flasher of figure 1.

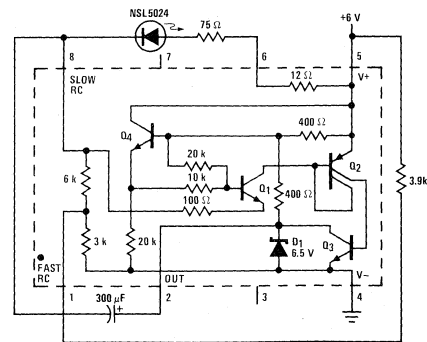


FIGURE 3b. 6 Volt Flasher

The 3.9k resistor in figure 3b connected from pin 1 to the 6 V supply raises voltage at the bottom of the 6k RC resistor. Charging current through that resistor is greatly reduced, bringing flashing rate down to about that of the 1.5 V circuit (1 Hz). As will be explained later, this biasing method also insures starting of oscillation even under unfavorable conditions.



Two precautions are taken for circuit reliability. The added 75  $\Omega$  series resistor for the LED keeps current peaks within safe limits for the diode and IC. Also, in operation above a 3 V supply, the electrolytic capacitor sees momentary voltage reversals. It should be rated for periodic reversals of 1.5 V.

A continuously appearing indicator light can also be powered from a single 1.5 V cell. Duty cycle and frequency of the current pulses to the LED are increased until the average energy supplied provides sufficient light. At frequencies above 2 kHz, even the fastest movement of the light source or the observer's head will not produce significant flicker.

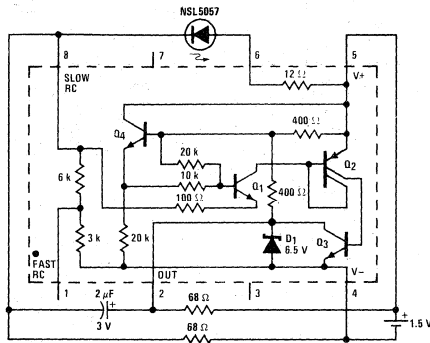


FIGURE 4. "Continuous" 1.5 V Indicator

Since this indicator powering circuit uses the smallest capacitor that will reliably provide full output voltage, its operating frequency is well above the 2 kHz point. The indicator is not, however, intended as a long life system, since battery drain is about 12 mA.

High frequency operation requires addition of two external resistors, typically of the same value. One, of course, shunts the high internal timing resistors. If only this one were used, the capacitor charging current would have to pass through the two 400  $\Omega$  resistors internally connected between pin 5 and the collector of Q<sub>3</sub>. Oscillation at a slower rate and lower duty cycle than desired would occur, and oscillation might cease alto-

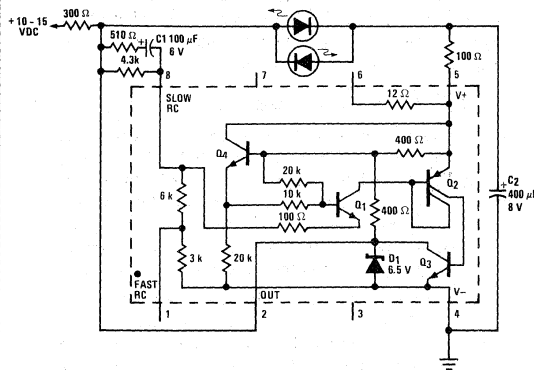


FIGURE 5. Alternating Flasher

gether before the battery was fully discharged. The second 68  $\Omega$  resistor shunting the two 400  $\Omega$  resistors eliminates these problems.

The circuit above is a relaxation type oscillator flashing 2 LEDs sequentially. With a 12 VDC supply, repetition rate is 2.5 Hz. C<sub>2</sub>, the timing and storage capacitor, alternately charges through the upper LED and is discharged through the other by the IC's power transistor, Q<sub>3</sub>.

If a red/green flasher is desired, the green LED should have its anode or plus lead toward pin 5 (like the lower LED). A shorter but higher voltage pulse is available in this position.

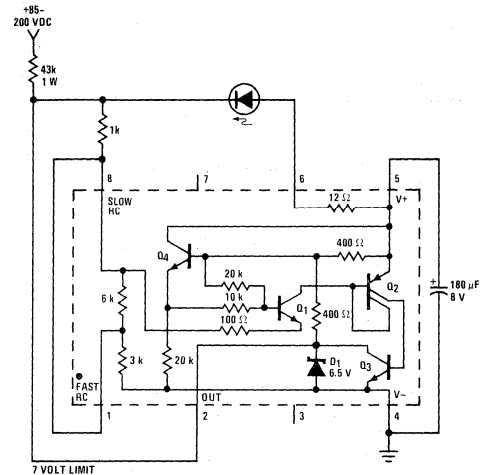


FIGURE 6. Safe, High Voltage Flasher

Indication or monitoring of a high voltage power supply at a remote location can be done much more safely than with neon lamps. If the dropping resistor (43k as in figure 6 above) is located at the source end, all other voltages on the line, the IC, and the LED will be limited to less than 7 V, above ground.

The timing capacitor is charged through the dropping resistor and the two 400  $\Omega$  collector loads between pins 2 and 5 of the IC. When capacitor voltage reaches about 5 V, there is enough voltage across the 1k resistor (to pin 8) to turn on Q<sub>1</sub>, and hence trigger on the whole IC to discharge the capacitor through the LED.

There are many other LED applications and variations of circuits. A chart outlining operation of the above circuit at various voltages appears on the LM3909 data sheet. Also shown are circuits for adjusting the flash rate, flashing 4 LEDs in parallel, and details for building a blinking locator light into an ordinary flashlight.

Incandescent bulbs can also be flashed, as already illustrated in figure 1. However, most such bulbs draw more than the 150 mA that the LM3909 can switch. The two following circuits therefore use an added power transistor rated at 1 A or more. In each circuit, an NPN transistor is used, so the power transistor's base drive is obtained from the common or ground pin of the flasher IC.

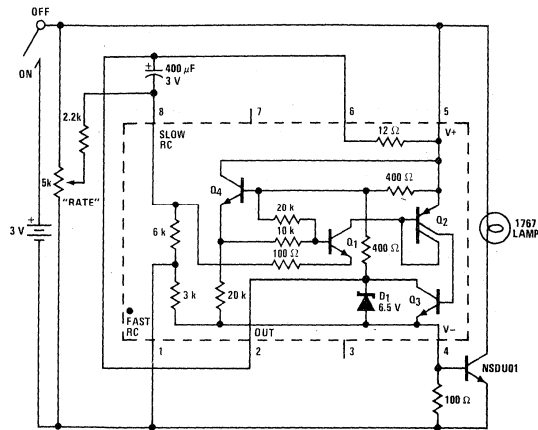


FIGURE 7. "Mini-Strobe" Variable Flasher

The 3 V "mini-strobe" of figure 7 may be used as a variable rate warning light or for advertising or special effects. The rate control is so wide range that it adjusts from no flashes at all to continuously on. Chosen for rapid response, the miniature 1767 lamp can be flashed several times a second.

A "mini-strobe" circuit was tested in a Lantern Flashlight with a large reflector. In a dark room, the flashes were almost fast enough to stop a person's motion. As a toy, the fast setting can mimic the strobes at rock concerts or the flicker of old-time movies.

Figure 8 below shows a higher power application such as would use an automotive storage battery for power. It provides about a 1 Hz flash rate and powers a lamp drawing a nominal 600 mA.


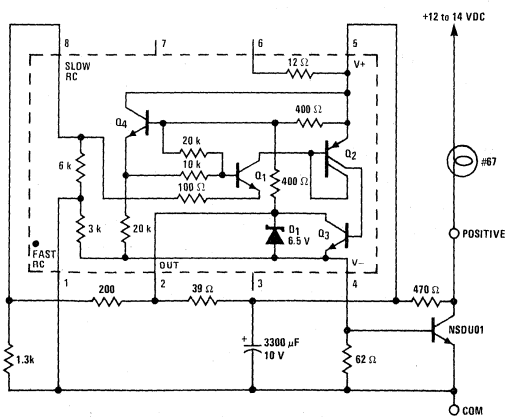


FIGURE 8. 12 Volt Flasher (2 Wire)

A particular advantage of this circuit is that it has only 2 external wires and thus may be hooked up in either of the two ways shown below in figure 9. Further, no circuit failure can cause a battery drain greater than that of the bulb itself, continuously lit.

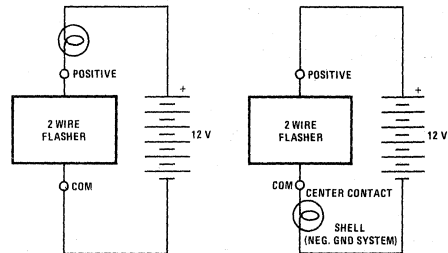In the circuit of figure 8, the 3300 µF capacitor performs a number of other functions. It makes the LM3909 immune to supply spikes, and provides the



NOTE: IF FLASHER CASE INSULATED, IT WILL OPERATE IN POSITIVE OR NEGATIVE GROUND SYSTEMS.

FIGURE 9. 2 Wire Flasher Usage

means of limiting the IC's supply voltage. Since the LM3909 can only operate with 7.5 V or less on pin 5 (in this circuit) the 200 Ω/1.3k divider attached to pin 8 of the IC causes it to turn fully on at 7 V or less on pin 5. Then the LM3909 discharges the timing capacitor (its own supply voltage) to 4 V or less, whereupon it turns off. The capacitor discharge current comes out of pin 4 of the IC, turning on the NSD U01 transistor. It is the large size of the timing capacitor that allows it to store all the needed energy for turning on the power transistor. This in turn permits the whole flasher circuit to operate as a 2 wire device.

Many other flasher possibilities exist. LED flash rate can be varied from 0 to 20 Hz, or a number of LEDs may be flashed in parallel. With a 3 V supply, yellow and green LEDs may be flashed. A 6 V incandescent "emergency lantern" can be made and its PR-13 bulb may be made to give continuous light or flash by switch selection. This is a more reliable, longer lived system than a lantern with a second thermal flasher bulb. The NSL4944 Current Regulated LED makes possible flashing many LEDs in parallel or with high voltages without series resistors.

#### APPLICATIONS: Audio & Oscillator

Very economical continuity checkers, tone generators, and alarms may be made from the LM3909. No matching transformer is needed because the 150 mA capability of the LM3909 output can drive many standard permanent magnet (transistor radio) loudspeakers directly. The 1.5 V battery used in most applications is both lower in cost and longer lasting than the conventional 9 V battery.

In the continuity checker of figure 10, a short, up to about 100 Ω, across the test probes provides enough power for audible oscillation. By probing 2 values in quick succession, small differences such as between a short and 5 Ω can be detected by differences in tone.

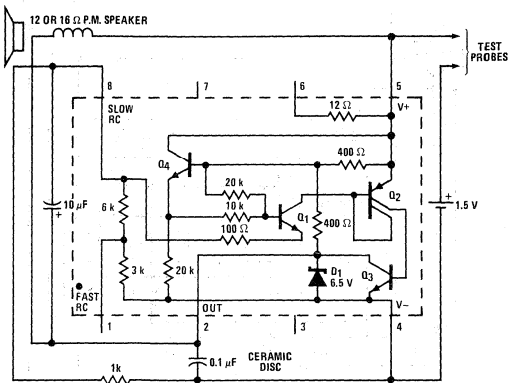


FIGURE 10. "Buzz Box" Continuity and Coil Checker

A novel use of this circuit is found in setting the timing of certain types of motorcycles. This is due to the difference in tone that can be heard from the tester depending whether there is a short or not across the low resistance primary of the 'cycle's ignition coil. In other words, the difference between a 1  $\Omega$  resistor and a 1  $\Omega$  inductor can be heard. Quick checks for shorts and opens in transformers and motors can therefore be made.

Darkrooms, laundry rooms, laboratories, and cellar workshops can often suffer damage from spills or water seepage ruining lumber, chemicals, fertilizer, bags of dry concrete, etc. The circuit of figure 11 is safe on potentially damp floors since there is no connection to

the power line. Further, its standby battery drain of 100  $\mu$ A yields a battery life close to (or, according to some experiments, exceeding) shelf life.

Without moisture, multivibrator transistor  $Q_a$  is completely off, and its collector load (6.2k) provides enough current to hold pin 8 of the LM3909 above 0.75 V where it cannot oscillate. When the sense electrodes pass about 0.25  $\mu$ A, due to moisture,  $Q_a$  starts turning on, and since  $Q_b$  is already partially biased on, positive feedback now occurs.  $Q_a$  and  $Q_b$  are now an astable multivibrator which starts at about 1 Hz and oscillates faster as more leakage passes across the sense electrodes.

This "multi" then acts as both an amplifier and a modulator. The pulse waveform at the collector of  $Q_a$  varies the timing current through the 3.9k resistor to pin 8 of the LM3909 resulting in a distinctively modulated tone output.

The sensor should be part of the base of the box the alarm circuitry is packaged in. It consists of two electrodes six or eight inches long spaced about 1/8 inch apart. Two strips of stainless steel on insulators, or the appropriate zig-zag path cut in the copper cladding of a circuit board will work well. The bare circuit board between the copper sensing areas should be coated with warm wax so that moisture on the floor, *not* that absorbed by the board, will be detected. The circuit and sensor can be tested by just touching a damp finger to the electrode gap.

Minimum cost, simplicity, and very low power drain are the aims of the Morse Code set of figure 12. One oscillator simultaneously drives speakers at both sending and receiving ends. Calculations and actual use tests indicate life of a single alkaline penlight cell to be 3 months to over a year depending on usage. "Buzzer" type sets use two or more batteries with much shorter life.

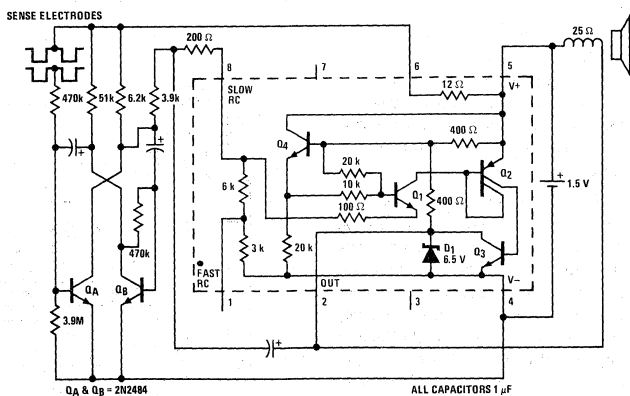


FIGURE 11. Water Seepage Alarm

Commonly available, low cost 8  $\Omega$  speakers are effectively in series to better match LM3909 characteristics. The three wire system and parallel telegraph keys allow beginners and children to use the set without having to understand use of a "send-receive" switch.

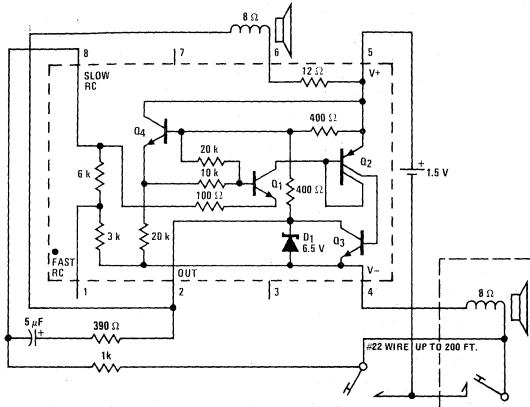


FIGURE 12. Morse Code Set

The two resistors are added to obtain a suitable average power output and electrically force the oscillator toward the desired 50% duty cycle. Acoustically, both speakers are operated at resonance (about 400 Hz in the prototype) for maximum pleasing tone with minimum power drain. Each of the two speaker enclosures has holes added to augment this resonance. For each different type or brand of speaker and size of box, hole and capacitor sizes will have to be determined by experiment for the most stable resonant tone over the expected battery voltage variation.

Experiments with the above circuit led to development of the circuit in figure 13. It is optimized to oscillate at any acoustic load frequency of resonance. With just a speaker, oscillation occurs at the speaker cone "free-air" resonance. If the speaker is in an enclosure with a higher resonant frequency . . . this becomes the frequency at which the circuit oscillates.

An educational audio demonstration device, or simply an enjoyable toy, has been fabricated as follows. A roughly cubical box of about 64 in.<sup>3</sup> was made with one end able to slide in and out like a piston. The box was stiffened with thin layers of pressed wood, etc. Minimum volume with the piston in was about 10 in.<sup>3</sup>. Speaker, circuit, battery, and all were mounted on the sliding end with the speaker facing out through a 2 1/4 in. hole. A tube was provided (2 1/2 in. long, 5/16 in. ID) to bleed air in and out as the piston was moved while not affecting resonant frequency.

"Slide tones" can be generated, or a tune can be played by properly positioning the piston part and working the push button. Position and direction of the piston are

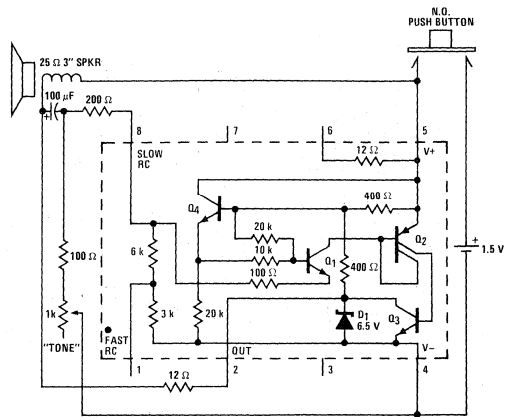


FIGURE 13. Electronic "Trombone"

rather intuitive, so it is not difficult to play a reasonable semblance of a tune after a few tries.

The 12  $\Omega$  resistor in series with pin 2 (output transistor Q<sub>3</sub>'s collector) and the speaker, decouples voltages generated by the resonating speaker system from the low impedance switching action of Q<sub>3</sub>. The 100  $\mu$ F feedback capacitor would normally set a low or even sub-audio oscillation frequency. Therefore, the major positive feedback voltage to pin 8 is the resonant motion generated voltage from the speaker voice coil. Therefore the LM3909 will continue to drive the speaker at the resonance with the highest combined amplitude and frequency.

It can be seen already that the LM3909, having direct speaker drive and resonance following capability, can do things that are a lot less practical with older timer and unijunction circuitry. Two final "sound effect" type of circuits are illustrated below.

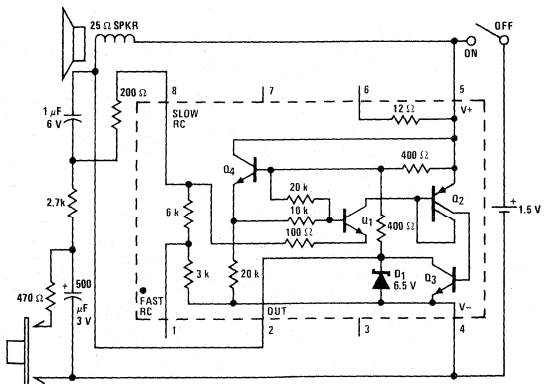


FIGURE 14a. Fire Siren

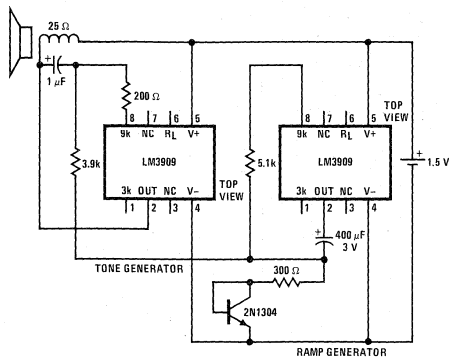


FIGURE 14b. Whooper Siren

The siren of figure 14a produces a rapidly rising wail upon pressing the button, and a slower "coasting down" upon release. If it is desirable to have the tone stop sometime after the button is released, an 18k resistor may be placed between pins 8 and 6 of the IC. The sound is then much like that of a motor driven siren.

In this circuit, the oscillation must not be influenced by acoustic resonances. The  $1\ \mu\text{F}$  capacitor and  $200\ \Omega$  resistor determine a pulse to the speaker that is wider than that for flashing LEDs, but much narrower than is used in the tuned systems of figures 12 and 13. The repetition rate of speaker pulses is determined by the  $2.7\text{k}$  resistor, and the charge on the  $500\ \mu\text{F}$  capacitor. Discharging this capacitor with the pushbutton increases current in the  $2.7\text{k}$  resistor causing a rapid upshift in tone.

The "whooper" of figure 14b sounds somewhat like the electronic sirens used on city police cars, ambulances, and airport "crash wagons." The rapid modulation makes the tone seem louder for the same amount of power input.

The tone generator is the same as in the previous siren. Instead of a pushbutton, a rapidly rising and falling modulating voltage is generated by a second LM3909 and its associated  $400\ \mu\text{F}$  capacitor. The 2N1304 transistor is used as a low voltage (germanium) diode. This transistor along with the large feedback resistor ( $5.1\text{k}$  to pin 8) forces the ramp generator LM3909 into an unusual mode of operation having longer "on" periods than "off" periods. This raises the average tone of the tone generator and makes the modulations seem more even.

#### APPLICATIONS: Trigger & Other

With its high pulse current capability, the LM3909 is a good pulse-transformer driver. Further, it uses fewer parts and operates more successfully from low voltage supplies than do the equivalent unijunction circuits. The "Triac" trigger of figure 15 operates from a 5 V logic supply and provides gate trigger pulses of up to 200 mA.

With no gate input, or a TTL logic high input, the LM3909 is biased off since pin 1 is tied to  $V+$ . With a logic low at the gate in, the IC provides  $10\ \mu\text{s}$  pulses at about a 7 kC rate. A TTL gate loaded only by this circuit is assumed since otherwise worst-case voltage swing may be insufficient. This trigger is not of the "Synchronized Zero Crossing" type since the first trigger pulse after gating on could occur at any time. However, the repetition rate is such that after the first cycle, a triac is triggered within 8 V of zero with a resistive load and a 115 VAC line.

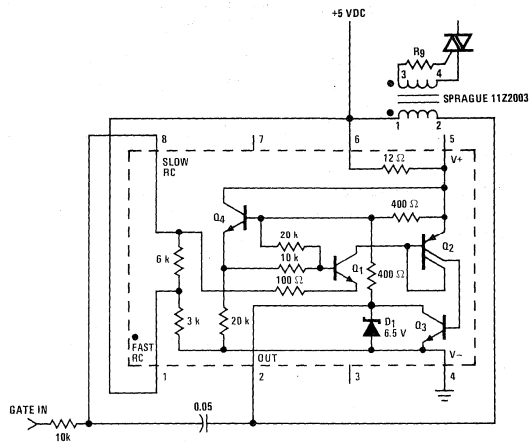


FIGURE 15. Triac Trigger

The standard Sprague PC mounting transformer provides a 2:1 current step-up, and suitable isolation between the low voltage circuitry and power lines up to 240 VAC. Resistor  $R_g$ , which includes transformer winding resistance, can be as little as 3 or  $4\ \Omega$  for high current triacs. Low current types may need excessive "holding" current with such low  $R_g$ , so it may be raised to as much as  $100\ \Omega$  with a sensitive gate triac.

Oscillation of the LM3909 will start when the DC bias at pin 8 is between 1.6 and 3.9 V. In figure 15, pin 8 is connected between the  $10\text{k}$  input resistor and a  $6\text{k}$  resistor to 5 V. With 3.8 V in, pin 8 is at 4.5 V so there is no oscillation. With 1 V, or less, in, pin 8 is at 3.5 V or below and oscillation occurs. From this example, it can be seen that other input resistors or bias dividers can be calculated to gate the LM3909 triac trigger from other logic levels.

A useful electronic lab device is a precision square wave generator/calibrator. If the output is held at a few tenths percent of 1 V, peak-to-peak, it is useful in calibrating oscilloscopes and adjusting scope probes. Many lower cost or battery-portable oscilloscopes do not have this feature built in. Also it is useful in checking gain and transient response of various amplifiers including "hi-fi" power amplifiers.

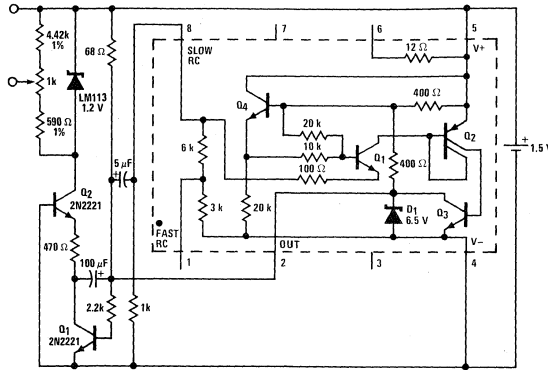


FIGURE 16. 'Scope Calibrator

Battery powered equipment is free from both the inconvenience of a line cord, and from some of the noise and hum effects of equipment attached to the power line. Operation for over five hundred hours from a single flashlight "D" cell is the bonus provided by the circuit below. The lowest reference voltage regulator available, the LM113, is used in conjunction with a current source, and the voltage boost characteristic of the LM3909.

Output is a clean rectangular wave which can be adjusted to exactly a 1 V amplitude. A rectangular wave of approximately 1.5 ms "on" and 5.5 ms "off" was chosen for circuit simplicity and low battery drain. Waveform clipping is virtually flat due to complete turn-off of the current switch  $Q_2$  and the typical "on" impedance of  $0.2 \Omega$  provided by the LM113. The 0.01% temperature coefficient of the LM113 at room temperature allows negligible drift of the waveform amplitude under laboratory conditions. Loading by a 'scope probe will also be insignificant.

The circuit will work properly down to battery voltages of 1.2 V. This is because the 100  $\mu\text{F}$  electrolytic capacitor drives the emitter of  $Q_2$  below the supply minus terminal. At a battery voltage of 1.2 V, the collector of  $Q_2$  can still swing more than 1.6 V.  $Q_1$  uses the "off" periods of the LM3909 to insure that the 100  $\mu\text{F}$  capacitor is charged to almost the entire battery voltage. Thus when the LM3909 turns on and pin 2 drives almost to the minus supply voltage, the negative side of the capacitor is driven 0.9 to 1.2 V below this terminal. Low battery voltage cannot lead to an undetected error in the 1 V squarewave. This is because the waveform becomes distorted rather than just decreasing in amplitude as battery voltage becomes too low.

Taking advantage of the versatility and the indestructibility of the LM3909 by a 1.5 V battery, the IC can become an ideal teaching means, or experimental device for the young electronic hobbyist. As well as the circuits already presented, the LM3909 can be made to work as amplifier, radio, and even logic type circuits. The ideas of negative and positive feedback can be presented. The circuits presented below are intended as illustrations or demonstrations of circuitry concepts such

as would be used in an experimenter's kit. They are not meant to be used as parts of finished commercial products with specific performance specifications. In other words, working circuits have been breadboarded, but no measurements of performance such as frequency range and distortion have been attempted.

Both tuned circuits above use standard AM radio ferrite antenna coils (loopsticks) with a tap 40% of the turns up from one end. The oscillator works up to 800 kHz or so, and the radio tunes the regular AM broadcast band. Both also use standard (360 pF) AM radio tuning capacitors.

The oscillator has the normal capacitive positive feedback used with LM3909 circuits, but with frequency determined by the tuned circuit loading the output circuit. Detailed operating descriptions of these experimenter's circuits will not be attempted in order to keep down the length of this note. Near the end, a discussion of the IC's general theory of operation will be given, which should help in understanding the individual circuits.

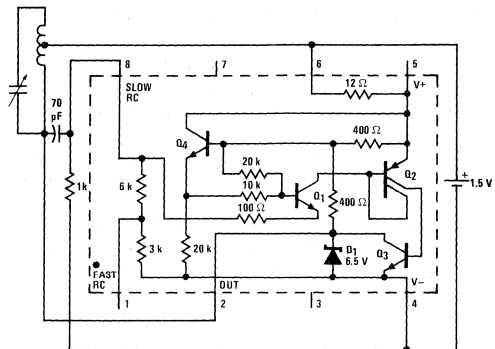


FIGURE 17. R.F. Oscillator

In the radio circuit of figure 18, the LM3909 acts as a detector amplifier. It does not oscillate because there is no positive feedback path from pin 2 to pin 8. The tuning ability is only as good as a simple "crystal set," but a local radio station can provide listenable volume

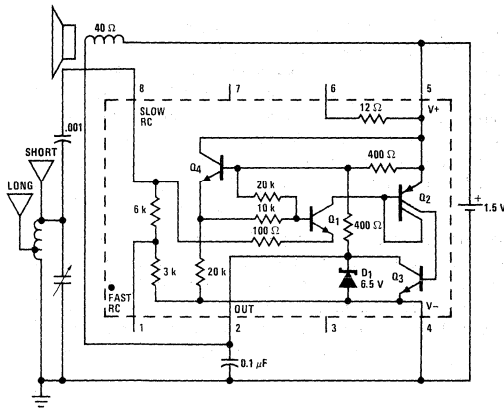


FIGURE 18. Radio

with an efficient 6 inch loudspeaker. Extremely low power drain allows a month of continuous radio operation from a single "D" flashlight cell.

Antennae for the radio circuit can be short (10 to 20 feet) and connected directly to the end of the antenna coil as illustrated. Longer antennae (30 to 100 feet) work better if attached to the previously mentioned tap on the coil . . . also illustrated.

The following two circuits are examples of logic or computer type functions. They use 3 V power supplies (2 cells) because the LM3909 was designed not to have any stable or "latching" states with a 1.5 V supply.

Switches on both the above circuits are momentary types. In each case a small charge or impulse affects the circuit's state. The circuit of figure 19 switches to and *holds* its condition whenever the switch changes sides, even if contact is made only very briefly. The circuit of figure 20 delivers about a 1/2 second flash from the LED every time its pushbutton makes contact, whether briefly or for a much longer period of time. Such circuits are used with keyboards, limit switches, and other mechanical contacts that must feed data into electronic digital systems.

By again leaving out the positive feedback capacitor, the LM3909 can become a low power amplifier. This little audio amplifier can be used as a one-way intercom or for "listening in" on various situations. Operating current is only 12 to 15 mA. It can hear fairly faint sounds, and someone speaking directly into the microphone generates a full 1.4 V peak-to-peak at the loudspeaker.

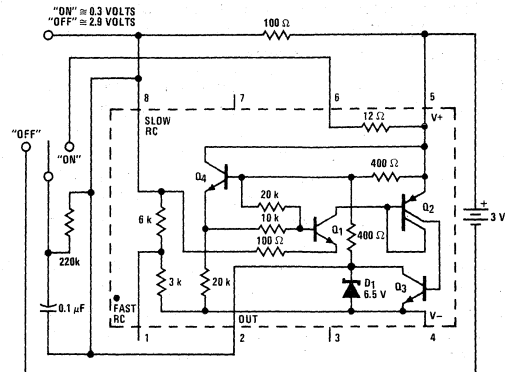


FIGURE 19. Latch Circuit

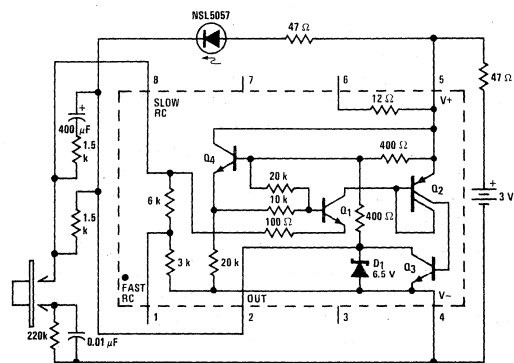


FIGURE 20. Indicating One-Shot

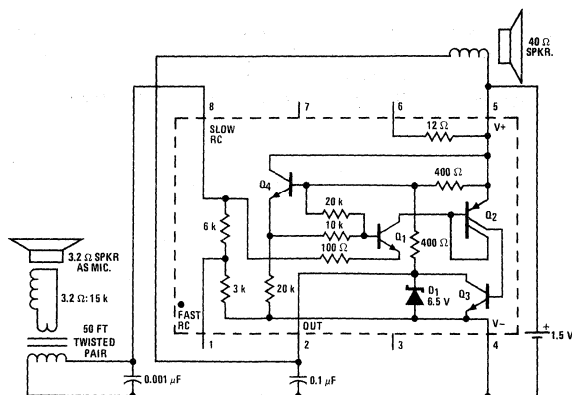


FIGURE 21. Mini-Power Amplifier

## APPLICATION HINTS

With 1.5 V supplies, certain problems can occur to stop oscillation or flashing. Due to the way gain is achieved and the type of feedback, too heavy a load may stop an LM3909 from oscillating. 20  $\Omega$  of pure resistive load will sometimes do it. Strangely enough, lamp filaments, probably because of some inductance, don't seem to follow this rule. Also in flasher circuits, an LED with leakage or conductivity between 0.9 and 1.2 V will stop the LM3909. Maybe 1% of LEDs will have this defect because they are not often tested for it.

Great frequency stability was not one of the design aims of the LM3909. In LED flasher circuits it is better than might be expected because the negative temperature coefficient of the LED partially compensates the IC. We planned it this way. Simple oscillators, without the LED, are uncompensated for temperature. This is due to using 1 2/3 of a silicon junction drop as the on-off trip point and the use of the integrated timing resistors with their positive temperature coefficient. Further, most capacitors of 1  $\mu$ F or over, shown in the circuits, will usually be electrolytics for size reasons. These, however, are not particularly stable with temperature and their initial tolerances vary greatly with type of capacitor.

In most of the oscillator circuits, frequency is also proportional to battery voltage. This must be considered when starting with a completely unused cell at 1.54 V or so and deciding what the "end-of-life" voltage is to be. This can be in the range of 1.1 to 0.9 V, a drastic change. It helps to remember how bright flashlights are with a fresh set of batteries, and how dim they are when the batteries are finally changed.

Flashers and tone generators for alarms are not, however, demanding for stability. Flash rate changes of 50% or tone shifts of 1/2 an octave are not particularly annoying or even too noticeable.

One interesting point is that the low operating power of most of the circuits presented allows them to be powered by solar cells as well as regular batteries. In bright sunlight, 3 to 4 cells in series will be needed. In dimmer light, 4 to 6 cells will do the job. Current from cells way under an inch in area generally will be sufficient, but circuits drawing a high pulse current (such as SCR triggers) will need a surge storage capacitor across the solar cell array.

The LM3909 was designed to be inherently self-starting as an oscillator, and LED flasher circuits are, at any voltage, because the load is nonlinear. A load with sufficient self inductance will always self-start, although

possibly at a higher than expected frequency. There is an exception for largely resistive loads on an oscillator operating with a supply larger than 2 or 2.5 V. A stable state exists with Q<sub>3</sub> turned completely "on" and the timing resistors from pin 8 to the supply minus still drawing current. A reliable solution is to bias pin 8 (for instance with a resistor to V+) so that its DC voltage is one half V less than half the supply voltage.

The duty cycle of the basic LED flasher is inherently low since the timing capacitor is also driving the very low LED "on" impedance. For other oscillators the "on" duty cycle can be stretched by adding resistance in series with the timing capacitor. Additionally, nonlinear resistance can be used as timing resistance. (See figure 14b.)

## CONCLUSION

Applications covered in this note range in use from toys to the laboratory, and in frequency from DC to RF. The LM3909 can be used to amuse, teach, or even upon occasion to save a life. As a practical cost consideration the LM3909 IC can often replace a circuit having a number of transistors, associated parts, and high assembly cost.

Further, the LM3909 demonstrates the practicality of very low voltage electronic circuits. They can work at high efficiencies if ingenuity is used to design around transistor junction drops. In such circuits stresses on parts are so low that extremely long life can be predicted. Often transistors, capacitors, etc. that would be rejects at higher voltages can be used. Voltage dividers, protective diodes, etc. often needed at higher voltages can be left out of designs. Power drains are so low that circuits can be made that will last months to years on a single cell.

A single cell is more reliable and has a higher energy density than multiple cells. This is due to lack of cell interconnections and insulation as well as elimination of packaging to hold multiple cells in place.



# Specifying A/D and D/A Converters

National Semiconductor  
Application Note 156  
Jim Sherwin  
February 1976



The specification or selection of analog-to-digital (A/D) or digital-to-analog (D/A) converters can be a chancey thing unless the specifications are understood by the person making the selection. Of course, you know you want an accurate converter of specific resolution; but how do you insure that you get what you want? For example, 12 switches, 12 arbitrarily valued resistors, and a reference will produce a 12-bit DAC exhibiting 12 quantum steps of output voltage. In all probability, the user wants something better than the expected performance of such a DAC. Specifying a 12-bit DAC or an ADC must be made with a full understanding of accuracy, linearity, differential linearity, monotonicity, scale, gain, offset, and hysteresis errors.

This note explains the meanings of and the relationships between the various specifications encountered in A/D and D/A converter descriptions. It is intended that the meanings be presented in the simplest and clearest practical terms. Included are transfer curves showing the several types of errors discussed. Timing and control signals and several binary codes are described as they relate to A/D and D/A converters.

## MEANING OF PERFORMANCE SPECS

**Resolution** describes the smallest standard incremental change in output voltage of a DAC or the amount of input voltage change required to increment the output of an ADC between one code change and the next adjacent code change. A converter with  $n$  switches can resolve 1 part in  $2^n$ . The least significant increment is then  $2^{-n}$ , or one least significant bit (LSB). In contrast, the most significant bit (MSB) carries a weight of  $2^{n-1}$ . Resolution applies to DACs and ADCs, and may be expressed in percent of full scale or in binary bits. For example, an ADC with 12-bit resolution could resolve 1 part in  $2^{12}$  (1 part in 4096) or 0.0245% of full scale. A converter with 10V full scale could resolve a 2.45mV input change. Likewise, a 12-bit DAC would exhibit an output voltage change of 0.0245% of full scale when the binary input code is incremented one binary bit (1 LSB). Resolution is a design parameter rather than a performance specification; it says nothing about accuracy or linearity.

**Accuracy** is sometimes considered to be a non-specific term when applied to D/A or A/D converters. A linearity spec is generally considered as more descriptive. An accuracy specification describes the worst case deviation of the DAC output voltage from a straight line drawn between zero and full scale; it includes all errors. A 12-bit DAC could not have a conversion accuracy better than  $\pm \frac{1}{2}$  LSB or  $\pm 1$  part in  $2^{12+1}$  ( $\pm 0.0122\%$  of full scale due to finite resolution). This would be the case in figure 1 if there were no errors. Actually,  $\pm 0.0122\%$  FS represents a deviation from 100% accuracy; therefore accuracy should be specified as 99.9878%. However, convention would dictate 0.0122% as being an accuracy spec rather than an inaccuracy (tolerance or error) spec.

Accuracy as applied to an ADC would describe the difference between the actual input voltage and the full-scale weighted equivalent of the binary output code; included are quantizing and all other errors. If a 12-bit ADC is stated to be  $\pm 1$  LSB accurate, this is equivalent to  $\pm 0.0245\%$  or twice the minimum possible quantizing error of 0.0122%. An accuracy spec describes the maximum sum of all errors including quantizing error, but is rarely provided on data sheets as the several errors are listed separately.

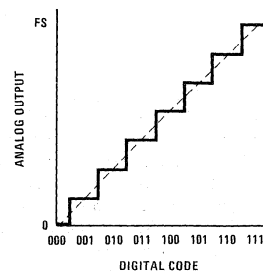


FIGURE 1. Linear DAC Transfer Curve Showing Minimum Resolution Error and Best Possible Accuracy

**Quantizing Error** is the maximum deviation from a straight line transfer function of a perfect ADC. As, by its very nature, an ADC quantizes the analog input into a finite number of output codes, only an infinite resolution ADC would exhibit zero quantizing error. A perfect ADC, suitably offset  $\frac{1}{2}$  LSB at zero scale as shown in figure 2, exhibits only  $\pm\frac{1}{2}$  LSB maximum output error. If not offset, the error will be  $\pm 1$  LSB as shown in figure 3. For example, a perfect 12-bit ADC will show a  $\pm\frac{1}{2}$  LSB error of  $\pm 0.0122\%$  while the quantizing error of an 8-bit ADC is  $\pm\frac{1}{2}$  part in  $2^8$  or  $\pm 0.195\%$  of full scale. Quantizing error is not strictly applicable to a DAC; the equivalent effect is more properly a resolution error.

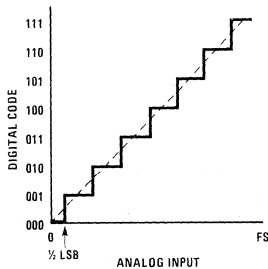


FIGURE 3. ADC Transfer Curve, No Offset

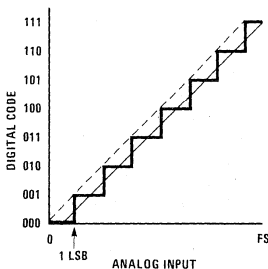


FIGURE 4. Linear, 1 LSB Scale Error

**Gain Error** is essentially the same as scale error for an ADC. In the case of a DAC with current and voltage mode outputs, the current output could be to scale while the voltage output could exhibit a gain error. The amplifier feedback resistors would be trimmed to correct the gain error.

**Offset Error** (zero error) is the output voltage of a DAC with zero code input, or it is the required mean value of input voltage of an ADC to set zero code out. (See figure 5.) Offset error is usually caused by amplifier or comparator input offset voltage or current; it can usually be trimmed to zero with an offset zero adjust potentiometer external to the DAC or ADC. Offset error may be expressed in % FS or in fractional LSB.

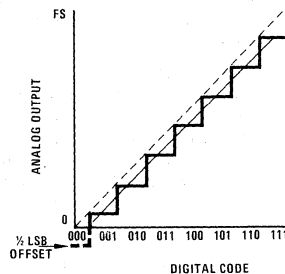


FIGURE 2. ADC Transfer Curve,  $\frac{1}{2}$  LSB Offset at Zero

**Scale Error** (full scale error) is the departure from design output voltage of a DAC for a given input code, usually full-scale code. (See figure 4.) In an ADC it is the departure of actual input voltage from design input voltage for a full-scale output code. Scale errors can be caused by errors in reference voltage, ladder resistor values, or amplifier gain, *et. al.* (See **Temperature Coefficient.**) Scale errors may be corrected by adjusting output amplifier gain or reference voltage. If the transfer curve resembles that of figure 7, a scale adjustment at  $\frac{1}{4}$  scale could improve the overall  $\pm$  accuracy compared to an adjustment at full scale.

**Hysteresis Error** in an ADC causes the voltage at which a code transition occurs to be dependent upon the direction from which the transition is approached. This is usually caused by hysteresis in the comparator inside an ADC. Excessive hysteresis may be reduced by design; however, some slight hysteresis is inevitable and may be objectionable in converters if hysteresis approaches  $\frac{1}{2}$  LSB.

**Linearity**, or, more accurately, non-linearity specifications describe the departure from a linear transfer curve for either an ADC or a DAC. Linearity error does not include quantizing, zero, or scale errors. Thus, a speci-

cation of  $\pm\frac{1}{2}$  LSB linearity implies error in addition to the inherent  $\pm\frac{1}{2}$  LSB quantizing or resolution error. In reference to figure 2, showing no errors other than quantizing error, a linearity error allows for one or more of the steps being greater or less than the ideal shown.

Figure 6 shows a 3-bit DAC transfer curve with no more than  $\pm\frac{1}{2}$  LSB non-linearity, yet one step shown is of zero amplitude. This is within the specification, as the maximum deviation from the ideal straight line is  $\pm 1$  LSB ( $\frac{1}{2}$  LSB resolution error plus  $\frac{1}{2}$  LSB non-linearity). With any linearity error, there is a differential non-linearity (see below). A  $\pm\frac{1}{2}$  LSB linearity spec guarantees monotonicity (see below) and  $\leq \pm 1$  LSB differential non-linearity (see below). In the example of figure 6, the code transition from 100 to 101 is the worst possible non-linearity, being the transition from 1 LSB high at code 100 to 1 LSB low at 110. Any fractional non-linearity beyond  $\pm\frac{1}{2}$  LSB will allow for a non-monotonic transfer curve. Figure 7 shows a typical non-linear curve; non-linearity is  $\frac{1}{4}$  LSB yet the curve is smooth and monotonic.

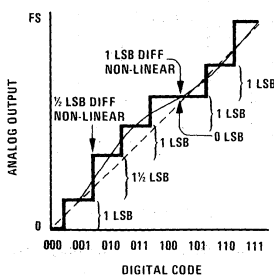


FIGURE 6.  $\pm\frac{1}{2}$  LSB Non-Linearity (Implies 1 LSB Possible Error), 1 LSB Differential Non-Linearity (Implies Monotonicity)

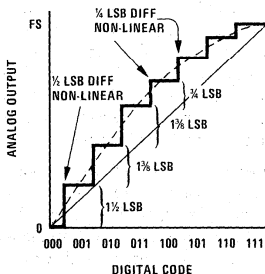


FIGURE 7.  $\frac{1}{4}$  LSB Non-Linear,  $\frac{1}{2}$  LSB Differential Non-Linearity

Linearity specs refer to either ADCs or to DACs, and do not include quantizing, gain, offset, or scale errors. Linearity errors are of prime importance along with differential linearity in either ADC or DAC specs, as all other errors (except quantizing, and temperature and long-term drifts) may be adjusted to zero. Linearity errors may be expressed in % FS or fractional LSB.

**Differential Non-Linearity** indicates the difference between actual analog voltage change and the ideal (1 LSB) voltage change at any code change of a DAC. For example, a DAC with a 1.5 LSB step at a code change would be said to exhibit  $\frac{1}{2}$  LSB differential non-linearity (see figures 6 and 7). Differential non-linearity may be expressed in fractional bits or in % FS.

Differential linearity specs are just as important as linearity specs because the apparent quality of a converter curve can be significantly affected by differential non-linearity even though the linearity spec is good. Figure 6 shows a curve with a  $\pm\frac{1}{2}$  LSB linearity and  $\pm 1$  LSB differential non-linearity while figure 7 shows a curve with  $\pm\frac{1}{4}$  LSB linearity and  $\pm\frac{1}{2}$  LSB differential non-linearity. In many user applications, the curve of figure 7 would be preferred over that of figure 6 because the curve is smoother. The differential non-linearity spec describes the smoothness of a curve; therefore it is of great importance to the user. A gross example of differential non-linearity is shown in figure 8 where the linearity spec is  $\pm 1$  LSB and the differential linearity spec is  $\pm 2$  LSB. The effect is to allow a transfer curve with grossly degraded resolution; the normal 8-step curve is reduced to 3 steps in figure 8. Similarly, a 16-step curve (4-bit converter) with only 2 LSB differential non-linearity could be reduced to 6 steps (a 2.6-bit converter?). The real message is, "Beware of the specs." Do not ignore or omit differential linearity characteristics on a converter unless the linearity spec is tight enough to guarantee the desired differential linearity. As this characteristic is impractical to measure on a production basis, it is rarely, if ever, specified, and linearity is the primary specified parameter. Differential non-linearity can always be as much as twice the non-linearity, but no more.

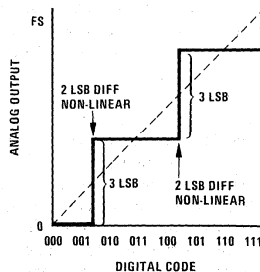


FIGURE 8.  $\pm 1$  LSB Linear,  $\pm 2$  LSB Differential Non-Linear

**Monotonicity.** A monotonic curve has no change in sign of the slope; thus all incremental elements of a monotonically increasing curve will have positive or zero, but never negative slope. The converse is true for decreasing curves. The transfer curve of a monotonic DAC will contain steps of only positive or zero height, and no negative steps. Thus a smooth line connecting all output voltage points will contain no peaks or dips. The transfer function of a monotonic ADC will provide no decreasing output code for increasing input voltage.

Figure 9 shows a non-monotonic DAC transfer curve. For the curve to be non-monotonic, the linearity error must exceed  $\pm\frac{1}{2}$  LSB no matter by how little. The greater the linearity error, the more significant the negative step might be. A non-monotonic curve may not be a special disadvantage in some systems; however, it is a disaster in closed-loop servo systems of any type (including a DAC-controlled ADC). A  $\pm\frac{1}{2}$  LSB maximum linearity spec on an n-bit converter guarantees monotonicity to n bits. A converter exhibiting more than  $\pm\frac{1}{2}$  LSB non-linearity may be monotonic, but is not necessarily monotonic. For example, a 12-bit DAC with  $\pm\frac{1}{2}$  bit linearity to 10 bits (not  $\pm\frac{1}{2}$  LSB) will be monotonic at 10 bits but may or may not be monotonic at 12 bits unless tested and guaranteed to be 12-bit monotonic.


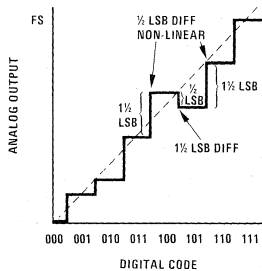


FIGURE 9. Non-Monotonic (Must be  $> \pm\frac{1}{2}$  LSB Non-Linear)


**Settling Time** is the elapsed time after a code transition for DAC output to reach final value within specified limits, usually  $\pm\frac{1}{2}$  LSB. (See also **Conversion Rate** below.) Settling time is often listed along with a slew rate specification; if so, it may not include slew time. If no slew rate spec is included, the settling time spec must be expected to include slew time. Settling time is usually summed with slew time to obtain total elapsed time for the output to settle to final value. Figure 10 delineates that part of the total elapsed time which is considered to be slew and that part which is settling time. It is apparent from this figure that the total time is greater for a major than for a minor code change due to amplifier slew limitations, but settling time may also be different depending upon amplifier overload recovery characteristics.

**Slew Rate** is an inherent limitation of the output amplifier in a DAC which limits the rate of change of output voltage after code transitions. Slew rate is usually anywhere from 0.2 to several hundred volts/ $\mu$ s. Delay in reaching final value of DAC output voltage is the sum of slew time and settling time as shown in figure 10.

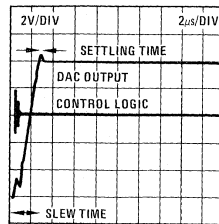**Overshoot and Glitches** occur whenever a code transition occurs in a DAC. There are two causes. The current output of a DAC contains switching glitches due to possible asynchronous switching of the bit currents (expected to be worst at half-scale transition when all



(a) Full-Scale Step

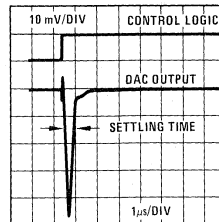

(b) 1 LSB Step

FIGURE 10. DAC Slew and Settling Time

bits are switched). These glitches are normally of extremely short duration but could be of  $\frac{1}{2}$  scale amplitude. The current switching glitches are generally somewhat attenuated at the voltage output of the DAC because the output amplifier is unable to slew at a very high rate; they are, however, partially coupled around the amplifier via the amplifier feedback network and seen at the output. The output amplifier introduces overshoot and some non-critically damped ringing which may be minimized but not entirely eliminated except at the expense of slew rate and settling time.

**Temperature Coefficient** of the various components of a DAC or ADC can produce or increase any of the several errors as the operating temperature varies. Zero scale offset error can change due to the TC of the amplifier and comparator input offset voltages and currents. Scale error can occur due to shifts in the reference, changes in ladder resistance or non-compensating RC product shifts in dual-slope ADCs, changes in beta or reference current in current switches, changes in amplifier bias current, or drift in amplifier gain-set resistors. Linearity and monotonicity of the DAC can be affected by differential temperature drifts of the ladder resistors and switches. Overshoot, settling time, and slew rate can be affected by temperature due to internal change in amplifier gain and bandwidth. In short, every specification except resolution and quantizing error can be affected by temperature changes.

**Long-Term Drift**, due mainly to resistor and semiconductor aging can affect all those characteristics which temperature change can affect. Characteristics most commonly affected are linearity, monotonicity, scale, and offset. Scale change due to reference aging is usually the most important change.

**Supply Rejection** relates to the ability of a DAC or ADC to maintain scale, offset, TC, slew rate, and linearity when the supply voltage is varied. The reference must, of course, remain constant unless considering a multiplying DAC. Most affected are current sources (affecting linearity and scale) and amplifiers or comparators (affecting offset and slew rate). Supply rejection is usually specified only as a % FS change at or near full scale at 25°C.

**Conversion Rate** is the speed at which an ADC or DAC can make repetitive data conversions. It is affected by propagation delay in counting circuits, ladder switches and comparators; ladder RC and amplifier settling times; amplifier and comparator slew rates; and integrating time of dual-slope converters. Conversion rate is specified as a number of conversions per second, or conversion time is specified as a number of microseconds to complete one conversion (including the effects of settling time). Sometimes, conversion rate is specified for less than full resolution, thus showing a misleading (high) rate.

**Clock Rate** is the minimum or maximum pulse rate at which ADC counters may be driven. There is a fixed relationship between the minimum conversion rate and the clock rate depending upon the converter accuracy and type. All factors which affect conversion rate of an ADC limit the clock rate.

**Input Impedance** of an ADC describes the load placed on the analog source.

**Output Drive Capability** describes the digital load driving capability of an ADC or the analog load driving capacity of a DAC; it is usually given as a current level or a voltage output into a given load.

## CODES

Several types of DAC input or ADC output codes are in common use. Each has its advantages depending upon the system interfacing the converter. Most codes are binary in form; each is described and compared below.

**Natural Binary** (or simply Binary) is the usual  $2^n$  code with 2, 4, 8, 16, . . . ,  $2^n$  progression. An input or output high or "1" is considered a signal, whereas a "0" is considered an absence of signal. This is a positive true binary signal. Zero scale is then all "zeros" while full scale is all "ones."

**Complementary Binary** (or Inverted Binary) is the negative true binary system. It is identical to the binary code except that all binary bits are inverted. Thus, zero scale is all "ones" while full scale is all "zeros."

**Binary Coded Decimal (BCD)** is the representation of decimal numbers in binary form. It is useful in ADC systems intended to drive decimal displays. Its advantage over decimal is that only 4 lines are needed to represent 10 digits. The disadvantage of coding DACs or ADCs in BCD is that a full 4 bits could represent 16 digits while only 10 are represented in BCD. The full-scale resolution of a BCD coded system is less than that of a binary

coded system. For example, a 12-bit BCD system has a resolution of only 1 part in 1000 compared to 1 part in 4096 for a binary system. This represents a loss in resolution of over 4:1.

**Offset Binary** is a natural binary code except that it is offset (usually  $\frac{1}{2}$  scale) in order to represent negative and positive values. Maximum negative scale is represented to be all "zeros" while maximum positive scale is represented as all "ones." Zero scale (actually center scale) is then represented as a leading "one" and all remaining "zeros." The comparison with binary is shown in figure 11.

**Twos Complement Binary** is an alternate and more widely used code to represent negative values. With this code, zero and positive values are represented as in natural binary while all negative values are represented in a twos complement form. That is, the twos complement of a number represents a negative value so that interface to a computer or microprocessor is simplified. The twos complement is formed by complementing each bit and then adding a 1; any overflow is neglected. The decimal number -8 is represented in twos complement as follows: start with binary code of decimal 8 (off scale for  $\pm$  representation in 4 bits so not a valid code in the  $\pm$  scale of 4 bits) which is 1000; complement it to 0111; add 0001 to get 1000. The comparison with offset binary is shown in figure 11. Note that the offset binary representation of the  $\pm$  scale differs from the twos complement representation only in that the MSB is complemented. The conversion from offset binary to twos complement only requires that the MSB be inverted.

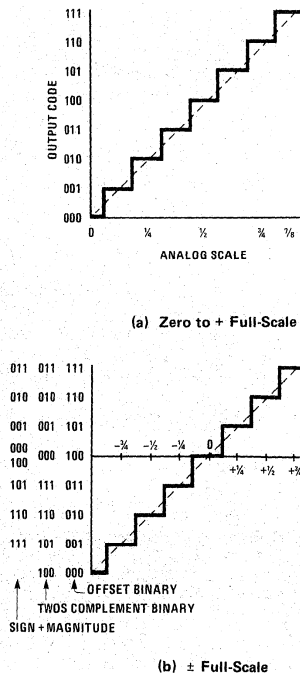


FIGURE 11. ADC Codes

**Sign Plus Magnitude** coding contains polarity information in the MSB (MSB = 1 indicates a negative sign); all other bits represent magnitude only. This code is compared to offset binary and twos complement in figure 11. Note that one code is used up in providing a double code for zero. Sign plus magnitude code is used in certain instrument and audio systems; its advantage is that only one bit need be changed for small scale changes in the vicinity of zero, and plus and minus scales are symmetrical. A DVM might be an example of its use.

#### **CONTROL**

Each ADC must accept and/or provide digital control signals telling it and/or the external system what to do and when to do it. Control signals should be compatible with one or more types of logic in common use. Control signal timing must be such that the converter or connected system will accept the signals. Common control signals are listed below.

**Start Conversion (SC)** is a digital signal to an ADC which initiates a single conversion cycle. Typically, an SC signal must be present at the fall (or rise) of the clock waveform to initiate the cycle. A DAC needs no SC signal; however, such could be provided to gate digital inputs to a DAC.

**End of Conversion (EOC)** is a digital signal from an ADC which informs the external system that the digital output

data is valid. Typically, an EOC output can be connected to an SC input to cause the ADC to operate in continuous conversion mode. In non-continuous conversion systems, the SC signal is a command from the system to the ADC. A DAC does not supply an EOC signal.

**Clock** signals are required or must be generated within an ADC to control counting or successive approximation registers. The clock controls the conversion speed within the limitations of the ADC. DACs do not require clock signals.

#### **CONCLUSION**

Once the user has a working knowledge of DAC or ADC characteristics and specifications, he should be able to select a converter to suit a specific system need. The likelihood of overspecification, and therefore an unnecessarily high cost, is likewise reduced. The user will also be aware that specific parameters, test conditions, test circuits, and even definitions may vary from manufacturer to manufacturer. For practical production reasons, parameters may not be tested in the same manner for all converter types, even those supplied by the same manufacturer. Using information in this note, the user should, however, be able to sort out and understand those specifications (from any manufacturer) pertinent to his needs.

## IC Voltage Reference has 1 ppm per Degree Drift

National Semiconductor  
Application Note 161  
Robert C. Dobkin  
June 1976



A new linear IC now provides the ultimate in highly stable voltage references. Now, a new monolithic IC the LM199, out-performs zeners and can provide a 6.9V reference with a temperature drift of less than 1 ppm/<sup>o</sup> and excellent long term stability. This new IC, uses a unique subsurface zener to achieve low noise and a highly stable breakdown. Included is an on-chip temperature stabilizer which holds the chip temperature at 90<sup>o</sup>C, eliminating the effects of ambient temperature changes on reference voltage.

The planar monolithic IC offers superior performance compared to conventional reference diodes. For example, active circuitry buffers the reverse current to the zener giving a dynamic impedance of 0.5Ω and allows the LM199 to operate over a 0.5 mA to 10 mA current range with no change in performance. The low dynamic impedance, coupled with low operating current significantly simplifies the current drive circuitry needed for operation. Since the temperature coefficient is independent of operating current, usually a resistor is all that is needed.

Previously, the task of providing a stable, low temperature coefficient reference voltage was left to a discrete zener diode. However, these diodes often presented significant problems. For example, ordinary zeners can show many millivolts change if there is a temperature gradient across the package due to the zener and temperature compensation diode not being at the same temperature. A 1<sup>o</sup>C difference may cause a 2 mV shift in reference voltage. Because the on-chip temperature stabilizer maintains constant die temperature, the IC reference is free of voltage shifts due to temperature gradients. Further, the temperature stabilizer, as well as eliminating drift, allows exceptionally fast warm-up over conventional diodes. Also, the LM199 is insensitive to stress on the leads—another source of error with ordinary glass diodes. Finally, the LM199 shows virtually no hysteresis in reference voltage when subject to temperature cycling over a wide temperature range. Temperature cycling the LM199 between 25<sup>o</sup>C, 150<sup>o</sup>C and back to 25<sup>o</sup>C causes less than 50μV change in reference voltage. Standard reference diodes exhibit shifts of 1 mV to 5 mV under the same conditions.

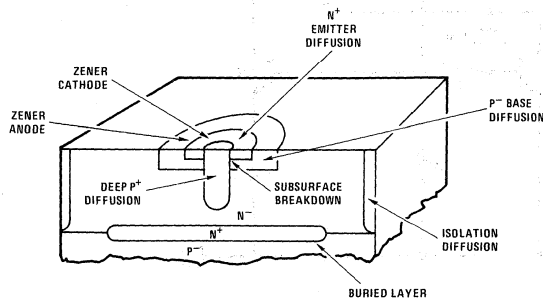


FIGURE 1. Subsurface Zener Construction

### SUB SURFACE ZENER IMPROVES STABILITY

Previously, breakdown references made in monolithic IC's usually used the emitter-base junction of an NPN transistor as a zener diode. Unfortunately, this junction breaks down at the surface of the silicon and is therefore susceptible to surface effects. The breakdown is noisy, and cannot give long-term stabilities much better than about 0.3%. Further, a surface zener is especially sensitive to contamination in the oxide or charge on the surface of the oxide which can cause short-term instability or turn-on drift.

The new zener moves the breakdown below the surface of the silicon into the bulk yielding a zener that is stable with time and exhibits very low noise. Because the new zener is made with well-controlled diffusions in a planar structure, it is extremely reproducible with an initial 2% tolerance on breakdown voltage.

A cut-away view of the new zener is shown in *Figure 1*. First a small deep P+ diffusion is made into the surface of the silicon. This is then covered by the standard base diffusion. The N+ emitter diffusion is then made completely covering the P+ diffusion. The diode then breaks down where the dopant concentration is greatest, that is, between the P+ and N+. Since the P+ is completely covered by N+ the breakdown is below the surface and at about 6.3V. One connection to the diode is to the N+ and the other is to the P base diffusion. The current flows laterally through the base to the P+ or cathode of the zener. Surface breakdown does not occur since the base P to N+ breakdown voltage is greater than the breakdown of the buried device. The buried zener has been in volume production since 1973 as the reference in the LX5600 temperature transducer.

### CIRCUIT DESCRIPTION

The block diagram of the LM199 is shown in *Figure 2*. Two electrically independent circuits are included on the same chip—a temperature stabilizer and a floating active zener. The only electrical connection between the two

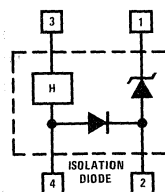


FIGURE 2. Functional Block Diagram

circuits is the isolation diode inherent in any junction-isolated integrated circuit. The zener may be used with or without the temperature stabilizer powered. The only operating restriction is that the isolation diode must never become forward biased and the zener must not be biased above the 40V breakdown of the isolation diode.

The actual circuit is shown in *Figure 3*. The temperature stabilizer is composed of Q1 through Q9. FET Q9 provides current to zener D2 and Q8. Current through Q8 turns a loop consisting of D1, Q5, Q6, Q7, R1 and R2. About 5V is applied to the top of R1 from the base of Q7. This causes  $400\mu\text{A}$  to flow through the divider R1, R2. Transistor Q7 has a controlled gain of 0.3 giving Q7 a total emitter current of about  $500\mu\text{A}$ . This flows through the emitter of Q6 and drives another controlled gain PNP transistor Q5. The gain of Q5 is about 0.4 so D1 is driven with about  $200\mu\text{A}$ . Once current flows through Q5, Q8 is reverse biased and the loop is self-sustaining. This circuitry ensures start-up.

The resistor divider applies 400 mV to the base of Q4 while Q7 supplies  $120\mu\text{A}$  to its collector. At temperatures below the stabilization point, 400 mV is insufficient to cause Q4 to conduct. Thus, all the collector current from

Q7 is provided as base drive to a Darlington composed of Q1 and Q2. The Darlington is connected across the supply and initially draws 140 mA (set by current limit transistor Q3). As the chip heats, the turn on voltage for Q4 decreases and Q4 starts to conduct. At about  $90^\circ\text{C}$  the current through Q4 appreciably increases and less drive is applied to Q1 and Q2. Power dissipation decreases to whatever is necessary to hold the chip at the stabilization temperature. In this manner, the chip temperature is regulated to better than  $2^\circ\text{C}$  for a  $100^\circ\text{C}$  temperature range.

The zener section is relatively straight-forward. A buried zener D3 breaks down biasing the base of transistor Q13. Transistor Q13 drives two buffers Q12 and Q11. External current changes through the circuit are fully absorbed by the buffer transistors rather than D3. Current through D3 is held constant at  $250\mu\text{A}$  by a 2k resistor across the emitter base of Q13 while the emitter-base voltage of Q13 nominally temperature compensates the reference voltage.

The other components, Q14, Q15 and Q16 set the operating current of Q13. Frequency compensation is accomplished with two junction capacitors.

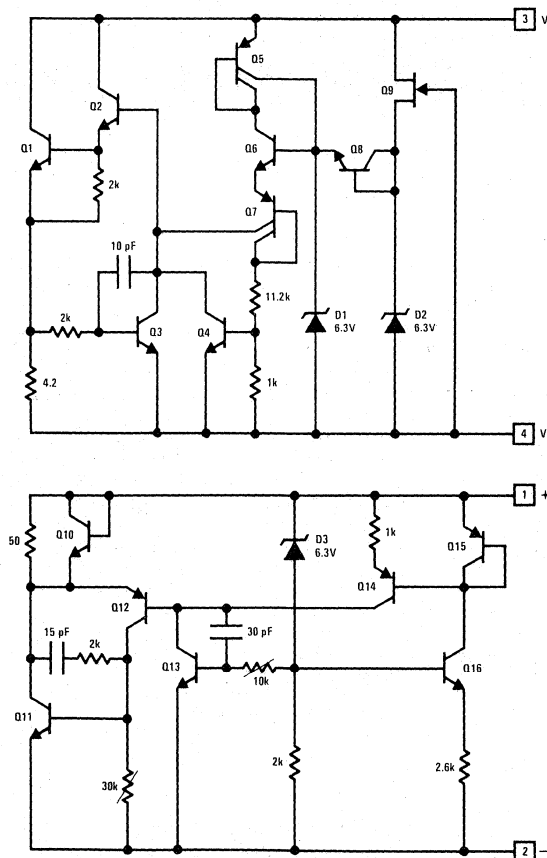


FIGURE 3. Schematic Diagram of LM199 Precision Reference



## PERFORMANCE

A polysulfone thermal shield, shown in *Figure 4*, is supplied with the LM199 to minimize power dissipation and improve temperature regulation. Using a thermal shield as well as the small, high thermal resistance TO-46 package allows operation at low power levels without the problems of special IC packages with built-in thermal isolation. Since the LM199 is made on a standard IC assembly line with standard assembly techniques, cost is significantly lower than if special techniques were used. For temperature stabilization only 300 mW are required at 25°C and 660 mW at -55°C.

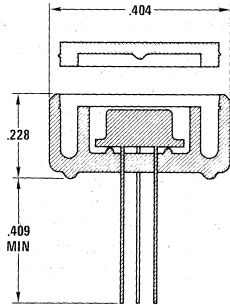


FIGURE 4. Polysulfone Thermal Shield

Temperature stabilizing the device at 90°C virtually eliminates temperature drift at ambient temperatures less than 90°C. The reference is nominally temperature compensated and the thermal regulator further decreases the temperature drift. Drift is typically only 0.3 ppm/°C. Stabilizing the temperature at 90°C rather than 125°C significantly reduces power dissipation but still provides very low drift over a major portion of the operating temperature range. Above 90°C ambient, the temperature coefficient is only 15 ppm/°C.

A low drift reference would be virtually useless without equivalent performance in long term stability and low noise. The subsurface breakdown technology yields both of these. Wideband and low frequency noise are both exceptionally low. Wideband noise is shown in *Figure 5* and low frequency noise is shown over a 10 minute period in the photograph of *Figure 6*. Peak to peak noise over a 0.01 Hz to 1 Hz bandwidth is only about 0.7µV.

Long term stability is perhaps one of the most difficult measurements to make. However, conditions for long-term stability measurements on the LM199 are considerably more realistic than for commercially available certified zeners. Standard zeners are measured in ±0.05°C temperature controlled both at an operating current of 7.5 mA ±0.05µA. Further, the standard devices must have stress-free contacts on the leads and the test must not be interrupted during the measurement interval. In contrast, the LM199 is measured in still air of 25°C to 28°C at a reverse current of 1 mA ±0.5%. This is more typical of actual operating conditions in instruments.

When a group of 10 devices were monitored for long-term stability, the variations all correlated, which indicates changes in the measurement system (limitation of 20 ppm) rather than the LM199.

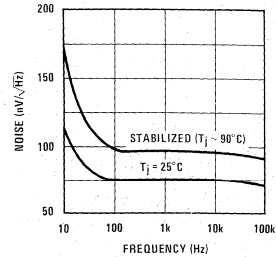


FIGURE 5. Wideband Noise of the LM199 Reference

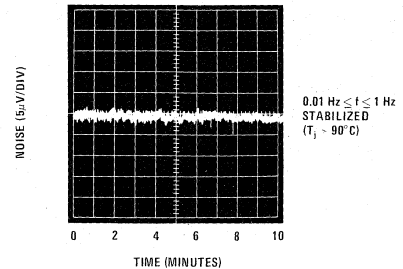


FIGURE 6. Low Frequency Noise Voltage

Because the planar structure does not exhibit hysteresis with temperature cycling, long-term stability is not impaired if the device is switched on and off.

The temperature stabilizer heats the small thermal mass of the LM199 to 90°C very quickly. Warm-up time at 25°C and -55°C is shown in *Figure 7*. This fast warm-up is significantly less than the several minutes needed by ordinary diodes to reach equilibrium. Typical specifications are shown in Table I.

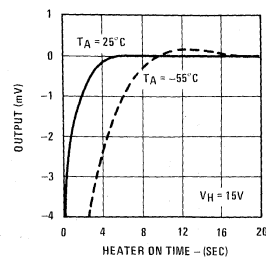


FIGURE 7. Fast Warmup Time of the LM199

Table I. Typical Specifications for the LM199

Reverse Breakdown Voltage	6.95V
Operating Current	0.5 mA to 10 mA
Temperature Coefficient	0.3 ppm/°C
Dynamic Impedance	0.5Ω
RMS Noise (10 Hz to 10 kHz)	7µV
Long-Term Stability	≤ 20 ppm
Temperature Stabilizer Operating Voltage	9V to 40V
Temperature Stabilizer Power Dissipation (25°C)	300 mW
Warm-up Time	3 Seconds

## APPLICATIONS

The LM199 is easier to use than standard zeners, but the temperature stability is so good—even better than precision resistors—that care must be taken to prevent external circuitry from limiting performance. Basic operation only requires energizing the temperature stabilizer from a 9V to 40V power source and biasing the reference with between 0.5 mA to 10 mA of current. The low dynamic impedance minimizes the current regulation required compared to ordinary zeners.

The only restriction on biasing the zener is the bias applied to the isolation diode. Firstly, the isolation diode must not be forward biased. This restricts the voltage at either terminal of the zener to a voltage equal to or greater than the  $V^-$ .

A dc return is needed between the zener and heater to insure the voltage limitation on the isolation diodes are not exceeded. Figure 8 shows the basic biasing of the LM199.

The active circuitry in the reference section of the LM199 reduces the dynamic impedance of the zener to about  $0.5\Omega$ . This is especially useful in biasing the reference. For example, a standard reference diode such as a 1N829 operates at 7.5 mA and has a dynamic impedance of  $15\Omega$ . A 1% change in current ( $75\mu\text{A}$ ) changes the reference voltage by 1.1 mV. Operating the LM199 at 1 mA with the same 1% change in operating current ( $10\mu\text{A}$ ) results in a reference change of only  $5\mu\text{V}$ . Figure 9 shows reverse voltage change with current.

Biasing current for the reference can be anywhere from 0.5 mA to 10 mA with little change in performance. This wide current range allows direct replacement of most zener types with no other circuit changes besides the temperature stabilizer connection. Since the dynamic impedance is constant with current changes regulation

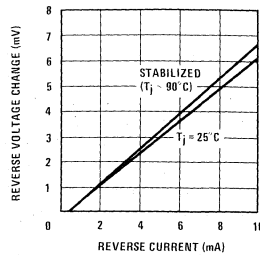


FIGURE 9. The LM199 Shows Excellent Regulation Against Current Changes

is better than discrete zeners. For optimum regulation, lower operating currents are preferred since the ratio of source resistance to zener impedance is higher, and the attenuation of input changes is greater. Further, at low currents, the voltage drop in the wiring is minimized.

Mounting is an important consideration for optimum performance. Although the thermal shield minimizes the heat loss, the LM199 should not be exposed to a direct air flow such as from a cooling fan. This can cause as much as a 100% increase in power dissipation degrading the thermal regulation and increasing the drift. Normal convection currents do not degrade performance.

Printed circuit board layout is also important. Firstly, four wire sensing should be used to eliminate ohmic drops in pc traces. Although the voltage drops are small the temperature coefficient of the voltage developed along a copper trace can add significantly to the drift. For example, a trace with  $1\Omega$  resistance and 2 mA current flow will develop 2 mV drop. The TC of copper is  $0.004\%/^{\circ}\text{C}$  so the 2 mV drop will change at  $8\mu\text{V}/^{\circ}\text{C}$ , this is an additional 1 ppm drift error. Of course, the effects of voltage drops in the printed circuit traces are eliminated with 4-wire operation. The heater current also should not be allowed to flow through the voltage reference traces. Over a  $-55^{\circ}\text{C}$  to  $+125^{\circ}\text{C}$  temperature

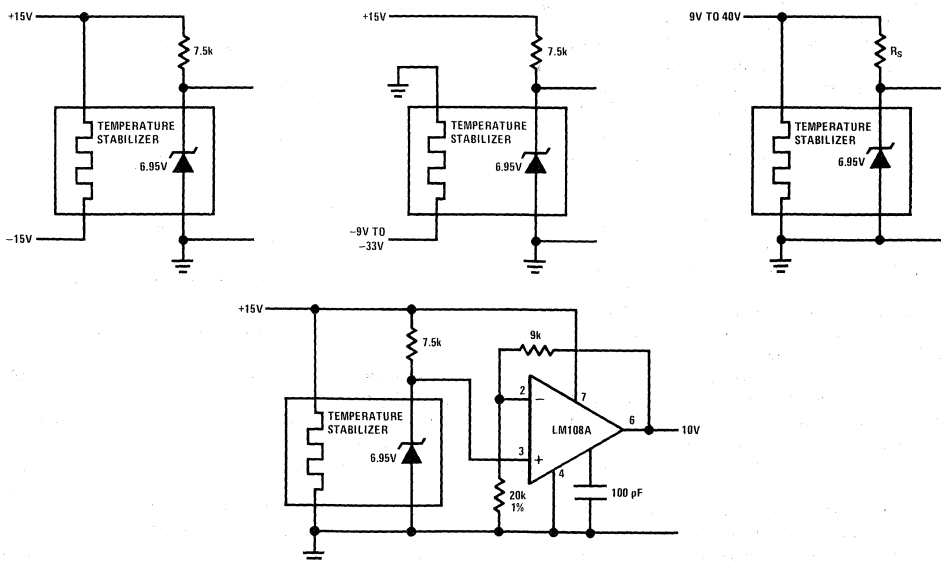


FIGURE 8. Basic Biasing of the LM199

range the heater current will change from about 1 mA to over 40 mA. These magnitudes of current flowing reference leads or reference ground can cause huge errors compared to the drift of the LM199.

Thermocouple effects can also cause errors. The kovar leads from the LM199 package form a thermocouple with copper printed circuit board traces. Since the package of the 199 is heated, there is a heat flow along the leads of the LM199 package. If the leads terminate into unequal sizes of copper on the p.c. board greater heat will be absorbed by the larger copper trace and a temperature difference will develop. A temperature difference of  $1^{\circ}\text{C}$  between the two leads of the reference will generate about  $30\mu\text{V}$ . Therefore, the copper traces to the zener should be equal in size. This will generally keep the errors due to thermocouple effects under about  $15\mu\text{V}$ .

The LM199 should be mounted flush on the p.c. board with a minimum of space between the thermal shield and the boards. This minimizes air flow across the kovar leads on the board surface which also can cause thermocouple voltages. Air currents across the leads usually appear as ultra-low frequency noise of about  $10\mu\text{V}$  to  $20\mu\text{V}$  amplitude.

It is usually necessary to scale and buffer the output of any reference to some calibrated voltage. *Figure 10* shows a simple buffered reference with a 10V output. The reference is applied to the non-inverting input of the LM108A. An RC rolloff can be inserted in series with the input to the LM108A to roll-off the high frequency noise. The zener heater and op amp are all powered

from a single 15V supply. About 1% regulation on the input supply is adequate contributing less than  $10\mu\text{V}$  of error to the output. Feedback resistors around the LM308 scale the output to 10V.

Although the absolute values of the resistors are not extremely important, tracking of temperature coefficients is vital. The  $1\text{ ppm}/^{\circ}\text{C}$  drift of the LM199 is easily exceeded by the temperature coefficient of most resistors. Tracking to better than 1 ppm is also not easy to obtain. Wirewound types made of Evenohm or Mangamin are good and also have low thermoelectric effects. Film types such as Vishay resistors are also good. Most potentiometers do not track fixed resistors so it is a good idea to minimize the adjustment range and therefore minimize their effects on the output TC. Overall temperature coefficient of the circuit shown in *Figure 10* is worst case  $3\text{ ppm}/^{\circ}\text{C}$ . About 1 ppm is due to the reference, 1 ppm due to the resistors and 1 ppm due to the op amp.

*Figure 11* shows a standard cell replacement with a 1.01V output. A LM321 and LM308 are used to minimize op amp drift to less than  $1\mu\text{V}/^{\circ}\text{C}$ . Note the adjustment connection which minimizes the TC effects of the pot. Set-up for this circuit requires nulling the offset of the op amp first and then adjusting for proper output voltage.

The drift of the LM321 is very predictable and can be used to eliminate overall drift of the system. The drift changes at  $3.6\mu\text{V}/^{\circ}\text{C}$  per millivolt of offset so 1 mV to 2 mV of offset can be introduced to minimize the overall TC.

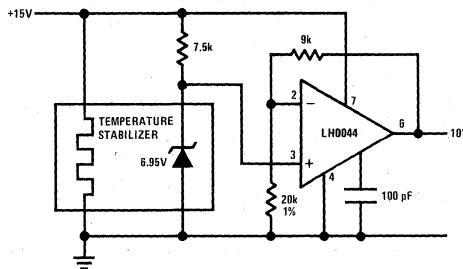


FIGURE 10. Buffered 10V Reference

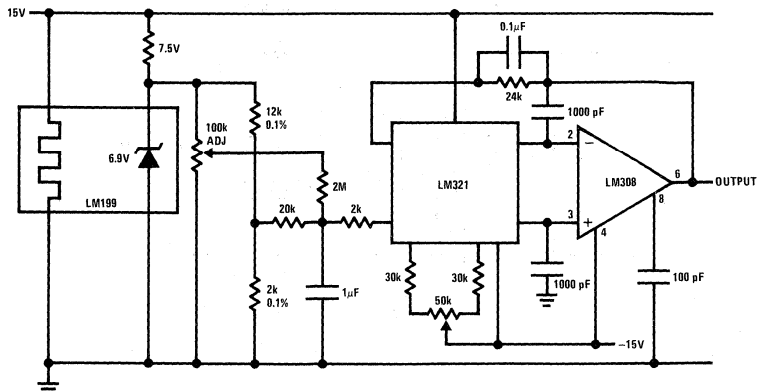


FIGURE 11. Standard Cell Replacement

For circuits with a wide input voltage range, the reference can be powered from the output of the buffer as is shown in Figure 12. The op amp supplies regulated voltage to the resistor biasing the reference minimizing changes due to input variation. There is some change due to variation of the temperature stabilizer voltage so extremely wide range operation is not recommended for highest precision. An additional resistor (shown 80 k $\Omega$ ) is added to the unregulated input to insure the circuit starts up properly at the application of power.

A precision power supply is shown in Figure 13. The output of the op amp is buffered by an IC power transistor the LM395. The LM395 operates as an NPN power device but requires only 5 $\mu$ A base current. Full overload protection inherent in the LM395 includes current limit, safe-area protection, and thermal limit.

A reference which can supply either a positive or a negative continuously variable output is shown in Figure 14. The reference is biased from the  $\pm 15$ V input supplies

as was shown earlier. A ten-turn pot will adjust the output from  $+V_Z$  to  $-V_Z$  continuously. For negative output the op amp operates as an inverter while for positive outputs it operates as a non-inverting connection.

Op amp choice is important for this circuit. A low drift device such as the LM108A or a LM108-LM121 combination will provide excellent performance. The pot should be a precision wire wound 10 turn type. It should be noted that the output of this circuit is not linear.

### CONCLUSIONS

A new monolithic reference which exceeds the performance of conventional zeners has been developed. In fact, the LM199 performance is limited more by external components than by reference drift itself. Further, many of the problems associated with conventional zeners such as hysteresis, stress sensitivity and temperature gradient sensitivity have also been eliminated. Finally, long-term stability and noise are equal of the drift performance of the new device.

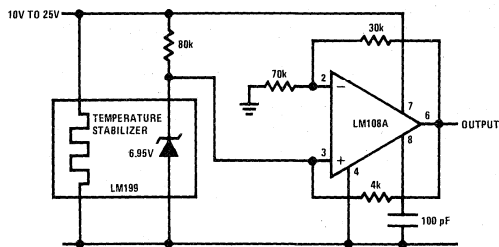


FIGURE 12. Wide Range Input Voltage Reference

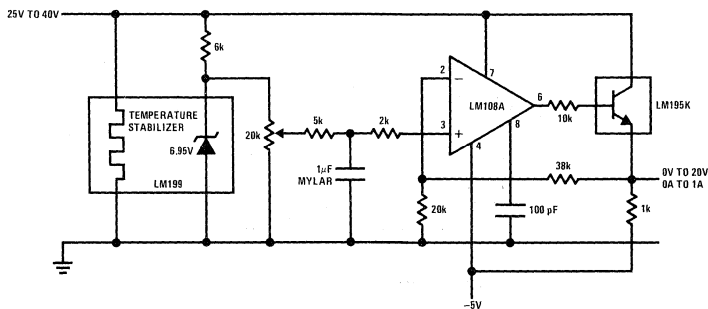


FIGURE 13. Precision Power Supply

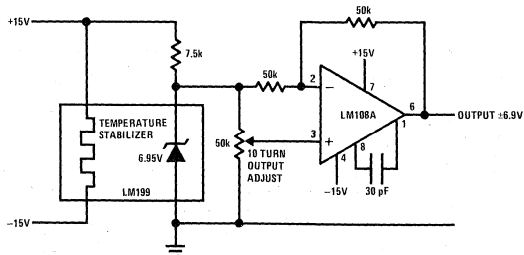


FIGURE 14. Bipolar Output Reference

# LM2907 Tachometer/ Speed Switch Building Block Applications

National Semiconductor  
Application Note 162  
Dave Long  
June 1976



## INTRODUCTION

Frequency to voltage converters are available in a number of forms from a number of sources, but invariably require significant additional components before they can be put to use in a given situation. The LM2907, LM2917 series of devices was developed to overcome these objections. Both input and output interface circuitry is included on chip so that a minimum number of additional components is required to complete the function. In keeping with the systems building block concept, these devices provide an output voltage which is proportional to input frequency and provide zero output at zero frequency. In addition, the input may be referred to ground. The devices are designed to operate

from a single supply voltage, which makes them particularly suitable for battery operation.

## PART I - GENERAL OPERATION PRINCIPLES

### Circuit Description

Referring to *Figure 1*, the family of devices all include three basic components: an input amplifier with built-in hysteresis; a charge pump frequency to voltage converter; and a versatile op amp/comparator with an uncommitted output transistor. LM2917 incorporates an active zener regulator on-chip. LM2907 deletes this option. Both versions are obtainable in 14-pin and in 8-pin dual-in-line molded packages, and to special order in other packages.

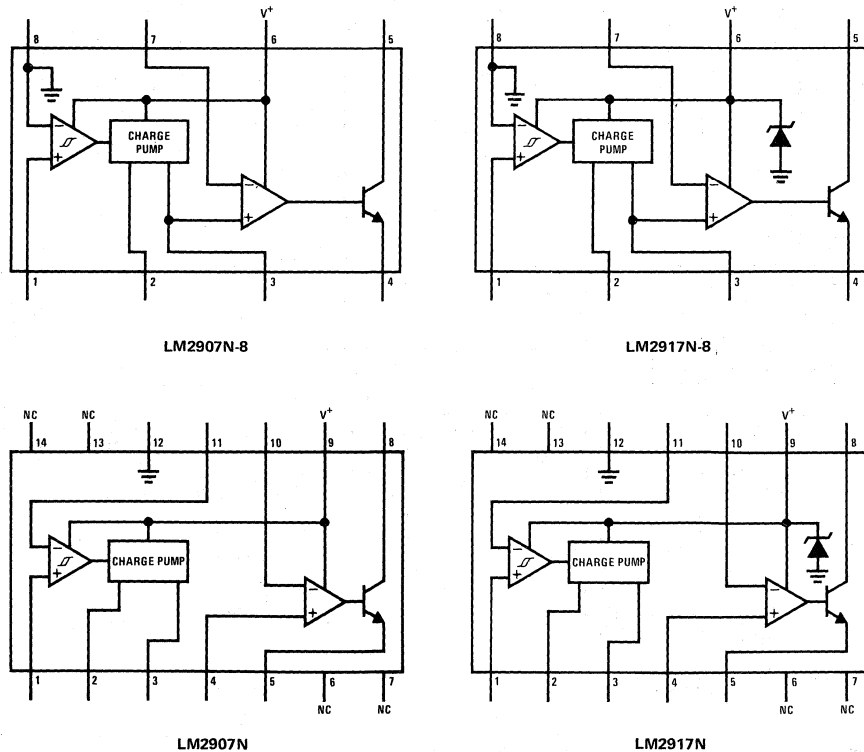


FIGURE 1. Block Diagrams


## Input Hysteresis Amplifier

The equivalent schematic diagram is shown in *Figure 2*. Q1 through Q11 comprise the input hysteresis amplifier. Q1 through Q4 comprise an input differential amplifier which, by virtue of PNP level shifting, enables the circuit to operate with signals referenced to ground. Q7, Q8, D4, and D5 comprise an active load with positive feedback. This load behaves as a bi-stable flip-flop which may be set or reset depending upon the currents supplied from Q2 and Q3. Consider the situation where Q2 and Q3 are conducting equally, i.e. the input differential voltage is zero. Assuming Q7 to be conducting, it will be noted that the current from Q3 will be drawn by Q7 and Q8 will be in the "OFF" state. This allows the current from Q2 to drive Q7 in parallel with D4 and a small resistor. D4 and Q7 are identical geometry devices, so that the resistor causes Q7 to be biased at a higher level than D4. Thus Q7 will be able to conduct more current than Q3 provides. In order to reverse the state of Q7 and Q8, it will be necessary to reduce the current from Q2 below that provided by Q3 by an amount which is established by R1. It can be shown that this requires a differential input to Q1 and Q4, of approximately 15 mV. Since the circuit is symmetrical, the threshold voltage to reverse

the state is 15 mV in the other direction. Thus the input amplifier has built-in hysteresis at  $\pm 15$  mV. This provides clean switching where noise may be present on the input signal, and allows total rejection of noise below this amplitude where there is no input signal.
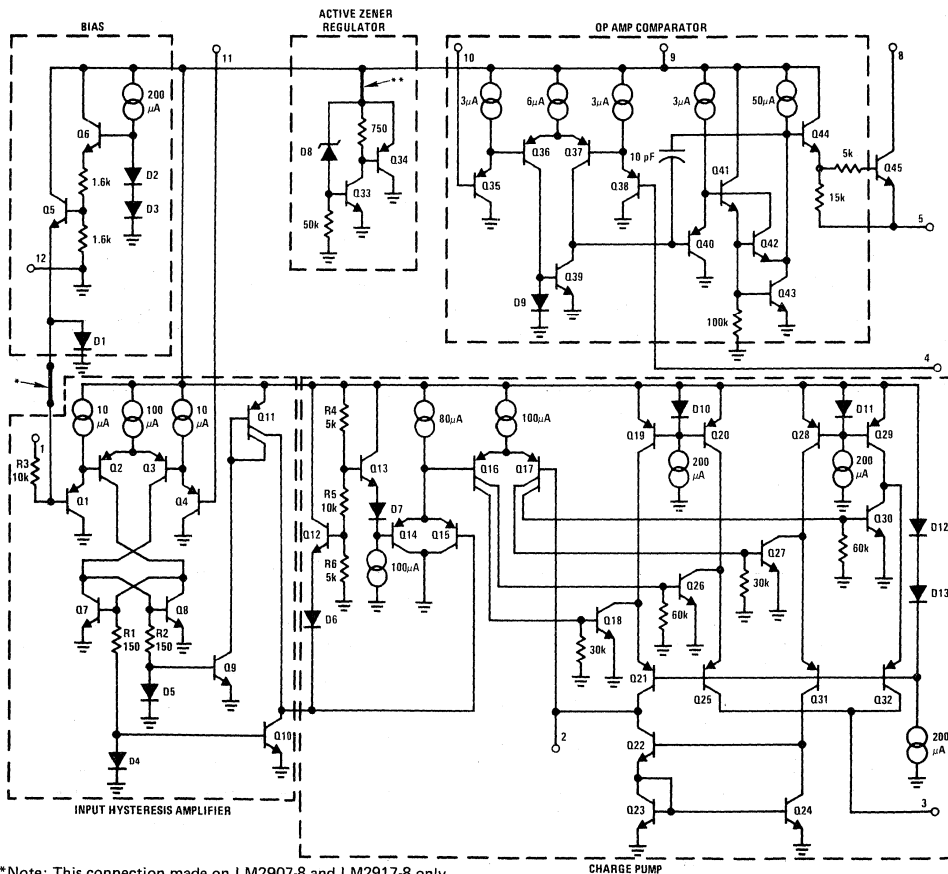
## Charge Pump

The charge pump is composed of Q12 through Q32. R4, R5, and R6 provide reference voltages equal to 1/4 and 3/4 of supply voltage to Q12 and Q13. When Q10 turns "ON" or "OFF," the base voltage at Q16 changes by an amount equal to the voltage across R5, that is  $1/2 V_{CC}$ . A capacitor connected between Pin 2 and ground is either charged by Q21 or discharged by Q22 until its voltage matches that on the base of Q16. When the voltage on Q16 base goes low, Q16 turns "ON," which results in Q18 and Q26 turning on, which causes the current, sourced by Q19 and Q20, to be shunted to ground. Thus Q21 is unable to charge pin 2. Meanwhile, Q27 and Q30 are turned off permitting the  $200\mu\text{A}$  sourced by Q28 and Q29 to enter the emitters of Q31 and Q32 respectively. The current from Q31 is mirrored by Q22 through Q24 resulting in a  $200\mu\text{A}$  discharge current through pin 2. The external capacitor on pin 2 is thus



\*Note: This connection made on LM2907-8 and LM2917-8 only.

\*\*Note: This connection made on LM2917 and LM2917-8 only.

Note: Pin numbers refer to 14-pin package.

FIGURE 2. Equivalent Schematic Diagram

discharged at a constant rate until it reaches the new base voltage on Q16. The time taken for this discharge to occur is given by:

$$t = \frac{CV}{I} \quad (1)$$

where C = capacitor on pin 2  
V = change in voltage on Q16 base  
I = current in Q22

During this time, Q32 sources an identical current into pin 3. A capacitor connected to pin 3 will thus be charged by the same current for the same amount of time as pin 2. When the base voltage on Q16 goes high, Q18 and Q26 are turned off while Q27 and Q3 are turned "ON." In these conditions, Q21 and Q25 provide the currents to charge the capacitors on pins 2 and 3 respectively. Thus the charge required to return the capacitor on pin 2 to the high level voltage is duplicated and used to charge the capacitor connected to pin 3. Thus in one cycle of input the capacitor on pin 3 gets charged twice with a charge of CV.

Thus the total charge pumped into the capacitor on pin 3 per cycle is:

$$Q = 2 CV \quad (2)$$

Now, since  $V = V_{CC}/2$

$$\text{then } Q = CV_{CC} \quad (3)$$

A resistor connected between pin 3 and ground causes a discharge of the capacitor on pin 3, where the total charge drained per cycle of input signal is equal to:

$$Q1 = \frac{V3 \cdot T}{R}$$

where V3 = the average voltage on pin 3  
T = period of input signal  
R = resistor connected to pin 3

In equilibrium  $Q = Q1$

$$\text{i.e., } CV_{CC} = \frac{V3 \cdot T}{R} \quad (4)$$

$$\text{and } V3 = V_{CC} \cdot \frac{RC}{T} \quad (5)$$

$$\text{or } V3 = V_{CC} \cdot R \cdot C \cdot f \quad (6)$$

where f = input frequency

#### Op Amp/Comparator

Again referring to *Figure 2*, the op amp/comparator includes Q35 through Q45. A PNP input stage again provides input common-mode voltages down to zero, and if pin 8 is connected to  $V_{CC}$  and the output taken from pin 5, the circuit behaves as a conventional, unity-gain-compensated operational amplifier. However, by allowing alternate connections of Q45 the circuit may be used as a comparator in which loads to either  $V_{CC}$  or ground may be switched. Q45 is capable of sinking

50 mA. Input bias current is typically 50 nA, and voltage gain is typically 200V/mV. Unity gain slew rate is 0.2V/ $\mu$ s. When operated as a comparator Q45 emitter will switch at the slow rate, or the collector of Q45 will switch at that rate multiplied by the voltage gain of Q45, which is user selectable.

#### Active Zener Regulator

The optional active zener regulator is also shown in *Figure 2*. D8 provides the voltage reference in conjunction with Q33. As the supply voltage rises, D8 conducts and the base voltage on Q33 starts to rise. When Q33 has sufficient base voltage to be turned "ON," it in turn causes Q34 to conduct current from the power source. This reduces the current available for D8 and the negative feedback loop is thereby completed. The reference voltage is therefore the zener voltage on D8 plus the emitter base voltage of Q33. This results in a low temperature coefficient reference voltage.

#### Input Levels and Protection

In 8-pin versions of the LM2907, LM2917, the non-inverting input of the op amp/comparator is connected to the output of the charge pump. Also, one input to the input hysteresis amplifier is connected to ground. The other input (pin 1) is then protected from transients by, first a 10 k $\Omega$  series resistor, R3 (*Figure 2*) which is located in a floating isolation pocket, and secondly by clamp diode D1. Since the voltage swing on the base of Q1 is thus restricted, the only restriction on the allowable voltage on pin 1 is the breakdown voltage of the 10 k $\Omega$  resistor. This allows input swings to  $\pm 28V$ . In 14-pin versions the link to D1 is opened in order to allow the base of Q1 to be biased at some higher voltage.

Q5 clamps the negative swing on the base of Q1 to about 300 mV. This prevents substrate injection in the region of Q1 which might otherwise cause false switching or erroneous discharge of one of the timing capacitors.

The differential input options (LM2907-14, LM2917-14), give the user the option of setting his own input switching level and still having the hysteresis around that level for excellent noise rejection in any application.

#### HOW TO USE IT

##### Basic f to V Converter

The operation of the LM2907, LM2917 series is best understood by observing the basic converter shown in *Figure 3*. In this configuration, a frequency signal is applied to the input of the charge pump at pin 1. The voltage appearing at pin 2 will swing between two values which are approximately  $1/4 (V_{CC}) - V_{BE}$  and  $3/4 (V_{CC}) - V_{BE}$ . The voltage at pin 3 will have a value equal to  $V_{CC} \cdot f_{IN} \cdot C1 \cdot R1 \cdot K$ , where K is the gain constant (normally 1.0).

The emitter output (pin 4) is connected to the inverting input of the op amp so that pin 4 will follow pin 3 and provide a low impedance output voltage proportional to input frequency. The linearity of this voltage is typically better than 0.3% of full scale.

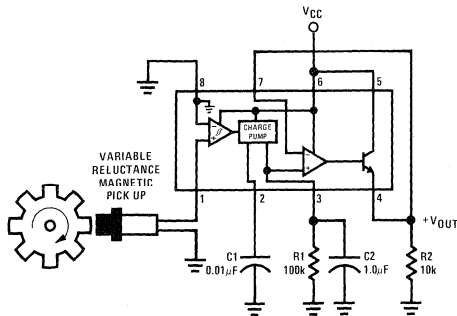


FIGURE 3. Basic f to V Converter

### Choosing R1, C1 and C2

There are some limitations on the choice of R1, C1 and C2 (Figure 3) which should be considered for optimum performance. C1 also provides internal compensation for the charge pump and should be kept larger than 100 pF. Smaller values can cause an error current on R1, especially at low temperatures. Three considerations must be met when choosing R1.

First, the output current at pin 3 is internally fixed and therefore  $V_3$  max, divided by R1, must be less than or equal to this value.

$$\therefore R1 \geq \frac{I_3 V_3 \text{ max}}{I_3 \text{ MIN}}$$

where  $V_3$  max is the full scale output voltage required  
 $I_3 \text{ MIN}$  is determined from the data sheet (150µA)

Second, if R1 is too large, it can become a significant fraction of the output impedance at pin 3 which degrades linearity. Finally, ripple voltage must be considered, and the size of C2 is affected by R1. An expression that describes the ripple content on pin 3 for a single R1, C2 combination is:

$$V_{\text{RIPPLE}} = \frac{V_{CC}}{2} \cdot \frac{C1}{C2} \left( 1 - \frac{V_{CC} \cdot f_{IN} \cdot C1}{I_2} \right) \text{ p-p}$$

It appears R1 can be chosen independent of ripple, however response time, or the time it takes  $V_{OUT}$  to stabilize at a new frequency increases as the size of C2 increases, so a compromise between ripple, response time, and linearity must be chosen carefully. R1 should be selected according to the following relationship:

C1 is selected according to:

$$C1 = \frac{V_3 \text{ Full Scale}}{R1 \cdot V_{CC} \cdot f_{\text{FULL SCALE}}}$$

Next decide on the maximum ripple which can be accepted and plug into the following equation to determine C2:

$$C2 = \frac{V_{CC}}{2} \cdot \frac{C1}{V_{\text{RIPPLE}}} \left( 1 - \frac{V_3}{2} \right)$$

The kind of capacitor used for timing capacitor C1 will determine the accuracy of the unit over the temperature range. Figure 15 illustrates the tachometer output as a function of temperature for the two devices. Note that the LM2907 operating from a fixed external supply has a negative temperature coefficient which enables the device to be used with capacitors which have a positive temperature coefficient and thus obtain overall stability. In the case of the LM2917 the internal zener supply voltage has a positive coefficient which causes the overall tachometer output to have a very low temperature coefficient and requires that the capacitor temperature coefficient be balanced by the temperature coefficient of R1.

### Using Zener Regulated Options (LM2917)

For those applications where an output voltage or current must be obtained independently of the supply voltage variations, the LM2917 is offered. The reference typically has an 11Ω source resistance. In choosing a dropping resistor from the unregulated supply to the device note that the tachometer and op amp circuitry alone require about 3 mA at the voltage level provided by the zener. At low supply voltages, there must be some current flowing in the resistor above the 3 mA circuit current to operate the regulator. As an example, if the raw supply varies from 9V to 16V, a resistance of 470Ω will minimize these zener voltage variations to 160 mV. If the resistor goes under 400Ω or over 600Ω the zener variation quickly rises above 200 mV for the same input variation. Take care also that the power dissipation of the IC is not exceeded at higher supply voltages. Figure 4 shows suitable dropping resistor values.

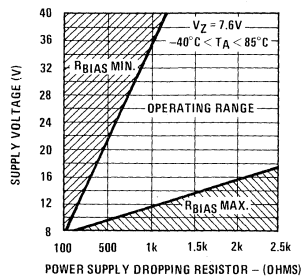


FIGURE 4. Zener Regular Bias Resistor Range

### Input Interface Circuits


The ground referenced input capability of the LM2907-8 allows direct coupling to transformer inputs, or variable reluctance pickups. Figure 5(a) illustrates this connection. In many cases, the frequency signal must be obtained from another circuit whose output may not go below ground. This may be remedied by using ac coupling to the input of the LM2907 as illustrated in Figure 5(b). This approach is very suitable for use with phototransistors for optical pickups. Noisy signal sources may be coupled as shown in Figure 5(c). The signal is bandpass filtered. This can be used, for example, for tachometers operating from breakerpoints on a conventional Kettering




ignition system. Remember that the minimum input signal required by the LM2907 is only 30 mVp-p, but this signal must be able to swing at least 15 mV on either side of the inverting input. The maximum signal which can be applied to the LM2907 input, is  $\pm 28V$ . The input bias current is a typically 100 nA. A path to ground must be provided for this current through the source or by other means as illustrated. With 14-pin package versions of LM2907, LM2917, it is possible to bias the inverting input to the tachometer as illustrated in *Figure 5(d)*. This enables the circuit to operate with input signals that do not go to ground, but are referenced at higher voltages. Alternatively, this method increases the noise immunity where large signal levels are available but large noise signals on ground are also present. To take full advantage of the common-mode rejection of the input differential stage, a balanced bias configuration must be provided. One such circuit is illustrated in *Figure 5(e)*. With this arrangement, the effective common-mode rejection may be virtually infinite, owing to the input hysteresis.
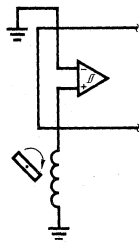
### Output Configurations


LM2907, LM2917 series devices incorporate an unusually flexible op amp/comparator device on-chip for interfacing with a wide variety of loads. This flexibility results from the availability of both the collector and emitter of the output transistor which is capable of driving up to 50 mA of load current. When the non-inverting input is higher than the inverting input, this output transistor is turned "ON." It may be used to drive loads to either the positive or the negative supply with the emitter or collector respectively connected to the other supply. For example, *Figure 6(a)*, a simple speed switch can be constructed in which the speed signal derived from the frequency to voltage converter is compared to a reference derived simply by a resistive divider from the power supply. When the speed signal exceeds the reference, the output transistor turns on the light emitting diode in the load. A small current limiting resistor should be placed in series with the output to protect the LED and the output transistor.




(a) Ground Referenced Inputs

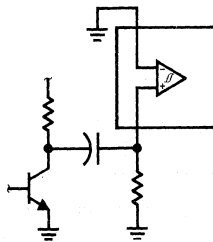


(b) AC Coupled Input

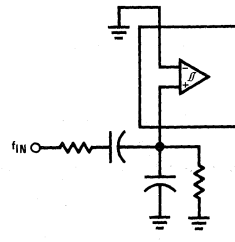

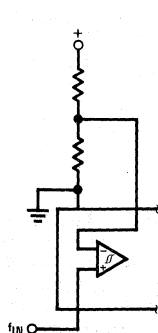(c) Bandpass Filtered Input Reduces Noise




(d) Above Ground Sensing

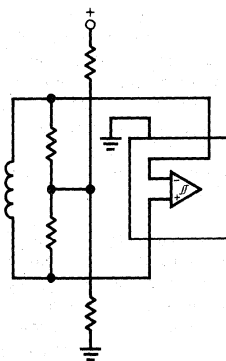


(e) High Common-Mode Rejection Input Circuit


FIGURE 5. Tachometer Input Configurations

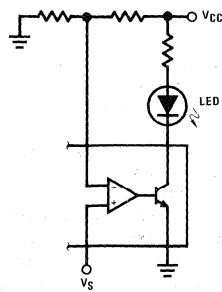


(a) Switching an LED

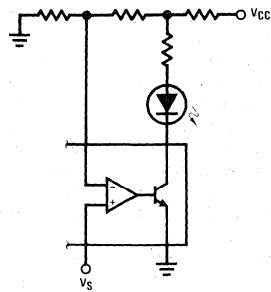


(b) Adding Hysteresis to LED Switch

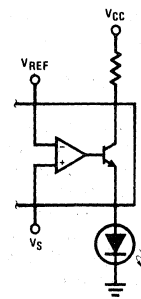


(c) Switching a Grounded Load

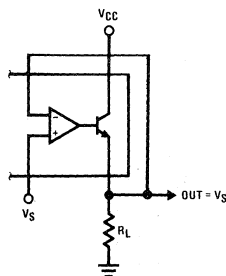

(d) Voltage Follower

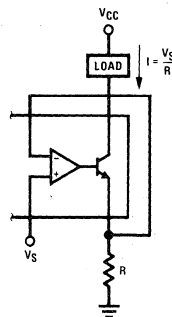

(e) Voltage to Current Converter

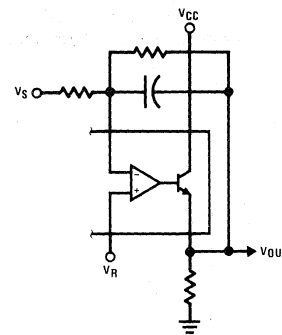

(f) Integrator

FIGURE 6. Output Configurations

This circuit has no hysteresis in it, i.e., the turn "ON" and turn "OFF" speed voltages are essentially equal. In cases where speed may be fluctuating at a high rate and a flashing LED would be objectionable, it is possible to incorporate hysteresis so that the switch-on speed is above the switch-off speed by a controlled amount. Such a configuration is illustrated in Figure 6(b). Figure 6(c) shows how a grounded load can also be switched by the circuit. In this case, the current limiting resistor is placed in the collector of the power transistor. The base current of the output transistor (Q45) is limited by a 5 k $\Omega$  base resistor (see Figure 2). This raises the output resistance so that the output swing will be reduced at full load.

The op amp/comparator is internally compensated for unity gain feedback configurations as in Figure 6(d). By directly connecting the emitter output to the non-inverting input, the op amp may be operated as a voltage follower. Note that a load resistor is required externally. The op amp can also be operated, of course, as an amplifier, integrator, active filter, or in any other normal operational amplifier configuration.

One unique configuration which is not available with standard operational amplifiers, is shown in Figure 6(e). Here the collector of the output transistor is used to

drive a load with a current which is proportional to the input voltage. In other words, the circuit is operating as a voltage to current converter. This is ideal for driving remote signal sensors and moving coil galvanometers. Figure 6(f) shows how an active integrator can be used to provide an output which falls with increasing speed.

These are the basic configurations obtainable with the op amp/comparator. Further combinations can be seen in the applications shown in Part II of this application note.

#### Transient Protection

Many application areas use unregulated power supplies which tend to expose the electronics to potentially damaging transients on the power supply line. This is particularly true in the case of automotive applications where two such transients are common.<sup>1</sup> First is the load dump transient. This occurs when a dead battery is being charged at a high current and the battery cable comes loose, so that the current in the alternator inductance produces a positive transient on the line in the order of 60V to 120V. The second transient is called field decay. This occurs when the ignition is turned "OFF" and the energy stored in the field winding of the alternator causes a negative 75V transient on the ignition line.

Figure 7 illustrates methods for protecting against these and other transients. Figure 7(a) shows a typical situation in which the power supply to the LM2907 can be provided through a dropping resistor and regulated by an external zener diode Z1, but the output drive is required to operate from the full available supply voltage. In this case, a separate protection zener Z2 must be provided if the voltage on the power supply line is expected to exceed the maximum rated voltage of the LM2907.

In Figure 7(b) and 7(c), the output transistor is required only to drive a simple resistive load and no secondary protection circuits are required. (Note that the dropping resistor to the zener also has to supply current to the output circuit). With the foregoing circuits, reverse supply protection is supplied by the forward biased zener diode. This device should be a low forward resistance unit in order to limit the maximum reverse voltage applied to the integrated circuit. Excessive reverse voltage on the IC can cause high currents to be conducted by the substrate diodes with consequent danger of permanent damage. Up to 1V negative can generally be tolerated. Versions with internal zeners may be self-protecting depending on the size of dropping resistor used. In applications where large negative voltage transients may be anticipated, a blocking diode may be connected in the power supply line to the IC as illustrated in Figure 7(d). During these negative transients, the diode D1 will be reverse biased and prevent reverse currents flowing in the IC. If these transients are short and the capacitor C1 is large enough, then the power to the IC can be sustained. This is useful to prevent change of state or change of charge in systems connected to it.

## Temperature Ranges and Packaging Considerations

The LM2907, LM2917 series devices are specified for operation over the temperature range  $-40^{\circ}\text{C}$  to  $+85^{\circ}\text{C}$ .

The devices are normally packaged in molded epoxy, dual-in-line packages. Other temperature ranges and other packages are available to special order. For reliability requirements beyond those of normal commercial application where the cost of military qualification is not bearable, other programs are available such as B+.

## PART II — APPLICATIONS

### INTRODUCTION

The LM2907, LM2917 series devices were designed not only to perform the basic frequency to voltage function required in many systems, but also to provide the input and output interface so often needed, so that low cost implementations of complete functions are available.

The concept of building blocks requires that a function be performed in the same way as it can be mathematically defined. In other words, a frequency to voltage converter will provide an output voltage proportional to frequency which is independent of the input voltage or other input parameters, except the frequency. In the same way, the output voltage will be zero when the input frequency is zero. These features are built into the LM2907.

Applications for the device range from simple speed switch for anti-pollution control device functions in automobiles, to motor speed controls in industrial

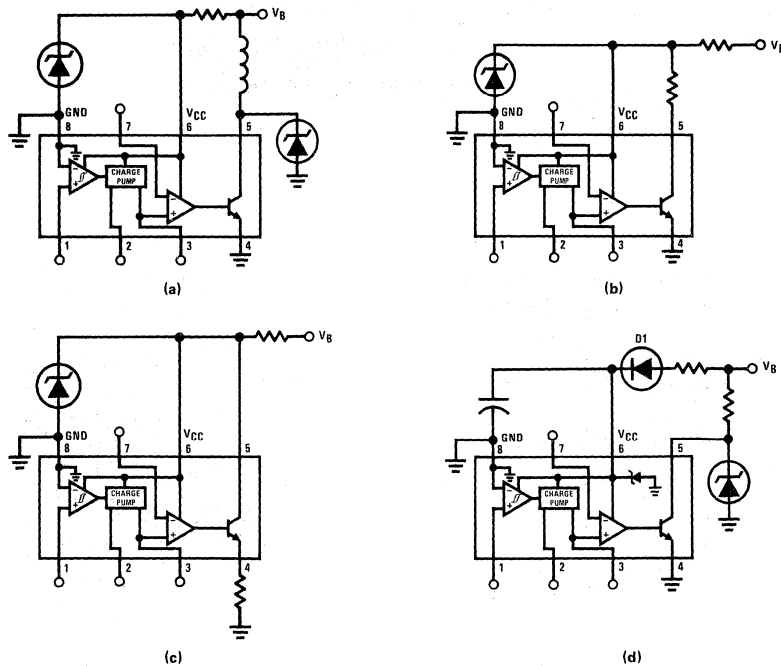


FIGURE 7. Transient Protection Schemes

applications. The applications circuits which follow are designed to illustrate some of the capabilities of the LM2907. In most cases, alternative input or output configurations can be mixed and matched at will and other variations can be determined from the description in Part I of this application note. For complete specifications, refer to the data sheet.

### Speed Switches

Perhaps the most natural application of the LM2907 is in interfacing with magnetic pickups, such as the one illustrated in *Figure 8* to perform speed switching functions. As an example, New York taxis are required to change the intensity of the warning horn above and below 45 mph. Other examples include an over-speed warning, where a driver may set the desired maximum speed and have an audible or visual warning of speeds in excess of that level. Many anti-pollution devices included on several recent automobile models have included a speed switch to disable the vacuum advance function until a certain speed is attained<sup>2</sup>. A circuit which will perform these kind of functions is shown in *Figure 9*. A typical magnetic pickup for automotive applications will provide a thousand pulses per mile so that at 60 mph the incoming frequency will be 16.6 Hz. If the reference level on the comparator is set by two equal resistors R1 and R2 then the desired value of C1 and R1 can be determined from the simple relationship:

$$\frac{V_{CC}}{2} = V_{CC} \cdot C_1 \cdot R_1 \cdot f.$$

or  $C_1 R_1 f = 0.5$

and hence  $C_1 R_1 = 0.03$

From the RC selection chart in *Figure 10* we can choose suitable values for R1 and C1. Examples are 100 kΩ and 0.3μF. The circuit will then switch at approximately 60 mph with the stated input frequency relationship to speed. To determine the ripple voltage refer back to the equation for ripple voltage (under "Choosing R1, C1 and C2"). From this we can determine that there will be about 10 mV of ripple at the switching level. To prevent this from causing chattering of the load a certain amount of hysteresis is added by including R3. This will provide typically 1% of supply as a hysteresis or 1.2 mph in the example. Note that since the reference to the comparator is a function of supply voltage as is the output from the charge pump there is no need to regulate the power supply. The frequency at which switching occurs is independent of supply voltage.

In some industrial applications it is useful to have an indication of past speed excesses, for example in notifying the need for checking of bearings. The LM2907 can be made to latch until the power supply is turned "OFF" in the case where the frequency exceeds a certain limit,

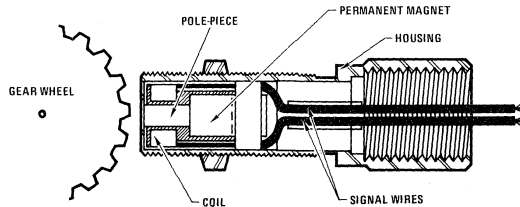


FIGURE 8. Typical Magnetic Pickup

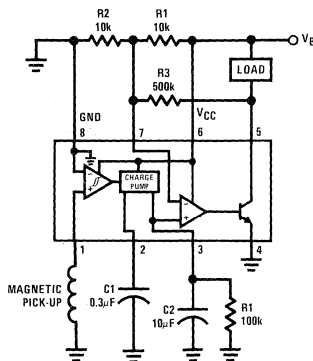


FIGURE 9. Simple Speed Switch Load is Energized when  $f_{IN} > \frac{1}{2C_1 R_1}$

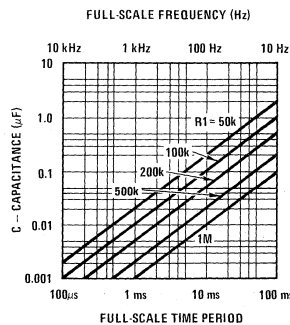


FIGURE 10. RC Selection Chart

by simply connecting the output transistor emitter back to the non-inverting input of the comparator as shown in Figure 11. It can also serve to shut off a tape recorder or editing machine at the end of a rewind cycle. When the speed suddenly increases, the device will sense the condition and shut down the motor.

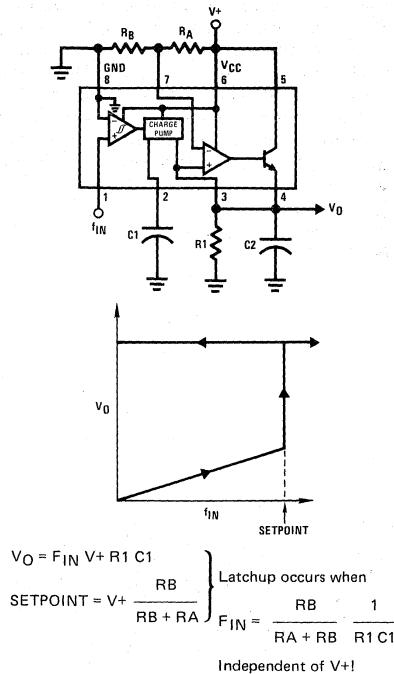


FIGURE 11. Overspeed Latch

### Analog Displays

The LM2907, LM2917 series devices are particularly useful for analog display of frequency inputs. In situations where the display device is a moving coil instrument the advantages of the uncommitted output transistor can be realized by providing a current drive to the meter. This avoids temperature tracking problems with the varying meter resistance and enables high resistance instruments to be driven accurately with relatively large voltages as illustrated in Figure 12. The LM2917 version is employed

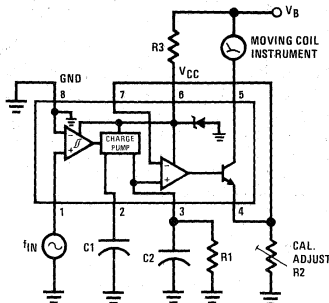


FIGURE 12. Analog Display of Frequency

here to provide a regulated current to the instrument. The onboard 7.6V zener is compatible with car and boat batteries and enables the moving coil instrument to employ the full battery voltage for its deflection. This enables high torque meters to be used. This is particularly useful in high vibration environments such as boats and motorcycles. In the case of boats, the most common speed pickup for the knot meter employs a rotating propeller driving a magnetic pickup device. Meteorologists employ a large number of anemometers for measuring wind velocities and these are frequently coupled by a magnetic pickup. In examples like these, where there is frequently a large distance between the display device and the sensor, the configuration of Figure 13 can be usefully employed to cut down on the

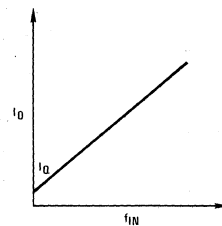
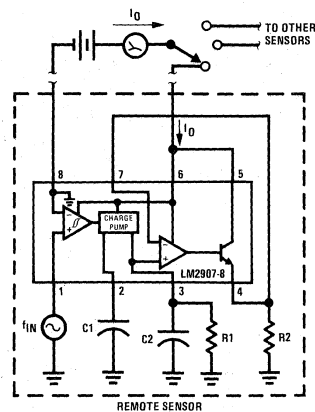


FIGURE 13. Two Wire Remote Speed Sensor

number of wires needed. Here the output current is conducted along the supply line so that a local current sensing device in the supply line can be used to get a direct reading of the frequency at the remote location where the electronics may also be situated. The small zero speed offset due to the device quiescent current may be compensated by offsetting the zero on the display device. This also permits one display device to be shared between several inputs.

### Automotive Tachometer

Not all inputs are derived from variable reluctance magnetic pickups; for example, in spark ignition engines the tachometer is generally driven from the spark coil. An interface circuit for this situation is shown in

Figure 14. This tachometer can be set up for any number of cylinders by linking the appropriate timing resistor as illustrated. A  $500\Omega$  trim resistor can be used to set up final calibration. A protection circuit composed of a  $10\Omega$  resistor and a zener diode is also shown as a safety precaution against the transients which are to be found in automobiles.

### Motor Speed Controls

DC motors with or without brushes can be purchased with ac tachometer outputs already provided by the manufacturer.<sup>3</sup> With these motors in combination with the LM2907, a very low cost speed control can be constructed. In Figure 16 the most simple version is

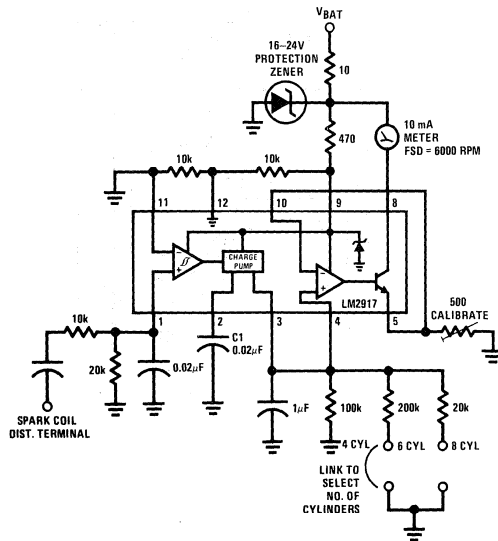


FIGURE 14. Gasoline Engine Tachometer

illustrated where the tachometer drives the non-inverting input of the comparator up towards the preset reference level. When that level is reached, the output is turned off and the power is removed from the motor. As the motor slows down, the voltage from the charge pump output falls and power is restored. Thus speed is maintained by operating the motor in a switching mode. Hysteresis can be provided to control the rate of switching. An alternative approach which gives proportional control is shown in Figure 17. Here the charge pump integrator is shown in a feedback connection around the operational amplifier. The output voltage for zero speed is equal to the reference voltage set up on the potentiometer on the non-inverting input. As speed increases,

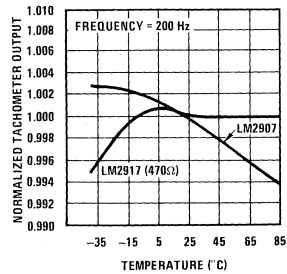


FIGURE 15. Normalized Tachometer Output vs Temperature

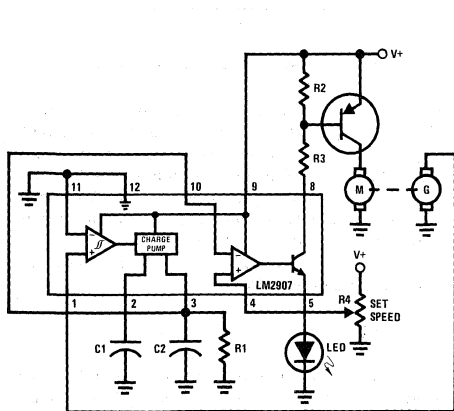


FIGURE 16. Motor Speed Control

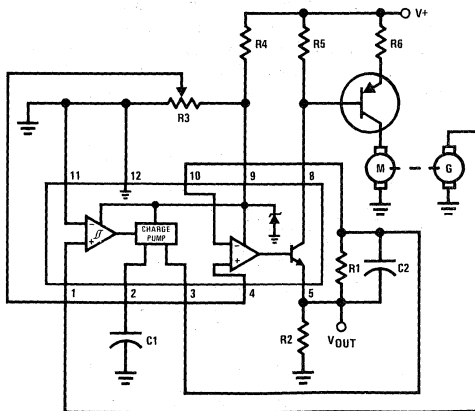


FIGURE 17. Motor Speed Control with Proportional Drive

the charge pump puts charge into capacitor C2 and causes the output  $V_{OUT}$  to fall in proportion to speed. The output current of the op amp transistor is used to provide an analog drive to the motor. Thus as the motor speed approaches the reference level, the current is proportionately reduced to the motor so that the motor gradually comes up to speed and is maintained without operating the motor in a switching mode. This is particularly useful in situations where the electrical noise generated by the switching mode operation is objectionable. This circuit has one primary disadvantage in that it has poor load regulation. A third configuration is shown in *Figure 18*. This employs an LM2907-8 acting as a shunt mode regulator. It also features an LED to indicate when the device is in regulation.

### Position Sensing

In addition to their use to complete tachometer feedback loops, used in position transducer circuits, the LM2907, LM2917 devices can also be used as position transducers. For example, the timing resistor can be removed from pin 3 so that the output current produces a staircase instead of a fixed dc level. If the magnetic pickup senses passing notches or items, a staircase signal is generated which can then be compared with a reference to initiate a switching action when a specified count is reached. For example, *Figure 19* shows a circuit which will count up a hundred input pulses and then switch on the output stage. Examples of this application can be found in automated packaging operations or in line printers.

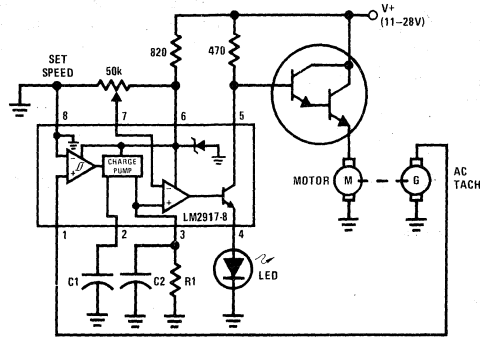


FIGURE 18. Motor Speed Control

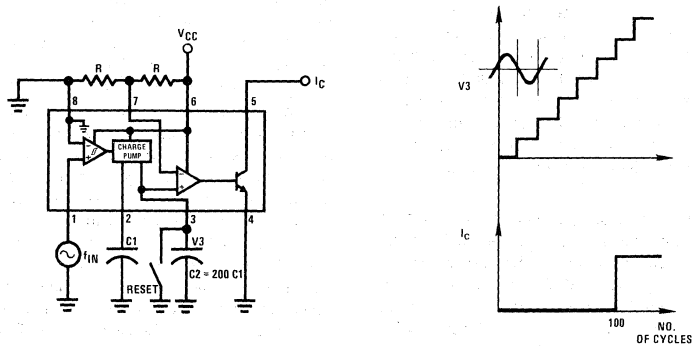


FIGURE 19. Staircase Counter

The output of the tachometer is proportional to the product of supply voltage, input frequency, a capacitor and a resistor. Any one of these may be used as the input variable or they may be used in combination to produce multiplication. An example of a capacitive transducer is illustrated in *Figure 20*, where a fixed input frequency is employed either from the 60 Hz line as a convenient source or from a stable oscillator. The capacitor is a variable element mechanically coupled to the system whose position is to be sensed. The output is proportional to the capacitance value, which can be arranged to have any desired relationship to the mechanical input by suitable shaping of the capacitor electrodes.

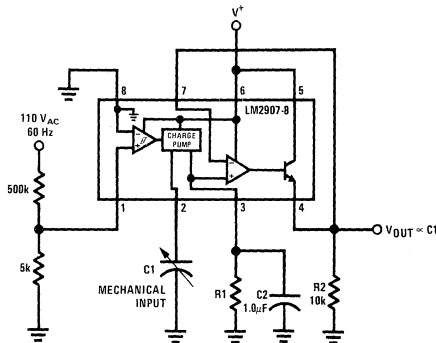


FIGURE 20. Capacitive Transducer

### Analog Systems Building Block

The LM2907, LM2917 series characterize systems building block applications by the feature that the output from the device is proportional only to externally programmed inputs. Any or all of these inputs may be controlled inputs to provide the desired output. For example, in *Figure 20* the capacitance transducer can be operated as a multiplier. In flow measurement indicators, the input frequency can be a variable depending on the flow rate, such as a signal generated from a paddle wheel, propeller or vortex sensor<sup>4</sup>. The capacitor can be an indication of orifice size or aperture size, such as in a throttle body. The product of these two will indicate volume flow. A thermistor could be added to R1 to convert the volume flow to mass flow. So a combination of these inputs, including control voltage on the supply, can be used to provide complex multiplicative analog functions with independent control of the variables.

Phase-locked loops (PLL) are popular today now that low cost monolithic implementations are available off the shelf. One of their limitations is the narrow capture range and hold-in range. The LM2907 can be employed as a PLL helper. The configuration is shown in *Figure 21*. The LM2907 here serves the function of a frequency-to-voltage converter which puts the VCO initially at approximately the right frequency to match the input frequency. The phase detector is then used to close the gap between VCO and input frequency by exerting a control on the summing point. In this way, given proper

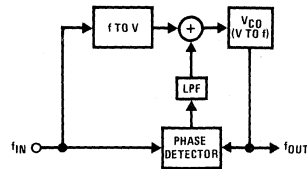


FIGURE 21. Phase-Locked Loop Helper  
Added f to V Greatly Increases Capture and Hold Range

tracking between the frequency-to-voltage converter and the VCO, (which is a voltage-to-frequency converter), a wide-range phase loop can be developed.

The linearity of voltage controlled oscillators can be improved by employing the LM2907 as a feedback control element converting the frequency back to voltage and comparing with the input voltage. This can often be a lower cost solution to linearizing the VCO than by working directly on the VCO itself in the open loop mode. The arrangement is illustrated in *Figure 22*.

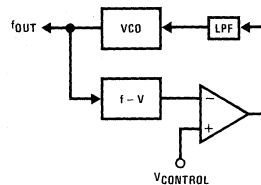


FIGURE 22. Feedback Controlled VCO



### Digital Interface

A growing proportion of the complex control systems today are being controlled by microprocessors and other digital devices. Frequently they require inputs to indicate position or time from some mechanical input. The LM2907 can be used to provide zero crossing datum to a digital system using the circuits illustrated in *Figure 23*. At each zero crossing of the input signal the charge pump changes the state of capacitor C1 and provides a one-shot pulse into the zener diode at pin 3. The width of this pulse is controlled by the internal current of pin 2 and the size of capacitor C1 as well as by the supply voltage. Since a pulse is generated by each zero crossing of the input signal we call this a "two-shot" instead of a "one-shot" device and this can be used for doubling the frequency that is presented to the microprocessor control system. If frequency doubling is not required and a square wave output is preferred, the circuit of *Figure 24* can be employed. In this case, the output swing is the same as the swing on pin 2 which is a swing of half supply voltage starting at  $1 V_{BE}$  below one quarter of supply and going to  $1 V_{BE}$  below three-quarters of supply. This can be increased up to the full output swing capability by reducing or removing the negative feedback around the op amp.



The staircase generator shown in Figure 19 can be used as an A-D converter. A suitable configuration is shown in Figure 25. To start a convert cycle the processor generates a reset pulse to discharge the integrating capacitor C2. Each complete clock cycle generates a charge and discharge cycle on C1. This results in two steps per cycle being added to C2. As the voltage on C2

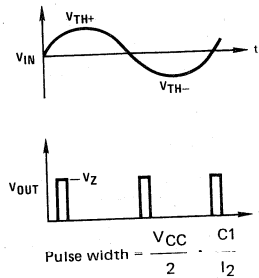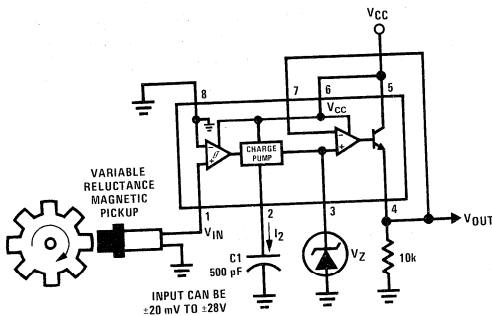increases, clock pulses are returned to the processor. When the voltage on C2 steps above the analog input voltage the data line is clamped and C2 ceases to charge. The processor, by counting the number of clock pulses received after the reset pulse, is thus loaded with a digital measure of the input voltage. By making  $C2/C1 = 1024$  an 8-bit A-D is obtained.



Output frequency equal twice input frequency.  $Pulse\ width = \frac{V_{CC}}{2} \cdot \frac{C1}{I2}$  Pulse height =  $V_{ZENER}$

FIGURE 23. "Two-Shot" Zero Crossing Detector


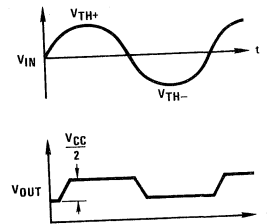
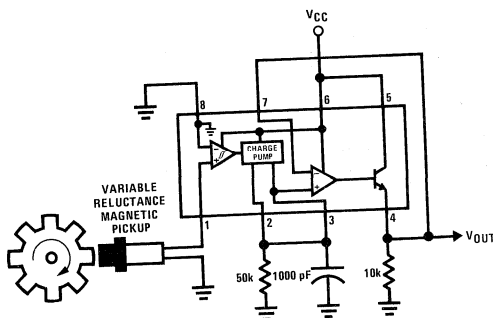
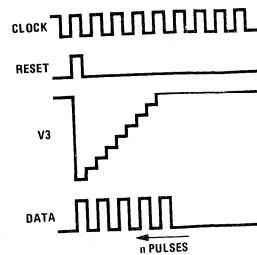


FIGURE 24. Zero Crossing Detector and Line Drivers

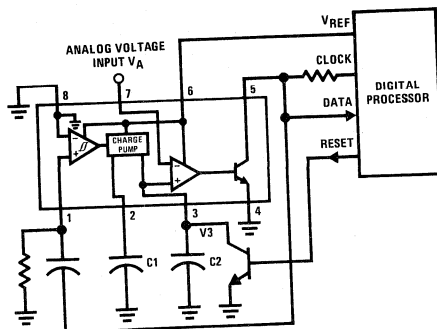

$$n = \frac{C2}{C1} \cdot \frac{VA}{VREF}$$

FIGURE 25. A-D Converter

### Anti-Skid Circuit Functions

Motor Vehicle Standards 121 place certain stopping requirements on heavy vehicles which require the use of electronic anti-skid control devices.<sup>5</sup> These devices generally use variable reluctance magnetic pickup sensors on the wheels to provide inputs to a control module. One of the questions which the systems designer must answer is whether to use the average from each of the two wheels on a given axle or to use the lower of the two speeds or to use the higher of the two speeds. Each of the three functions can be generated by a single pair of LM2907-8 as illustrated in Figures 26-28. In Figure 26 the input frequency from each wheel sensor is converted to a voltage in the normal manner. The op amp/

comparator is connected with negative feedback with a diode in the loop so that the amplifier can only pull down on the load and not pull up. In this way, the outputs from the two devices can be joined together and the output will be the lower of the two input speeds. In Figure 27 the output emitter of the onboard op amp provides the pullup required to provide a select-high situation where the output is equal to the higher of two speeds. The select average circuit in Figure 28 saves components by allowing the two charge pumps to operate into a single RC network. One of the amplifiers is needed then to buffer the output and provide a low impedance output which is the average of the two input frequencies. The second amplifier is available for other applications.


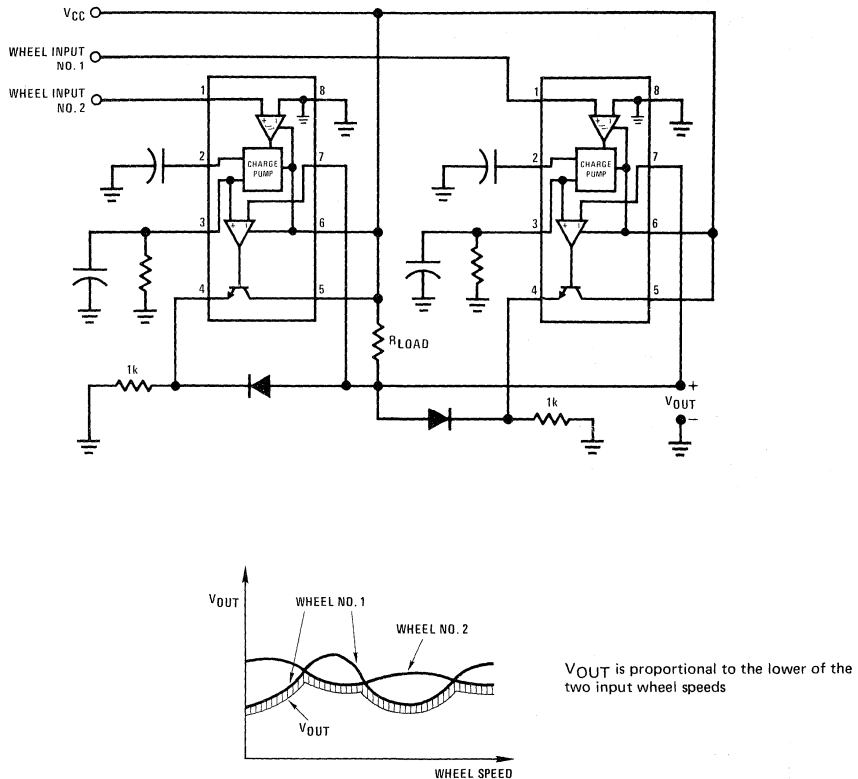
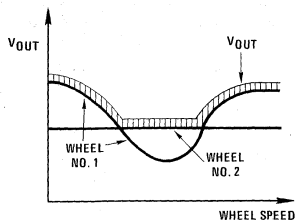


FIGURE 26. "Select-Low" Circuit

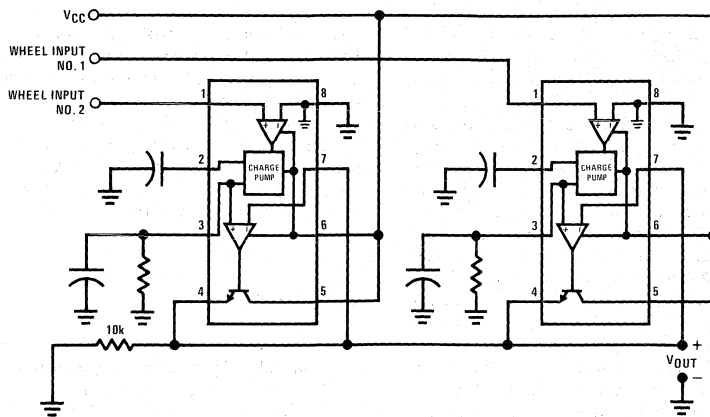

$V_{OUT}$  is proportional to the higher of the two input wheel speeds

FIGURE 27. "Select-High" Circuit

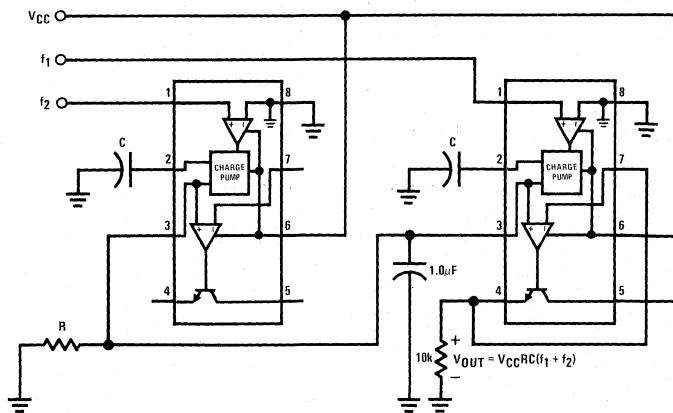


FIGURE 28. "Select-Average" Circuit

### Transmission and Clutch Control Functions

Electric clutches can be added to automotive transmissions to eliminate the 6% slip which typically occurs during cruise and which results in a 6% loss in fuel economy. These devices could be operated by a pair of LM2907's as illustrated in Figure 29. Magnetic pickups are connected to input and output shafts of the transmission respectively and provide frequency inputs  $f_1$  and  $f_2$  to the circuit. Frequency,  $f_2$ , being the output shaft speed, is also a measure of vehicle road speed. Thus the LM2907-8 No. 2 provides a voltage proportional to road speed at pin 3. This is buffered by the op amp in LM2907-8 No. 1 to provide a speed output  $V_{OUT1}$  on pin 4. The input shaft provides charge pulses at the rate of  $2f_1$  into the inverting node of op amp 2. This node has the integrating network R1, C3 going back to the output of the op amp so that the charge pulses are integrated and provide an inverted output voltage proportional to the input speed. Thus the output  $V_{OUT2}$  is proportional to the difference between the two input frequencies. With these two signals—the road speed and the difference between road speed and input shaft speed—it is possible to develop a number of control functions including the electronic clutch and a complete electronic transmission control. (In the configuration shown, it is not possible for  $V_{OUT2}$  to go below zero so that there is a limitation to the output swing in this direction. This may be overcome by returning R3 to a negative bias supply instead of to ground.)

### CONCLUSION

The applications presented in this note indicate that the LM2907, LM2917 series devices offer a wide variety of uses ranging from very simple low cost frequency to voltage conversion to complex systems building blocks. It is hoped that the ideas contained here have given suggestions which may help provide new solutions to old problems. Additional applications ideas are included in the data sheet, which should be referred to for all specifications and characteristics.

### REFERENCES

1. Society of Automotive Engineers: Preliminary Recommended Environmental Practices for Electronic Equipment Design. October 1974.
2. See for example: Pollution Control Installers Handbook—California Bureau of Automotive Repair No. BAR H-001 § 5.5.4 NOX control systems.
3. TRW Globe Motors, 2275 Stanley Avenue, Dayton, Ohio 45404.
4. S.A.E. Paper #760018 Air Flow Measurement for Engine Control—Robert D. Joy.
5. Code of Federal Regulations. Title 49 Transportation; Chapter V—National Highway Traffic Safety Administration, Dept. of Transportation; Part 571—Federal Motor Vehicle Safety Standards; Standard No. 121.

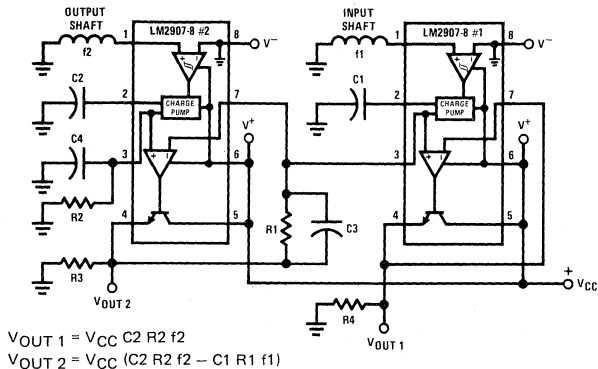


FIGURE 29. Transmission or Clutch Control Functions

# IC Zener Eases Reference Design

National Semiconductor  
Application Note 173  
Robert C. Dobkin  
November 1976



## description

A new IC Zener with low dynamic impedance and wide operating current range significantly simplifies reference or regulator circuit design. The low dynamic impedance provides better regulation against operating current changes, easing the requirements on the biasing supply. Further, the temperature coefficient is independent of operating current, so that the LM129 can be used at any convenient current level. Other characteristics such as temperature coefficient, noise and long term stability are equal to or better than good quality discrete Zeners.

The LM129 uses a new subsurface breakdown IC Zener combined with a buffer circuit to lower dynamic impedance. The new subsurface Zener has low noise and excellent long term stability since the breakdown is in the bulk of the silicon. Circuitry around the Zener supplies internal biasing currents and buffers external current changes from the Zener. The overall breakdown is about 6.9 V with devices selected for temperature coefficients.

The Zener is relatively straightforward. A buried Zener D1 breaks down biasing the base of transistor Q1. Transistor Q1 drives two buffers Q2 and Q3. External current changes through the circuit are fully absorbed by the buffer transistors rather than by D1. Current through D1 is held constant at 250  $\mu$ A by a 2k resistor across the emitter base of Q1 while the emitter-base voltage of Q1 nominally temperature compensates the reference voltage.

The other components, Q4, Q5 and Q6, set the operating current of Q1. Frequency compensation is accomplished with two junction capacitors.

All that is needed for biasing in most applications is a resistor as shown in figure 2. Biasing current can be anywhere from 0.6 mA to 15 mA with little change in performance. Optimally, however, the biasing current should be as low as possible for the best regulation. The dynamic impedance of the LM129 is about 1  $\Omega$  and is independent of current. Therefore, the regulation of the LM129 against voltage changes is 1/Rs.

Lower currents or higher Rs give better regulation. For example, with a 15 V supply and 1 mA operating current, the reference change for a 10% change in the 15 V supply is 180  $\mu$ V. If the LM129 is run at 5 mA, the change is 900  $\mu$ V or 5 times worse. By comparison, a standard IN821 Zener will change about 17 mV. All discrete Zeners have about the same regulation since their dynamic impedance is inversely proportional to operating current.

If the Zener does not have to be grounded, a bridge compensating circuit can be used to get virtually perfect regulation, as shown in figure 3. A small compensating voltage is generated across R1, which matches the dynamic impedance of the LM129. Since the dynamic impedance of the LM129 is linear with current, this circuit will work even with large changes in the unregulated input voltage.

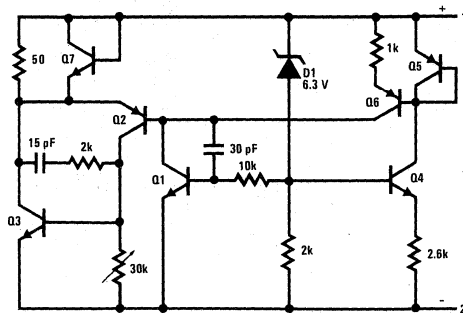


FIGURE 1. IC Reference Zener

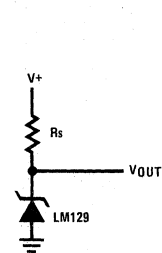


FIGURE 2. Basic Biasing

Other output voltages are easily obtained with the simple op-amp circuit shown in figure 4. A simple non-inverting amplifier is used to boost and buffer the Zener to 10 V. The reference is run directly from the input power rather than the output of the op-amp. When the Zener is powered from the op-amp, special starting circuitry is sometimes necessary to insure the output comes up in the right polarity. For outputs lower than the breakdown of the LM129 a divider can be connected across the Zener to drive the op-amp.

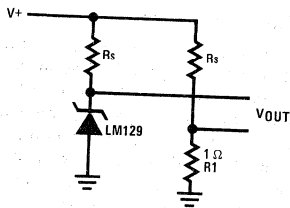


FIGURE 3. Bridge Compensation for Line Changes

An AC square wave or bipolarity output reference can easily be made with an op-amp and FET switch as shown in figure 5. When Q1 is "ON," the LM108 functions as a normal inverting op-amp with a gain of -1 and an output of -6.9 V. With Q1 "OFF" the op-amp acts as a giving 6.9 V at the output. Some non-symmetry will occur from loading change on the LM129 in the different states and mismatch of R1 and R2. Trimming either R1 or R2 can make the output exactly symmetrical around ground.

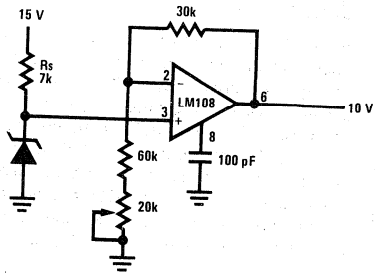


FIGURE 4. 10 Volt Buffered Output Reference

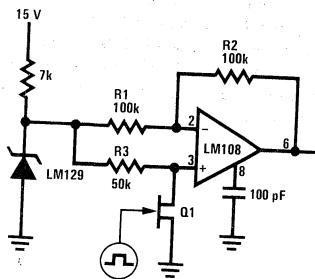


FIGURE 5. Bipolar Output Reference

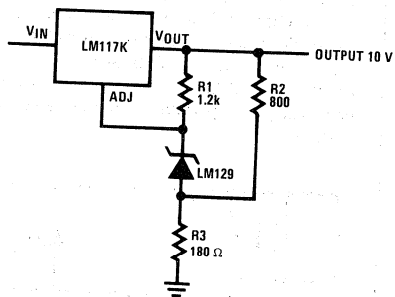


FIGURE 6. High Stability 10V Regulator

By combining the LM129 with an LM117 three-terminal regulator a high stability power regulator can be made. This is shown in figure 6. Resistor R1 biases the LM129 at about 1 mA from the 1.25 V reference in the LM117. The voltage of the LM129 is added to the 1.25 V of the LM117 to make a total reference voltage of 8.1 V. The output voltage is then set at 10 V by R2 and R3. Since the internal reference of the LM117 contributes only about 20% of the total reference voltage, regulation and drift are essentially those of the external Zener. The regulator has 0.2% load and line regulation and if a low drift Zener such as the LM129A is used overall temperature coefficient is less than 0.002%/°C.

The new Zener can be used as the reference for conventional IC voltage regulators for enhanced performance. Noise is lower, time stability is better, and temperature coefficient can be better depending on the device selected. Further, the output voltage is independent of power changes in the regulator.

Figure 7 shows an LM723 using an external LM129 reference. The internal 7 V reference is not used and a single resistor biases the LM129 as the reference. The 5k resistor chosen provides sufficient operating current for the Zener over the 10 V to 40 V input voltage range of the LM723. Since the dynamic impedance of the LM129 is so low, the reference regulation against line changes is only 0.02%/V. This is small compared to the regulation of 0.1%/V for the LM723; however, the resistor can be replaced by a 1 mA to 5 mA FET used as a constant current source for improved regulation. When the FET

is used reference regulation is easily 0.001%/V. Output voltage is set in the standard manner except that for low output voltages sufficient current must be run through the Zener to power the voltage divider supplying the reference to the LM723.

An overload protected power shunt regulator is shown in figure 8. The output voltage is about 7.8 V — the 7 V breakdown of the LM129 plus the 0.8 V emitter-base voltage of the LM395. The LM395 is an IC, 1.5 A power transistor with complete overload protection on the chip. Included on the chip are current limiting and thermal limiting, making the device virtually blowout-proof. Further, the base current is only 5  $\mu$ A, making it easy to drive as a shunt regulator. As the input voltage rises, more drive is applied to the base of the LM395, turning it on harder and dropping more voltage across the series resistance. Should the input voltage rise too high, the LM395 will current limit or thermal limit, protecting itself.

The new IC Zener can replace existing Zeners in just about any application with improved performance and simpler external circuitry. As with any Zener reference, devices are selected for temperature coefficient and operating temperature range. Since the devices are made by a standard integrated circuit process, cost is low and good reproducibility is obtained in volume production.

Finally, since the device is actually an IC, it is packaged in a rugged TO-46 metal can package or a 3-lead plastic transistor package.

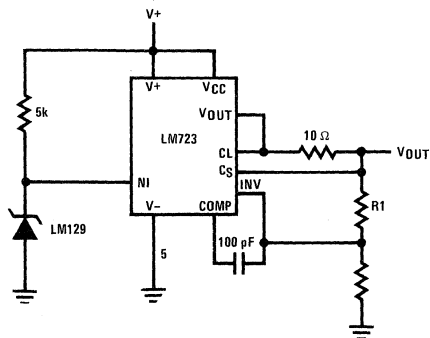


FIGURE 7. External Reference For IC

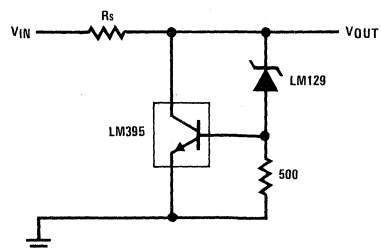


FIGURE 8. Power Shunt Regulator





# Applications for an Adjustable IC Power Regulator

National Semiconductor  
Application Note 178  
Robert C. Dobkin  
January 1977



A new 3-terminal adjustable IC power regulator solves many of the problems associated with older, fixed regulators. The LM117, a 1.5A IC regulator is adjustable from 1.2V to 40V with only 2 external resistors. Further, improvements are made in performance over older regulators. Load and line regulation are a factor of 10 better than previous regulators. Input voltage range is increased to 40V and output characteristics are fully specified for loads of 1.5A. Reliability is improved by new overload protection circuitry as well as 100% burn-in of all parts. The table below summarizes the typical performance of the LM117.

TABLE I.

Output Voltage Range	1.25V–40V
Line Regulation	0.01%/V
Load Regulation $I_L = 1.5A$	0.1%
Reference Voltage	1.25V
Adjustment Pin Current	50 $\mu A$
Minimum Load Current (Quiescent Current)	3.5 mA
Temperature Stability	0.01%/°C
Current Limit	2.2A
Ripple Rejection	80 dB

The overload protection circuitry on the LM117 includes current limiting, safe-area protection for the internal power transistor and thermal limiting. The current limit is set at 2.2A and, unlike presently available positive regulators, remains relatively constant with temperature. Over a  $-55^{\circ}C$  to  $+150^{\circ}C$  temperature range, the current limit only shifts about 10%.

At high input-to-output voltage differentials the safe-area protection decreases the current limit. With the LM117, full output current is available to 15V differential and, even at 40V, about 400 mA is available. With some regulators, the output will shut completely off when the input-to-output differential goes above 30V, possibly causing start-up problems. Finally, the thermal limiting is always active and will protect the device even if the adjustment terminal should become accidentally disconnected.

Since the LM117 is a floating voltage regulator, it sees only the input-to-output voltage differential. This is of benefit, especially at high output voltage. For example, a 30V regulator nominally operating with a 38V input can have a 70V input transient before the 40V input-to-output rating of the LM117 is exceeded.

## BASIC OPERATION

The operation of how a 3-terminal regulator is adjusted can be easily understood by referring to *Figure 1*, which shows a functional circuit. An op amp, connected as a unity gain buffer, drives a power Darlington. The op amp and biasing circuitry for the regulator is arranged so that all the quiescent current is delivered to the regulator output (rather than ground) eliminating the need for a separate ground terminal. Further, all the circuitry is designed to operate over the 2V to 40V input-to-output differential of the regulator.

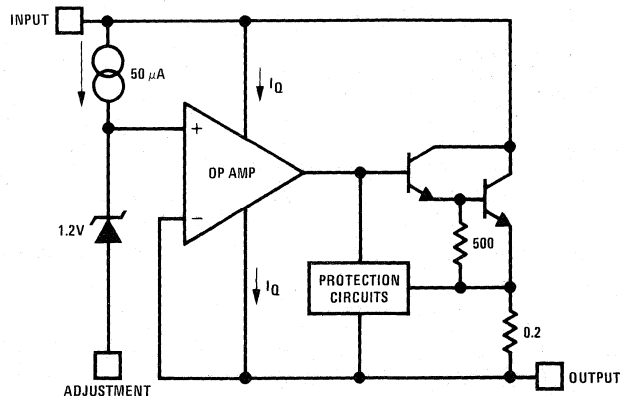


FIGURE 1. Functional Schematic of the LM117

A 1.2V reference voltage appears inserted between the non-inverting input of the op amp and the adjustment terminal. About 50  $\mu$ A is needed to bias the reference and this current comes out of the adjustment terminal. In operation, the output of the regulator is the voltage of the adjustment terminal plus 1.2V. If the adjustment terminal is grounded, the device acts as a 1.2V regulator. For higher output voltages, a divider R1 and R2 is connected from the output to ground as is shown in Figure 2. The 1.2V reference across resistor R1 forces 10 mA of current to flow. This 10 mA then flows through R2, increasing the voltage at the adjustment terminal and therefore the output voltage. The output voltage is given by:

$$V_{OUT} = 1.2V \times \left( 1 + \frac{R2}{R1} \right) + 50 \mu A R2$$

The 50  $\mu$ A biasing current is small compared to 5 mA and causes only a small error in actual output voltages. Further, it is extremely well regulated against line voltage or load current changes so that it contributes virtually no error to dynamic regulation. Of course, programming currents other than 10 mA can be used depending upon the application.

Since the regulator is floating, all the quiescent current must be absorbed by the load. With too light of a load,

regulation is impaired. Usually, a 5 mA programming current is sufficient; however, worst case minimum load for commercial grade parts requires a minimum load of 10 mA. The minimum load current can be compared to the quiescent current of standard regulators.

## APPLICATIONS

An adjustable lab regulator using the LM117 is shown in Figure 2 and has a 1.2V to 25V output range. A 10 mA program current is set by R1 while the output voltage is set by R2. Capacitor C1 is optional to improve ripple rejection so that 80 dB is obtained at any output voltage. The diode, although not necessary in this circuit since the output is limited to 25V, is needed with outputs over 25V to protect against the capacitors discharging through low current nodes in the LM117 when the input or output is shorted.

The programming current is constant and can be used to bias other circuitry, while the regulator is used as the power supply for the system. In Figure 3, the LM117 is used as a 15V regulator while the programming current powers an LM129 zener reference. The LM129 is an IC zener with less than 1  $\Omega$  dynamic impedance and can operate over a range of 0.5 mA to 15 mA with virtually no change in performance.

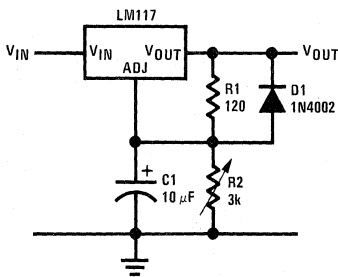


FIGURE 2. Basic Voltage Regulator

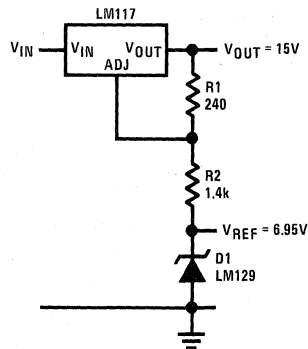


FIGURE 3. Regulator and Voltage Reference

Another example of using the programming current is shown in *Figure 4* where the output setting resistor is tapped to provide multiple output voltage to op amp buffers. An additional transistor is included as part of the overload protection. When any of the outputs are shorted, the op amp will current limit and a voltage will be developed across its inputs. This will turn "ON" the transistor and pull down the adjustment terminal of the LM117, causing all outputs to decrease, minimizing possible damage to the rest of the circuitry.

Ordinary 3-terminal regulators are not especially attractive for use as precision current regulators. Firstly, the

quiescent current can be as high as 10 mA, giving at least 1% error at 1A output currents, and more error at lower currents. Secondly, at least 7V is needed to operate the device. With the LM117, the only error current is 50  $\mu$ A from the adjustment terminal, and only 4.2V is needed for operation at 1.5A or 3.2V at 0.5A. A simple 2-terminal current regulator is shown in *Figure 5* and is usable anywhere from 10 mA to 1.5A.

*Figure 6* shows an adjustable current regulator in conjunction with the voltage regulator from *Figure 2* to make constant voltage/constant current lab-type supply. Current sensing is done across R1, a 1 $\Omega$  resistor,

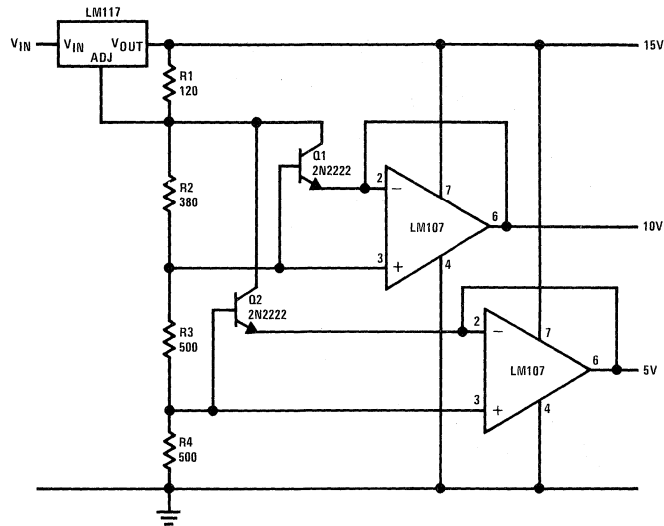


FIGURE 4. Regulator with Multiple Outputs

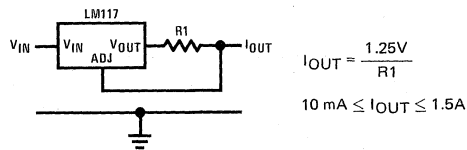


FIGURE 5. 2-Terminal Current Regulator

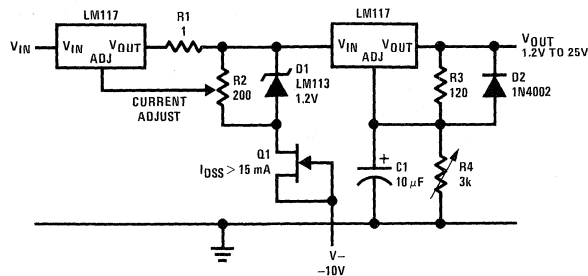


FIGURE 6. Adjustable Regulator. Constant Voltage/Constant Current, 10 mA to 1.2A

while R2 sets the current limit point. When the wiper of R2 is connected, the  $1\Omega$  sense resistor current is regulated at 1.2A. As R2 is adjusted, a portion of the 1.2V reference of the LM117 is cancelled by the drop across the pot, decreasing the current limit point. At low output currents, current regulation is degraded since the voltage across the  $1\Omega$  sensing resistor becomes quite low. For example, with 50 mA output current, only 50 mV is dropped across the sense resistor and the supply rejection of the LM117 will limit the current regulation to about 3% for a 40V change across the device. An alternate current regulator is shown in Figure 7 using an additional LM117 to provide the reference, rather than an LM113 diode. Both current regulators need a negative supply to operate down to ground.

Figure 8 shows a 2-wire current transmitter with 10 mA to 50 mA output current for a 1V input. An LM117 is biased as a 10 mA current source to set the minimum current and provide operating current for the control circuitry. Operating off the 10 mA is an LM108 and an LM129 zener. The zener provides a common-mode voltage for operation of the LM108 as well as a 6.9V reference, if needed. Input signals are impressed across R3, and the current through R3 is delivered to the output of the regulator by Q1 and Q2. For a  $25\Omega$  resistor, this gives a 40 mA current change for a 1V input. This circuit can be used in 4 mA to 20 mA applications, but the LM117 must be selected for low quiescent current. Minimum operating voltage is about 12V.

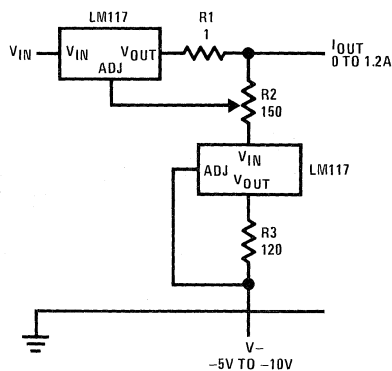


FIGURE 7. Adjustable Current Regulator

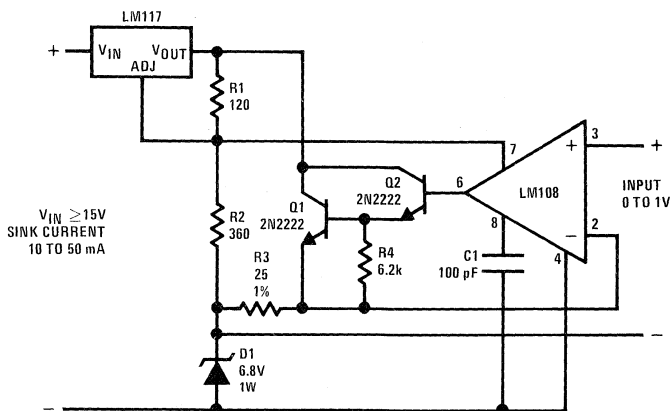


FIGURE 8. 10 mA to 50 mA 2-Wire Current Transmitter

# Analog-to-Digital Converter Testing

National Semiconductor  
Application Note 179  
Dennis Dauenhauer  
Doug Falco  
April 1977



Attempting to test an analog-to-digital converter can be a challenging and rewarding experience. The recent increased interest in converter products has spawned renewed interest in test equipment dedicated to testing converters. Unfortunately, the broad range of converter products available makes testing by a single piece of equipment difficult at best.

A crude method of testing would be to monitor an analog signal at the converter input using a precision DVM and compare that with the converter output. This is simple enough to do, but in most cases this would prove impractical. For a 10-bit converter, this would require plotting 1,024 such readings. Automatic equipment can be used, but in all cases will require some sophisticated interface hardware and software routines. A person favoring auto test equipment can expect to pay around \$10,000 for the hardware and at least that much for the software. What will be described is a method which costs a couple hundred dollars in components and which gives a device characteristic in a relatively short time period.

Because very little standardization has occurred for converter products, the user must adhere to the old adage "caveat emptor" or "buyer beware". The only universal statement that can be made for definitions of terms characterizing converter products is that they are universally inconsistent. For this reason, this application note will provide a simple method of providing a very graphic means of testing several of National's A/D converter products. It is also recommended that the reader refer to Application Note AN-156 for additional information concerning converter products definitions. Specific parameters which will be focused on in this paper are zero error, scale error, non-linearity error, differential non-linearity, monotonicity, total unadjusted error and quantizing error.

The block diagram of *Figure 1* shows the basic blocks of the complete test circuit of *Figure 2*. A storage scope is required to provide a continuous display. A Tektronix 7633 or equivalent is recommended. A typical characteristic for the ADC0800 shown in *Figure 3*.

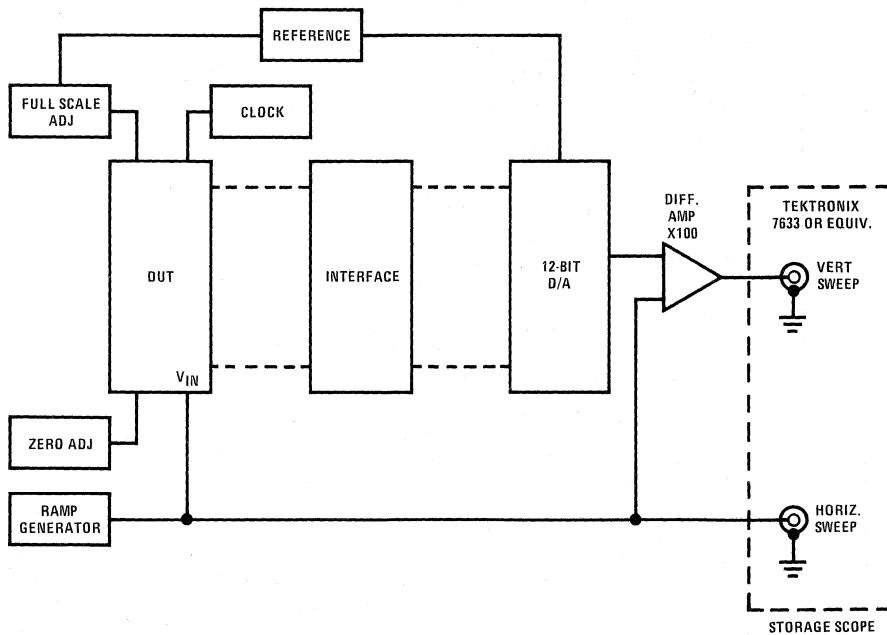


FIGURE 1. Block Diagram for A/D Tester



The ramp generator provides a linear output voltage from 0V to 10V. This voltage is used as a) the horizontal amplifier input to the scope b) as a reference voltage to the difference amplifier and c) as the analog input voltage to the device under test.

The storage scope is used as an X-Y display with the horizontal input functioning as an input amplifier. The vertical input (Y-direction) displays the difference between the converter's analog input voltage and the equivalent output voltage of the same converter. The equivalent output voltage is generated by the 12-bit digital-to-analog converter (DAC1200). The horizontal input (X-direction) displays the difference voltage over the entire analog input voltage range. For a reference voltage set to 10.24V, the range is 0V to 10.24V. In the case of an 8-bit A/D, there would be 256 different voltages displayed across the entire range of the reference.

The test circuit shown in *Figure 2* can be used to test the ADC0800, ADC1211 or the ADC1210. These are 8-bit, 10-bit and 12-bit analog-to-digital converters.

Zero and full scale adjustment circuits are provided to allow a more accurate computation of non-linearity error.

The DAC1200D is a 12-bit D/A converter. It is quite adequate for the 8-bit and 10-bit parts but may be replaced by a higher resolution part if testing 12-bit A/D converters. The LH0044AH is a precision low noise amplifier and the LH0002CH is a buffer amplifier. The output of the reference must be adjusted to the full scale input voltage to assure proper output from the DAC1200. This is done by adjusting R-100.

## TESTING

*Figure 3* shows a typical output characteristic for the ADC0800, an 8-bit A/D converter. The reference line is set by switching the vertical channel (Y-axis amplifier) to dc and triggering the ramp generator. The adjustment is made using the horizontal positioning. The vertical range should be set to 5V/division. The 50 mV/division shown is the effective range of the channel taking into account that the difference amplifier has a gain of 100.

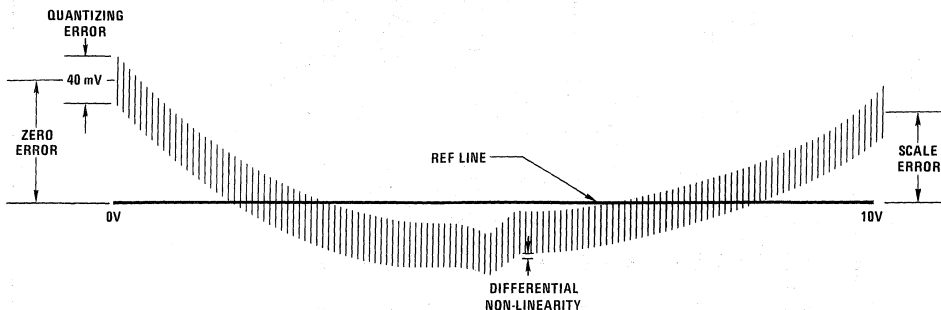


FIGURE 3. Typical Output Characteristic for the ADC0800

When the initial set-up is completed, it is relatively easy to get readings for zero error, scale error, non-linearity error, differential non-linearity error, quantizing error, and to detect missing codes.

Zero error is simply the deviation from the reference line to the middle of the quantizing error when the input voltage is zero. All errors can be expressed as percent of full scale of in LSB's (least significant bits). For a 0V to 10.24V analog input 8-bit converter;

$$1 \text{ LSB} = \frac{10\text{V}}{2^8} = 40 \text{ mV} = 0.40\% \text{ FS}$$

Scale error is the same as the zero error except that it occurs when the analog input voltage is at full scale.

In most applications, it is not the non-linearity in itself which is important, but rather the slope of the non-linearity. For instance, in an application using an A/D to sense gas in a tank and then to compute the remaining miles or time based on the current rate of usage, you do not want a large non-linearity slope. This gives the typical analog gas gauge effect of getting what appears to be good mileage over a certain range and poorer mileage over another range. Specifying non-linearity error and differential non-linearity error provides an error band around which to limit this change in slope or rate of change.

Non-linearity error can be defined in either of 2 ways. Shown in *Figure 3* is the "best straight line" definition for non-linearity. This is the more traditional definition for non-linearity and is the one use for the ADC0800 because of the inherent unidirectional nature of the error. A more conservative definition of "ideal straight line linearity" or more appropriately "total error" is twice that of the best straight line error. This linearity error is the maximum deviation from a straight line drawn between zero and full scale. The ADC1210 and ADC1211, 12-bit and 10-bit A/D converters, use this definition of non-linearity because the deviation can be in either direction.





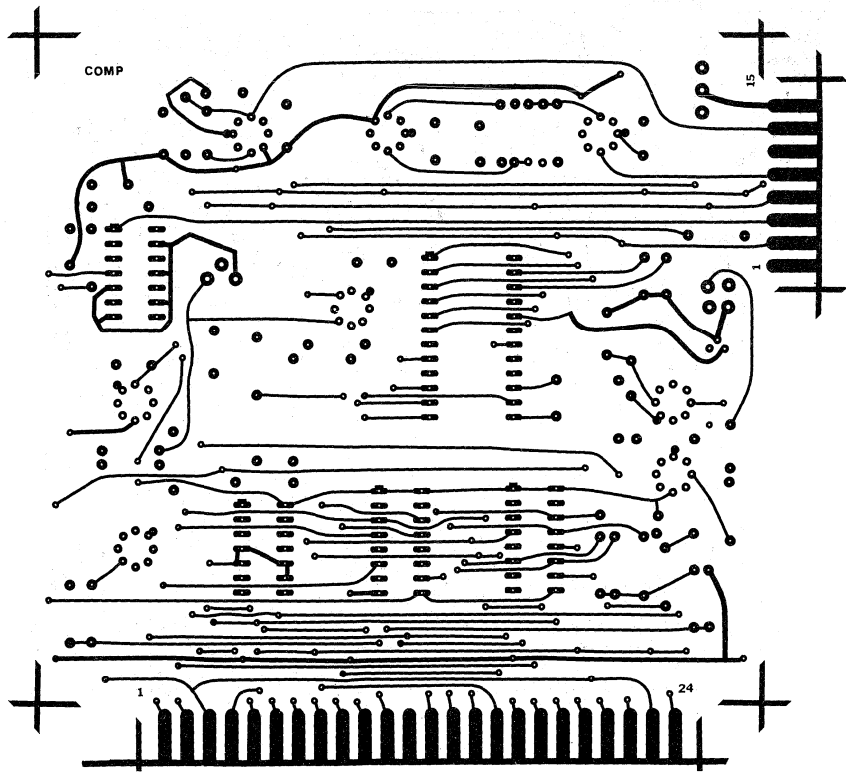


FIGURE 5. Component Side of P.C. Board Layout

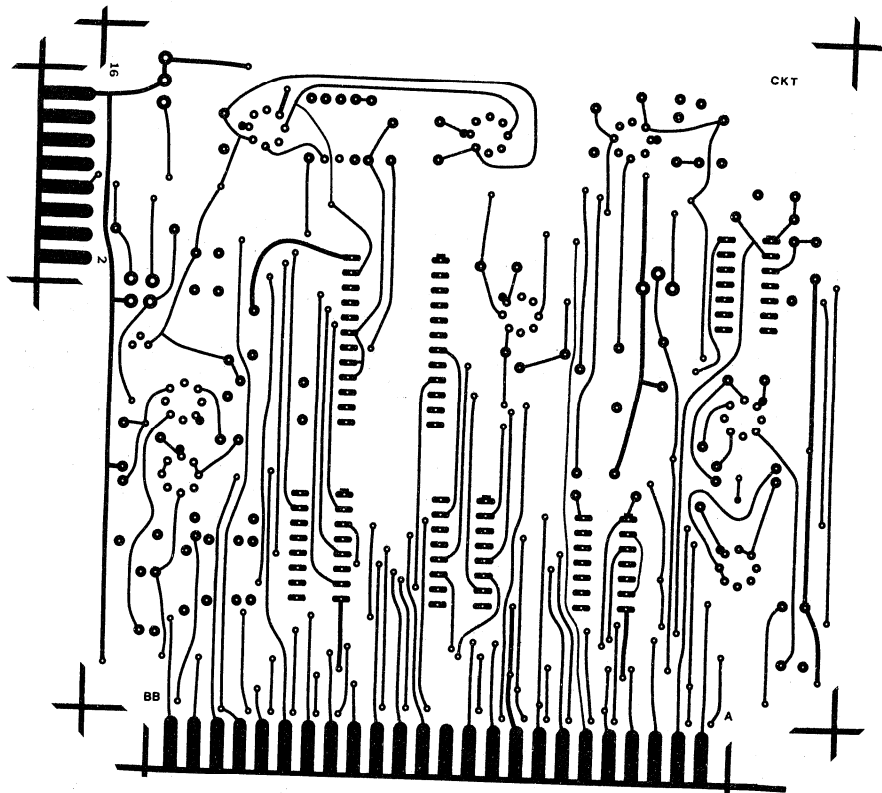


FIGURE 6. Backside of P.C. Board Layout

# 3-Terminal Regulator is Adjustable

National Semiconductor  
Application Note 181  
Robert C. Dobkin  
March 1977



## INTRODUCTION

Until now, all of the 3-terminal power IC voltage regulators have a fixed output voltage. In spite of this limitation, their ease of use, low cost, and full on-chip overload protection have generated wide acceptance. Now, with the introduction of the LM117, it is possible to use a single regulator for any output voltage from 1.2V to 37V at 1.5A. Selecting close-tolerance output voltage parts or designing discrete regulators for particular applications is no longer necessary since the output voltage can be adjusted. Further, only one regulator type need be stocked for a wide range of applications. Additionally, an adjustable regulator is more versatile, lending itself to many applications not suitable for fixed output devices.

In addition to adjustability, the new regulator features performance a factor of 10 better than fixed output regulators. Line regulation is 0.01%/V and load regulation is only 0.1%. It is packaged in standard TO-3 transistor packages so that heat sinking is easily accomplished with standard heat sinks. Besides higher performance, overload protection circuitry is improved, increasing reliability.

## ADJUSTABLE REGULATOR CIRCUIT

The adjustment of a 3-terminal regulator can be easily understood by referring to *Figure 1*, which shows a functional circuit. An op amp, connected as a unity gain buffer, drives a power Darlington. The op amp and biasing circuitry for the regulator are arranged so that all the quiescent current is delivered to the regulator output (rather than ground) eliminating the need for a separate ground terminal. Further, all the circuitry is designed to operate over the 2V to 40V input to output differential of the regulator.

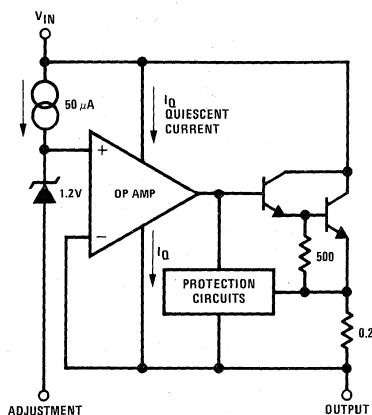



FIGURE 1. Functional Schematic of the LM117

A 1.2V reference voltage appears inserted between the non-inverting input of the op amp and the adjustment terminal. About 50  $\mu$ A is needed to bias the reference and this current comes out of the adjustment terminal. In operation, the output of the regulator is the voltage of the adjustment terminal plus 1.2V. If the adjustment terminal is grounded, the device acts as a 1.2V regulator. For higher output voltages, a divider R1 and R2 is connected from the output to ground as is shown in *Figure 2*. The 1.2V reference across resistor R1 forces 5 mA of current to flow. This 5 mA then flows through R2, increasing the voltage at the adjustment terminal and therefore the output voltage. The output voltage is given by:

$$V_{OUT} = 1.2V \left( 1 + \frac{R2}{R1} \right) + 50 \mu A R2$$

The 50  $\mu$ A biasing current is small compared to 5 mA and causes only a small error in actual output voltages. Further, it is extremely well regulated against line voltage or load current changes so that it contributes virtually no error to dynamic regulation. Of course, programming currents other than 5 mA can be used depending upon the application.

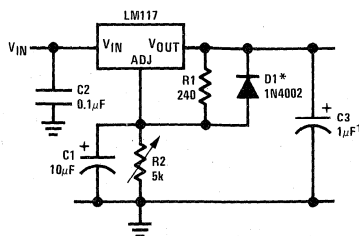Since the regulator is floating, all the quiescent current must be absorbed by the load. With too light of a load, regulation is impaired. Usually the 5 mA programming current is sufficient; however, worst case minimum load for commercial grade parts requires a minimum load of 10 mA. The minimum load current can be compared to the quiescent current of standard regulators.



†Solid tantalum

\*Discharges C1 if output is shorted to ground

FIGURE 2. Adjustable Regulator with Improved Ripple Rejection

## OVERLOAD PROTECTION CIRCUITRY

An important advancement in the LM117 is improved current limit circuitry. Current limit is set internally at about 2.2A and the current limit remains constant with temperature. Older devices such as the LM309 or LM7800 regulators use the turn-on of an emitter-base junction of a transistor to set the current limit. This causes current limit to typically change by a factor of 2 over a  $-55^{\circ}\text{C}$  to  $+150^{\circ}\text{C}$  temperature range. Further, to insure adequate output current at  $150^{\circ}\text{C}$  the current limit is relatively high at  $25^{\circ}\text{C}$ , which can cause problems by overloading the input supply.

Also included is safe-area protection for the pass transistor to decrease the current limit as input-to-output voltage differential increases. The safe area protection circuit in the LM117 allows full output current at 15V differential and does not allow the current limit to drop to zero at high input-to-output differential voltages, thus preventing start up problems with high input voltages. *Figure 3* compares the current limit of the LM117 to an LM340 regulator.

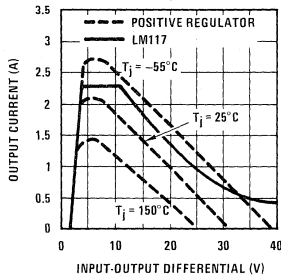


FIGURE 3. Comparison of LM117 Current Limit with Older Positive Regulator

Thermal overload protection, included on the chip, turns the regulator OFF when the chip temperature exceeds about  $170^{\circ}\text{C}$ , preventing destruction due to excessive heating. Previously, the thermal limit circuitry required about 7V to operate. The LM117 has a new design that is operative down to about 2V. Further, the thermal limit and current limit circuitry in the LM117 are functional, even if the adjustment terminal should be accidentally disconnected.

## OPERATING THE LM117

The basic regulator connection for the LM117, as shown in *Figure 2*, only requires the addition of 2 resistors and a standard input bypass capacitor. Resistor R2 sets the output voltage while R1 provides the 5 mA programming current. The 2 capacitors on the adjustment and output terminals are optional for improved performance.


Bypassing the adjustment terminal to ground improves ripple rejection. This bypass capacitor prevents ripple from being amplified as the output voltage is increased. With a  $10\ \mu\text{F}$  bypass capacitor, 80 dB ripple rejection is obtainable at any output level. Increases over  $10\ \mu\text{F}$  do not appreciably improve the ripple rejection at 120 Hz. If a bypass capacitor is used, it is sometimes necessary

to include protection diodes as discussed later, to prevent the capacitor from discharging through internal low current paths in the LM117 and damaging the device.

Although the LM117 is stable with no output capacitors, like any feedback circuit, certain values of external capacitance can cause excessive ringing. This occurs with values between 500 pF and 5000 pF. A  $1\ \mu\text{F}$  solid tantalum (or  $25\ \mu\text{F}$  aluminum electrolytic) on the output swamps this effect and insures stability. When external capacitors are used with any IC regulator, it is sometimes necessary to add protection diodes to prevent the capacitors from discharging through low current points into the regulator. Most  $10\ \mu\text{F}$  capacitors have low enough internal series resistance to deliver 20A spikes when shorted. Although the surge is short, there is enough energy to damage parts of the IC.

When an output capacitor is connected to a regulator and the input is shorted, the output capacitor will discharge into the output of the regulator. The discharge current depends on the value of the capacitor, the output voltage of the regulator, and the rate of decrease of  $V_{IN}$ . In the LM117, this discharge path is through a large junction that is able to sustain a 20A surge with no problem. This is not true of other types of positive regulators. For output capacitors of  $25\ \mu\text{F}$  or less, there is no need to use diodes.

The bypass capacitor on the adjustment terminal (C2) can discharge through a low current junction. Discharge occurs when either the input or output is shorted. Internal to the LM117 is a  $50\ \Omega$  resistor which limits the peak discharge current. No protection is needed for output voltages of 25V and less than  $10\ \mu\text{F}$  capacitance. *Figure 4* shows an LM117 with protection diodes included for use with outputs greater than 25V and high values of output capacitance.

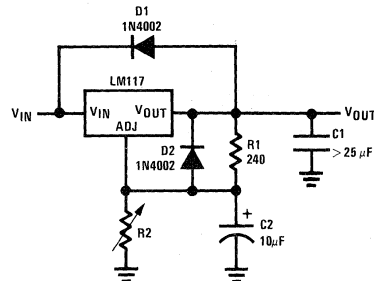

$$V_{OUT} = 1.25V \left( 1 + \frac{R2}{R1} \right) + R2 \cdot I_{ADJ}$$

D1 protects against C1 (input shorts)

D2 protects against C2 (output shorts)

FIGURE 4. Regulator with Protection Diodes Against Capacitor Discharge

Some care should be taken in making connection to the LM117 to achieve the best load regulation. Series resistance between the output of the regulator and programming resistor R1 should be minimized. Any voltage drop due to load current through this series resistance appears as a change in the reference voltage and degrades regulation. If possible, 2 wires should be connected to the output—1 for load current and 1 for

resistor R1. The ground of R2 can be returned near the ground of the load to provide remote sensing and improve load regulation.

## APPLICATIONS

Figure 5 shows a 0V to 25V general purpose lab supply. Operation of the LM317 down to 0V output requires the addition of a negative supply so that the adjustment terminal can be driven to  $-1.2V$ . An LM329 6.9V reference is used to provide a regulated  $-1.2V$  reference to the bottom of adjustment pot R2. The LM129 is an IC zener which has exceptionally low dynamic impedance so the negative supply need not be well regulated. Note that a 10 mA programming current is used since lab supplies are often used with no-load, and the LM317 requires a worst-case minimum load of 10 mA.

The 1.2V minimum output of the LM117 makes it easy to design power supplies with electrical shut-down. At 1.2V, most circuits draw only a small fraction of their normal operating current. In Figure 6 a TTL input signal causes Q1 to ground the adjustment terminal decreasing the output to 1.2V. If true zero output is desired, the adjustment can be driven to  $-1.2V$ ; however, this does require a separate negative supply.

When fixed output voltage regulators are used as on-card regulator for multiple cards, the normal output voltage tolerance of  $\pm 5\%$  between regulators can cause as much as 10% difference in operating voltage between cards.

This can cause operating speed differences in digital circuitry, interfacing problems or decrease noise margins.

Figure 7 shows a method of adjusting multiple on-card regulators so that all outputs track within  $\pm 100$  mV. The adjustment terminals of all devices are tied together and a single divider is used to set the outputs. Programming current is set at 10 mA to minimize the effects of the  $50 \mu A$  biasing current of the regulators and should further be increased if many LM117's are used. Diodes connected across each regulator insure that all outputs will decrease if 1 regulator is shorted.

Two terminal current regulators can be made with fixed-output regulators; however, their high output voltage and high quiescent current limit their accuracy. With the LM117 as shown in Figure 8, a high performance current source useful from 10 mA to 1.5A can be made. Current regulation is typically 0.01%/V even at low currents since the quiescent current does not cause an error. Minimum operating voltage is less than 4V, so it is also useful as an in-line adjustable current limiter for protection of other circuitry.

Low cost adjustable switching regulators can be made using an LM317 as the control element. Figure 9 shows the simplest configuration. A power PNP is used as the switch driving an L-C filter. Positive feedback for hysteresis is applied to the LM317 through R6. When the PNP switches, a small square wave is generated across R5. This is level shifted and applied to the adjustment terminal of the regulator by R4 and C2, causing it to

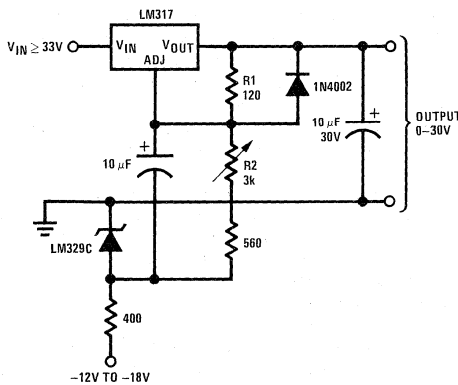


FIGURE 5. General Purpose 0-30V Power Supply

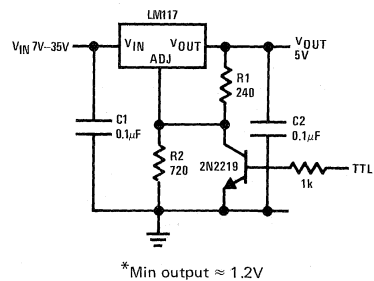


FIGURE 6. 5V Logic Regulator with Electronic Shutdown\*



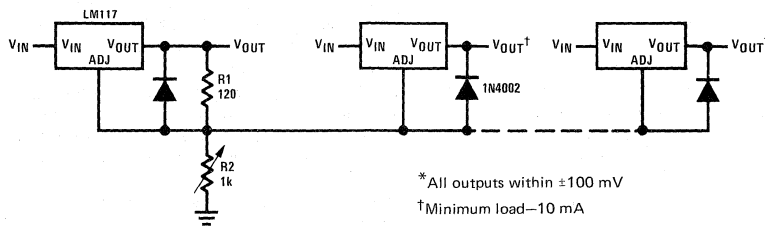


FIGURE 7. Adjusting Multiple On-Card Regulators with Single Control\*

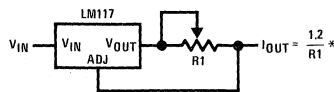

$$*0.8\Omega \leq R1 \leq 120\Omega$$

FIGURE 8. Precision Current Limiter

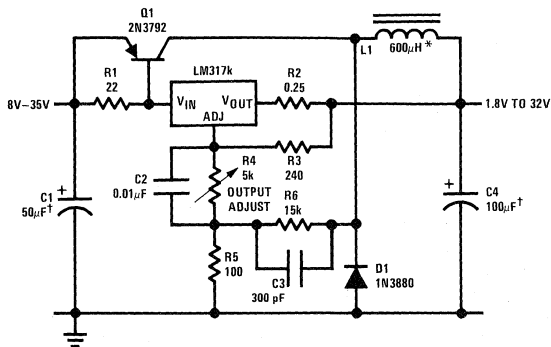

†Solid tantalum

\*Core—Arnold A-254168-2 60 turns

FIGURE 9. Low Cost 3A Switching Regulator

switch ON or OFF. Negative feedback is taken from the output through R3, making the circuit oscillate. Capacitor C3 acts as a speed-up, increasing switching speed, while R2 limits the peak drive current to Q1.

The circuit in *Figure 9* provides no protection for Q1 in case of an overload. A blow-out proof switching regulator is shown in *Figure 10*. The PNP transistor has been replaced by a PNP-NPN combination with LM395's used as the NPN transistors. The LM395 is an IC which acts as an NPN transistor with overload protection. Included on the LM395 is current limiting, safe-area protection and thermal overload protection making the device virtually immune to any type of overload.

Efficiency for the regulators ranges from 65% to 85%, depending on output voltage. At low output voltages, fixed power losses are a greater percentage of the total output power so efficiency is lowest. Operating frequency is about 30 kHz and ripple is about 150 mV, depending upon input voltage. Load regulation is about 50 mV and line regulation about 1% for a 10V input change.


One of the more unique applications for these switching regulators is as a tracking pre-regulator. The only DC connection to ground on either regulator is through the 100Ω resistor (R5 or R8) that sets the hysteresis. Instead of tying this resistor to ground, it can be connected to the output of a linear regulator so that the switching regulator maintains a constant input-to-output differential on the linear regulator. The switching regulator would typically be set to hold the input voltage to the linear regulator about 3V higher than the output.

Battery charging is another application uniquely suited for the LM117. Since battery voltage is dependent on electrochemical reactions, the charger must be designed specifically for the battery type and number of cells. Ni-Cads are easily charged with the constant current sources shown previously. For float chargers on lead-acid type batteries all that is necessary is to set the output of the LM117 at the float voltage and connect it to the battery. An adjustable regulator is mandatory since, for long battery life the float voltage must be precisely controlled. The output voltage temperature coefficient can be matched to the battery by inserting diodes in series with the adjustment resistor for the regulator and coupling the diodes to the battery.

A high performance charger for gelled electrolyte lead-acid batteries is shown in *Figure 11*. This charger is designed to quickly recharge a battery and shut off at full charge.

Initially, the charging current is limited to 2A by the internal current limit of the LM117. As the battery voltage rises, current to the battery decreases and when the current has decreased to 150 mA, the charger switches to a lower float voltage preventing overcharge. With a discharged battery, the start switch is not needed since the charger will start by itself; however, it is included to allow topping off even slightly discharged batteries.

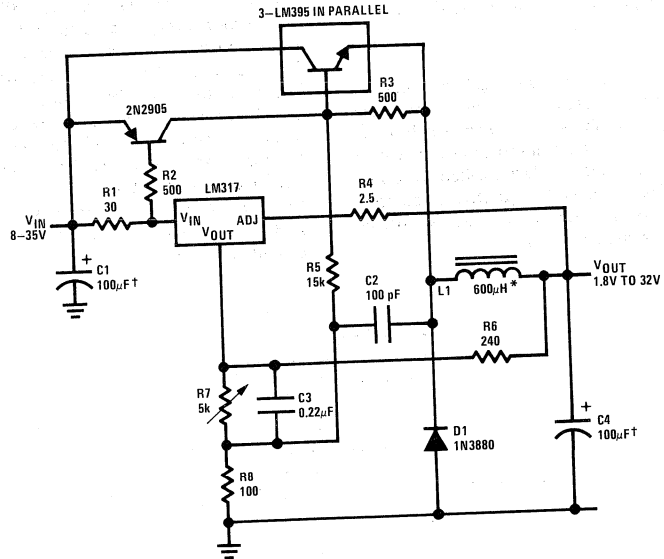When the start switch is pushed, the output of the charger goes to 14.5V set by R1, R2 and R3. Output current is sensed across R6 and compared to a fraction of the 1.2V reference (across R2) by an LM301A op



†Solid tantalum

\*Core—Arnold A-254168-2 60 turns

FIGURE 10. 4A Switching Regulator with Overload Protection

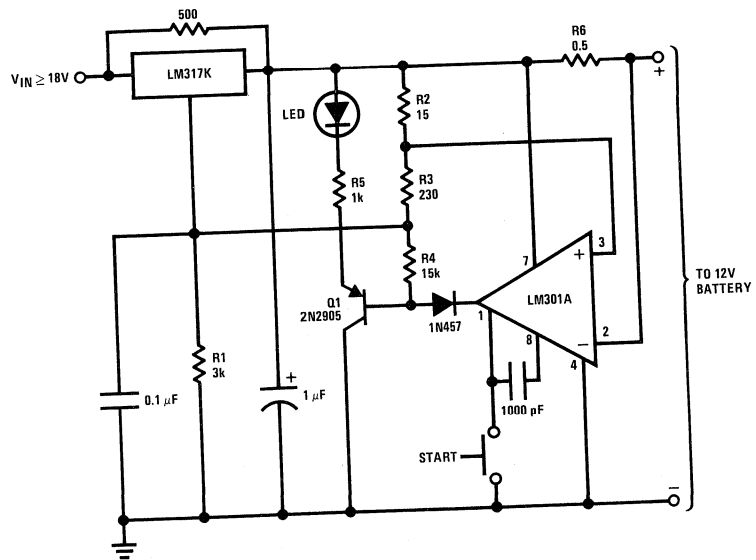


FIGURE 11. 12V Battery Charger

amp. As the voltage across R6 decreases below the voltage across R2, the output of the LM101A goes low shunting R1 with R4. This decreases the output voltage from 14.5V to about 12.5V terminating the charging. Transistor Q1 then lights the LED as a visual indication of full charge.

The LM117 can even be used as a peak clipping AC voltage regulator. Two regulators are used, 1 for each polarity of the input as shown in *Figure 12*. Internal to the LM117 is a diode from input-to-output which conducts the current around the device when the opposite regulator is active. Since each regulator is operating independently, the positive and negative peaks must be set separately for a symmetrical output.

## CONCLUSIONS

A new IC power voltage regulator has been developed which is significantly more versatile than older devices. The output voltage is adjustable, in addition to improved regulation specifications. Further, reliability is increased in 2 fashions. Overload protection circuitry has been improved to make the device less susceptible to fault conditions and under short circuit conditions, minimum stress is transmitted back to the input power supply. Secondly, the device is 100% burned-in under short circuit conditions at the time of manufacture. Finally, the LM117 is made with a standard IC production process and packaged in a standard TO-3 power package, keeping costs low.

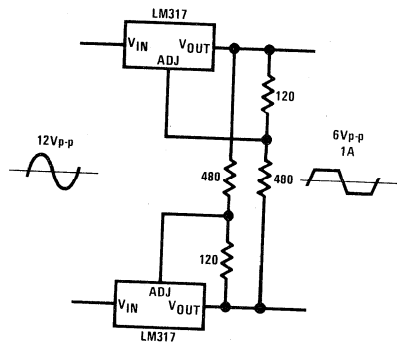


FIGURE 12. AC Voltage Regulator



# Improving Power Supply Reliability with IC Power Regulators

National Semiconductor  
Application Note 182  
Robert C. Dobkin  
April 1977



Three-terminal IC power regulators include on-chip overload protection against virtually any normal fault condition. Current limiting protects against short circuits fusing the aluminum interconnects on the chip. Safe-area protection decreases the available output current at high input voltages to insure that the internal power transistor operates within its safe area. Finally, thermal overload protection turns off the regulator at chip temperatures of about 170°C, preventing destruction due to excessive heating. Even though the IC is fully protected against normal overloads, careful design must be used to insure reliable operation in the system.

## SHORT CIRCUITS CAN OVERLOAD THE INPUT

The IC is protected against short circuits, but the value of the on-chip current limit can overload the input rectifiers or transformer. The on-chip current limit is usually set by the manufacturer so that with worst-case production variations and operating temperature the device will still provide rated output current. Older types of regulators, such as the LM309, LM340 or LM7800 can have current limits of 3 times their rated output current.

The current limit circuitry in these devices uses the turn-on voltage of an emitter-base junction of a transistor to set the current limit. The temperature coefficient of this junction combined with the temperature coefficient of the internal resistors gives the current limit a  $-0.5/^\circ\text{C}$  temperature coefficient. Since devices must operate and provide rated current at 150°C, the 25°C current limit is 120% higher than typical. Production variations will add another  $\pm 20\%$  to initial current limit tolerance so a typical 1A part may have a 3A current limit at 25°C. This magnitude of overload current can blow the input transformer or rectifiers if not considered in the initial design—even though it does not damage the IC.

One way around this problem (other than fuses) is by the use of minimum size heat sinks. The heat sink is designed for only normal operation. Under overload conditions, the device (and heat sink) are allowed to heat up to the thermal shut-down temperature. When the device shuts down, loading on the input is reduced.

Newer regulators have improved current limiting circuitry. Devices like the LM117 adjustable regulator, LM123 3A, 5V logic regulator or the LM120 negative regulators have a relatively temperature-stable current limit. Typically these devices hold the current limit within  $\pm 10\%$  over the full  $-55^\circ\text{C}$  to  $+150^\circ\text{C}$  operating range. A device rated for 1.5A output will typically have a 2.2A current limit, greatly easing the problem of input overloads.

Many of the older IC regulators can oscillate when in current limit. This does not hurt the regulator and is mostly dependent upon input bypassing capacitors. Since there is a large variability between regulator types and manufacturers, there is no single solution to eliminating oscillations. Generally, if oscillations cause other circuit problems, either a solid tantalum input capacitor or a solid tantalum in series with 5Ω to 10Ω will cure the problem. If one doesn't work, try the other.

Start-up problems can occur from the current limit circuitry too. At high input-output differentials, the current limit is decreased by the safe-area protection. In most regulators the decrease is linear, and at input-output voltages of about 30V the output current can decrease to zero. Normally this causes no problem since, when the regulator is initially powered, the output increases as the input increases. If such a regulator is running with, for example, 30V input and 15V output and the output is momentarily shorted, the input-output differential increases to 30V and available output current is zero. Then the output of the regulator stays at zero even if the short is removed. Of course, if the input is turned OFF, then ON, the regulator will come up to operating voltage again. The LM117 is the only regulator which is designed with a new safe-area protection circuit so output current does not decrease to zero, even at 40V differential.

This type of start-up problem is particularly load dependent. Loads to a separate negative supply or constant-current devices are among the worst. Another, usually overlooked, load is pilot lights. Incandescent bulbs draw 8 times as much current when cold as when operating. This severely adds to the load on a regulator,

and may prevent turn-on. About the only solutions are to use an LM117 type device, or bypass the regulator with a resistor from input to output to supply some start-up current to the load. Resistor bypassing will not degrade regulation if, under worst-case conditions of maximum input voltage and minimum load current, the regulator is still delivering output current rather than absorbing current from the resistor. *Figure 1* shows the output current of several different regulators as a function of output voltage and temperature.

When a positive regulator (except for the LM117) is loaded to a negative supply, the problem of start-up can be doubly bad. First, there is the problem of the safe-area protection as mentioned earlier. Secondly, the internal circuitry cannot supply much output current when the output pin is driven more negative than the ground pin of the regulator. Even with low input voltages, some positive regulators will not start when loaded by 50 mA to a negative supply. Clamping the output to ground with a germanium or Schottky diode usually solves this problem. Negative regulators, because of different internal circuitry, do not suffer from this problem.

#### DIODES PROTECT AGAINST CAPACITOR DISCHARGE

It is well recognized that improper connections to a 3-terminal regulator will cause its destruction. Wrong polarity inputs or driving current into the output (such as a short between a 5V and 15V supply) can force high currents through small area junctions in the IC, destroying them. However, improper polarities can be applied accidentally under many normal operating conditions, and the transient condition is often gone before it is recognized.

Perhaps the most likely sources of transients are external capacitors used with regulators. *Figure 2* shows the discharge path for different capacitors used with a positive regulator. Input capacitance, C1, will not cause a problem under any conditions. Capacitance on the ground pin (or adjustment pin in the case of the LM117) can discharge through 2 paths which have low current junctions.

If the output is shorted, C2 will discharge through the ground pin, possibly damaging the regulator. A reverse-biased diode, D2, diverts the current around the regulator, protecting it. If the input is shorted, C3 can discharge through the output pin, again damaging the regulator. Diode D1 protects against C3, preventing damage. Also, with both D1 and D2 in the circuit, when the input is shorted, C2 is discharged through both diodes, rather than the ground pin.

In general, these protective diodes are a good idea on all positive regulators. At higher output voltages, they become more important since the energy stored in the capacitors is larger. With negative regulators and the LM117, there is an internal diode in parallel with D1 from output-to-input, eliminating the need for an external diode if the output capacitor is less than 25  $\mu$ F.

Another transient condition which has been shown to cause problems is momentary loss of the ground connection. This charges the output capacitor to the unregulated input voltage minus a 1–2V drop across the regulator. If the ground is then connected, the output capacitor, C3, discharges through the regulator output to the ground pin, destroying it. In most cases, this problem occurs when a regulator (or card) is plugged into a powered system and the input pin is connected

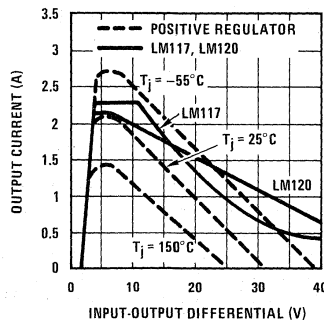


FIGURE 1. Comparison of LM117 Current Limit with Older Positive Regulator

before the ground. Control of the connector configuration, such as using 2 ground pins to insure ground is connected first, is the best way of preventing this problem. Electrical protection is cumbersome. About the only way to protect the regulator electrically is to make D2 a power zener 1V to 2V above the regulator voltage and include  $10\Omega$  to  $50\Omega$  in the ground lead to limit the current.

#### LOW OPERATING TEMPERATURE INCREASES LIFE

Like any semiconductor circuit, lower operating temperature improves reliability. Operating life decreases at high junction temperatures. Although many regulators are rated to meet specifications at  $150^{\circ}\text{C}$ , it is not a good idea to design for continuous operation at that temperature. A reasonable maximum operating temperature would be  $100^{\circ}\text{C}$  for epoxy packaged devices and  $125^{\circ}\text{C}$  for hermetically sealed (TO-3) devices. Of course, the lower the better, and decreasing the above temperatures by  $25^{\circ}\text{C}$  for normal operation is still reasonable.

Another benefit of lowered operating temperatures is improved power cycle life for low cost soft soldered packages. Many of today's power devices (transistors included) are assembled using a TO-220 or TO-3 aluminum soft solder system. With temperature excursions, the solder work-hardens and with enough cycles the solder will ultimately fail. The larger the temperature change, the sooner failure will occur. Failures can start at about 5000 cycles with a  $100^{\circ}\text{C}$  temperature excursion. This necessitates, for example, either a large heat sink or a regulator assembled with a hard solder, such as steel packages, for equipment that is continuously cycled ON and OFF.

#### THERMAL LIMITING GIVES ABSOLUTE PROTECTION

Without thermal overload protection, the other protection circuitry will only protect against short term overloads. With thermal limiting, a regulator is not destroyed by long time short circuits, overloads at high temperatures or inadequate heat sinking. In fact, this overload protection makes the IC regulator tolerant of virtually any abuse, with the possible exception of high-voltage transients, which are usually filtered by the capacitors in most power supplies.

One problem with thermal limiting is testing. With a 3-terminal regulator, short-circuit protection and safe-area protection are easily measured electrically. For thermal limiting to operate properly, the electrical circuitry on the IC must function and the IC chip must be well die-attached to the package so there are no hot spots. About the only way to insure that thermal limiting works is to power the regulator, short the output, and let it cook. If the regulator still works after 5 minutes (or more) the thermal limit has protected the regulator.

This type of testing is time consuming and expensive for the manufacturer so it is not always done. Some regulators, such as the LM117, LM137, LM120 and LM123, do receive an electrical burn-in in thermal shutdown as part of their testing. This insures that the thermal limiting works as well as reducing infant mortality. If it is probable that a power supply will have overloads which cause the IC to thermally limit, testing the regulator is in order.

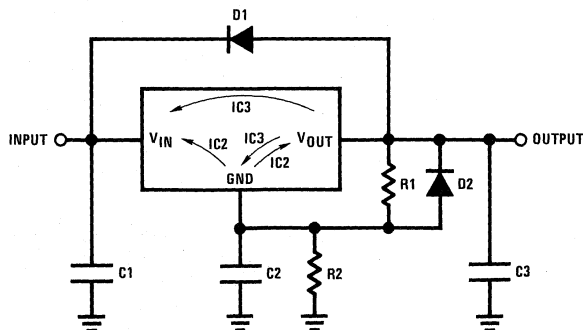


FIGURE 2. Positive Regulator with Diode Protection Against Transient Capacitor Discharge



## References for A/D Converters

National Semiconductor  
 Application Note 184  
 Robert C. Dobkin  
 July 1977



Interfacing between digital and analog signals is becoming increasingly important with the proliferation of digital signal processing. System accuracy is often limited by the accuracy of the converter and a limitation of the converter is the voltage reference. Design can be difficult if the reference is external.

The accuracy of any converter is limited by the temperature drift or long term drift of the voltage reference, even if conversion linearity is perfect. Assuming that the voltage reference is allowed to add 1/2 least significant bit error (LSB) to the converter, it is surprising how good the reference must be when even small temperature excursions are considered. When temperature changes are large, the reference design is a major problem. Table I shows the reference requirements for different converters while Table II shows how the same problems exist with digital panel meters.

The voltage reference circuitry is required to do several functions to maintain a stable output. First, input power supply changes must be rejected by the reference circuitry. Secondly, the zener used in the reference must be biased properly, while other parts of circuitry scale the typical zener voltage and provides a low impedance output. Finally, the reference circuitry must reject ambient temperature changes so that the temperature drift of the reference circuitry plus the drift of the zener does not exceed the desired drift limit.

While zener temperature coefficient is obviously critical to reference performance, other sources of drift can easily add as much error as zener — even in voltage references with modest performance of 20 ppm/°C temperature drift. Zener drift and op amp drift add directly to the drift error, while resistor error is only a function of how well the scaling resistors track. Resistors which have a high TC can be used if they track.

For a 10V output with a 6.9V zener, the drift contribution of resistor mistracking is about 0.4 since the gain is 1.4. The range of temperature coefficient errors for different components used to make a 10V reference from a 6.9V zener are shown in Table III. Another potential source of error, input supply variations, are negligible if the input is 1% regulated, and the resistor feeding the zener is stable to 1%.

Less frequently specified sources of error in voltage reference zeners are hysteresis and stress sensitivity. Stress on either a zener-diode junction or the series-temperature-compensating junction will cause voltage shifts. The axial leads on discrete devices can transmit stress from outside the package to the junction, causing 1 mV to 5 mV shifts.

Temperature cycling the discrete zener can also induce non-reversible changes in zener voltage. If a zener is heated from 25°C to 100°C and then back to 25°C, the zener voltage may not return to its original value. This is because the temperature cycle has permanently changed the stress in the die, changing the voltage. This effect can be as high as 5 mV in some diodes and may be cumulative with many temperature cycles. The new planar IC zeners, such as the LM199 (temperature stabilized) or the LM129 are insensitive to stress and show only about 50 μV of hysteresis for a 150°C temperature cycle since the package does not stress the silicon chip.

### DESIGNING THE REFERENCE

If moderate temperature performance such as 20 ppm/°C is all that is needed, 2 different approaches can be used in the reference design. In the first, the temperature drift error is split equally between the zener and the amplifier or scaling resistors. This requires a moderately low drift zener and op amp with 10 ppm resistors.

TABLE I. Maximum Allowable Reference Drift for 1/2 Least Significant Bits Error of Binary Coded Converter

TEMP CHANGE	BITS					
	6	8	10	12		14
25°C	310	80	20	5	1.25	ppm/°C
50°C	160	40	10	2.5	0.6	ppm/°C
100°C	80	20	5	1.2	0.3	ppm/°C
125°C	63	16	3	1	0.2	ppm/°C

TABLE II. Maximum Allowable Reference Drift for 1/2 Digit Error of Digital Meters

TEMP CHANGE	DIGITS								
	2	2 1/2	3	3 1/2	4	4 1/2	5	5 1/2	
25°C	200	100	20	10	2	1	0.2	0.1	ppm/°C
5°C			100	50	10	5	1	0.5	ppm/°C

\*0.01%/°C = 100 ppm/°C, 0.001%/°C = 10 ppm/°C, 0.0001%/°C = 1 ppm/°C

TABLE III. Drift Error Contribution From Reference Components for a 10V Reference

DEVICE	ERROR	10V OUTPUT DRIFT
<b>Zener</b>		
<b>Zener Drift</b>		
LM199A	0.5 ppm/°C	0.5 ppm/°C
LM199, LM399A	1 ppm/°C	1 ppm/°C
LM399	2 ppm/°C	2 ppm/°C
1N829, LM3999	5 ppm/°C	5 ppm/°C
LM129, 1N823A, 1N827A, LM329A	10–50 ppm/°C	10–50 ppm/°C
LM329, 1N821, 1N825	20–100 ppm/°C	20–100 ppm/°C
<b>Op Amp</b>		
<b>Offset Voltage Drift</b>		
LM725, LH0044, LM121	1 μV/°C	0.15 ppm/°C
LM108A, LM208A, LM308A	5 μV/°C	0.7 ppm/°C
LM741, LM101A	15 μV/°C	2 ppm/°C
LM741C, LM301A, LM308	30 μV/°C	4 ppm/°C
<b>Resistors</b>		
<b>Resistance Ratio Drift</b>		
1% (RN55D)	50–100 ppm	20–40 ppm/°C
0.1% (Wirewound)	5–10	2–4 ppm
Tracking 1 ppm Film or Wirewound	—	0.4 ppm/°C

The second approach uses a very low drift zener and allows the buffer amplifier or scaling resistor to cause most of the drift error. This type of design is now made economical by the availability of low cost temperature stabilized IC zeners with virtually no TC. Further, the temperature coefficient of this reference is easily upgraded, if necessary. The 2 reference circuits are shown in *Figure 1a* and *Figure 1b*.

In *Figure 1a*, an LM308 op amp is used to increase the typical zener output to 10V while adding a worst-case drift of 4 ppm/°C to the 10 ppm/°C of the zener. Resistors R3 and R4 should track to better than 10 ppm bringing the total error so far to 18 ppm. Since the output must be adjusted to eliminate the initial zener tolerance, a pot, R5 and R2 have been added. The loading on the pot by R2 is small, and there is no tracking requirement between the pot and R2. It is necessary for R2 to track R3 and R4 within 50 ppm.

In *Figure 1b*, a low drift reference and op amp are used to give a total drift, exclusive of resistors of 3 ppm/°C. Now the resistor tracking requirement is relaxed to about 50 ppm, allowing ordinary 1% resistors to be used. The circuit in *Figure 1b* is modified easily for applications requiring 3 ppm/°C to 5 ppm/°C overall drift by tightening the tracking of the resistors. For more accurate applications, the Kelvin sensing for both output and ground should be used. For even lower drifts, substituting a 1 μV/°C op amp, 1 ppm tracking resistors and an LM199A zener, overall drifts of 1 ppm/°C can be achieved. In both of the circuits, it is important to remember that the tracking of resistors can, at worst-case, be twice temperature drift of either resistance.

In both circuits, the zener is biased by a single resistor from the supply, rather than from the reference output. This eliminates possible start-up problems and, because of the 1Ω dynamic impedance of the IC zeners, only


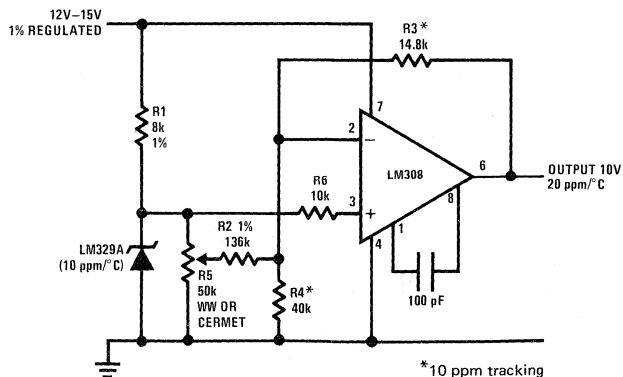


FIGURE 1a. 10V, 20 ppm Reference Using a Low Cost Zener and Low Drift Resistors

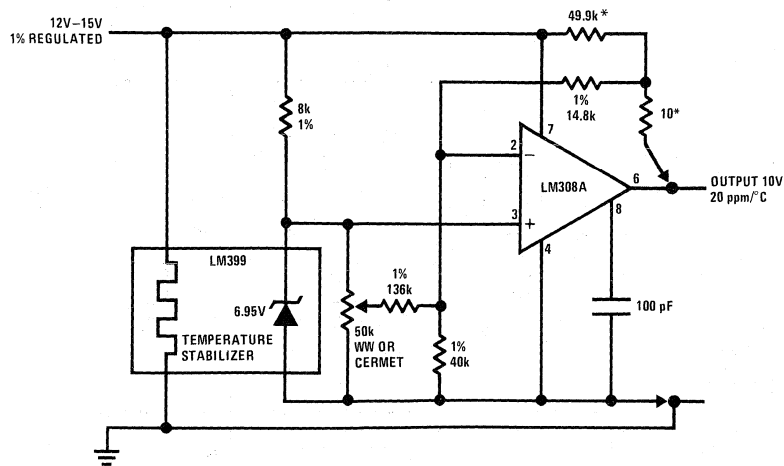

\*Optional—improves line regulation

FIGURE 1b. 10V Reference has Low Drift Reference and Standard 1% Resistors. Kelvin Sensing is Shown with Compensation for Line Changes.

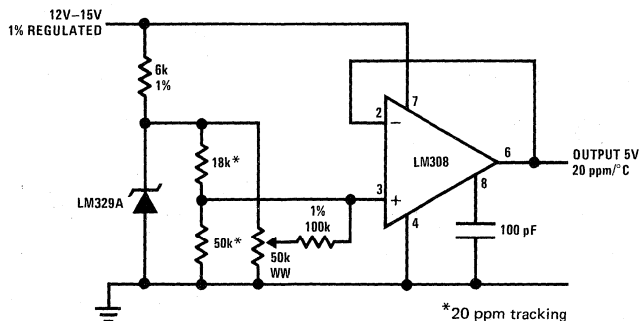


FIGURE 2. Low Voltage Reference

adds about  $20 \mu\text{V}$  of error. Compensation for input changes is shown in Figure 1b. Conventional zeners do not allow this biasing. A conventional 5 ppm reference such as the 1N829 has a dynamic impedance of about  $15\Omega$ . If it is biased from a resistor from a 1% regulated 15V supply, the operating current can change by 1.7% or  $127 \mu\text{A}$ . This will shift the zener voltage by 1.9 mV or 60 ppm. With the IC zeners operating at 1 mA, a 1% shift in the supply will change the reference by  $20 \mu\text{V}$  or 3 ppm. Further, power dissipation in the IC is only 7 mW, giving low warm-up drift compared to 7.5 mA zeners. The biasing resistor for the IC zener need not be any better than an ordinary 1% resistor since performance is independent of current.

When output voltages less than the zener voltage are desired, the IC zeners significantly simplify circuit design since no auxiliary regulator is needed for biasing. Figure 2 shows a 5V reference circuit for use with a 15V input.

In this case, zener drift contributes proportionally to the output drift while op amp offset drift adds a greater rate. With the 10V reference,  $15 \mu\text{V}/^\circ\text{C}$  from the op amp contributed  $2 \text{ ppm}/^\circ\text{C}$  drift, but for the 5V reference,  $15 \mu\text{V}/^\circ\text{C}$  adds  $3 \text{ ppm}/^\circ\text{C}$ . This makes op amp choice more important as the output voltage is lowered. Of course, if a high output impedance is tolerable, the op amp can be eliminated.

#### APPROACHING THE ULTIMATE DRIFT

To obtain the lowest possible drifts, temperature coefficient trimming is necessary. With discrete zeners, the operating current can sometimes be trimmed to change the TC of the reference; however, the temperature coefficient is not always linear or predictable. With the new IC zeners, TC is independent of operating current so trimming must be done elsewhere in the circuit. The lowest drift components should be used since

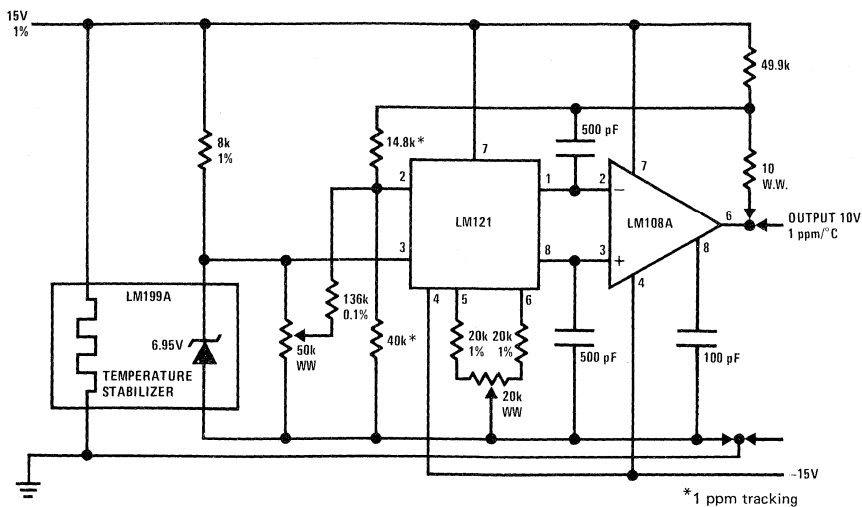


FIGURE 3. Ultra Low Drift Reference

trimming can only remove a linear component of drift. High TC devices can have a highly non-linear drift, making trimming difficult.

Figure 3 shows a circuit suitable for trimming. An LM199A reference with  $0.5 \text{ ppm}/^\circ\text{C}$  drift is used with a 121/108 op amp. Resistors should be 1 ppm tracking to give overall untrimmed drifts of about 0.9 ppm. The 121/108 is a low drift amplifier combination where drift is predictably proportional to offset voltage. An offset can be set for the 108/121 combination to cancel the measured drift with 1 pass calibration.

Trimming procedure is as follows: the zener is disconnected and the input of the op amp grounded. Then the offset of the op amp is nulled out to zero. Reconnecting the zener, the output is adjusted to precisely 10V. A temperature run is made and the drift noted. The op amp will drift  $3.6 \mu\text{V}/^\circ\text{C}$  for every 1 mV of offset, so for every  $5 \mu\text{V}/^\circ\text{C}$  drift at the output, the offset of the op amp is adjusted 1 mV (1.4 mV measured at the output) in the opposite direction. The output is readjusted to 10V and the drift checked.

Although this trimming scheme was chosen since only a single adjustment is usually required, compensation is not always perfect. Hysteresis effects can appear in resistors or op amps as well as zeners. Best results can be obtained by cycling the circuit to temperature a few times before taking data to relieve assembly stresses on the components. Also, oven testing can sometimes cause thermal gradients across circuits, giving  $50 \mu\text{V}$  to  $100 \mu\text{V}$  of error. However, with careful layout and trimming, overall reference drifts of  $0.1 \text{ ppm}/^\circ\text{C}$  to  $0.2 \text{ ppm}/^\circ\text{C}$  can be achieved.

There are 2 other possible problem areas to be considered before final layout. Good single point grounding is important. Traces on a PC board can easily have  $0.1\Omega$  and only 10 mA will cause a 1 mV shift. Also, since these references are close to high-speed digital circuitry, shielding may be necessary to prevent pick-up at the inputs of the op amp. Transient response to pick-up or rapid loading changes can sometimes be improved by a large capacitor ( $1 \mu\text{F}$ – $10 \mu\text{F}$ ) directly on the op amp output; but this will depend on the stability of the op amp.



# Single Chip Data Acquisition System Simplifies Analog-to-Digital Conversion

National Semiconductor  
Application Note 193  
Jake Buurma  
July 1977



Until recently, building an analog data acquisition system required a hardy cross-breed of both analog design and digital design. Now National Semiconductor has simplified the design problem of a data acquisition system with the introduction of the ADC0816 (MM74C948). This CMOS device incorporates many of the standard features of a data acquisition system onto a single chip. Included on-chip is an 8-bit analog-to-digital converter with bus oriented outputs, a 16-channel expandable multiplexer for external signal conditioning, and logic control for systems interface. This chip marks the advent of a new generation in A/D converters, bringing versatility, performance, and economy using a technology ideally suited to data acquisition systems.

structure of a data acquisition system while relieving the user from multichip interface and compatibility problems. A wide range of functional options allows extremely versatile operation of the device in a wide range of applications.

The ADC0816 uses National's low voltage, metal gate technology. The device operates from a single +5 volt supply and features a 16-channel multiplexer with address input latches, latched TRI-STATE outputs and a true eight-bit-accurate analog-to-digital converter. It consumes only 20 milliwatts of power. Total conversion time of an analog signal is 100 microseconds. By using a patented A/D conversion technique the converter is guaranteed to have no missing codes and to be monotonic. The internal chopper stabilized comparator is the key element in minimizing both long term drift and temperature coefficients of other error terms.

Figure 1 shows a block diagram of the functions provided within a single package. The chip duplicates the classical

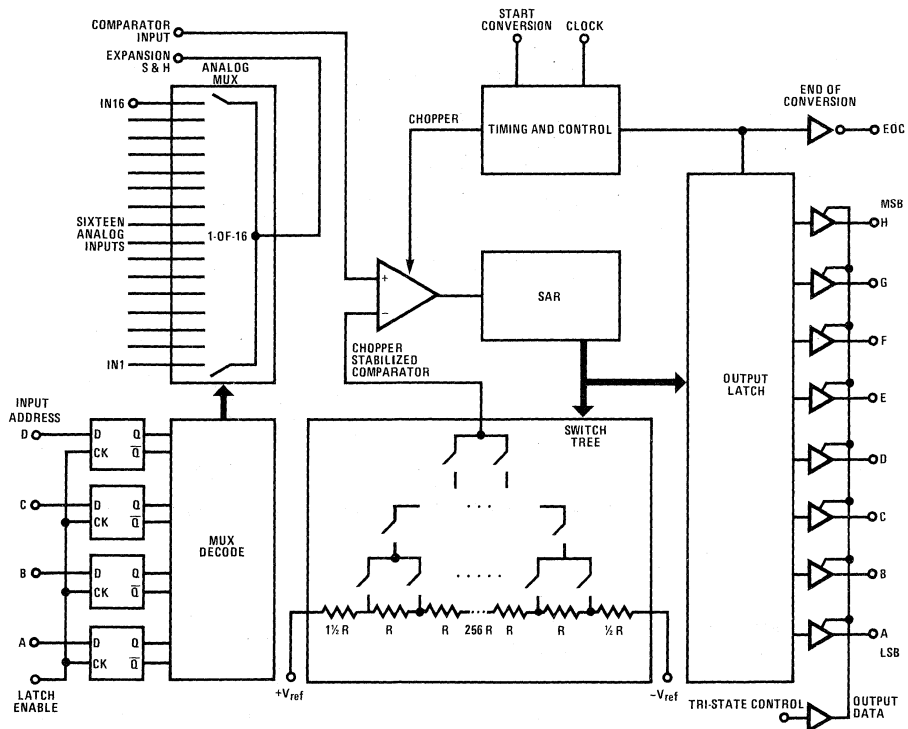


Figure 1. ADC0816/MM74C948 Block Diagram

Figure 2 shows a typical application employing the ADC0816 for use in a microprocessor-based environmental control system. In this system the microprocessor can select a channel, monitor a particular sensor reading, convert that signal to a digital word, and make a system decision based upon that input. Many other areas of process control, machine control, or multi-input analog system can utilize this basic configuration.

### THE CONVERTER

The heart of this single-chip data acquisition system is its 8-bit analog-to-digital converter. The converter is designed to give fast, accurate, and repeatable conversions over a wide range of temperatures. The converter is partitioned into three major sections: the 256R ladder network, the successive approximation register, and the comparator.

The 256R ladder network approach was chosen over the conventional R/2R ladder because of its inherent monotonicity. Monotonicity is particularly important in closed-loop feedback control systems. A non-monotonic relationship can cause oscillations that could be catastrophic. Additionally, the 256R network does not cause load variations on the reference voltage.

Figure 3 shows a comparison of the output characteristic for the two approaches with a variation in the ladder resistance. In the 256R approach with unequal or shorted resistors the slope of the output transfer function cannot be different from the slope of the analog input. For the R/2R ladder network, mismatches in the resistor values can cause the slope of the output digital code to be different from the analog input signal.

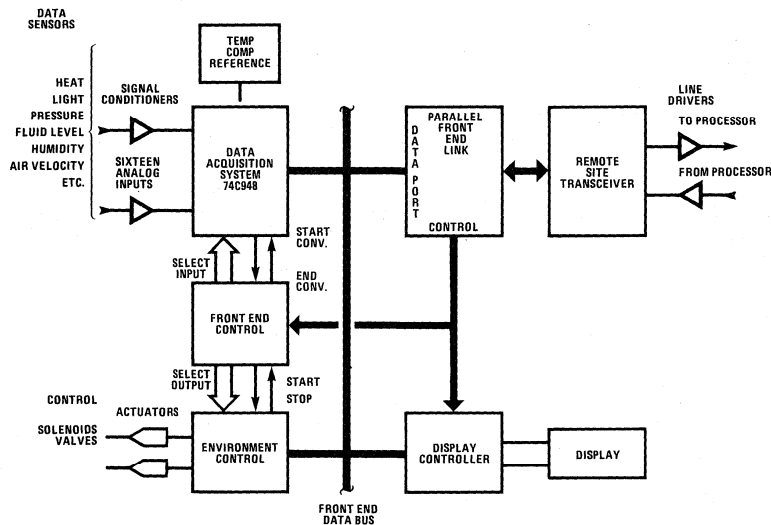


Figure 2. Remote Environmental Control System

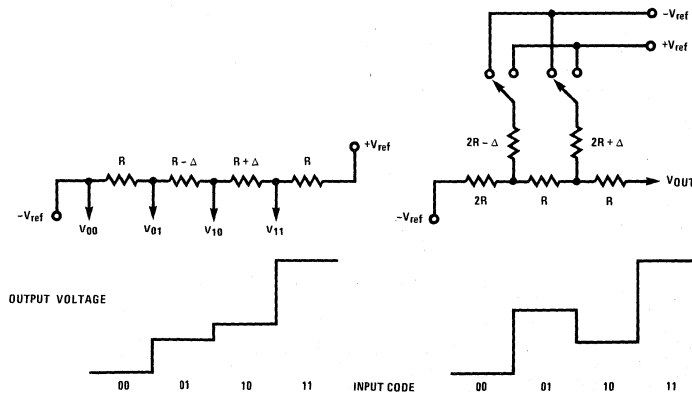


Figure 3.  $2^nR$  and  $R/2R$  Ladder Transfer Curves. In a  $2^nR$  ladder the most unequal resistors can do is cause a nonuniform voltage step. Since a single voltage is across the ladder it must be monotonic. In a  $R/2R$  ladder unequal resistors may cause a sign change in the transfer curve, causing it to be nonmonotonic.

The bottom resistor and the top resistor of the ladder network in figure 4 are not the same value as the remainder of the network. The difference in these resistors causes the output characteristic to be symmetrical with the zero and full-scale points of the transfer curve. The first output transition occurs when the analog signal has reached  $+1/2$  LSB and succeeding output transitions occur every 1 LSB later up to full-scale.

The successive approximation register (SAR) performs eight iterations to approximate the input voltage. For any SAR-type converter,  $n$  iterations are required for an  $n$ -bit converter. Figure 4 shows a typical example of a 3-bit converter with an input voltage of  $1/4$  full-scale. Since the initial approximation at  $7/16$  of full-scale is too high, a zero is posted for the most significant bit (MSB). The second approximation is too low, therefore a one is posted for the second bit. The final approximation is determined to be too high, so a zero is posted for the least significant bit (LSB). In the ADC0816/MM74C948 the approximation technique is extended to eight bits using the 256R network.

The most important section of the A/D converter is the comparator. It is this section which is responsible for the ultimate accuracy of the entire converter. It is also the comparator drift which has the greatest influence on the respectability of the device. A chopper stabilized comparator provides the most effective method of satisfying all the converter requirements.

The chopper stabilized comparator converts the DC input signal into an AC signal. This signal is then fed through a high gain AC amplifier and has the DC level restored. This technique limits the drift component of the amplifier since the drift is a DC component which is not passed by the AC amplifier. This makes the entire A/D converter extremely insensitive to temperature, long-term drift, and input offset errors.

The design of this A/D converter has been optimized by incorporating the most desirable aspects of several conversion techniques. The ADC0816 offers high speed, high accuracy, low temperature dependence, excellent long-term accuracy and repeatability, and consumes minimal power. These features make this device ideally suited to applications such as process control, industrial control, and machine control.

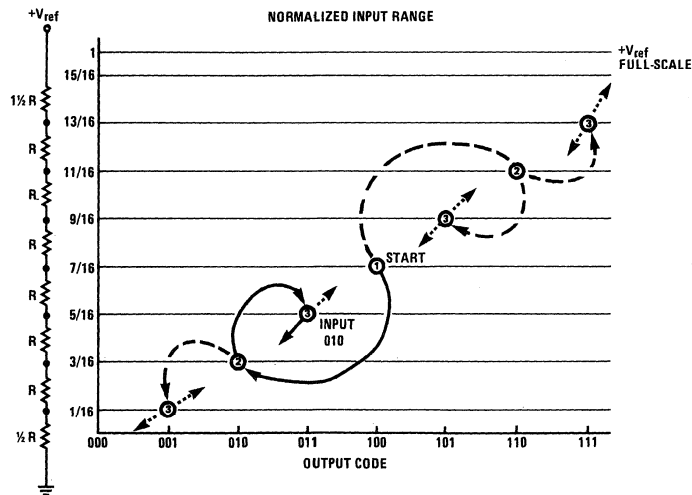


Figure 4. Offset-Adjusted 8 R Ladder gives  $\pm 1/2$  LSB quantizing error of 3 bits with three comparisons. The output code is derived by posting a one when upward arrows are followed and a zero when downward arrows are followed to the input voltage.



# New Phase-Locked-Loops Have Advantages as Frequency to Voltage Converters (and more)

National Semiconductor  
Application Note 210  
Robert Pease  
April 1979




AN-210 New Phase-Locked-Loops Have Advantages as Frequency to Voltage Converters (and more)

A phase-locked-loop (PLL) is a servo system, or, in other words, a feedback loop that operates with frequencies and phases. PLL's are well known to be quite useful (powerful, in fact) in communications systems, where they can pluck tiny signals out of large noises. Here, however, we will discuss a new kind of PLL which cannot work with low-level signals immersed in noise, but has a new set of advantages, instead. It does require a clean noise-free input frequency such as a square wave or pulse train.

This PLL can operate over a wide frequency range, not just 1 or 2 octaves but over 1 or 2 or 3 decades. It naturally provides a voltage output which responds quickly to frequency changes, yet does not have any inherent ripple. Thus, it can be used as a frequency-

to-voltage (F-to-V) converter which does not have any of the classical limitations or compromises of (large ripple) vs (slow response), which most F-to-V converters have. The linearity of this F-to-V converter will be as good as the linearity of the V-to-F converter used, and this linearity can easily be better than 0.01%. Other advantages will be apparent as we study the circuit further.

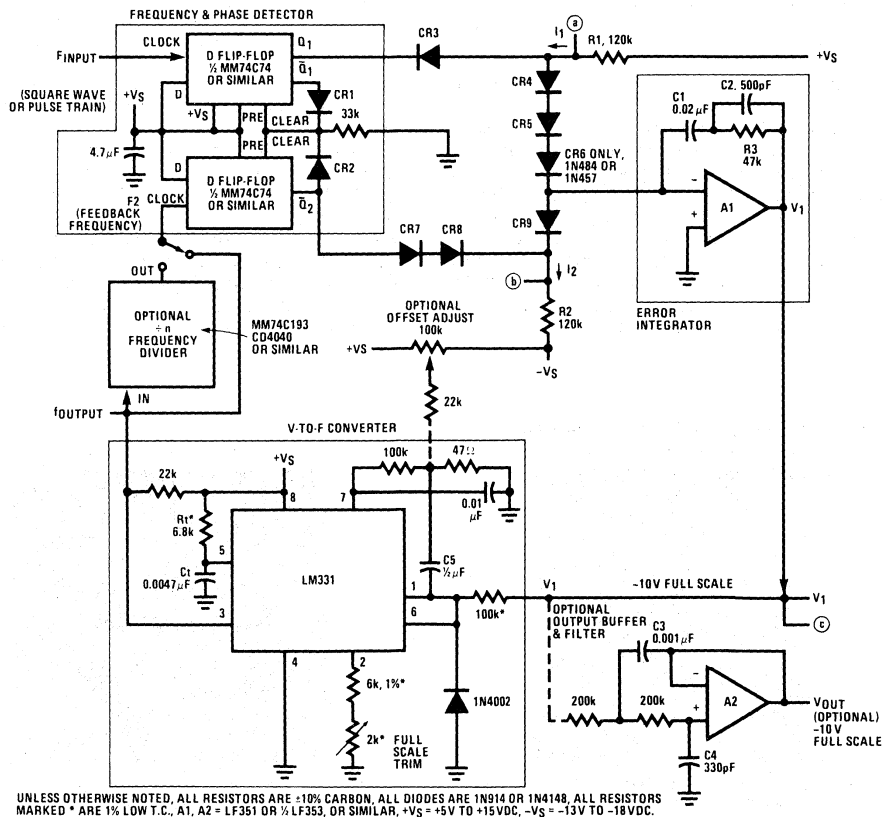The basic circuit shown in Figure 1 has all the functional blocks of a standard PLL. The frequency and phase detection do not consist of a quadrature detector, but of a standard dual-D flip-flop. When the frequency input is larger than  $F_2$ , Q1 will be forced high a majority of the time, and provide a positive error signal (via CR3, 4, 5, and 6) to the integrator.



UNLESS OTHERWISE NOTED, ALL RESISTORS ARE  $\pm 10\%$  CARBON, ALL DIODES ARE 1N914 OR 1N4148, ALL RESISTORS MARKED \* ARE  $\pm 1\%$  LOW T.C., A1, A2 - LF351 OR  $\frac{1}{2}$  LF353, OR SIMILAR, +VS = +5V TO +15VDC, -VS = -13V TO -18VDC.

Figure 1. Basic Wide-Range Phase-Locked Loop

1. AN-207. V-to-F and F-to-V Converter Applications.

If  $F$  input and  $F_2$  are the same, but the rising edges of  $F$  input lead the rising edges of  $F_2$ , the duty cycle of  $Q1 = HI$  will be proportional to the phase error. Thus, the error signal fed to the integrator will decrease to nearly zero, when the loop has achieved phase-lock, and the phase error between  $F_{IN}$  and  $F_2$  is zero. Actually, in this condition,  $Q1$  will put out 30 nanosecond positive pulses, at the same time that  $Q2$  puts out 30 nanosecond negative pulses, and the net effect as seen by the integrator is zero net charge. The 30 nanosecond pulses at  $Q1$  and  $Q2$  enable both flip-flops to be CLEARED, and prepared for the next cycle. This phase-detector action is substantially the same as that of an MC4044 Phase-Detector, but the MM74C74 is cheaper and uses less power. It is fast enough for frequencies below 1 MHz. (At higher frequencies, a DM74S74 can be used similarly, with very low delays.)

The error integrator takes in the current from  $R1$  or  $R2$ , as gated by the  $Q1$  and  $\overline{Q2}$  outputs of the flip-flop. For example, when  $F_{IN}$  is higher, and  $Q1$  is HIGH,  $I_1$  will flow through  $CR4$ ,  $5$ , and  $6$  and cause the integrator's output to go more negative. This is the direction to make the V-to-F converter run faster, and bring  $F_2$  up to  $F$  input. Note that  $A1$  does not merely integrate this current in  $C1$  (a mistake which many amateur PLL designers make!). The resistor  $R3$  in series with  $C1$  makes a phase lead in the loop response, which is essential to loop stability. The small capacitor  $C2$  across  $R3$  is not essential, but has been observed to offer improved settling at the voltage output.

The output of the integrator,  $V1$ , is fed to a voltage-to-frequency (V-to-F) converter. The example shown here utilizes a LM331. This converter runs on a single supply, and responds quickly with nonlinearity better than 0.05% (even though an op-amp is not used nor needed). The output of the VFC is fed back to  $F_2$ , as a feedback frequency, either directly or through an (optional) frequency divider. Any number of standard frequency dividers such as MM74C193, CD4029, or CD4018, can be used, subject to reasonable limits. A divider of 2, 3, 10, or 16 is often used. The output voltage of the integrator will be proportional to the  $F$  input, as linearly as the

V-to-F can make it. Thus, the integrator's output voltage  $V1$  can be used as the output of an ultralinear F-to-V converter. However during the brief pulses when the flip-flop is CLEARing itself, there will be small glitches found on the output of  $A1$ . The RMS value of this noise may be very small, typically 0.5 to 5mV, but the peak amplitude, sometimes 10 to 100mV, can be annoying in some systems. And, no additional filtering can be added in the main loop's path, for any further delay in the route to the VFC would cause loop instability. Instead, the output may be obtained from a separate filter and buffer which operates on a branch path.  $A2$  provides a simple 2-pole active filter (as discussed in Reference 1) which cuts the steady-state ripple and noise down below 1mV peak-to-peak, an excellent level for such a quick F-to-V (as we shall see).

What is not obvious about  $A2$  is that its output can settle (within a specified error-band such as  $\pm 10$  millivolts from the final DC value) earlier and more quickly than  $A1$ 's output. The waveforms in Figure 2 show  $F_{IN}$  stepping up instantly from 5kHz to 10kHz; it also shows  $F_2$  stepping up very quickly. The error signal at  $Q1$  is also shown. The critical waveforms are shown in Figure 3, the outputs of  $A1$  and  $A2$ . While  $A1$  puts out large spikes (caused by  $I1$  flowing through  $R3$ ), these large spikes cause the V-to-F converter to jump from 5kHz to 10kHz without any delay. There is, as shown in Figure 2, a significant phase error between  $F_{IN}$  and  $F_2$ , but an inspection of these frequencies shows that frequency lock has been substantially instantaneous. Not one cycle has been lost! The phase lock and settling takes longer to achieve. Still, we know that if the frequency out of the VFC is 10kHz, its input voltage must be  $-10$  VDC. If there is noise on it, all we have to do is filter it in  $A2$ . Figure 3 shows that  $A2$  settles very quickly — actually, in 2.0 milliseconds, which is just 20 cycles of the new frequency.  $A2$ 's output has settled (i.e., the frequency has settled), while  $A1$ 's output error (which is indicative of phase error being servo'ed out) continues to settle out for another 12ms. Thus, this filter permits its output voltage to settle faster than its input, and it is responsible for the remarkable quickness of this circuit as an F-to-V converter. The

Vertical sensitivity = 10V/DIV (CMOS logic levels)  
Horizontal sensitivity = 0.5ms/DIV

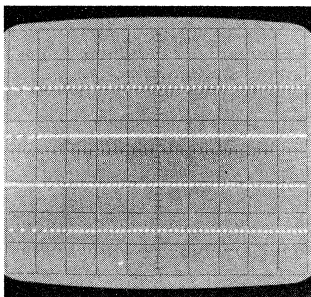


Figure 2a.  $F$  output steps up from 5kHz to 10kHz as quickly as the input, never missing a beat.  
Top Trace = input " $F_{IN}$ " to PLL.  
Bottom Trace = output " $F_{OUT}$ " from PLL.

Vert = 10V/DIV, Horiz = 0.5ms/DIV

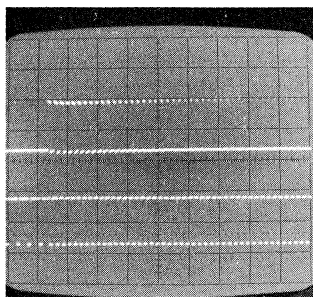


Figure 2b. Error Signal.  
Top Trace = error signal at  $Q1$ .  
Bottom Trace = output " $F_{OUT}$ " from PLL.

waveforms of Figure 3 can be compared to the response (shown in Figure 4) of a conventional F-to-V converter. The upper trace is the output of a conventional FVC after a 4-pole filter; and the lower trace is the output of

the circuit of Figure 1. The phase-locked-loop F-to-V converter is quicker yet quieter.

2. AN-207, V-to-F and F-to-V Converter Applications.

Vert = 2V/DIV, Horiz = 2ms/DIV

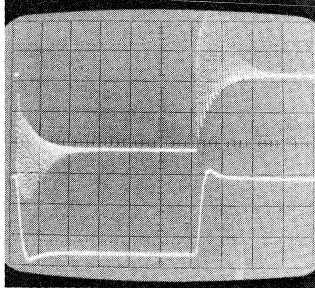


Figure 3a. Settling waveforms, as  $F_{IN}$  goes from 5 kHz to 10 kHz and back again, using circuit of Figure 1. Top Trace = output of integrator (V1). Bottom Trace = output of filter ( $V_{OUT}$ ).

Vert = 2V/DIV, Horiz = 0.5ms/DIV

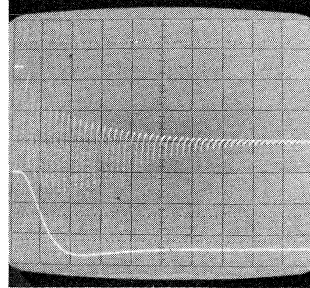


Figure 3b. PLL Settling Waveforms. The same waveform as in Figure 3a, but time base is expanded to 0.5ms/DIV to show fine detail of settling.

Vert = 2V/DIV, Horiz = 20ms/DIV

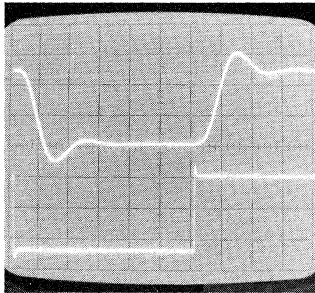


Figure 4a. FVC Response vs PLL Response. The PLL can settle rather more quickly than a conventional F-to-V converter. Top Trace = conventional F-to-V converter with 4-pole active filter, responding to a 5 kHz to 10 kHz step. Bottom Trace = PLL FVC, with the same input, circuit of Figure 1.

Vert = 2V/DIV, Horiz = 20ms/DIV

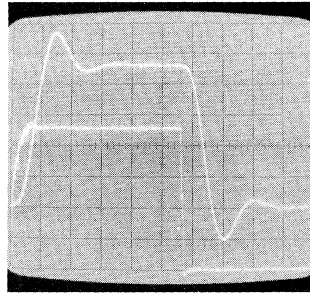


Figure 4b. FVC Step Response. This waveform is similar to that in Figure 4a, but the frequency change covers a 10:1 ratio, from 10 kHz to 1 kHz and back to 10 kHz. For this waveform, the adaptive current sources of Figure 5 connect to Figure 1 (whereas for Figure 4a  $R_1 = R_2 = 120k$ ).

Vert = 2V/DIV, Horiz = 5ms/DIV

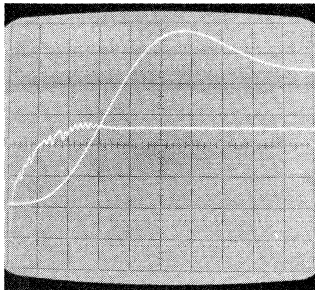


Figure 4c. FVC Response. The same as Figure 4b, but time base expanded to 5ms/DIV, to show detail of rise time. Top Trace = conventional FVC. Bottom Trace = PLL FVC.

Vert = 2V/DIV, Horiz = 5ms/DIV

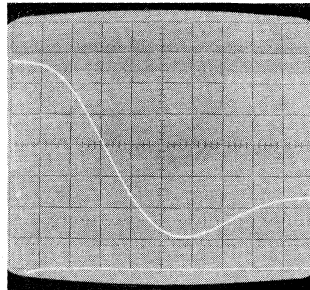


Figure 4d. FVC Response. The same as Figure 4b, but expanded to 5ms/DIV to show details of fall time. Top Trace = conventional FVC. Bottom Trace = PLL FVC.

Vert = 0.2 V/DIV. Horiz = 50 ms/DIV

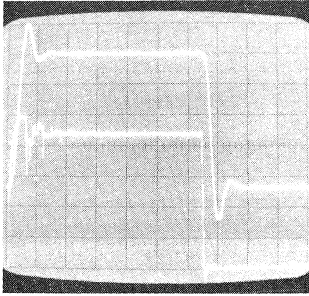


Figure 4e. PLL Settling Waveforms at Low Frequencies.

The same idea as in Figure 4b, but 10x slower, from 1.0kHz to 100 Hz (and back). The settling to 1 kHz is still distinctly faster for the PLL, but at 100 Hz, it is a bit slower. Still, the PLL is faster than the FVC at all speeds from 200 Hz to 10 kHz.

So far we have shown a PLL which operates nicely over a frequency range of about 3:1. If the frequency is decreased below 3kHz, the loop gain becomes excessive, and the currents I1 and I2 are large enough to cause loop instability. The loop gain increases at lower frequencies, because a given initial phase error will cause the fixed current from R1 or R2 to be integrated for a longer time, causing a larger output change at the integrator's output, and a larger change of frequency. When the frequency is thus corrected, and the period of one cycle is changed, at a low frequency it may be overcorrected, and the phase error on the next cycle may be as large as (or larger than) the initial phase error, but with reversed sign.<sup>3</sup> To avoid this and to maintain loop stability at lower frequencies, e.g. 0.5 to 1kHz, R1 and R2 can be simply raised to 1.5 MΩ. However, response to a step will be proportionally slower. To achieve a wide frequency range (20:1), and optimum quickness at all frequencies, it is necessary to servo I1 and I2 to be proportional to the frequency. Fortunately, as V1 is normally proportional to F, it is easy to generate current sources I1' and I2' which are proportional to F. The circuit of Figure 5 can be connected to the basic PLL,


instead of R1 and R2, and provides good, quick loop stability over a 30:1 frequency range, from 330 Hz to 10 kHz. For best results over a 30:1 frequency range, change R3, the damping resistor in Figure 1, from 47k to 100k. However, if the frequency range is smaller (such as 2:1 or 3:1), constant resistors for R1 and R2 or very simple current sources may give adequate response in many systems. (To cover wider frequency ranges than 30:1 with optimum response, the circuits in the precision phase-locked-loop, below, are much more suitable.)

Often a frequency multiplier is needed, to provide an output frequency 2 or 3 or 10 or n times higher than the input. By inserting a -n frequency divider in the feedback loop, this is easily accomplished. [Of course, a -m frequency divider can be inserted ahead of the frequency input, to provide correct scaling, and the output frequency then will be  $F_{IN}(n/m)$ .]

To obtain good loop stability in a frequency multiplier with  $n=2$ , remember that a 20kHz V-to-F converter followed by a  $\times 2$  circuit has exactly the same loop response and stability needs as a 10kHz V-to-F converter, because it is a 10kHz V-to-F converter, even though it provides a useful 20kHz output. Thus, the frequency of the  $F_2$  (minimum and maximum) will determine what loop gains and loop damping components are needed.

To accommodate a 1kHz V-to-F loop, simply make C1 and C2 10 times bigger than the values of Figure 1; treat C3, C4, C5 and Ct similarly if used. To accommodate a 100Hz V-to-F, increase them by another factor of 10.

If the PLL is to be used primarily as a frequency multiplier, it may be unnecessary to use stable, low-temperature-coefficient components, because the accuracy of  $V_{OUT}$  will not be important. The parts cost can be cut considerably. (Make sure that the VFC does not run out of range to handle all frequencies of interest.) On the other hand, the damping components will be chosen quite a bit differently if slow, stable jitter-free response is needed or if quick response is required. The circuits shown are just a starting place, to start optimizing your own circuit.

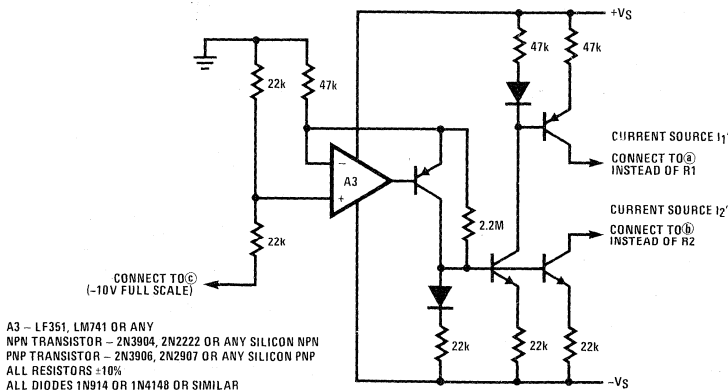

A3 - LF351, LM741 OR ANY  
NPN TRANSISTOR - 2N3904, 2N2222 OR ANY SILICON NPN  
PNP TRANSISTOR - 2N3906, 2N2907 OR ANY SILICON PNP  
ALL RESISTORS  $\pm 10\%$   
ALL DIODES 1N914 OR 1N4148 OR SIMILAR

Figure 5. Proportional Current Source for Basic PLL

3. Optimize phase-lock loops to meet your needs or determine why you can't. Andrzej B. Przedpelski. *Electronic Design*, September 13, 1978.



## A Single-Supply PLL

The single-supply PLL is shown in Figure 6 as an example of a simple circuit which is effective when battery operation or single-supply operation is necessary. This circuit will function accurately over a 10:1 frequency range from 1kHz to 10kHz, but will not respond as quickly as the basic PLL of Figure 1. The reason is the use of the CD4046 frequency detector. When an  $F_{IN}$  edge occurs ahead of a  $F$  feedback pulse, pin 13 of the CD4046 pulls up on C1 via  $R1 = 1k\Omega$ . This current cannot be controlled or manipulated over as wide a range as "11" in Figure 1. As a consequence, the response of this PLL is never as smooth nor fast-settling as the basic PLL, but it is still better behaved than most F-to-V converters. As with the basic PLL, the

detector feeds a current to be integrated in C1 (and R2 provides the necessary "lead"). A1 acts simply as a buffer for the R1, C1 integrator. A3, optional, can provide a nicely filtered output. And A2 servos Q1, drawing a current out of C6 which is proportional to  $V2$ . Here the LM331 acts as a current-to-frequency converter, and  $F$  output is precisely proportional to the collector current of Q1. As with the basic circuit, this PLL can be used as a quick and/or quiet F-to-V converter, or as a frequency multiplier. One of the most important uses of an F-to-V is to demodulate the frequency of a V-to-F converter, which may be situated at a high common-mode voltage, isolated by photo-isolators, or to recover a telemetered signal. An F-to-V converter of this sort can provide good bandwidth for demodulating such a signal.


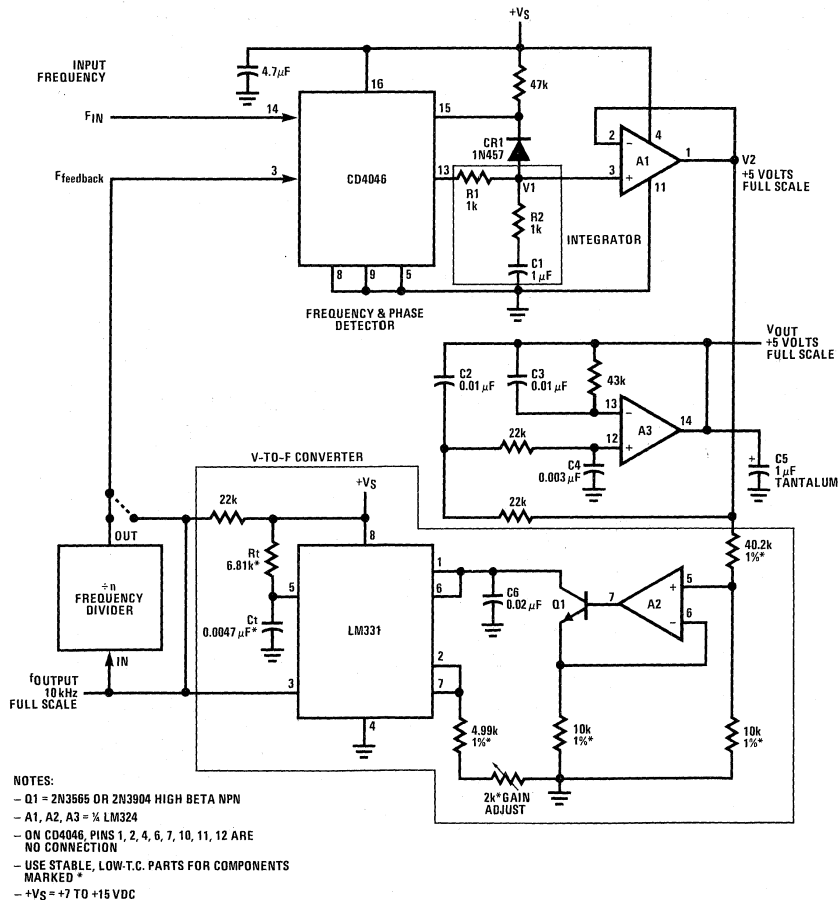


Figure 6. Single Supply Phase Locked Loop

The precision PLL in Figure 7 acts very much the same as the basic PLL, with refinements in various places.

- The flip-flops in the detector have a gate G1 to CLEAR them, for quicker response.
- The currents which A1 integrates are steered through Q1, Q2 and Q3, Q4 because transistors are quicker than diodes, yet have much lower leakage.

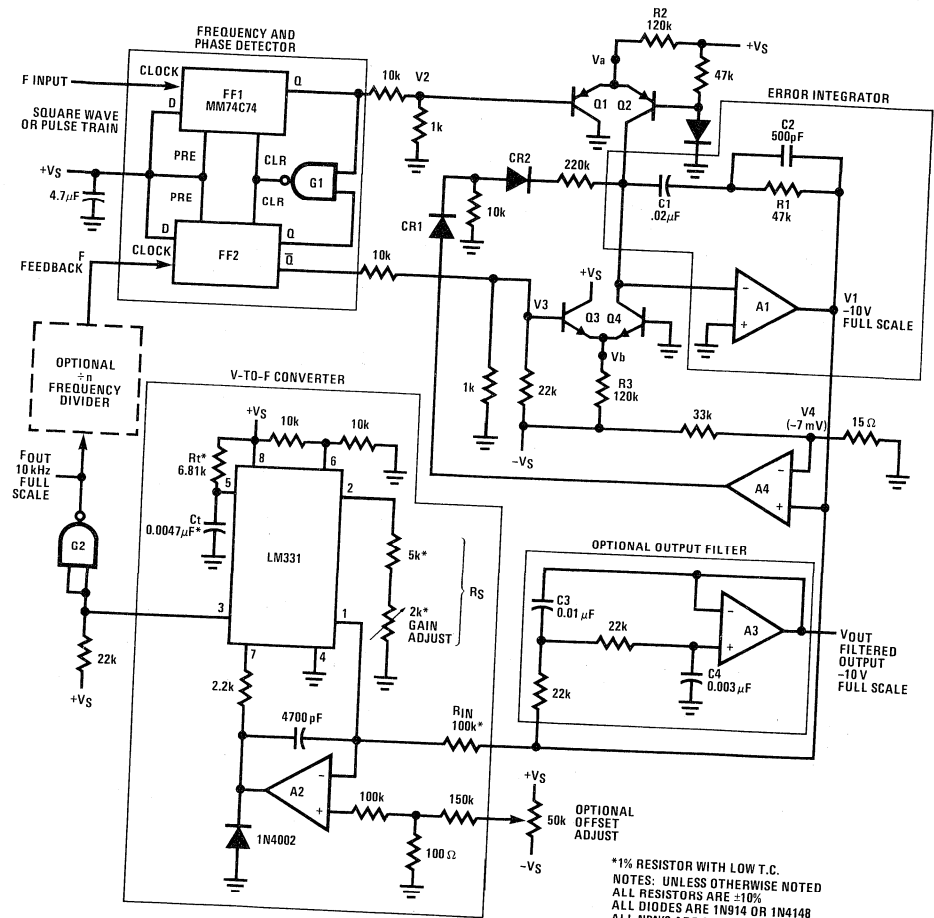- The V-to-F converter uses A2 as an op-amp integrator, to get better than 0.01% nonlinearity (max).
- G2 is recommended as an inverter, to invert the signal on the LM331's pin 3, avoid a delay, and improve loop stability. (However, we never found any *real* improvement in loop stability, despite theories that insist it must be there. Comments are invited.)



\*1% RESISTOR WITH LOW T.C.  
 NOTES: UNLESS OTHERWISE NOTED  
 ALL RESISTORS ARE  $\pm 10\%$   
 ALL DIODES ARE 1N914 OR 1N4148  
 ALL NPN'S ARE SILICON, 2N3904 OR SIMILAR  
 ALL PNP'S ARE SILICON, 2N3906 OR SIMILAR  
 □ = 1/4 MM74C00 OR CD4011  
 A3, A1 = LF351; 1/2 LF353, OR SIMILAR  
 A2 = LF351B, LM308A, OR SIMILAR  
 A4 = LF351, LM741C, OR ANY  
 +V<sub>S</sub> = +12 TO +15 VDC  
 -V<sub>S</sub> = -14 TO -16 VDC

Figure 7. Precision PLL

- A4 is included as an (optional) limiter, to prevent V1 from ever going positive. This will facilitate quick startup and recovery from overdrive conditions.

Also, in Figure 8, the wide-range current pump for the precision PLL is a "semiprecision" circuit, and provides an output current proportional to  $-V_1$ , give or take 10 or 15%, over a 3-decade range. The  $22\text{ M}\Omega$  resistors prevent the current from shutting off in case  $-V$  becomes positive (probably unnecessary if A4 is used). For best results over a full 3-decade range (11 kHz to 9 Hz), do use A4, delete the four  $22\text{ M}\Omega$  resistors, and insert the (diode parallel to the  $470\text{ k}\Omega$ ) in series with the  $R_G$  as shown. This will give good stability at all

frequencies (although stability cannot be extended below  $1/1500$  of full scale without extra efforts).

This PLL has been widely used in testing of VFCs, as it can force the LM331 to run at a crystal-controlled frequency (established as the F input), and the output voltage at  $V_{OUT}$  is promptly measured by a 6-digit (1 ppm nonlinearity, max) digital voltmeter, with much greater speed and precision than can be obtained by forcing a voltage and trying to read a frequency. While at 10 kHz, the advantages are clearcut; at 50 Hz it is even more obvious. Measuring a 50 Hz signal with  $\pm 0.01\text{ Hz}$  resolution cannot be done (even with the most powerful computing counter-timer) as accurately, quickly, and conveniently as the PLL's voltage output settles.

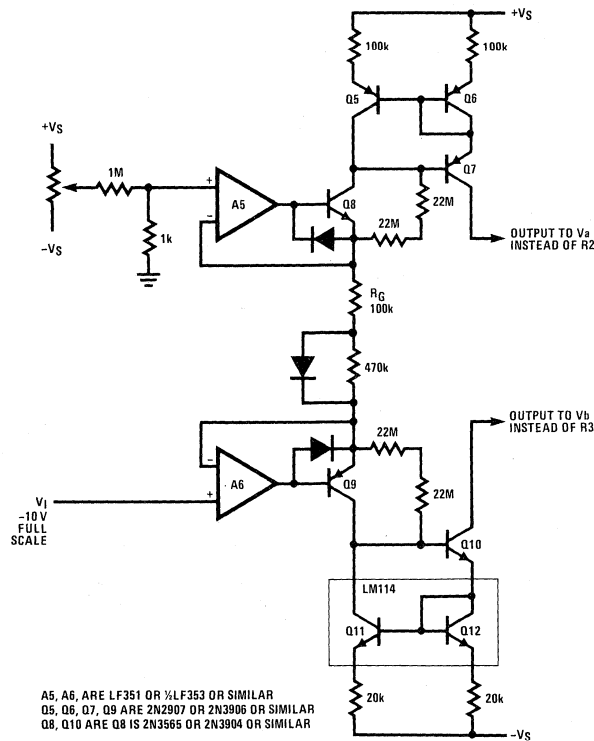


Figure 8. Wide Range Current Pumps for Precision PLL of Figure 7

One final application of this PLL is as a wide-range sine generator. The VFC in Figure 9 puts out an adequate sine-shaped output, but does not have good V-to-F linearity, and its frequency stability is not much better than 0.2%. An LM331 makes an excellent linear stable V-to-F converter, with a pulse output; but it can not make sines. But it can command, via a PLL, to force the sine VFC to run at the correct frequency. Simply connect the sine VFC

of Figure 9 into one of the PLLs, instead of the LM331 VFC circuit. Then use a precise linear low-drift VFC based on the LM331 to establish the  $F_{IN}$  to the PLL. If the voltage needed by the sine VFC to put out a given frequency drifts a little, that is okay, as the integrator will servo and make up the error. The use of a controlled sine-wave generator in a test system was the first of many applications for a wide-range phase-locked-loop.

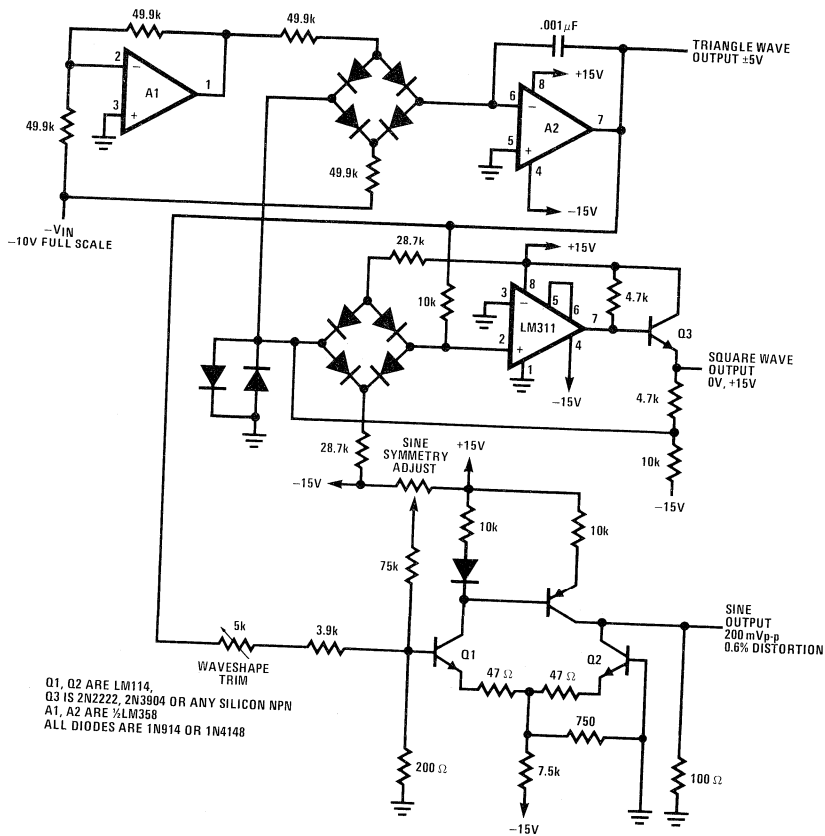


Figure 9. Sine-Wave VFC to Use with PLL

# New Op Amp Ideas

Robert J. Widlar  
Apartado Postal 541  
Puerto Vallarta, Jalisco  
Mexico



Robert C. Dobkin and Mineo Yamatake  
National Semiconductor Corporation  
Santa Clara, California  
U.S.A.

December 1978

**Abstract:** An op amp and voltage reference capable of single supply operation down to 1.1V is introduced. Performance is uncompromised and compares favorably with standard, state-of-the-art devices. In a departure from conventional approaches, the circuit can operate in a floating mode, powered by residual voltages, independent of fixed supplies. A brief description of the IC design is given, but emphasis is on applications. Examples are given for a variety of remote comparators and two-wire transmitters for analog signals. Regulator designs with outputs ranging from a fraction of a volt to several hundred volts are discussed. In general, greater precision is possible than with existing ICs. Designs for portable instruments are also looked into. These applications serve to emphasize the flexibility of the new part and can only be considered a starting point for new designs.

## Introduction

Integrated circuit operational amplifiers have reached a certain maturity in that there no longer seems to be a pressing demand for better performance. Devices are available at low cost for all but the most exacting needs. Of course, there is always room for improvement, but even substantial changes in specifications cannot be expected to cause much excitement.

A new approach to op amp design and application has been taken here. First, the amplifier has been equipped to function in a floating mode, independent of fixed supplies. This, however, in no way restricts conventional operation. Second, it has been combined with a voltage reference, since these two functions are often interlocked in equipment design. Third, the minimum operating voltage has been reduced to nearly one volt. It will be seen that these features open broad new areas of application.

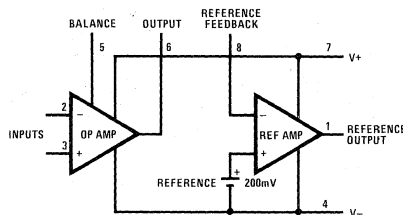


Figure 1. Functional Diagram of the New IC

A functional diagram of the new device is shown in figure 1. Even though a voltage reference and a reference amplifier have been added, it can still be supplied in an eight-pin TO-5 or mini-DIP. The pin connections for the op amp are the same as the industry standards. And offset balancing that tends to minimize drift has been provided. Both the op amp and the reference amplifier are internally compensated for unity-gain feedback.

Table I shows that, except for bias current, the general specifications are much as good as the popular LM108. But the new circuit has a common mode range that includes  $V^-$  and the output swings within 50mV of the supplies with 50 $\mu$ A load, or within 0.4V with 20mA load. These parameters are specified in table I as the conditions under which gain and common-mode rejection are measured. Table II indicates that the reference compares favorably with the better ICs on the market today.

Table I. Typical Performance of the Operational Amplifier at 25°C.

Parameter	Conditions	Value
Input Offset Voltage		0.3mV
Offset Voltage Drift	$-55^\circ\text{C} \leq T_A \leq 125^\circ\text{C}$	$2\mu\text{V}/^\circ\text{C}$
Input Offset Current		0.25nA
Offset Current Drift	$-55^\circ\text{C} \leq T_A \leq 125^\circ\text{C}$	$2\text{pA}/^\circ\text{C}$
Input Bias Current		10nA
Bias Current Drift	$-55^\circ\text{C} \leq T_A \leq 125^\circ\text{C}$	$40\text{pA}/^\circ\text{C}$
Common-Mode Rejection	$V^- \leq V_{CM} \leq V^+ - .85\text{V}$	102dB
Supply-Voltage Rejection	$1.2\text{V} \leq V_S \leq 40\text{V}$	96dB
Unloaded Voltage Gain	$V_S = \pm 20\text{V}$ , $V_O = \pm 19.95\text{V}$ , $I_O \leq 50\mu\text{A}$	400V/mV
Loaded Voltage Gain	$V_S = \pm 20\text{V}$ , $V_O = \pm 19.6\text{V}$ , $R_L = 980\Omega$	130V/mV
Unity-Gain Bandwidth	$1.2\text{V} \leq V_S \leq 40\text{V}$	0.3MHz
Slew Rate	$1.2\text{V} \leq V_S \leq 40\text{V}$	0.15V/ $\mu$ s

Table II. Typical Performance of the Reference at 25°C.

Parameter	Conditions	Value
Line Regulation	$1.2\text{V} \leq V_S \leq 40\text{V}$	0.001%/V
Load Regulation	$0 \leq I_O \leq 1\text{mA}$	0.01%
Feedback Sense Voltage		200mV
Temperature Drift	$-55^\circ\text{C} \leq T_A \leq 125^\circ\text{C}$	0.002%/°C
Feedback Bias Current		20nA
Amplifier Gain	$0.2\text{V} \leq V_O \leq 35\text{V}$	75V/mV
Total Supply Current	$1.2\text{V} \leq V_S \leq 40\text{V}$	270 $\mu$ A

Since worst-case internal dissipation can easily exceed 1W under overload conditions, thermal overload protection is included. Thus at higher ambient temperatures, this circuit is better protected than conventional op amps with lesser output capabilities.

Figures 2 and 5 are simplified schematics of the op amp, the reference and the internal current regulator. A complete circuit description is a subject in itself and is covered in detail elsewhere [1]. However, a brief run through the circuit is in order to give some understanding of the details that affect application.

### The Op Amp

Referring to figure 2, lateral PNPs are used for the op amp input because this was the only reasonable way to get  $V^-$  included in the common-mode range while meeting the minimum-voltage requirement. These transistors typically have  $h_{FE} > 100$  at  $I_C = 1\mu A$  and appear to match better than their NPN counterparts. Current gain is less affected by temperature, resulting in a fairly flat bias current over temperature (figure 3). At elevated temperature the sharp decrease in bias current for  $V_{CM} > V^-$  is caused by the same substrate leakage that affects bi-FET op amps.

Protective resistors have been included in the input leads so that current does not become excessive when the inputs are forced below the negative supply, forward biasing the base tubs of the lateral PNPs.

Offset nulling is accomplished by connecting the balance terminal to a variable voltage derived from the reference output, as shown in figure 4. Both the input stage collector voltage and the reference are well regulated and have a low temperature drift. The resistance of the adjustment potentiometer can be made very much lower than the resistance looking

back into the balance pin. Therefore, no matching of temperature coefficients is required and offset nulling will tend to produce a minimum-drift condition.

With 200mV on the balance control, the balance range is asymmetrical. Standard parts are trimmed to bring them into the  $-1mV$  to  $8mV$  adjustment range. Null sensitivity can be reduced for low-offset premium parts by adding a resistor on the top end of R1.

Proceeding through the circuit, the input stage is buffered by vertical PNP followers, Q3 and Q4. From here, the differential signal is converted to single ended and fed to the base of the second stage amplifier, Q7.

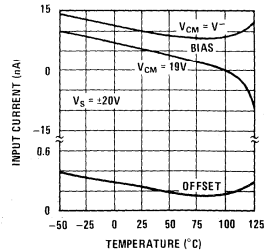


Figure 3. Variation of Input Current with Temperature

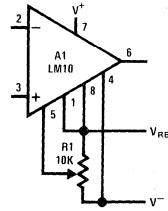


Figure 4. Op Amp Offset Adjustment

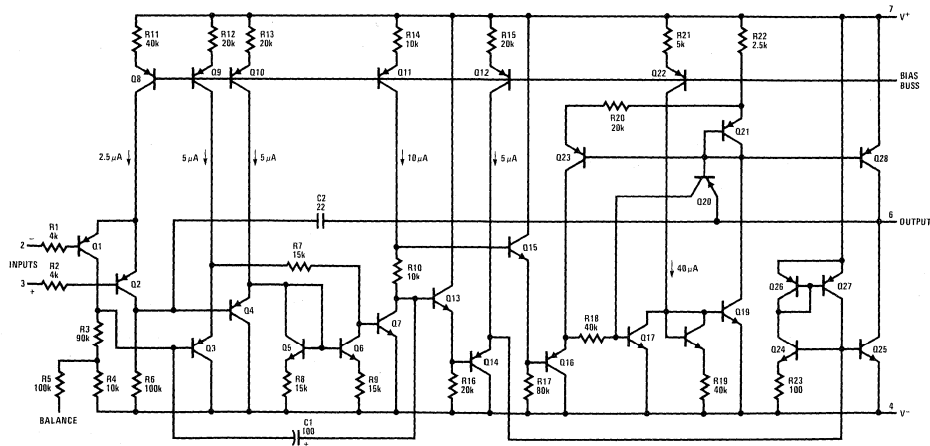


Figure 2. Essential Details of the Op Amp

This configuration is not inherently balanced in that the emitter-base voltage of the PNP transistors is required to match that of the NPNs. The final design includes circuitry to correct for the expected variations.

From the collector of Q7, the signal splits, driving separate halves of the complementary class-B output stage. The NPN output transistor, Q25, is driven through Q13 and Q14. This complementary emitter follower arrangement provides the necessary current gain without requiring the extra bias voltage of the Darlington connection.

Base drive for the NPN output transistor is initially supplied by Q12, but a boost circuit has also been added to increase the available drive as a function of load current. This is accomplished by Q24 in conjunction with a current inverter.

Drive for the PNP half of the output is somewhat more complicated. Again, a compound buffer, Q15 and Q16, is used, although to maintain circuit balance rather than for current gain. The signal proceeds through two inverters, Q17 and Q19, to obtain the correct phase relationship and DC level shift before it is fed to the PNP output transistor, Q28.

This path has three common-emitter stages and, potentially, much higher gain than the NPN side. The gain is equalized, however, by the shunting action of Q18-R19 and Q21-R22 as well as negative feedback through Q23.

When the output PNP saturates, Q20 serves to limit its base overdrive with a feedback path to the base of Q17. As will be seen, Q20 is also important to floating-mode operation in that it disables the PNP drive circuitry when the op-amp output is shorted to  $V^+$ .

## The Reference

A simplified version of the reference circuitry and internal current regulator is shown in figure 5. The design of the band-gap reference is unconventional both in its configuration and because it compensates for the second-order nonlinearities in the emitter-base voltage as well as those introduced by resistor drift. Thus, the bowed characteristic of conventional designs is eliminated, with better temperature stability resulting.

The reference element itself is formed by Q40 and Q41, with the output on the emitter of Q41. The  $V_{BE}$  component of the output is developed across R30, while the  $\Delta V_{BE}$  component is obtained by operating Q41 at a much lower current density than Q40. The output is made less sensitive to variations in biasing current by the action of R29. Curvature correction results from the different temperature coefficients of bias current for the two transistors.

The 200mV reference voltage is fed to both the reference amplifier and the internal current regulator. The reference amplifier design is straightforward, consisting of two stages with an emitter follower output. Unlike the op amp, the output can only swing within 0.8V of the positive supply. This should be kept in mind when designing low-voltage circuitry.

A minimal sink current ( $\sim 20\mu A$ ) is supplied by Q34. And since the reference is not included in the thermal protection control loop, conventional current limit is included on the final circuit to limit maximum output current to about 3mA.

The current regulator is also relatively uncomplicated. A control loop drives the current source bias bus so that the output of one current source (Q51) is proportional to the reference voltage. The remaining current sources are slaved into regulation by virtue of matching.

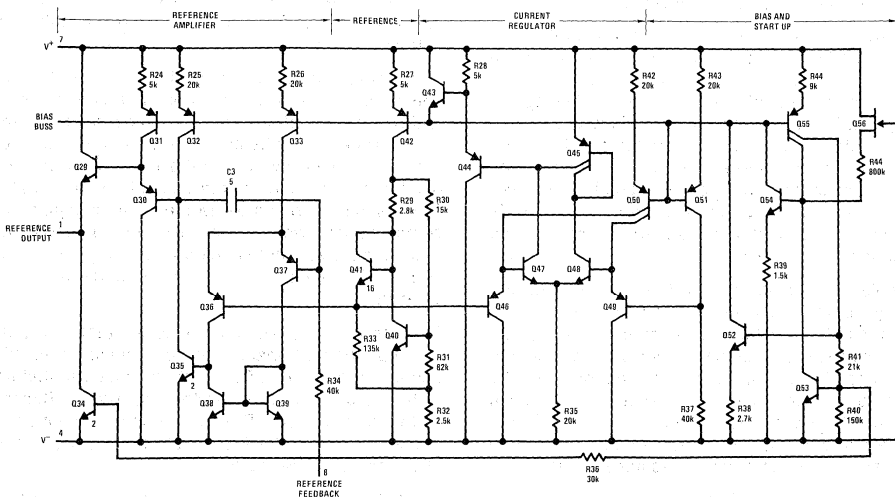


Figure 5. Simplified Schematic of the reference and Internal Current Regulator

The remaining circuitry generates a trickle current for start-up and biases internal circuitry.

An analysis of the complete circuit would serve only to bring into focus a multitude of detail such as second-order DC compensation terms, minor-loop frequency stabilization, clamps, overload protection, etc. Although necessary, these particulars tend to obscure the principles being put forward. So, having gained some insight into circuit operation, it is appropriate to proceed to some of the novel applications made possible with this new IC.

### Floating Comparators

The light-level detector in figure 6 illustrates floating-mode operation of the IC. Shorting the op-amp output to  $V^+$  disables the PNP half of the class-B output stage, as mentioned earlier. Thus, with a positive input signal, neither half of the output conducts and the current between the supply terminals is equal to the quiescent supply current. With negative input signals, the NPN portion of the output begins to turn on, reaching the short circuit current for a few hundred microvolts overdrive. This is shown in figure 7.

Figure 7 also shows the terminal characteristics for the case where the output is shorted to  $V^-$  so that only the PNP side can be activated. This mode of operation has not been so thoroughly investigated, but it gives a slightly lower ON voltage at moderate currents and the gain is generally higher below  $70^\circ\text{C}$ . With ON currents less than about 1 mA, the terminal voltage drops low enough to disrupt the internal regulators and the reference, producing some hysteresis. Further, there is a tendency to oscillate over about a  $50\mu\text{V}$  range of input voltage in the linear region of comparator operation.

The above is not intended to preclude operation with the output connected to  $V^-$ , if there is a good reason for doing so. It is meant only to draw attention to the problems that might be encountered.

In figure 6, the internal reference supplies the bias that determines the transition threshold. At crossover, the voltage across the photodiode is equal to the offset voltage of the op amp, so leakage is negligible. The circuit can directly drive such loads as logic circuits or silicon controlled rectifiers. The IC can be located remotely with the sensor, with the output transmitted along a twisted-pair line. Alternatively, a common ground can be used if there is sufficient noise immunity; and the signal can be transmitted on a single line.

It should be remembered that this particular design is fully compensated as a feedback amplifier. As such it is not particularly fast in comparator applications. With low-level signals, delays a few hundred microseconds can be expected; and once in the linear region, the maximum change of terminal voltage is  $0.15\text{V}/\mu\text{s}$ . This is illustrated in the plots of figures 8 and 9. In general, high accuracy cannot be obtained with switch frequencies above 100 Hz.

Hysteresis can be provided as shown in figure 6 by feedback to the balance terminal. About 1 mV of

hysteresis is obtained for a 5V output swing. However, this disappears near 10 Hz operating frequency because of gain loss.

Figure 10 shows a flame detector that can drive digital circuitry directly. The platinum-rhodium thermocouple gives an 8 mV output at  $800^\circ\text{C}$ . This threshold is established by connecting the balance pin to the reference output.

### Linear Operation

The IC can also operate linearly in the floating mode. The simplest examples of this are the shunt voltage regulator in figure 11 and the current regulator in figure 12. The voltage regulator is straightforward, but the current regulator is a bit unusual in that the supply current of the IC flows through the sense resistor and does not affect accuracy as long as it is less than the desired output current.

It is also possible to use remote amplifiers with two-wire signal transmission, as was done with the comparators. Remote sensors can be particularly troublesome when low-level analog signals are involved. Transmission problems include induced noise, ground currents, shunting from cable capacitance, resistance drops and thermoelectric potentials. These problems can be largely eliminated by amplifying the signal at the source and altering impedances to levels more suitable for transmission.

Figure 13 is an example of a remote amplifier. It boosts the output of a high-impedance crystal transducer and provides a low impedance output. No extra wires are needed because DC power is fed in on the signal line.

Figure 14 is a remote signal conditioner that operates in the current mode. A modification of the current source in figure 12, it delivers an output current inversely proportional to sensor resistance. The output can be transmitted over a twisted pair for maximum noise immunity or over a single line with common ground if the signal is slow enough that sufficient noise bypass can be put on the line.

A current-mode signal conditioner for a thermocouple is shown in figure 15. A thermocouple is in reality a two-junction affair that measures temperature differential. Absolute temperature measurements are made by controlling the temperature of one junction, usually by immersing it in an ice bath. This complication can be avoided with cold-junction compensation, which is an absolute thermometer that measures cold-junction temperature and corrects for any deviation from the calibration temperature.

In figure 15, the IC temperature sensor (S1) generates an output proportional to absolute temperature. This current flows through R2, which is chosen so that its voltage drop has the same temperature coefficient as the thermocouple. Thus, changes in cold-junction temperature will not affect calibration as long as it is at the same temperature as S1.

In addition to powering S1, the reference is used to generate an offset voltage such that the output



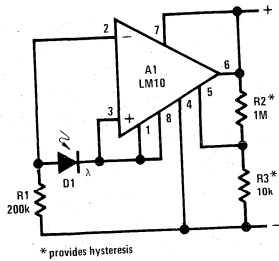


Figure 6. Two Terminal Light-Level Detector with Hysteresis

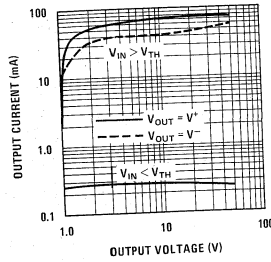


Figure 7. Terminal Characteristics Above and Below Threshold

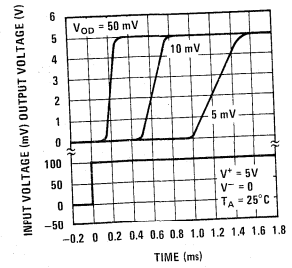


Figure 8. Comparator Response Times for Various Input Overdrives

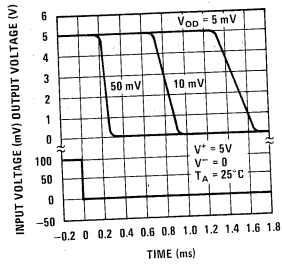


Figure 9. Comparator Response Times for Various Input Overdrives

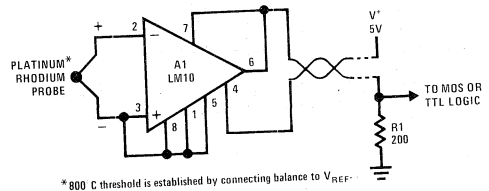


Figure 10. Flame Detector

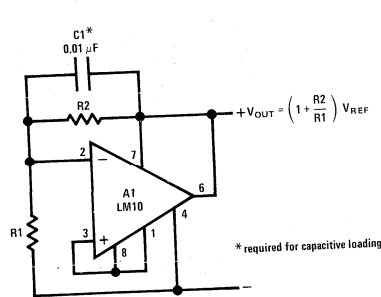


Figure 11. Shunt Voltage Regulator

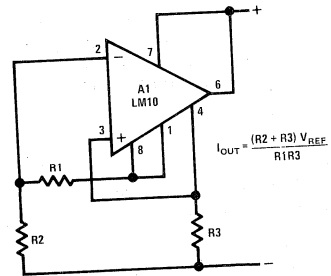


Figure 12. Current Regulator

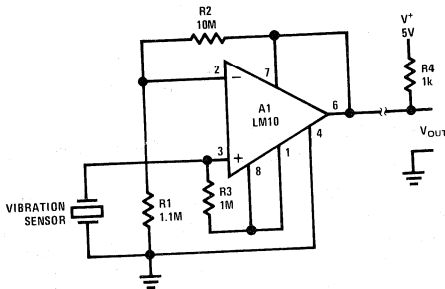


Figure 13. Remote Amplifier

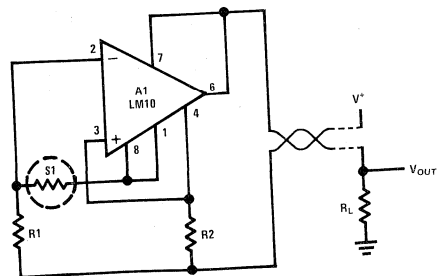


Figure 14. Two-Wire Transmitter for Variable-Resistance Sensor

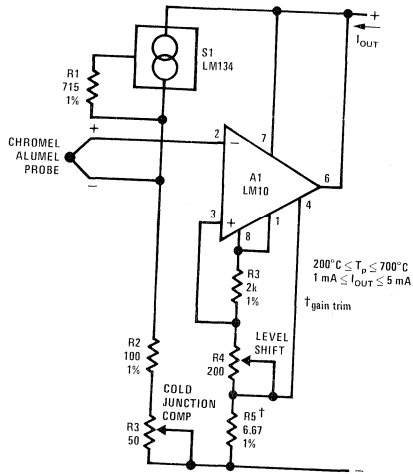


Figure 15. Current Transmitter for Thermocouple Including Cold Junction Compensation

current is within operating limits for temperatures of interest. It is important that the reference be stable because drift will show up as signal.

The indicated output-current range was chosen because it is one of the standards for two-wire transmission. With the new IC, the dynamic range can be increased by a factor of five in some cases (0.8mA-20mA) because the supply current is low. This could be used to advantage with a unidirectional signal where zero must be preserved: the less the offset required to put zero on scale, the less the offset-drift error.

The circuit in figure 16 is the same thermocouple amplifier operating in the voltage mode. The output voltage range was chosen arbitrarily in that there are no set standards for voltage-mode transmission.

The choice between voltage- and current-mode operation will depend on the peculiarities of the

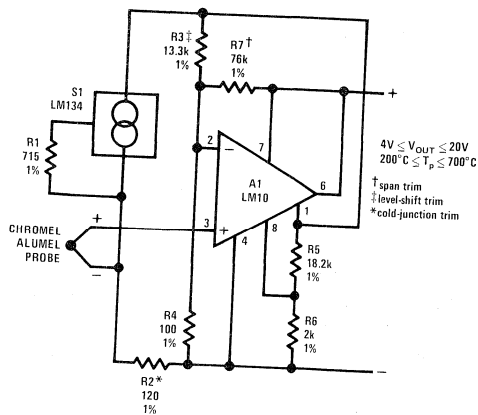


Figure 16. Voltage Transmitter for Thermocouple, Including Cold Junction Compensation

application, although current mode seems to be favored overall. If there is sufficient supply voltage, the dynamic range of both approaches is about equal, provided the transmitter is capable of working at both low voltage and current. This situation could be modified by the voltage and current requirements of the sensor or conditioning circuitry.

With voltage-mode operation, the line resistance can cause error because the DC current that powers the amplifier and sensor circuitry must flow through it. Ground potentials, if they cannot be swamped out with signal swing, would require that twisted pair lines be used. This is not so with current mode.

An important consideration is that cable capacitance does not affect the loop stability of the current-mode amplifier. However, large-amplitude noise appearing across the output can give problems. Figure 17 shows the noise rejections of the LM10. The negative supply rejection applies in current-mode operations with the output connected to  $V^+$ . The rejection in this mode is not overly impressive, but transmission can be reduced by bypassing the load resistor. This done, noise slew limiting is the restricting factor in that excessive slew can give rise to a DC error. The maximum noise amplitude that can be tolerated for a  $100\mu V$  input-referred DC error is plotted in figure 18. These limits are not to be pushed as error increases rapidly above them.

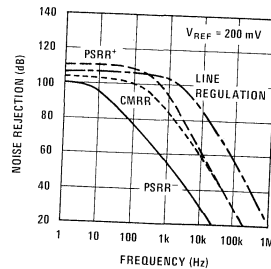


Figure 17. Noise Rejection for the Various Elements of the Circuit

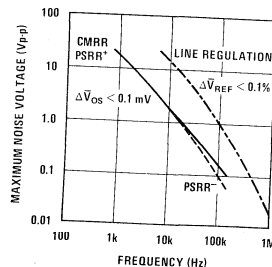


Figure 18. Noise Frequency and Amplitude Required to Give Indicated Error

With voltage-mode, the circuit reacts to capacitive loading like any other op amp. If there are problems, the load should be isolated with a resistor, taking DC feedback from the load and AC feedback from the op amp output. With the LM10, it is also possible to bypass the output with a single, large capacitor ( $20\mu F$  electrolytic) if speed is no consideration.

With bridge sensors, these techniques not only reduce noise problems but only require two leads to both power the bridge and retrieve the signal.

The relevant circuit is shown in figure 19. The op amp is wired for a high-impedance differential input so as not to load the bridge. The reference supplies the offset to put the amplifier in the center of its operating range when the bridge is balanced. It also powers the bridge. The low voltage available from the reference regulator is ideal for driving wire strain gauges that usually have low resistances.

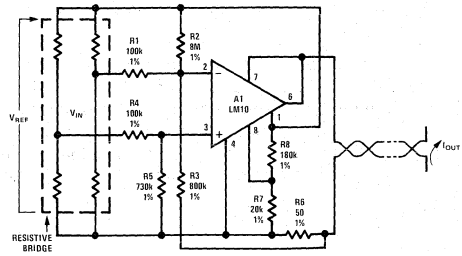


Figure 19. Two-Wire Transmitter for Resistive Bridge

Another form of remote signal processing is shown in figure 20. A logarithmic conversion is made on the output current of a photodiode to compress a four-decade, light-intensity variation into a standard transmission range. The circuit is balanced at mid-range, where R3 should be chosen so that the current through it equals the photodiode current. The log-conversion slope is temperature compensated with R6. Setting the reference output to 1.22V gives a current through R2 that is proportional to absolute temperature, because of D1, so that this level-shift voltage matches the temperature coefficient of R6. C1 has been added so that large area photodiodes with high capacitance do not cause frequency instabilities.

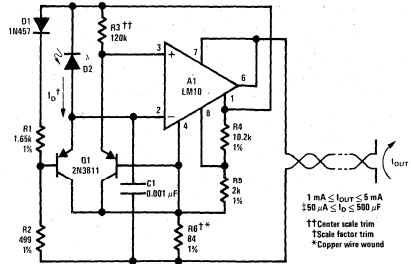


Figure 20. Log Converter/Transmitter for a Photodiode

Figure 21 shows a setup that optically measures the temperature of an incandescent body. It makes use of the shift in the emission spectrum of a black body toward shorter wavelengths as temperature is increased. Optical filters are used to split the emission spectrum, with one photodiode being illuminated by short wavelengths (visible light) and the other by long (infrared). The photocurrents are converted to logarithms by Q1 and Q2. These are subtracted to generate an output that varies as the log of the ratio of the illumination intensities. Thus, the circuit is sensitive to changes in spectral distribution, but not intensity. Otherwise, the circuit is quite similar to that in figure 20.

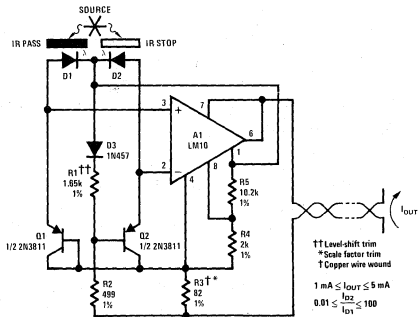


Figure 21. Optoelectric Pyrometer with Transmitter

The laws of physics dictate that the output is not a simple function of temperature, so point-by-point calibration is necessary. Sensitivity for a particular temperature range is optimized with the crossover point of the optical filter, longer wavelengths giving lower temperatures.

Figure 22 shows how a low-drift preamplifier can be added to improve the measurement resolution of a thermocouple. The preamp is powered from the reference regulator, and bridge feedback is used to bias the preamp input within its common-mode range. Cold-junction compensation is provided with the offset voltage set into A1, it being directly proportional to absolute temperature.

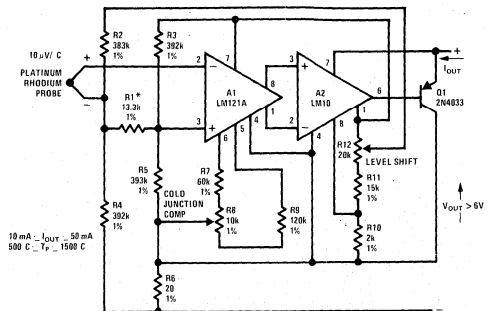


Figure 22. Precision Thermocouple Amplifier/Transmitter

The maximum drift specification for the preamp is  $0.2\mu\text{V}/^\circ\text{C}$ . For this particular circuit, an equal drift component would result for  $0.004\%/^\circ\text{C}$  on the reference,  $0.001\%/^\circ\text{C}$  mismatch on the bridged-feedback resistors (R2-R4) or  $3\mu\text{V}/^\circ\text{C}$  on the op amp offset voltage. The op amp drift might be desensitized by raising the preamp gain (lowering R7-R9), but this would require raising the output voltage of

the reference regulator and the minimum terminal voltage.

In this application, the preamp is run at a lower voltage than standard parts are tested with, and the maximum supply current specified is high. However, there should be no problem with the voltage; and a lower, maximum supply current can be expected at the lower voltage. Even so, some testing may be in order.

### Regulators

The op amp and voltage reference are combined in figure 23 to make a positive voltage regulator. The output can be set between 0.2V and the breakdown voltage of the IC by selecting an appropriate value for R2. The circuit regulates for input voltages within a saturation drop of the output (typically 0.4V @ 20mA and 0.15V @ 5mA). The regulator is protected from shorts or overloads by current limiting and thermal shutdown.

Typical regulation is about 0.05% load and 0.003%/V line. A substantial improvement in regulation can be effected by connecting the op amp as a follower and setting the reference to the desired output voltage. This has the disadvantage that the minimum input-output differential is increased to a little more than a diode drop. If the op amp were connected for a gain of 2, the output could again saturate. But this requires an additional pair of precision resistors.

The regulator in figure 23 could be made adjustable to zero by connecting the op amp to a potentiometer on the reference output. This has the disadvantage that the regulation at the lower voltage settings is not as good as it might otherwise be.

It is also possible to make a negative regulator with this device, as can be seen from figure 24. A discrete transistor is used to level shift the reference current. This increases the minimum operating voltage to about 1.8V.

Output voltage cannot be reduced below 0.85V because of the common-mode limit of the op amp. The minimum input-output differential is equal to the voltage across R1 plus the saturation voltage of Q1, about 400mV.

It is necessary that Q1 have a high current gain, or line regulation and thermal drift will be degraded. For example, with a nominal current gain of 100, a 1% drift will be introduced between -55°C and 125°C. With the device specified, drift contribution should be less than 0.3% over the same range; but operation is limited to 30V on the input.

Floating-mode operation can also be useful in regulator applications. In figure 25, the op amp controls the turn-on voltage of the pass transistor in such a way that it does not see either the output voltage or the supply voltage. Therefore, maximum voltages are limited only by the external transistors.

A three-stage emitter follower is used for the pass transistor primarily to insure adequate bias voltage for the IC under worst-case, high-temperature

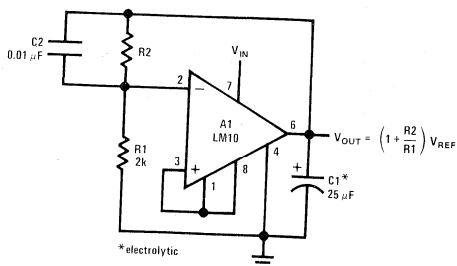


Figure 23. Adjustable Positive Regulator

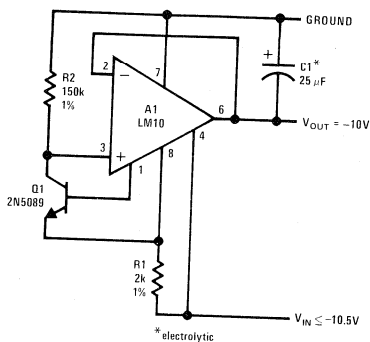


Figure 24. Negative Regulator

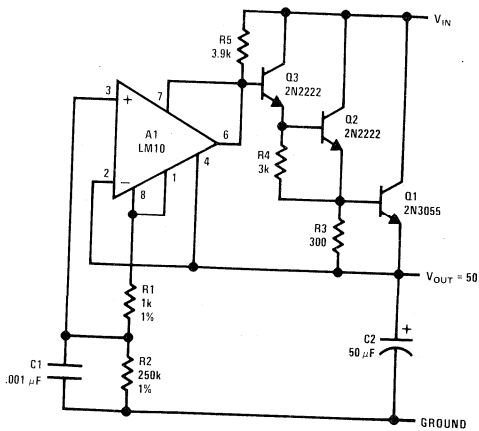


Figure 25. Bootstrapped Regulator

conditions. With lower output currents Q2 and R4 could be replaced with a diode.

Load regulation is better than 0.01%. Worst-case line regulation is better than  $\pm 0.1\%$  for a  $\pm 10V$  change in input voltage. If the op amp output were buffered with a discrete PNP, load and line regulation could be made essentially perfect, except for thermal drift.

Current limiting, although not shown, could easily be provided by the addition of a sense resistor and an NPN transistor. A foldback characteristic could be obtained with two more resistors.

A fully adjustable voltage and current regulator is shown in figure 26. A second IC (A2) is added to provide regulation in the current-limit mode. Both the regulated voltage and the current can be adjusted close to zero.

The circuit has a tendency to overshoot when a short circuit is removed. This is suppressed with Q2, R5 and C3, which limit the rate at which the output can rise. Low-level oscillations at the dropout threshold are eliminated with C2 and R4.

The current-limit amplifier takes about  $100\mu s$  to respond to a shorted output. Therefore, Q6 has been added to limit the peak current during this interval.

With high-voltage regulators, powering the IC through the drive resistor for the pass transistors can become quite inefficient. This is avoided with the circuit in figure 27. The supply current for the IC is derived from Q1. This allows R4 to be increased by an order of magnitude without affecting the dropout voltage.

Selection of the output transistors will depend on voltage requirements. For output voltages above

200V, it may be more economical to cascode lower-voltage transistors.

Figure 28 shows a more detailed circuit for a high-voltage regulator. Foldback current limiting has been added to protect the pass transistors from blowout caused by excessive heating or secondary breakdown. This limiting must be fairly precise to obtain reasonable start-up characteristics while conforming to worst case specifications for the transistors. This accounts for the complexity of the circuit.

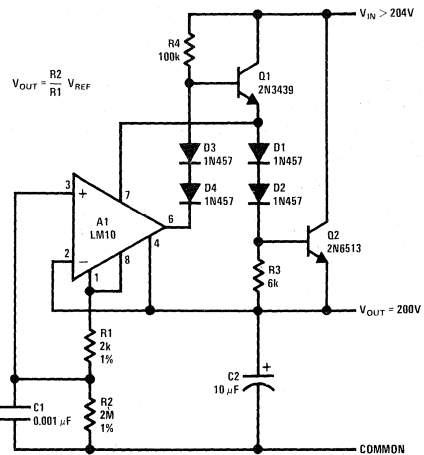


Figure 27. High-Voltage Regulator

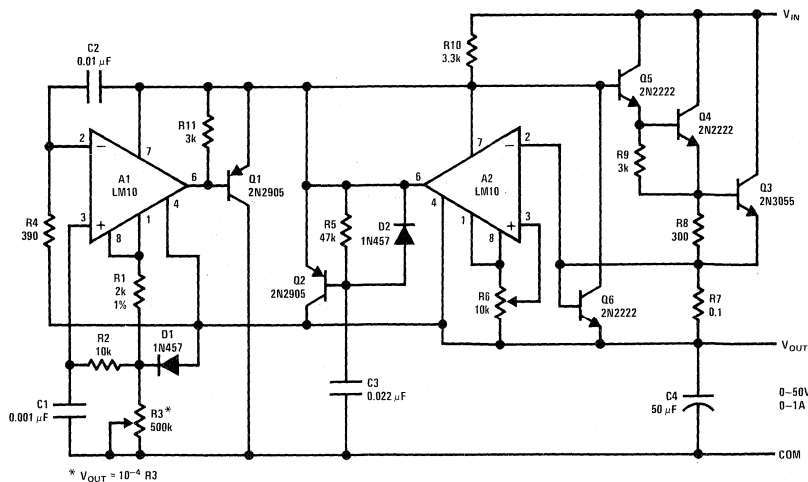


Figure 26. Detailed Schematic of an Adjustable Voltage and Current Regulator

The output current is sensed across R8. This is delivered to the current limit amplifier through R7, across which the foldback potential is developed by R6 with a threshold determined by D4. The values given limit the peak power below 20W and shut off the pass transistors when the voltage across them exceeds 310V. With unregulated input voltages above this value, start-up is initiated solely by the current through R5. Q4 is added to provide some control on current before A2 has time to react.

The design could be considered overly conservative, but this may not be inappropriate considering the state of the art for high-voltage power transistors. Their maximum operating current is in the tens of milliamperes at maximum voltage. Cutting off the power transistor before the maximum input-output voltage differential is reached can cause start-up problems, depending on the nature of the load (those that tend toward a constant-current characteristic being worst).

If a tighter design is required for start-up, the values of R6 and D4 can be altered. In addition, R5 can be lowered, although it may be necessary to add a PNP buffer to A2 in place of D3.

The leakage current of Q3 can be more than several milliamperes. That is why a hard turn-off is provided with D2.

The circuit is stable with an output capacitor greater than about 2 $\mu$ F. Spurious oscillations in current limit are suppressed by C2 and R4, while a strange, latch-mode oscillation coming out of current limit is killed with C1 and R1.

Switching regulators operating directly from the power lines are seeing increased usage not only because of the reduced weight and size when compared to a 60 Hz transformer but also because they operate over a wide voltage range giving a regulated output with reasonable efficiency. Electrical isolation of the load is generally required in these applications for reasons of safety. Therefore, if precise regulation is needed on the secondary, there must be some way of transmitting the error signal back to the primary.

Figure 29 shows a design that provides this function. The IC serves as a reference and error amplifier, transmitting the error signal through an optical coupler. The loop gain may be controlled by the addition of R1, and C1 and R5 may be added to develop the phase lead that is helpful in frequency stabilizing the feedback.

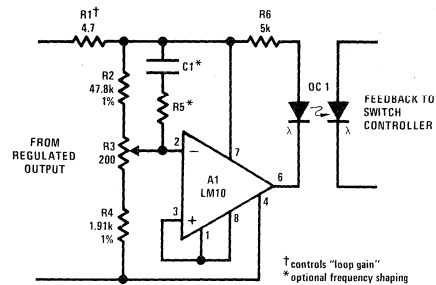


Figure 29. Isolated Sensor for an Off-Line Switching Regulator

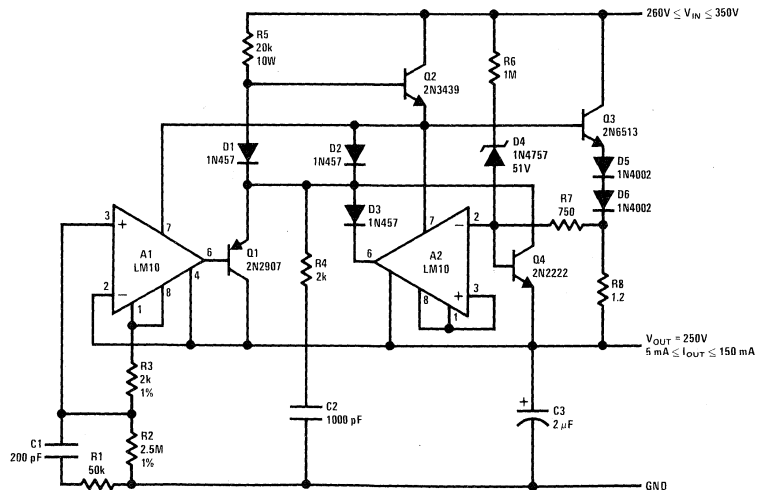


Figure 28. High Voltage Regulator with Foldback Current Limit

## Voltage Level Indicators

In battery-powered circuitry, there is some advantage to having an indicator to show when the battery voltage is high enough for proper circuit operation. This is especially true for instruments that can produce erroneous data.

The battery status indicator drawn in figure 30 is designed for a 9V source. It begins dimming noticeably below 7V and extinguishes at 6V. If the warning of incipient battery failure is not desired, R3 can be removed and the value of R1 halved.

A second circuit that also regulates the current through the light-emitting diode is shown in figure 31. This is important so that adequate current is available at minimum voltage, but excessive current is not drawn at maximum voltage. Current regulation is accomplished by using the voltage on the balance pin (5) as a reference for the op amp. This is controlled at approximately 23mV, independent of temperature, by an internal regulator. When the voltage on the reference-feedback terminal (8) drops below 200mV, the reference output (1) rises to supply the feedback voltage to the op amp through D2, so the LED current drops to zero.

The minimum threshold voltage for these circuits is basically limited by the bias voltage for the LEDs. Typically, this is 1.7V for red, 2V for green and 2.5V for yellow. These two circuits can be made to operate satisfactorily for threshold voltages as low as 2V if a red diode is used. However, the circuit in figure 31 is preferred in that difficulties caused by voltage change across the diode biasing resistor are eliminated.

When operating with a single cell, it is necessary to incorporate switching circuitry to develop sufficient voltage to drive the LED. A circuit that accomplishes this is drawn in figure 32. Basically, it is a voltage-controlled asymmetrical multivibrator with a minimum operating threshold given by

$$V_{TH} = \frac{R4(R1 + R2)}{R1(R3 + R4)} V_{REF} \quad (1)$$

Above this threshold, the flash frequency increases with voltage. This is a far more noticeable indication of a deteriorating battery than merely dimming the LED. In addition, the indicator can be made visible with considerably less power drain. With the values shown, the flash rate is  $1.4 \text{ sec}^{-1}$  at 1.2V with a  $300 \mu\text{A}$  drain and  $5.5 \text{ sec}^{-1}$  at 1.55V with  $800 \mu\text{A}$  drain. Equivalent visibility for continuous operation would require more than 5mA drain.

The maximum threshold voltage of this circuit is limited because the LED can be turned on directly through R5. Once this happens, the full supply voltage is not delivered to R2, which is how the threshold is determined. This problem can be overcome with the circuit illustrated in figure 33. This design repositions the indicator diode, requiring an input voltage somewhat greater than the diode bias voltage needed.

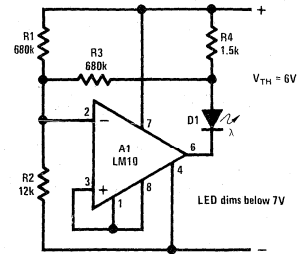


Figure 30. Battery Status Indicator

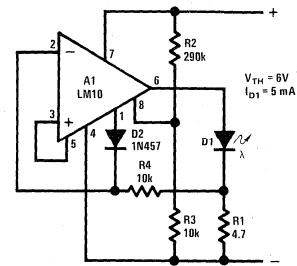


Figure 31. Battery Level Indicator with Regulated LED Current

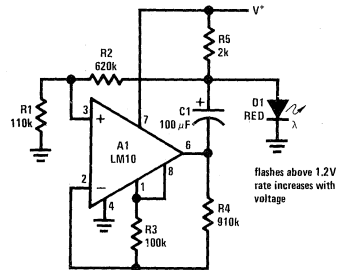


Figure 32. Undervoltage Indicator for Single Cell

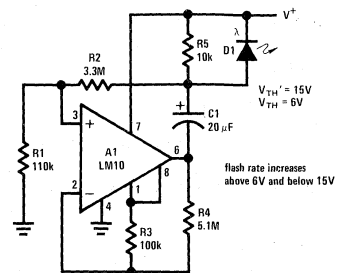


Figure 33. Double-Ended Voltage Monitor

This circuit has the added feature that it can sense an overvoltage condition. The lower activation threshold is given by equation (1), but above a threshold,

$$V_{TH} = \frac{R4(R1 + R2)V_{REF}}{R1(R3 + R4) - R3(R1 + R2)} \quad (2)$$

oscillation again ceases. (Below  $V_{TH}$  the op amp output is saturated negative while above  $V_{TH}$  it is saturated positive.) The flash rate approaches zero near either limit.

The minimum/maximum limits possible with this circuit along with the possibility of estimating the proximity to the limit and the low power drain ( $\sim 500\mu A$ ) make it attractive for a variety of simple, low-cost test equipment. This could include everything from the measurement of power-line voltage to in-circuit testers for digital equipment.

### Meter Circuits

One obvious application for this IC is a meter amplifier. Accuracy can be maintained over a  $15^\circ C$  to  $55^\circ C$  range for a full-scale sensitivity of 10mV and 100nA using the design in figure 34. In fact, initial tests indicate negligible zero drift with 1mV and 10nA sensitivities, although balancing is troublesome with low-cost potentiometers. Offset voltage error is nulled with R5, and the bias current can be balanced out with R4. The zeroing circuits operate from the reference output and are essentially unaffected by changes in battery voltage, so frequent adjustments should not be necessary.

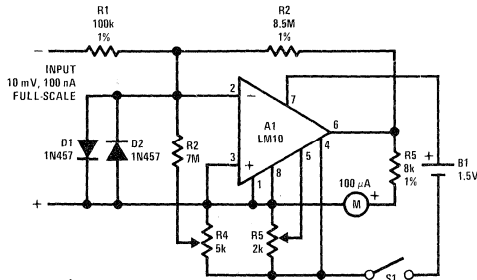


Figure 34. Meter Amplifier

Under overload conditions, the current delivered to the meter is kept well in hand by the limited output swing of the op amp. The same is true for polarity reversals. Input clamp diodes protect the circuit from gross overloads.

Total current drain is under 0.5mA, giving an approximate life of 3-6 months with an "AA" cell and over a year with a "D" cell. With these lifetimes an ON/OFF switch may be unnecessary. A test switch that converts to a battery-test mode may be of greater value.

If the meter amplifier is used in building a multi-meter, the internal reference can also be used in measuring resistance. This would make the usual frequent recalibration with falling cell voltage unnecessary.

A portable light-level meter with a five-decade dynamic range is shown in figure 35. The circuit is calibrated at mid-range with the appropriate illumination by adjusting R2 such that the amplifier output equals the reference and the meter is at center scale. The emitter-base voltage of Q2 will vary with supply voltage; so R4 is included to minimize the effect on circuit balance. If photocurrents less than 50nA are to be measured, it is necessary to compensate the bias current of the op amp.

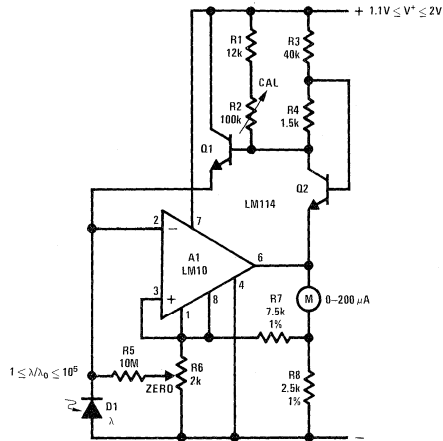


Figure 35. Logarithmic Light-Level Meter

The logging slope is not temperature compensated. With a five-decade response, the error at the scale extremes will be about 40% (a half stop in photography) for a  $\pm 18^\circ C$  temperature change.

If temperature compensation is desired, it is best to use a center-zero meter to introduce the offset, rather than the reference voltage. This done, temperature compensation can be obtained by making the resistor in series with the meter a copper wire-wound unit.

If this design is to be used for photography, it is important to remember that silicon photodiodes are sensitive to near infrared, whereas ordinary film is not. Therefore, an infrared-stop filter is called for. A blue-enhanced photodiode or an appropriate correction filter would also give best results.

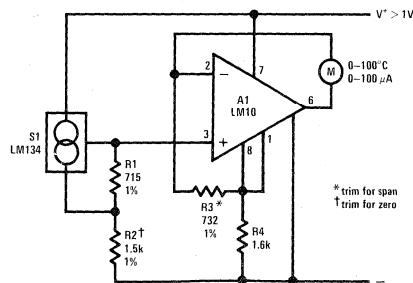


Figure 36. Electronic Thermometer



An electronic thermometer design, useful in the range of  $-55^{\circ}\text{C}$  to  $150^{\circ}\text{C}$ , is shown in figure 36. The sensor, S1, develops a current that is proportional to absolute temperature. This is given the required offset and range expansion by the reference and op amp, resulting in a direct readout in either  $^{\circ}\text{C}$  or  $^{\circ}\text{F}$ .

Although it can operate down to 1V with better than  $0.5^{\circ}\text{C}$  accuracy, the LM134 is not tested below 1.5V. Maverick units were observed to develop a  $1^{\circ}\text{C}$  error going from 1.5V to 1.2V. This should be kept in mind for high-accuracy applications.

The thermocouple transmitter in figure 15 can easily be modified to work with a meter if a broader temperature range is of interest. It would likewise be no great problem adapting resistance or thermistor sensors to this function.

### Audio Circuits

As mentioned earlier, the frequency response of the LM10 is not as good as might be desired. The frequency-response curve in figure 37 shows that only moderate gains can be realized in the audio range. However, considering the reference, there are two independent amplifiers available, so that reasonable overall performance can be obtained.

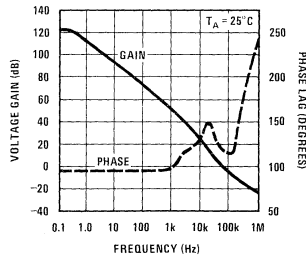


Figure 37. Open Loop Frequency Response

This is illustrated with the microphone amplifier shown in figure 38. The reference, with a 500kHz unity-gain bandwidth, is used as a preamplifier with a gain of 100. Its output is fed through a gain-control potentiometer to the op amp which is connected for

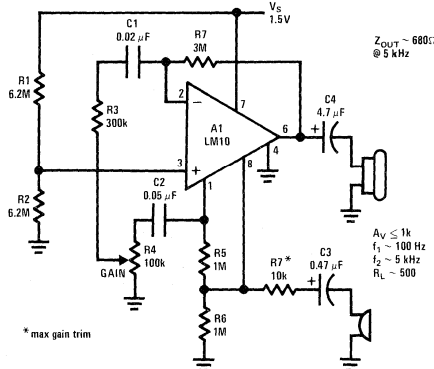


Figure 38. Microphone Amplifier

a gain of 10. The combination gives a 60dB gain with a 10kHz bandwidth, unloaded, and 5kHz loaded at  $500\Omega$ . Input impedance is  $10 \text{ k}\Omega$ .

Potentially, using the reference as a preamplifier in this fashion can cause excess noise. However, because the reference voltage is low, the noise contribution, which adds root-mean-square, is likewise low. The input noise voltage in this connection is  $40 - 50 \text{ nV}/\sqrt{\text{Hz}}$ , about equal to that of the op amp.

One point to observe with this connection is that the signal swing at the reference output is strictly limited. It cannot swing much below 150mV nor closer than 800mV to the supply. Further, the bias current at the reference feedback terminal lowers the output quiescent level and generates an uncertainty in this level. These facts limit the maximum feedback resistance (R5) and require that R6 be used to optimize the quiescent operating voltage on the output. Even so, the fact that limited swing on the preamplifier can reduce maximum output power with low settings on the gain control must be considered.

In this design, no DC current flows in the gain control. This is perhaps an arbitrary rule, designed to insure long life with noise-free operation. If violations of this rule are acceptable, R5 can be used as the gain control with only the bias current for the reference amplifier ( $<75 \text{ nA}$ ) flowing through the wiper. This simplifies the circuit and gives more leeway on getting sufficient output swing from the preamplifier.

The circuit in figure 38 can also be modified to provide two-wire transmission for a microphone output.

### Conclusions

The applications described here show that some truly unique functions can be performed by the LM10 because of the low-voltage capability and floating-mode operation. Among these are accurate, two-terminal comparators that interface directly with most logic forms. They can also drive SCRs in control circuits using low-level sensors like photodiodes or thermocouples, although this was not explored here.

Two-wire transmitters for analog signals were shown to work with a variety of transducers, even to the extent of remotely performing computational functions. These might be used for anything from a microphone preamplifier to a strain gauge measuring stress at some remote location in an aircraft. The power requirements of this IC are modest enough to insure a wide dynamic range and permit operation with lower-voltage supplies.

The IC also proves to be quite useful in regulator circuits, as might be expected from a combined op amp and voltage reference. It makes an efficient series regulator at low voltages. And as a low-level, on-card regulator, it offers greater precision than existing devices. It is also easily applied as a shunt regulator or current regulator.

In the floating mode, it operates with the precision required of laboratory supplies, as either a voltage or

current regulator. Maximum output voltage is limited only by discrete pass transistors, because the control circuit sees, at most, a couple volts. Therefore, output voltages of several hundred volts are entirely practical.

A few examples were given of amplifiers and signal conditioners for portable instruments. Emphasis was placed on single-cell operation as this gives the longest life at lowest cost from the smallest power source. The IC is well suited to single-supply operation, where it can be used in any number of standard applications. This can be put to use in digital systems where some linear functions must be performed. The availability of a reference allows precise level shifting or comparisons even when the supply is poorly regulated. The reference can also be used to create an elevated pseudo-ground so that split-supply techniques can be used.

Even when split supplies are available, the increased output capability (40V @ 20mA) coupled with lower power consumption could well recommend the LM10. This is combined with the more satisfactory fault protection provided by thermal limiting.

#### **Acknowledgement**

The authors would like to thank Dick Wong for his assistance in building and checking out the applications described here.

#### **References**

1. R. J. Widlar, "Low Voltage Techniques," *IEEE J. Solid-State Circuits*, Dec. 1978.

# Super Matched Bipolar Transistor Pair Sets New Standards for Drift and Noise

National Semiconductor  
Application Note 222  
Carl T. Nelson  
July 1979



AN-222 Super Matched Bipolar Transistor Pair Sets New Standards for Drift and Noise

Matched bipolar transistor pairs are a very powerful design tool, yet have received less and less attention over the last few years. This is primarily due to the proliferation of high-performance monolithic circuits which are replacing many designs previously implemented with discrete components. State-of-the-art circuitry, however, is still the realm of the discrete component, especially because of recent improvements in the components themselves.

It has become clear in the past few years that ultimate performance in monolithic transistor pairs was being limited by statistical fluctuations in the material itself and in the processing environment. This led to a matched transistor pair fabricated from many different individual transistors physically located in a manner which tended to average out any residual process or material gradients. At the same time, the large number of parallel devices would reduce random fluctuations by the square root of the number of devices.

The LM194 is the end result. It is a monolithic bipolar matched transistor pair which offers an order-of-magnitude improvement in matching properties and parasitic base and emitter resistance over conventional transistor pairs. This was accomplished without compromising breakdown voltage or current gain. The LM194 is specified at 40V minimum collector-to-emitter breakdown voltage and has a minimum  $h_{FE}$  of 500 at 1mA collector current. Maximum offset voltage is  $50\mu\text{V}$  over a collector current range of  $1\mu\text{A}$  to 1mA. Maximum  $h_{FE}$  mismatch is 2%. Common mode rejection of offset voltage ( $dV_{os}/dV_{cb}$ ) is 124dB minimum. An added benefit of paralleling many transistors is the resultant drop in overall  $r_{bb'}$  and  $r_{ee'}$ , which are  $40\Omega$  and  $0.4\Omega$  respectively. This makes the logarithmic conformity of emitter-base voltage to collector current excellent even at higher current levels where other devices become non-theoretical. In addition, broadband noise is extremely low, especially at higher operating currents.

The key to the success of the LM194 is the nearly one-to-one correlation between measured parameters and those predicted by a theoretical bipolar transistor model. The relationship between

emitter-base voltage and collector current, for instance, is perfectly logarithmic over an extremely wide range of collector currents, deviating in the pA range because of leakage currents and above several milliamperes due to the finite  $0.4\Omega$  emitter resistance. This gives the LM194 a distinct advantage in non-linear designs where true logarithmic behavior is essential to circuit accuracy. Of equal importance is the absolute nature of the logarithmic constant, both between the two halves of the device and from unit to unit. The relationship can be expressed as:

$$V_{BE1} - V_{BE2} = \frac{kT}{q} \ln \left( \frac{I_{C1}}{I_{C2}} \right)$$

This relationship holds true both within a single transistor where  $I_{C1}$  and  $I_{C2}$  represent two different operating currents and between the two halves of the LM194 where collector currents are unbalanced. Of particular importance is the fact that the  $kT/q$  logarithmic constant is an absolute quantity dependent only on Boltzman's constant ( $k$ ), absolute temperature ( $T$ ), and the charge on the electron ( $q$ ). Since these values are independent of processing, there is virtually no variation from unit to unit at a fixed temperature. Lab measurements indicate that the logarithmic constant measured at a 10:1 collector current ratio does not vary more than  $\pm 0.5\%$  from its theoretical value. Applications such as logarithmic converters, multipliers, thermometers, voltage references, and voltage-controlled amplifiers can take advantage of this inherent accuracy to provide adjustment-free precision circuits.

## APPROACHING THEORETICAL NOISE

In many low-level amplifier applications, the limiting factor on performance is noise. With bipolar transistors, the theoretical value for emitter-base voltage noise is a function only of absolute temperature and collector current.

$$e_n = kT \sqrt{\frac{2}{qI_C}} \quad \text{Volts}/\sqrt{\text{Hz}}$$

This formula indicates that voltage noise can be reduced to low levels by simply raising collector

current. In fact, that is exactly what happens until collector current reaches a level where parasitic transistor noise limits any further reduction. This "noise floor" is usually created by and modeled as an equivalent resistor ( $r_{bb'}$ ) in series with the base of the transistor. Low parasitic base resistance is therefore an important factor in ultra-low-noise applications where collector current is pushed to the limits. The  $40\Omega$  equivalent  $r_{bb'}$  of the LM194 is considerably lower than that of other small-signal transistors. In addition, this device has no excess noise at lower current levels and coincides almost exactly with the predicted values. A low-noise design can be done on paper with a minimum of bench testing.

Another noise component in bipolar transistors is base current noise. For any finite source impedance, current noise must be considered as a quadrature addition to voltage noise.

$$\text{total equivalent input voltage noise} = e_N = \sqrt{e_n^2 + (i_n \cdot r_s)^2} \text{ Volts}/\sqrt{\text{Hz}}$$

where  $r_s$  is the source impedance

In the LM194, base current noise is a well-defined function of collector current and can be expressed as:

$$i_n = \sqrt{\frac{2q \cdot I_C}{h_{FE}}} \text{ Amps}/\sqrt{\text{Hz}}$$

To find the collector current which yields the minimum overall equivalent input noise with a given source impedance, the total noise formula can be differentiated with respect to  $I_C$  and set equal to zero for finding a minimum.

$$e_N^2 = e_n^2 + (i_n^2 \cdot r_s^2) + 4kT \cdot r_s$$

$$(4kT \cdot r_s = \text{noise}^2 \text{ of } r_s)$$

$$= \frac{2k^2 \cdot T^2}{q \cdot I_C} + \frac{2q \cdot I_C \cdot r_s^2}{h_{FE}} + 4kT \cdot r_s$$

$$\frac{d(V_N^2)}{d(I_C)} = \frac{-2k^2 \cdot T^2}{q \cdot I_C^2} + \frac{2q \cdot r_s^2}{h_{FE}} = 0$$

$$I_C (\text{optimum}) = \frac{kT}{q} \cdot \frac{\sqrt{h_{FE}}}{r_s}$$

For very low source impedances, the  $40\Omega$   $r_{bb'}$  of the LM194 should be added to  $r_s$  in this calculation. A plot of noise figure versus collector current (see curve) shows that the formula does indeed predict the optimum value. The curves are very shallow, however, and actual current can be varied by 3:1 without losing more than 1 dB noise figure in most cases. This may be a worthwhile tradeoff if low bias current ( $I_C < I_{opt}$ ) or wide bandwidth ( $I_C > I_{opt}$ ) is also important. Figure 1 is a plot of best obtainable noise

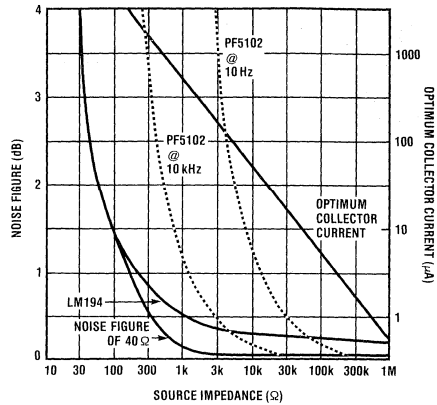


Figure 1. Noise Figure vs Source Impedance

figure versus source impedance for the LM194 and a very low noise junction FET (PF5102). Collector current for the LM194 is optimized for each source impedance and is also plotted on the graph using the right side scale. The PF5102 is operated at a constant 1 mA. It is obvious that the bipolar device gives significantly better noise figures for low source impedances and/or low frequencies. FETs are particularly poor at very low frequencies ( $< 10$  Hz) and offer advantages only for very high source impedances.

## REACTIVE SOURCES

Calculations may also be done to derive an optimum collector current when the signal source is reactive. In this case, upper and lower frequencies ( $f_H$  and  $f_L$ ) must be specified. Also, optimum current is different for an amplifier with a summing junction input ( $Z_{IN} = 0$ ) as compared to a high impedance input ( $Z_{IN} \gg X_C, X_L$ ). The formulas below give optimum collector current for noise within the frequency band  $f_L$  to  $f_H$ . For audio applications, lowest "perceived" noise may be somewhat different because of the variation in sensitivity of the ear to frequencies in the audio range (Fletcher-Munson effect).

Capacitive source into high impedance:

$$I_C (\text{opt}) = \frac{kT}{q} \cdot C \cdot 2\pi \cdot \sqrt{h_{FE}} \cdot \sqrt{f_H \cdot f_L}$$

Capacitive source into summing junction:

$$I_C (\text{opt}) =$$

$$\frac{kT}{q} \cdot \frac{\sqrt{h_{FE}}}{R_i} \sqrt{\frac{4\pi^2 \cdot R_i^2 \cdot C^2 (f_L^2 + f_H^2 + f_L \cdot f_H) + 4\pi \cdot R_i \cdot C \cdot (f_H + f_L)}{3} + \frac{1}{2}}$$

Inductive source into high impedance:

$$I_C(\text{opt}) = \frac{kT}{q} \frac{\sqrt{h_{FE}}}{2\pi \cdot L} \sqrt{\frac{3}{f_L^2 + f_H^2 + f_L \cdot f_H}}$$

Keep in mind that the simple formula for total input-referred noise, though accurate in itself, does not take into account the effects of noise created in additional stages or noise injected from supply lines. In most cases voltage gain of the LM194 stage will be sufficient to swamp out second stage effects. For this to be true, first stage gain must be at least  $3 \cdot v_{n2}/v_N$ , where  $v_{n2}$  is the voltage noise of the second stage and  $v_N$  is the desired total input referred voltage noise. A simple formula for voltage gain of an LM194 stage, assuming no second stage loading, is given by:

$$A_V = \frac{(R_L)(I_C)}{kT/q} \quad \text{where } R_L \text{ is the load resistor}$$

Noise injected from power supplies is an often overlooked problem in low noise designs. This is probably in part due to the use of IC op amps with their high power supply rejection ratio and differential inputs. Many low-noise designs are single-ended and do not enjoy the inherent supply rejection of differential designs. For a single-ended amplifier with its load resistor tied directly to the power supply, noise on the supply must be no higher than  $(R_L \cdot I_C \cdot v_N)/(3kT/q)$  or noise performance will be degraded. For a differential stage (see Figure 2) with the common emitter resistor tied to the negative supply and the collector resistors tied to the positive supply, supply noise is not generally a problem, at least at low frequencies. For this to be true at higher frequencies, the capacitance at the collector nodes must be kept low and balanced. In an unbalanced situation, noise from either supply will feed through unattenuated at higher frequencies where the reactance of the capacitor is much lower than the collector resistance.

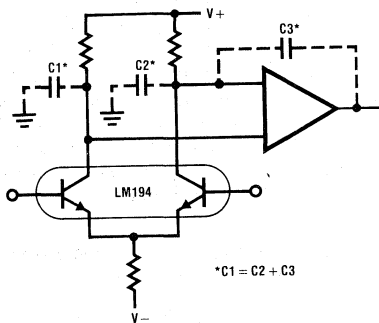


Figure 2. High Frequency Power Supply Rejection

## BANDWIDTH CONSIDERATIONS

Because of its large area, the LM194 has capacitance-limited bandwidth. The  $h_{fe} \cdot f$  product is roughly 0.08 MHz per microampere of collector current, yielding an  $f_t$  of 80 MHz at  $I_C = 1 \text{ mA}$  and 800 kHz at  $I_C = 10 \mu\text{A}$ .

Collector-base capacitance on the LM194 is somewhat higher than ordinary small-signal transistors due to the large device geometry.  $C_{ob}$  is 17 pF at  $V_{CE} = 5 \text{ V}$ . For high gain stages with finite source impedance, the Millering effect of  $C_{ob}$  will usually be the limiting factor on voltage gain bandwidth. At  $I_C = 100 \mu\text{A}$  and  $R_L = 50 \text{ k}\Omega$ , for instance, DC voltage gain will be  $(R_L)(I_C)/(kT/q) = 200$ , but bandwidth will be limited to

$$BW = \frac{kT/q}{(2\pi)(R_L)(I_C)(R_s)(C_{ob})} = 50 \text{ kHz}$$

for a source impedance ( $R_s$ ) of 1 k $\Omega$ .


## LOW NOISE APPLICATIONS

Figures 3 and 4 represent two different approaches to low noise designs. In Figure 3, the LM194 is used to replace the input stage of an LM118 high speed operational amplifier to create an ultra-low-distortion, low-noise RIAA-equalized phono preamplifier. The internal input stage of the LM118 is shut off by tying the unused inputs to the negative supply. This allows the LM194 to be used in place of the internal input stage, avoiding the loop stability problems created when extra stages are added. The stability problem is especially critical in an RIAA circuit where 100% feedback is used at high frequencies. Performance of this circuit exceeds the ability of most test equipment to measure it. As shown in the accompanying chart, Figure 3, harmonic distortion is below the measurable 0.002% level over most of the operating frequency and amplitude range. Noise referred to a 10 mV input signal is 90 dB down, measuring  $0.55 \mu\text{V}_{\text{RMS}}$  and  $70 \text{ pA}_{\text{RMS}}$  in a 20 kHz bandwidth. More importantly, the noise figure is less than 2 dB when the amplifier is used with standard phono cartridges, which have an equivalent wideband (20 kHz) noise of  $0.7 \mu\text{V}$ .<sup>1</sup> Further improvements in amplifier noise characteristics would be of little use because of the noise generated by the cartridge itself.

A special test was performed to check for "Transient Intermodulation Distortion."<sup>2</sup> 10 kHz and 11 kHz were mixed 1:1 at the input to give an RMS output voltage of 2 V (input = 200 mV). The resulting 1 kHz intermodulation product measured at the output was  $80 \mu\text{V}$ . This calculates to 0.004% distortion, an incredibly low level considering that the 1 kHz has 14 dB (5:1) gain with respect to the 10 kHz signal in an RIAA circuit. Of special interest also is the use of all

1. See National's *Audio Handbook*.

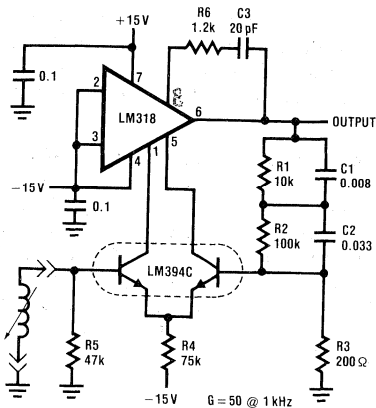2. *The Audio Amateur*, volume VIII, number 1, Feb. 1977.




NOTE: CARTRIDGE IS ASSUMED TO HAVE LESS THAN 5 kΩ DC RESISTANCE. DO NOT CAPACITOR COUPLE THE CARTRIDGE. R1, R2, AND R3 SHOULD BE LOW NOISE METAL FILM RESISTORS.

FREQUENCY (Hz)	TOTAL HARMONIC DISTORTION				
	0.03	0.1	0.3	1.0	5.0
20	< 0.002	< 0.002	< 0.002	< 0.002	< 0.002
100	< 0.002	< 0.002	< 0.002	< 0.002	< 0.002
1k	< 0.002	< 0.002	< 0.002	< 0.002	< 0.002
10k	< 0.002	< 0.002	< 0.002	0.0025	< 0.003
20k	< 0.002	< 0.002	0.004	0.004	0.007
	0.03	0.1	0.3	1.0	5.0

OUTPUT AMPLITUDE (V) RMS

Figure 3. Ultra Low Noise RIAA Phono Preamplifier

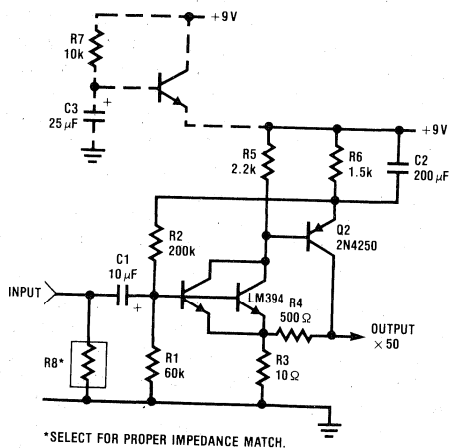

\*SELECT FOR PROPER IMPEDANCE MATCH.

Figure 4. Ultra Low Noise Preamplifier

DC coupling. This eliminates the overload recovery problems associated with coupling and bypass capacitors. Worst case DC output offset voltage is about 1V with a cartridge having 1 kΩ DC resistance.

The single-ended amplifier shown in Figure 4 was designed for source impedances below 250Ω. At this level, the LM194 should be biased at 2.5mA (or higher) collector current. Unfortunately,  $r_{bb'}$ , even at 40Ω, is the limiting factor on noise at these current levels. To achieve better performance, the two halves of the LM194 are paralleled to reduce  $r_{bb'}$  to 20Ω. Total input voltage noise for this design is given by:

$$e_N = \sqrt{4kT(r_{bb'} + R_3) + e_n^2}$$

$$= \sqrt{0.504 + 0.096} = 0.775 \text{ nV}/\sqrt{\text{Hz}}$$

The current noise is  $1.2 \text{ pA}/\sqrt{\text{Hz}}$ , and when this flows through a 250Ω source resistance, it causes an additional  $0.30 \text{ nV}/\sqrt{\text{Hz}}$ . Since the Johnson noise of a 250Ω resistor is  $2.0 \text{ nV}/\sqrt{\text{Hz}}$ , the noise figure is:

$$\text{NF} = 20 \log \frac{\sqrt{(2\text{nV})^2 + (0.3\text{nV})^2 + (0.775\text{nV})^2}}{2\text{nV}} = 0.74 \text{ dB}$$

Several unique features of this circuit should be pointed out. First, it has only one internal capacitor which functions as an AC bypass for both stages. Second, no input stage load resistor bypassing is used, yet the circuit achieves 56dB supply rejection referred to input. The optional supply filter shown in dotted lines improves this by an additional 50dB and is necessary only if supply noise exceeds  $20 \text{ nV}/\sqrt{\text{Hz}}$ . Finally, the problem of AC coupling the 10Ω feedback impedance is eliminated by using a DC biasing scheme which biases both stages simultaneously without relying on feedback from the output.

Harmonic distortion is very low for a "simple" two stage design. At 300mV output, total harmonic distortion measured 0.016%. For normal signal levels of 50mV and below, distortion was lost in the noise floor. Small-signal bandwidth is 3MHz.

An ideal application for this amplifier is as a head pre-amp for moving-coil phono cartridges. These cartridges have very low output impedance ( $< 50 \Omega$  at low frequencies) and have a full-output signal below 1mV. Obviously, the preamp used for such a low signal level must have superb noise properties. The amplifier shown has a total RMS input noise of  $0.11 \mu\text{V}$  in a 20kHz bandwidth, yielding a signal-to-noise ratio of 70dB when used with a 40Ω source impedance at a 0.5mV signal level.

#### LOW-NOISE, LOW-DRIFT INSTRUMENTATION AMPLIFIER HAS WIDE BANDWIDTH

The circuit in Figure 5 is a high-performance instrumentation amplifier for low-noise, low-drift, wide-bandwidth applications. Input noise voltage is

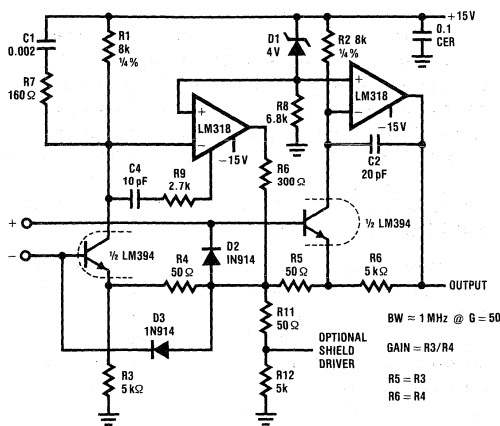


Figure 5. Low Drift-Low Noise Instrumentation Amplifier

$2nV/\sqrt{Hz}$  up to 20kHz, rising to  $3.5nV/\sqrt{Hz}$  at 100kHz. Bandwidth at a gain of 50 is 1 MHz and gain can be varied over the range of 10-100 simply by changing the value of  $R_3$  and  $R_6$ . Input offset voltage drift is determined by the LM194 and the tracking of the ( $R_1$ - $R_2$ ), ( $R_3$ - $R_6$ ), and  $R_4$ - $R_5$ ) pairs. 20 ppm/ $^{\circ}C$  mismatch on all pairs will generate  $1.1 \mu V/^{\circ}C$  referred to input, dominating the drift due to the LM194. Resistor pairs which track to 5 ppm/ $^{\circ}C$  or better are recommended for very low drift applications. Input bias current is about  $1 \mu A$ , rather high for general purpose use, but necessary in this case to achieve wide bandwidth and low noise. The tight matching of the LM194, however, reduces input offset current to 20 nA, and input offset current drift to  $0.5 nA/^{\circ}C$ . Input bias current drift is under  $10 nA/^{\circ}C$ . In terms of source impedance, total input referred voltage drift will be degraded  $1 \mu V/^{\circ}C$  for each  $100 \Omega$  of unbalanced source resistance and  $0.05 \mu V/^{\circ}C$  for each  $100 \Omega$  of balanced source resistance. DC common mode rejection of this amplifier is extremely good, depending mostly on the match of the ratio of  $R_3/R_4$  to  $R_5/R_6$ . 0.1% matching gives better than 90 dB. Rejection will improve with tighter matching and is not limited by the LM194 until CMRR approaches 120 dB. High frequency CMRR is also very good, measuring 80 dB at 20 kHz and 60 dB at 100 kHz. Settling time for a 10V output step is  $1.5 \mu s$  to 0.1%, and  $5 \mu s$  to 0.01%. Distortion with 10V<sub>p-p</sub> output is virtually unmeasurable ( $< 0.002\%$ ) at low frequencies, rising to 0.1% at 50 kHz, and 1% at 200 kHz.

### LOW DRIFT DESIGNS

Offset voltage drift in the LM194 quite closely follows the theoretical value derived by differentiating the logarithmic formula. In other words it is a function only of the original offset voltage. If  $V_{os}$  is

the original room temperature offset voltage, drift of offset as given by differentiation yields:

$$\frac{d(V_{os})}{dT} = \left( \frac{d}{dT} kT/q \ln e^{\frac{V_{os}}{kT/q}} \right) = \frac{V_{os}}{T}$$

At room temperature ( $T = 297^{\circ}K$ ), 1 mV of offset voltage will generate  $1 mV/297^{\circ}K = 3.37 \mu V/^{\circ}C$  drift. The LM194 with a maximum offset voltage of  $50 \mu V$  could be expected to have a maximum offset voltage drift of  $0.17 \mu V/^{\circ}C$ . Lab measurements indicate that it does not deviate from this theoretical drift by more than  $0.1 \mu V/^{\circ}C$ . This means the LM194 can be specified at  $0.3 \mu V/^{\circ}C$  drift without an individual drift test on each device. In addition, if initial offset voltage is zeroed out, maximum drift will be less than  $0.1 \mu V/^{\circ}C$ . The zeroing, of course, must be done in a way that theoretically zeroes drift. This is best done as shown in Figure 6 with a small trimpot used to unbalance collector load resistors. (See National's Application Note AN-3.)


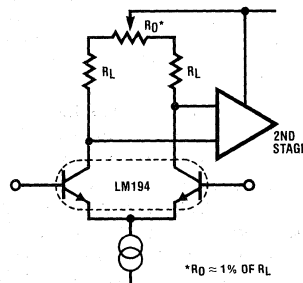


Figure 6. Zeroing Offset and Drift

To obtain optimum performance from such a low-drift device, strict attention must be paid to sources of drift external to the device itself. These include thermocouple effects, mismatch in load-resistor temperature coefficients, second-stage loading, collector leakage, and finite source impedance.

Thermocouple effects in ultra-low-drift amplifiers are often the limiting factor in performance. The copper-to-Kovar (LM194 leads) thermocouple will generate  $35 \mu V/^{\circ}C$ . This sounds extremely high, but is not a problem if all input leads on the LM194 are at the same temperature. For optimum drift performance, the differential lead temperature where copper connects to Kovar should not exceed 0.5 millidegrees per degree change in ambient. If the LM194 is mounted on a printed circuit board, emitter and base leads should be soldered to identical size pads and the package orientation should place emitter and base leads on isothermal lines if any significant power is being dissipated on the board. The board

should be kept in a still-air environment to minimize the effects of circulating air currents. "Still" air is particularly important when the LM194 leads are soldered directly to wires and when low (< 10Hz) noise is critical. Individual wires in air can easily generate a differential end temperature of 10 millidegrees in an ordinary room ambient, even with the wires twisted together. This can cause up to  $1\mu\text{V}_{\text{p-p}}$  fluctuation in offset voltage. The 0.001Hz to 10Hz noise of the LM194 operating differentially at  $100\mu\text{A}$  is typically  $40\text{nV}_{\text{p-p}}$  (see Figure 7), so the thermally generated signal represents a 25:1 degradation of low frequency noise.

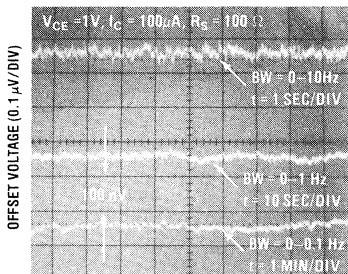

**Figure 7. Low Frequency Noise of Differential Pair.**  
Unit must be in still air environment so that differential lead temperature is held to less than  $0.0003^\circ\text{C}$ .

If the load resistors used to bias the LM194 do not have identical temperature coefficients, they will contribute to offset voltage drift. A  $1\text{ppm}/^\circ\text{C}$  mismatch in resistor drift will generate  $0.026\mu\text{V}/^\circ\text{C}$  drift in the LM194. Resistors with  $10\text{ppm}/^\circ\text{C}$  differential drift will seriously degrade the drift of an otherwise perfect circuit design. Resistors specified to track better than  $2\text{ppm}/^\circ\text{C}$  are available from several manufacturers including Vishay, Julie, RCL, TRW, and Tel Labs.

Source impedance must be considered in a low-drift amplifier since voltage drift at the output can result from drift of the base currents of the LM194. Base current changes at about  $-0.8\%/^\circ\text{C}$ . This is equal to  $2\text{nA}/^\circ\text{C}$  at a collector current of  $100\mu\text{A}$  and an  $h_{\text{FE}}$  of 400. If drift error caused by the changing base current is to be kept to less than  $0.05\mu\text{V}/^\circ\text{C}$ , source unbalance cannot exceed  $25\Omega$  in this example. If a balanced condition exists, source impedance is still limited by the base current mismatch of the LM194. Worst case offset in the base current is 2%, and this offset can have a temperature drift of up to  $2\%/^\circ\text{C}$ , yielding a change in offset current of up to

$$(2\%)(100\mu\text{A})(2\%/^\circ\text{C})/h_{\text{FE}} = 0.1\text{nA}/^\circ\text{C}$$

at a collector current of  $100\mu\text{A}$ . This limits balanced source impedances to  $500\Omega$  at collector currents of  $100\mu\text{A}$  if drift error is to be kept under  $0.05\mu\text{V}/^\circ\text{C}$ . For higher source impedances, collector current must be reduced, or drift trimming must be used.


Collector-leakage effects on drift are generally very low for temperatures below  $50^\circ\text{C}$ . At higher temperatures, leakage can be a factor, especially at low collector currents. At  $70^\circ\text{C}$ , total collector leakage (to base and substrate) is typically  $2\text{nA}$ , increasing at  $0.2\text{nA}/^\circ\text{C}$ . Assuming a 10% mismatch between collector leakages, input-referred drift will be  $0.05\mu\text{V}/^\circ\text{C}$  at a collector current of  $10\mu\text{A}$ , and  $0.005\mu\text{V}/^\circ\text{C}$  at  $100\mu\text{A}$ . At  $125^\circ\text{C}$ , input referred drift will be  $1.5\mu\text{V}/^\circ\text{C}$  and  $0.15\mu\text{V}/^\circ\text{C}$  respectively.

The amplifier used in conjunction with the LM194 may contribute significantly to drift if its own drift characteristics are poor. An LM194 operated with  $2.5\text{V}_{\text{DC}}$  across its load resistors has a voltage gain of approximately 100. If the second stage amplifier has a voltage drift of  $20\mu\text{V}/^\circ\text{C}$  (normal for an amplifier with  $V_{\text{OS}} = 6\text{mV}$ ) the drift referred to the LM194 inputs will be  $0.2\mu\text{V}/^\circ\text{C}$ , a significant degradation in drift. Amplifiers with low drift such as the LM108A or LM308A ( $5\mu\text{V}/^\circ\text{C}$  max) are recommended.

For the ultimate in low drift applications, the residual drift of the LM194 can be zeroed out. This is particularly easy because of the known relationship between a change in room-temperature offset and the resultant change in offset drift. The zeroing technique involves only one oven test to establish initial drift. The drift can then be reduced to below  $0.03\mu\text{V}/^\circ\text{C}$  with a simple room-temperature adjustment. The procedure is as follows: (See Figure 8.)

1. Zero the offset voltage at room temperature ( $T_A$ ).
2. Raise oven temperature to desired level ( $T_H$ ) and measure offset voltage.
3. Bring circuit back to room temperature and adjust offset voltage to  $(V_{\text{OS}} \text{ at } T_H) \cdot (T_A)/(T_H - T_A)$ . ( $T$  is in  $^\circ\text{K}$ .)
4. Re-adjust offset voltage to zero with an external reference source by summing the two signals. (Do not re-adjust the offset of the LM194.)

This technique can be extended to include drift correction for source-generated drift as well since the basic correcting mechanism is independent of the source of drift.

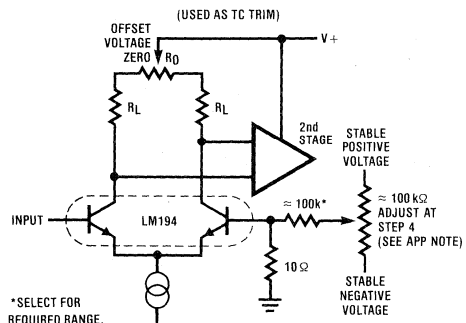

**Figure 8. Correcting for Residual or Source Generated Drift**



## VOLTAGE REFERENCE

Voltage references utilizing the bandgap voltage of silicon were first used 8 years ago, and have since gained wide acceptance in such circuits as the LM109, LM113, LM340, LM117,  $\mu$ A7800, AD580, and REF 01. The theory has been well publicized and is not reiterated here.

The circuit in Figure 9 is a micropower version of a bandgap technique first used by Analog Devices. It operates off a single 2.5V to 6V supply and draws only 25 $\mu$ A idling current. Two AA penlight cells will power the reference for over a year of continuous operation. Maximum output current is 0.5mA, with an output resistance of 0.2 $\Omega$ . Line regulation is  $\sim$ 0.01%/V and output noise is 20 $\mu$ V<sub>RMS</sub> over a 10kHz bandwidth. Temperature drift is less than  $\pm$ 50ppm/ $^{\circ}$ C when the output is trimmed to 1.21V. Much lower drift can be obtained by adjusting the output of each reference to the optimum value. A 1% shift in output voltage changes drift 33ppm/ $^{\circ}$ C. Temperature range is  $-25^{\circ}$ C to  $+100^{\circ}$ C.

The LM194 is the entire reference in this design, supplying both  $V_{BE}$  and  $\Delta V_{BE}$  portions of the reference. One half LM114 delivers a constant bias current to the LM4250. The other half, in conjunction with the 2N4250 PNP, ensures startup of the circuit under worst cast (2.4k) load current.  $R_1$ - $R_2$  and  $R_4$ - $R_5$  should track to 50ppm/ $^{\circ}$ C.  $R_6$  should have a TC of under 250ppm/ $^{\circ}$ C. The circuit is stable for capacitive loads up to 0.047 $\mu$ F.  $C_2$  is optional, for improved ripple rejection.

## STRAIN GAUGE AMPLIFIER

The instrumentation amplifier shown in Figure 10 is an example of an ultra-low-drift design specifically

optimized for strain-gauge applications. A typical strain-gauge bridge has one end grounded and the other driven by a 3-to-10-volt precision voltage reference. The differential output signal of the bridge has a 1.5 to 5 volt common-mode level and a typical full-scale differential signal level of 5–50mV. Source impedance is in the range of 100 $\Omega$  to 500 $\Omega$ , with an impedance imbalance of less than 2%. This amplifier has been specifically optimized for these types of signals. It has a +1V to +10V common mode range, a full scale input of 20mV (1mV to 100mV is possible) and fully balanced inputs with a differential input impedance  $>$  10M $\Omega$ . Common mode input impedance is 100M $\Omega$ . Common mode rejection ratio is 120dB at 60Hz, 114dB at 1kHz, and 94dB at 10kHz referred to input. Power supply rejection at DC is 114dB on the  $V_+$  supply and 108dB on the  $V_-$  supply. Small signal bandwidth is  $>$  50kHz and slew rate is 0.1V/ $\mu$ s. Gain error is determined by the accuracy of  $R_9$ ,  $R_8$ ,  $R_4$ , and  $R_3$ . For the values shown, gain is 500.  $R_3$  can be varied to set gain as desired from 250 (800 $\Omega$ ) to 10,000 (20 $\Omega$ ). Gain non-linearity is  $<$  0.05% for a 10V output and  $<$  0.012% for a 5V output).  $R_7$  is a +0.3%/ $^{\circ}$ C positive-temperature-coefficient wirewound resistor for compensation of gain with temperature. Without this resistor, gain change with temperature is 0.007%/ $^{\circ}$ C. If  $R_7$  is omitted, replace  $R_9$  with 12.4k $\Omega$ .

Input offset voltage drift is determined primarily by resistor mismatches between  $R_1/R_2$  and  $R_5/R_6$ . If either of these ratios drifts by 5ppm/ $^{\circ}$ C, an input offset voltage drift of 0.15 $\mu$ V/ $^{\circ}$ C will be created. Other resistor drifts contribute to gain error only.  $R_{12}$  is used to adjust room temperature offset voltage to zero.

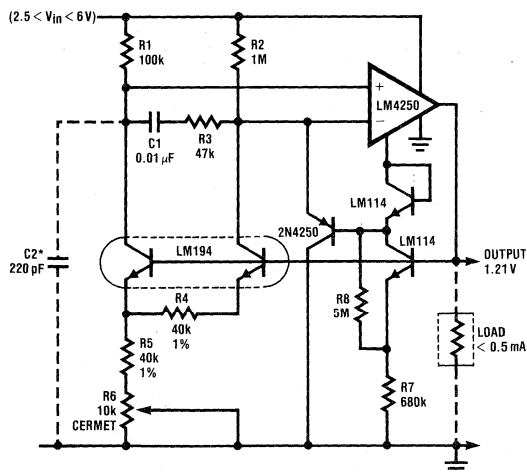


Figure 9. Micropower Reference


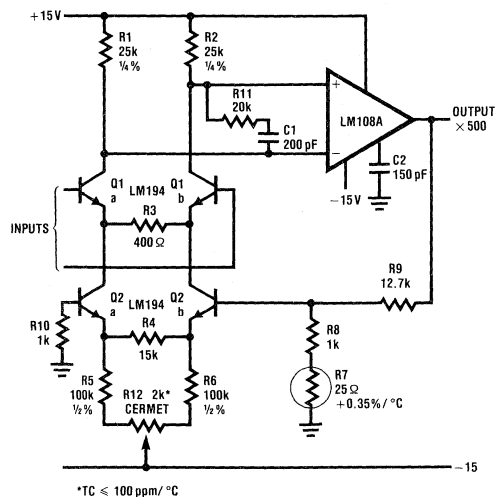


Figure 10. Strain Gauge Instrumentation Amplifier

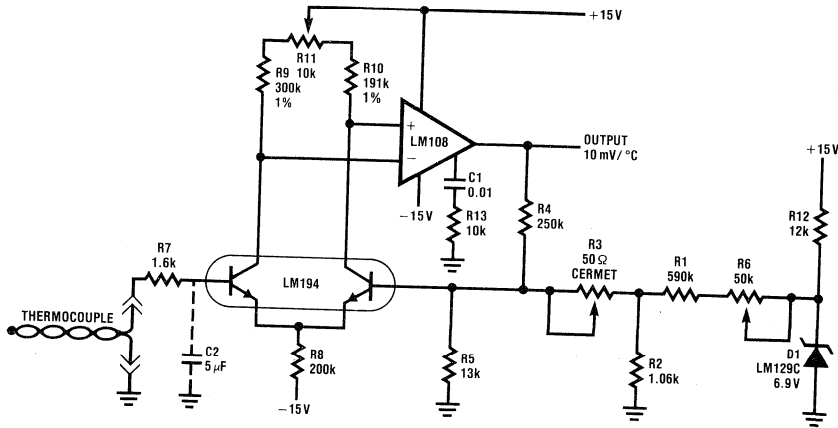

1. Select  $R9 = 300 \text{ k}\Omega$
2. Set  $R10$  equal to  $R9 \cdot e^{-\alpha(1.16 \times 10^4)}$
3.  $R8 = 200\text{k}$
4. Select  $R4$  in the range  $50 \text{ k}\Omega$  to  $250 \text{ k}\Omega$
5.  $R5 = \frac{(R4)(T_1)(\alpha)}{S(T_1 - T_0) - \alpha(T_1)}$
6.  $R2 = \frac{\alpha(R4)(R5)(1 - E^*/100)}{(S - \alpha) \left[ R5 - \frac{\alpha(R4)}{S - \alpha} \right]}$
7.  $R1 = \frac{[(R2) \cdot V_z - \alpha(T_1)]}{\alpha(T_1)} (0.95)$
8.  $R3 = \frac{(E)(R2)}{50}$
9.  $R7 = (R9/R10)(R2)$
10.  $R6 = R1/10$

$E =$  Gain error allowed for ( $\approx 2.5\%$ )

$T_1 =$  Temperature in  $^{\circ}\text{K}$  at which it is desired to have the gain control not interact with the zero control

$T_0 =$  Temperature in  $^{\circ}\text{K}$  at which the desired temperature scale ( $^{\circ}\text{C}$  or  $^{\circ}\text{F}$ ) is equal to zero

$S =$  Required output scale factor. Use  $\text{V}/^{\circ}\text{C}$  even though actual output may be in  $^{\circ}\text{F}$

$V_z =$  Zener reference voltage

$\alpha =$  Thermocouple output in  $\text{V}/^{\circ}\text{C}$

Values shown on schematic are for  $10 \text{ mV}/^{\circ}\text{C}$ .

See below for  $10 \text{ mV}/^{\circ}\text{F}$  values using a Chromel-Alumel thermocouple with room temperature for  $T_1$ .

$R1 = 367\text{k}$ ,  $R2 = 629 \Omega$ ,  $R3 = 30 \Omega$ ,  $R4 = 250\text{k}$ ,  $R5 = 4.08\text{k}$ ,  $R6 = 50\text{k}$ ,  $R7 = 1\text{k}$ ,  $R10 = 191\text{k}$

#### CALIBRATION: \*

- a. Set oven to  $T_1$  and adjust  $R6$  to give proper output (zero adjust).
- b. Raise (or lower) oven to  $T_2$  and adjust  $R3$  to give proper output at  $T_2$  (gain adjust).
- c. Return to room temperature and short thermocouple and  $D1$  to ground. Adjust  $R11$  to give proper output (room ambient) in  $^{\circ}\text{K}$  or  $^{\circ}\text{R}$ . For  $10 \text{ mV}/^{\circ}\text{C}$ , this is  $2.98 \text{ V}$  @  $T_A = 25^{\circ}\text{C}$ . For  $10 \text{ mV}/^{\circ}\text{F}$ , this is  $5.37 \text{ V}$  @  $T_A = 77^{\circ}\text{F}$ .
- d. Remove shorts and re-adjust  $R6$  if necessary to zero output.

Note: Steps C and D can be eliminated if exact cold junction compensation is not required.  $R11$  is simply shorted out. Compensation will be within  $\pm 5\%$  without adjustment ( $\leq 0.05^{\circ}\text{C}/^{\circ}\text{C}$ ).

\*Thermocouple only in oven.

Figure 11. Thermocouple Amplifier with Cold-Junction Compensation

## THERMOCOUPLE AMPLIFIER WITH COLD JUNCTION COMPENSATION

Thermocouple amplifiers need low offset voltage drift, good gain accuracy, low noise, and most importantly, cold-junction compensation. The amplifier in Figure 11 does all that and more. It is specifically designed for ease of calibration so that repeated oven cycling is not required for calibration of gain and zero. Also, no mathematical calculations are required in the calibration procedure.

The circuit is basically a non-inverting amplifier with the gain set to give 10mV/(°F or °C) at the output. This output sensitivity is arbitrary and can be set higher or lower. Cold-junction compensation is achieved by deliberately unbalancing the collector currents of the LM194 so that the resulting input offset voltage drift is just equal to the thermocouple output ( $\alpha$ ) at room temperature. By combining the formulas for offset voltage versus current imbalance and offset voltage drift, the required ratio of collector currents is obtained.

$$\frac{d(V_{os})}{dT} = \frac{V_{os}}{T} = \frac{k}{q} \ln \frac{I_{C1}}{I_{C2}}$$

$$\ln \frac{I_{C1}}{I_{C2}} = \frac{q \cdot V_{os}}{k \cdot T} = \frac{q \cdot \alpha}{k}$$

$$\frac{I_{C1}}{I_{C2}} = e^{\frac{q \cdot \alpha}{k}}$$

( $\alpha$  = thermocouple output in V/°C)

This technique does require that the LM194 be at the same temperature as the thermocouple cold junction. The thermocouple leads should be terminated close to the LM194.

The deliberate offset voltage created across the LM194 inputs must be subtracted out with an external reference which is also used to zero shift the output to read directly in °C or °F. This is done in a special way so that at some arbitrarily selected temperature ( $T_1$ ), the gain adjustment has no effect on zero, vastly simplifying the calibration procedure. Design equations for the circuit are shown with the schematic in descending order of their proper use. Also shown is the calibration procedure, which requires only one oven trip for both gain and zero. Use of the nearest pocket calculator should yield all resistor values in a few minutes. The values shown on the schematic are for a 10mV/°C output with a Chromel-Alumel thermocouple delivering 40 $\mu$ V/°C, with  $T_1$  selected at room temperature (297°K). All resistors except  $R_8$  and  $R_{12}$  should be 1% metal film types for low thermocouple effects (resistors do generate thermocouple voltages if their ends are at different temperatures) and should have low temperature coefficients.  $R_9$  and  $R_{10}$  should track to 10ppm/°C.  $R_3$ ,  $R_6$ , and  $R_{11}$  should not have a TC

higher than 250ppm/°C.  $R_1$ ,  $R_2$ , and  $R_4$  should track to 20ppm/°C.  $C_2$  can be added to reduce spikes and noise from long thermocouple lines.

Input impedance for this circuit is >100M $\Omega$ , so high thermocouple impedance will not affect scale factor. "Zero shift" due to input bias current is approximately 1°C for each 400 $\Omega$  of thermocouple lead resistance with a 40 $\mu$ V/°C thermocouple.

No provision is made for correction of thermocouple non-linearity. This could be accomplished with a slight nonlinearity introduced into  $R_4$  with additional resistors and diodes. Another possibility is to digitize the output and correct the nonlinearity digitally with a ROM programmed for a specific thermocouple type.

## POWER METER

The power meter in Figure 12 is a good example of minimum-parts-count design. It uses only one transistor pair to provide the complete (X):(Y) function. The circuit is intended for 117V<sub>AC</sub>  $\pm$  50V<sub>AC</sub> operation, but can be easily modified for higher or lower voltages. It measures true (non-reactive) power being delivered to the load and requires no external power supply. Idling power drain is only 0.5W. Load current sensing voltage is only 10mV, keeping load voltage loss to 0.01%. Rejection of reactive load currents is better than 100:1 for linear loads. Non-linearity is about 1% full scale when using a 50 $\mu$ A meter movement. Temperature correction for gain is accomplished by using a copper shunt (+0.32%/°C) for load-current sensing. This circuit measures power on negative cycles only, and so cannot be used on rectifying loads.

## LOW COST MATHEMATICAL FUNCTIONS

Many analog circuits require a mathematical function to be performed on one or more signals other than the standard addition, subtraction, or scaling which can be accomplished with resistor networks. The circuits shown in Figures 13 through 15 are examples of low-cost function generating circuits using the LM394 with operational amplifiers. The logarithmic relationship of  $V_{BE}$  to  $I_C$  on the LM394 is utilized in each case to log-antilog the input signals so that addition and subtraction can be used to multiply, divide, square, etc. When transistors are used in this manner, matching is very critical. A 1mV offset in  $V_{BE}$  appears as a 4% of signal error even in the best case where operation is restricted to one quadrant. Parasitic emitter or base resistance ( $r_{ee}$ ,  $r_{bb}$ ) can also seriously degrade accuracy. At  $I_C = 100\mu$ A and  $h_{FE} = 100$ , each ohm of emitter resistance and each 100 $\Omega$  of base resistance will cause 0.4% signal error. Most matched transistor

pairs available today have significant parasitic resistances which severely limit their use in high-accuracy circuits. The LM394, with offset guaranteed below 0.15mV and a typical emitter-referred total parasitic resistance of 0.4Ω gives an order of magnitude improvement in accuracy to nonlinear designs at all current levels.

#### MULTIPLIER/DIVIDER

The circuit in Figure 13 will give an output proportional to the product of the (X) and (Y) inputs divided by the Z input. All inputs must be positive, limiting operation to one quadrant, but this restriction removes the large error terms found in 2- and 4-quadrant designs. In a large percentage of cases, analog signals requiring multiplication are of one polarity only and can be inverted if negative. A nice feature of this design is that all gain errors can be trimmed to zero at one point.  $R_5$  is paralleled with 2.4 MΩ to drop its nominal value 2%.  $R_8$  then gives a ±2% gain trim to account for errors in  $R_1$ ,  $R_2$ ,  $R_5$ ,  $R_7$ , and any offset in  $Q_1$  or  $Q_2$ . For very low level inputs, offset voltage in the LM308s may create large percentage errors referred to input. A simple scheme for offsetting any of the LM308s to zero is shown in dotted lined; the + input of the appropriate LM308 is simply tied to  $R_x$  instead of ground for zeroing. The summing mode of operation on all inputs allows easy scaling on any or all inputs. Simply set the input resistor equal to  $(V_{IN(max)})/(200\mu A)$ .  $V_{OUT}$  is equal to:

$$V_{OUT} = \frac{\left(\frac{X}{R_1}\right)\left(\frac{Y}{R_2}\right)(R_5)}{\frac{Z}{R_7}}$$

Input voltages above the supply voltage are allowed because of the summing mode of operation. Several inputs may be summed at "X," "Y," or "Z."

Proper scaling will improve accuracy by preventing large current imbalances in  $Q_1$  and  $Q_2$ , and by creating the largest possible output swing. Keep in mind that any multiplier scheme must have a reference and this circuit is no different. For a simple (X)·(Y) or (X)/Z function, the unused input must be tied to a reference voltage. Perturbations in this reference will be seen at the output as scale factor changes, so a stable reference is necessary for precision work. For less critical applications, the unused input may be tied to the positive supply voltage, with  $R = V^+/200\mu A$ .

#### SQUARE ROOT

The circuit in Figure 14 will generate the square root function at low cost and good accuracy. The output is a current which may be used to drive a meter directly or be converted to a voltage with a summing junction current-to-voltage converter. The -15V supply is used as a reference, so it must be stable. A 1% change in the -15V supply will give a ½% shift in output reading. No positive supply is required when an LM301A is used because its inputs may be used at the same voltage as the positive supply (ground). The two 1N457 diodes and the 300kΩ resistor are used to temperature compensate the current through the diode-connected ½ LM394.

#### SQUARING FUNCTION

The circuit in Figure 15 will square the input signal and deliver the result as an output current. Full scale input is 10V, but this may be changed simply by changing the value of the 100kΩ input resistor. As in the square root circuit, the -15V supply is used as the reference. In this case, however, a 1% shift in supply voltage gives a 1% shift in output signal. The 150kΩ resistor across the base-emitter of ½ LM394 provides slight temperature compensation of the reference current from the -15V supply. For improved accuracy at low input signal levels, the offset voltage of the LM301A should be zeroed out, and a 100kΩ resistor should be inserted in the positive input to provide optimum DC balance.

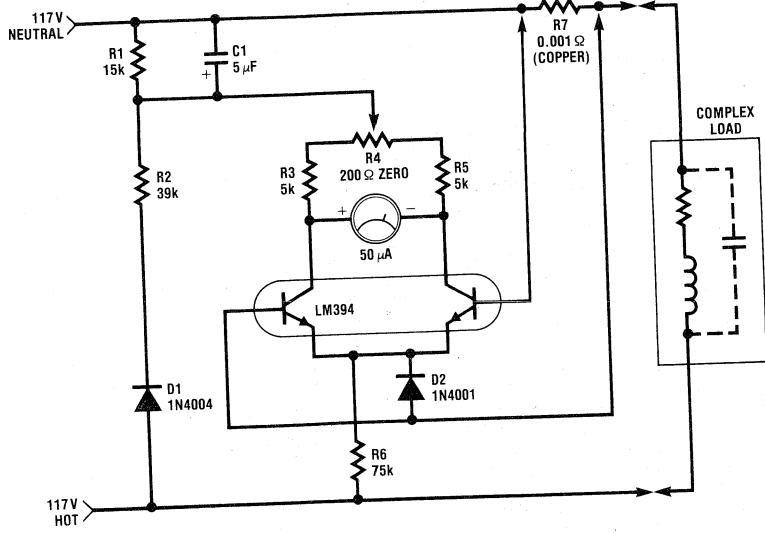


Figure 12. Power Meter (1 kW f.s.)



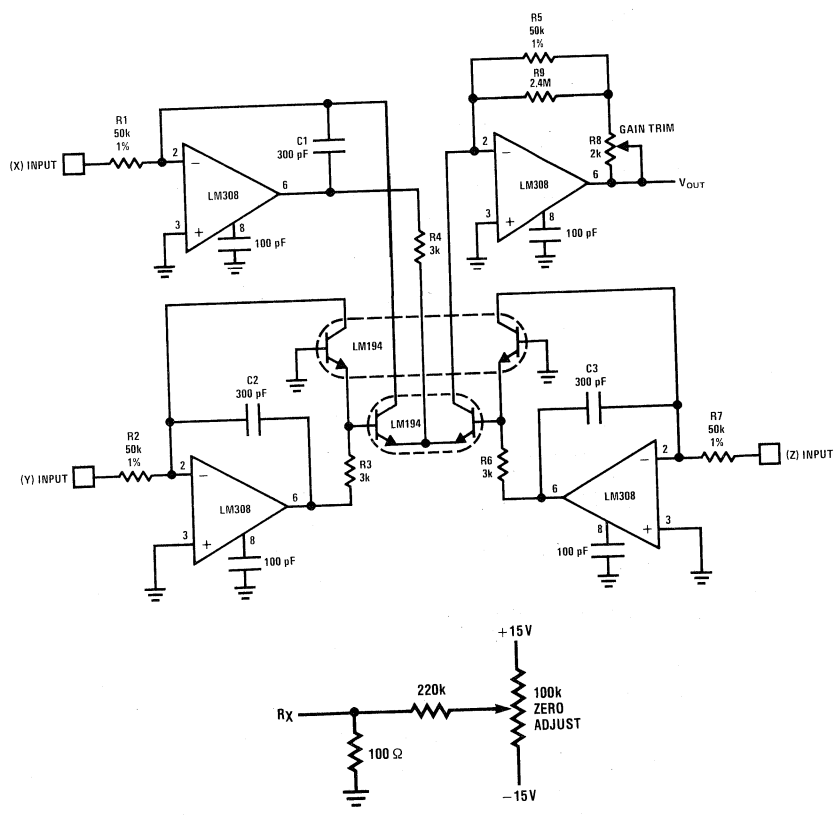


Figure 13. High Accuracy One Quadrant Multiplier/Divider

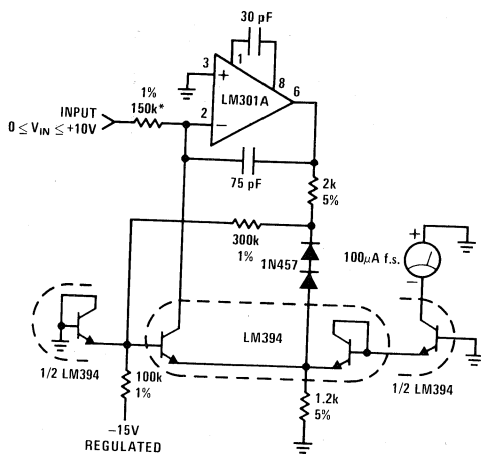

\*TRIM FOR FULL SCALE ACCURACY.

Figure 14. Low Cost Accurate Square Root Circuit  
 $I_{OUT} = 10^{-5} \cdot \sqrt{10 V_{IN}}$

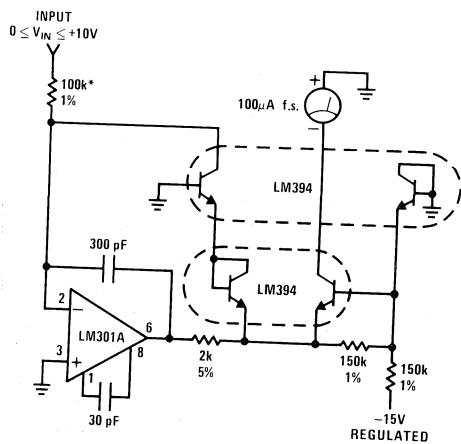

\*TRIM FOR FULL SCALE ACCURACY.

Figure 15. Low Cost Accurate Squaring Circuit  
 $I_{OUT} = 10^{-6} (V_{IN})^2$

# IC Temperature Sensor Provides Thermocouple Cold-Junction Compensation

National Semiconductor  
Application Note 225  
Michael X. Maida  
April 1979



## INTRODUCTION

Due to their low cost and ease of use, thermocouples are still a popular means for making temperature measurements up to several thousand degrees centigrade. A thermocouple is made by joining wires of two different metals as shown in *Figure 1*. The output voltage is approximately proportional to the temperature difference between the measuring junction and the reference junction. This constant of proportionality is known as the Seebeck coefficient and ranges from  $5 \mu\text{V}/^\circ\text{C}$  to  $50 \mu\text{V}/^\circ\text{C}$  for commonly used thermocouples.

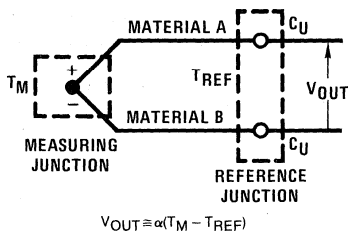


FIGURE 1. Thermocouple

Because a thermocouple is sensitive to a temperature difference, the temperature at the reference junction must be known in order to make a temperature measurement. One way to do this is to keep the reference junction in an ice bath. This has the advantage of zero output voltage at  $0^\circ\text{C}$ , making thermocouple tables usable. A more convenient approach, known as cold-junction compensation, is to add a compensating voltage to the thermocouple output so that the reference junction appears to be at  $0^\circ\text{C}$  independent of the actual temperature. If this voltage is made proportional to temperature with the same constant of proportionality as the thermocouple, changes in ambient temperature will have no effect on output voltage.

An IC temperature sensor such as the LM135/LM235/LM335, which has a very linear voltage vs. temperature characteristic, is a natural choice to use in this compensation circuit. The LM135 operates by sensing the difference of base-emitter voltage of two transistors running at different current levels and acts like a zener diode with a breakdown voltage proportional to absolute temperature at  $10 \text{ mV}/^\circ\text{K}$ . Furthermore, because the LM135 extrapolates to zero output at  $0^\circ\text{K}$ , the temperature coefficient of the compensation circuit can be adjusted at room temperature without requiring any temperature cycling.

## SOURCES OF ERROR

There will be several sources of error involved when measuring temperature with thermocouples. The most

basic of these is the tolerance of the thermocouple itself, due to varying composition of the wire material. Note that this tolerance states how much the voltage vs. temperature characteristic differs from that of an ideal thermocouple and has nothing to do with nonlinearity. Tolerance is typically  $\pm 3/4\%$  of reading for J, K, and T types or  $\pm 1/2\%$  for S and R types, so that a measurement of  $1000^\circ\text{C}$  may be off by as much as  $7.5^\circ\text{C}$ . Special wire is available with half this error guaranteed.

Additional error can be introduced by the compensation circuitry. For perfect compensation, the compensation circuit must match the output of an ice-point-referenced thermocouple at ambient. It is difficult to match the thermocouple's nonlinear voltage vs. temperature characteristic with a linear absolute temperature sensor, so a "best fit" linear approximation must be made. In *Figure 2* this nonlinearity is plotted as a function of temperature for several thermocouple types. The K type is the most linear, while the S type is one of the least linear. When using an absolute temperature sensor for cold-junction compensation, compensation error is a function of both thermocouple nonlinearity and also the variation in ambient temperature, since the straight-line approximation to the thermocouple characteristic is more valid for small deviations.

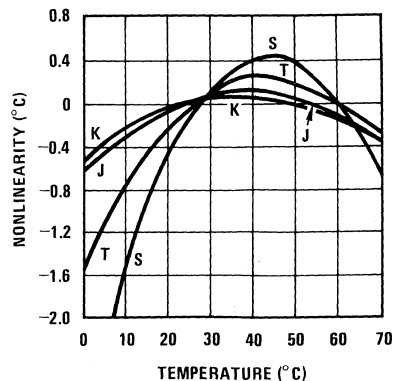


FIGURE 2. Thermocouple Nonlinearity

Of course, increased error results if, due to component inaccuracies, the compensation circuit does not produce the ideal output. The LM335 is very linear with respect to absolute temperature and introduces little error. However, the complete circuit must contain resistors and a voltage reference in order to obtain the proper offset and scaling. Initial tolerances can be trimmed out, but the temperature coefficient of these external components is usually the limiting factor (unless this drift is measured and trimmed out).

## CIRCUIT DESCRIPTION

A single-supply circuit is shown in Figure 3. R3 and R4 divide down the 10 mV/°K output of the LM335 to match the Seebeck coefficient of the thermocouple. The LM329B and its associated voltage divider provide a voltage to buck out the 0°C output of the LM335. To calibrate, adjust R1 so that  $V1 = \alpha T$ , where  $\alpha$  is the Seebeck coefficient\* and T is the ambient temperature in degrees Kelvin. Then, adjust R2 so that V1-V2 is equal to the thermocouple output voltage at the known ambient temperature.

To achieve maximum performance from this circuit the resistors must be carefully chosen. R3 through R6 should be precision wirewounds, Vishay bulk metal or precision metal film types with a 1% tolerance and a temperature coefficient of  $\pm 5$  ppm/°C or better. In addition to having a low TCR, these resistors exhibit low thermal emf when the leads are at different temperatures, ranging from 3  $\mu$ V/°C for the TRW MAR to only 0.3  $\mu$ V/°C for the Vishay types. This is especially important when using S or R type thermocouples that output only 6  $\mu$ V/°C. R7 should have a temperature coefficient of  $\pm 25$  ppm/°C or better and a 1% tolerance. Note that the potentiometers are placed where their absolute resistance is not important so that their TCR is not critical. However, the trim pots should be of a stable cermet type. While multi-turn pots are usually considered to have the best resolution, many modern single-turn pots are just as easy to set to within  $\pm 0.1\%$  of the desired value as the multi-turn pots.

Also single-turn pots usually have superior stability of setting, versus shock or vibration. Thus, good single-turn

cermet pots (such as Allen Bradley type E, Weston series 840, or CTS series 360) should be considered as good candidates for high-resolution trim applications, competing with the more obvious (but slightly more expensive) multi-turn trimpots such as Allen Bradley type RT or MT, Weston type 850, or similar.

With a room temperature adjustment, drift error will be only  $\pm 1/2^\circ\text{C}$  at 70°C and  $\pm 1/4^\circ\text{C}$  at 0°C. Thermocouple nonlinearity results in additional compensation error. The chromel/alumel (type K) thermocouple is the most linear. With this type, a compensation accuracy of  $\pm 3/4^\circ\text{C}$  can be obtained over a 0°C-70°C range. Performance with an iron-constantan thermocouple is almost as good. To keep the error small for the less linear S and T type thermocouples, the ambient temperature must be kept within a more limited range, such as 15°C to 50°C. Of course, more accurate compensation over a narrower temperature range can be obtained with any thermocouple type by the proper adjustment of voltage TC and offset.

Standard metal-film resistors cost substantially less than precision types and may be substituted with a reduction in accuracy or temperature range. Using 50 ppm/°C resistors, the circuit can achieve 1/2°C error over a 10°C range. Switching to 25 ppm resistors will halve this error. Tin oxide resistors should be avoided since they generate a thermal emf of 20  $\mu$ V for 1°C temperature difference in lead temperature as opposed to 2  $\mu$ V/°C for nichrome or 4.3  $\mu$ V/°C for cermet types. Resistor networks exhibit good tracking, with 50 ppm/°C obtainable for thick film and 5 ppm/°C for thin film. In order to obtain the large resistor ratios needed, one can use series and parallel connections of resistors on one or more substrates.

\* See Appendix A for calculation of Seebeck coefficient.

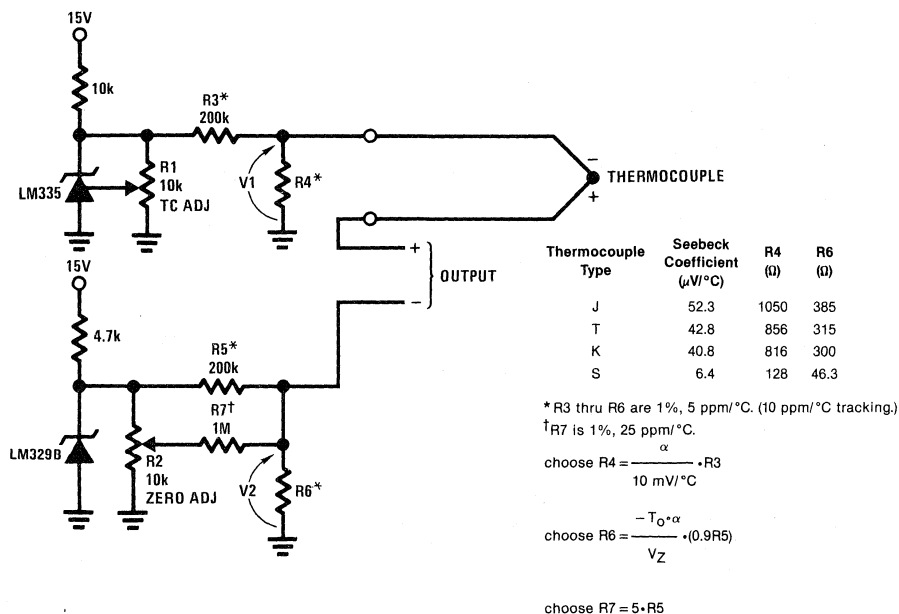


FIGURE 3. Thermocouple Cold-Junction Compensation using Single Power Supply



A circuit for use with grounded thermocouples is shown in Figure 4. If dual supplies are available, this circuit is preferable to that of Figure 3 since it achieves similar performance with fewer low TC resistors. To trim, short out the LM329B and adjust R4 so that  $V_O = \alpha T$ , where  $\alpha$  is the Seebeck coefficient of the thermocouple and T is the absolute temperature. Remove the short and adjust R5 so that  $V_O$  equals the thermocouple output voltage at ambient. A good grounding system is essential here, for any ground differential will appear in series with the thermocouple output.

An electronic thermometer with a 10 mV/°C output from 0°C to 1300°C is seen in Figure 5. The trimming procedure is as follows:

first short out the LM329B, the LM335 and the thermocouple. Measure the output voltage (equal to the input offset voltage times the voltage gain). Then apply a 50 mV input voltage and adjust the GAIN ADJUST pot until the output voltage is 12.25V above the previously measured value. Next, short out the thermocouple again and remove the short across the LM335. Adjust the TC ADJUST pot so that the output voltage equals 10 mV/°K times the absolute temperature. Finally, remove the short across the LM329B and adjust the ZERO ADJUST pot so that the output voltage equals 10 mV/°C times the ambient temperature in °C.

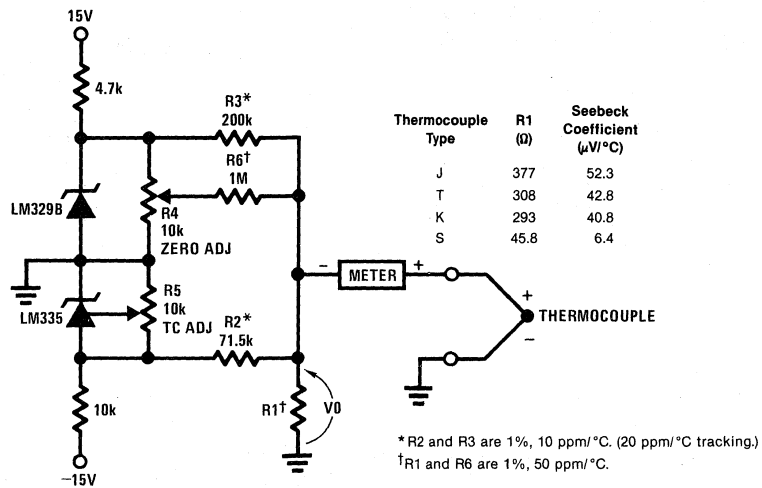


FIGURE 4. Cold-Junction Compensation for Grounded Thermocouple

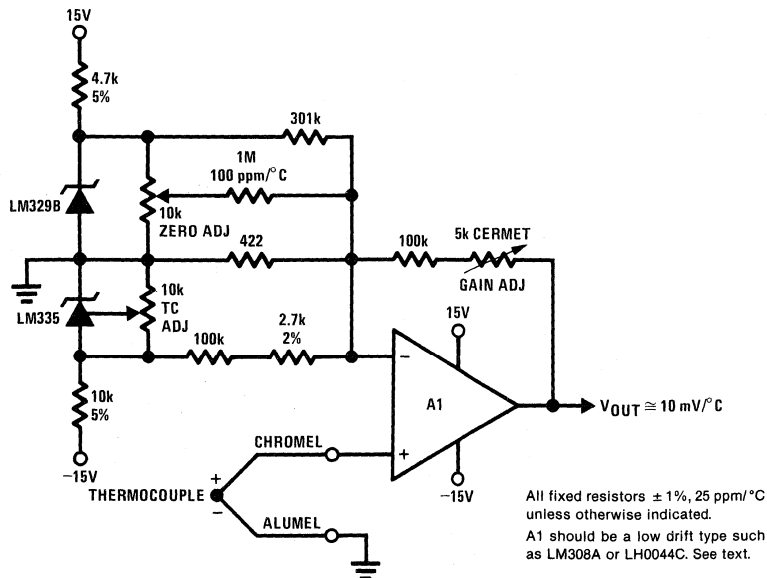


FIGURE 5. Centigrade Thermometer with Cold-Junction Compensation

The error over a 0°C to 1300°C range due to thermocouple nonlinearity is only 2.5% maximum. Table I shows the error due to thermocouple nonlinearity as a function of temperature. This error is under 1°C for 0°C to 300°C but is as high as 17°C over the entire range. This may be corrected with a nonlinear shaping network. If the output is digitized, correction factors can be stored in a ROM and added in via hardware or software.

The major cause of temperature drift will be the input offset voltage drift of the op amp. The LM308A has a specified maximum offset voltage drift of 5  $\mu\text{V}/^\circ\text{C}$  which will result in a 1°C error for every 8°C change in ambient. Substitution of an LH0044C with its 1  $\mu\text{V}/^\circ\text{C}$  maximum offset voltage drift will reduce this error to 1°C per 40°C. If desired, this temperature drift can be trimmed out with only one temperature cycle by following the procedure detailed in Appendix B.

#### CONSTRUCTION HINTS

The LM335 must be held isothermal with the thermocouple reference junction for proper compensation. Either of the techniques of *Figures 6a or 6b* may be used.

Hermetic ICs use Kovar leads which output 35  $\mu\text{V}/^\circ\text{C}$  referenced to copper. In the circuit of *Figure 5*, the low level thermocouple output is connected directly to the op amp input. To avoid this causing a problem, both input leads of the op amp must be maintained at the same temperature. This is easily achieved by terminating both leads to identically sized copper pads and keeping them away from thermal gradients caused by components that generate significant heat.


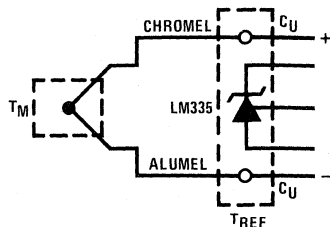


FIGURE 6a

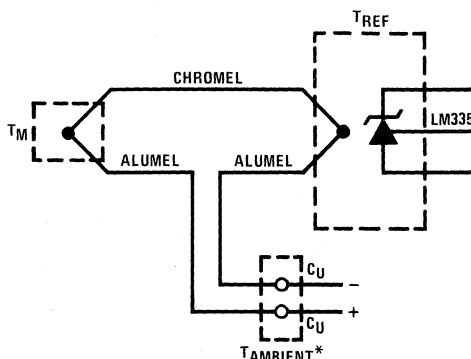

\*Has no effect on measurement.

FIGURE 6b

FIGURE 6. Methods for Sensing Temperature of Reference Junction

TABLE I. NONLINEARITY ERROR OF THERMOMETER USING TYPE K THERMOCOUPLE (SCALE FACTOR 25.47°C/ $\mu\text{V}$ )

°C	Error (°C)	°C	Error (°C)
10	-0.3	200	-0.1
20	-0.4	210	-0.2
30	-0.4	220	-0.4
40	-0.4	240	-0.6
50	-0.3	260	-0.5
60	-0.2	280	-0.4
70	0	300	-0.1
80	0.2	350	1.2
90	0.4	400	2.8
100	0.6	500	7.1
110	0.8	600	11.8
120	0.9	700	15.7
130	0.9	800	17.6
140	0.9	900	17.1
150	0.8	1000	14.0
160	0.7	1100	8.3
170	0.5	1200	-0.3
180	0.3	1300	-13
190	0.1		

Before trimming, all components should be stabilized. A 24-hour bake at 85°C is usually sufficient. Care should be taken when trimming to maintain the temperature of the LM335 constant, as body heat nearby can introduce significant errors. One should either keep the circuit in moving air or house it in a box, leaving holes for the trimpots.

### CONCLUSION

Two circuits using the LM335 for thermocouple cold-junction compensation have been described. With a single room temperature calibration, these circuits are accurate to  $\pm 3/4^\circ\text{C}$  over a  $0^\circ\text{C}$  to  $70^\circ\text{C}$  temperature range using J or K type thermocouples. In addition, a thermocouple amplifier using an LM335 for cold-junction compensation has been described for which worst case error can be as low as  $1^\circ\text{C}$  per  $40^\circ\text{C}$  change in ambient.

### APPENDIX A DETERMINATION OF SEEBECK COEFFICIENT

Because of the nonlinear relation of output voltage vs. temperature for a thermocouple, there is no unique value of its Seebeck coefficient  $\alpha$ . Instead, one must approximate the thermocouple function with a straight line and determine  $\alpha$  from the line's slope for the temperature

range of interest. On a graph, the error of the line approximation is easily visible as the vertical distance between the line and the nonlinear function. Thermocouple nonlinearity is not so gross, so that a numerical error calculation is better than the graphical approach.

Most thermocouple functions have positive curvature, so that a linear approximation with minimum mean-square error will intersect the function at two points. As a first cut, one can pick these points at the 1/3 and 2/3 points across the ambient temperature range. Then calculate the difference between the linear approximation and the thermocouple.<sup>†</sup> This error will usually then be a maximum at the midpoint and endpoints of the temperature range. If the error becomes too large at either temperature extreme, one can modify the slope or the intercept of the line. Once the linear approximation is found that minimizes error over the temperature range, use its slope as the Seebeck coefficient value when designing a cold-junction compensator.

An example of this procedure for a type S thermocouple is shown in Table II. Note that picking the two intercepts (zero error points) close together results in less error over a narrower temperature range.

<sup>†</sup> A collection of thermocouple tables useful for this purpose is found in the Omega Temperature Measurement Handbook published by Omega Engineering, Stamford, Connecticut.

TABLE II. LINEAR APPROXIMATIONS TO TYPE S THERMOCOUPLE

Centigrade Temperature	Type S Thermocouple Output ( $\mu\text{V}$ )	Approximation #1 Zero Error at 25°C and 60°C			Approximation #2 Zero Error at 30°C and 50°C		
		Linear Approx.	Error		Linear Approx.	Error	
			$\mu\text{V}$	$^\circ\text{C}$		$\mu\text{V}$	$^\circ\text{C}$
0°	0	-17	-17	-2.7°	-16	-16	-2.8°
5°	27	15	-12	-1.9°	16	-11	-1.7°
10°	55	46	-9	-1.4°	47	-8	-1.3°
15°	84	78	-6	-0.9°	78	-6	-0.9°
20°	113	110	-3	-0.5°	110	-3	-0.5°
25°	142	142	0	0	142	-1	-0.2°
30°	173	174	1	0.2°	173	0	0
35°	203	206	3	0.5°	204	1	0.2°
40°	235	238	3	0.5°	236	1	0.2°
45°	266	270	4	0.6°	268	2	0.3°
50°	299	301	2	0.3°	299	0	0
55°	331	333	2	0.3°	330	-1	-0.2°
60°	365	365	0	0	362	-3	-0.5°
65°	398	397	-1	-0.2°	394	-4	-0.6°
70°	432	429	-3	-0.5°	425	-7	-1.1°
		$\alpha = 6.4 \mu\text{V}/^\circ\text{C}$			$\alpha = 6.3 \mu\text{V}/^\circ\text{C}$		
		0.6°C error for 20°C < T < 70°C			0.3°C error for 25°C < T < 50°C		

Note: Error is the difference between linear approximation and actual thermocouple output in  $\mu\text{V}$ . To convert error to  $^\circ\text{C}$ , divide by Seebeck coefficient.

## APPENDIX B

### TECHNIQUE FOR TRIMMING OUT OFFSET DRIFT

Short out the thermocouple input and measure the circuit output voltage at 25 °C and at 70 °C. Calculate the output voltage temperature coefficient,  $\beta$  as shown.

$$\beta = \frac{V_{OUT}(70^{\circ}\text{C}) - V_{OUT}(25^{\circ}\text{C})}{45^{\circ}\text{K}} \text{ in mV/}^{\circ}\text{K}$$

Next, short out the LM329B and adjust the TC ADJ pot so that  $V_{OUT} = (20 \text{ mV/}^{\circ}\text{K} - \beta) \times 298^{\circ}\text{K}$  at 25 °C. Now remove the short across the LM329B and adjust the ZERO ADJUST pot so that  $V_{OUT} = 246 \text{ mV}$  at 25 °C (246 times the 25 °C output of an ice-point-referenced thermocouple).

This procedure compensates for all sources of drift, including resistor TC, reference drift ( $\pm 20 \text{ ppm/}^{\circ}\text{C}$  maximum for the LM329B) and op amp offset drift. Performance will be limited only by TC nonlinearities and measurement accuracy.

### REFERENCES

R.C. Dobkin, "Low Drift Amplifiers," National Semiconductor LB-22, June 1973.

Carl T. Nelson, "Super Matched Bipolar Transistor Pair Sets New Standards for Drift and Noise," National Semiconductor AN-222, February 1979.

# The A/D Easily Allows Many Unusual Applications

National Semiconductor  
Application Note 233  
July 1980



## Accommodation of Arbitrary Analog Inputs

Two design features of the ADC0801 series of A/D converters provide for easy solutions to many system design problems. The combination of differential analog voltage inputs and a voltage reference input which can range from near zero to  $5V_{DC}$  are key to these application advantages.

In many systems the analog signal which has to be converted does not range clear to ground ( $0.00V_{DC}$ ) nor does it reach up to the full supply or reference voltage value. This presents two problems: 1) a "zero-offset" provision is needed — and this may be volts, instead of the few millivolts which are usually provided; and 2) the "full scale" needs to be adjusted to accommodate this reduced span. ("Span" is the actual range of the analog input signal, from  $V_{INMIN}$  to  $V_{INMAX}$ .) This is easily handled with the converter as shown in Figure 1.

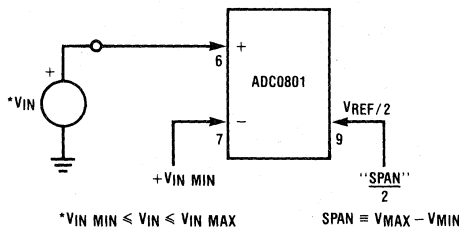


Figure 1. Providing Arbitrary Zero and Span Accommodation

Note that when the input signal,  $V_{IN}$ , equals  $V_{INMIN}$  the "differential input" to the A/D is zero volts and therefore a digital output code of zero is obtained. When  $V_{IN}$  equals  $V_{INMAX}$ , the "differential input" to the A/D is equal to the "span" (for reference applications convenience, there is an internal gain of two to the voltage which is applied to pin 9, the  $V_{REF/2}$  input), therefore the A/D will provide a digital full scale. In this way a wide range of analog input voltages can be easily accommodated.

An example of the usefulness of this feature is when operating with ratiometric transducers which do not output the complete supply voltage range. Some, for example, may output 15% of the supply voltage for a zero reading and 85% of the supply for a full scale reading. For this case, 15% of the supply should be applied to the  $V_{IN(-)}$  pin and the  $V_{REF/2}$  pin should be biased at one-half of the span, which is  $\frac{1}{2}(85\% - 15\%)$  or 35% of the supply. This properly shifts the zero and adjusts the full scale for this application. The  $V_{IN(-)}$  input can be provided by a resistive divider which is driven by the power supply voltage and the  $V_{REF/2}$  pin should be driven by an op amp. This op amp can be a unity-gain voltage follower which also obtains an input voltage from a resistive divider. These can be combined as shown in Figure 2.

This application can allow obtaining the resolution of a greater than 8-bit A/D. For example, 9-bit performance with the 8-bit converter is possible if the span of the analog input voltage should only use one-half of the available 0V to 5V span. This would be a span of approximately 2.5V which could start anywhere over the range of 0V to  $2.5V_{DC}$ .

The RC network on the output of the op amp of Figure 2 is used to isolate the transient displacement current demands of the  $V_{REF/2}$  input from the op amp.

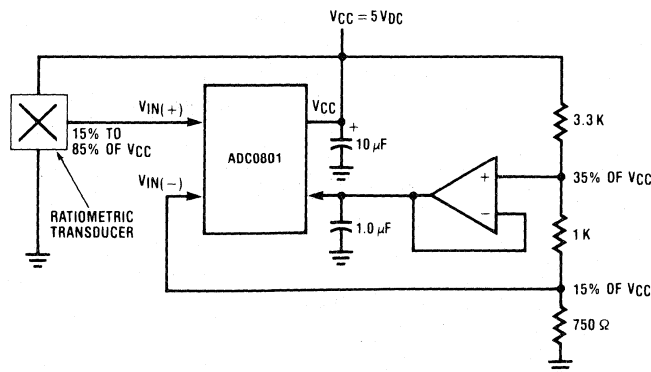


Figure 2. Operating with a Ratiometric Transducer which Outputs 15% to 85% of  $V_{CC}$

## Limits of $V_{REF}/2$ Voltage Magnitude

A question arises as to how small in value the span can be made. An ADC0801 part is shown in Figure 3 where the  $V_{REF}/2$  voltage is reduced in steps: from A), 2.5V (for a full scale reading of 5V); to B), 0.625V (for a full scale reading of 1.25V — this corresponds to the resolution of a 10-bit converter over this restricted range); to C), 0.15625V (for a full scale reading of 0.3125V — which corresponds to the resolution of a 12-bit converter). Note that at 12 bits the linearity error has increased to  $\frac{1}{2}$  LSB.

For these reduced reference applications the offset voltage of the A/D has to be adjusted as the voltage value of the LSB changes from 20mV to 5mV and finally to 1.25mV as we go from A) to B) to C). This offset adjustment is easily combined with the setting of the  $V_{INMIN}$  value at the  $V_{IN(-)}$  pin.

Operation with reduced  $V_{REF}/2$  voltages increases the requirement for good initial tolerance of the reference voltage (or requires an adjustment) and also the allowed changes in the  $V_{REF}/2$  voltage over temperature are reduced.

An interesting application of this reduced reference feature is to directly digitize the forward voltage drop of a silicon diode as a simple digital temperature sensor.

### A 10-Bit Application

This analog flexibility can be used to increase the resolution of the 8-bit converter to 10 bits. The heart of the idea is shown in Figure 4. The two extra bits are provided by the 2-bit external DAC (resistor string) and

the analog switch, SW1. Note that the  $V_{REF}/2$  pin of the converter is supplied with  $\frac{1}{8}V_{REF}$  so each of the four spans which are encoded will be:

$$2 \times \frac{1}{8} V_{REF} = \frac{1}{4} V_{REF}$$

In an actual implementation of this circuit, the switch would be replaced by an analog multiplexer (such as the CD4066 quad bilateral switch) and a microprocessor would be programmed to do a binary search for the two MS bits. These two bits plus the 8 LSBs provided by the A/D give the 10-bit data. For a particular application, this basic idea can be simplified to a 1-bit ladder to cover a particular range of analog input voltages with increased resolution. Further, there may exist *a priori* knowledge by the CPU which could locate the analog signal to within the 1 or 2 MSBs without requiring a search algorithm.

### A Microprocessor Controlled Voltage Comparator

In applications where set points (or "pick points") are set up by analog voltages, the A/D can be used as a comparator to determine whether an analog input is greater than or less than a reference DC value. This is accomplished by simply grounding the  $V_{REF}/2$  pin (to provide maximum resolution) and applying the reference DC value to the  $V_{IN(-)}$  input. Now with the analog signal applied to the  $V_{IN(+)}$  input, an all zeros code will be output for  $V_{IN(+)}$  less than the reference voltage and an all ones code for  $V_{IN(+)}$  greater than the

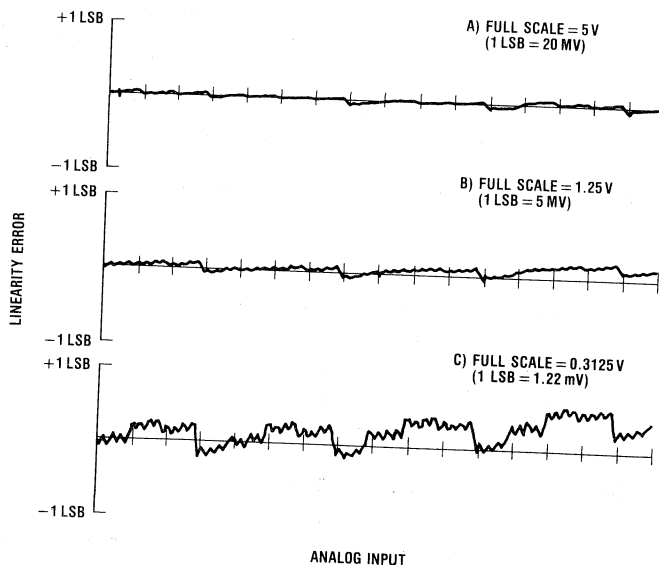


Figure 3. Linearity Error for Reduced Analog Input Spans

reference voltage. This reduces the computational loading of the CPU. Further, using analog switches, a single A/D can encode some analog input channels in the "normal" way and can provide this comparator operation, under microprocessor control, for other analog input channels.

#### DACs Multiply and A/Ds Divide

Computation can be directly done with converter components to either increase the speed or reduce the loading on a CPU. It is rather well known that DACs multiply — and for this reason many are actually called "MDACs" to signify "multiplying DAC." An analog product voltage is provided as an output signal from a DAC for a hybrid pair of input signals — one is analog (the  $V_{REF}$  input) and the other is digital.

The A/D provides a digital quotient output for two analog input signals. The numerator or the dividend is the normal analog input voltage to the A/D and the denominator or the divisor is the  $V_{REF}$  input voltage.

High speed computation can be provided external to the CPU by either or both of these converter products. DACs are available which provide full 4-quadrant multiplications (the MDACs and MICRO-DACs™), but A/Ds are usually limited to only one quadrant.

#### Combine Analog Self-Test with Your Digital Routines

A new innovation is the digital self-test and diagnostic routines which are being used in equipment. If an 8-bit A/D converter and an analog multiplexer are added, these testing routines can then check all power supply

voltage levels and other set point values in the system. This is a major application area for the new generation converter products.

#### Control Temperature Coefficients with Converters

The performance of many systems can be improved if voltages within the system can be caused to change properly with changes in ambient temperature. This can be accomplished by making use of low cost 8-bit digital to analog converters (DACs) which are used to introduce a "dither" or small change about the normal operating values of DC power supplies or other voltages within the system. Now, a single measurement of the ambient temperature and one A/D converter with a MUX can be used by the microprocessor to establish proper voltage values for a given ambient temperature. This approach easily provides non-linear temperature compensation and generally reduces the cost and improves the performance of the complete system.

#### Save an Op Amp

In applications where an analog signal voltage which is to be converted may only range from, for example,  $0V_{DC}$  to  $500mV_{DC}$ , an op amp with a closed-loop gain of 10 is required to allow making use of the full dynamic range ( $0V_{DC}$  to  $5V_{DC}$ ) of the A/D converter. An alternative circuit approach is shown in Figure 5. Here we, instead, attenuate the magnitude of the reference voltage by 10:1 and apply the 0 to 500 mV signal directly to the A/D converter. The  $V_{IN(-)}$  input is now used for a  $V_{OS}$  adjust, and due to the "sampled-data" operation of the A/D there is essentially no  $V_{OS}$  drift with temperature changes.

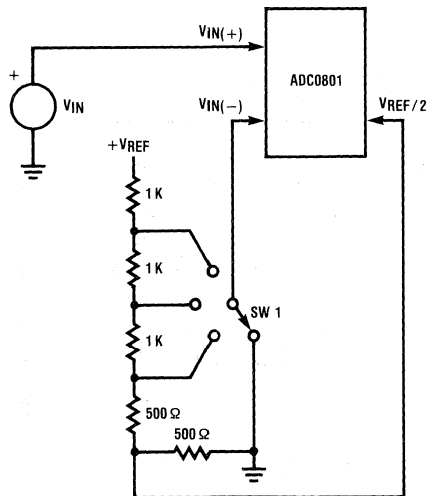


Figure 4. 10-Bit A/D Using the 8-Bit ADC0801

As shown in Figure 5, all zeros will be output by the A/D for an input voltage (at the  $V_{IN(+)}$  input) of  $0V_{DC}$  and all ones will be output by the A/D for a  $500mV_{DC}$  input signal. Operation of the A/D in this high sensitivity mode can be useful in many low cost system applications.

### Digitizing a Current Flow

In system applications there are many requirements to monitor the current drawn by a PC card or a high current load device. This typically is done by sampling the load current flow with a small valued resistor. Unfortunately, it is usually desired that this resistor be placed in series with the  $V_{CC}$  line. The problem is to remove the large common-mode DC voltage, amplify the differential signal, and then present the ground referenced voltage to an A/D converter.

All of these functions can be handled by the A/D using the circuit shown in Figure 6. Here we are making use of the differential input feature and the common-mode rejection of the A/D to directly encode the voltage drop across the load current sampling resistor. An offset voltage adjustment is provided and the  $V_{REF}/2$  voltage is reduced to 50 mV to accommodate the input voltage span of 100 mV. If desired, a multiplexer can be used to allow switching the  $V_{IN(-)}$  input among many loads.

### Conclusions

At first glance it may appear that the A/D converters were mainly designed for an easy digital interface to the microprocessor. This is true, but the analog interface has also been given attention in the design and a very useful converter product has resulted from this combination of features.

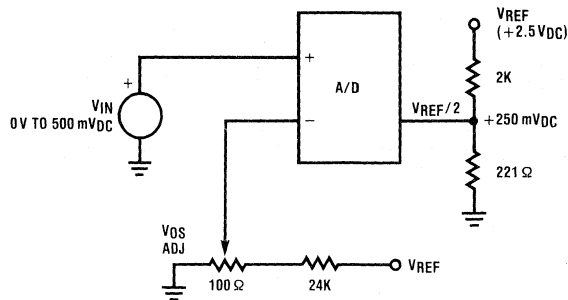


Figure 5. Directly Encoding a Low Level Signal

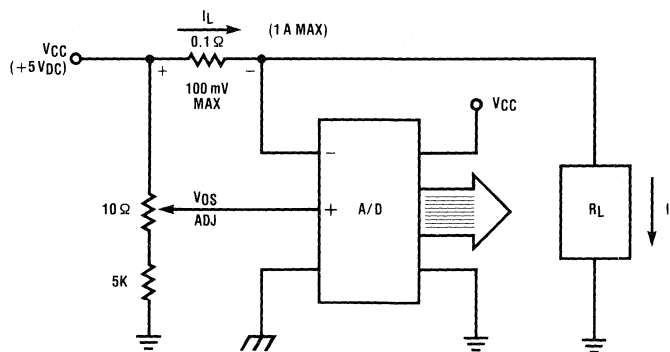


Figure 6. Digitizing a Current Flow



# A Microprocessor-Controlled Pressure Regulator

National Semiconductor  
Application Note 234  
Duane Tandeske  
July 1979



AN-234 A Microprocessor-Controlled Pressure Regulator

## Introduction

In pneumatic systems, some form of pressure regulation is usually required. The most popular method has been the mechanical pressure regulator. For more than one pressure or vacuum, however, multiple pressure regulators must be employed. Using a microcontroller<sup>1</sup> with a pressure transducer and suitable valving, multiple values of both pressure and vacuum can be controlled by a single system. The microcontrolled regulator can be used for either specific or delta pressures and lends itself to generation of pressure cycles. The entire system is under program control, providing additional advantages of flexibility, self-test, and improved reliability.

## Basic Pressure Regulator

To implement the pressure regulator, the microcontroller is used in a closed-loop configuration. As shown in Figure 1, the microprocessor alternately measures the chamber pressure and bleeds valves to bring the pressure to the desired value. Photo 1 shows a valve array for pressure control. Each pressure measurement is auto-referenced,<sup>2</sup> to compensate for measurement offset<sup>3</sup> errors, and chamber pressure is corrected with a coarse/fine valve system, which allows a simple microprocessor interface yet maintains

regulator speed and accuracy.<sup>3</sup> The total system accuracy is determined by the repeatability and resolution of each measurement.

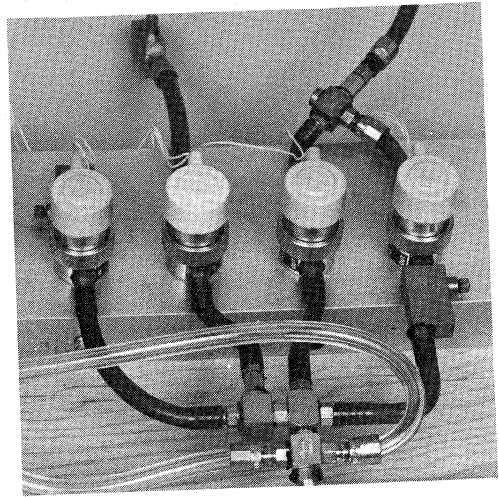


Photo 1. Pressure Regulator Valve Array.

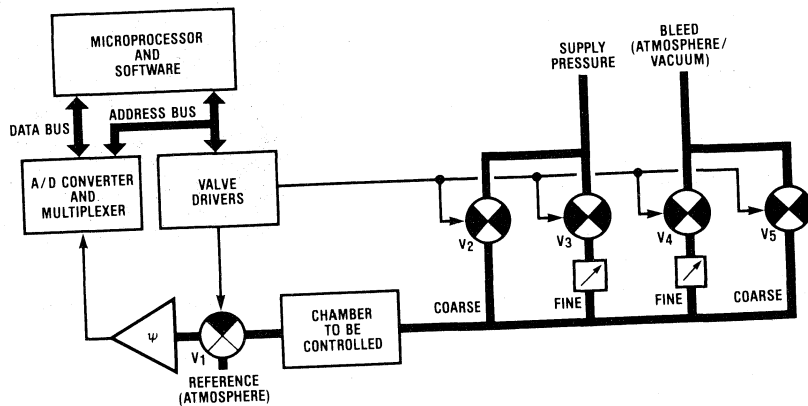


Figure 1. Basic Microcontrolled Pressure Regulator.

## Pressure Measurement — Auto-Referencing

As shown in Figure 2, the chamber pressure is measured with an A/D converter and a pressure transducer connected to the chamber via a three-way valve. This valve allows the measurements to be corrected for offset errors by auto-referencing to a stable reference pressure. To control either specific gage pressure or delta pressures, the stable reference can be the ambient atmosphere. (Delta pressure can be the difference in the pressures of two chambers at the same time or of one chamber at different times.)

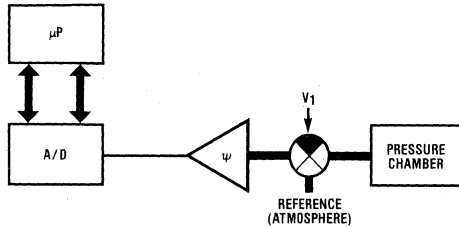


Figure 2. Pressure Measurement Channel.

The program steps required for autoreferencing are shown in Figure 3. The microprocessor first reads and stores the reference pressure then subtracts the stored value from each measurement of chamber pressure. This automatically corrects each measurement for offset errors due to time and temperature. The reference pressure normally needs to be read only once for a large number of measurements, since offset drift is slow by comparison.

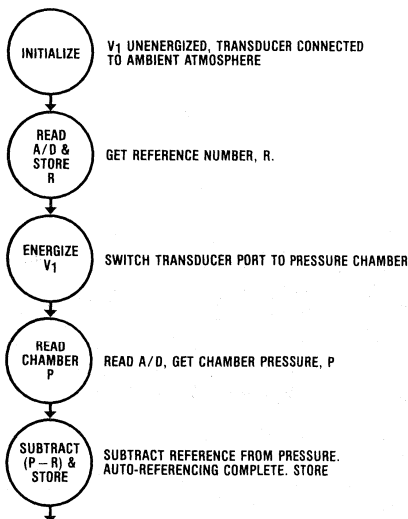


Figure 3. Pressure Measurement Cycle.

In designing the measurement channel, the transducer and A/D converter should be treated as a single component, with individual linearity,<sup>3</sup> resolution, and temperature coefficients<sup>3</sup> combined to determine resolution and accuracy. This is straightforward arithmetically, but finding an A/D converter and pressure transducer that are directly compatible in voltage level (offset) and swing (span)<sup>3</sup> may not be an easy task.

Most A/D manufacturers have standardized input ranges of 0 to 5V, 0 to 10V, or -5V to +5V; whereas, the output levels of pressure transducers can vary widely. This means that some form of signal conditioning,<sup>4</sup> such as level shifting or span adjustment, will most likely be required.

In addition, care must be taken to ensure that time and temperature-induced errors do not cause the transducer output to exceed the input range of the A/D converter.

For example, if the chosen A/D converter has an input range of 0 to 10V, and the transducer has a maximum offset drift of  $\pm 0.4V$ , the transducer output should be 0.5V to 9.5V for the desired pressure range. For transducer errors that increase with applied pressure, it may be necessary to allow a larger margin at the upper limit. This will ensure that the transducer output never exceeds the A/D converter limits over the working temperature range. Photo 2 shows a 12-bit A/D and 16 channel MUX Card.

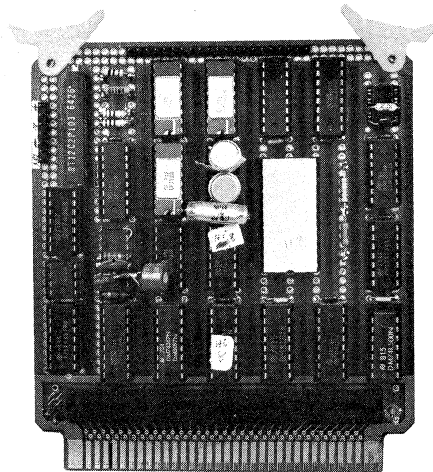


Photo 2. A/D and MUX Card.

## Pressure Control — Coarse/Fine Valves

After measuring pressure the microcontroller corrects the chamber pressure by pulsing solenoid valves. These connect the chamber to *bleed* if pressure is too high and to *supply* if too low. The pressure change resulting

from a single pulse will depend on chamber volume, source pressure, pulse duration, and size of the valve orifice.

While individual fine valves could be used for *supply* and *bleed* corrections, improved accuracy versus speed can be achieved using coarse and fine valves with different orifice sizes. The function of the valves is analogous to an A/D converter, as shown in Figure 4. A "counting" A/D, which is similar to the fine valve approach, is much slower because of the high number of counts required. The use of several degrees of coarseness is similar to the successive approximation A/D, where the number of bits determines accuracy and speed is constant. The higher order bits get close to the desired value, and the low order bits determine tolerance. Analogously, in the coarse/fine regulator, the coarse valve quickly brings the pressure near the desired value, then the fine valve brings it within tolerance.

Coarse/fine control is implemented in the program by setting up fine and coarse limits, as shown in Figure 5. If the measured pressure is outside the coarse limits, the coarse valve is activated. This brings the pressure within the coarse limits, after which the fine valve is used. Within the fine limits, the pressure is within tolerance, and no correction is needed. To avoid hunting, the following conditions should hold:

$$\begin{aligned} \text{Fine Increment} &\leq 2x \pm \text{Fine Limit} \\ \text{Coarse Increment} &\leq 2x \pm \text{Coarse Limit} \end{aligned}$$

Appropriate delays may also be needed in the program to allow pressure to change by the desired amount.

### The Control Program

The flow diagram for the basic pressure regulator (Figure 1) is shown in Figure 6. This program must include the values and limits for each pressure to be controlled, with separate limits for the coarse and fine

valves. These values will probably have to be entered as binary numbers.

The initial valve conditions are:  $V_2$  through  $V_5$  are closed, and  $V_1$  is connected to atmosphere; and the system is ready to read and store the first atmospheric pressure value. Since atmospheric pressure changes slowly, it may be read only once for each major cycle, which may include many pressure settings.

With the atmospheric pressure stored in memory, the program "gets" the control pressure value then reads the chamber pressure. The microprocessor then performs the auto-reference step by subtracting atmospheric pressure from chamber pressure. The auto-referenced value is subtracted from the control pressure value, then the difference is compared with the coarse limits. If it is outside coarse limits, a coarse adjustment is made; if inside, a fine adjustment is made; until the chamber pressure is within tolerance.

For example, if the tolerance is  $\pm 0.15$  psi, the fine limits are set to  $\pm 0.15$  psi, and the fine valves can be set for 0.2 psi increments to avoid hunting:

$$|0.2| \leq 2x \pm 2.6|$$

Likewise, if the coarse increment is set for 5 psi, the coarse limits could be set for  $\pm 2.6$  psi.

Then, if the first control pressure value is 12 psig, and the chamber is initially at atmospheric pressure, 0 psig, or 12 psi below control pressure, the coarse valve is actuated. The chamber pressure is then read again as 5 psig, 7 psig below the desired value. A second coarse pressure increment brings the chamber to 10 psig, which is 2 psi low but within the coarse limits ( $\pm 2.6$  psi).

Next, the chamber pressure error is compared with the fine limits. Since the pressure is 2 psi low, the fine valve will be pulsed 10 times and the chamber pressure read after each pulse. After the tenth pulse, the chamber pressure is read to be within the fine limits, now 12 psig  $\pm 0.15$  psi, and the system can either continue regulating to that pressure or get the next control pressure value.

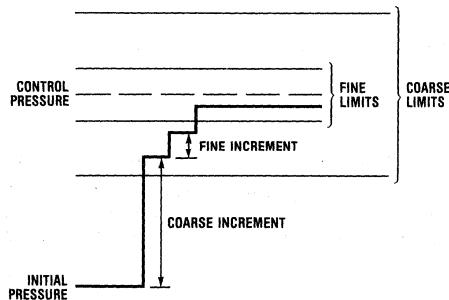


Figure 4. Single vs Multiple Valves.

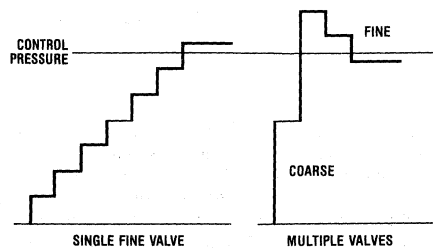


Figure 5. Fine and Coarse Limits.

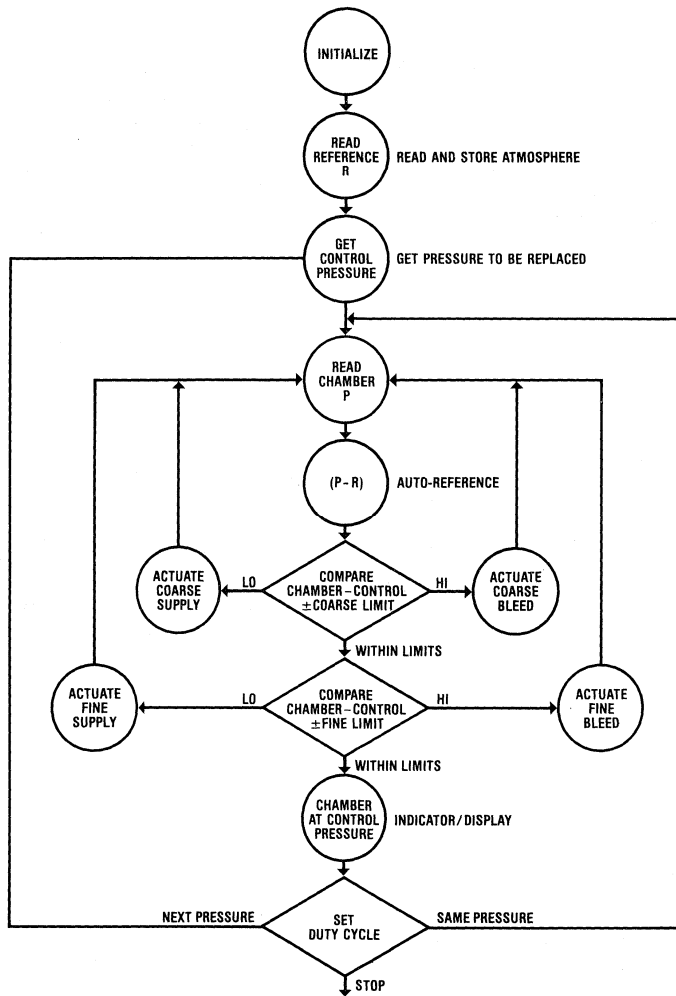


Figure 6. Flow Diagram for Basic Pressure Regulator.

To minimize tolerance build-up for delta pressure readings, the last pressure reading should be saved and used as a base for the next control pressure value. For example, if the control pressures are 12 psig, 17 psig, and 28 psig, 5 psi would be added to the last 12 psig reading to obtain the 17 psig control value, and 11 psi would be added to the last 17 psig reading to obtain the 28 psig value. The deltas would then be 5 psi  $\pm 0.15$  psi and 11 psi  $\pm 0.3$  psi. If the specific pressure is important, rather than the delta value, the numeric value of each control pressure would be entered and used as the basis for regulation.

#### Options and Expansion — Additional Hardware

The microcontrolled pressure regulator is highly flexible and can be modified or expanded to provide improved accuracy and reliability as well as additional functions.

With one additional valve, the source pressure could be monitored and an alarm or pump command given if it goes below a certain value. Displays indicating when chamber pressures are within tolerance could also be added (Figure 6).

If a wide range of pressures are to be controlled, additional measurement channels can enhance accuracy at lower pressures, as shown in Figure 7. An extra channel can also provide self-test and improved reliability. If additional chambers are to be controlled, the regulator can be expanded by adding a 3-way valve and a 2-way valve for each additional chamber, as shown in Figure 8.

An external timer, or analog inputs to the A/D converter, would allow the regulator to generate specific pressure-time sequences, with additional programming, of course. Another use of the timer would be coarse/fine pressure control using pulse length variation rather than multiple valves with different orifice sizes.

With additional software, the pressure chamber could be checked for leaks or usage rate, or statistical data, such as numbers of cycles per day or week, could be recorded automatically.

## Summary

As evidenced by easily available hardware and the simplicity of programming, the microcontrolled pressure regulator is a viable alternative to the mechanical type regulators used in the past. Yet, because of its high degree of flexibility, it can be much more: a total solution to the problem of pressure control, with all the advantages of easy software control of system parameters, self-test, monitoring, and display.

## References — National Semiconductor Publications

1. AN218, A Pressure Microcontroller, Duane Tandeske.
2. 1977 Pressure Transducer Handbook, Section 7.
3. 1977 Pressure Transducer Handbook, Sections 3 and 16.
4. 1977 Pressure Transducer Handbook, Section 8.

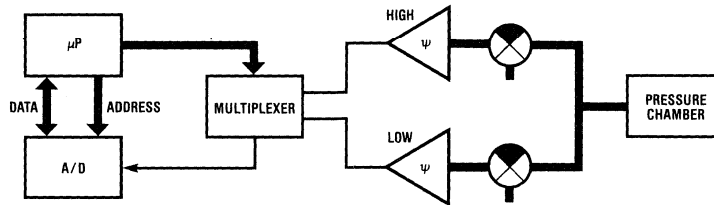


Figure 7. Dual Transducers for Wide Pressure Range.

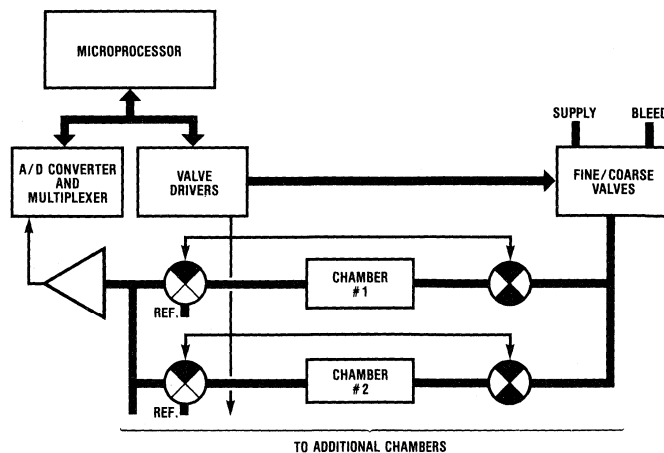


Figure 8. Expansion to Multiple Chambers.



# Improving Response Time of IC Temperature Transducers

National Semiconductor  
Application Note 238  
Carl Nelson  
December 1979



In many applications of temperature transducers, the thermal time constant ( $\tau$ ) of the transducer is too slow for overall system requirements. The most often used method of reducing  $\tau$  is to reduce the physical size of the transducer. This reduces the thermal capacitance at a faster rate than thermal resistance and gives an overall net reduction in time constant. This technique can be carried only so far, however, and in the case of IC transducers, is somewhat impractical. The smallest package available at present from National Semiconductor is the TO-46 which weighs  $\approx 0.35$  gram. Time constant in still air is over 30 seconds, and even in rapidly moving air improves to only 5 seconds (see Figure 3).

Fortunately, a pure electrical technique exists for making large improvements in the apparent time constant of transducers. The technique is general and can be applied to any signal with a single time constant, regardless of its origination. The only requirement is knowledge of the input time constant. Nothing need be known about wave-shape, amplitude, or frequency. The major restrictions on overall  $\tau$  improvement are the presence of multiple  $\tau$  signals, input noise at frequencies above  $1/\tau$  and variation of input  $\tau$  with amplitude, time, temperature, etc.

The basic technique used in  $\tau$  reduction is to differentiate (in the time domain) the input signal and sum the signal

and the differential in the proper ratio. The mathematics are as follows: Let  $V_{IN}$  be represented as  $A(1-e^{-t/\tau})$ . Differentiation yields  $K \cdot A \cdot e^{-t/\tau}$ , where  $K$  is a constant of the electronic differentiation technique. If the two expressions are summed with  $K = \tau$ , the exponential term drops out, leaving only  $A$ . This implies that a step input signal with a finite rise and fall time will be transformed to a step output with zero rise time. In practice,  $\tau$  improvement is usually limited to about 10:1 due mainly to the presence of multiple  $\tau$ s in the input signal. Nevertheless, this represents a dramatic improvement in transducer response time.

The circuit in Figure 1 is a universal  $\tau$  reducer. A1 is an inverting differentiator with adjustable gain. Its output is combined with the original input at A2 to make the complete conversion. The overall transfer function is given by:

$$V_{OUT} = V_{IN} + \frac{dV_{IN}}{dt} C2R3 \frac{R4}{R4W}$$

Where  $R4W$  is the portion of  $R4$  between wiper and ground.

In this circuit,  $\tau$  is equal to  $C2R3 \frac{R4}{R4W}$ .

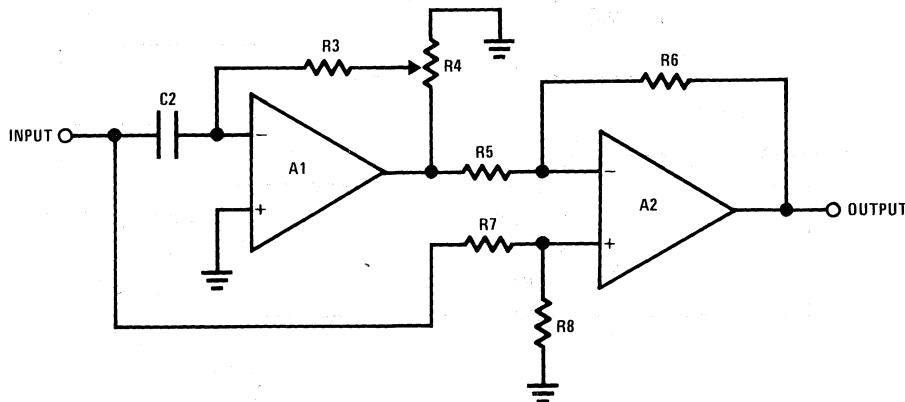


FIGURE 1

In Figure 2, a three pole low pass filter consisting of R2/C2, C3/  $\frac{R3R4}{R4W}$ , and C4/R6 is used to reject input noise occurring at frequencies above  $1/\tau$ .

Even if the input is relatively noise free, one or more of these filters is usually necessary (especially R2/C2) to control internally generated noise. Time constants for the filters should be carefully chosen to provide adequate filtering without limiting the maximum obtainable  $\tau$  improvement. Typical filter time constants would be  $0.05 \tau$ . Figure 4 shows anticipator gain versus frequency for several values of filter time constant. This graph can be used to estimate rejection of transducer noise at various frequencies. Figure 5 shows the limitation on improvement for various ratios of filter to circuit time constant. Note that  $\tau$  is adjusted by R4, but since R4 has very little effect on the steady state output, the circuit can be quickly adjusted for optimum output settling without

generating steady state errors. The values shown were used for  $\tau = 10$  seconds. Output settling to 1% was 4 seconds.

If large transient signals are expected on the input, clamping may be necessary on the differentiator to prevent the summing node from lifting off ground. If this happens, the R3/C2 time constant can generate long settling delays while excess charge is bled from C2. Maximum dv/dt allowed before clamping occurs may be calculated from:

$$\frac{dv}{dt} (\text{Max}) = \frac{V_{\text{clamp}}}{C2R3}$$

Output accuracy is lost while clamping occurs, but is unaffected by the clamps as soon as input dv/dt falls below the critical value.

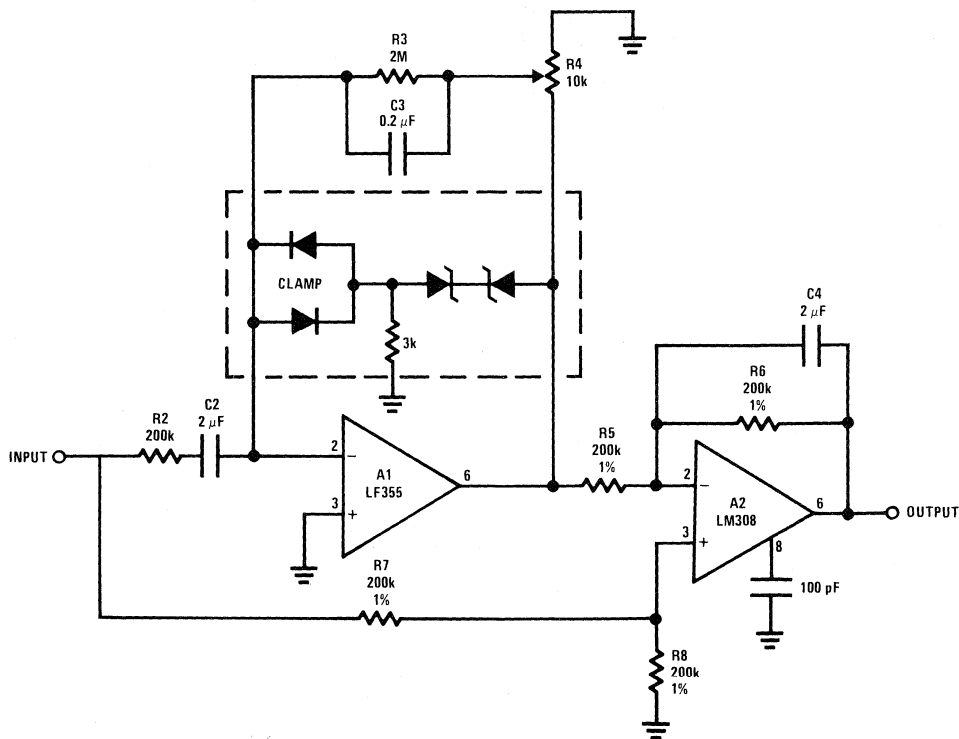


FIGURE 2



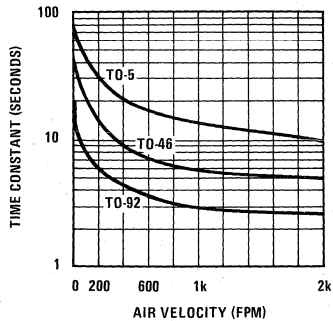


FIGURE 3. Thermal Time Constant

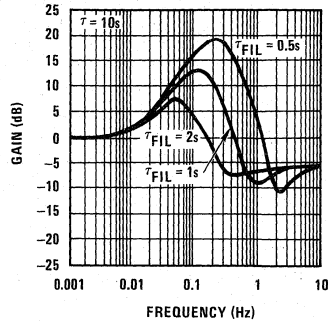


FIGURE 4. Anticipator Gain vs Frequency

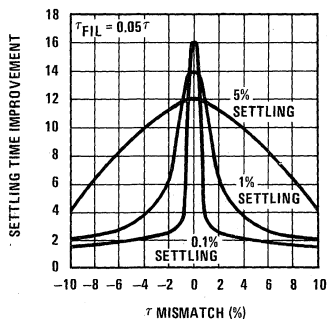


FIGURE 5. Settling vs  $\tau$  Mismatch

#### IC TEMPERATURE TRANSDUCER TIME CONSTANTS

Time constants for National Semiconductor transducers can vary from one second to several minutes depending on the environment. Rapidly stirred oil will reduce  $\tau$  to one second for the TO-46 package, while dead still air around a TO-5 package will stretch  $\tau$  to well over one minute. See Figure 3 for  $\tau$  as a function of air velocity.

When the transducer is fastened to a heatsink of even modest proportions,  $\tau$  is determined by the thermal properties of the sink. The circuit in Figure 2 is limited to  $\tau$  correction of several minutes or less, although A1 could be replaced with an ultra low input current device with C2 and R3 in the  $1\ \mu\text{F}$ - $10\ \mu\text{F}$ / $10\ \text{M}\Omega$ - $100\ \text{M}\Omega$  range to extend  $\tau$ s up to 1000 seconds.

#### MISMATCH OF $\tau$

In most practical applications of transducers, some variation of  $\tau$  is expected. In Figure 5, settling time improvement is shown as a function of  $\tau$  mismatch. This graph indicates, for instance, that for a 5% mismatch, 1% settling will be improved by a factor of 3. Mismatches can occur after calibration due to fluid velocity changes, transducer orientation, or temperature variations of thermal capacity or conductivity. The IC transducers themselves contribute very little to  $\tau$  variation unit-to-unit because package size and construction is rigidly controlled. In a well-controlled ambient situation, significant settling time improvement can be obtained without individual calibration of each transducer.

## SOME APPLICATIONS

The most important application of  $\tau$  reduction is measuring air temperature. Without this technique, most of the calibration and test time is wasted just waiting for the unit under test to stabilize at temperature. The use of stirred oil can reduce wait time to under 10 seconds, but oil is messy and malodorous. The combination of a collimated air stream and  $\tau$  reduction can bring total test time to under 10 seconds without any additional time for cleanup. A calibrated sensor identical to the device under test is located symmetrically with respect to the unit under test and differential measurements are used. This eliminates errors due to air stream temperature, air velocity and transducer temperature rise caused by internal power dissipation. Note that the reference device should be calibrated in the exact environment in which the transducer will be used because temperature rise will be a factor in actual use (see LM134 data sheet).

In temperature control applications, it is often necessary to add "anticipation" to the control loop to correct for heater and sensor lag. If the output of the  $\tau$  reducer is used in a control loop instead of the actual sensor output,

much quicker settling can be obtained without overshoot problems. This technique can be applied to general control applications as well.

Temperature testing of semiconductors with hot/cold probes, dry ice, etc., can be greatly speeded up with  $\tau$  reduction. The measured parameter is simply converted to a DC voltage and fed into the  $\tau$  reducer. Wait time can be reduced from the typical 30-60 seconds to under 10 seconds. Two precautions are in order when using this technique; first, the measured parameter must be reasonably linear with temperature (leakage, for instance, is not) and second, the measured parameter must not be too sensitive to thermal gradients in the package or leads. An example of the latter problem is offset voltage drift of operational amplifiers. Thermocouple effects created by temperature gradients between device leads (KOVAR/Cu = 30  $\mu\text{V}/^\circ\text{C}$ ) will cause drift measurements to be in error by up to 1  $\mu\text{V}/^\circ\text{C}$ . For the majority of analog testing, however,  $\tau$  reduction offers an attractive alternative to complex oven setups.

# Wide-Range Current-to-Frequency Converters

National Semiconductor  
Application Note 240  
Robert A. Pease  
May 1980



Does an analog-to-digital converter cost you a lot if you need many bits of accuracy and dynamic range? Absolute accuracy better than 0.1% is likely to be expensive. But a capability for wide dynamic range can be quite inexpensive. Voltage-to-frequency (V-to-F) converters are becoming popular as a low-cost form of A-to-D conversion because they can handle a wide dynamic range of signals with good accuracy.

Most voltage-to-frequency (V-to-F) converters actually operate with an input current which is proportional to the voltage input:

$$I_{IN} = \frac{V_{IN}}{R_{IN}}$$

(Figure 1). This current is integrated by an op amp, and a charge dispenser acts as the feedback path, to balance out the average input current. When an amount of charge  $Q = I \cdot T$  (or  $Q = C \cdot V$ ) per cycle is dispensed by the circuit,

then the frequency will be:

$$f = \left( \frac{V_{IN} - V_{OS}}{R_{IN}} + I_b \right) \times \frac{1}{Q}$$

When  $V_{IN}$  is large:

$$f \approx \frac{V_{IN}}{R_{IN}} \times \frac{1}{Q}$$

When  $V_{IN}$  covers a wide dynamic range, the  $V_{OS}$  and  $I_b$  of the op amp must be considered, as they greatly affect the usable accuracy when the input signal is very small. For example, when the full-scale input is 10V, a signal which is 100 dB below full-scale will be only 100  $\mu$ V. If the op amp has an offset drift of  $\pm 100 \mu$ V, (whether caused by time or temperature), that would cause a  $\pm 100\%$  error at this signal level. However, a current-to-frequency converter can easily cover a 120 dB range because the voltage offset problem is not significant when the input signal is actually a current source. Let's study the architecture and design of a current-to-frequency converter, to see where we can take advantage of this.

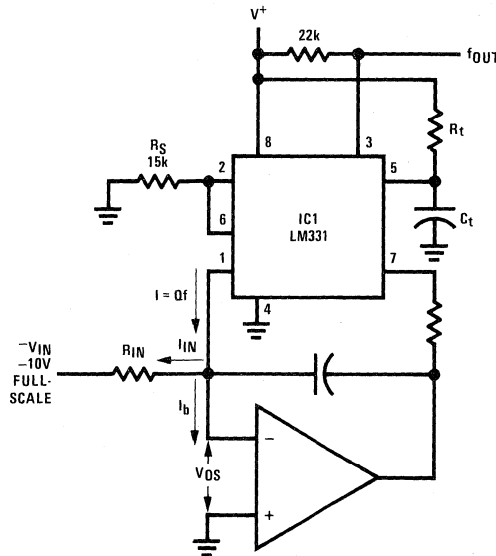


FIGURE 1. Typical Voltage-to-Frequency Converter

When the input signal is a current, the use of a low-voltage-drift op amp becomes of no advantage, and low bias current is the prime specification. A low-cost BI-FET™ op amp such as the LF351A has  $I_b < 100$  pA, and temperature coefficient of  $I_b$  less than  $10$  pA/°C, at room temperature. In a typical circuit such as Figure 2, the leakage of the charge dispenser is important, too. The LM331 is only specified at  $10$  nA max at room temperature, because that is the smallest current which can be measured economically on high-speed test equipment. The leakage of the LM331's current-source output at pin 1 is usually  $2$  pA to  $4$  pA, and is always less than the  $100$  pA mentioned above, at  $25^\circ\text{C}$ .

The feedback capacitor  $C_F$  should be of a low-leakage type, such as polypropylene or polystyrene. (At any temperature above  $35^\circ\text{C}$ , mylar's leakage may be excessive.) Also, low-leakage diodes are recommended to protect the

circuit's input from any possible fault conditions at the input. (A 1N914 may leak  $100$  pA even with only  $1$  millivolt across it, and is unsuitable.)

After trimming this circuit for a low offset when  $I_{IN}$  is  $1$  nA, the circuit will operate with an input range of  $120$  dB, from  $200$   $\mu\text{A}$  to  $100$  pA, and an accuracy or linearity error well below ( $0.02\%$  of the signal plus  $0.0001\%$  of full-scale).

The zero-offset drift will be below  $5$  or  $10$  pA/°C, so when the input is  $100$  dB down from full-scale, the zero drift will be less than  $2\%$  of signal, for a  $\pm 5^\circ\text{C}$  temperature range. Another way of indicating this performance is to realize that when the input is  $1/1000$  of full-scale, zero drift will be less than  $1\%$  of that small signal, for a  $0^\circ\text{C}$  to  $70^\circ\text{C}$  temperature range.

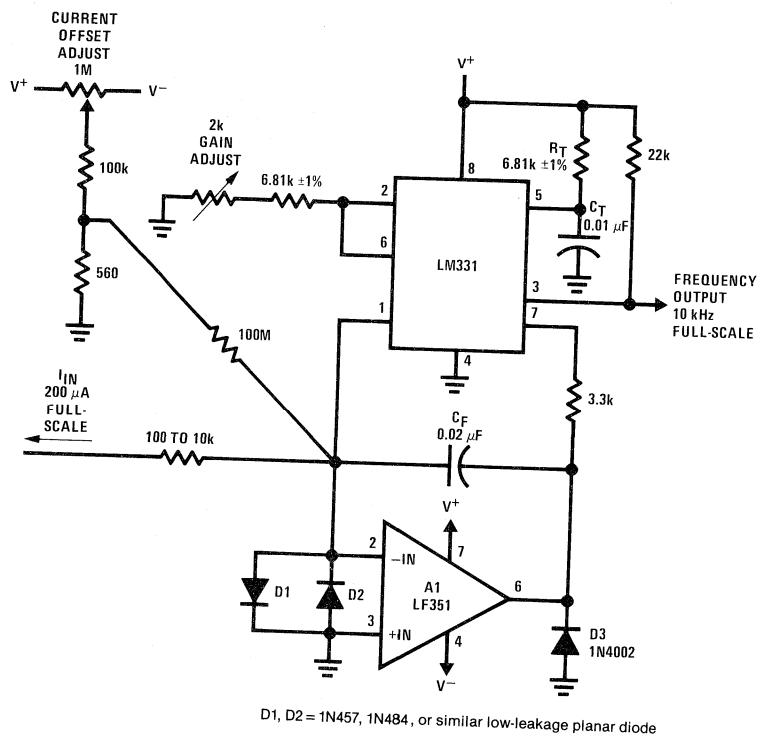


FIGURE 2. Practical Wide-Range Current-to-Frequency Converter

What if this isn't good enough? You *could* get a better op amp. For example, an LH0022C has 10 pA max  $I_b$ . But it is silly to pay for such a good op amp, with low V offset errors, when only a low input current specification is needed. The circuit of Figure 3a shows the simple scheme of using FET followers ahead of a conventional op amp. An LF351 type is suitable because it is a cheap, quick amplifier, well suited for this work. The 2N5909s have a maximum  $I_b$  of 1.0 pA, and at room temperature it will drift only 0.1 pA/°C. Typical drift is 0.02 pA/°C.

The voltage offset adjust pot is used to bring the summing point within a millivolt of ground. With an input signal big enough to cause  $f_{OUT} = 1$  second per cycle, trim the V offset adjust pot so that closing the *test* switch makes no

effect on the output frequency (or, output period). Then adjust the input current offset pot, to get  $f_{OUT} = 1/1000$  of full-scale when  $I_{IN}$  is 1/1000 of full-scale. When  $I_{IN}$  covers the 140 dB range, from 200  $\mu$ A to 20 pA, the output will be stable, with very good zero offset stability, for a limited temperature range around room temperature. Note these precautions and special procedures:

1. Run the LM331 on 5V to 6V to keep leakage down and to cut the dissipation and temperature rise, too.
2. Run the FETs with a 6V drain supply.
3. Guard all summing point wiring away from all other voltages.

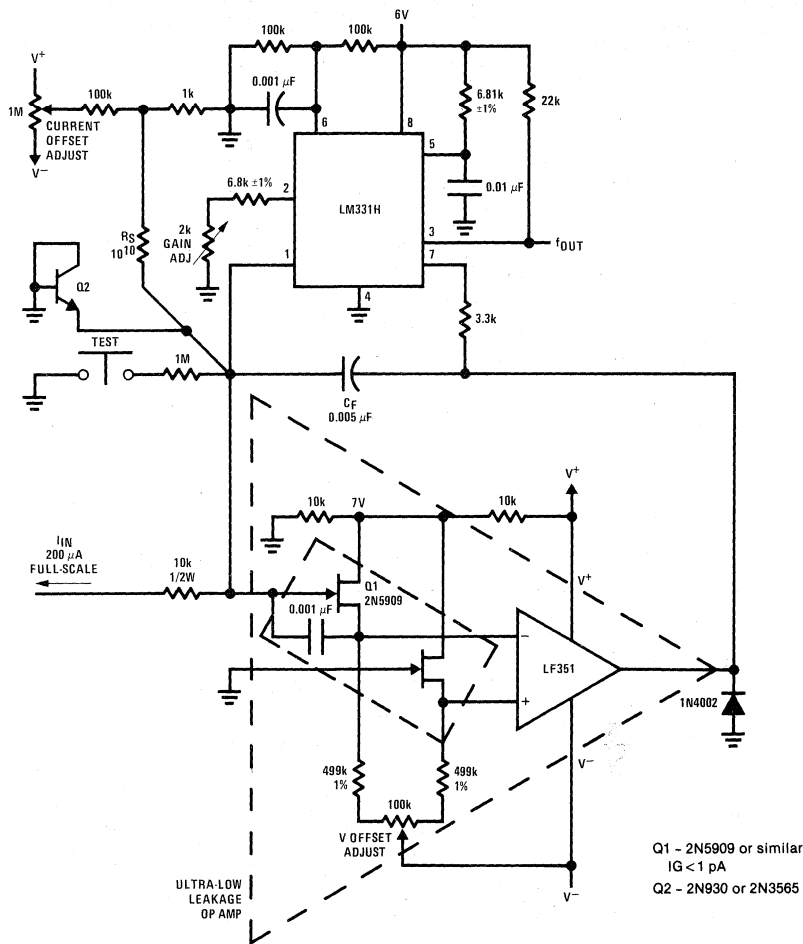


FIGURE 3a. Very-Wide-Range Current-to-Frequency Converter

An alternate approach, shown in *Figure 3b*, uses an LM11C as the input pre-amplifier. The LM11C has much better voltage drift than any of the other amplifiers shown here (normally less than  $2 \mu\text{V}/^\circ\text{C}$ ) and excellent current drift, less than  $1 \text{ pA}/^\circ\text{C}$  by itself, and typically  $0.2 \text{ pA}/^\circ\text{C}$  when trimmed with the 2N3904 bias current compensation circuit as shown. Of course, the LM331's leakage of  $1 \text{ pA}/^\circ\text{C}$  will still double every  $10^\circ\text{C}$ , so that having an amplifier with excellent  $I_b$  characteristics does not solve the whole problem, when trying to get good accuracy with a  $100 \text{ pA}$  signal. For that job, even the leakage of the LM331 must be guarded out!

What if even lower ranges of input current must be accepted? While it might be possible to use a current-to-voltage converter ahead of a V-to-F converter, offset voltage drifts would hurt dynamic range badly. Response and zero-drift of such an I-V will be disappointing. Also, it is not feasible to starve the LM331 to an arbitrary extent.

For example, while its  $I_{\text{OUT}}$  (full-scale) of  $280 \mu\text{A}$  DC can be cut to  $10 \mu\text{A}$  or  $28 \mu\text{A}$ , it cannot be cut to  $1 \mu\text{A}$  or  $2.8 \mu\text{A}$  with good accuracy at  $10 \text{ kHz}$ , because the internal switches in

the integrated circuit will not operate with best speed and precision at such low currents.

Instead, the output current from pin 1 of the LM331 can be fed through a current attenuator circuit, as shown in *Figure 4*. The LM334 (temperature-to-current converter IC) causes  $-120 \text{ mV}$  bias to appear at the base of Q2. When a current flows out of pin 1 of the LM331,  $1/100$  of the current will flow out of Q1's collector, and the rest will go out of Q2's collector. As the LM334's current is linearly proportional to Kelvin temperature, the  $-120 \text{ mV}$  at Q2's base will change linearly with temperature so that the Q1/Q2 current divider stays at 1:100, invariant of temperature, according to the equation:

$$i_1/i_2 = e^{\frac{q(V_{b1}-V_{b2})}{kT}}$$

This current attenuator will work stably and accurately, even at high speeds, such as for  $4 \mu\text{s}$  current pulses. Thus, the output of Q1 is a charge pump which puts out only  $10$  picocoulombs per pulse, with surprisingly good accuracy. Note also that the LM331's leakage is substantially attenuated also, by a factor of  $100$  or more, so that source of

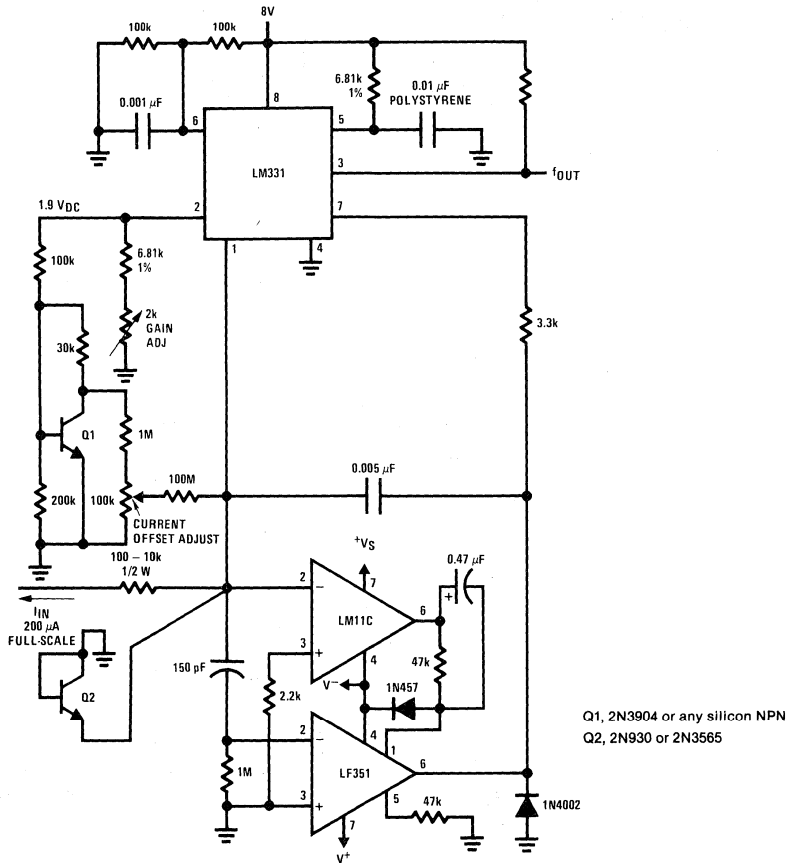


FIGURE 3b. Very-Wide-Range I-to-F Converter with Low Voltage Drift



If a positive signal is of interest, the LM331 can be applied with a current reflector as in Figure 5. This current reflector has high output impedance, and low leakage. Its output can go directly to the summing point, or via a current attenuator made with NPN transistors, similar to the PNP circuit of Figure 4. This circuit has been observed to cover a wide (130 dB) range, with 0.1% of signal accuracy.

What is the significance of this wide-range current-to-frequency converter? In many industrial systems the question of using an inexpensive 8-bit converter instead of an expensive 12-bit data converter is a battle which is decided every day. But if the signal source is actually a current source, then you can use a V-to-F converter to make a cheap 14-bit converter or an inexpensive converter with 18 bits of dynamic range. The choice is yours.

Why use an I-to-F converter?

- It is a natural form of A-to-D conversion.
- It naturally facilitates integration, as well.

- There are many signals in the world, such as photo-spectrometer currents, which like to be digitized and integrated as a standard part of the analysis of the data.
- Similarly: photocurrents, dosimeters, ionization currents, are examples of currents which beg to be integrated in a current-to-frequency meter.
- Other signal sources which provide output currents are:
  - Phototransistors
  - Photo diodes
  - Photoresistors (with a fixed voltage bias)
  - Photomultiplier tubes
  - Some temperature sensors
  - Some IC signal conditioners

Why have a fast frequency out?

- A 100 kHz output full-scale frequency instead of 10 kHz means that you have 10 times the resolution of the signal. For example, when  $I_{IN}$  is 0.01% of full-scale, the  $f$  will be 10 Hz. If you integrate or count that frequency for just 10 seconds, you can resolve the signal to within 1% - a factor of 10 better than if the full-scale frequency were slower.

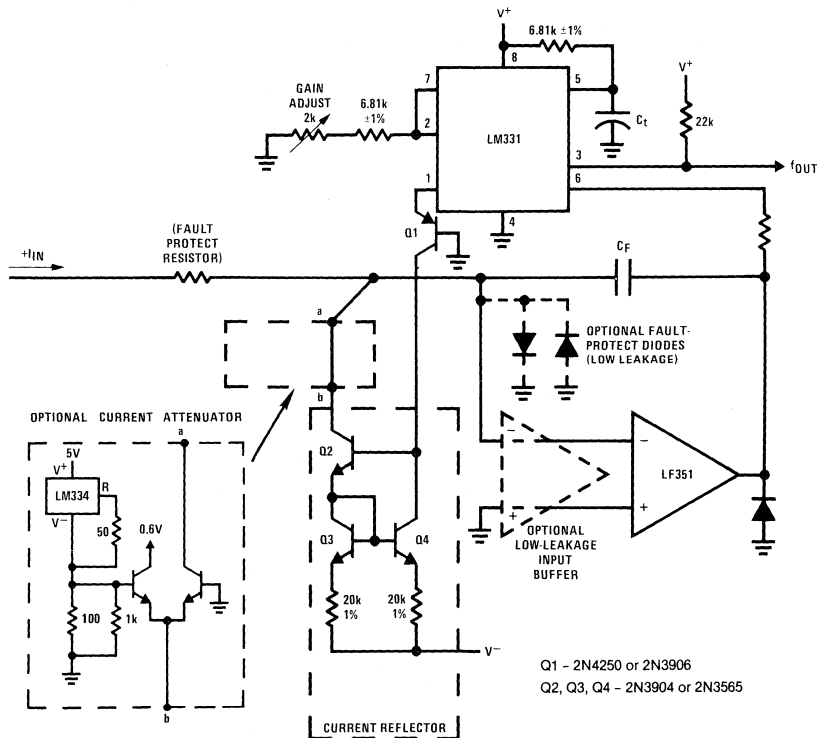


FIGURE 5. Current-to-Frequency Converter For Positive Signals



# Working with High Impedance Op Amps

National Semiconductor  
Application Note 241  
February 1980



Robert J. Widlar  
Puerto Vallarta, Jalisco  
Mexico

**Abstract.** *New developments have dramatically reduced the error currents of IC op amps, especially at high temperatures. The basic techniques used to obtain this performance are briefly described. Some of the problems associated with working at the high impedance levels that take advantage of these low error currents are discussed along with their solutions. The areas involved are printed-circuit board leakage, cable leakage and noise generation, semiconductor-switch leakages, large-value resistors and capacitor limitations.*

## introduction

A new, low cost op amp reduces dc error terms to where the amplifier may no longer be the limiting factor in many practical circuits. FET bias currents are equalled at room temperature; but unlike FETs, the bias current is relatively stable even over a  $-55^{\circ}\text{C}$  to  $125^{\circ}\text{C}$  temperature range. Offset voltage and drift are low because bipolar inputs and on-wafer trimming are used. The  $100\ \mu\text{V}$  offset voltage and  $25\ \text{pA}$  bias current are expected to advance the state of the art for high impedance sensors and signal conditioners.

## bias currents


There has been a continual effort to reduce the bias current of IC op amps ever since the  $\mu\text{A}709$  was introduced in 1965. The LM101A, announced in 1968, dropped this current by an order of magnitude through improved processing that gave better transistor current gain at low

operating currents. In 1969, super-gain transistors (see appendix) were applied in the LM108 to beat FET performance when temperatures above  $85^{\circ}\text{C}$  were involved.


In 1974 FETs were integrated with bipolar devices to give the first FET op amp produced in volume, the LF155. These devices were faster than general purpose bipolar op amps and had lower bias current below  $70^{\circ}\text{C}$ . But FETs exhibit higher offset voltage and drift than bipolars. Long-term stability is also about an order of magnitude worse. Typically, this drift is  $100\ \mu\text{V}/\text{year}$ , but a small percentage could be as bad as  $1\ \text{mV}$ . Laser trimming and other process improvements have lowered initial offset but have not eliminated the drift problem.

The new IC is an extension of super-gain bipolar techniques. As can be seen from figure 1, it provides low bias currents over a  $-55^{\circ}\text{C}$  to  $125^{\circ}\text{C}$  temperature range. The offset current is so low as to be lost in the noise. This level of performance has previously been unavailable for either low-cost industrial designs or high reliability military/space applications.

This low bias current has not been obtained at the expense of offset voltage or drift. Typical offset voltage is under a millivolt and provision is made for on-wafer trimming to get it below  $100\ \mu\text{V}$ . The low drift exhibited in figure 2 indicates that the circuit is inherently balanced for exceptionally low drift, typically  $1\ \mu\text{V}/^{\circ}\text{C}$  below  $100^{\circ}\text{C}$ .

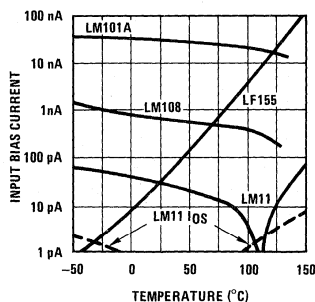

**Figure 1.** Comparison of typical bias currents for various types of IC op amps. New bipolar device not only has lower bias current over practical temperature ranges but also lower drift. Offset current is unusually low with the new design.

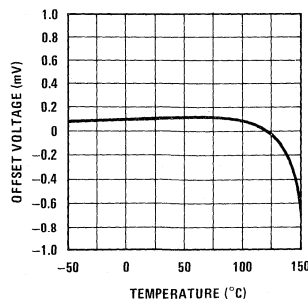


**Figure 2.** Bipolar transistors have inherently low offset voltage and drift. The low drift of the LM11 over a wide temperature range shows that there are no design problems degrading performance.

## the new op amp

The LM11 is, in essence, a refinement of the LM108. A modified Darlington input stage has been added to reduce bias currents. With a standard Darlington, one transistor is biased with the base current of the other. This degrades dc amplifier performance because base current is noisy, subject to wide variation and generally unpredictable.

Supplying a bleed current greater than the base current, as shown in figure 3, removes this objection. The 60 nA provided is considerably in excess of the 1 nA base current. The bleed current is made to vary as absolute temperature to maintain constant impedance at the emitters of Q1 and Q2. This stabilizes frequency response and also reduces the thermal variation of bias current. Parasitic capacitances of the current generator have been bootstrapped so that the 0.3V/ $\mu$ s slew rate of the basic amplifier is unaffected.

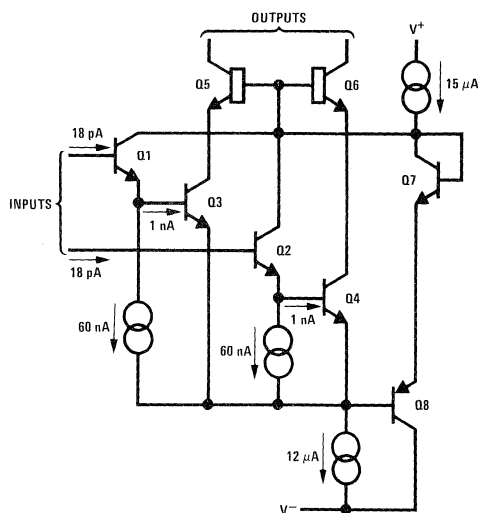

**Figure 3. Modifying Darlington with bleed current reduces offset voltage, drift and noise. Unique circuitry provides well-controlled current with minimal stray capacitance so that speed of the basic amplifier is unaffected.**


Results to date suggest that the base currents of this modified Darlington input are better matched than the simple differential amplifier. In fact, offset current is so low as to be unmeasurable on production test systems. Therefore, guaranteed limits are determined by the test equipment rather than the IC.

### noise

Operating transistors at very low currents does increase noise. Thus, the LM11 is about a factor of four noisier than the LM108. But the low frequency noise, plotted in figure 4, is still slightly less than that of FET amplifiers. Long-term measurements indicate that the offset voltage shift is under 10  $\mu$ V.

In contrast to the noise voltage, low frequency noise current is subject to greater unit-to-unit variation. Generally, it is below 1 pA, peak-to-peak, about the same magnitude as the offset current.

With the LM11, both voltage and current related dc errors have been reduced to the point where overall circuit performance could well be noise limited, particularly in limited temperature range applications.

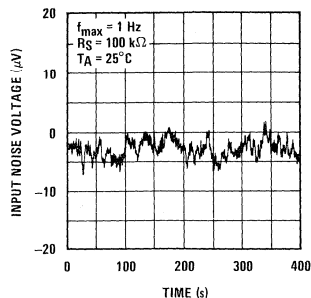

**Figure 4. Lower operating currents increase noise, but low frequency noise is still slightly lower than IC FET amplifiers. Long-term stability is much improved.**

### reliability

The reliability of the LM11 is not expected to be substantially different than the LM108, which has been used extensively in military and space applications. The only significant difference is the input stage. The low current nodes introduced here might possibly be a problem were they not bootstrapped, biased and guarded to be virtually unaffected by both bulk and surface leakages. This opinion is substantiated by preliminary life-test data.

This IC could, in fact, be expected to improve reliability when used to replace discrete or hybrid amplifiers that use selected components and have been trimmed and tweaked to give the required performance.


From an equipment standpoint, reliability analysis of insulating materials, surface contamination, cleaning procedures, surface coating and potting are at least as important as the IC and other components. These factors become more important as impedance levels are raised. But this should not discourage designers. If poor insulation and contamination cause a problem when impedance levels are raised by an order of magnitude, it is best found out and fixed.

Even so, it may not be advisable to take advantage of the full potential of the LM11 in all cases, especially when hostile environments are involved. For example, there should be no great difficulty in finding an LM11 with offset current less than 5 pA over a  $-55^{\circ}\text{C}$  to  $125^{\circ}\text{C}$  temperature range. But anyone designing high-reliability equipment that is going to be in trouble if combined leakages are greater than 10 pA at  $125^{\circ}\text{C}$  had best know what he is about.

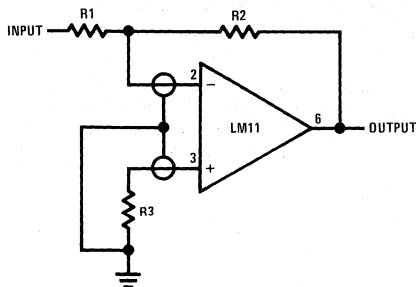
### electrical guarding

The effects of board leakage can be minimized using an old trick known as guarding. Here the input circuitry is surrounded by a conductive trace that is connected to a low impedance point at the same potential as the inputs. The electrical connection of the guard for the basic op amp configurations is shown in figure 5. The guard absorbs the leakage from other points on the board, drastically reducing that reaching the input circuitry.


To be completely effective, there should be a guard ring on both sides of the printed-circuit board. It is still recommended for single-sided boards, but what happens on the unguarded side is difficult to analyze unless Teflon inserts are used on the input leads. Further, although surface leakage can be virtually eliminated, the reduction in bulk leakage is much less. The reduction in bulk leakage for double-sided guarding is about an order of magnitude, but this depends on board thickness and the width of the guard ring. If there are bulk leakage problems, Teflon inserts on the through holes and Teflon or kel-F standoffs for terminations can be used. These two materials have excellent surface properties without surface treatment even in high-humidity environments.



a. inverting amplifier

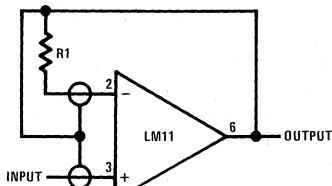


b. follower

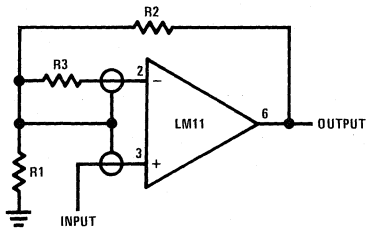

c. non-inverting amplifier

**Figure 5. Input guarding for various op amp connections. The guard should be connected to a point at the same potential as the inputs with a low enough impedance to absorb board leakage without introducing excessive offset.**

An example of a guarded layout for the metal-can package is shown in figure 6. Ceramic and plastic dual-in-line packages are available for critical applications with guard pins adjacent to the inputs both to facilitate board layout and to reduce package leakage. These guard pins are not internally connected.

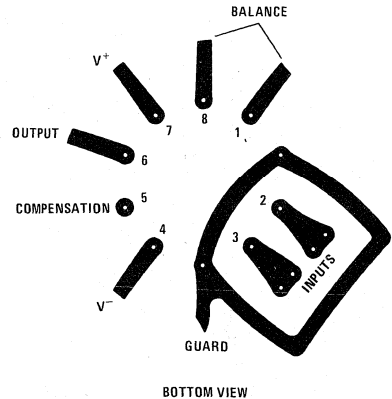


**Figure 6. Input guarding can drastically reduce surface leakage. Layout for metal can is shown here. Guarding both sides of board is required. Bulk leakage reduction is less and depends on guard ring width.**

#### signal cables


It is advisable to locate high impedance amplifiers as close as possible to the signal source. But sometimes connecting lines cannot be avoided. Coaxially shielded cables with good insulation are recommended. Polyethylene or virgin (not reconstituted) Teflon is best for critical applications.

In addition to potential insulation problems, even short cable runs can reduce bandwidth unacceptably with high source resistances. These problems can be largely avoided by bootstrapping the cable shield. This is shown for the follower connection in figure 7. In a way, bootstrapping is positive feedback; but instability can be avoided with a small capacitor on the input.

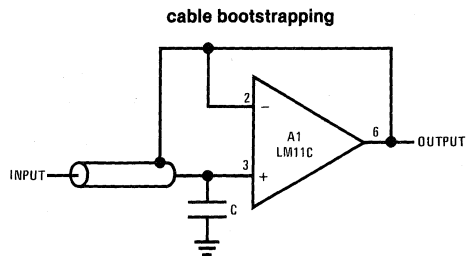

**Figure 7. Bootstrapping input shield for a follower reduces cable capacitance, leakage and spurious voltages from cable flexing. Instability can be avoided with small capacitor on input.**

With the summing amplifier, the cable shield is simply grounded, with the summing node at virtual ground. A small feedback capacitor may be required to insure stability with the added cable capacitance. This is shown in figure 8.

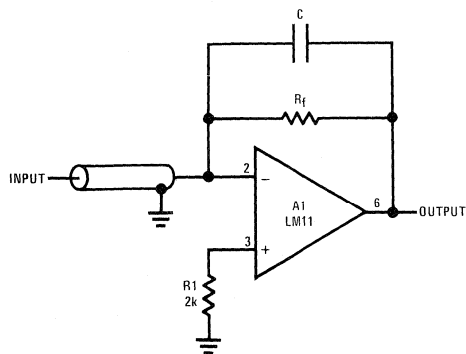

**Figure 8. With summing amplifier, summing node is at virtual ground so input shield is best grounded. Small feedback capacitor insures stability.**

An inverting amplifier with gain may require a separate follower to drive the cable shield if the influence of the capacitance, between shield and ground, on the feedback network cannot be accounted for.

High impedance circuits are also prone to mechanical noise (microphonics) generated by variable stray capacitances. A capacitance variation will generate a noise voltage given by


$$e_n = \frac{\Delta C}{C} V,$$

where V is the dc bias on the capacitor. Therefore, the wiring and components connected to sensitive nodes should be mechanically rigid.

This is also a problem with flexible cables, in that bending the cable can cause a capacitance change. Bootstrapping the shield nearly eliminates dc bias on the cable, minimizing the voltage generated. Another problem is electrostatic charge created by friction. Graphite lubricated Teflon cable will reduce this.

#### switch leakage

Semiconductor switches with leakage currents as low as the bias current of the LM11 are not generally available when operation much above 50°C is involved. The sample-and-hold circuit in figure 9 shows a way around this problem. It is arranged so that switch leakage does not reach the storage capacitor.

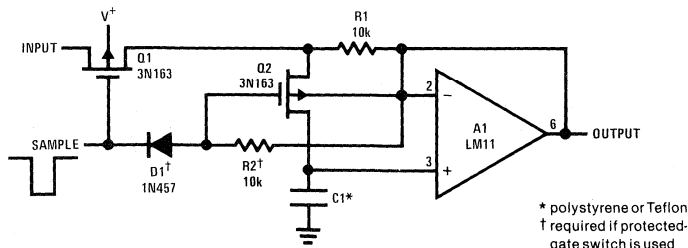

**Figure 9. Switch leakage in this sample and hold does not reach storage capacitor. If Q2 has an internal gate-protection diode, D1 and R2 must be included to remove bias from its junction during hold.**

Isolating leakage current requires that two switches be connected in series. The leakage of the first, Q1, is absorbed by R1 so that the second, Q2, only has the offset voltage of the op amp across its junctions. This can be expected to reduce leakage by at least two orders of magnitude. Adjusting the op amp offset to zero at the maximum operating temperature will give the ultimate leakage reduction, but this is not usually required with the LM11.

MOS switches with gate-protection diodes are preferred in production situations as they are less sensitive to damage from static charges in handling. If used, D1 and R2 should be included to remove bias from the protection diode during hold. This may not be required in all cases but is advised since leakage from the protection diode depends on the internal geometry of the switch, something the designer does not normally control.


A junction FET could be used for Q1 but not Q2 because there is no equivalent to the enhancement mode MOSFET. The gate of a JFET must be reverse biased to turn it off, and leakage on its output cannot be avoided.

#### high-value resistors

Using op amps at very high impedance levels can require unusually large resistor values. Standard precision resistors are available up to 10 MΩ. Resistors up to 1 GΩ can be obtained at a significant cost premium. Larger values are quite expensive, physically large and require careful handling to avoid contamination. Accuracy is also a problem. There are techniques for raising effective resistor values in op amp circuits. In theory, performance is degraded; in practice, this may not be the case.


With a buffer amplifier, it is sometimes desirable to put a resistor to ground on the input to keep the output under control when the signal source is disconnected. Otherwise it will saturate. Since this resistor should not load the source, very large values can be required in high-impedance circuits.

Figure 10 shows a voltage follower with a 1 GΩ input resistance built using standard resistor values. With the input disconnected, the input offset voltage is multiplied by the same factor as R2; but the added error is small because the offset voltage of the LM11 is so low. When the input is connected to a source less than 1 GΩ, this error is reduced. For an ac-coupled input, a second 10 MΩ resistor could be connected in series with the inverting input to virtually eliminate bias current error; bypassing it would give minimal noise.

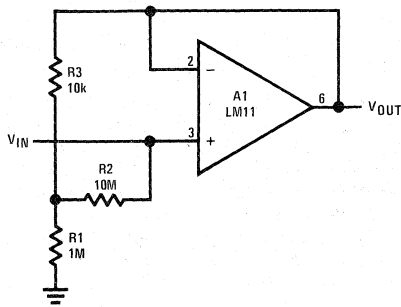

**Figure 10.** Follower input resistance is 1 GΩ. With the input open, offset voltage is multiplied by 100, but the added error is not great because the op amp offset is low.

The voltage-to-current converter in figure 11 uses a similar method to obtain the equivalent of a 10 GΩ feedback resistor. Output offset is reduced because the error can be made dependent on offset current rather than bias current. This would not be practical with large value resistors because of cost, particularly for matched resistors, and because the summing node would be offset several hundred millivolts from ground. In figure 11, this offset is limited to several millivolts. In addition, the output can be nulled with the usual balance potentiometer. Further, gain trimming is easily done.

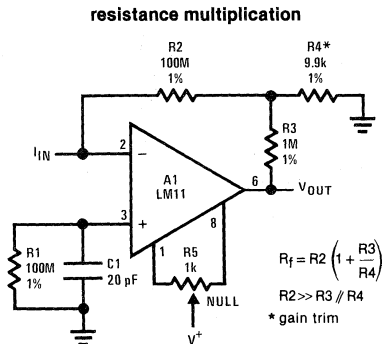

**Figure 11.** Equivalent feedback resistance is 10 GΩ, but only standard resistors are used. Even though the offset voltage is multiplied by 100, output offset is actually reduced because error is dependent on offset current rather than bias current. Voltage on summing junction is less than 5 mV.

This circuit would benefit from lower offset current than can be tested and guaranteed with automatic test equipment. But there should be no problem in selecting a device for critical applications.

#### capacitors

Op amp circuits impose added requirements on capacitors, and this is compounded with high-impedance circuitry. Frequency shaping and charge measuring circuits require control of the capacitor tolerance, temperature drift and stability with temperature cycling. For smaller values, NPO ceramic is best while a polystyrene-polycar-


bonate combination gives good results for larger values over a  $-10^{\circ}\text{C}$  to  $85^{\circ}\text{C}$  range.

Dielectric absorption can also be a problem. It causes a capacitor that has been quick-charged to drift back toward its previous state over many milliseconds. The effect is most noticeable in sample-and-hold circuits. Polystyrene, Teflon and NPO ceramic capacitors are most satisfactory in this regard. Choice depends mainly on capacitance and temperature range.

Insulation resistance can clearly become a problem with high-impedance circuitry. Best performer is Teflon, with polystyrene being a good substitute below  $85^{\circ}\text{C}$ . Mylar capacitors should be avoided, especially where higher temperatures are involved.

Temperature changes can also alter the terminal voltage of a capacitor. Because thermal time constants are long, this is only a problem when holding intervals are several minutes or so. The effect is reported to be as high as  $10 \text{ mV}/^{\circ}\text{C}$ , but Teflon capacitors that hold it to  $0.5 \text{ mV}/^{\circ}\text{C}$  are available\*.

An op amp with lower bias current can ease capacitor problems, primarily by reducing size. This is obvious with a sample and hold because the capacitor value is determined by the hold interval and the amplifier bias current. The circuit in figure 12 is another example. An RC time constant of more than a quarter hour is obtained with standard component values. Even when such long time constants are not required, reducing capacitor size to where NPO ceramics can be used is a great aid in precision work.

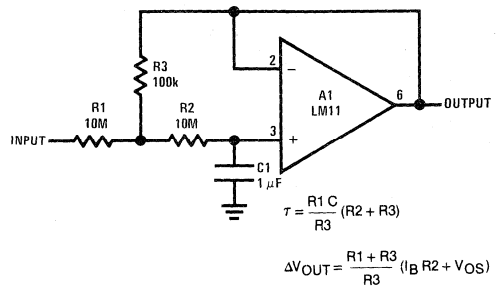

**Figure 12.** This circuit multiplies RC time constant to 1000 seconds and provides low output impedance. Cost is lowered because of reduced resistor and capacitor values.

#### conclusions

A low cost IC op amp has been described that not only has low offset voltage but also advances the state of the art in reducing input current error, particularly at elevated temperatures. Designers of industrial as well as military/space equipment can now work more freely at high impedance levels.

Although high-impedance circuitry is more sensitive to board leakages, wiring capacitances, stray pick-up and leakage in other components, it has been shown how input guarding, bootstrapping, shielding and leakage isolation can largely eliminate these problems.

\* Component Research Co., Inc., Santa Monica, California.

## acknowledgement

The author would like to acknowledge the assistance of the staff at National Semiconductor in implementing this design and sorting out the application problems. Discussions with Bob Dobkin, Bob Pease, Carl Nelson and Mineo Yamatake have been most helpful.

## APPENDIX

### super-gain techniques

Super-gain transistors are not new, having been developed for the LM102/LM110 voltage followers in 1967 and later used on the LM108 general-purpose op amp. They are similar to regular transistors, except that they are diffused for high current gains (2,000–10,000) at the expense of breakdown voltage. A curve-tracer display of a typical device is shown in figure A1. In an IC, super-gain transistors can be made simultaneously with standard

transistors by including a second, light base predeposition that is diffused less deeply.

Super-gain transistors can be connected in cascode with regular transistors to form a composite device with both high gain and high breakdown. The simplified schematic of the LM108 input stage in figure A2 shows how it is done. A common base pair, Q3 and Q4, is bootstrapped to the input transistors, Q1 and Q2, so that the latter are operated at nearly zero collector-base voltage, no matter what the input common-mode. The regular NPN transistors are distinguished by drawing them with wider base regions.

Operating the input transistors at very low collector-base voltage has the added advantage of drastically reducing collector-base leakage. In this configuration bipolar transistors are affected little by the leakage currents that limit performance of FET amplifiers.

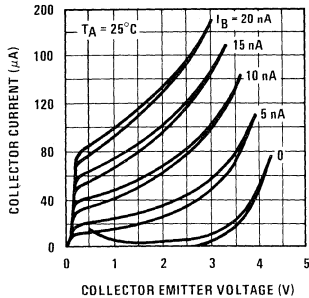


Figure A1. Curve tracer display of a super-gain transistor

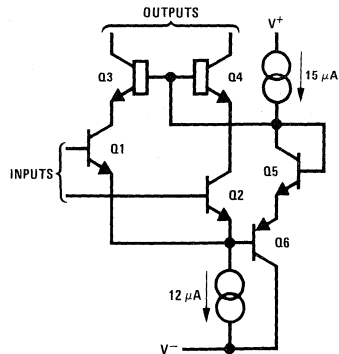


Figure A2. A bootstrapped input stage

# Applying a New Precision Op Amp

National Semiconductor  
Application Note 242  
April 1980



Robert J. Widlar  
Puerto Vallarta, Jalisco  
Mexico

Bob Pease and Mineo Yamatake  
National Semiconductor Corporation  
Santa Clara, California  
U.S.A.

**Abstract:** A new bipolar op amp design has advanced the state of the art by reducing offset voltage and bias current errors. Its characteristics are described here, indicating an ultimate input resolution of  $10 \mu\text{V}$  and  $1 \text{pA}$  under laboratory conditions. Practical circuits for making voltmeters, ammeters, differential instrumentation amplifiers and a variety of other designs that can benefit from the improved performance are covered in detail. Methods of coupling the new device to existing fast amplifiers to take advantage of the best characteristics of both, even in follower applications, are explored.

## Introduction

A low cost, mass-produced op amp with electrometer-type input currents combined with low offset voltage and drift is now available. Designated the LM11, this IC can minimize production problems by providing accuracy without adjustments, even in high-impedance circuitry. On the other hand, if pushed to its full potential, what has been impossible in the past becomes entirely practical.

Significantly, the LM11 is not restricted to commercial and industrial use. Devices can be completely specified over a  $-55^\circ\text{C}$  to  $125^\circ\text{C}$  range. Preliminary data indicates that reliability is the same as standard ICs qualified for military and space applications.


The essential details of the design along with an introduction to the peculiarities of high-impedance circuits have been presented elsewhere\*. This will be expanded here. Practical circuitry that reduces effective bias current for those applications where performance cannot be made dependent on offset current are described. In addition, circuits combining the dc characteristics of the new part with the ac performance of existing fast amplifiers will be shown. This will be capped with a number of practical designs to provide some perspective into what might be done.

## dc errors

Barring the use of chopper or reset stabilization, the best offset voltage, drift and long-term stability are obtained

using bipolar transistors for the op amp input stage. This has been done with the LM11. On-wafer trimming further improves performance. Typically, a  $100 \mu\text{V}$  offset with  $1 \mu\text{V}/^\circ\text{C}$  drift results.

Transistors with typical current gains of 5000 have been used in the manufacture of the LM11. The input stage employs a Darlington connection that has been modified so that offset voltage and drift are not degraded. The typical input currents, plotted in figure 1, demonstrate the value of the approach.

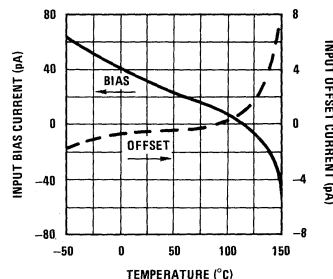

**Figure 1.** Below  $100^\circ\text{C}$ , bias current varies almost linearly with temperature. This means that simple circuitry can be used for compensation. Offset current is unusually low.

The offset current of this op amp is so low that it cannot be measured on existing production test equipment. Therefore, it probably cannot be specified tighter than  $10 \text{pA}$ . For critical applications, the user should have little difficulty in selecting to a tighter limit.

The bias current of the LM11 equals that of monolithic FET amplifiers at  $25^\circ\text{C}$ . Unlike FETs, it does not double every  $10^\circ\text{C}$ . In fact, the drift over a  $-55^\circ\text{C}$  to  $125^\circ\text{C}$  temperature range is about the same as that of a FET op amp during normal warm up.

\*R. J. Widlar, "Working with High Impedance Op Amps", National Semiconductor AN-241.

Other characteristics are summarized in table I. It can be seen that the common-mode rejection, supply-voltage rejection and voltage gain are high enough to take full advantage of the low offset voltage. The unspectacular  $0.3V/\mu s$  slew rate is balanced by the  $300\mu A$  current drain.

**Table I. Typical characteristics of the LM11 for  $T_j = 25^\circ C$  and  $V_S = \pm 15V$ . Operation is specified down to  $V_S = \pm 2.5V$ .**

parameter	conditions	value
input offset voltage		$100\mu V$
input offset current		$500\text{ fA}$
input bias current		$25\text{ pA}$
input noise voltage	$0.01\text{ Hz} \leq f \leq 10\text{ Hz}$	$8\mu V_{pp}$
input noise current	$0.01\text{ Hz} \leq f \leq 10\text{ Hz}$	$1\text{ pApp}$
long term stability	$T_j = 25^\circ C$	$10\mu V$
offset voltage drift	$-55^\circ C \leq T_j \leq 125^\circ C$	$1\mu V/^\circ C$
offset current drift	$-55^\circ C \leq T_j \leq 125^\circ C$	$20\text{ fA}/^\circ C$
bias current drift	$-55^\circ C \leq T_j \leq 125^\circ C$	$500\text{ fA}/^\circ C$
voltage gain	$V_{OUT} = \pm 12V$ , $I_{OUT} = \pm 0.5\text{ mA}$	$1,200V/mV$
	$V_{OUT} = \pm 12V$ , $I_{OUT} = \pm 2\text{ mA}$	$300V/mV$
common-mode rejection	$-12.5V \leq V_{CM} \leq 14V$	$130\text{ dB}$
supply-voltage rejection	$\pm 2.5V \leq V_S \leq \pm 20V$	$118\text{ dB}$
slew rate		$0.3V/\mu s$
supply current		$300\mu A$


As might be expected, the low bias currents were obtained with some sacrifice in noise. But the low frequency noise voltage is still a bit less than a FET amplifier and probably more predictable. The latter is important because this noise cannot be tested in production. Long term measurements have not indicated any drift in excess of the noise. This is not the case for FETs.

It is worthwhile noting that the drift of offset voltage and current is low enough that dc accuracy is noise limited in room-temperature applications.

### bias current compensation

The LM11 can operate from megohm source resistances with little increase in the equivalent offset voltage, as can be seen in figure 2. This is impressive considering the low initial offset voltage. The situation is much improved if the design can be configured so that the op amp sees equal resistance on the two inputs. However, this cannot be done with all circuits. Examples are integrators, sample and holds, logarithmic converters and signal-conditioning amplifiers. And even though the LM11 bias current is low, there will be those applications where it needs to be lower.


Referring back to figure 1, it can be seen that the bias current drift is essentially linear over a  $-50^\circ C$  to  $100^\circ C$  range. This is a deliberate consequence of the input stage design. Because of it, relatively simple circuitry can be used to develop a compensating current.

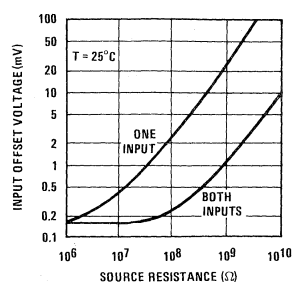


**Figure 2. The LM11 operates from megohm source resistances with little dc error. With equal source resistances, accuracy is essentially limited by low frequency current noise.**

Bias current compensation is not new, but making it effective with even limited temperature excursions has been a problem. An early circuit suggested for bipolar ICs is shown in figure 3a. The compensating current is determined by the diode voltage. This does not vary as rapidly with temperature as bias current nor does it match the usual non-linearities.

With the improved circuit in figure 3b, the temperature coefficient can be increased by using a transistor and including R2. The drop across R2 is nearly constant with temperature. The voltage delivered to the potentiometer has a  $2.2\text{ mV}/^\circ C$  drift while its magnitude is determined by R2. Thus, as long as the bias current varies linearly with temperature, a value for R2 can be found to effect compensation.

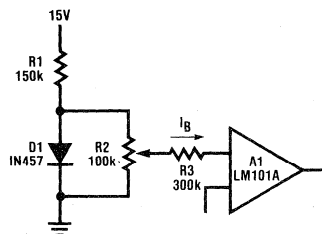

**a. original circuit**

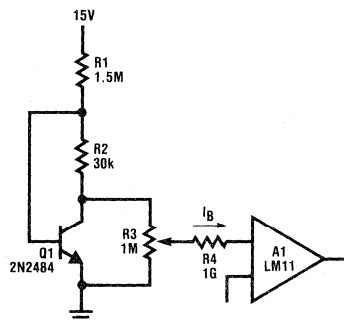


**b. improved version**

**Figure 3. Bias-current compensation. With the improved version, the temperature coefficient of the compensating current can be varied with R2. It is effective only if bias current has linear, negative temperature coefficient.**



In production, altering resistors based on temperature testing is to be avoided if at all possible. Therefore, the results that can be obtained with simple nulling at room temperature and a fixed value for R2 are of interest. Figure 4 gives this data for a range of parts with different initial bias currents. This was obtained from pre-production and initial-production runs. The bias current variations were the result of both  $h_{FE}$  variations and changes in internal operating currents and represent the worst as well as best obtained. They are therefore considered a realistic estimate of what would be encountered among various production lots.

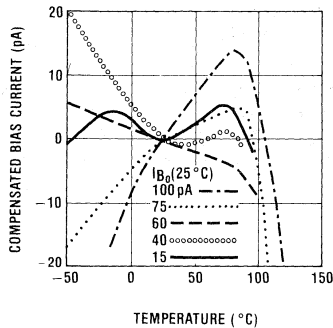


**Figure 4.** Compensated bias current for five representative units with a range of initial bias currents. The circuit in figure 3b was used with balancing at 25°C. High drift devices could be improved further by altering R2.

Little comment need be made on these results, except that the method is sufficiently predictable that another factor of five reduction in worst case bias current could be made by altering R2 based on the results of a single temperature run.

One disadvantage of the new circuit is that it is more sensitive to supply variations than the old. This is no problem if the supplies are regulated to 1%. But with worse regulation it suffers because, with R2, the transistor no longer functions as a regulator and because much tighter compensation is obtained.

The circuit in figure 5 uses pre-regulation to solve this problem. The added reference diode has a low breakdown so that the minimum operating voltage of the op amp is unrestricted. Because of the low breakdown, the drop across R3 can no longer be considered constant. But it will vary linearly with temperature, so this is of no consequence. The fact that this reference can be used for other functions should not be overlooked because a regulated voltage is frequently required in designs using op amps.

In figure 5, a divider is used so that the resistor feeding the compensating current to the op amp can be reduced. There will be an error current developed for any offset voltage change across R6. This should not be a problem with the LM11 because of its low offset voltage. But for tight compensation, mismatch in the temperature characteristics of R4 and R5 must be considered.

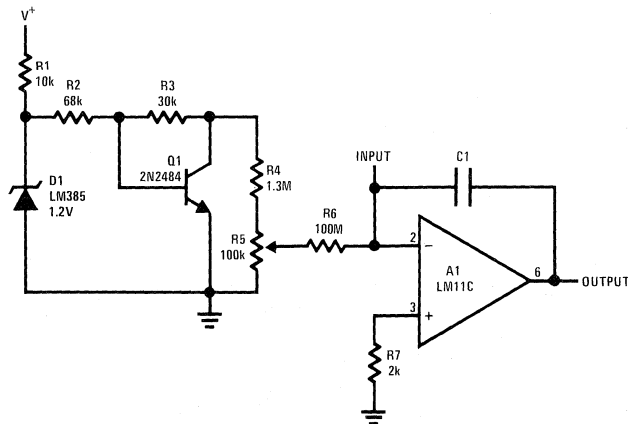

**Figure 5.** Bias current compensation for use with unregulated supplies. Reference voltage is available for other circuitry.

Bias current compensation is more difficult for non-inverting amplifiers because the common-mode voltage varies. With a voltage follower, everything can be bootstrapped to the output and powered by a regulated current source, as shown in figure 6. The LM334 is a temperature sensor. It regulates against voltage changes and its output varies linearly with temperature, so it fits the bill.

Although the LM334 can accommodate voltage changes fast enough to work with the LM11, it is not fast enough for the high-speed circuits to be described. But compensation can still be obtained by using the zener diode pre-regulator bootstrapped to the output and powered by either a resistor or FET current source. The LM385 fits well here because both the breakdown voltage and minimum operating current are low.

With ordinary op amps, the collector base voltage of the input transistors varies with the common-mode voltage. A 50% change in bias current over the common-mode range is not unusual, so compensating the bias current of a

follower has limited value. However, the bootstrapped input stage of the LM11 reduces this to about 2 pA for a  $\pm 20V$  common-mode swing, giving a  $2 \times 10^{13}\Omega$  common-mode input resistance.

### fast amplifiers

A precision dc amplifier, although slow, can be used to stabilize the offset voltage of a less precise fast amplifier. As shown in figure 7, the slow amplifier senses the voltage across the input terminals and supplies a correction signal to the balance terminals of the fast amplifier. The LM11 is particularly interesting in this respect as it does not degrade the input bias current of the composite even when the fast amplifier has a FET input.

Surprisingly, with the LM11, this will work for both inverting and non-inverting connections because its common-mode slew recovery is a lot faster than that of the main loop. This was accomplished, even with circuitry running under 100 nA, by proper clamping and by bootstrapping of internal stray capacitances.

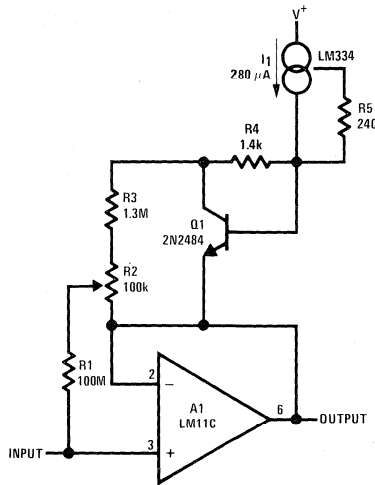


Figure 6. This circuit shows how bias current compensation can be used on a voltage follower.

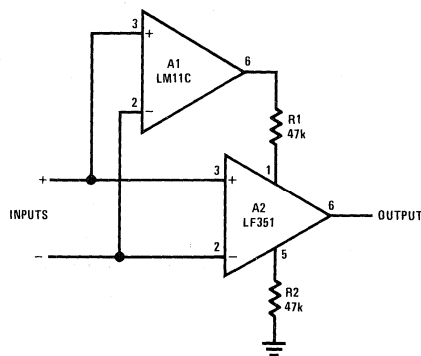


Figure 7. A slow amplifier can be used to null the offset of a fast amplifier.

An optimized circuit for the inverting amplifier connection is shown in figure 8. The LM11 is dc coupled to the input and drives the balance terminals of the fast amplifier. The fast amplifier is ac coupled to the input and drives the output. This isolates FET leakage from the input circuitry.


As can be seen, the method of coupling into the balance terminals will vary depending on the internal configuration of the fast amplifier. If the quiescent voltage on the balance terminals is beyond the output swing of the LM11, a differential coupling must be used, as in figure 8a. A lead capacitor, C2, reduces the ac swing required at the LM11 output. The clamp diode, D1, insures that the LM11 does not overdrive the fast amplifier in slew.

If the quiescent voltage on the balance terminals is such that the LM11 can drive directly, the circuit in figure 8b can be used. A clamp diode from the other balance terminal to internal circuitry of the LM11 keeps the output from swinging too far from the null value, and a resistor may be required in series with its output to insure stability.


Measurements indicate that the slew rate of the fast amplifier is unimpaired, as is the settling time to 1 mV for a 20V output excursion. If the composite amplifier is overdriven so that the output saturates, there will be an added recovery delay because the coupling capacitor to the fast amplifier takes on a charge with the summing node off ground. Therefore, C1 should be made as small as possible. But going below the values given may introduce gain error.

If the bias current of the fast amplifier meets circuit requirements, it can be direct-coupled to the input. In this case, offset voltage is improved, not bias current. But overload recovery can be reduced. The ac coupling to the fast-amplifier input might best be eliminated for limited-temperature-range operation.

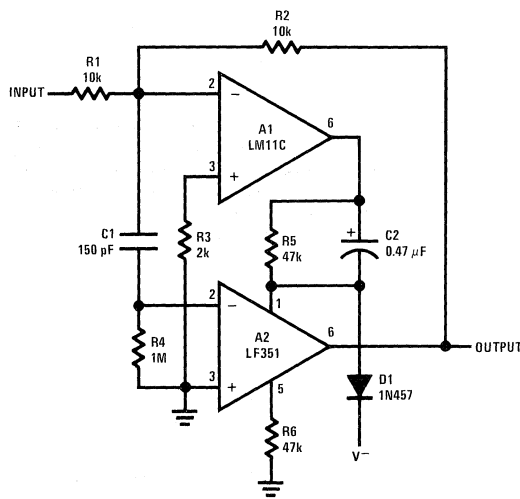This connection also increases the open-loop gain beyond that of the LM11, particularly since two-pole compensation can be effected to reduce ac gain error at moderate frequencies. The dc gains measured showed something in excess of 140 dB.




a. with standard BI-FET

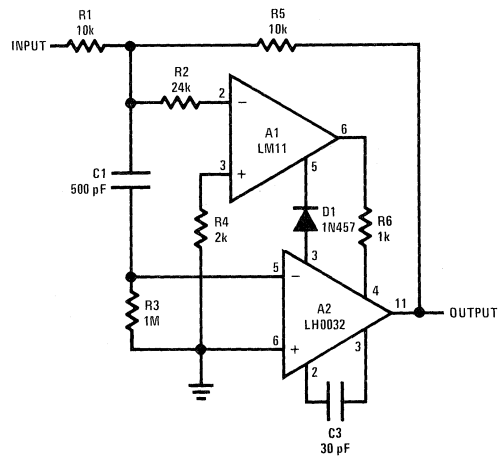

b. with fast hybrid

**Figure 8.** These inverters have bias current and offset voltage of LM11 along with speed of the FET op amps. Open loop gain is about 140 dB and settling time to 1 mV about 8  $\mu$ s. Excess overload-recovery delay can be eliminated by direct coupling the FET amplifier to summing node.

A voltage-follower connection is given in figure 9. The coupling circuitry is similar, except that R5 was added to eliminate glitches in slew. Overload involves driving the fast amplifier outside its common-mode range and should be avoided by limiting the input. Thus, ac coupling the fast amplifier is less a problem. But the repetition frequency of the input signal must also be limited to 10 kHz for  $\pm 10V$  swing. Higher frequencies produce a dc error, believed to result from rectification of the input signal by the voltage sensitive input capacitance of the FET amplifier used. A fast bipolar amplifier like the LM118 should work out better in this respect. To avoid confusion, it should be emphasized that this problem is related to repetition frequency rather than rise time.

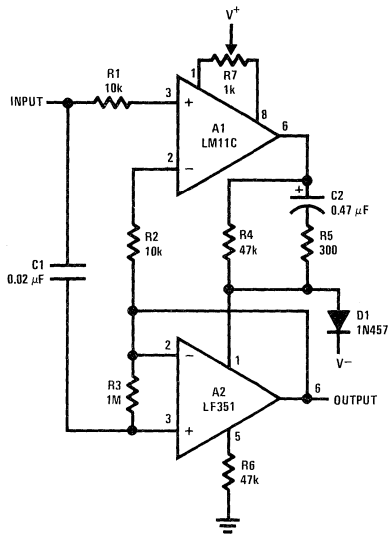

**Figure 9.** Follower has 10  $\mu s$  settling to 1 mV, but signal repetition frequency should not exceed 10 kHz if the FET amplifier is ac coupled to input. The circuit does not behave well if common-mode range is exceeded.


A precision dc amplifier with a 100 MHz gain-bandwidth product is shown in figure 10. It has reasonable recovery ( $\sim 7\mu s$ ) from a 100% overload; but beyond that, ac coupling to the fast amplifier causes problems. Alone, the gain error and thermal feedback of the LH0032 are about 20 mV, input referred, for  $\pm 10V$  output swing. Adding the LM11 reduces this to microvolts.

#### picoammeter


Ideally, an ammeter should read zero with no input current and have no voltage drop across its inputs even with full-scale deflection. Neither should spurious indications nor inaccuracy result from connecting it to a low impedance. Meeting all these requirements calls for a dc amplifier, and one in which both bias current and offset voltage are controlled.

The summing amplifier connection is best for measuring current, because it minimizes the voltage drop across the

input terminals. However, when the inputs are shorted, the output state is indeterminate because of offset voltage. Adding degeneration as shown in figure 11 takes care of this problem. Here, R2 is the feedback resistor for the most sensitive range, while R1 is chosen to get the meter deflection out of the noise with a shorted input. Adding the range resistor, as shown, does not affect the degeneration, so that there is minimal drop across the input for full-scale on all ranges.

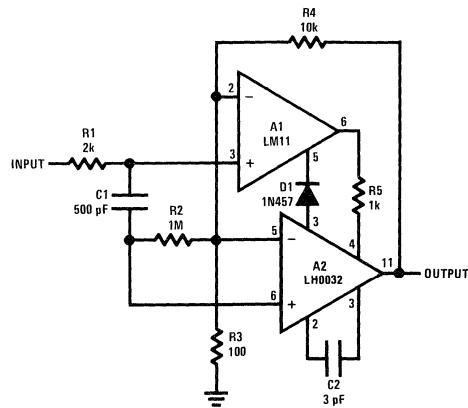

**Figure 10.** This 100X amplifier has small and large signal bandwidth of 1 MHz. The LM11 greatly reduces offset voltage, bias current and gain error. Eliminating long recovery delay for greater than 100% overload requires direct coupling of A2 to input.

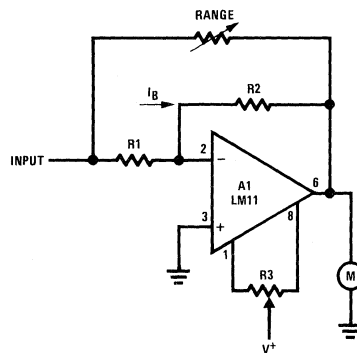

**Figure 11.** An ammeter that has constant voltage drop across its input at full-scale, no matter what the range. It can have a reasonably-behaved output even with shorted inputs, yet a maximum drop of ten times the op amp noise voltage.

The complete meter circuit in figure 12 uses a different scheme. A floating supply is available so that the power ground and the signal ground can be separated with R12. At full-scale, the meter current plus the measured current flow through this resistor, establishing the degeneration. This method has the advantage of allowing even-value range resistors on the lower ranges but increases degeneration as the measured current approaches the meter current.

Bias-current compensation is used to increase the meter sensitivity so there are two zeroing adjustments; current balancing, that is best done on the most sensitive range where it is needed, and voltage balancing that should be done with the inputs shorted on a range below 100  $\mu$ A, where the degeneration is minimal.

With separate grounds, error could be made dependent on offset current. This would eliminate bias-current compensation at the expense of more complicated range switching.

The op amp input has internal, back-to-back diodes across it, so R6 is added to limit current with overloads. This type of protection does not affect operation and is recommended whenever more than 10 mA is available to the inputs. The output buffers are added so that input overloads cannot drag down the op amp output on the least-sensitive range, giving a false meter indication. These would not be required if the maximum input current did not approach the output current limit of the op amp.


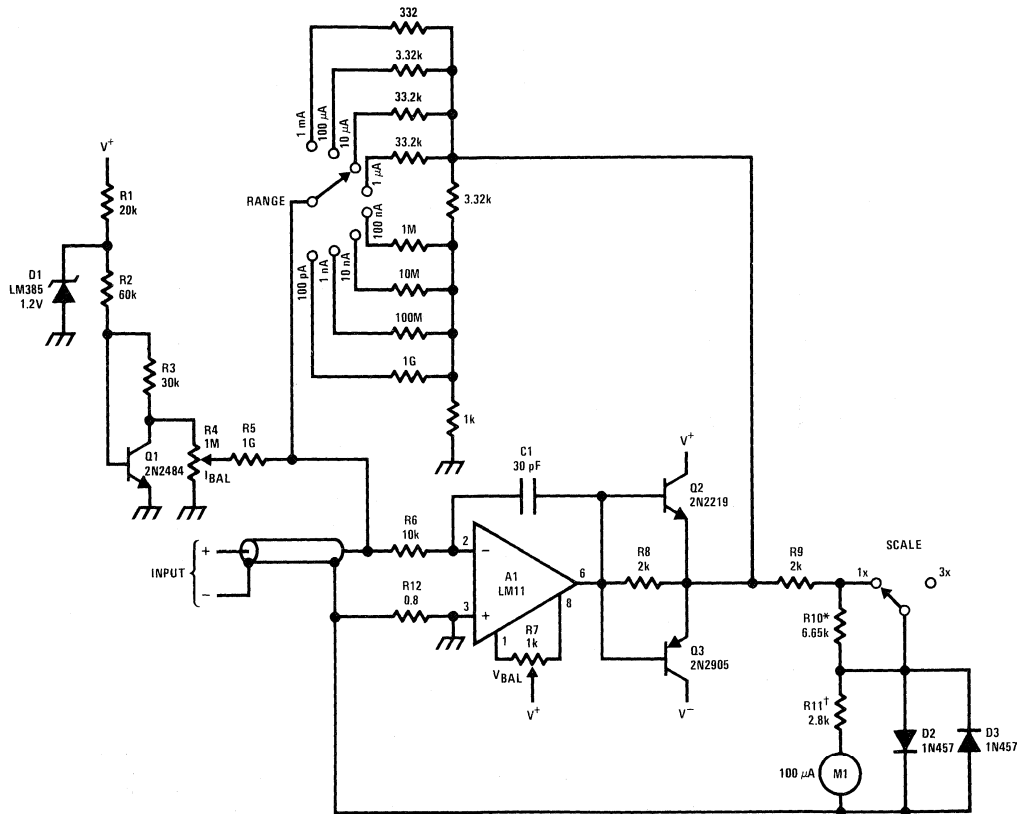


Figure 12. Current meter ranges from 100 pA to 3 mA, full-scale. Voltage across input is 100  $\mu$ V at lower ranges rising to 3 mV at 3 mA. Buffers on op amp are to remove ambiguity with high-current overload. Output can also drive DVM or DPM.


## millivoltmeter

An ideal voltmeter has requirements analogous to those discussed for the ammeter, and figure 13 shows a circuit that will satisfy them. In the most-sensitive position, the range resistor is zero and the input resistance equals R1. As voltage measurement is desensitized by increasing the range resistor, the input resistance is also increased, giving the maximum input resistance consistent with zero stability with the input open. Thus, at full-scale, the source will be loaded by whatever multiple of the noise current is required to give the desired open-input zero stability.

This technique is incorporated into the voltmeter circuit in figure 14 to give a 100 MΩ input resistance on the 1 mV scale rising to 300 GΩ on the 3V scale. The separation of power and signal grounds has been used here to simplify bias-current compensation. Otherwise, a separate op amp would be required to bootstrap the compensation to the input.

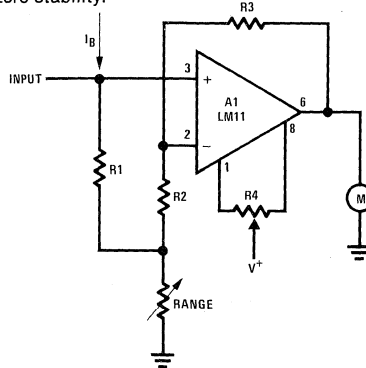

**Figure 13.** This voltmeter has constant full-scale loading independent of range. This can be only ten times the noise current, yet the output will be reasonably behaved for open input.

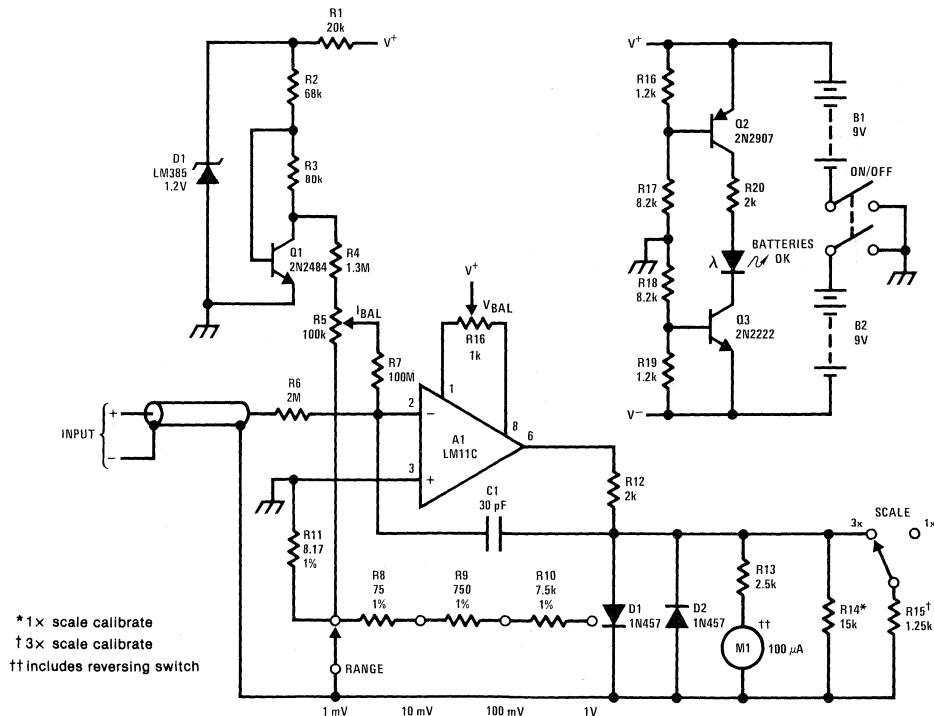

**Figure 14.** High input impedance millivoltmeter. Input current is proportional to input voltage, about 10 pA at full-scale. Reference could be used to make direct reading linear ohmmeter.

The input resistor, R6, serves two functions. First, it protects the op amp input in the event of overload. Second, it insures that an overload will not give a false meter indication until it exceeds a couple hundred volts.

Since the reference is bootstrapped to the input, this circuit is easily converted into a linear, direct-reading ohmmeter. A resistor from the top of D1 to the input establishes the measurement current so that the voltage drop is proportional to the resistance connected across the input.

#### current sources

The classical op amp circuit for voltage-to-current conversion is shown in figure 15. It is presented here because the

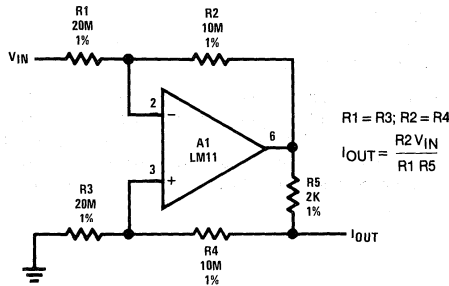


Figure 15. Output resistance of this voltage/current converter depends both on high value feedback resistors and their matching.

output resistance is determined by both the matching and the value of the feedback resistors. With the LM11, these resistors can be raised while preserving dc stability.

While the circuit in figure 15 can provide bipolar operation, better performance can be obtained with fewer problems if a unipolar output is acceptable. A complete, battery-powered current source suitable for laboratory use is given in figure 16 to illustrate this approach. The op amp regulates the voltage across the range resistors at a level determined by the voltage on the arm of the calibrated potentiometer, R3. The voltage on the range resistors is established by the current through Q2 and Q3, which is delivered to the output.

The reference diode, D1, determines basic accuracy. Q1 is included to insure that the LM11 inputs are kept within the common-mode range with diminishing battery voltage. A light-emitting diode, D2, is used to indicate output saturation. However, this indication cannot be relied upon for output-current settings below about 20 nA unless the value of R6 is increased. The reason is that very low currents can be supplied to the range resistors through R6 without developing enough voltage drop to turn on the diode.

If the LED illuminates with the output open, there is sufficient battery voltage to operate the circuit. But a battery-test switch is also provided. It is connected to the base of the op amp output stage and forces the output toward V<sup>+</sup>.

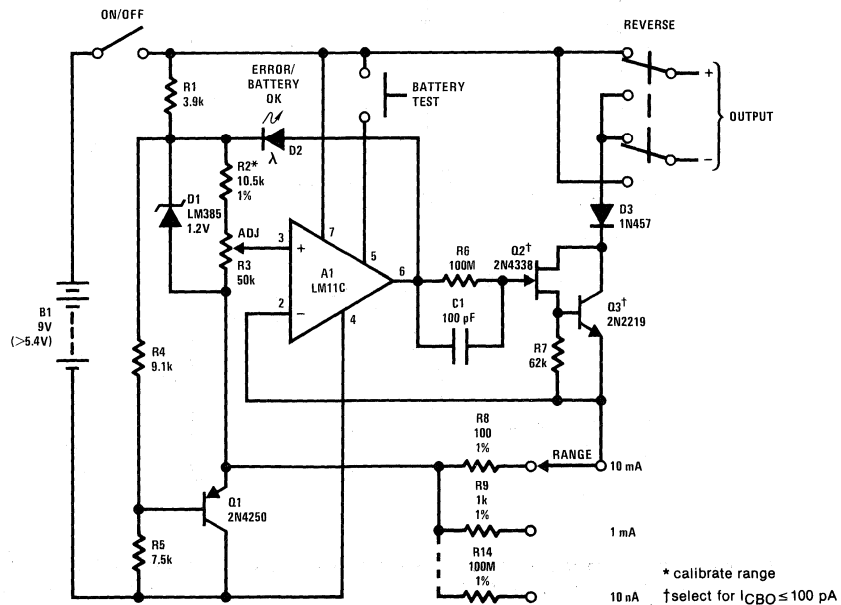


Figure 16. Precision current source has 10 nA to 10 mA ranges with output compliance of 30V to -5V. Output current is fully adjustable on each range with a calibrated, ten-turn potentiometer. Error light indicates output saturation.





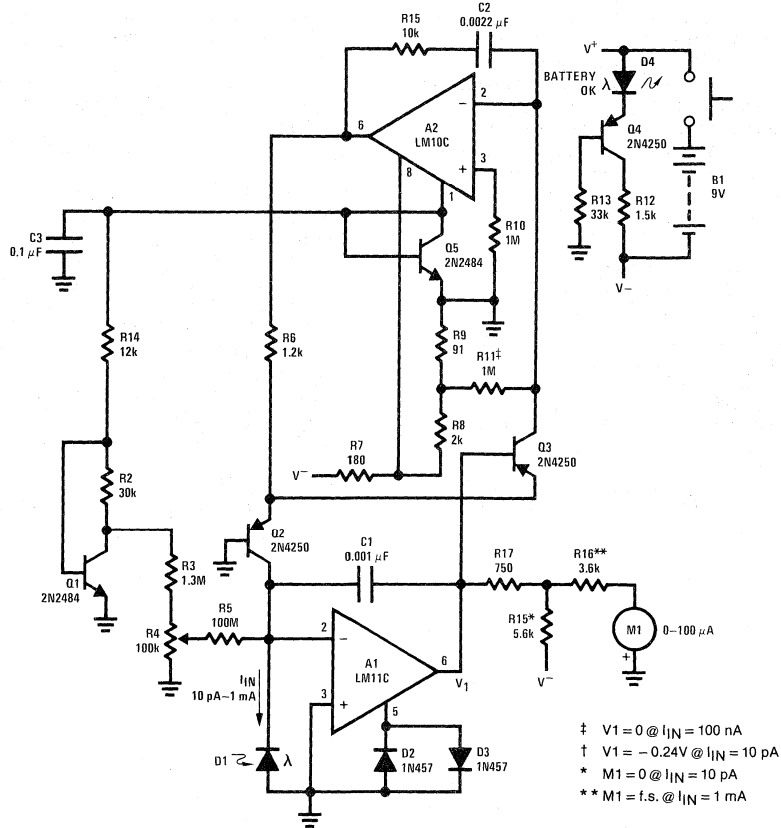


Figure 18. Light meter has eight-decade range. Bias current compensation can give input current resolution of better than  $\pm 2$  pA over  $15^\circ\text{C}$  to  $55^\circ\text{C}$ .

Figure 19 shows the classic op amp differential amplifier connection. It is not widely used because the input resistance is much lower than alternate methods. But when the input common-mode voltage exceeds the supply voltage for the op amp, this cannot be avoided. At least with the LM11, large feedback resistors can be used to reduce loading without affecting dc accuracy. The impedances looking into the two inputs are not always the same. The values given equalize them for common-mode signals because they are usually larger. With single-ended inputs, the input resistance on the inverting input is  $R_1$ , while that on the non-inverting input is the sum of  $R_2$ ,  $R_4$  and  $R_5$ .

Provision is made to trim the circuit for maximum dc and ac common-mode rejection. This is advised because well matched high-value resistors are hard to come by and because unbalanced stray capacitances can cause severe deterioration of ac rejection with such large values. Particular attention should be paid to resistor tracking over temperature as this is more of a problem with high-value resistors. If higher gain or gain trim is required,  $R_6$  and  $R_7$  can be added.


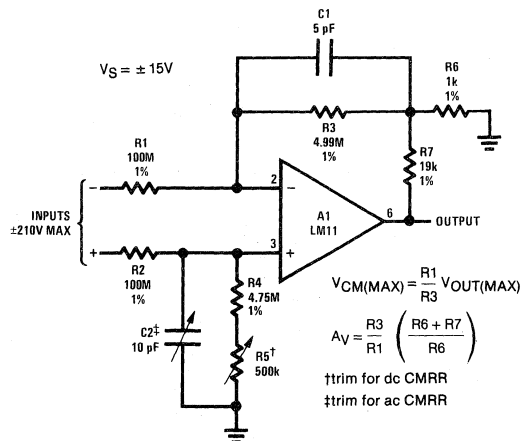


Figure 19. This differential amplifier handles high input voltages. Resistor mismatches and stray capacitances should be balanced out for best common-mode rejection.

The simplest connection for making a high-input-impedance differential amplifier using op amps is shown in figure 20. Its main disadvantage is that the common-mode signal on the inverting input is delayed by the response of A1 before being delivered to A2 for cancellation. A selected capacitor across R1 will compensate for this, but ac common-mode rejection will deteriorate as the characteristics of A1 vary with temperature.

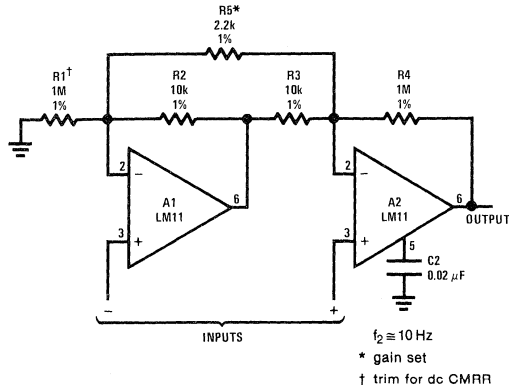

**Figure 20. Two-op-amp instrumentation amplifier has poor ac common-mode rejection. This can be improved at the expense of differential bandwidth with C2.**


When slowly varying differential signals are of interest, the response of A2 can be rolled off with C2 to reduce the

sensitivity of the circuit to high frequency common-mode signals. If single-resistor gain setting is desired, R5 can be added. Otherwise, it is unnecessary.

A full-blown differential amplifier with extremely high input impedance is shown in figure 21. Gain is fixed at 1000, but it can be varied with R10. Differential offset balancing is provided on both input amplifiers by R18.

The ac common-mode rejection is dependent on how well the frequency characteristics of A2 and A3 match. This is a far better situation than encountered with the previous circuit. When ac rejection must be optimized, amplifier differences as well as the effects of unbalanced stray capacitances can be compensated for with a capacitor across R13 or R14, depending on which side is slower. Alternately, C1 can be added to control the differential bandwidth and make ac common-mode rejection less dependent on amplifier matching. The value shown gives approximately 100 Hz differential bandwidth, although it will vary with gain setting.

A separate amplifier is used to drive the shields of the input cables. This reduces cable leakage currents and spurious signals generated from cable flexing. It may also be required to neutralize cable capacitance. Even short cables can attenuate low-frequency signals with high enough source resistance. Another balance potentiometer, R8, is included so that resistor mismatches in the drive to the bootstrapping amplifier can be neutralized. Adding the bootstrapping amplifier also provides a connection point, as shown, for bias-current compensation if the ultimate in performance is required.

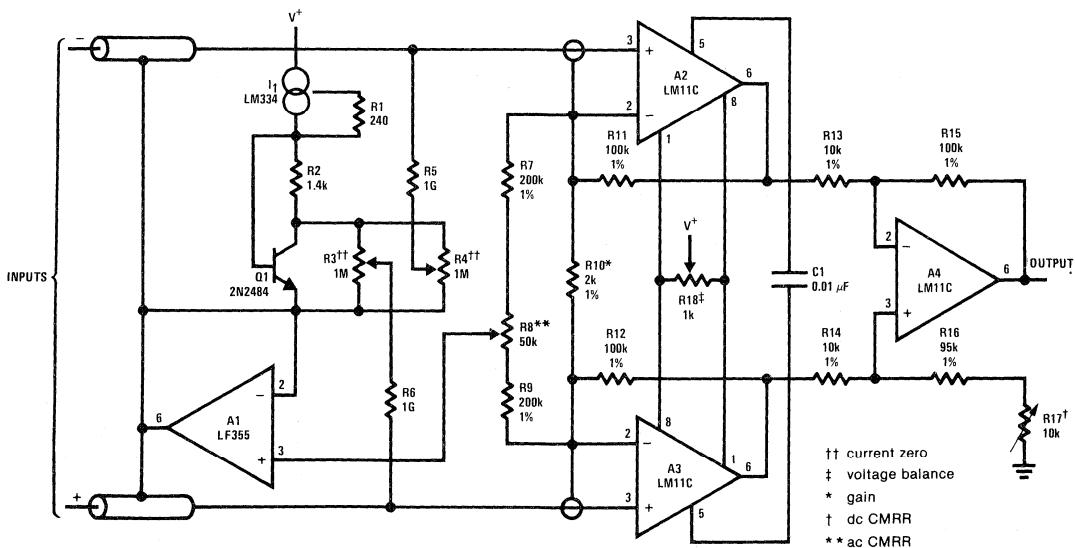

**Figure 21. High gain differential instrumentation amplifier includes input guarding, cable bootstrapping and bias current compensation. Differential bandwidth is reduced by C1 which also makes common-mode rejection less dependent on matching of input amplifiers.**

As can be seen in figure 22, connecting the input amplifiers as follows simplifies the circuit considerably. But single resistor gain control is no longer available and maximum bandwidth is less with all the gain developed by A3. Resistor matching is more critical for a given common-mode rejection, but ac matching of the input amplifiers is less a problem. Another method of trimming ac common-mode rejection is shown here.

#### integrator reset

When pursuing the ultimate in performance with the LM11, it becomes evident that components other than the op amp can limit performance. This can be the case when semiconductor switches are used. Their leakage easily exceeds the bias current when elevated temperatures are involved.

The integrator with electrical reset in figure 23 gives a solution to this problem. Two switches in series are used to shunt the integrating capacitor. In the off state, one switch, Q2, disconnects the output while the other, Q1, isolates the leakage of the first. This leakage is absorbed by R3. Only the op amp offset appears across the junctions of Q1, so its leakage is reduced by two orders of magnitude.

A junction FET could be used for Q1 but not for Q2 because there is no equivalent to the enhancement mode MOSFET. The gate of a JFET must be reverse biased to turn it off and leakage on its output cannot be avoided.

MOS switches with gate-protection diodes are preferred in production situations as they are less sensitive to

damage from static charges in handling. If used, D1 and R2 should be included to remove bias from the internal protection diode when the switch is off.

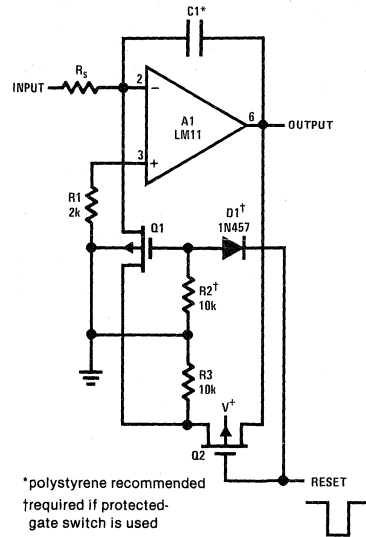


Figure 23. Reset is provided for this integrator and switch leakage is isolated from the summing junction. Greater precision can be provided if bias-current compensation is included.

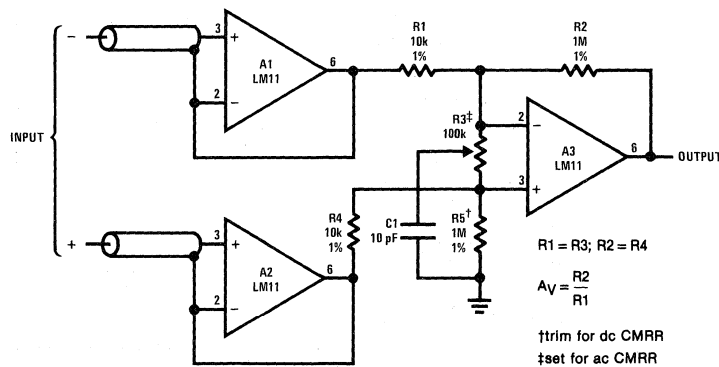


Figure 22. For moderate-gain instrumentation amplifiers, input amplifiers can be connected as follows. This simplifies circuitry, but A3 must also have low drift.




Temperature sensing is done with a bridge, one leg of which is formed by an IC temperature sensor, S1, and a reference diode, D1. Frequency stabilization is done with C2 providing a lag that is finally broken out by C1. If the control transistor, Q2, is put inside the oven for maximum heating efficiency, some level of regulation is suggested for the heater supply when precise control is required. With Q2 in the oven, abrupt supply changes will alter heating, which must be compensated for by the loop. This takes time, causing a small temperature transient.


Because the input bias current of the LM11 does not increase with temperature, it can be installed inside the oven for best performance. In fact, when an oven is available in a piece of equipment, it would be a good idea to put all critical LM11s inside the oven if the temperature is less than 100°C.

#### ac amplifier

Figure 26 shows an op amp used as an ac amplifier. It is unusual in that dc bootstrapping is used to obtain high input resistance without requiring high-value resistors. In theory, this increases the output offset because the op amp offset voltage is multiplied by the resistance boost.

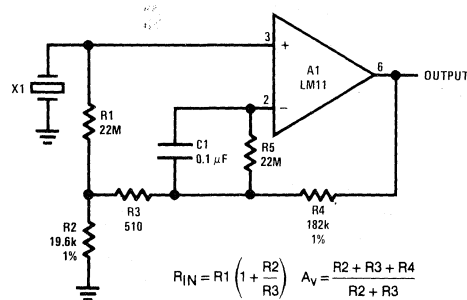

**Figure 26.** A high input impedance ac amplifier for a piezoelectric transducer. Input resistance of 880 MΩ and gain of 10 is obtained.

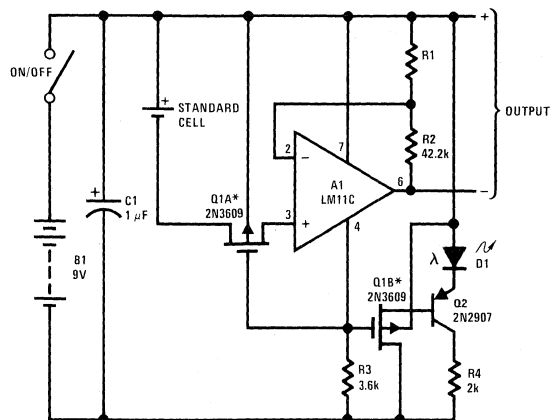

\* cannot have gate protection diode;  $V_{TH} > V_{OUT}$

**Figure 27.** Battery powered buffer amplifier for standard cell has negligible loading and disconnects cell for low supply voltage or overload on output. Indicator diode extinguishes as disconnect circuitry is activated.

But when conventional resistor values are used, it is practical to include R5 to eliminate bias-current error. This gives less output offset than if a single, large resistor were used. C1 is included to reduce noise.

#### standard cell buffer

The accuracy and lifetime of a standard cell deteriorate with loading. Further, with even a moderate load transient, recovery is measured in minutes, hours or even days. The circuit in figure 27 not only buffers the standard cell but also disconnects it in the event of malfunction.

The fault threshold is determined by the gate turn-on voltage of Q1. As the voltage on the gate approaches the threshold either because of low battery voltage or excessive output loading, the MOS switch will begin to turn off. At the turn off threshold, the output voltage can rise because of amplifier bias current flowing through the increasing switch resistance. Therefore, a LED indicator is included that extinguishes as the fault condition is approached. The MOS threshold should be higher than the buffer output so that the disconnect and error indicator operates before the output saturates.

### **conclusions**

Although the LM11 does not provide the ultimate in performance in either offset voltage or bias current for nominal room temperature applications, the combination offered is truly noteworthy. With significant temperature excursions, the results presented here are much more impressive. With full-temperature-range operation, this device does represent the state of the art when high-impedance circuitry is involved.

Combining this new amplifier with fast op amps to obtain the best features of both is also interesting, particularly since the composite works well in both the inverting and non-inverting modes. However, making high-impedance circuits fast is no simple task. If higher temperatures are not involved, using the LM11 to reduce the offset voltage of a FET op amp without significantly increasing bias current may be all that is required.

An assortment of measurement and computational circuits making use of the unique capabilities of this IC were presented. These circuits have been checked out and the results should be of some value to those working with high impedances. These applications are by no means all-inclusive, but they do show that an amplifier with low input current can be used in a wide variety of circuits.

Although emphasis was on high-performance circuits requiring adjustments, the LM11 will see widest usage in less demanding applications where its low initial offset voltage and bias current can eliminate adjustments.

### **acknowledgement**

The authors would like to thank Dick Wong for his assistance in building and checking out the applications described here.

# Instrumentation Amplifier

National Semiconductor  
Linear Brief 1  
Robert C. Dobkin  
March 1969



The differential input single-ended output instrumentation amplifier is one of the most versatile signal processing amplifiers available. It is used for precision amplification of differential dc or ac signals while rejecting large values of common mode noise. By using integrated circuits, a high level of performance is obtained at minimum cost.

Figure 1 shows a basic instrumentation amplifier which provides a 10 volt output for 100 mV input, while rejecting greater than  $\pm 11V$  of common mode noise. To obtain good input characteristics, two voltage followers buffer the input signal. The

LM102 is specifically designed for voltage follower usage and has  $10,000 M\Omega$  input impedance with  $3 nA$  input currents. This high of an input impedance provides two benefits: it allows the instrumentation amplifier to be used with high source resistances and still have low error; and it allows the source resistances to be unbalanced by over 10,000 ohms with no degradation in common mode rejection. The followers drive a balanced differential amplifier, as shown in Figure 1, which provides gain and rejects the common mode voltage. The gain is set by the ratio of  $R_4$  to  $R_2$  and  $R_5$  to  $R_3$ . With the values shown, the gain for differential signals is 100.

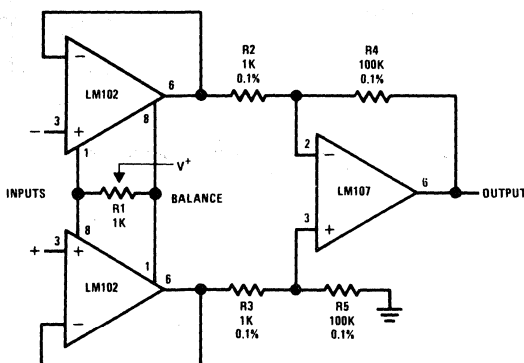


FIGURE 1. Differential-Input Instrumentation Amplifier

Figure 2 shows an instrumentation amplifier where the gain is linearly adjustable from 1 to 300 with a single resistor. An LM101A, connected as a fast inverter, is used as an attenuator in the feedback loop. By using an active attenuator, a very low impedance is always presented to the feedback resistors, and common mode rejection is unaffected by gain changes. The LM101A, used as shown, has a greater bandwidth than the LM107, and may be used in a feedback network without instability. The gain is linearly dependent on  $R_6$  and is equal to  $10^{-4} R_6$ .

To obtain good common mode rejection ratios, it is necessary that the ratio of  $R_4$  to  $R_2$  match the ratio of  $R_5$  to  $R_3$ . For example, if the resistors in circuit shown in Figure 1 had a total mismatch of 0.1%, the common mode rejection would be 60 dB times the closed loop gain, or 100 dB. The circuit shown in Figure 2 would have constant common

mode rejection of 60 dB, independent of gain. In either circuit, it is possible to trim any one of the resistors to obtain common mode rejection ratios in excess of 100 dB.

For optimum performance, several items should be considered during construction.  $R_1$  is used for zeroing the output. It should be a high resolution, mechanically stable potentiometer to avoid a zero shift from occurring with mechanical disturbances. Since there are several ICs operating in close proximity, the power supplies should be bypassed with .01  $\mu$ F disc capacitors to insure stability. The resistors should be of the same type to have the same temperature coefficient.

A few applications for a differential instrumentation amplifier are: differential voltage measurements, bridge outputs, strain gauge outputs, or low level voltage measurement.

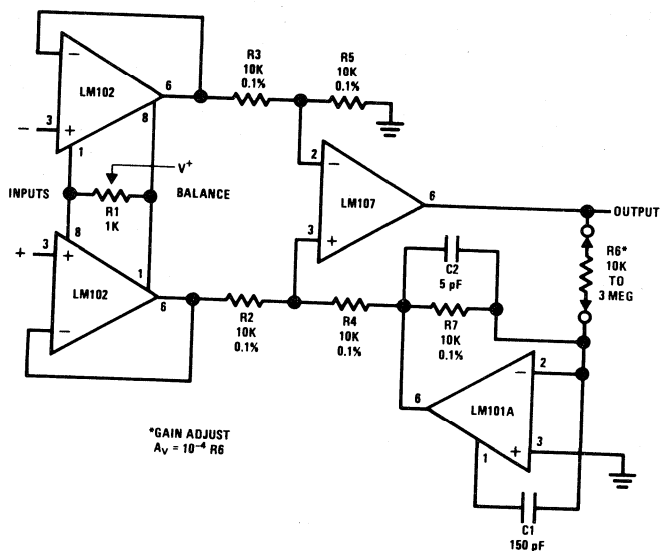


FIGURE 2. Variable Gain, Differential-Input Instrumentation Amplifier



# Feedforward Compensation Speeds Op Amp

National Semiconductor  
 Linear Brief 2  
 Robert C. Dobkin  
 March 1969



A feedforward compensation method increases the slew rate of the LM101A from  $0.5/\mu\text{s}$  to  $10\text{V}/\mu\text{s}$  as an inverting amplifier. This extends the usefulness of the device to frequencies an order of magnitude higher than the standard compensation network. With this speed improvement, IC op amps may be used in applications that previously required discretes. The compensation is relatively simple and does not change the offset voltage or current of the amplifier.

In order to achieve unconditional closed loop stability for all feedback connections, the gain of an operational amplifier is rolled off at 6 dB per octave, with the accompanying 90 degrees of phase shift, until a gain of unity is reached. The frequency compensation networks shape the open loop response to cross unity gain before the amplifier phase shift exceeds 180 degrees. Unity gain for the LM101A is designed to occur at 1 MHz. The reason for this is the lateral PNP transistors used for level shifting have poor high frequency response and exhibit excess phase shift about 1 MHz. Therefore, the stable closed loop bandwidth is limited to approximately 1 MHz.

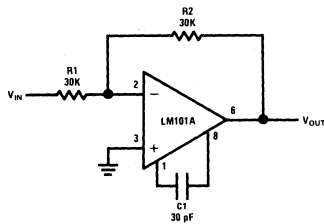


FIGURE 1. Standard Frequency Compensation

Usually, the LM101A is frequency compensated by a single 30 pF capacitor between Pins 1 and 8, as shown in Figure 1. This gives a slew rate of  $0.5\text{V}/\mu\text{s}$ . The feedforward is achieved by connecting a 150 pF capacitor between the inverting input, Pin 2, and one of the compensation termi-

nals, Pin 1, as shown in Figure 2. This eliminates the lateral PNP's from the signal path at high frequencies. Unity gain bandwidth is 10 MHz and the slew rate is  $10\text{V}/\mu\text{s}$ . The diode can be added to improve slew with high speed input pulses.

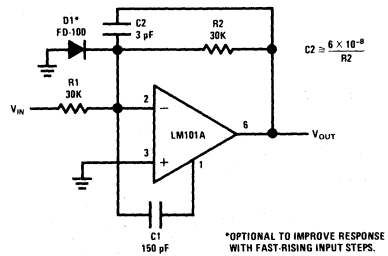


FIGURE 2. Feedforward Frequency Compensation

Figure 3 shows the open loop response in the high and low speed configuration. Higher open loop gain is realized with the fast compensation, as the gain rolls off at about 6 dB per octave until a gain of unity is reached at about 10 MHz. Figures 4 and 5 show the small signal and large signal transient response. There is a small amount of ringing; however, the amplifier is stable over a  $-55^\circ\text{C}$  to  $+125^\circ\text{C}$  temperature range. For comparison, large signal transient response with 30 pF frequency compensation is shown in Figure 6.

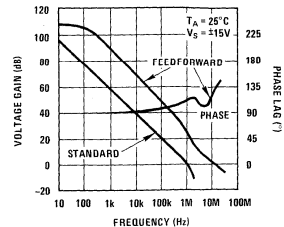


FIGURE 3. Open Loop Response for Both Frequency Compensation Networks

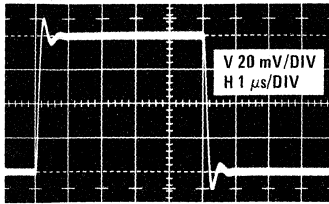


FIGURE 4. Small Signal Transient Response with Feedforward Compensation

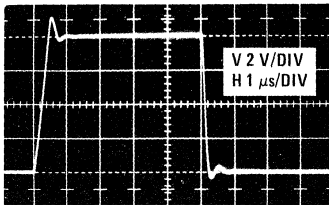


FIGURE 5. Large Signal Transient Response with Feedforward Compensation

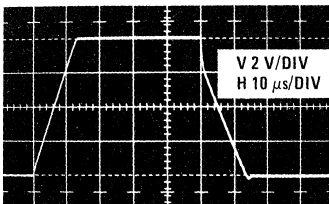


FIGURE 6. Large Signal Transient Response with Standard Compensation

As with all high frequency, high-gain amplifiers, certain precautions should be taken to insure stable operation. The power supplies should be bypassed near the amplifier with  $.01 \mu\text{F}$  disc capacitors. Stray capacitance, such as large lands on printed circuit boards, should be avoided at Pins 1, 2, 5, and 8. Load capacitance in excess of  $75 \text{ pF}$  should be decoupled, as shown in Figure 7; however,  $500 \text{ pF}$  of load capacitance can be tolerated without decoupling at the expense of bandwidth

by the addition of  $3 \text{ pF}$  between Pins 1 and 8. A small capacitor  $C_2$  is needed as a lead across the feedback resistor to insure that the rolloff is less than  $12 \text{ dB}$  per octave at unity gain. The capacitive reactance of  $C_2$  should equal the feedback resistance between 2 and 3 MHz. For integrator applications, the lead capacitor is isolated from the feedback capacitor by a resistor, as shown in Figure 8.

Feedforward compensation offers a marked improvement over standard compensation. In addition to having higher bandwidth and slew, there is vanishingly small gain error from DC to  $3 \text{ kHz}$ , and less than  $1\%$  gain error up to  $100 \text{ kHz}$  as a unity gain inverter. The power bandwidth is also extended from  $6 \text{ kHz}$  to  $250 \text{ kHz}$ . Some applications for this type of amplifier are: fast summing amplifier, pulse amplifier, D/A and A/D systems, and fast integrator.

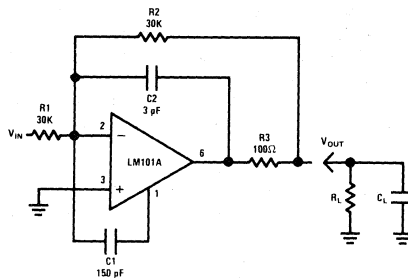


FIGURE 7. Capacitive Load Isolation

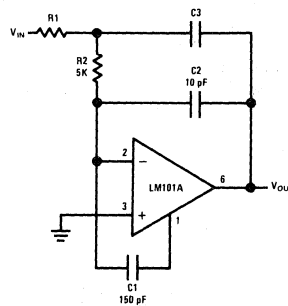


FIGURE 8. Fast Integrator

## Worst Case Power Dissipation in Linear Regulators

National Semiconductor  
 Linear Brief 3  
 April 1969



The most frequent cause of failures of voltage regulators is excessive dissipation in the semiconductor components. Regulators using integrated circuits are no exception to this. In fact, IC regulators are more prone to overdissipation because they are not generally available in power packages, because complete integrated circuits must be operated at a lower, maximum junction temperature than silicon power transistors, and because the package must be able to dissipate the quiescent operating power of the control circuitry in addition to the power in the pass transistor.

The problems and solutions presented here give examples of the worst case calculations that should be used in designing voltage regulators with ICs. These questions were used in a contest sponsored by National Semiconductor. The entries received clearly showed that engineers have a marked tendency to be overly optimistic about the dissipation capability of the IC regulators as well as the power ratings of the external power transistors used with them. In a surprising number of cases the errors were of such a magnitude to cause almost certain, premature failure of the regulator under the conditions specified. The questions and answers follow:

1. What is the power limited full-load current for a 24V regulator using the LM100 (without a heat sink) when the worst case operating conditions are 125°C ambient and 40V input voltage?

The maximum chip temperature of the LM100 is 150°C, and the thermal resistance of the TO-5 package is 150°C/W when no heat sink is used. The permissible, junction-to-ambient temperature rise is 25°C with a 125°C ambient, so the maximum allowable package dissipation is 167 mW.

The worst case quiescent current of the LM100 is 3.0 mA. With a 40V input voltage, this produces an internal dissipation of 120 mW, even with no load. Therefore, the device can only dissipate another 47 mW in supplying the load current. With 40V in and 24V out, the input-output voltage differential is 16V. This means that 2.95 mA can be supplied through the internal pass transistor without exceeding the ratings.

The divider resistors required on the LM100 feedback to give a 24V output are 26.6k and 2.1k. For a 1.8V sense voltage on the feedback terminal, the divider current will be 0.85 mA. Since this current must be supplied by the integrated circuit, it must be subtracted from the available load current. Hence the maximum output current, taking into account worse case conditions, is 2.1 mA.

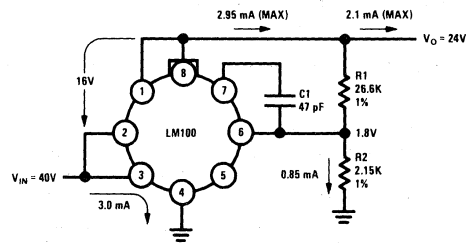


FIGURE 1. Circuit Used in the Solution of Question 1.

2. What is the maximum allowable short-circuit current for an LM104 regulator circuit, with a 2N2905A series pass transistor (without a heat sink) when the worst case input is 20V at an ambient of 85°C?

The 2N2905A, without a heat sink, can dissipate a maximum of 0.6W at 25°C. However, this must be derated by 3.42 mW/°C for operation at higher temperatures. Since an 85°C ambient is 60°C higher than the temperature at which the transistors are specified, the maximum power rating must be reduced by 205 mW, to 395 mW. With a shorted output, the voltage dropped across the current limit sense resistor is 0.5V, so the voltage across the external pass transistor will be 19.5V for 20V input. This means that the 395 mW maximum dissipation rating will be exceeded for short-circuit currents greater than 20.2 mA.

3. In the previous example, what is the maximum current when the case temperature of the 2N2905A is held to 100°C?

The maximum dissipation of the 2N2905A is 3W at 25°C case temperature, but this must be derated by 17.2 mW/°C for higher case temperatures. With a 100°C case temperature, the allowable dissipation is reduced by 1.29W to 1.71W.

As in the previous example, the voltage across the pass transistor will be 19.5V. This gives a dissipation-limited short-circuit current of 88 mA.

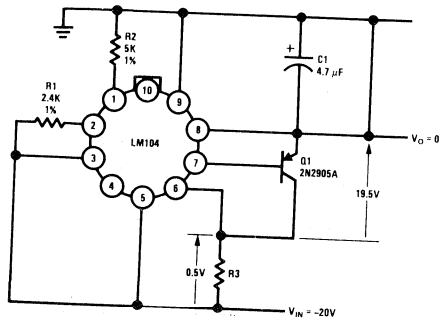


FIGURE 2. Circuit Used in the Solution of Questions 2 and 3.

4. In the negative regulator with foldback current limiting, what will be the worst case dissipation in the PNP driver, Q<sub>1</sub>, with full load and a 24V input voltage?

The 2N3772 is specified to have a minimum current gain of 15 at 10A and 25°C. It would be reasonable to assume a minimum current gain of 15 at 5A for elevated temperatures

where dissipation is most significant. This means that the base current for a 5A load current will be 0.33A. The worst case emitter-base voltage of the 2N3772 at 5A will be about 1V, so the current through the 68Ω emitter-base resistor will be 15 mA. Hence, the PNP driver must supply a total current of 345 mA.

The voltage dropped across the PNP driver will be the 12V input output voltage differential, less the 1V dropped across the current sense resistor and the 1V dropped across the emitter-base junction of the 2N3772. Therefore, the PNP driver operates with 10V across it and dissipates about 3.5W.

5. Could a 2N2905A be used in the example above if the maximum ambient were 85°C?

Even with an infinite heat sink, the 2N2905A can dissipate only 2W at 85°C. Therefore, it cannot be used.

The answers to these questions show that the maximum output current of a regulator can be substantially less than might be expected from a cursory analysis of the circuit. Detailed analysis under worst case conditions is necessary to insure a reliable design. These calculations are more important than most other design calculations because errors do not result in somewhat degraded performance that usually shows up in checking out the equipment. Instead, these errors cause failures that do not always show up during checkout, but can occur in field operation.

Additional information on the design of reliable voltage regulators is given in application notes AN-21 and AN-23, available from National Semiconductor.

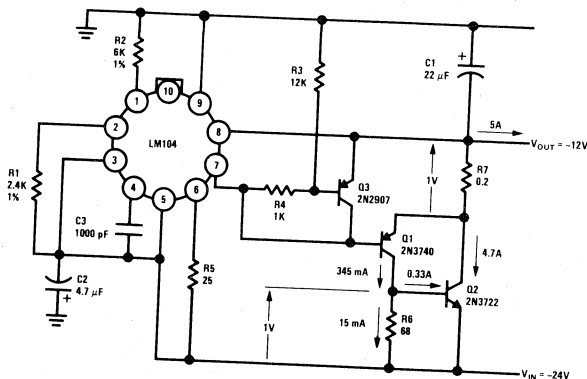


FIGURE 3. Circuit Used in the Solution of Questions 4 and 5.

# Fast Compensation Extends Power Bandwidth

National Semiconductor  
Linear Brief 4  
Robert C. Dobkin  
April 1969



In all IC operational amplifiers the power bandwidth depends on the frequency compensation. Normally, compensation for unity gain operation is accompanied by the lowest power bandwidth. A technique is presented which extends the power bandwidth of the LM101A for non-inverting gains of unity to ten, and also reduces the gain error at moderate frequencies.

In order to achieve unconditional stability, an operational amplifier is rolled off at 6 dB per octave, with an accompanying 90 degrees of phase shift, until a gain of unity is reached. Unity gain in most monolithic operational amplifiers is limited to 1 MHz, because the lateral PNP's used for level shifting have poor frequency response and exhibit excess phase shift at frequencies above 1 MHz. Hence, for stable operation, the closed loop bandwidth must be less than 1 MHz where the phase shift remains below 180 degrees.

For high closed loop gains, less severe frequency compensation is necessary to roll the open loop gain off at 6 dB per octave until it crosses the closed loop gain. The frequency where it crosses must, as previously mentioned, be less than

1 MHz. For closed loop gains between 1 and 10, more frequency compensation must be used to insure that the open loop gain has been rolled off soon enough to cross the closed loop gain before 1 MHz is reached.

The power bandwidth of an operational amplifier depends on the current available to charge the frequency compensation capacitors. For unity gain operation, where the compensation capacitor is largest, the power bandwidth of the LM101A is 6 kHz. Figure 1 shows an LM101A with unity gain

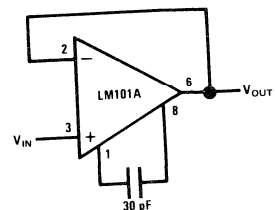


FIGURE 1. LM101A With Standard Frequency Compensation.

compensation and Figure 3 shows the open loop gain as a function of frequency.

A two-pole frequency compensation network, as shown in Figure 2, provides more than a factor of

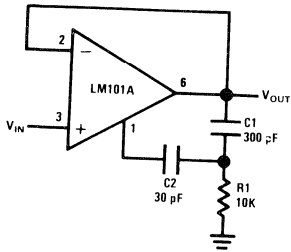


FIGURE 2. LM101A with Frequency Compensation to Extend Power Bandwidth.

two improvement in power bandwidth and reduced gain error at moderate frequencies. The network consists of a 30 pF capacitor, which sets the unity gain frequency at 1 MHz, along with a 300 pF capacitor and a 10k resistor. By dividing the ac output voltage with the 10k resistor and 300 pF capacitor, there is less ac voltage across the 30 pF capacitor and less current is needed for charging. Since the voltage division is frequency sensitive, the open loop gain rolls off at 12 dB per octave until a gain of 20 is reached at 50 kHz. From 50 kHz to 1 MHz the 10k resistor is larger

than the impedance of the 300 pF capacitor and the gain rolls off at 6 dB per octave. The open loop gain plot is shown in Figure 3. To insure sufficient drive to the 300 pF capacitor, it is connected to the output, Pin 6, rather than Pin 8. With this frequency compensation method, the power bandwidth is typically 15–20 kHz as a follower, or unity gain inverter.

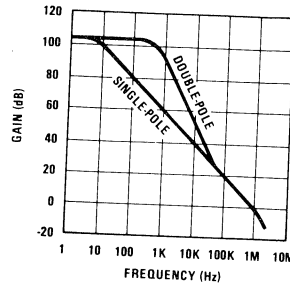


FIGURE 3. Open Loop Response for Both Frequency Compensation Networks.

This frequency compensation, in addition to extending the power bandwidth, provides an order of magnitude lower gain error at frequencies from DC to 5 kHz. Some applications where it would be helpful to use the compensation are: differential amplifiers, audio amplifiers, oscillators, and active filters.

# High Q Notch Filter

National Semiconductor  
 Linear Brief 5  
 Robert C. Dobkin  
 March 1969



The twin "T" network is one of the few RC filter networks capable of providing an infinitely deep notch. By combining the twin "T" with an LM102 voltage follower, the usual drawbacks of the network are overcome. The Q is raised from the usual 0.3 to something greater than 50. Further, the voltage follower acts as a buffer, providing a low output resistance; and the high input resistance of the LM102 makes it possible to use large resistance values in the "T" so that only small capacitors are required, even at low frequencies. The fast response of the follower allows the notch to be used at high frequencies. Neither the depth nor the frequency of the notch are changed when the follower is added.

Figure 1 shows a twin "T" network connected to an LM102 to form a high Q, 60 Hz notch filter.

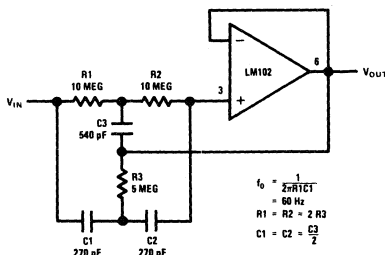


FIGURE 1. High Q Notch Filter

The junction of  $R_3$  and  $C_3$ , which is normally connected to ground, is bootstrapped to the output of the follower. Because the output of the follower is a very low impedance, neither the depth nor the frequency of the notch change; however, the Q is raised in proportion to the amount of signal fed back to  $R_3$  and  $C_3$ . Figure 2 shows the response of a normal twin "T" and the response with the follower added.

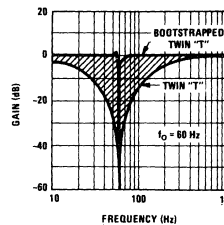


FIGURE 2. Response of High and Low Q Notch Filter

In applications where the rejected signal might deviate slightly from the null of the notch network, it is advantageous to lower the Q of the network. This insures some rejection over a wider range of input frequencies. Figure 3 shows a circuit where the Q may be varied from 0.3 to 50. A fraction of the output is fed back to  $R_3$  and  $C_3$  by a second voltage follower, and the notch Q is dependent on the amount of signal fed back. A second follower is necessary to drive the twin "T"

from a low-resistance source so that the notch frequency and depth will not change with the poten-

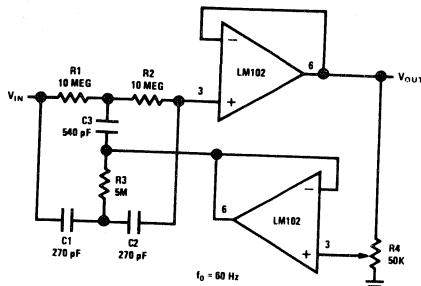


FIGURE 3. Adjustable Q Notch Filter

tiometer setting. Depending on the potentiometer setting, the circuit in Figure 3 will have a response that falls in the shaded area of Figure 2.

An interesting change in the high Q twin "T" occurs when components are not exactly matched in ratio. For example, an increase of 1 to 10 percent in the value of  $C_3$  will raise the Q, while degrading the depth of the notch. If the value of  $C_3$  is raised by 10 to 20 percent, the network provides voltage gain and acts as a tuned amplifier. A voltage gain of 400 was obtained during testing. Further increases in  $C_3$  cause the circuit to oscillate, giving a clipped sine wave output.

The circuit is easy to use and only a few items need be considered for proper operation. To minimize notch frequency shift with temperature, silver mica, or polycarbonate, capacitors should be used with precision resistors. Notch depth depends on component match, therefore, 0.1 percent resistors and 1 percent capacitors are suggested to minimize the trimming needed for a 60 dB notch. To insure stability of the LM102, the power supplies should be bypassed near the integrated circuit package with .01  $\mu\text{F}$  disc capacitors.



# Fast Voltage Comparators with Low Input Current

National Semiconductor  
Linear Brief 6  
May 1969




Monolithic voltage comparators are available today which are both fast and accurate. They can detect the height of a pulse with a 5 mV accuracy within 40 ns. However, these devices have relatively high input currents and low input impedances, which reduces their accuracy and speed when operating from high source resistances. This is probably a basic limitation since the input transistors of the integrated circuit must be operated at a relatively high current to get fast operation. Further, the circuit must be gold doped to reduce storage time, and this limits the current gain that can be obtained in the transistors. High gain transistors operating at low collector currents are necessary to get good input characteristics.

One way of overcoming this difficulty is to buffer the input of the comparator. A voltage follower is available which is ideally suited for this job. This device, the LM102\*, is both fast and has a low input current. It can reduce the effective input current of the comparator by more than three orders of magnitude without greatly reducing speed.


A comparator circuit for an A/D converter which uses this technique is shown in Figure 1a. An LM102 voltage follower buffers the output of a ladder network and drives one input of the comparator. The analog signal is fed to the other input of the comparator. It should come from a low impedance source such as the output of a signal processing amplifier, or another LM102 buffer amplifier.

Clamp diodes,  $D_1$  and  $D_2$ , are included to make the circuit faster. These diodes clamp the output of the ladder so that it is never more than 0.7V different from the analog input. This reduces the voltage excursion that the buffer must handle on the most significant bit and keeps it from slewing. If fast, low-capacitance diodes are used, the signal to the comparator will stabilize approximately 200 ns after the most significant bit is switched in. This is about the same as the stabilization time of the ladder network alone, as its speed is limited by stray capacitances. The diodes also limit the voltage swing across the inputs of the comparator, increasing its operating speed and insuring that the device is not damaged by excessive differential input voltage.

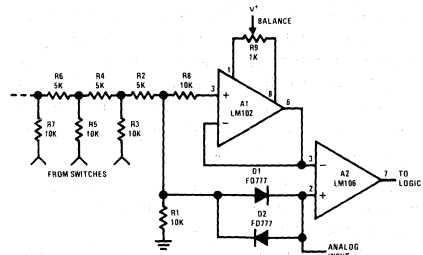The buffer reduces the loading on the ladder from 45  $\mu$ A to 20 nA, maximum, over a  $-55^\circ\text{C}$  to  $125^\circ\text{C}$  temperature range. Hence, in most applications the input current of the buffer is totally insignificant. This low current will often permit



a. Using a Ladder Network

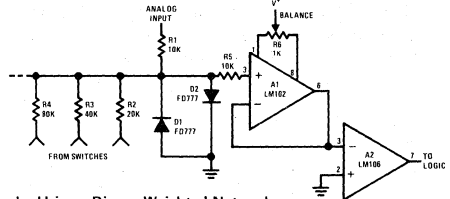

b. Using a Binary-Weighted Network

FIGURE 1. Comparator Circuits for Fast A/D Converters  
the use of larger resistances in the ladder which simplifies design of the switches driving it.

It is possible to balance out the offset of the LM102 with an external 1 k $\Omega$  potentiometer,  $R_9$ . The adjustment range of this balance control is large enough so that it can be used to null out the offset of both the buffer and the comparator. A 10 k $\Omega$  resistor should be installed in series with the input to the LM102, as shown. This is required to make the short circuit protection of the device effective and to insure that it will not oscillate. This resistor should be located close to the integrated circuit.

A similar technique can be used with A/D converters employing a binary-weighted resistor network. This is shown in Figure 1b. The analog input is fed into a scaling resistor,  $R_1$ . This resistor is selected so that the input voltage to the LM102 is zero when the output of the D/A network corresponds to the analog input voltage. Hence, if the D/A output is too low, the output of the LM106 will be a logical zero; and the output will change to a logical one as the D/A output exceeds the analog signal.

The analog signal must be obtained from a source impedance which is low by comparison to  $R_1$ . This can be either another LM102 buffer or the output of the signal-processing amplifier. Clamp diodes,  $D_1$  and  $D_2$ , restrict the signal swing and speed up the circuit. They also limit the input signal seen by the LM106 to protect it from over-


loads. Operating speed can be increased even further by using silicon backward diodes (a degenerate tunnel diode) in place of the diodes shown, as they will clamp the signal swing to about 50 mV. The offset voltage of both the LM102 and the LM106 can be balanced out, if necessary, with  $R_6$ .

The binary weighted network can be driven with single pole, single-throw switches. This will result in a change in the output resistance of the network when it switches, but circuit performance will not be affected because the input current of the LM102 is negligible. Hence, using the LM102 greatly simplifies switch design.


Although it is possible to use a 710 as the voltage comparator in these circuits, the LM106 offers several advantages. First, it can drive a fan out of 10 with standard, integrated DTL or TTL. It also has two strobe terminals available which disable the comparator and give a high output when either of the terminals is held at a logical zero. This adds logic capability to the comparator in that it makes it equivalent to a 710 and a two-input NAND gate. If not needed, the strobe pins can be left unconnected without affecting performance. The voltage gain of the LM106 is about 45,000, which is 30 times higher than that of the 710. The increased gain reduces the error band in making a comparison. The LM106 will also operate from the same supply voltage as the LM102, and other operational amplifiers, for  $\pm 12V$  supplies. However, it can also be operated from  $\pm 15V$  supplies if a 3V zener diode is connected in series with the positive supply lead.

It is necessary to observe a few precautions when working with fast circuits operating from relatively high impedances. A good ground is necessary, and a ground plane is advisable. All the individual points in the circuit which are to be grounded, including bypass capacitors, should be returned separately to the same point on the ground so that voltages will not be developed across common lead inductance. The power supply leads of the integrated circuits should also be bypassed with low inductance 0.01  $\mu F$  capacitors. These capacitors, preferably disc ceramic, should be installed with short leads and located close to the devices. Lastly, the output of the comparator should be shielded from the circuitry on the input of the buffer, as stray coupling can also cause oscillation.

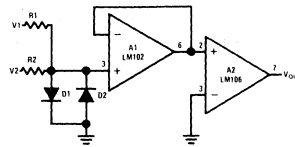
Although the circuits shown so far were designed for use in A/D converters, the same techniques apply to a number of other applications. Figure 2 gives examples of circuits which can put stringent input current requirements on the comparator. The first is a comparator for signals of opposite



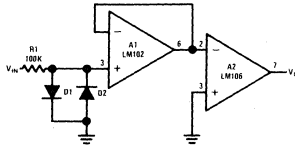a. Comparator for Signals of Opposite Polarity



b. Zero Crossing Detector

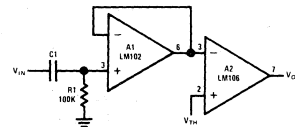

c. Comparator for AC Coupled Signals

FIGURE 2. Applications Requiring Low Input Current Comparators

polarity. Resistors ( $R_1$  and  $R_2$ ) are required to isolate the two signal sources. Frequently, these resistors must be relatively large so that the signal sources are not loaded. Hence, the input current of the comparator must be reduced to prevent inaccuracies. Another example is the zero-crossing detector in Figure 2b. When the input signal can exceed the common mode range of the comparator ( $\pm 5V$  for the LM106), clamp diodes must be used. It is then necessary to isolate the comparator from the input with a relatively large resistance to prevent loading. Again, bias currents should be reduced. A third example, in Figure 2c, is a comparator with an ac coupled input. An LM106 will draw an input current which is twice the specified bias current when the signal is above the comparison threshold. Yet, it draws no current when the signal is below the threshold. This asymmetrical current drain will charge any coupling capacitor on the input and produce an error. This problem can be eliminated by using a buffer, as the input current will be both low and constant.

The foregoing has shown how two integrated circuits can be combined to provide state-of-the-art performance in both speed and input current. Equivalent results will probably not be achievable in a single circuit for some time, as the technologies required are not particularly compatible. Further, considering the low cost of monolithic circuits, approaches like this are certainly economical.

## Tracking Voltage Regulators

National Semiconductor  
 Linear Brief 7  
 Robert C. Dobkin  
 August 1969



Integrated circuit voltage regulators are available today which are economical and offer a high degree of performance. There are both positive and negative regulators capable of achieving better than 0.1% regulation under normal fluctuations in input supply and load. Due to production variations, the internal reference voltage in these regulators may vary as much as 10% from unit to unit. Normally, this causes no problems as most power supply circuits have an adjustment potentiometer which is varied to obtain the correct output voltage. In systems with more than one regulated output voltage, it is sometimes desirable to adjust all supplies with a single potentiometer. This results in savings by eliminating one or more potentiometers as well as eliminating the need to adjust the supplies individually.

Figure 1 shows a 5V and a 15V regulator with both outputs adjusted with a single potentiometer. Although the technique is not exact, the error is typically under 2%. As shown in Figure 1, the internal reference voltages for the LM105\* regulators, available at pin 5, are tied together. This insures that both regulators operate with the same reference voltage. The lower resistors of the output divider,  $R_2$ , are connected through a common adjustment potentiometer to ground.  $R_5$  adjusts both regulators for variations in the 1.8V reference. Note that the wiper of  $R_5$  is connected to one side of the potentiometer. If a rheostat connection were used, the arm might open circuit during adjustment, causing large transients on the output.

The calculations of resistor values for the output divider resistors are made with the consideration that the adjustment is not exact and that two

regulators are adjusted. The bottom resistor of the divider,  $R_2$ , is fixed at 2K. The top of the divider,  $R_1$ , is then calculated for the output voltage using 1.6V as the reference voltage. To help compensate for the inaccuracies in the adjustment, output voltages are calculated slightly off from the desired values. For the 5 and 15V regulators,  $R_1$  is calculated to give a 2% low output voltage on the 5V regulator and a 2% high output voltage on the 15V regulator.

$$R_1 = \frac{(V_{OUT} - 1.6V) 2000\Omega}{1.6V}$$

$R_5$  will now adjust both regulators to within 2% of the desired output for reference variations from 1.6V to 2.0V. From the previous calculations, a 1.6V reference yields outputs of 4.9V and 15.3V. If the reference is 2.0V,  $R_5$  is adjusted to 324 ohms and the output voltages are 5.1V and 14.9V. If the reference is near the typical value of 1.8V, both outputs are within 1% of nominal.

These calculations do not account for resistor inaccuracies. If 1% resistors are used there is an additional worst case error of 2% for each regulator. Resistor errors are inherent in any type of tracking regulator system, even if the adjustment is theoretically exact.

Actually, any number of regulators may be connected to a single adjustment resistor. The adjustment accuracy of this technique depends on the output voltage differences among the regulators. The previous example was a severe difference, and had only 2% accuracy. With close output voltages, such as 12V and 15V, the error is much smaller. The 12V regulator is calculated to 1/2% low and 15V regulator 1/2% high with the 1.6V reference. Both regulators are then within 1/2% for reference variations of 1.6 to 2.0 volts. This adjustment method is, of course, exact if two regulators have the same output.

\*R. J. Widlar, "The LM105—An Improved Positive Regulator," National Semiconductor Corporation, AN 23, January, 1969.

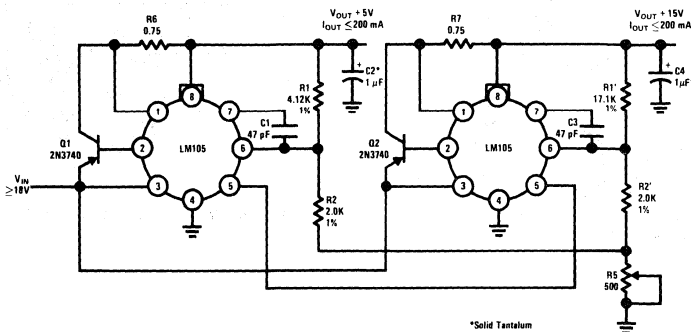


FIGURE 1. Tracking Positive Regulators

Using a negative regulator to track a positive regulator is a somewhat easier task. An inverting operational amplifier may be used to provide a negative output voltage while using a positive voltage as a reference. The LM104<sup>†</sup> negative regulator is easily adapted for use as an inverting amplifier and provides several advantages over conventional operational amplifiers. It is designed to drive boost transistors for higher output current as well as providing a convenient method of current limiting the output. Further, the frequency compensation used on the LM104 is optimized for transient response to line and load changes. Figure 2 shows tracking  $\pm 15V$  regulators.

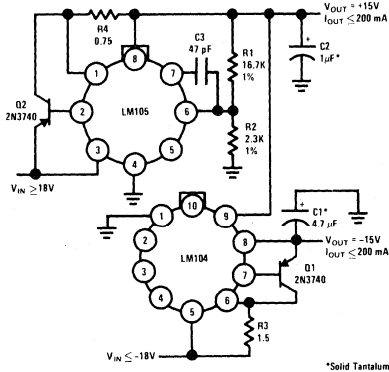


FIGURE 2. Tracking Positive and Negative Regulators

Operation is most easily understood by referring to the functional schematic of the LM104 in Figure 3. The non-inverting input of the internal amplifier, pin 1, is connected to ground. The positive 15V reference is connected through an internal 15K ohm input resistor,  $R_{16}$ , to the inverting input. Feedback resistor,  $R_{15}$ , is also 15K ohm. This forms a unity gain inverting amplifier with a negative output voltage equal to the positive input voltage. The 15K ohm resistors in the LM104 are

<sup>†</sup>R. J. Widlar, "Designs for Negative Regulators," National Semiconductor Corporation, AN-21, December, 1968.

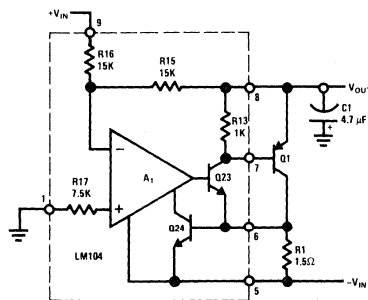


FIGURE 3. Functional Diagram of the LM104 Used as an Amplifier

typically matched to 1%. This means that the output of both regulators may be adjusted with 1% accuracy by changing  $R_1$  in Figure 2.

The LM104 may also be used with inverting gain for negative output voltages greater than the positive reference voltage. Figure 4 shows a circuit where the -15V supply tracks a +5V supply. In this configuration the non-inverting input is not grounded, but tied to divider,  $R_5$ ,  $R_6$ , between the negative output and ground. The output voltage equals

$$V_{OUT} = V^+ \left[ \frac{R_5 + R_6}{R_6 - R_5} \right]$$

where  $V^+$  is the positive reference.

The line regulation and temperature drift are determined primarily by the positive reference, with the negative output tracking. The reference must be a low impedance source, such as an LM105 regulator, to insure that current drawn by pin 9 of the LM104 does not affect the reference voltage. Since the LM104 is connected to a positive voltage instead of ground, it sees a total voltage equal to the sum of the unregulated negative input and the positive reference voltage. This reduces the maximum unregulated negative input voltage allowable, and should be considered during design. If the negative output voltage must be less than the positive reference or the decrease in maximum unregulated input voltage cannot be tolerated, an alternate method of constructing tracking regulators is given elsewhere<sup>†</sup>. Of course, many negative regulators may be slaved to a single positive regulator.

Using standard linear integrated circuits, multiple output positive and negative supplies may be adjusted to within 2% or less by a single resistor. Although the absolute output is not exact, the regulation accuracy is still within 0.1%. These techniques can result in savings by the elimination of both time and materials when used.

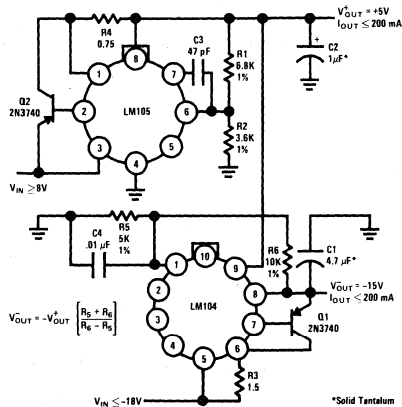


FIGURE 4. Tracking Regulators With Different Output Voltages

# Precision AC/DC Converters

National Semiconductor  
 Linear Brief 8  
 Robert C. Dobkin  
 August 1969



Although semiconductor diodes available today are close to "ideal" devices, they have severe limitations in low level applications. Silicon diodes have a 0.6V threshold which must be overcome before appreciable conduction occurs. By placing the diode in the feedback loop of an operational amplifier, the threshold voltage is divided by the open loop gain of the amplifier. With the threshold virtually eliminated, it is possible to rectify millivolt signals.

Figure 1 shows the simplest configuration for eliminating diode threshold potential. If the voltage at the non-inverting input of the amplifier is positive,

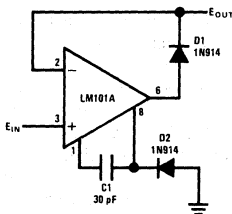


FIGURE 1. Precision Diode

the output of the LM101A swings positive. When the amplifier output swings 0.6V positive,  $D_1$  becomes forward biased; and negative feedback through  $D_1$  forces the inverting input to follow the non-inverting input. Therefore, the circuit acts as a voltage follower for positive signals. When the input swings negative, the output swings negative and  $D_1$  is cut off. With  $D_1$  cut off no current flows in the load except the 30 nA bias current of the LM101A. The conduction threshold is very small since less than 100  $\mu$ V change at the input will cause the output of the LM101A to swing from negative to positive.

A useful variation of this circuit is a precision clamp, as is shown in Figure 2. In this circuit the

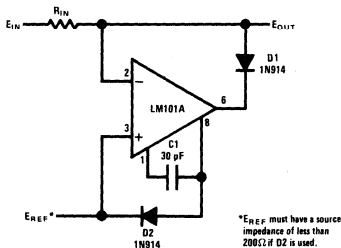


FIGURE 2. Precision Clamp

output is precisely clamped from going more positive than the reference voltage. When  $E_{IN}$  is more positive than  $E_{REF}$ , the LM101A functions as a summing amplifier with the feedback loop closed through  $D_1$ . Neglecting offsets, negative feedback keeps the summing node, and therefore the output, within 100  $\mu$ V of the voltage at the non-inverting input. When  $E_{IN}$  is about 100  $\mu$ V more negative than  $E_{REF}$ , the output swings positive, reverse biasing  $D_1$ . Since  $D_1$  now prevents negative feedback from controlling the voltage at the inverting input, no clamping action is obtained. On both of the circuits in Figures 1 and 2 an output clamp diode is added at pin 8 to help speed response. The clamp prevents the operational amplifier from saturating when  $D_1$  is reverse biased.

When  $D_1$  is reverse biased in either circuit, a large differential voltage may appear between the inputs of the LM101A. This is necessary for proper operation and does no damage since the LM101A is designed to withstand large input voltages. These circuits will not work with amplifiers protected with back to back diodes across the inputs. Diode protection conducts when the differential input voltage exceeds 0.6V and would connect the input and output together. Also, unprotected devices such as the LM709, are damaged by large differential input signals.

The circuits in Figures 1 and 2 are relatively slow. Since there is 100% feedback for positive input signals, it is necessary to use unity gain frequency compensation. Also, when  $D_1$  is reverse biased, the feedback loop around the amplifier is opened and the input stage saturates. Both of these conditions cause errors to appear when the input frequency exceeds 1.5 kHz. A higher performance precision half wave rectifier is shown in Figure 3. This circuit will provide rectification with 1% accuracy at frequencies from dc to 100 kHz. Further, it is easy to extend the operation to full wave rectification for precision ac/dc converters.

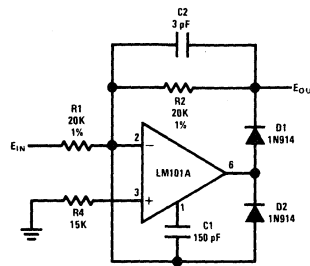


FIGURE 3. Fast Half Wave Rectifier

This precision rectifier functions somewhat differently from the circuit in Figure 1. The input signal is applied through  $R_1$  to the summing node of an inverting operational amplifier. When the signal is negative,  $D_1$  is forward biased and develops an output signal across  $R_2$ . As with any inverting amplifier, the gain is  $R_2/R_1$ . When the signal goes positive,  $D_1$  is non-conducting and there is no output. However, a negative feedback path is provided by  $D_2$ . The path through  $D_2$  reduces the negative output swing to  $-0.7V$ , and prevents the amplifier from saturating.

Since the LM101A is used as an inverting amplifier, feedforward\* compensation can be used. Feedforward compensation increases the slew rate to  $10V/\mu s$  and reduces the gain error at high frequencies. This compensation allows the half wave rectifier to operate at higher frequencies than the previous circuits with no loss in accuracy.

The addition of a second amplifier converts the half wave rectifier to a full wave rectifier. As is shown in Figure 4, the half wave rectifier is connected to inverting amplifier  $A_2$ .  $A_2$  sums the half wave rectified signal and the input signal to provide a full wave output. For negative input signals the output of  $A_1$  is zero and no current flows through  $R_3$ . Neglecting for the moment  $C_2$ ,

\*R. C. Dobkin, "Feedforward Compensation Speeds Op Amp," *National Semiconductor Corporation, LB-2*, March, 1969.

the output of  $A_2$  is  $-\frac{R_7}{R_6} E_{IN}$ . For positive input signals,  $A_2$  sums the currents through  $R_3$  and  $R_6$ ; and

$$E_{OUT} = R_7 \left[ \frac{E_{IN}}{R_3} - \frac{E_{IN}}{R_6} \right]$$

If  $R_3$  is  $1/2 R_6$ , the output is  $\frac{R_7}{R_6} E_{IN}$ . Hence, the output is always the absolute value of the input.

Filtering, or averaging, to obtain a pure dc output is very easy to do. A capacitor,  $C_2$ , placed across  $R_7$  rolls off the frequency response of  $A_2$  to give an output equal to the average value of the input. The filter time constant is  $R_7 C_2$ , and must be much greater than the maximum period of the input signal. For the values given in Figure 4, the time constant is about 2.0 seconds. This converter has better than 1% conversion accuracy to above 100 kHz and less than 1% ripple at 20 Hz. The output is calibrated to read the rms value of a sine wave input.

As with any high frequency circuit some care must be taken during construction. Leads should be kept short to avoid stray capacitance and power supplies bypassed with  $.01 \mu F$  disc ceramic capacitors. Capacitive loading of the fast rectifier circuits must be less than 100 pF or decoupling becomes necessary. The diodes should be reasonably fast and film type resistors used. Also, the amplifiers must have low bias currents.

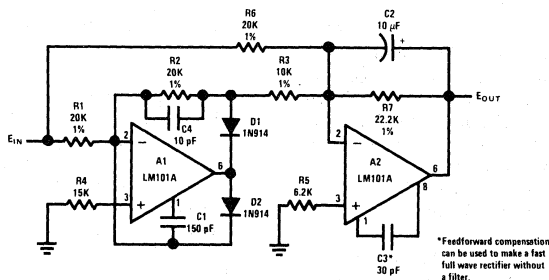



FIGURE 4. Precision AC to DC Converter

# Universal Balancing Techniques

National Semiconductor  
 Linear Brief 9  
 Robert C. Dobkin  
 August 1969



IC op amps are widely accepted as a universal analog component. Although the circuit designs may vary, most devices are functionally interchangeable. However, offset voltage balancing remains a personality trait of the particular amplifier design. The techniques shown here allow offset voltage balancing without regard to the internal circuitry of the amplifier.

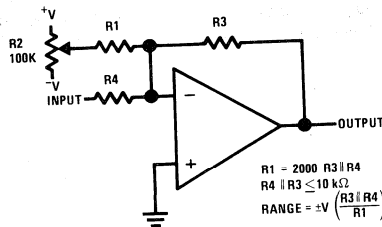


**FIGURE 1. Offset Voltage Adjustment for Inverting Amplifiers Using 10 kΩ Source Resistance or Less**

The circuit shown in Figure 1 is used to balance out the offset voltage of inverting amplifiers having a source resistance of 10 kΩ or less. A small current is injected into the summing node of the amplifier through R<sub>1</sub>. Since R<sub>1</sub> is 2000 times as large as the source resistance the voltage at the arm of the pot is attenuated by a factor of 2000 at the summing node. With the values given and ±15V supplies the output may be zeroed for offset voltages up to ±7.5 mV.


If the value of the source resistance is much larger than 10 kΩ, the resistance needed for R<sub>1</sub> becomes too large. In this case it is much easier to balance out the offset by supplying a small voltage at the non-inverting input of the amplifier. Figure 2 shows such a scheme. Resistors R<sub>1</sub> and R<sub>2</sub> divide the voltage at the arm of the pot to supply a ±7.5 mV adjustment range with ±15V supplies.

This adjustment method is also useful when the feedback element is a capacitor or non-linear device.

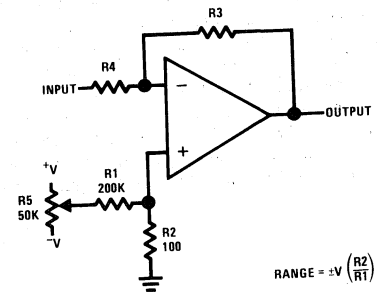

**FIGURE 2. Offset Voltage Adjustment for Inverting Amplifiers Using Any Type of Feedback Element**

This technique of supplying a small voltage effectively in series with the input is also used for adjusting non-inverting amplifiers. As is shown in Figure 3, divider R<sub>1</sub>, R<sub>2</sub> reduces the voltage at the arm of the pot to ±7.5 mV for offset adjustment. Since R<sub>2</sub> appears in series with R<sub>4</sub>, R<sub>2</sub> should be considered when calculating the gain. If R<sub>4</sub> is greater than 10 kΩ the error due to R<sub>2</sub> is less than 1%.

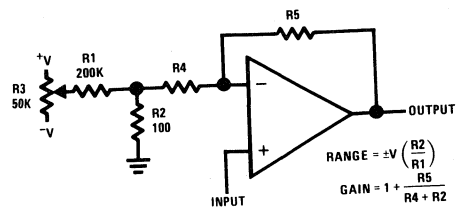

**FIGURE 3. Offset Voltage Adjustment for Non-Inverting Amplifiers**

A voltage follower may be balanced by the technique shown in Figure 4.  $R_1$  injects a current which produces a voltage drop across  $R_3$  to cancel the offset voltage. The addition of the adjustment resistors causes a gain error, increasing the gain by 0.05%. This small error usually causes no problem. The adjustment circuit essentially causes the offset voltage to appear at full output, rather than at low output levels, where it is a large percentage error.

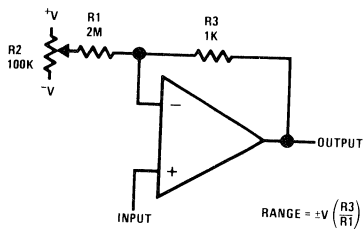


FIGURE 4. Offset Voltage Adjustment for Voltage Followers

Differential amplifiers are somewhat more difficult to balance. The offset adjustment used for a differential amplifier can degrade the common mode rejection ratio. Figure 5 shows an adjustment circuit which has minimal effect on the common mode rejection. The voltage at the arm of the pot is divided by  $R_4$  and  $R_5$  to supply an offset correction of  $\pm 7.5$  mV.  $R_4$  and  $R_5$  are chosen such that the common mode rejection ratio is limited by the amplifier for values of  $R_3$  greater than

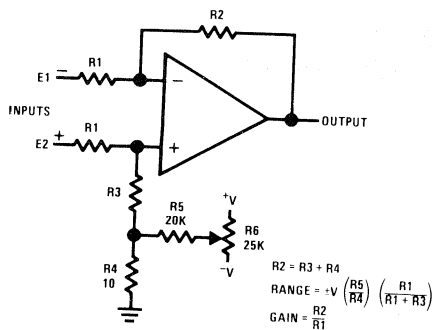


FIGURE 5. Offset Voltage Adjustment for Differential Amplifiers

1 k $\Omega$ . If  $R_3$  is less than 1K the shunting of  $R_4$  by  $R_5$  must be considered when choosing the value of  $R_3$ .

The techniques described for balancing offset voltage at the input of the amplifier offer two main advantages: First, they are universally applicable to all operational amplifiers and allow device interchangeability with no modifications to the balance circuitry. Second, they permit balancing without interfering with the internal circuitry of the amplifier. The electrical parameters of the amplifiers are tested and guaranteed without balancing. Although it doesn't usually happen, balancing could degrade performance.



# IC Regulators Simplify Power Supply Design

National Semiconductor  
Linear Brief 10  
Robert C. Dobkin  
January 1970



LB-10 IC Regulators Simplify Power Supply Design

Although power supply requirements vary, IC voltage regulators can fulfill the majority of needs. Power supplies designed with ICs can give predictable regulation better than 0.1% with a minimum of engineering effort. Output voltages between 0 and 40V at currents of 10A are easily achieved. Further, with a minimum of changes, a single regulator circuit can be used for a wide variety of output voltages and currents.

A basic 200 mA positive regulator circuit is shown in Figure 1. The LM105<sup>1</sup> contains the voltage reference and control circuitry while the external

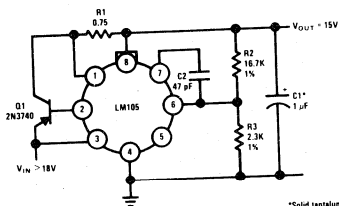


FIGURE 1. 200 mA Positive Regulator

components set the output voltage, current limit and increase power handling capacity of the IC. The output voltage is set by  $R_2$  and  $R_3$ . A fraction of the output voltage is compared by an error amplifier with an internal 1.8V reference. Any error is amplified and used to drive the 2N3740 power transistor. Since the open loop gain is large, there is little error and a high degree of regulation.

Current limiting is set by  $R_1$ . The voltage drop across  $R_1$  is applied to the emitter base junction of a transistor in the IC. When the transistor is turned on, it removes drive from the series pass transistor; and the regulator output exhibits a constant current characteristic. Since the turn on voltage of a transistor is temperature dependent, so is the current limit. The current limit sense voltage is about 0.4V at 25°C decreasing linearly to 0.3V at 125°C. Therefore, the current limit resistor must be chosen to provide adequate output current at the maximum operating temperature.

To regulate negative voltages, the circuit in Figure 2 is used. An LM104<sup>2</sup> contains the voltage reference and control circuitry while an external

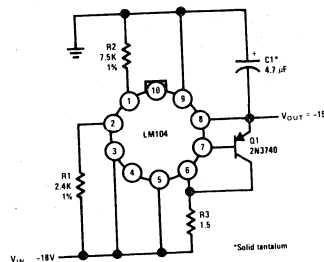


FIGURE 2. 200 mA Negative Regulator

transistor is used to increase the power handling capacity. A reference voltage is generated by driving a constant current, determined by  $R_1$ , through  $R_2$ . The voltage across this resistor is fed into an error amplifier. The error amplifier controls the output voltage at twice the voltage across  $R_2$ . The output voltage is resistor programmable with  $R_2$  and adjustable down to zero.

Current limit in the LM104 is similar to the LM105. Voltage across  $R_3$  turns on an internal transistor that decreases drive to the output transistors. This current limit sense voltage is also temperature dependent, decreasing from 0.65V at 25°C to 0.45V at 125°C.

Boosting the available output current from 200 mA is relatively simple. Figure 3 shows posi-

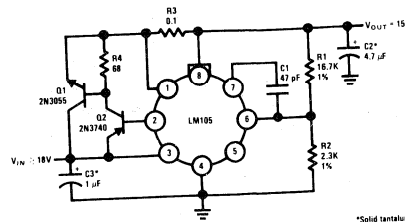


FIGURE 3a. 2A Positive Regulator

tive and negative 2A regulators. An additional power transistor increases the current handling capability of the regulator. Adding the boost tran-

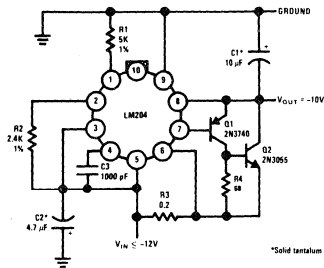


FIGURE 3b. 2A Negative Regulator

sistors increases the output current without increasing the minimum input-output voltage differential. The minimum differential will be 2 to 3V, depending on the drive current required from the integrated circuit and operating temperature. Low input-output voltage differential allows more efficient regulation.

Although the regulators are relatively simple, some precautions must be taken to eliminate possible problems. First, when the regulator is used with boost transistors, a solid tantalum output capacitor is needed. Unlike electrolytics, solid tantalum capacitors have low internal impedance at high frequencies. This suppresses possible high frequency minor loop oscillations as well as providing low output impedance at high frequency. Also, for the LM104, the output capacitor frequency compensates the regulator and must have good frequency characteristics.

The power transistors recommended are single-diffused, wide-base devices. These devices have fewer oscillation problems than double-diffused, planar transistors. Also, they seem less prone to failure under overload conditions. Of course, like the power transistors in any regulator, adequate heat sinking is necessary. The heat sink should keep the transistor junction temperature at an acceptable level for worst case conditions of maximum input voltage, maximum ambient temperature and shorted output. By far, the major cause of regulator failures is inadequate heat sinking.

Good construction techniques are also important for regulator performance. If proper care is not taken, ground loop errors and lead resistance drops can easily become greater than regulator errors. For example, 0.05" wide, 2 oz. printed circuit conductor has a resistance of about 0.007Ω per inch. For a 200 mA, 15V regulator, ten inches of conductor would decrease the regulation by a factor of 2.

Ground loops are worst yet, since voltage drops can be amplified and appear at the regulator's output. In Figure 3, voltage drops between Pin 4 of the LM105 and the bottom of R<sub>3</sub> are amplified by the ratio of R<sub>2</sub>/R<sub>3</sub> and appear at the output.

When the regulator is powered from ac that is rectified and filtered, current flowing in the filter can sometimes cause an unusual ground loop problem. For capacitor input filters, the peak charging current is many times the average load current. Even a few milliohms of resistance can cause appreciable voltage drop during the peak of the charging. When the charging current produces a voltage drop between R<sub>3</sub> and Pin 4 of the LM105, it appears as excessive ripple on the output of the regulator.

Of course, single point grounding eliminates these problems, but this is not always possible. Usually it is sufficient to insure that load current does not generate a voltage drop between the ground side of the voltage setting resistor and the ground of the IC.

In most cases, short circuit protection is the only fault protection needed. However, for some regulator circuits, such as positive and negative regulators used together, additional protection is necessary. If the positive and negative supplies are shorted together, it is possible to cause the output voltage of one of the supplies to reverse, blowing the IC. This is especially true if the current capabilities are different, such as a 200 mA negative supply and a 2A positive supply. A clamp diode between the output and ground of each supply will prevent such polarity reversals. Also, clamp diodes should be used to prevent input polarity reversal and input-output voltage differential reversal.

The use of ICs in regulator circuits can enhance power supply performance while minimizing cost and engineering time. Since only one IC is needed for a wide range of outputs, the part cost, board space and purchasing problems are less when compared to discrete designs. Also engineering time is saved since typical and worst case performance data, as well as application data, is available from the manufacturer before design is begun.

#### REFERENCES:

1. R.J. Widlar, "An Improved Positive Regulator," *National Semiconductor AN-23*, January, 1969.
2. R.J. Widlar, "Designs for Negative Regulators," *National Semiconductor AN-21*, October, 1968.

# The LM110 — An Improved IC Voltage Follower

National Semiconductor  
Linear Brief 11  
March 1970



There are quite a few applications where op amps are used as voltage followers. These include sample and hold circuits and active filters as well as general purpose buffers for transducers or other high-impedance signal sources. The general usefulness of such an amplifier is particularly enhanced if it is both fast and has a low input bias current. High speed permits including the buffer in the signal path or within a feedback loop without significantly affecting response or stability. Low input current prevents loading of high impedance sources, which is the reason for using a buffer in the first place.


The LM102, introduced in 1967, was designed specifically as a voltage follower. Therefore, it was possible to optimize performance so that it worked better than general purpose IC amplifiers in this application. This was particularly true with respect to obtaining low input currents along with high-speed operation.

One secret of the LM102's performance is that followers do not require level shifting. Hence, lateral PNP's can be eliminated from the gain path. This has been the most significant limitation on


the frequency response of general purpose amplifiers. Secondly, it was the first IC to use super-gain transistors. With these devices, high speed operation can be realized along with low input currents.

The LM110 is a voltage follower that has been designed to supersede the LM102. It is considerably more flexible in its application and offers substantially improved performance. In particular, the LM110 has lower offset-voltage drift, input current and noise. Further, it is faster, less prone to oscillations and operates over a wider range of supply voltages.

The advantages of the LM110 over the LM102 are described by the following curves. Improvements not included are increased output swing under load, larger small-signal bandwidth, and elimination of oscillations with low-impedance sources. The performance of these devices is also compared with general-purpose op amps in Tables I and II. The advantages of optimizing an IC for this particular slot are clearly demonstrated. Lastly, some typical applications for voltage followers with the performance capability of the LM110 are given.

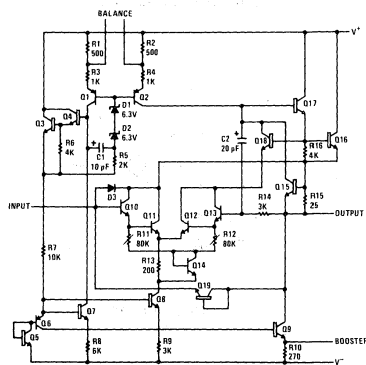


LM102

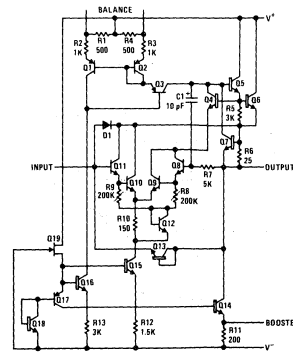


LM110

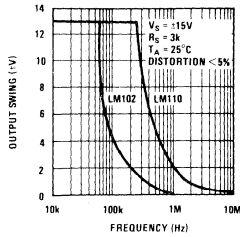
Biggest design difference between the LM102 and LM110 is the elimination of the zener diodes (D1 and D2) in the biasing circuit. This reduces noise and permits operation at low supply voltages.



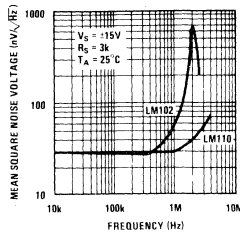Power bandwidth of the LM110 is five times larger than the LM102.



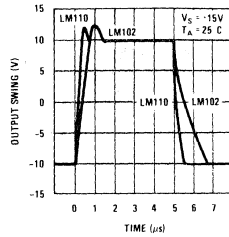Eliminating zeners reduces typical high frequency noise by nearly a factor of 10. Worst case noise is reduced even more. High frequency noise of LM102 has caused problems when it was included inside feedback loop with other IC op amps.



Large signal pulse response shows  $40V/\mu s$  slew for LM110 and  $10V/\mu s$  for LM102. Leading edge overshoot on LM110 is virtually eliminated, so external clamp diode frequently required on the LM102 is not needed.

DEVICE	OFFSET** VOLTAGE (mV)	BIAS** CURRENT (nA)	SLEW† RATE (V/μs)	BANDWIDTH† (MHz)	SUPPLY* CURRENT (mA)
LM110	6.0	10	40	20	5.5
LM102	7.5	100	10	10	5.5
MC1556	6.0	30	2.5	1	1.5
μA715	7.5	4000	20	10	7.0
LM108	3.0	3	0.3	1	0.6
LM108A	1.0	3	0.3	1	0.6
LM101A	3.0	100	0.6	1	3.0
μA741	6.0	1500	0.6	1	3.0

\*\*Maximum for  $-55^{\circ}C \leq T_A \leq 125^{\circ}C$

\*Maximum at  $25^{\circ}C$

†Typical at  $25^{\circ}C$


Table I. Comparing Performance of Military Grade IC Op Amps in the Voltage-Follower Connection.

DEVICE	OFFSET* VOLTAGE (mV)	BIAS* CURRENT (nA)	SLEW† RATE (V/μs)	BANDWIDTH† (MHz)	SUPPLY* CURRENT (mA)
LM310	7.5	7.0	40	20	5.5
LM302	15	30	20	10	5.5
MC1456	10	30	2.5	1	1.5
μA715C	7.5	1500	20	10	10
LM308	7.5	7.0	0.3	1	0.8
LM308A	0.5	7.0	0.3	1	0.8
LM301A	7.5	250	0.6	1	3.0
μA741C	6.0	500	0.6	1	3.0


\*Maximum at  $25^{\circ}C$

†Typical at  $25^{\circ}C$


Table II. Comparison of Commercial Grade Devices.

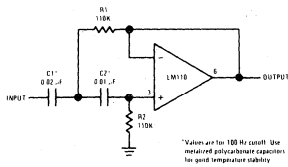


High Pass Active Filter

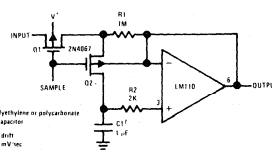

Low Drift Sample and Hold\*

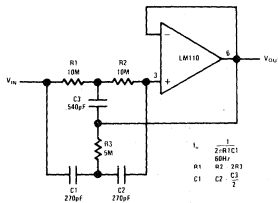

High Q Notch Filter

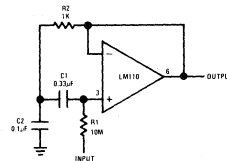

Bandpass Filter

# An IC Voltage Comparator for High Impedance Circuitry

National Semiconductor  
Linear Brief 12  
January 1970



The IC voltage comparators available in the past have been designed primarily for low voltage, high speed operation. As a result, these devices have high input error currents, which limit their usefulness in high impedance circuitry. An IC is described here that drastically reduces these error currents, with only a moderate decrease in speed.

This new comparator is considerably more flexible than the older devices. Not only will it drive RTL, DTL and TTL logic; but also it can interface with MOS logic and FET analog switches. It operates from standard  $\pm 15V$  op amp supplies and can switch 50V, 50 mA loads, making it useful as a driver for relays, lamps or light-emitting diodes. A unique output stage enables it to drive loads referred to either supply or ground and provide ground isolation between the comparator inputs and the load.

Another useful feature of the circuit is that it can be powered from a single 5V supply and drive DTL or TTL integrated circuits. This enables the designer to perform linear functions on a digital-circuit card without using extra supplies. It can, for example, be used as a low-level photodiode detector, a zero crossing detector for magnetic transducers, an interface for high-level logic or a precision multivibrator.

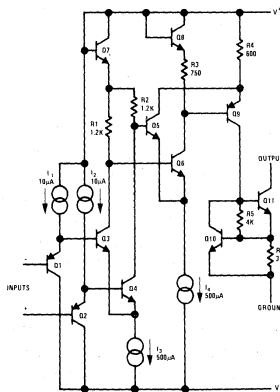


FIGURE 1. Simplified Schematic of the LM111

Figure 1 shows a simplified schematic of this versatile comparator. PNP transistors buffer the differential input stage to get low input currents without sacrificing speed. Because the emitter base breakdown voltage of these PNPs is typically 70V, they can also withstand a large differential input

voltage. The PNPs drive a standard differential stage. The output of this stage is further amplified by the  $Q_5$ - $Q_6$  pair. This feeds a lateral PNP,  $Q_9$ , that provides additional gain and drives the output stage.

The output transistor is  $Q_{11}$  which is driven by the level shifting PNP. Current limiting is provided by  $R_6$  and  $Q_{10}$  to protect the circuit from intermittent shorts. Both the output and the ground lead are isolated from other points within the circuit, so either can be used as the output. The  $V^-$  terminal can also be tied to ground to run the circuit from a single supply. The comparator will work in any configuration as long as the ground terminal is at a potential somewhere between the supply voltages. The output terminal, however, can go above the positive supply as long as the breakdown voltage of  $Q_{11}$  is not exceeded.

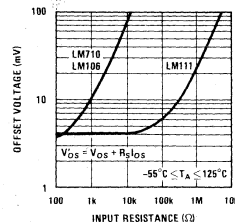


FIGURE 2. Illustrating the Influence of Source Resistance on Worst Case, Equivalent Input Offset Voltage.

Figure 2 shows how the reduced error currents of the LM111 improve circuit performance. With the LM710 or LM106, the offset voltage is degraded for source resistances above 200Ω. The LM111, however, works well with source resistances in excess of 30 kΩ. Figure 2 applies for equal source resistances on the two inputs. If they are unequal, the degradation will become pronounced at lower resistance levels.

Table 1 gives the important electrical characteristics of the LM111 and compares them with the specifications of older ICs.

A few, typical applications of the LM111 are illustrated in Figure 3. The first is a zero crossing detector driving a MOS analog switch. The ground terminal of the IC is connected to  $V^-$ ; hence, with  $\pm 15V$  supplies, the signal swing delivered to the gate of  $Q_1$  is also  $\pm 15V$ . This type of circuit is useful where the gain or feedback configuration of

**Table I. Comparing the LM111 with earlier IC comparators.** Values given are worst case over a  $-55^{\circ}\text{C}$  to  $125^{\circ}\text{C}$  temperature range, except as noted.

Parameter	LM111	LM106	LM710	Units
Input Offset Voltage	4	3	3	mV
Input Offset Current	0.02	7	7	$\mu\text{A}$
Input Bias Current	0.15	45	45	$\mu\text{A}$
Common Mode Range	$\pm 14$	$\pm 5$	$\pm 5$	V
Differential Input Voltage Range	$\pm 30$	$\pm 5$	$\pm 5$	V
Voltage Gain †	200	40	1.7	V/mV
Response Time †	200	40	40	ns
Output Drive Voltage	50	24	2.5	V
Output Drive Current	50	100	1.6	mA
Fan Out (DTL/TTL)	8	16	1	
Power Consumption	80	145	160	mW

†Typical at  $25^{\circ}\text{C}$ .


an op amp circuit must be changed at some precisely-determined signal level. Incidentally, it is a simple matter to modify the circuit to work with junction FETs.

The second circuit is a zero crossing detector for a magnetic pickup such as a magnetometer or shaft-position pickoff. It delivers the output signal directly to DTL or TTL logic circuits and operates from the 5V logic supply. The resistive divider,  $R_1$  and  $R_2$ , biases the inputs 0.5V above ground, within the common mode range of the device. An optional offset balancing circuit,  $R_3$  and  $R_4$ , is included.


The next circuit shows a comparator for a low-level photodiode operating with MOS logic. The output changes state when the diode current reaches  $1\ \mu\text{A}$ . At the switching point, the voltage across the photodiode is nearly zero, so its leakage current does not cause an error. The output switches between ground and  $-10\text{V}$ , driving the data inputs of MOS logic directly.

The last circuit shows how a ground-referred load is driven from the ground terminal of the LM111. The input polarity is reversed because the ground terminal is used as the output. An incandes-

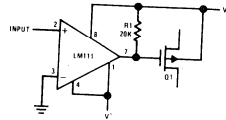
cent lamp, which is the load here, has a cold resistance eight times lower than it is during normal operation. This produces a large inrush current, when it is switched on, that can damage the switch. However, the current limiting of the LM111 holds this current to a safe value.



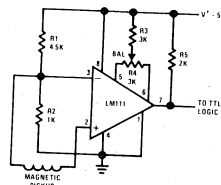
a. Zero Crossing Detector Driving Analog Switch



b. Detector for Magnetic Transducer

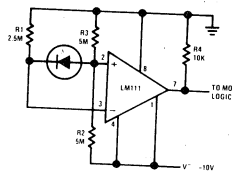

c. Comparator for Low Level Photodiode

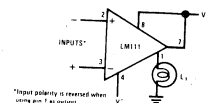

d. Driving Ground—Referred Load

**FIGURE 3. Typical Applications of the LM111.**

The applications described above show that the output-circuit flexibility and wide supply-voltage range of the LM111 opens up new fields for IC comparators. Further, its low error currents permit its use in circuits with impedance levels above  $1\ \text{k}\Omega$ . Although slower than older devices, it is more than an order of magnitude faster than op amps used as comparators.

The LM111 has the same pin configuration as the LM710 and LM106. It is interchangeable with these devices in applications where speed is not of prime concern.

# Speed Up the LM108 Feedforward Compensation

National Semiconductor  
Linear Brief 14  
Robert C. Dobkin  
November 1970



Feedforward frequency compensation of operational amplifiers can provide a significant increase in slew rate and bandwidth over standard lag compensation. When feedforward compensation is applied to the LM101A operational amplifier,<sup>1</sup> an order of magnitude increase in bandwidth results. A simple feedforward network has also been developed for use with the LM108 micropower amplifier to give a factor of five improvement in speed. It uses no active components and does not degrade the excellent dc characteristics of the LM108.

Figure 1 shows a schematic of an LM108 using the new compensation. The signal from the inverting input is fed forward around the input stage by a 500 pF capacitor,  $C_1$ . At high frequencies it provides a phase lead. With this lead, overall phase

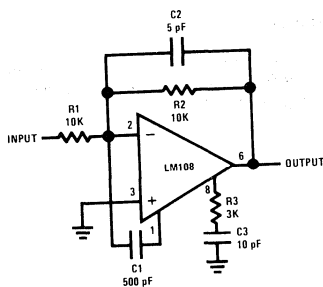


FIGURE 1. LM108 with Feedforward Compensation

shift is reduced and less compensation is needed to keep the amplifier stable. The  $C_2 - R_1$  network provides lag compensation, insuring that the open loop gain is below unity before 180° phase shift occurs. The open loop gain and phase as a function of frequency is compared with standard compensation in Figure 2.

The slew rate is increased from 0.3V/μs to about 1.3V/μs and the 1 kHz gain is increased from 500 to 10,000. Small signal bandwidth is extended to 3 MHz. The bandwidth must be limited to 3 MHz because the phase shift through the lateral PNP transistors used in the second stage becomes excessive at higher frequencies. With the LM101A, 10 MHz bandwidth was possible since the signal was bypassed around the low frequency lateral PNP's. Nonetheless, 3 MHz is very respectable for a micropower amplifier drawing only 300 μA quiescent current.

When the LM108 is used with feedforward compensation, it is less tolerant of capacitive loading and stray capacitance. Precautions must be taken

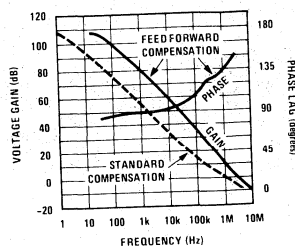


FIGURE 2. Open Loop Voltage Gain

to insure stability. If load capacitance is greater than about 75 to 100 pF, it must be isolated as shown in Figure 3. A small capacitor is always needed to provide a lead across the feedback resistor to compensate for strays at the input. About 3 to 5 pF is the minimum value capacitor. Care must be taken to minimize stray capacitance at Pins 1, 2 and 8 when feedforward compensation is used. Additionally, when the source resistance on the noninverting input is greater than 10k, it should be bypassed with a .01 μF capacitor.

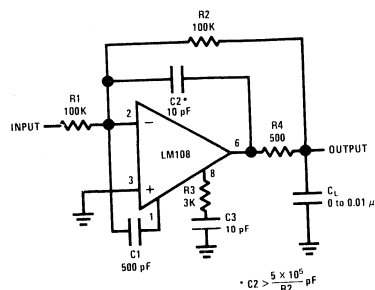


FIGURE 3. Decoupling Load Capacitance

As with any externally compensated amplifier, increasing the compensation of the LM108 increases the stability at the expense of slew and bandwidth. The circuit shown is for the fastest response. Increasing the size of  $C_2$  to 20 or 30 pF

will provide 2 or 3 times greater stability and capacitive load tolerance. Therefore, the size of the compensation capacitor should be optimized for the bandwidth of the particular application.

The stability of the LM108 with feedforward compensation is indicated by the small signal transient responses shown in Figure 4. It is quite stable since there is little overshoot and ringing even though the amplifier is loaded with a 50 pF capacitor. Large signal transient response for a 20V square wave is shown in Figure 5. The small positive overshoot is not severe and usually causes no problems.

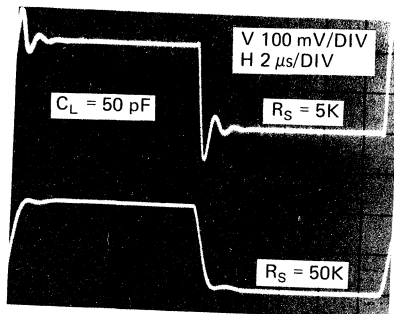


FIGURE 4. Small Signal Transient Response of LM108 with Feedforward Compensation

The LM108 is unusually insensitive to power supply bypassing with the new compensation. Even with several feet of wire between the device and power supply, it does not become unstable. How-

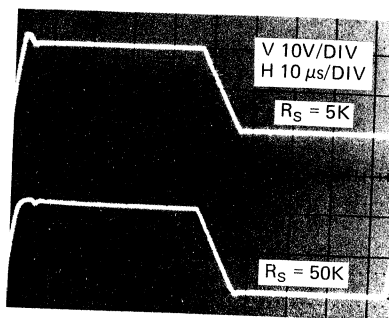


FIGURE 5. Large Signal Transient Response of LM108 with Feedforward Compensation

ever, it is still wise to bypass the supplies for drill since noise on the  $V^+$  line can be injected to the summing junction by the 500 pF feedforward capacitor.

The new feedforward compensation is easy to use and offers a factor of five improvement over standard compensation. Slew rate is increased to  $1.3V/\mu s$  and power bandwidth extended to 20 kHz. Also, gain error at high frequencies is reduced. This makes the LM108 more useful in precision applications where low dc error as well as low ac error is desired.

#### REFERENCE:

1. Robert C. Dobkin, "Feedforward Compensation Speeds Op Amp," *National Semiconductor LB-2*, March, 1969.



## High Stability Regulators

National Semiconductor  
 Linear Brief 15  
 Robert C. Dobkin  
 January 1971



Monolithic IC's have greatly simplified the design of general purpose power supplies. With an IC regulator and a few external components 0.1% regulation with 1% stability can be obtained. However, if the application requires better performance, it is advisable to use some other design approach.

Precision regulators can be built using an IC op amp as the control amplifier and a discrete zener as a reference, where the performance is determined by the reference. Figures 1 and 2 show schematics of simple positive and negative regulators. They are capable of providing better than 0.01% regulation for worst case changes of line, load and temperature. Typically, the line rejection is 120 dB to 1 kHz; and the load regulation is better than 10  $\mu$ V for a 1A change. Temperature is the worst source of error; however, it is possible to achieve less than a 0.01% change in the output voltage over a  $-55^{\circ}\text{C}$  to  $+125^{\circ}\text{C}$  range.

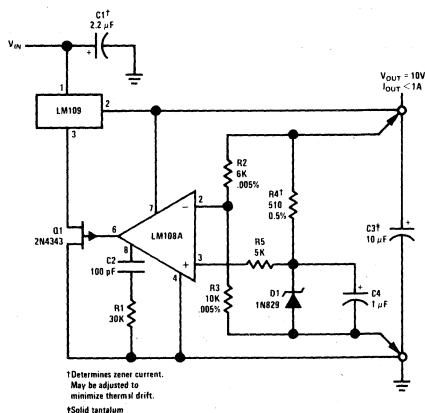


FIGURE 1. High Stability Positive Regulator

The operation of both regulators is straightforward. An internal voltage reference is provided by a high-stability zener diode. The LM108A<sup>1</sup> operational amplifier compares a fraction of the output voltage with reference. In the positive regulator, the output of the op amp controls the ground terminal of an LM109<sup>2</sup> regulator through source follower, Q<sub>1</sub>. Frequency compensation for the regulator is provided by both the R<sub>1</sub>C<sub>2</sub> combination and output capacitor, C<sub>3</sub>.

The negative regulator shown in Figure 2 operates similarly, except that discrete transistors are used for the pass element. A transistor, Q<sub>1</sub>, level shifts the output of the LM108 to drive output transistors, Q<sub>3</sub> and Q<sub>4</sub>. Current limiting is provided by Q<sub>2</sub>. Capacitors C<sub>3</sub> and C<sub>4</sub> frequency compensate the regulator.

In the positive regulator the use of an LM109 instead of discrete power transistors has several advantages. First, the LM109 contains all the biasing and current limit circuitry needed to supply a 1A load. This simplifies the regulator. Second, and probably most important, the LM109 has thermal overload protection, making the regulator virtually burn-out proof. If the power dissipation becomes excessive or if there is inadequate heat sinking, the LM109 will turn off when the chip temperature reaches 175°C, preventing the device from being destroyed. Since no such device is available for use in the negative regulator, the heat sink should be large enough to keep the junction temperature of the pass transistors at an acceptable level for worst case conditions of maximum ambient temperature, maximum input voltage and shorted output.

Although the regulators are relatively simple, some precautions must be taken to eliminate possible problems. A solid tantalum output capacitor must be used. Unlike electrolytics, solid tantalum capacitors have low internal impedance at high frequencies. Low impedance is needed both for frequency compensation and to eliminate possible minor loop oscillations. The power transistor recommended for the negative regulator is a single-diffused wide-base device. This transistor type has fewer oscillation problems than double diffused transistors. Also, it seems less prone to failure under overload conditions.

Some unusual problems are encountered in the construction of a high stability regulator. Component choice is most important since the resistors, amplifier and zener can contribute to temperature drift. Also, good circuit layout is needed to eliminate the effect of lead drops, pickup, and thermal gradients.

The resistors must be low-temperature-coefficient wirewound or precision metal film. Ordinary 1% carbon film, tin oxide or metal film units are not suitable since they may drift as much as 0.5% over temperature. The resistor accuracy need not be 0.005% as shown in the schematic; however, they should track better than 1 ppm/°C. Additionally, wirewound resistors usually have lower thermo-electric effects than film types. The resistor driving



# Easily Tuned Sine Wave Oscillators

National Semiconductor  
Linear Brief 16  
Robert C. Dobkin  
March 1971



One approach to generating sine waves is to filter a square wave. This leaves only the sine wave fundamental as the output. Since a square wave is easily amplitude stabilized by clipping, the sine wave output is also amplitude stabilized. A clipping oscillator eliminates the problems encountered with agc stabilized oscillators such as those using Wein bridges. Additionally, since there is no slow agc loop, the oscillator starts quickly and reaches final amplitude within a few cycles.

amplitude of the square wave fed back to the filter input. Starting is insured by  $R_6$  and  $C_5$  which provide dc negative feedback around the comparator. This keeps the comparator in the active region.

If a lower distortion oscillator is needed, the circuit in Figure 2 can be used. Instead of driving the tuned circuit with a square wave, a symmetrically clipped sine wave is used. The clipped sine wave, of course, has less distortion than a square wave and yields a low distortion output when filtered.

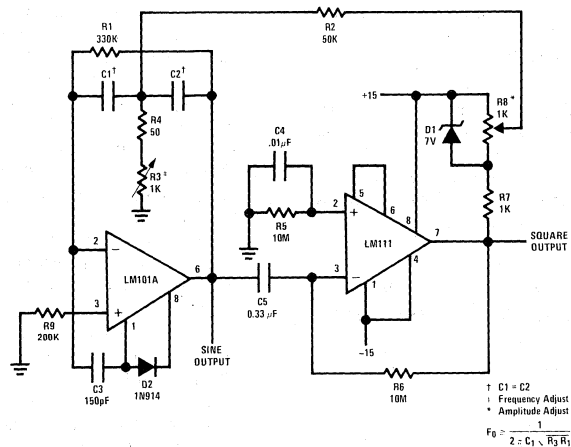


FIGURE 1. Easily Tuned Sine Wave Oscillator

The circuit in Figure 1 will provide both a sine and square wave output for frequencies from below 20 Hz to above 20 kHz. The frequency of oscillation is easily tuned by varying a single resistor. This is a considerable advantage over Wein bridge circuits where two elements must be tuned simultaneously to change frequency. Also, the output amplitude is relatively stable when the frequency is changed.

An operational amplifier is used as a tuned circuit, driven by square wave from a voltage comparator. Frequency is controlled by  $R_1$ ,  $R_2$ ,  $C_1$ ,  $C_2$ , and  $R_3$ , with  $R_3$  used for tuning. Tuning the filter does not affect its gain or bandwidth so the output amplitude does not change with frequency. A comparator is fed with the sine wave output to obtain a square wave. The square wave is then fed back to the input of the tuned circuit to cause oscillation. Zener diode,  $D_1$ , stabilizes the

This circuit is not as tolerant of component values as the one shown in Figure 1. To insure oscillation, it is necessary that sufficient signal is applied to the zeners for clipping to occur. Clipping about 20% of the sine wave is usually a good value. The level of clipping must be high enough to insure oscillation over the entire tuning range. If the clipping is too small, it is possible for the circuit to cease oscillation due to tuning, component aging, or temperature changes. Higher clipping levels increase distortion. As with the circuit in Figure 1, this circuit is self-starting.

Table 1 shows the component values for the various frequency ranges. Distortion from the circuit in Figure 1 ranges between 0.75% and 2% depending on the setting of  $R_3$ . Although greater tuning range can be accomplished by increasing the size of  $R_3$  beyond  $1k\Omega$ , distortion becomes

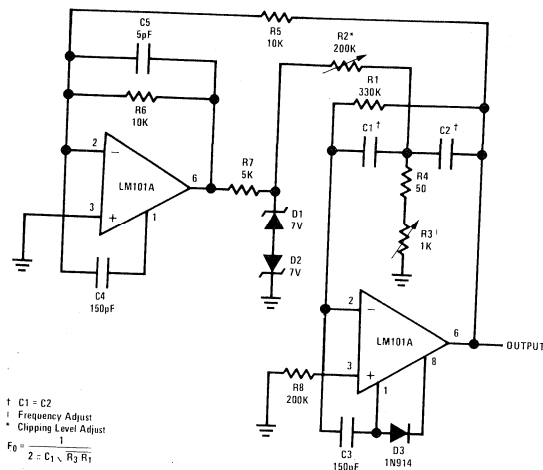


FIGURE 2. Low Distortion Sine Wave Oscillator

excessive. Decreasing  $R_3$  lower than  $50\Omega$  can make the filter oscillate by itself. The circuit in Figure 2 varies between 0.2% and 0.4% distortion for 20% clipping.

About 20 kHz is the highest usable frequency for these oscillators. At higher frequencies the tuned circuit is incapable of providing the high Q band-pass characteristic needed to filter the input into a clean sine wave. The low frequency end of oscillation is not limited except by capacitor size.

C <sub>1</sub> , C <sub>2</sub>	TABLE 1	
	MIN. FREQUENCY	MAX. FREQUENCY
0.47 $\mu$ F	18 Hz	80 Hz
0.1 $\mu$ F	80 Hz	380 Hz
.022 $\mu$ F	380 Hz	1.7 kHz
.0047 $\mu$ F	1.7 kHz	8 kHz
.002 $\mu$ F	4.4 kHz	20 kHz

In both oscillators, feedforward compensation<sup>3</sup> is used on the LM101A amplifiers to increase their bandwidth. Feedforward increases the bandwidth to over 10 MHz and the slew rate to better than 10V/ $\mu$ s. With standard compensation the maximum output frequency would be limited to about 6 kHz.

Although these oscillators are not particularly tricky, good construction techniques are important. Since the amplifiers and the comparators are both wide band devices, proper power supply

bypassing is in order. Both the positive and negative supplies should be bypassed with a 0.1 $\mu$ F disc ceramic capacitor. The fast transition at the output of the comparator can be coupled to the sine wave output by stray capacitance, causing spikes on the output. Therefore the output of the comparator with the associated circuitry should be shielded from the inputs of the op amp.

Component choice is also important. Good quality resistors and capacitors must be used to insure temperature stability. Capacitor should be mylar, polycarbonate, or polystyrene — electrolytics will not work. One percent resistors are usually adequate.

The circuits shown provide an easy method of generating a sine wave. The frequency of oscillation can be varied over greater than a 4 to 1 range by changing a single resistor. The ease of tuning as well as the elimination of critical a/c loops make these oscillators well suited for high volume production since no component selection is necessary.

#### References:

1. N.P. Doyle, "Swift, Sure Design of Active Bandpass Filters," *EDN*, Vol. 15, No. 2, January 15, 1970.
2. R.J. Widlar, "Precision IC Comparator Runs from 5V Logic Supply," *National Semiconductor AN-41*, October, 1970.
3. Robert C. Dobkin, "Feedforward Compensation Speeds Op Amp," *National Semiconductor LB-2*, March, 1969.

# LM118 Op Amp Slews 70V/ $\mu$ sec

National Semiconductor  
Linear Brief 17  
Robert C. Dobkin  
September 1971



One of the greatest limitations of today's monolithic op amps is speed. With unity gain frequency compensation, general purpose op amps have 1 MHz bandwidth and 0.3 V/ $\mu$ s slew rate. Optimized compensation as well as feedforward compensation can improve op amp speed for some applications. Specialized devices such as fast, unity-gain buffers are available which provide partial solutions. This paper will describe a new high speed monolithic amplifier that offers an order of magnitude increase in speed with no loss in flexibility over general purpose devices.

The LM118 is constructed by the standard six mask monolithic process and features 15 MHz bandwidth and 70 V/ $\mu$ s slew rate. It operates over a  $\pm 5$  to  $\pm 18$ V supply range with little change in speed. Additionally, the device has internal unity-gain frequency compensation and needs no external components for operation. However, unlike other internally compensated amplifiers, external feedforward compensation may be added to approximately double the bandwidth and slew rate.

### DESIGN CONCEPTS

In general purpose amplifiers the unity-gain bandwidth is limited by the lateral PNP transistors used for level shifting. The response above 2 MHz is so poor that they cannot be used in a feedback amplifier. If the PNP transistors are used for level shifting only at DC or low frequencies and the signal is fed forward around the PNP transistors at high frequencies, wide bandwidth can be obtained without the excessive phase shift of the PNP transistors.

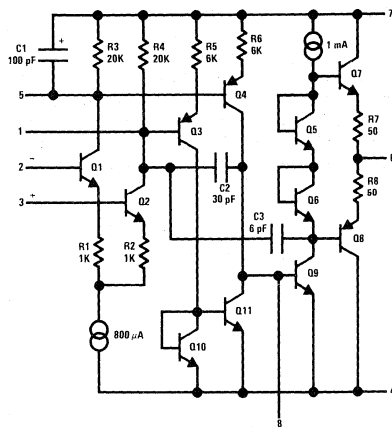


FIGURE 1. Simplified Circuit of the LM118

Figure 1 shows a simplified schematic of the LM118. Transistors  $Q_1$  and  $Q_2$  are a conventional differential input stage with emitter degeneration and resistive collector loads.  $Q_3$  and  $Q_4$  form the second stage which further amplify the signal and level shift the signal towards  $V^-$ . The collectors of  $Q_3$  and  $Q_4$  drive a current inverter,  $Q_{10}$  and  $Q_{11}$  to convert from differential to single ended.  $Q_9$ , which has a current source load for high gain, drives a class B output. The collectors of the input stage and the base of  $Q_9$  are available for offset balancing and external compensation.

Frequency compensation is accomplished with three internal capacitors.  $C_1$  rolls off on half the differential input stage so that the high frequency signal path is single-ended. Also, at high frequencies, the signal is fed forward around the lateral PNP transistors by a 30 pF capacitor,  $C_2$ . This eliminates the excessive phase shift. Overall frequency response is then set by capacitor,  $C_3$ , which rolls off the amplifier at 6 dB/octive. As previously mentioned feedforward compensation for inverting applications can be applied to the base of  $Q_9$ . Figure 2 shows the open loop frequency response of an LM118. Table 1 gives typical specifications for the new amplifier.

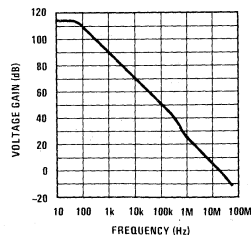


FIGURE 2. Open Loop Voltage Gain as a Function of Frequency for LM118.

TABLE 1. Typical Specifications for the LM118

Input Offset Voltage	2 mV
Input Bias Current	200 nA
Offset Current	20 nA
Voltage Gain	200K
Common Mode Range	$\pm 11.5$ V
Output Voltage Swing	$\pm 13$ V
Small Signal Bandwidth	15 MHz
Slew Rate	70 V/ $\mu$ s

## OPERATING CONFIGURATION

Although considerable effort was taken to make the LM118 trouble free, high frequency amplifiers are more prone to oscillations than low frequency devices such as the LM101A. Care must be taken to minimize the stray capacitance at the inverting input and at the output; however the LM118 will drive a 100 pF load. Good power supply bypassing is also in order—0.1  $\mu$ F disc ceramic capacitors should be used within a few inches of the amplifier. Additionally, a small capacitor is usually necessary across the feedback resistor to compensate for unavoidable stray capacitance.

Figure 3 shows feedforward compensation of the LM118 for fast inverting applications. The signal is fed from the summing junction to the output stage driver by  $C_1$  and  $R_4$ . Resistors  $R_5$ ,  $R_6$  and  $R_7$  have two purposes: they increase the internal operating current of the output stage to increase slew rate and they provide offset balancing. The current boost is necessary to drive internal stray capacitance at the higher slew rate. Mismatch of the external resistors can cause large voltage offsets so offset balancing is necessary. For supply voltages other than  $\pm 15$ V,  $R_5$  and  $R_6$  should be selected to draw about 500  $\mu$ A from Pins 1 and 5.

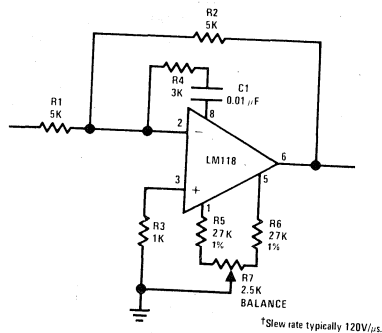


FIGURE 3. Feedforward Compensation for Greater Inverting Slew Rate†

When using feedforward, resistor  $R_4$  should be optimized for the application. It is necessary to have about 8 k $\Omega$  in the path from the output of the amplifier through the feedback resistor and through feedforward network to Pin 8 of the device. The series resistance is needed to limit the bandwidth and prevent minor loop oscillation.

At high gains, or with high value feedback resistors  $R_4$  can be quite low—but not less than 100 $\Omega$ . When the LM118 is used as a fast integrator, with a large feedback capacitor or with low values of feedback resistance,  $R_4$  must be increased to 8 k $\Omega$  to insure stability over a full  $-55^\circ\text{C}$  to  $125^\circ\text{C}$  temperature range.

One of the more important considerations for a high speed amplifier is settling time. Poor settling time can cancel the advantages of having high slew rate and bandwidth. For example—an amplifier can have severe ringing after a step input. A relatively long time is then needed before the output voltage can be read accurately. Settling time is the time necessary for the output to slew through a defined voltage change and settle to within a defined error of its final output voltage. Figure 4 shows optimized compensation for settling to

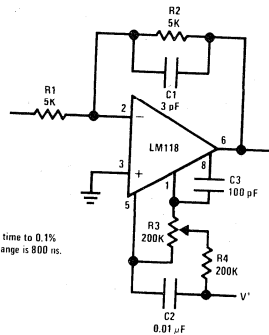


FIGURE 4. Compensation for Minimum Settling† Time

within 0.1% error. Typically the settling time is 800 ns for a simple inverter circuit as shown. Settling time is, of course, subject to operating conditions external to the IC such as closed loop gain, circuit layout, stray capacitance and source resistance. An optional offset balancing circuit,  $R_3$  and  $R_4$  is included.

The LM118 opens up new fields for IC operational amplifiers. It is more than an order of magnitude faster than general purpose amplifiers while retaining the ease of use features. It is ideally suited for analog to digital converters, active filters, sample and hold circuits and wide band amplification. Further, the LM118 has the same pin configuration as the LM101A or LM741 and is interchangeable with these devices when speed is of prime concern.

# +5 to -15 Volts DC Converter

National Semiconductor  
Linear Brief 18  
Helge H. Mortensen  
July 1972



## INTRODUCTION

It is frequently necessary to convert a DC voltage to another higher or lower DC-voltage while maximizing efficiency. Conventional switching regulators are capable of converting from a high input DC voltage to a lower output voltage and satisfying the efficiency criteria. The problem is a little more troublesome if a higher output voltage than the input voltage is desired. Particularly, generating DC voltage with opposite polarity to the input voltage usually involves a complicated design.

This brief demonstrates the use of the switching regulator idea for a +5 volts to -15 volts converter. The converter has an application as a power supply for MOS memories in a logic system where only +5 volts is available. However, the principle used can be applied for almost any input output combination.

## OPERATION

The method by which the regulator generates the opposite polarity is explained in Figure 1. The transistor Q is turned ON and OFF with a given duty cycle. If the base drive is sufficient the voltage across the inductor is equal to the supply

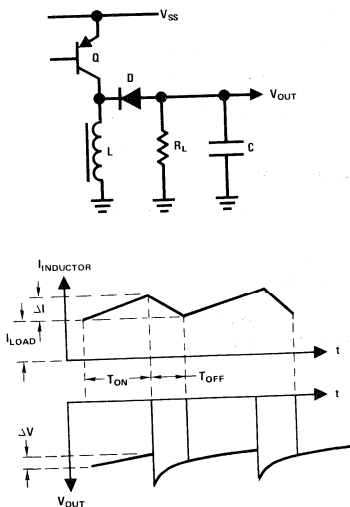


FIGURE 1. Switching Circuit for Voltage Conversion

voltage minus  $V_{SAT}$ . The current change in the inductor is given by:

$$\Delta I = \frac{V_{SS} - V_{SAT}}{L} \times T_{ON} \approx \frac{V_{SS}}{L} T_{ON} \quad (1)$$

Turning OFF the transistor the inductor current has a path through the catch diode and this in turn builds up a negative voltage across  $R_L$ .

The figure also shows the current and voltage levels versus time. A capacitor in parallel to the resistor will prevent the voltage from dropping to zero during the transistor ON time.

Assuming a large capacitor, we can also write the current change as:

$$\Delta I = \frac{V_{OUT} - V_D}{L} \times T_{OFF} \approx \frac{V_{OUT}}{L} \times T_{OFF} \quad (2)$$

In order to get a general idea of the operation for certain input output conditions, we will develop a set of equations.

During the transistor ON time, energy is loaded into the inductor. In the same time interval, the capacitor is drained due to the load resistor  $R_L$ .

Drop in capacitor voltage:

$$\Delta V = \frac{I_{LOAD} \times T_{ON}}{C} \quad (3)$$

During the  $T_{OFF}$  time the stored energy in the inductor is transferred to the load and capacitor. A rough estimate of  $T_{OFF}$  can be expressed as:

$$T_{OFF} = \frac{V_{SS}}{V_{OUT}} \times T_{ON} \quad (4)$$

The capacitor voltage will be restored with a average current given by:

$$I_C = \frac{\Delta V \times C}{T_{OFF}} = \frac{I_{LOAD} \times V_{OUT}}{V_{SS}} \quad (5)$$

The total inductor current during the OFF time can be written as:

$$I_{INDUCTOR} = I_{LOAD} + I_C \quad (6)$$

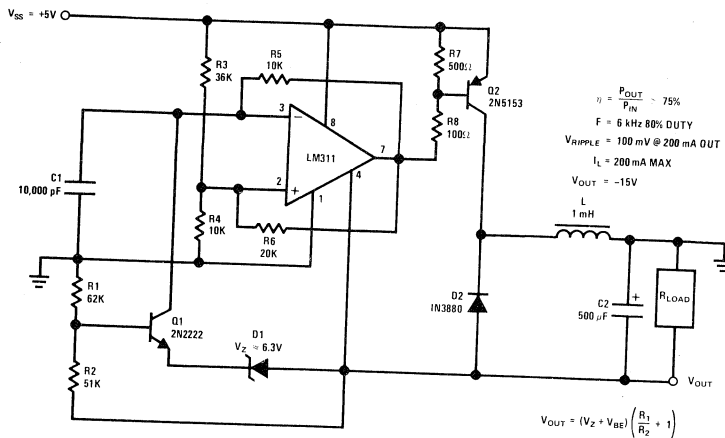


FIGURE 2. Switching Regulator for Voltage Conversion

Inspecting Figure 1. We find:

$$I_C = \frac{\Delta I}{2} = \frac{V_{SS} \times T_{ON}}{2 \times L} \quad (7)$$

which yields:

$$T_{ON} = \frac{2 \times L \times I_{LOAD} \times V_{OUT}}{V_{SS}^2} \quad (8)$$

Taking into account that the efficiency is in the order of 75% the final expression is:

$$T_{ON} = \frac{1.5 \times L \times I_{LOAD} \times V_{OUT}}{V_{SS}^2} \quad (9)$$

The above equations will be applied to the regulator shown at Figure 2. The regulator must deliver -15 volts at 200 mA from a +5 volt supply. Using a 1 mH inductor the  $T_{ON}$  time for  $Q_2$  is 0.18 ms from equation 9.  $T_{OFF}$  is 60  $\mu$ s from equation 4 and the oscillator frequency to:

$$F = \frac{1}{T_{ON} + T_{OFF}} \approx 4 \text{ kHz}$$

The LM311 performs a free running multivibrator with high duty cycle. The IC is designed to operate from a standard single 5 volt supply and has a high output current capability for driving the switching transistor  $Q_2$ . The duty cycle is given by the voltage divider  $R_3$  and  $R_4$  and the frequency of  $C_1$  in conjunction with  $R_5$ .

By setting the duty cycle higher than first calculated, the output voltage will tend to increase above the desired output voltage of 15 volts. However, an extra loop performed by  $Q_1$  and the zener diode in conjunction with the resistor network will modify the oscillator duty cycle until the desired output level is obtained.

The output voltage is given by:

$$V_{OUT} = (V_Z + V_{BE}) \left( \frac{R_1}{R_2} + 1 \right)$$

Data and results obtained with the design:

$$V_{IN} = 5 \text{ volts}$$

$$V_{OUT} = -15 \text{ volts}$$

$$I_{OUT} = \text{max } 200 \text{ mA}$$

$$\text{Efficiency} \approx 75\%$$

$$\text{Frequency} \approx 6 \text{ kHz } 80\% \text{ duty cycle}$$

$$V_{RIPPLE} \approx 100 \text{ mV @ } 200 \text{ mA load}$$

$$\text{Line regulation: } V_{IN} = 5\text{V to } 10\text{V} < 3\% V_{OUT}$$

$$I_{LOAD} = 200 \text{ mA}$$

$$\text{Load regulation: } V_{IN} = 5\text{V} < 3\% V_{OUT}$$

$$I_{LOAD} = 0 - 100 \text{ mA}$$

## REFERENCE

Widlar, R. J., "Designing Switching Regulators", AN2, National Semiconductor Corp.



# Predicting Op Amp Slew Rate Limited Response

National Semiconductor  
Linear Brief 19  
Marvin Vander Kooi  
August 1972



The following analysis of sine and step voltage responses applies to all single dominant pole op amps such as the LM101A, LM107, LM108A, LM112, LM118 and the LM741. Each of these op amps has an open loop response curve with a shape similar to the one shown in Figure 1. The distinguishing feature of this curve is the single low frequency turnover from a flat response to a uniform -20 dB per decade of frequency (-6 dB/octave) drop in gain, at least until the curve passes through the 0 dB line. Closing the loop to 40 dB (X100) as shown with a dotted line on Figure 1 does not change the shape of the curve, but it does move the turnover to a higher frequency. These open loop and closed loop response curves determine the gain applied to small signal inputs. The logical question then arises as to when a signal can no longer be treated as a small signal and the amplifier response begins to deviate from this curve.

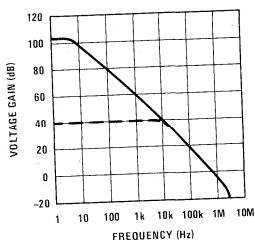


FIGURE 1. Open and Closed Loop Frequency Response

The answer lies in the slew rate limit of the op amp. The slew rate limit is the maximum rate of change of the amplifier's output voltage and is due to the fact that the compensation capacitor inside the amplifier only has finite currents<sup>1</sup> available for charging and discharging. A sinusoidal output signal will cease being small signal when its maximum rate of change equals the slew rate limit  $S_r$  of the amplifier. The maximum rate of change for a sine wave occurs at the zero crossing and may be derived as follows:

$$v_o = V_p \sin 2\pi ft \quad (1)$$

$$\frac{dv_o}{dt} = 2\pi f V_p \cos 2\pi ft \quad (2)$$

$$\left. \frac{dv_o}{dt} \right|_{t=0} = 2\pi f V_p \quad (3)$$

$$S_r = 2\pi f_{\max} V_p \quad (4)$$

where:  $v_o$  = output voltage  
 $V_p$  = peak output voltage

$$S_r = \text{maximum} \frac{dv_o}{dt}$$

The maximum sine wave frequency an amplifier with a given slew rate will sustain without causing the output to take on a triangular shape is therefore a function of the peak amplitude of the output and is expressed as:

$$f_{\max} = \frac{S_r}{2\pi V_p} \quad (5)$$

Equation 5 demonstrates that the borderline between small signal response and slew rate limited response is not just a function of the peak output signal but that by trading off either frequency or peak amplitude one can continue to have a distortion free output. Figure 2 shows a quick reference graphical presentation of equation 5 with the area above any  $V_{PEAK}$  line representing an undistorted small signal response and the area below a given  $V_{PEAK}$  line representing a distorted sine wave response due to slew rate limiting.

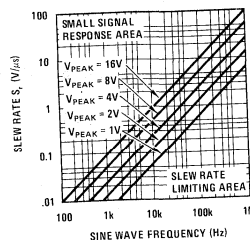


FIGURE 2. Sine Wave Response

As a matter of convenience, amplifier manufacturers often give a "full-power bandwidth" or "large signal response" on their specification sheets.

This frequency can be derived by inserting the amplifier slew rate and peak rated output voltage into equation 5. The bandwidth from DC to the resulting  $f_{max}$  is the full-power bandwidth or "large signal response" of the amplifier. For example the full-power bandwidth of the LM741 with a  $0.5V/\mu s$   $S_r$  is approximately 6 kHz while the full-power bandwidth of the LM118 with an  $S_r$  of  $70V/\mu s$  is approximately 900 kHz.

The step voltage response at the output of an op amp can also be divided into a small signal response and a slew rate limited response. The single turnover and uniform  $-20$  dB/decade slope shown in the small signal frequency response curve of Figure 1 are also characteristic of a low pass filter and one can in fact model an op amp as a low pass RC filter followed by a very wideband amplifier. Figure 3 shows a model of a X100 circuit with a 3 dB down rolloff frequency of 10 kHz.

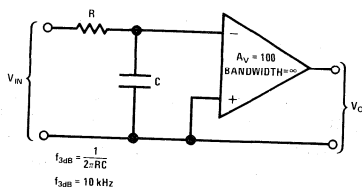


FIGURE 3. Small Signal Op Amp Model

theory<sup>2</sup> the 10% to 90% rise time of single pole low pass filter is:

$$t_r = \frac{0.35}{f_{3dB}} \quad (6)$$

which for this example would be  $35 \mu s$ . Again this small signal or low pass filter response ceases when the required rate of change of the output voltage exceeds the slew rate limit  $S_r$  of the amplifier. Mathematically stated:

$$\frac{V_{STEP}}{t_r} \geq S_r \quad (7)$$

This means that as soon as the amplitude of the output step voltage divided by the rise time of the circuit exceeds the  $S_r$  of the amplifier, the amplifier

will go into slew rate limiting. The output will then be a ramp function with a slope of  $S_r$  and a rise time equal to:

$$t'_r = \frac{V_{STEP}}{S_r} \quad (8)$$

Substituting equation 6 into equation 7 gives the critical value of  $V_{STEP}$  directly in terms of  $f_{3dB}$ :

$$\frac{V_{STEP} f_{3dB}}{0.35} \geq S_r \quad (9)$$

which can be graphed as shown in Figure 4. Any point in the area above a  $V_{STEP}$  line represents an undistorted low pass filter type response and any point in the area below a given  $V_{STEP}$  line represents a slew rate limited response.

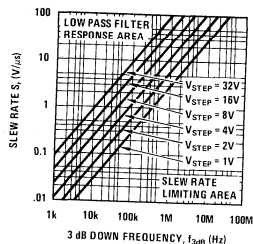


FIGURE 4. Step Voltage Response

The above equations and graphs should allow one to avoid the pitfalls of slew rate limiting and also provide a means of using engineering tradeoffs to extend the response of the single dominant pole type of amplifier.

## REFERENCES

1. Solomon, J.E.; Davis, W.R.; and Lee, P.L.: "A Self-Compensated Monolithic Operational Amplifier With Low Input Current and High Slew Rate", pp 14-15, ISSCC Digest Tech. Papers, February 1969.
2. Millman, J. and Hawkiass, C.C.: "Electronic Devices and Circuits", pp 465-466, McGraw-Hill Book Company, New York, 1967.

# A Fully Differential Input Voltage Amplifier

National Semiconductor  
Linear Brief 20  
Helge H. Mortensen  
December 1972



## INTRODUCTION

The instrumentation amplifier is useful for amplifying small differential signals which may be riding on high common mode voltage levels. These amplifiers are particularly useful in amplifying signals in the milli-volt range which are supplied from a high impedance source ( $>2k\Omega$ ).

This brief will demonstrate how a low cost, high performance instrumentation amplifier can be built using the newly introduced LM3900 quad amplifier. It is also indicated how a compact transducer bridge amplifier system can be developed to take advantage of the versatility of the LM3900.

## BASIC AMPLIFIER OPERATION

Figure 1 shows the basic operation of the amplifier. The bias of the LM3900 is set by the resistors  $R_2$  and  $R_3$  (neglecting for now, the transistors  $Q_1$  and  $Q_2$ ). Current which enters the non-inverting input of the LM3900 will be "mirrored" about  $V^-$  and then will be drawn into the inverting input terminal. This causes the current to flow through the feedback resistor,  $R_3$ , which establishes the output voltage level. If  $R_2 = R_3$  and further, if  $R_2$  is connected to ground (0V), then the output voltage biasing level will also be exactly zero volts. It should be noticed that an *OUTPUT OFFSET CONTROL* can be implemented by supplying a reference voltage,  $E_R$ , between  $R_2$  and ground.

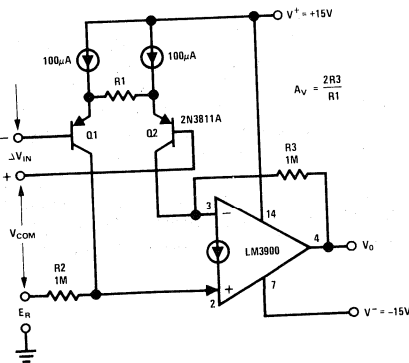


FIGURE 1. Basic Instrumentation Amplifier.

Adding transistors  $Q_1$  and  $Q_2$ , as shown in Figure 1 will not disturb this biasing if the two collector

currents of the transistors are well matched for a 0V differential input signal. The current sources which bias  $Q_1$  and  $Q_2$ , are chosen to be  $100\mu A$  each to guarantee high  $\beta$  and low offset voltage in  $Q_1$  and  $Q_2$ .

The gain of the amplifier is calculated as follows: Any differential input voltage,  $\Delta V_{IN}$ , appears across  $R_1$ , and produces a current change  $\Delta I$ , which is given by:

$$\Delta I = \frac{\Delta V_{IN}}{R_1} \quad (1)$$

This current change will show up in the collectors of  $Q_1$  and  $Q_2$  with opposite polarity. The input mirror of the LM3900 returns  $\Delta I_{Q1}$  to the inverting input terminal where it is added (with sign) to  $\Delta I_{Q2}$  yielding a total current change of  $2\Delta I$ . This current flows through the feedback resistor,  $R_3$ , which causes an output voltage change,  $\Delta V_o$ , which is given by:

$$\Delta V_o = 2\Delta I \times R_3 = 2 \times \frac{\Delta V_{IN}}{R_1} \times R_3 \quad (2)$$

to yield a gain,

$$A_V = 2 \frac{R_3}{R_1} \quad (3)$$

At this point it is convenient to evaluate the result obtained. The gain can be established by one resistor ( $R_1$ ) according to equation (3). Conventional instrumentation amplifiers usually have a gain given by:

$$A_V = 1 + \frac{\text{Constant}}{R} \quad (4)$$

This means that the minimum gain of unity is obtained if  $R$  is left out ( $R = \infty$ ). Note that this is different from the result indicated in equation (3) where unity gain is obtained for

$$R_1 = 2R_3 \quad (5)$$

and minimum gain (or maximum attenuation) is obtained if  $R_1$  is left out ( $R_1 = \infty$ ). This suggests that the amplifier can be turned OFF without disturbing the output voltage dc bias.

The two current sources for  $Q_1$  and  $Q_2$  are implemented with a dual transistor ( $Q_3$  and  $Q_4$ ) in conjunction with an additional amplifier of the LM3900 as shown in Figure 2. The operation can be easily understood if  $R_4$  and  $R_5$  are incorporated within the amplifier, which then takes the form of a conventional opamp closed loop regulator which maintains a reference voltage (the drop across  $R_6$ ) at the emitter of  $Q_4$ .

## PERFORMANCE

The performance of the complete instrumentation amplifier of Figure 2 is outlined below (Table 1 and Figure 3).

TABLE 1. Typical Performance Characteristics

<b>GAIN</b>	
Range of gain	-34 dB ( $R_1 = \infty$ ) to 72 dB ( $R_1 = 0$ )
Gain is set according to:	$A_v = \frac{2R_2}{R_1}$
<b>INPUT</b>	
Voltage offset referred to input is adjustable to zero.	
Common-mode and differential input voltage	Pos. supply less 2.4 V Neg. supply less 200 mV
Common-mode rejection ratio at 10 Hz	115 dB (gain of 1000)
Bias current (either input)	200 nA
<b>OUTPUT</b>	
Output offset is adjustable to zero.	
Output noise	12 mV <sub>rms</sub> (open loop) 3 mV <sub>rms</sub> ( $A_{CL} = 66$ dB)
<b>FREQUENCY RESPONSE</b>	
Small signal frequency response (-3 dB)	1 MHz (gain of 1000) 3 MHz (gain of 1)

Since quantitative discussion of the sources of offset voltage is beyond the scope of this brief,

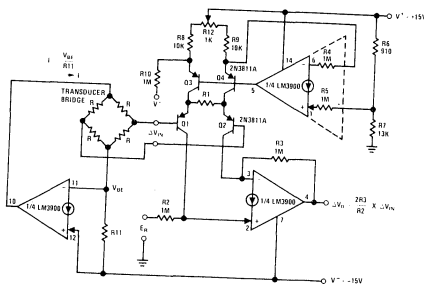


FIGURE 2. Bridge Amplifier

only the procedure for nulling the amplifier will be included.

Letting  $R_1$  go to zero causes the amplifier to operate in the open-loop mode. The main offset

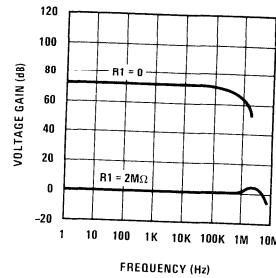


FIGURE 3. Frequency Response

voltage source is now the  $V_{BE}$  mismatch of  $Q_1$  and  $Q_2$ . The output can be nulled by the *OUTPUT OFFSET CONTROL* (the reference voltage for  $R_2$ ) or by adjusting the value of  $R_2$ . With  $R_1 = \infty$ , the main offset voltage source is the mismatch in the collector currents of  $Q_3$  and  $Q_4$ . This is easily adjusted via  $R_{12}$ . These first and second adjustments interact, however, after repeating the procedure a couple of times a good result is obtained.

## TRANSDUCER BIAS SOURCE

Having in mind that the LM3900 consists of four independent amplifiers makes it relatively easy to bias a transducer bridge with a constant current source using only one more of the amplifiers and one resistor. The technique is self-explanatory and is also shown in Figure 2.

## CONCLUSION

A brief review of a new concept for an instrumentation amplifier has been presented. Many applications can be derived from this basic connection which require amplifying the low level differential signals which are obtained from sensors such as strain gages, pressure transducers, and thermocouples. The performance of this instrumentation amplifier is adequate for many system applications. (See National Semiconductor Application Note 72, "The LM3900 - A New Current-Differencing Quad of  $\pm$  Input Amplifiers" for further information.)

# Instrumentational Amplifiers

National Semiconductor  
 Linear Brief 21  
 Robert C. Dobkin  
 June 1973



## INTRODUCTION

One of the most useful analog subsystems is the true instrumentation amplifier. It can faithfully amplify low level signals in the presence of high common mode noise. This aspect of its performance makes it especially useful as the input amplifier of a signal processing system. Other features of the instrumentation amplifier are high input impedance, low input current, and good linearity.

It has never been easy to design a high performance instrumentation amplifier; however, the availability of high performance IC's considerably simplify the problem. IC op amps are available today that can give very low drifts as well as low bias currents; however, most of the circuits have some drawback.

The most commonly used instrumentation amplifier designs utilize either 2 or 3 op amps and several precision resistors. These are capable of excellent performance; however, for high performance they require very precisely matched resistors. The common mode rejection of these designs depends on resistor matching and overall gain. Since op amps are now available with exceedingly high CMRR this is no longer a problem. The CMRR of the instrumentation amplifier is approximately equal to half resistor mismatch plus the gain. For a 1% resistor mismatch the CMRR is limited to 46 dB plus the gain—referred to the input.

Referred to the output, the common mode error is independent of gain and fixed by the resistor mismatch. For 1% match the error is 0.5%, and for 0.1% match the error is 0.05%. These errors are not trivial in high precision systems.

An instrumentation amplifier is shown here that compares favorably with multiple op amp designs, yet does not require precisely matched resistors. Further, the design allows a single resistor to adjust the gain. In comparing this instrumentation amp to multiple op amp types there are of course

some drawbacks. The gain linearity and accuracy are not as good as the multiple op amp circuits.

The errors appearing in multiple op amp circuits are independent of the output signal level. For example, a common mode error at the output of 0.5% of full scale is a 33% error if the desired output signal is only 1.5% of full scale. With the new circuit maximum errors at full scale output and the percentage of output error decreases at lower output levels.

Figure 1 shows a general purpose instrumentation amplifier optimized for wide bandwidth. It can provide gains from under 1 to over 1000 with a single resistor adjustment. Gain linearity is worst for unity-gain at 0.4%, and gain stability is better than 1.5% from  $-55^{\circ}\text{C}$  to  $+125^{\circ}\text{C}$ . Typically over a  $0^{\circ}\text{C}$  to  $+70^{\circ}\text{C}$  range gain stability is 0.2%. Common mode rejection ratio is about 100 dB— independent of gain.

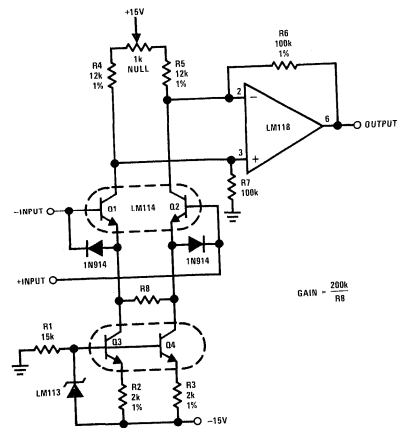


FIGURE 1. Instrumentation Amplifier

Transistor pair, Q1 and Q2, are operated open-loop as the input stage to give a floating, fully differential input. Current sources, Q3 and Q4, set the operating current of the input pair. To obtain good linearity the output current of Q3 and Q4 are set at about twice the current in R8 at full differential voltage. The temperature sensitivity of the transconductance of Q1 and Q2 is compensated by making their operating current directly proportional to absolute temperature. It has been shown that by biasing the base of transistor current sources at 1.22V, the output current varies as absolute temperature. The LM113 diode provide a constant 1.22V to the current sources. Both the compensated gm of Q1 and Q2 and the large degeneration from R8 give the amplifier stable gain over a wide temperature range.

In operation transistors Q1 and Q2 convert a differential input voltage to a differential output current at their collectors. This is fed into a standard differential amplifier to obtain a single ended output voltage. Since the diff amp does not see the common mode input voltage, 1% resistors are adequate. Gain is set by the ratio of R8 (plus the  $r_e$  of Q1 and Q2) to the sum of R6 and R7.

As mentioned previously this circuit is optimized for wide bandwidth: however, it is easily modified for other applications. If low bias current is needed all resistors can be increased by a factor of 100 and an LM108 substituted for the LM318. Other possible improvements are cascoded current sources and a modified Darlington input stage.

## Low Drift Amplifiers

National Semiconductor  
Linear Brief 22  
Robert C. Dobkin  
June 1973



### INTRODUCTION

Since the introduction of the monolithic IC amplifier, there has been a continued improvement in dc accuracy. Bias currents have been decreased by five orders of magnitude over the past five years. Low offset voltage drift is also necessary in high-accuracy circuits. This is evidenced by the popularity of low-drift amplifier types as well as requests for selected low-drift op amps. However, little has been written about the problems associated with handling microvolt signals with a minimum of errors.

A very low-drift amplifier poses some uncommon application and testing problems. Many sources of error can cause the apparent circuit drift to be much higher than would be predicted. In many cases, the low drift of the op amp is completely swamped by external effects while the amplifier is blamed for the high drift.

Thermocouple effects caused by temperature gradient across dissimilar metals are perhaps the worst offenders. Whenever dissimilar metals are joined, a thermocouple results. The voltage generated by the thermocouple is proportional to the temperature difference between the junction and the measurement end of the metal. This voltage can range between essentially zero and hundreds of microvolts per degree, depending on the metals used. In any system using integrated circuits, a minimum of three metals are found: copper, solder, and kovar (lead material of the IC).

Nominally, most parts of the circuit are at the same temperature. However, a small temperature gradient can exist across even a few inches—and this is a big problem with low level signals. Only a few degrees gradient can cause hundreds of microvolts of error. Two places where this shows up, generally, are the package-to-printed-circuit-board interface and temperature gradients across resistors. Keeping package leads short and the two input leads close together help greatly.

For example, a very low-drift amplifier was constructed and the output monitored over a 1-minute period. During the 1 minute it appeared to have input referred offset variations of  $\pm 5.0\mu\text{V}$ . Shielding the circuit from air currents reduced this to  $\pm 0.5\mu\text{V}$ . The  $10\mu\text{V}$  error was due to thermal gradients across the circuit from air currents.

Resistor choice as well as physical placement is important for minimizing thermocouple effects. Carbon, oxide film, and some metal-film resistors can cause large thermocouple errors. Wirewound resistors of evenohm or managanin are best since they only generate about  $2.0\mu\text{V}/^\circ\text{C}$  referenced to copper. Of course, keeping the resistor ends at the same temperature is important. Generally, shielding a low-drift stage electrically and thermally yields good results.

Resistors can cause other errors besides gradient generated voltages. If the gain setting resistors do not track with temperature, a gain error will result. For example, a gain-of-1000 amplifier with a constant 10 mV input will have a 10V output. If the resistors mistrack by 0.5% over the operating temperature range, the error at the output is 50 mV. Referred to input, this is a  $50\mu\text{V}$  error. Most precision resistors use different material for different ranges of resistor values. It is not unexpected that a resistor differing by a factor of 1000 does not track perfectly with temperature. For best results, ensure that the gain fixing resistors are of the same material or have tracking temperature coefficients.

It is appropriate to mention offset balancing as this can have a large effect on drift. Theoretically, the drift of a transistor differential amplifier depends on the offset voltage. For every millivolt of offset voltage the drift is  $3.6\mu\text{V}/^\circ\text{C}$ . Therefore, if the offset is nulled, the drift should be zero. When working with IC op amps, this is not the case. Other effects, such as second-stage drift and internal resistor TC, make the drift nontheoretical.

Certain types of amplifiers are optimized to have lower drift with offset balancing such as the LM121 and LM725. With this type of device offset, nulling improves the drift, and offset nulling should be used. Other types of devices, such as selected LM741's or LM308's, are selected for drift without offset nulling connected to the device. The addition of a balancing network changes the internal currents and thus changes the drift—probably for worse—so any offset balancing should be done at the input.

No matter which null network is applied highly stable resistors must be used. They should have low TC and track. Wirewound pots are usually a good choice. Finally, when the null network reduces a drift, the balancing of the amplifier as close to zero offset as possible minimizes the drift.

Testing low-drift amplifiers is also difficult. Standard drift testing techniques such as heating the

device in an oven and having the leads available through a connector, thermoprobe, or the soldering iron method do not work. Thermal gradients cause much greater errors than the amplifier drift. Coupling microvolt signal through connectors is especially bad since the temperature difference across the connector can be 50°C or more. The device under test along with the gain setting resistor should be isothermal. The circuit in Figure 1 will yield good results if well constructed.

### CONCLUSION

Low-drift amplifiers need extreme care to achieve reproducible low drift. Thermal and electrical shielding minimize thermocouple effects. Resistor choice is also important as they can introduce large errors. Careful attention to circuit layout offset balancing circuitry is also necessary.

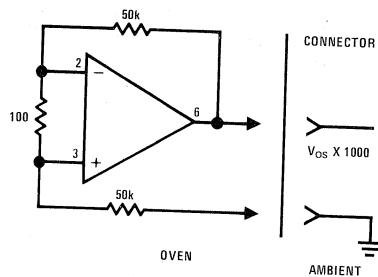


FIGURE 1. Drift Measurement Circuit



## Precise Tri-Wave Generation

National Semiconductor  
Linear Brief 23  
Robert C. Dobkin  
June 1973



### INTRODUCTION

The simple Tri-wave generator has become an often used analog circuit. Tri-wave oscillators are more easily designed, require less circuitry, and are more easily stabilized than sine wave oscillators. Further, the highly linear output of today's Tri-wave generators make them useful in many "sweep" circuits and test equipment.

This article describes a triangle wave generator with an easily controlled peak-to-peak amplitude. The positive and negative peak amplitude is controllable to an accuracy of about  $\pm 0.01V$  by a dc input. Also, the output frequency and symmetry are easily adjustable.

### CIRCUIT DESCRIPTION

The Tri-wave oscillator consists of an integrator and two comparators—one comparator sets the positive peak and the other the negative peak of the Tri-wave. To understand the operation, assume that the output of the comparator is low ( $-5V$ ). Then  $-5.0V$  is applied through R1 to the input of the integrator. The LM118 will integrate positive until its output is equal to the positive reference on pin 9 of the LM119. Since the comparator outputs are low, D1 is reverse biased and the full output of the integrator is applied to the non-inverting input of comparator A. As the integrator output crosses the positive reference, comparator A switches "plus" and latches "plus" from positive feedback through D1 and R4. Now the polarity of the current to the integrator has changed and the integrator starts ramping negative. When the output reaches the negative reference voltage, comparator B swings negative. This forces the output of comparator A negative, also, and stops the positive feedback through D1 from holding

the comparators' outputs positive. Once the positive feedback loop is broken, the outputs of the comparators stay low. With the comparators outputs low the integrator ramps positive again.

The frequency of operation is dependent upon R1, C1 and the reference voltages. Frequency is given by:

$$F = \frac{5.0V}{2R1 C1 (V_{REF}^+ - V_{REF}^-)}$$

The maximum frequency of operation is limited by circuit delay to about 200 kHz. Also, the maximum difference in reference voltages is 5.0V.

### APPLICATIONS

Regulator or op amp testing is made easier with precise triangle waves. For example, IC voltage regulators are usually specified to operate over a certain input voltage range such as 7.0V to 25V. The Tri-wave generator can be set to deliver a 0.7V to 2.5V output. This output is then amplified by a factor of 10 by an op amp and used to sweep the regulator input over its operating range. With op amps, the generator can be used to sweep common mode voltages, power supply voltages, or even to test output swing. The output of the device can be displayed on an oscilloscope and performance monitored over the entire operating range.

Another application is a voltage controlled oscillator. Since the frequency depends on the input reference voltage, varying the reference varies the frequency. The useful VCO range is about 2



# Versatile IC Preamplifier Makes Thermocouple Amplifier with Cold Junction Compensation

National Semiconductor  
 Linear Brief 24  
 Robert C. Dobkin  
 June 1973



## INTRODUCTION

Accurate electronic temperature measurements are not simple. There exists a large array of temperature sensors; each with its own peculiarities. The major sensors are thermistors, resistance sensors, and thermocouples. (Diodes and transistors have been used but they are not normally sold for this purpose.) Thermistors are highly non-linear, making wide range measurements difficult. Resistance sensors are large, require a bridge, and tend to be relatively costly. Thermocouples are small, relatively linear, inexpensive, but require reference junction temperature compensation.

Thermocouples are made when wires of different metals are joined. A voltage is produced proportional to the temperature *difference* between the junction and the output ends of the wire. This voltage is the Seebeck coefficient and is usually specified in volts (or microvolts) per degree. Depending on the material, it can range from nearly zero to volts—for some semiconductors. Commercially available thermocouples produce an output of between  $10\mu\text{V}/^\circ\text{C}$  and  $50\mu\text{V}/^\circ\text{C}$ .

Since the output voltage of thermocouples is proportional to temperature difference, the ambient temperature or measurement end of the thermocouple must be known. Alternatively, compensation can be applied for temperature changes. This is done either by terminating the thermocouple in a temperature controlled environment or with electrical compensation circuitry. The amplifier shown here provides a direct reading

output of  $10\text{ mV}/^\circ\text{C}$  and automatically compensates for reference junction temperature changes. Further, calibration is relatively simple.


## CIRCUIT DESCRIPTION

An LM321 preamp is used in conjunction with an LM308A op amp to form a precision, low-drift, operational amplifier. The LM321 is specifically designed for use with general purpose op amps to obtain drifts of  $1\mu\text{V}/^\circ\text{C}$ . When the offset voltage is nulled, the drift is also nulled. There is a theoretical relationship between the offset voltage and drift when the offset is not nulled to zero. The drift of the amplifier is then used to compensate the thermocouple for ambient temperature variations. Drift given by:

$$\frac{dV_{os}}{dT} = \frac{V_{os}}{T}$$

where T is in degrees Kelvin.

Resistors R1, R2, and R3 set the operating current of the preamp, and R3 is used to adjust the offset. The offset and drift are amplified by the ratio of the feedback resistors R4 and R5 and appears at the output. R6 and R7 attenuate the thermocouple's output to  $10\mu\text{V}/^\circ\text{C}$  to match the amplifier drift and set the scale factor at  $10\text{ mV}/^\circ\text{C}$ . The LM113 provides a temperature stable reference for offsetting the output to read directly in degrees centigrade.

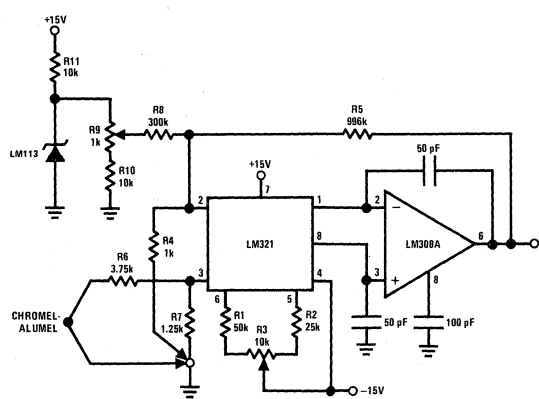

## CALIBRATION

Calibration is independent of thermocouple type; however, circuit values are for chromel alumel. R6 and R7 must be changed for different thermocouples. First, the thermocouple is replaced by a short of copper wire and the LM113 is shorted to ground. Then the offset is adjusted so the output reads the ambient temperature at  $10 \text{ mV}/^\circ\text{K}$ —for  $25^\circ\text{C}$  this is 2.98V. The short across the LM113 is removed and R9 is adjusted for the correct output in degrees centigrade. Connect the thermocouple, and it's ready to go.

## PERFORMANCE

It should be mentioned that for stable performance, good construction techniques are necessary. Resistor R4, R6, and R7 should be wirewound so they contribute a minimum of error due to thermocouple effects from temperature gradients across

the circuit. The entire circuit should be enclosed in a box with the end of the thermocouple terminated in the box near the LM321. This will minimize temperature gradients across the circuit and insure close thermal coupling between the LM321 and the reference end of the thermocouple.

Typically, the LM321 will track temperature changes with less than  $0.03^\circ\text{C}$  error per degree change. Self-heating of the LM321 will change its temperature by about  $2^\circ\text{C}$ ; this is calibrated out initially. Reference and resistor drift can be expected to contribute about  $0.02^\circ\text{C}/^\circ\text{C}$ . Of course, no compensation is made for nonlinearities of the thermocouple output voltage as a function of temperature. Over a wide measurement range with relatively stable ambient temperature, thermocouple error will be the major inaccuracy.

# True rms Detector

National Semiconductor  
Linear Brief 25  
Robert C. Dobkin  
June 1973



## INTRODUCTION


The op amp precision rectifier circuits have greatly eased the problems of ac to dc conversion. It is possible to measure millivolt ac signal with a dc meter with better than 1% accuracy. Inaccuracy due to diode turn-on and nonlinearity is eliminated, and precise rectification of low level signals is obtained.

Once the signal is rectified, it is normally filtered to obtain a smooth dc output. The output is proportional to the average value of the ac input signal, rather than the root mean square. With known input waveforms such as a sine, triangle, or square; this is adequate since there is a known proportionality between rms and average values. However, when the waveform is complex or unknown, a direct readout of the rms value is desirable.

The circuit shown will provide a dc output equal to the rms value of the input. Accuracy is typi-

cally 2% for a 20 V<sub>p-p</sub> input signal from 50 Hz to 100 kHz, although it's usable to about 500 kHz. The lower frequency is limited by the size of the filter capacitor. Further, since the input is dc coupled, it can provide the true rms equivalent of a dc and ac signal.

Basically, the circuit is a precision absolute value circuit connected to a one-quadrant multiplier/divider. Amplifier A1 is the absolute value amplifier and provides a positive input current to amplifiers A2 and A4 independent of signal polarity. If the input signal is positive, A1's output is clamped at -0.6V, D2 is reverse biased, and no signal flows through R5 and R6. Positive signal current flows through R1 and R2 into the summing junctions of A2 and A4. When the input is negative, an inverted signal appears at the output of A1 (output is taken from D2). This is summed through R5 and R6 with the input signal from R1 and R2. Twice the current flows through R5 and R6 and the net input to A2 and A4 is positive.

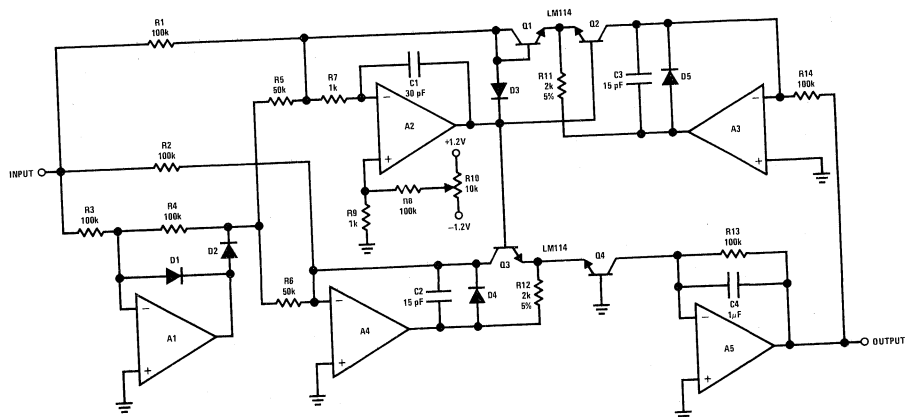

NOTE 1: ALL OPERATIONAL AMPLIFIERS ARE LM118.  
NOTE 2: ALL RESISTORS ARE 1% UNLESS OTHERWISE SPECIFIED.  
NOTE 3: ALL DIODES ARE 1N914.  
NOTE 4: SUPPLY VOLTAGE ±15V.

Amplifiers A2 through A5 with transistors Q1 through Q4 form a log multiplier/divider. Since the currents into the op amps are negligible, all the input currents flow through the logging transistors. Assuming the transistors to be matched, the  $V_{be}$  of Q4 is:

$$V_{be}(Q4) = V_{be}(Q1) + V_{be}(Q3) - V_{be}(Q2)$$

The  $V_{be}$ 's of these transistors are logarithmically proportional to their collector currents so

$$\log(I_{C4}) = \log(I_{C1}) + \log(I_{C3}) - \log(I_{C2})$$

$$\text{or } I_{C4} = \frac{I_{C1} I_{C3}}{I_{C2}}$$

where  $I_{C1}$ ,  $I_{C2}$ ,  $I_{C3}$ , and  $I_{C4}$  are the collector currents of transistors Q1 - Q4.

Since  $I_{C1}$  equals  $I_{C3}$  and is proportional to the input, the square of the input signal is generated. The square of the input appears as the collector

current of Q4. Averaging is done by C4, giving a mean square output. The filtered output of Q4 is fed back to Q2 to perform continuous division where the divisor is proportional to the output signal for a true root mean square output.

Due to mismatches in transistors, it is necessary to calibrate the circuit. This is accomplished by feeding a small offset into amplifier A2. A 10V dc input signal is applied, and R10 is adjusted for a 10V dc output. The adjustment of R10 changes the gain of the multiplier by adding or subtracting voltage from the log voltages generated by the transistors. Therefore, both the resistor inaccuracies and  $V_{be}$  mismatches are corrected.

For best results, transistors Q1 through Q4 should be matched, have high beta, and be at the same temperature. Since dual transistors are common, good results can be obtained if Q1, Q2 and Q3, Q4 are paired. They should be mounted in close proximity or on a common heat sink, if possible. As a final note, it is necessary to bypass all op amps with 0.1 $\mu$ F disc capacitors.

## Specifying Selected Op Amps and Comparators

National Semiconductor  
 Linear Brief 26  
 Robert C. Dobkin  
 October 1973



It is not infrequent that commercially available standard IC components do not fit a particular application as they are specified. Often, however, a standard device selected to tighter limits will work. Thereupon, the IC manufacturer may be requested to supply a specially tested device.

The usual chain of events for a selected part is as follows: A specification is sent to the manufacturer with a request for quote. It is evaluated at the manufacturer for feasibility, yield, and testing requirements. Then price and delivery are quoted to the customer. (Sometimes this route is shortened by calling the manufacturer—but this does not always work.)

Some insight into the IC design and IC testing can help both the manufacturer and IC user with special selection. Proper specification helps the manufacturer test as well as reduce IC costs. Ambiguous or impossible specs will usually result in the return of the specification to the customer for clarification and delay the delivery of the required parts.

The manufacturer is usually familiar with the product and production spread of devices. Further, test equipment is available for measuring parameters specified by the data sheet. In general, tightening selected data sheet parameters causes no problems. Further, no additional test equipment is needed for these tests—only the limits need be changed.

Perhaps one of the largest problems is over-specification. Each tightened specification reduces

the number of parts available to the specification. For example, tightening several specifications at once could result in a 1% or 0.1% yield; to supply 100 parts at this yield, between 10,000 and 100,000 parts might have to be tested, and that gets expensive.

Of course, spec limits cannot be tightened to any desired value. This is due to limitations on the IC design. For example, bias current, which depends on transistor  $H_{fe}$ , can not be tightened by a factor of 10. This would require beta's 10 times higher than normal. Also, some specifications are not independent; such as op amp bandwidth and slew-rate.

### OP AMP AND COMPARATORS

These are the two most popular linear IC components requiring selection. Since many of the same specifications apply to both types of devices, they will be covered together. Table I shows the most common parameters tested on these devices and the relative difficulty of testing on high speed equipment.

Selected offset voltage and drift are very commonly specified parameters. Offset voltage and drift depends on component matching. In general, drift is not usually tested on general purpose devices; although, it may be guaranteed. Offset voltage can be correlated to drift, and the offset limits are set to guarantee the standard drift specification. Of course, very low drift devices must be 100% tested for drift, making them relatively expensive. Drift testing requires measuring the offset voltage at three or more temperatures; then subtracting

TABLE I

PARAMETER	OP AMP	COMPARATOR	COST
Offset Voltage	Easy	Easy	Low
Offset Current	Easy	Easy	Low
Bias Current	Easy	Easy	Low
Supply Current	Easy	Easy	Low
Common Mode/Supply Rejection	Easy	Easy	Low
Gain	Moderate	Moderate	Low
Input Resistance	Guaranteed by Bias Current Measurement	Guaranteed by Bias Current Measurement	Not Tested
Slew Rate	Moderate	Moderate	Relatively Low
Band Width/Response Time	Difficult	Difficult	Moderate
Offset Voltage Drift	Very Difficult	Very Difficult	High
Offset Current Drift	Very Difficult	Very Difficult	High

and dividing by the temperature change to obtain the drift—a long and tedious measurement.

In some cases tightened offset voltage specifications over the operating temperature range offer the same performance as a drift tested device, but are less expensive. This is because offset voltage measurement can be a go/no-go measurement. For example,  $15\mu\text{V}/^\circ\text{C}$  can be guaranteed over a  $100^\circ\text{C}$  range by limiting the maximum offset voltage to  $\pm 0.75\text{ mV}$  or a  $1.5\text{ mV}$  band. If the application has an error budget of  $\pm "X"$  volts, it may be better to tighten the offset voltage rather than have the manufacturer to drift test. Drift testing a comparator is virtually impossible since they are not designed to operate closed loop.

Other parameters dependent upon matching are: offset current, common mode rejection, and supply rejections. These can be greatly tightened at the expense of yield.

Bias current, supply current, gain, slew rate, and response time are dependent upon both device design and processing. The limits for tighter parameters on these specifications are more restrictive. Table II gives reasonable special selection limits. This is only a guideline and, of course, depends on the device.

Noise testing is in a class by itself. Op amp noise will vary between manufacturers of the same device. Further, noise will vary between different types of devices from the same manufacturer.

Since noise on a particular device is mostly process dependent, it will be relatively consistent from a single IC producer.

Noise can be broken into two categories: white noise, and popcorn noise. Both of these noise sources can be either voltage or current noise. It is possible with advanced processing to make IC transistors as good as the best discrete low noise transistors. With good processing only a very small percentage of op amps will have any popcorn noise.

Noise measurements are time consuming and costly. Popcorn noise testing may take as much as 30 seconds per unit which limits production to about 100 devices per hour. This low production rate will increase costs. If not absolutely necessary—do not specify noise.

As a final note, some mention should be made of other special testing. Anything reasonable can be done; however, it should be kept in mind that accurate specification in terms of the IC parameters is necessary. It is unlikely a positive result will come from a specification showing a system schematic, system output, and stating "select devices to produce desired outputs." Although this is an exaggeration, it points out the type of specification to be avoided. Performance specification should apply to the IC not to a circuit using the IC. Many manufacturers have circuits available showing the various electrical tests and the way they are done.

TABLE II. Guideline to Tightened Specifications

PARAMETERS	LIMIT	COMMENTS
Offset Voltage	0.1 mV	Matching
Offset Current	-50% of Nominal	Matching
Bias Current	-50% of Nominal	Depends on $H_{fe}$
Supply Current	-25% of Nominal	Depends on Various Process Parameters
Gain	+100% of Nominal	Set by Design
Common Mode/Supply Rejection	+200% of Nominal	Matching
Slew Rate	+30% of Nominal	Set by Design
Bandwidth	+30% of Nominal	Set by Design
Response Time	-30% of Nominal	Set by Design and Processing
Offset Voltage Drift	$0.2\mu\text{V}/^\circ\text{C} - 5\mu\text{V}/^\circ\text{C}$	Lower Limit May Not Apply to Many Op Amps
Offset Current Drift	Guarantee by Offset Current Limit	



# Micropower Thermometer

National Semiconductor  
 Linear Brief 27  
 Robert C. Dobkin  
 January 1974



The introduction of a monolithic temperature transducer for the  $-55^{\circ}\text{C}$  to  $+125^{\circ}\text{C}$  temperature range can considerably simplify the problems encountered in temperature measurement. The three most common sensors—thermistors, resistance sensors, and thermocouples—require a reasonable amount of circuitry for use. Thermistors are highly nonlinear, resistance sensors and thermistors require a stable excitation voltage, and thermocouples have low output. Further, none of these sensors provide an output directly calibrated in a known temperature scale.

The new monolithic temperature transducer provides an output directly proportional to absolute temperature at  $10\text{ mV}/^{\circ}\text{K}$ . The chip includes a temperature stable voltage reference and op amp. These allow the output to be offset and scaled to provide any desired temperature scale factor and zero output temperature.

## THERMOMETER DESIGN


The circuit shown will provide a temperature sensitive output with both zero and scale factor independently selectable. Since the temperature

transducer requires about  $1.0\text{ mA}$  for normal operation, the thermometer is pulsed at a low duty cycle to reduce power consumption. A continuous output is obtained between pulses by a sample and hold. Since temperature does not usually change rapidly, the pulsed operation of the thermometer does not detract from its usefulness.

With the components shown, duty cycle is about  $0.2\%$  with a one second sample rate. This gives an average current drain of about  $25\mu\text{A}$  plus the output current. It is designed to operate over a supply voltage of  $8.0\text{V}$  to  $12\text{V}$  with good results. A small  $8.4\text{V}$  mercury battery can give an operational life in excess of one year.

The output of the thermometer is a current proportional to temperature which can be used to drive a meter for a direct readout. Alternatively, a resistor or op amp can be used to obtain a voltage output.

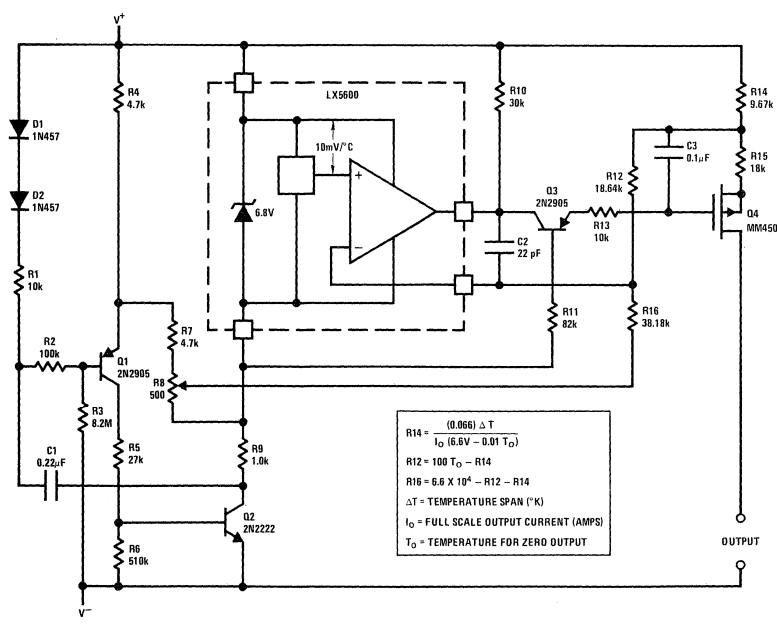A complementary astable multivibrator, made of Q1 and Q2, drives the LX5600 through R9. The timing is set by several components. C1 and R3



Micropower Thermometer Circuit Diagram

control the off-time and C1, R1, R4 and R7 control the on-time. R9 sets the operating current of the transducer to 1.0 mA at the lowest supply voltage.

When the transducer is "on," sample transistor Q3 is also on. The output of the op amp drives the sample capacitor, C3, and MOSFET, Q4. Feedback is obtained from R12, R14 and R16 which set both the zero and scale factor of the thermometer. When the transducer is turned off, a continuous output is provided by C3 and Q4. Resistor R15 decreases the circuit's sensitivity to MOSFET gm, allowing almost any MOSFET to be used. About 2.0V should be dropped across

R15 at full scale output. R8 is used to trim the thermometer, correcting for zener tolerance, temperature error in the sensor and resistor tolerance. With the values shown, a 0 to 50 $\mu$ A output is obtained for a +50°F to +100°F temperature change. Other ranges can be selected by using the formulas shown in the box on the circuit diagram.

The low power consumption makes this thermometer especially attractive for battery operated equipment. Further, the current source output allows long lines to be driven with no loss of accuracy. Finally, the circuit is easy to set up for almost any desired temperature range.

# General Purpose Power Supply

National Semiconductor  
Linear Brief 28  
Robert C. Dobkin  
June 1974



## INTRODUCTION


A general purpose lab type constant voltage/constant current power supply is easily made using standard integrated circuits. The circuit shown will provide up to 25V at up to 10A output with both the output voltage and current adjustable down to zero. Although relatively simple, very high performance is obtained.

Lab supplies must withstand considerable abuse. Good control of maximum output current is mandatory both to protect the supply and the powered circuitry. One of the shortcomings of many commercial supplies is the use of a large output capacitor to help frequency compensate the regulator loop. This output capacitor can discharge many times the peak output current of the supply into the load as well as degrade the ac output impedance when the supply is used as a constant current source. (Of course, the output capacitor helps keep the ac output impedance low when the supply

is used as a constant voltage source.) The circuit shown has good response both as a constant voltage or constant current source.

The use of the LM395 monolithic power transistor as the pass element considerably simplifies the design power. The LM395 acts as a 2A current limited, thermally limited, high gain power transistor. Since only a maximum of 10 $\mu$ A is needed to drive the pass elements and complete overload protection is included on the chip, external biasing and protection circuitry is minimized. Only two control op amps are needed— one for voltage control and one for current control.

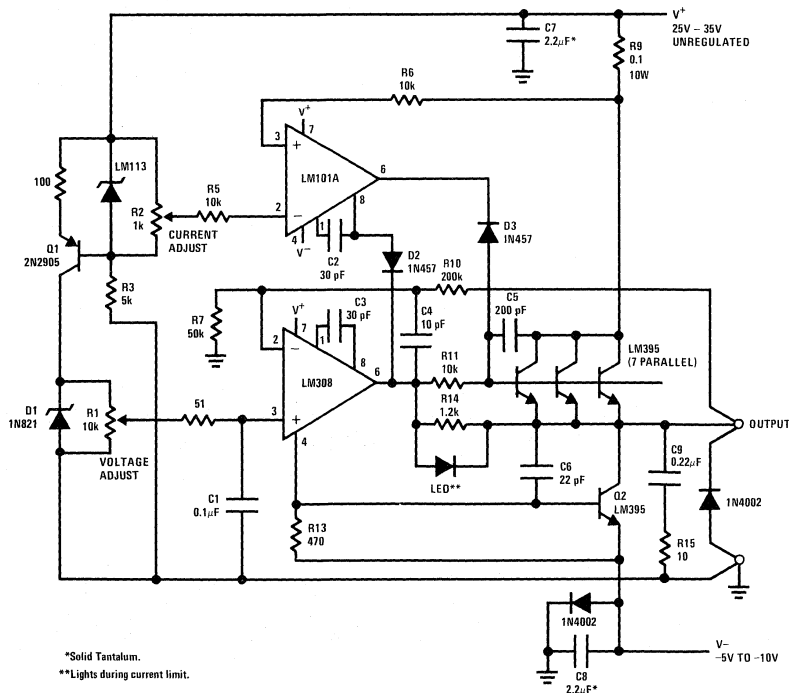In constant voltage operation, a reference voltage is fed from voltage control pot, R1, through a high frequency filter into the non-inverting input of an LM308 op amp. The output of the LM308 drives seven paralleled LM395's as emitter followers to obtain a 10A capability.



Feedback is taken through R10 directly from the output with the overall gain set at 5 by the ratio of R10 to R7. An additional LM395 is driven from the negative power supply lead of the LM308 to provide some output current sink capability (2A) so the supply can be quickly programmed even with large capacitive loads. Frequency compensation is achieved with C3 for the LM308 and C4 for the overall loop. Resistor R11, capacitors C5 and C6 and network R15 — C9 suppress parasitic high frequency oscillations.

When the circuit is used in the constant current mode, the LM101A overcomes the constant voltage loop to control the output. Output current is sensed in R9 and compared with the voltage between  $V^+$  and the arm of R2. R2 is connected across an LM113 low voltage reference diode to provide a 0V to 1.2V reference for 0A to 12A output. When the output current is below

the set level, the LM101A output is positive, reverse biasing D3 and the LM308 control the output. When the current increases to the control point the output of the LM101A swings negative and decreases the drive to the output pass devices through D3, limiting the current. (Note that no separate positive supply is needed since the common mode operative range of the LM101A is equal to the positive supply.) Diode, D2, clamps the output of the LM101A when it is not regulating, decreasing the switchover time from voltage to current mode operation.

A few special precautions are needed in construction for proper operation. All LM395's should be mounted on the same heat sink to insure good current sharing. Also, a large heat sink is necessary since 300W will be dissipated under worst case conditions. Since the LM395's are high devices, the supply bypasses should be near the power transistors.

# Low Cost AM Radio System using LM1820 and LM386

National Semiconductor  
 Linear Brief 29  
 Elias S. Papanicolaou  
 Helge H. Mortensen  
 February 1975



## INTRODUCTION

The majority of linear integrated circuits being produced today is in the field of op amps, comparators and regulators. This has come about for the reason that these types of devices can take advantage of the well matched characteristics of monolithic components. However, in recent years the monolithic integrated circuit has found its place in communication systems such as radios and televisions. The basic philosophy in this area, and the consumer industry as a whole, has mainly been cost reduction over discrete counterparts, improved performance and higher reliability.

An integrated circuit which meets the above criteria is the LM1820 AM-RADIO SYSTEM, designed primarily

for superheterodyne AM receiver applications utilizing an RF-amplifier stage ahead of the mixer-oscillator. However, this linear brief describes how the LM1820 and LM386 can be incorporated in the design of a conventional low cost AM-radio without an RF-amplifier stage.

## RADIO DESCRIPTION

The block diagram of the radio is depicted in *Figure 1*. A complete schematic is shown in *Figure 2*. The building blocks for the Mixer-Oscillator, the two IF stages, and the AGC section, are contributed by the LM1820. Power output of 1/4W into an 8Ω speaker is obtained by the LM386, the gain of which is externally set to 200. The LM1820 is operated from a 6V supply, that is, below the voltage of zener diode D6, see *Figure 3*.

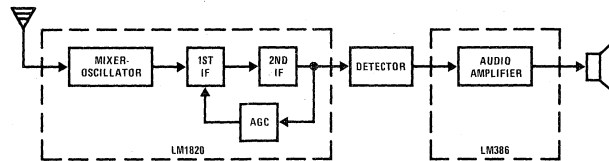


FIGURE 1. Radio Block Diagram

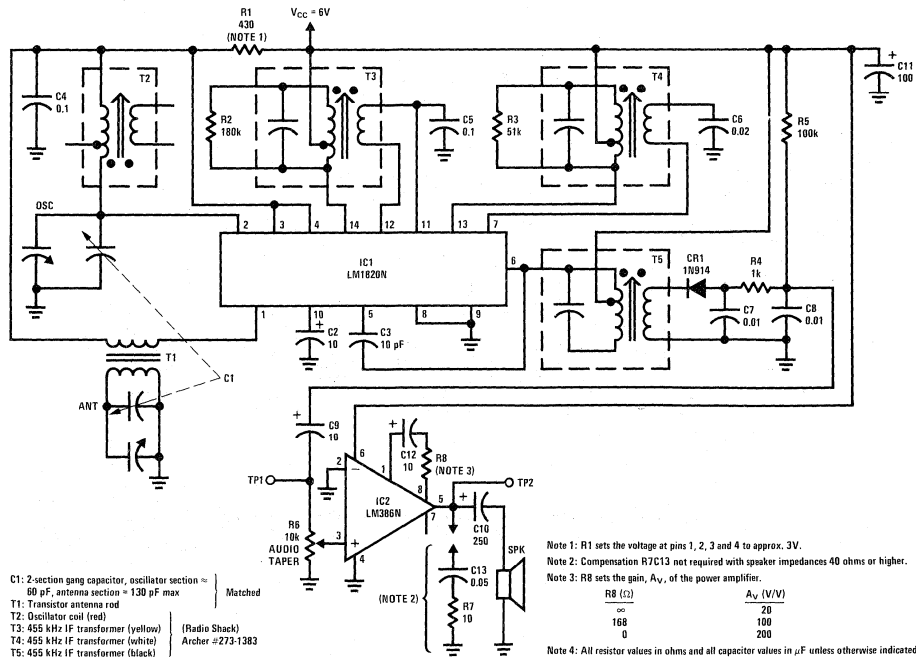


FIGURE 2. Radio Schematic

Pins 1, 2, 3 and 4 are biased from the same supply through a 430Ω dropping resistor. This reduces the total current consumption to approximately 10 mA making the operation from a 6V battery feasible. The dc return of pin 1 and 4 to pin 3 improves component count and prevents transistor Q4 in the oscillator section from saturating. Large swings are preserved by returning the collectors at pins 14, 13 and 6 to  $V_{CC}$  via the primary windings of transformers T3, T4 and T5 respectively. For better linearity, detector diode 1N914 is biased slightly in the forward direction. Radio performance concerning distortion, AGC, sensitivity and signal-to-noise is shown in Figure 4. These data are taken with the radio laid out as shown in Figure 5.

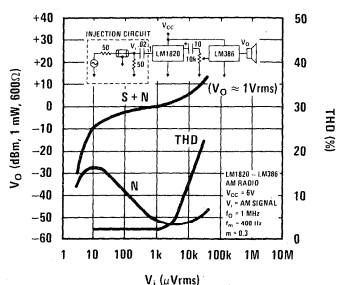


FIGURE 4. Radio Performance Plots

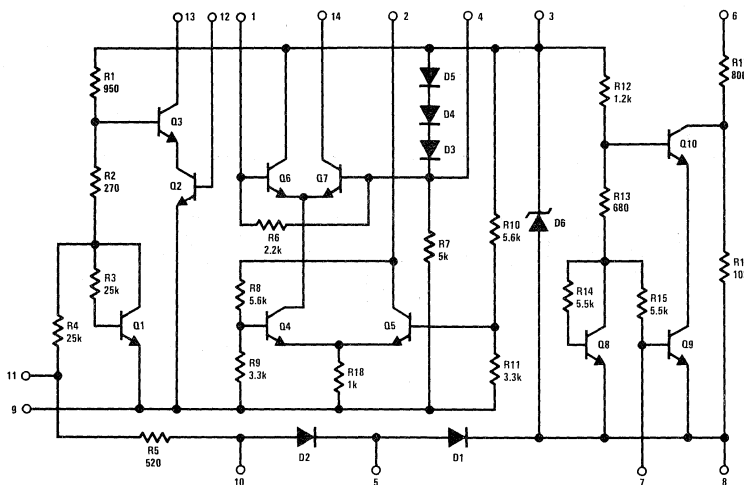


FIGURE 3. LM1820 Schematic

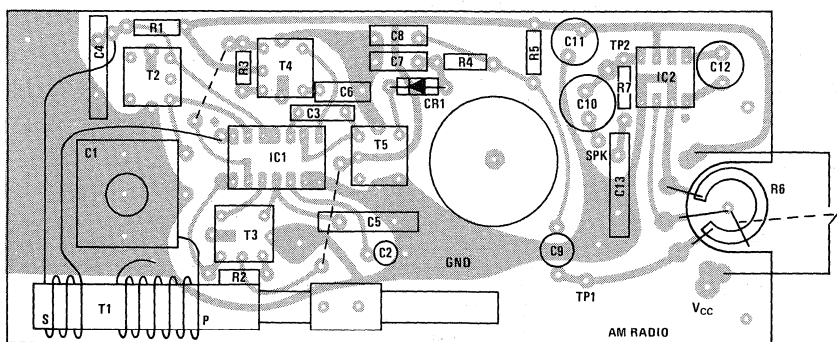


FIGURE 5. Typical Printed Circuit Board Radio Layout (Bottom View)  
(Not Shown Full Size)

# Microvolt Comparator

National Semiconductor  
Linear Brief 32  
Peter Lefferts  
June 1976



## INTRODUCTION

Comparison of dc signal levels within microvolts of each other can be made by using an LM121A pre-amp and an LM111 comparator IC. Implementing this with two separate IC's decreases noise, eliminates troublesome thermal effects, and achieves a maximum offset drift of  $0.22\mu\text{V}/^\circ\text{C}$  (Figure 1).

Designing a practical comparator with a voltage gain of 10 million involves protecting the *input* stage from temperature changes or gradients, and avoiding problems of including the noise filter within the positive feedback loop. The circuit as shown has a  $5\mu\text{V}$  hysteresis which can be trimmed to  $1\mu\text{V}$  under certain conditions. Further, delays *decrease* with increasing overdrive (see chart) due to elimination of input stage thermal effects, saturating stages, and dielectric soak or polarization effects on signal filter capacitors (Table 1).

## DESIGNING WITH A PRE-AMP

With the bias network shown, the LM121A input stage has an open-loop temperature stable voltage gain of close to 100. The  $100\text{k}\Omega$  output impedance of the LM121A is shunted by  $C_S$  to filter out pickup and internally generated noise. No feedback to the inputs of the pre-amp is employed to avoid degrading common-mode rejection of the system.

The separate pre-amp with a gain of 100 provides two major advantages over single comparator designs. First,  $V_{OS}$  and other small errors attributed to the LM111 are reduced by the 100 gain factor. More important, temperature gradient changes which occur within the LM111 when switching any output load, are completely isolated by the separate packages and do not affect the pre-amp. If the entire microvolt comparator were on a single silicon chip, a temperature variation of as little

TABLE 1. Typical Overdrive Delays

HYST. SET	$R_H$	$R_S$	$C_S$	DELAYS WITH VARIOUS OVERDRIVES			
				25%	100%	1000%	100 mV
$5\mu\text{V}$	$75\text{ k}\Omega$	$10\text{ k}\Omega$ Max.	$6800\text{ pF}$	2 ms	1.8 ms	$600\mu\text{s}$	$560\mu\text{s}$

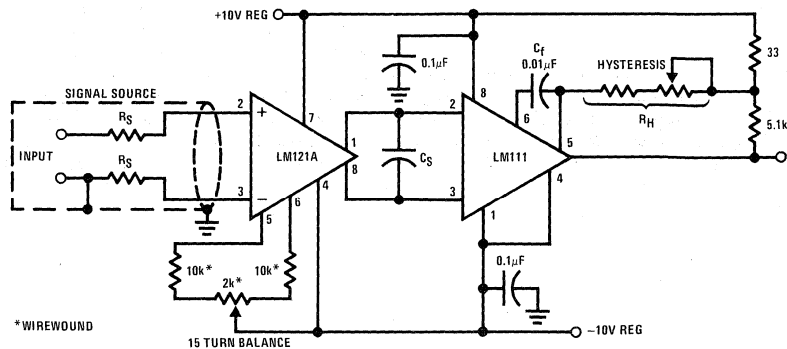


FIGURE 1. Schematic Diagram

as  $1/1000^{\circ}\text{C}$  across the input stage could have a significant effect.

This effect is a major reason for designing circuits sensitive and stable to microvolt dc signals with a *separate* pre-amplifier. Further, the special 4-transistor input stage, when adjusted to zero offset with the "balance" control between pins 5 and 6, automatically reduces  $V_{OS}$  change with temperature to almost zero.

#### FILTERING

The pre-amp/comparator system generates a continuous stream of very fast pulses if assembled without a filter, even with positive feedback for hysteresis. This is caused by both stray output-input feedback, and noise. The noise is both thermal and pickup from the environment, including power switching transients and fluorescent light hash. To cure this, shunt filter capacitor  $C_S$  is used.

Placing this capacitor outside the positive feedback loop has two advantages. It eliminates a tendency for the comparator to oscillate during slow transitions. Also, response time to small signals is halved since the positive hysteresis feedback signal is not stored on the filter capacitor.

A higher frequency filter ( $C_f$ ) is needed to provide a low impedance shunt to any high frequency noise and stray feedback that may be picked up between LM111 terminals 5 and 6. These two terminals have almost the same voltage sensitivity as the normal input terminals. The positive feedback to terminal 5, as described below, is only delayed slightly by this filter.

#### FEEDBACK

The positive feedback provided by the  $5.1\text{k}/33\Omega$  voltage divider with  $R_H$  is needed to insure clean, rapid changes of state. It is applied to one of the "balance" terminals (pin 5) of the LM111 to simplify the circuit over a balanced feedback network, and to minimize signal stored on  $C_S$  as previously described. The current fed back to terminal 5 is single ended with respect to the balance adjust network between these terminals, and hence injects a dc offset of the desired polarity and amplitude for a few microvolts of latching.

#### PERFORMANCE

A tabulation is shown for one of the many possible combinations of input circuits, filters, etc. For large amplitude signals,  $C_S$  can be decreased and hysteresis increased for greater speed. Conversely, to obtain hysteresis as low as  $1\mu\text{V}$ , trim  $R_H$  (to about 300k) use

a  $C_S$  of  $0.01\mu\text{F}$  to  $0.1\mu\text{F}$  and have a low impedance source of signals.

For reduced ambient range and drift specifications, an LM321 can be paired with the LM311 for a cost saving while maintaining the same comparison sensitivity.

#### DESIGN TIPS FOR MICROVOLT SIGNALS

Even with high performance devices such as the LM121, microvolts of error can occur from thermocouple effects, common-mode signals, "microphonics," or unbalances in the input or nulling circuits. As pointed out in application note AN-79, Kovar lead to copper circuit board thermocouple effects can cause a  $3.5\mu\text{V}$  offset voltage for only  $0.1^{\circ}\text{C}$  difference across the input leads. A compact layout of input connections and shielding from air currents will minimize this problem.

Although the LM121A has excellent common-mode rejection ( $> 120\text{ dB}$ ), a 1V change in common-mode voltage can induce up to  $1\mu\text{V}$  of error voltage. For this reason common-mode voltage changes should be kept to a minimum. Also, common-mode voltages allow mechanical vibrations in the probe cable to induce "microphonic" noise signals. Short, stiff, low capacitance and symmetrical input shielded wires are recommended.

If it is possible to have a signal source balanced with regard to ground, it will help decrease errors due to bias currents, and noise due to common-mode and microphonic effects. Matched, low temperature coefficient parts should be used in the balance network, and care should be exercised in shielding input circuits and eliminating ground-loops.

#### APPLICATIONS

The microvolt comparator is particularly well suited to controllers or test equipment having thermocouples or strain gauges as inputs. This includes wind speed indicators, RMS to dc converters, vacuum gauges, gas analysis equipment, conductivity gauges, and hot wire controls. The strain gauges can be used in materials testing, electronic weighing, pressure transducers, and load limiting sensors for cranes, hoists, and rolling mills.

As a temperature controller,  $1/8$  degree or less on-off differential can be obtained using thermocouple types E, J, T or K. Other microvolt signals used for control may come from Hall effect sensors, Bolometers, slide-wires, and heat-flow thermopiles. A microvolt comparator will be useful in "Go/No-Go" testing of low resistances such as switch and relay contacts, RTDs, coil and fuse resistances, and pressure-sensitive-plastic conductors.



# High Speed Warning Device for Automobiles

National Semiconductor  
Linear Brief 33  
Dave Long  
June 1976



Conventional speed warning devices require the addition of a multipole electromagnetic transducer in the transmission or the speedometer cable as a source for the speed signal. The proposed circuit uses the engine speed signal available at the primary of the spark coil and a switch in the transmission which is closed only in high gear. Lowest cost display would be a light emitting diode driven directly from the integrated circuit. Add a durawatt transistor, and an incandescent lamp can be driven. Two NSN71 1/3 inch high 7-segment numeric displays can be hard wired to display the speed at which the limit is set. For best effect, the visual warning should be accompanied by an audible alarm such as a buzzer. A more elegant solution which sounds better and costs little more uses a tone generator to drive a miniature moving coil loudspeaker.

The circuit shown in *Figure 1* employs an LM2900 quad Norton op amp to perform all the above functions. Specifically, A1 amplifies and regulates the signal from the spark coil. A2 converts frequency to voltage so that its output is a voltage proportional to engine RPM. This signal could be used to directly drive a tachometer

if desired. A3 compares the tachometer voltage with the reference voltage and turns on the output transistor at the set speed. A small amount (2%) of positive feedback is provided to prevent annoying intermittent operation. Amplifier A4 is used to generate an audible tone whenever the set speed is exceeded. R1 is adjusted in the factory according to the gear and axle ratios, number of cylinders, wheel and tire size, etc. Note that the 2900 is capable of directly driving the loudspeaker.

In operation, the circuit is powered up so that the tachometer drive is always available. When the transmission moves to top gear, switch S1 closes and connects the output light and speaker displays to the power source. When the vehicle speed exceeds the set value (56 mph U.S. or 82 km/hr South American) the light and tone will be energized. To extinguish these warnings, the driver will have to slow the vehicle to below the value set by the hysteresis (say 55 mph or 80 km/hr). The integrating 10 $\mu$ F capacitor on the frequency to voltage converter, A2, could be increased so that the alarm is not sounded during momentary excursions above the set speed.

TABLE I. Component Distribution

	PRE-AMP & FILTER	FREQ TO VOLTAGE (TACH)	COMP & OUTPUT	TONE GEN	PROT & REG	TOTAL
Resistors	4	2	5	4	1	16
Capacitors	1	2		1	1	5
Diodes	1	1		1		3
Transistors			1*		1	2
IC's	1/4	1/4	1/4	1/4		1
Other			LED	Speaker		<u>2</u>
						29

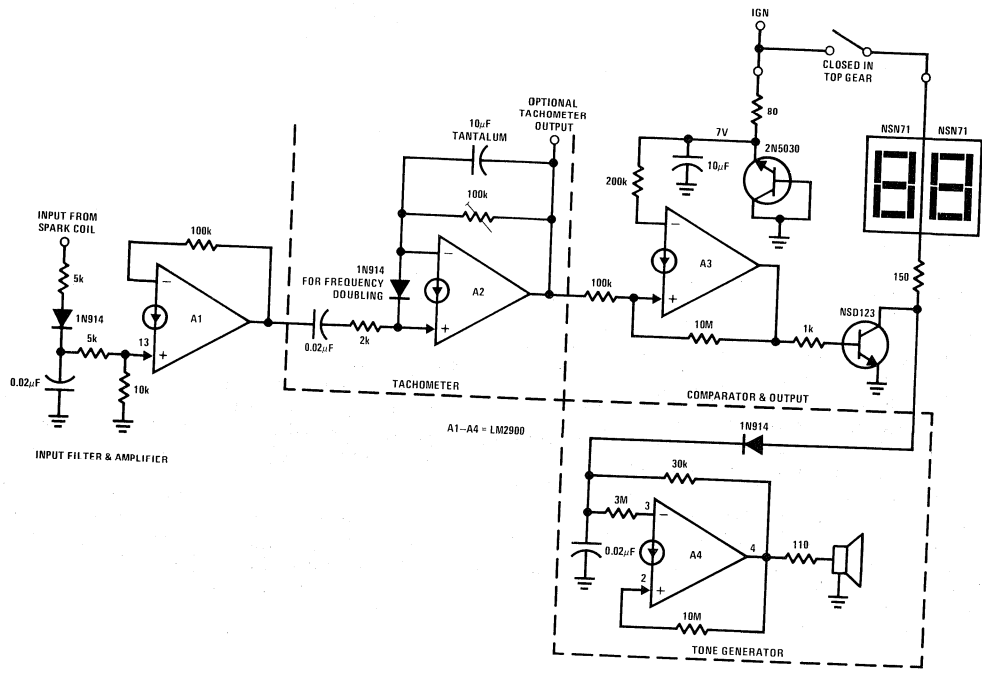


FIGURE 1. High Speed Warning Device

Note: Since this linear brief was written, the LM2907, LM2917 Frequency to Voltage Converter was developed which performs the same function as described here. See Application Note AN-162.

# A Micropower Voltage Reference

National Semiconductor  
Linear Brief 34  
Nello Savastopoulos  
June 1976



A low-drift voltage reference can be easily made by converting a zero temperature coefficient current to a voltage. JFETs biased slightly below pinch-off exhibit a zero temperature coefficient drain current ( $I_D$ ) as shown in *Figure 1*. With the above property and a micropower operational amplifier, used to convert the drain current to a voltage, a low power consumption voltage reference can be built as shown in *Figure 2*. The consumption of LM4250 op amp is programmed through resistor  $R_{SET}$ . Potentiometer  $P1$  should be adjusted for low output ( $V_{REF}$ ) temperature coefficient. Actually, it can be trimmed for positive, negative or zero temperature coefficient. The output voltage is trimmed through  $P2$  and it is expressed by:

$$V_{REF} = I_{D1}(P2' + R1 + R2),$$

$$R2 = R3, I_{D1} \approx I_{DSS} \left[ 1 - \frac{V_{GS}}{V_P} \right]^2$$

With the values shown in *Figure 2*, the temperature coefficient of the output is  $0.002\%/^{\circ}C$  and the overall

standby current less than  $100\mu A$ . The characteristics of the LM4250 are a function of its supply current, which depends on  $R_{SET}$ , and  $V^+$ .  $V^+$  can be provided by  $V_{REF}$  through the addition of a second FET,  $J2$ , shown in *Figure 3*. This way the parameters of the op amp will be independent of the unregulated input. The reference voltage output can be taken from the wiper of the potentiometer  $P2$  ( $V_{REF} = V^+$ ) or from the source of  $J2$  ( $V_{REF} > V^+$ ). In the first case, the output impedance of the circuit is quite high and buffering may be required according to the application. The output impedance in the second case is low, essentially the  $1/gm$  of ( $J2$ ) divided by the loop gain of the circuit. In this case, a small temperature coefficient due to the supply current of the LM4250 is going to be added and be compensated for by an additional trimming of  $P1$ .  $V_{REF}$  is computed by:

$$V_{REF} \approx I_{D1} [P2 + R1 + R2] + P2'' [I_S + I_{D1}],$$

$$R2 = R3, I_S \approx \frac{6(V^+ - V_{BE})}{R_{SET}}$$

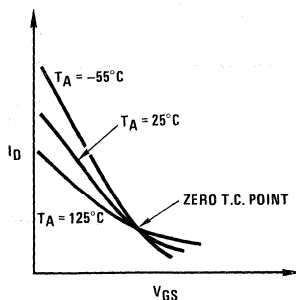


FIGURE 1. FET Transfer Characteristics

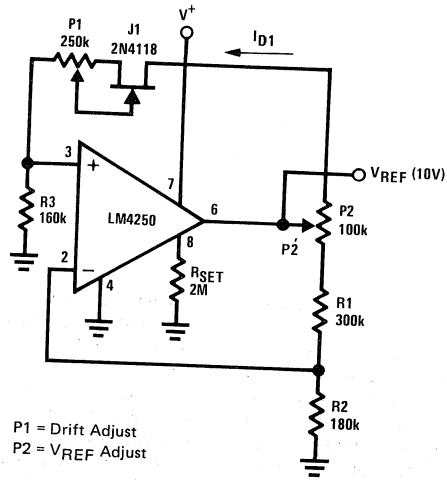


FIGURE 2. Basic Voltage Reference

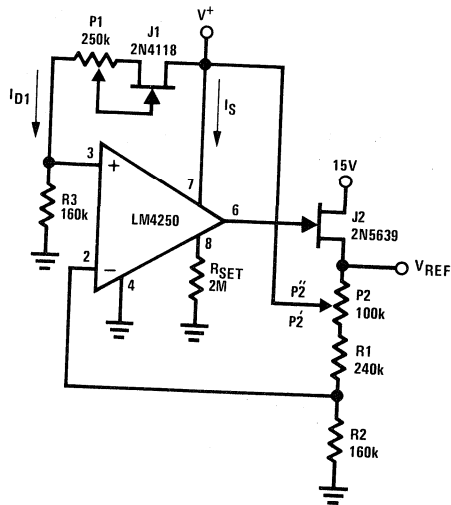


FIGURE 3. Improved Voltage Reference

# Adjustable 3-Terminal Regulator for Low-Cost Battery Charging Systems

National Semiconductor  
Linear Brief 35  
Robert C. Dobkin  
August 1976



LB-35 Adjustable 3-Terminal Regulator for Low-Cost Battery Charging Systems

With the introduction of the LM317, a 3-terminal adjustable regulator, it becomes relatively easy to design high-performance, low-cost battery charging systems. Even single battery cells can be charged on this new regulator, which is adjustable down to 1.2V. The internal protection circuitry can be used to limit charging current as well as to protect against overloads. The output voltage is easily adjusted so multiple voltage chargers can be made.

The ability to accurately adjust the output voltage of the LM317 makes it especially attractive for constant voltage battery charging applications. Batteries are most quickly charged by "constant-voltage" charging circuits; however, close control of the charging voltage is necessary to prevent overcharging, especially with nickel cadmium cells. The internal protection circuitry of the LM317 is helpful in protecting against accidental overload conditions commonly occurring in charging systems.

## INTERNAL CURRENT LIMIT

The peak charging current or output current is controlled by the internal current limit of the LM317. This current limit will work even if a battery is connected backwards to the output of the charger. Should a fault condition exist for an extended period of time, the thermal limiting circuitry will decrease the output current, protecting the regulator as well as the transformer. A constant voltage charger circuit is shown in Figure 1. The output voltage is set with resistors R2 and R3 and given by

$$V_{OUT} = 1.25 \left( 1 + \frac{R3}{R2} \right)$$

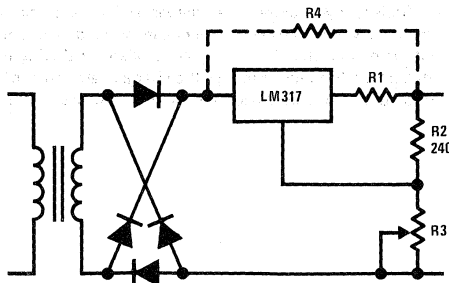


FIGURE 1. Constant Voltage Charging Circuit

Since, in low-cost applications, no filter capacitors are used on the output of the rectifier, the battery is only charged on the peaks of the sine wave. This requires the peak output voltage from the transformer to be at least 50% greater than the battery voltage plus 3V. However, little cost premium should result since the average current from the transformer is lower than capacitive input filter circuits. Optional resistors R1 and R2 are used to further control the charging characteristics. Resistor R1 controls the output impedance of the charger allowing a "taper-charge" characteristic to be generated. The LM317 can also be used to limit the peak charging current to a partially charged battery at a value other than the regulator current limit. With R1 in the circuit, the output impedance is:

$$Z_{OUT} = R1 \left( 1 + \frac{R3}{R2} \right)$$

Including R1 in the feedback loop decreases the value of resistor needed for a particular output impedance reducing cost and power dissipation.

For example, with a 6V gelled electrolyte battery the regulator can be set to give a 6.9V output. Nominally, the battery is discharged to about 5V, making R1 0.4Ω output impedance and limiting the charging current to 0.5A at the start of charging rather than the internal current limit of the regulator. With a fully discharged battery or under short circuit conditions, the peak output current is still 2A for the LM317K with the resistor dissipating 1.6A as opposed to 8W if a 2Ω resistor were used directly in series with the battery.

Resistor R4 can be included to provide a low "topping-up" current for a charged battery.

This regulator configuration provides some other important features to the charger. If input power is removed and a fully charged battery is connected to the charger output, there is no damage. Under these conditions about 5 mA of current will be drawn by divider R2, R3. Since there is no ground connection to the LM317 regulator, very little current flows through the LM317. In this respect, the LM317 differs from other 3-terminal regulators, which can be damaged by applying power to the output terminal with the input open-circuited. If the battery is connected backwards, the LM317 will current limit and thermal limit normally, protecting the charger.

## DECREASING CURRENT LIMIT

Adding a single NPN transistor can be used to decrease the current limit of the charge as shown in *Figure 2*.

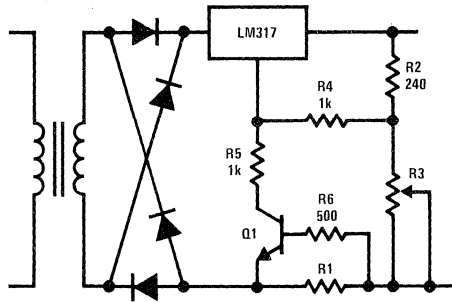


FIGURE 2. Constant Voltage Charger with Peak Current Limiting

Resistor R1 senses the output current and turns on Q1 when  $I_{OUT} R1$  equals about 0.6V. Transistor Q1 pulls the adjustment terminal negatively decreasing the output voltage and controlling the output current. A limitation of this circuit is that it does not work for direct short circuits. The output voltage must be above about 0.6V for the external current limiting to be active. The internal current limit of the LM317, of course, is still operative. This is not usually a problem since batteries charge to above 0.6V very quickly. Resistors R4, R5 and R6 protect the regulator and transistor for both direct short circuits or reverse battery connections.

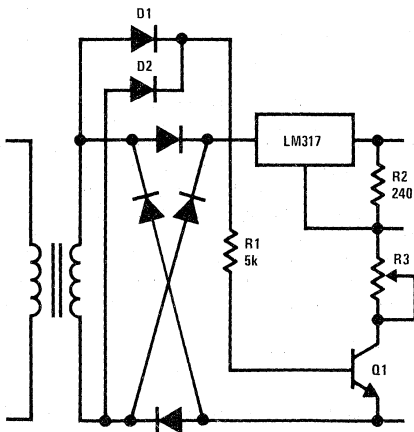


FIGURE 3. Charger with No Battery Loading when Power is "OFF"

As illustrated in *Figure 3*, in float or standby applications, it is desirable to remove all loading from the battery when input power is "OFF." When power is "ON," Q1 is saturated, grounding the voltage setting divider R2, R3 and the circuit works in a similar manner to the charger circuit in *Figure 1*. When power is "OFF," Q1 is open, eliminating any loading on the battery. A separate pair of low current diodes D1, D2 are necessary to bias Q1, rather than the power bridge rectifier. If R1 was tied to the output of the bridge, reverse current flow through the LM317 would keep Q1 "ON" and loading the battery.

A simple constant current charger for any type of battery is shown in *Figure 4*. A resistor R1 between the adjustment terminal and the output of the regulator sets the output current at:

$$I_{OUT} = \frac{1.25}{R1}$$

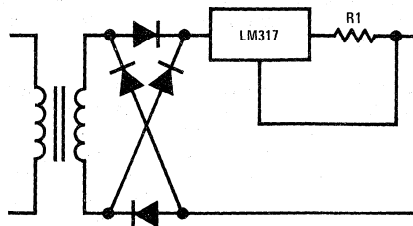


FIGURE 4. Constant Current Charger

Current can be set at anywhere between 10 mA and 1.5A by appropriate resistor choice. Current regulation is very tight at any current level since only 50 $\mu$ A flows out of the adjustment terminal. This circuit is also immune to damage from shorts or reverse battery connections. The input voltage for regulation should also be about 1.5 times the battery voltage plus 3V.

## UNIQUELY SUITED

The ability to adjust the output of the LM317 3-terminal regulator makes it uniquely suited for battery charging systems. Little has been included about charging specific types of batteries, since the characteristics of the charger should be matched to the battery. These charger circuits, although very simple, perform well. They are easily modified for voltage, current or even temperature coefficient by making the divider string temperature sensitive. More complex chargers can be made since the output of the LM317 is easily controlled by driving the adjustment terminal. Finally, the chargers are inherently protected against overloads and fault conditions.

# Simple Temperature Control

National Semiconductor  
Linear Brief 36  
Robert C. Dobkin  
December 1976



The new LX5600 monolithic temperature transducer is well-suited to simple "ON"/"OFF" temperature control applications. Included in the transducer are all the basic components needed for the controller—a sensor, reference and amplifier—so all that is needed is appropriate external power circuitry to realize a full controller. The circuit shown here can provide  $\pm 1^\circ\text{C}$  control over a  $-55^\circ\text{C}$  to  $+125^\circ\text{C}$  temperature range.

A basic circuit of the transducer is shown in *Figure 1*. Across the power supply pins is an active shunt regulator to provide a constant 6.8V reference. The sensor is directly calibrated in degrees Kelvin at  $10\text{ mV}/^\circ\text{K}$  and drives the non-inverting input of an internal op amp. The inverting input and the output are both available at pins 2 and 1, respectively.

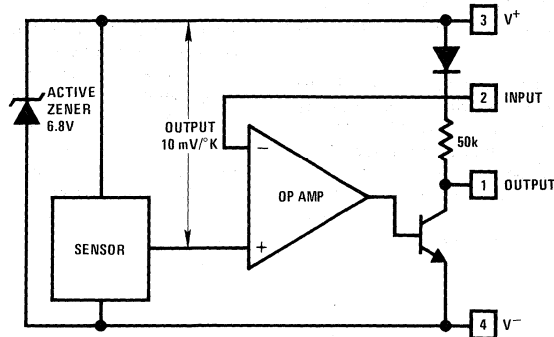


FIGURE 1. Simplified Circuit of the LX5600, LX5700

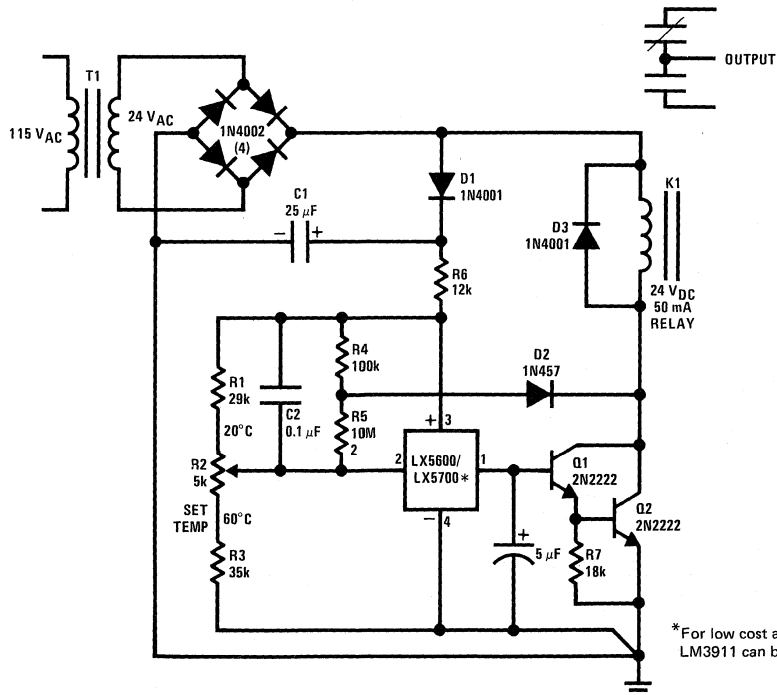


FIGURE 2. Temperature Controller

\* For low cost applications, an LM3911 can be used

Figure 2 shows the complete circuit of the controller. Transformer T1 provides 24 VAC to a full wave bridge rectifier. Since power for the transducer is only about 3 mA, a decoupling diode, D1, and filter capacitor, C1, are used to supply filtered dc to the transducer while unfiltered power is used for the relay—greatly decreasing capacitor size and cost. Resistor, R6, sets the current through the shunt regulator in the transducer at about 3 mA.

A resistive divider, R1, R2 and R3 is connected across the transducer and is used to set the temperature. The divider is set up to provide voltages at the ends of R2 corresponding to the minimum and maximum control temperature at  $10 \text{ mV}/^\circ\text{K}$ . With the values shown, the control range is from about  $15^\circ\text{C}$  to  $60^\circ\text{C}$  for a nominal 6.8V shunt regulator voltage. Other dividers are easily calculated for other temperature ranges; however, be sure to note that the voltages for the divider are referred to pin 3, not ground.

Capacitor, C2, eliminates noise and pickup in the divider string. Since the gain of the internal amplifier is very high, hysteresis is added to insure positive "ON"/"OFF" control. Diode, D2, in conjunction with resistor R4 and R5 provide a  $\pm 10 \text{ mV}$  change at the arm of the pot giving  $\pm 1^\circ\text{C}$  of hysteresis. Decreasing R5 will increase the hysteresis. The output of the sensor drives Darlington to obtain a 50 mA (or more) output.

The sensor is in a standard TO-5 or TO-46 package. For surface or air temperature sensing, there are many small clip-on heat sinks available which can be used with the sensor. A simple probe can be made using heat-shrink tubing and RTV silicon rubber. Three-leads-plus-shield cable is a good choice for wire with the shield connected to pin 4.

To make the probe, wires are soldered to the leads of the IC and shrink tubing is used for insulation. Then silicon rubber is smeared over the wires and IC. A larger piece of shrink tubing is then put over the probe and leads. When the large piece of tubing is shrunk, it will force out excess silicon rubber and provide a seal around the IC. The finished probe is relatively sturdy and waterproof if made carefully.

When setting up a temperature controlled system, the sensor should be as near the heater as possible. If there is a long lag between the heat application and the sensing, the system will overshoot and large variation in temperature can occur.

Applications for this controller are wide. It can be used for baths, ovens, over-temperature protection or even home thermostats. Long-term stability and repeatability is better than  $0.5^\circ\text{C}$ .



# Low Current Ammeter

National Semiconductor  
 Linear Brief 37  
 Robert C. Dobkin  
 February 1977




Submicroamp current measurements, although not easy, are relatively straightforward. Firstly, an ultra low input current amplifier is needed. Ideally, the input current of the amplifier should be negligible compared to the measured current. Present day IC op amps have currents in the pico-amp range; and for the majority of applications are sufficient. Secondly, high value precision resistors are needed for scaling the current to a more easily handled level. Since precision resistors in the 1000 MΩ range are relatively expensive, a different method of scaling is used here.

The circuit shown can measure currents from 100 pA to 100 μA without the use of high value resistors. Accuracy is better than 1% over most of the range, depending upon the accuracy of the divider resistor and

the input bias current of the op amp. Using the LM216A as the input amplifier limits the low end measurement to 100 pA due to the 20 pA input bias current.

The LM216A is an ultra low input current bipolar op amp. Unlike FET op amps, which can give better accuracy at 25°C, performance over a 0°C to +70°C range is better with a bipolar op amp. FET input current doubles every 10°C while the input current of the LM216A only changes 1%/°C. This low change makes it easy to compensate for the input current of the op amp over the operating temperature range.

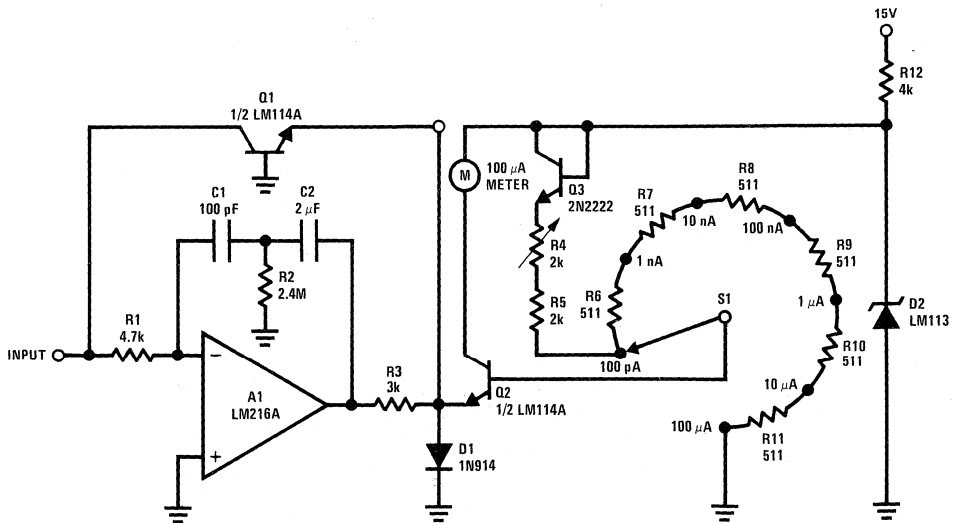One of the requirements for a good current meter is low series voltage drop. Since the voltage across the



inputs of an op amp is forced to virtually zero, it makes a good choice for the input of a current meter. Amplifier A1 is used as an inverting amplifier for the input. This ensures only a few millivolts drop at any current level.

Feedback around the op amp is accomplished with a transistor, rather than a resistor. The op amp forces the collector current of Q1 to equal the input current. This causes the emitter-base voltage of Q1 to be proportional to the log of the input current. Resistors R1, R2, R3 and capacitors C1, C2 frequency compensate the log circuit since Q1 provides gain in the feedback loop.

The output of A1 from the log amplifier is taken from the emitter of Q1 to drive Q2. Q2 anti-logs the output and drives the meter. The output of Q2 is proportional to the input current ( $V_{be}$  of Q1) scaled by a constant proportional to the voltage from divider through S1.

For transistor operating at different current levels, the  $V_{be}$  difference equals

$$\Delta V_{be} = \frac{kT}{q} \ln \frac{IC_2}{IC_1}$$

solving for  $IC_3$

$$IC_2 = IC_1 e \exp \left( \frac{\Delta V_{be} q}{kT} \right)$$

Where  $IC_1$  and  $IC_2$  are the collector currents of Q1,  $Q$  is the charge of an electron,  $k$  is Boltzmann's constant,  $T$  is temperature in degrees Kelvin, and  $\Delta V_{be}$  is the voltage applied to the base of Q2. If  $\Delta V_{be}$  varies as absolute temperature, the exponent will be a constant.

The voltage driving the divider is obtained from a 1.22V low voltage reference diode (LM113) through a 2N2222 transistor and resistor string. The voltage across the divider varies as absolute temperature, keeping the multiplier constant.

Calibration is simple, requiring only one adjustment. R4 is used to adjust for full scale deflection with a  $1 \mu A$  input current. This will give maximum accuracy over the operating range of currents. As mentioned, the low end accuracy is limited by the bias current of the op amp. On the maximum input current scale ( $100 \mu A$ ), the 0.5 mV offset of the transistor pair will introduce another 1% to 2% error.

# Wide Range Timer

National Semiconductor  
Linear Brief  
Robert C. Dobkin  
February 1977



One of the problems encountered in potentiometer controlled circuits is dynamic range. With a linear pot, about a 100:1 range is the limit. Although the pot resolution may be better than 1%, the angular displacement for good control becomes too small. Usually, range switching is then used.

A logarithmic control is a possible solution. With log controls, the resolution is the same anywhere within the operating range. For example, if 40° rotation is equal to a change from 10% to 100% of full scale, then 40° rotation is also equal to a change from 0.01% to 0.1% of full scale. It is easy to control a function over a

1,000,000:1 range with good control anywhere within the range.

The exponential relationship between the emitter-base voltage of a transistor and its collector current is well known. This relationship holds true within a few percent over extremely wide ranges. Using a transistor pair, and an op amp, it is easy to make a current source controllable over a 6 decade range.

Figure 1 shows a timer which can be adjusted from 2 ms to 2000 seconds with a single control. An LM122 is

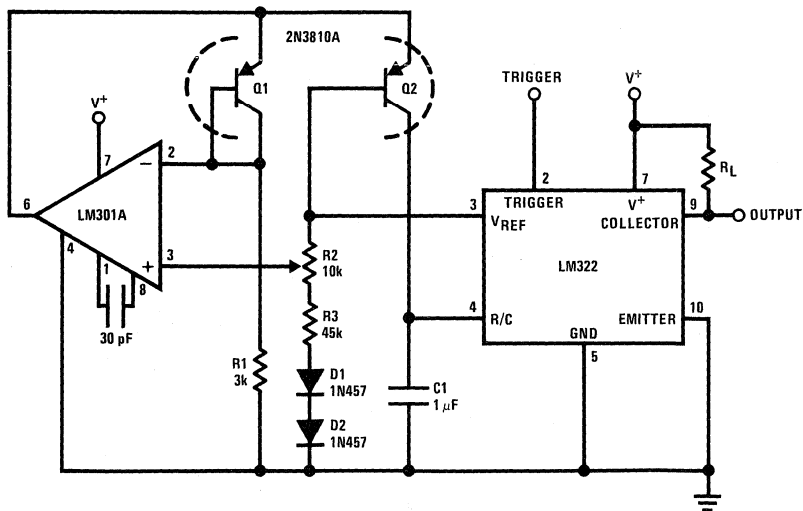


FIGURE 1. 2 ms to 2000 Second Timer

used for the timing function in conjunction with a current source that is logarithmically controlled from a pot. The operation is as follows:

Transistors Q1 and Q2 are a matched PNP pair. Resistor R1 and the op amp set up a constant current of 1 mA through Q1 using the internal 3V reference from the timer. With R2 at the most positive end of its range, the non-inverting input of the op amp is at  $V_{REF}$ . This forces the emitter-base voltage of Q2 to equal Q1 and since the transistors are matched, the collector current of Q2 is also 1 mA. A time-out period of 2 ms results.

Rotating R2 subtracts the voltage between the arm of the pot and  $V_{REF}$  from the emitter-base voltage of Q2—lowering its collector current. The current is decreased by a factor of 10 for every 60 mV developed. A total of 360 mV is dropped across the pot, allowing a reduction in Q2 collector current by a factor of 1,000,000 or from 1 mA to 1 nA. A 1 nA charging current gives a 2000

second time out. (At maximum time, there is about a 30% error due to the 0.3 nA input current of the comparator). Finally, diodes D1 and D2 temperature compensate the voltage across the pot.

Calibrating the circuit is relatively easy (except for obtaining a log dial for the pot). Resistor R1 is adjusted for the minimum operating time removing for mismatch in the transistors, capacitor tolerance, and the offset of the op amp. R3 is used to calibrate the full scale time by adjusting the drop across R2 to 360 mV.

This type of log control is not limited to timers. If used in oscillator or function generator circuits, an ultra wide range VCO can be made. Also, in power supply circuitry, it is possible for a regulator to have as much resolution when adjusted for 0.001V output as when the output is 10V. Finally, a log current generator makes an easily adjusted low value current source without high value resistors.

# Circuit Techniques for Avoiding Oscillations in Comparator Applications

National Semiconductor  
Linear Brief 39  
Peter Lefferts  
January 1978




When a high-speed comparator such as the LM111 is used with fast input signals and low source impedances, the output response will normally be fast and stable, assuming that the power supplies have been bypassed (with  $0.1 \mu\text{F}$  disc capacitors), and that the output signal is routed well away from the inputs (pins 2 and 3) and also away from pins 5 and 6.

However, when the input signal is a voltage ramp or a slow sine wave, or if the signal source impedance is high ( $1 \text{ k}\Omega$  to  $100 \text{ k}\Omega$ ), the comparator may burst into oscillation near the crossing-point. This is due to the high gain and wide bandwidth of comparators like the LM111. To avoid oscillation or instability in such a usage, several precautions are recommended, as shown in *Figure 1* below.

1. The trim pins (pins 5 and 6) act as unwanted auxiliary inputs. If these pins are not connected to a trim-pot, they should be shorted together. If they are connected to a trim-pot, a  $0.01 \mu\text{A}$  capacitor C1 between pins 5 and 6 will minimize the susceptibility to AC coupling. A smaller capacitor is used if pin 5 is used for positive feedback as in *Figure 1*.
2. Certain sources will produce a cleaner comparator output waveform if a  $100 \text{ pF}$  to  $1000 \text{ pF}$  capacitor C2 is connected directly across the input pins.
3. When the signal source is applied through a resistive network,  $R_s$ , it is usually advantageous to choose an  $R_s'$  of substantially the same value, both for DC and for dynamic (AC) considerations. Carbon, tin-oxide, and metal-film resistors have all been used successfully in comparator input circuitry. Inductive wirewound resistors are not suitable.

4. When comparator circuits use input resistors (e.g. summing resistors), their value and placement are particularly important. In all cases the body of the resistor should be close to the device or socket. In other words there should be very little lead length or printed-circuit foil run between comparator and resistor to radiate or pick up signals. The same applies to capacitors, pots, etc. For example, if  $R_s = 10 \text{ k}\Omega$ , as little as 5 inches of lead between the resistors and the input pins can result in oscillations that are very hard to damp. Twisting these input leads tightly is the only (second best) alternative to placing resistors close to the comparator.

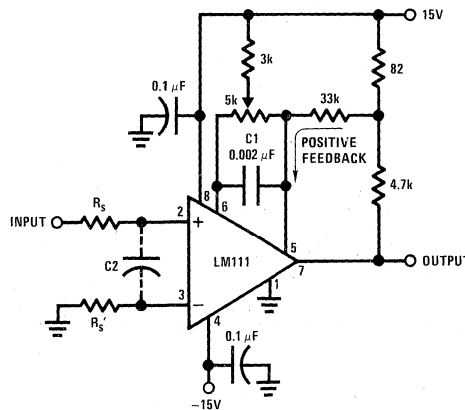5. Since feedback to almost any pin of a comparator can result in oscillation, the printed-circuit layout should be engineered thoughtfully. Preferably there should be a groundplane under the LM111 circuitry, for example, one side of a double-layer circuit card. Ground foil (or, positive supply or negative supply foil) should extend between the output and the inputs, to act as a guard. The foil connections for the inputs should be as small and compact as possible, and should be essentially surrounded by ground foil on all sides, to guard against capacitive coupling from any high-level signals (such as the output). If pins 5 and 6 are not used, they should be shorted together. If they are connected to a trim-pot, the trim-pot should be located, at most, a few inches away from the LM111, and the  $0.01 \mu\text{F}$  capacitor should be installed. If this capacitor cannot be used, a shielding printed-circuit foil may be advisable between pins 6 and 7. The power supply bypass capacitors should be located within a couple inches of the LM111. (Some other comparators require the power-supply bypass to be located immediately adjacent to the comparator.)



Pin connections shown are for LM111H in 8-lead TO-5 hermetic package


FIGURE 1. Improved Positive Feedback

6. It is a standard procedure to use hysteresis (positive feedback) around a comparator, to prevent oscillation, and to avoid excessive noise on the output because the comparator is a good amplifier for its own noise. In the circuit of *Figure 2*, the feedback from the output to the positive input will cause about 3 mV of hysteresis. However, if the value of  $R_5$  is larger than  $100\Omega$ , such as  $50\text{ k}\Omega$ , it would not be reasonable to simply increase the value of the positive feedback resistor above  $510\text{ k}\Omega$ . The circuit of *Figure 3* could be used, but it is rather awkward. See paragraph 7, below, for the alternative.

7. When both inputs of the LM111 are connected to active signals, or if a high-impedance signal is driving the positive input of the LM111 so that positive feedback would be disruptive, the circuit of *Figure 1* is

ideal. The positive feedback is to pin 5 (one of the offset adjustment pins). It is sufficient to cause 1 to 2 mV hysteresis and ensure sharp output transitions with input triangle waves from a few Hz to hundreds of kHz. The positive feedback signal across the  $82\Omega$  resistor swings 240 mV below the positive supply. This signal is centered around the nominal voltage at pin 5, so this feedback does not add to the  $V_{OS}$  of the comparator. As much as 8 mV of  $V_{OS}$  can be trimmed out, using the  $5\text{ k}\Omega$  pot and  $3\text{ k}\Omega$  resistor as shown.

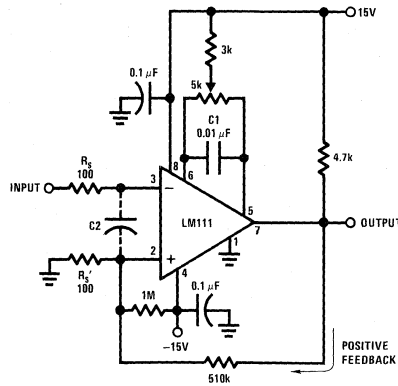8. These application notes apply specifically to the LM111, LM211, LM311, and LF111 families of comparators, and are applicable to all high-speed comparators in general, (with the exception that not all comparators have trim pins).



Pin connections shown are for LM111H in 8-lead TO-5 hermetic package

FIGURE 2. Conventional Positive Feedback

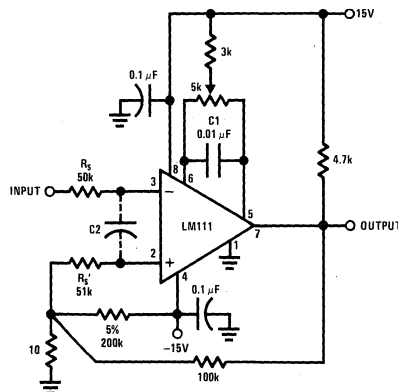


FIGURE 3. Positive Feedback With High Source Resistance

# Two Wire Current Transmitters

National Semiconductor  
Linear Brief 40  
Robert C. Dobkin  
December 1978



Transmitting analog information from remote points is not easy. Line resistance and ground loop voltages tend to degrade accuracy unless special precautions are taken.

The most common method of signal transmission is to use a 4-wire system. Two wires are used for power to the remote station and 2 wires are used to return the signal. At the receiving end, a high input impedance differential amplifier is used to eliminate the effects of ground loop voltages. By transmitting power and signal over the same wires, system cost is reduced.

The system shown here can accurately transmit data over long distances, with a minimum of problems. Rather than transmit the data as voltage, a precise current is used. Further, the system needs only 2 leads. Remote-station power and analog information are transmitted over the same 2 wires.

Figure 1 shows a simple 2-wire current transmitter. An LM304 voltage regulator is used as a specialized op-amp for current control. The LM304 has an op-amp, output stage and voltage reference which make it especially suitable for this application. The op-amp input and output stage will operate with common-mode voltages equal to the positive supply voltage.

The inverting input, positive supply, and outputs (pins 7, 8 and 9) are tied together. This forces the total device

current to flow through R3. The input signal is applied through R5 to the non-inverting input. Since the current into the non-inverting input is negligible, an input voltage causes a current flow through R5 equal to

$$I = \frac{V_{IN}}{10 \text{ k}\Omega}$$

This same current flows through R2 and causes the input voltage to also appear across R2. The LM304 forces the voltage between pins 1 and 7, 8, and 9 to be equal so the input voltage also appears across R3 with a resulting current of

$$\frac{V_{IN}}{R3}$$

The total current from the supply is drawn through R2 and R3 is therefore well defined and easily calculated.

$$I_{SUPPLY} = \frac{V_{IN}}{R5} \frac{(1 + R2)}{R3} + \frac{2.4V}{R1} \frac{(1 + R2)}{R3}$$

Since the LM304 must draw some supply current, the output current for zero input signal must be greater than zero. This zero signal current is set by R1 from the

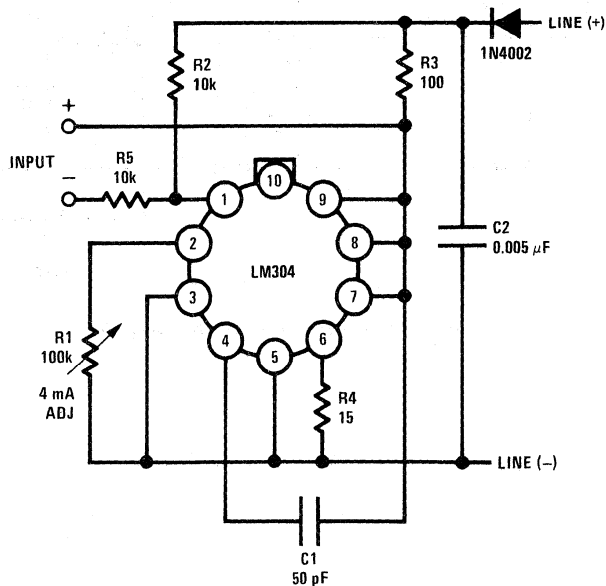


FIGURE 1. Basic Current Transmitter

internal reference of the LM304. A constant 2.4V is held across R1 and the current through R1 is delivered to pin 1 of the device. The current then flows through R2 to set the minimum supply current. For the values given this is about 4 mA. Capacitors C1 and C2 frequency compensate the LM104 and R4 sets the maximum output current at about 40 mA.

Figure 2 shows a current transmitter interfaced with an op-amp for additional gain. The output of the op-amp drives the LM304 through R1. The "zero input" current, in this case is set by R1 and the LM336 reference diode instead of the internal reference of the LM304.

$$I_{OUT} = \frac{V_{IN} R_f}{R_1 R_s} \frac{(1 + R_2)}{R_3} + \frac{2.5V}{R_1} \frac{(1 + R_2)}{R_3}$$

Although both of these circuits are designed for voltage inputs, resistance sensors can be used too. The circuit in Figure 1 is especially suitable for resistance inputs. R2

can be replaced with a resistance sensor and R1 used to set the excitation current. The output current is then given by:

$$I_{OUT} = \frac{2.4}{R_1} \frac{(1 + R_2)}{R_3}$$

The maximum excitation current should be limited to 2 mA and the minimum "zero" current level set to about 4 mA.

The performance of both current transmitters is excellent. Linearity is better than 0.1% and current change with voltage is about 7  $\mu$ A per volt. Operating voltage range is 10V to 40V; however at high voltages and high currents the LM304 should be operated either with a boost transistor or heat sink to minimize device heating.

At the receiving end, either a simple op-amp circuit or just a resistor can be used to convert the current back to a voltage. Noise is easily filtered by a capacitor across the line.

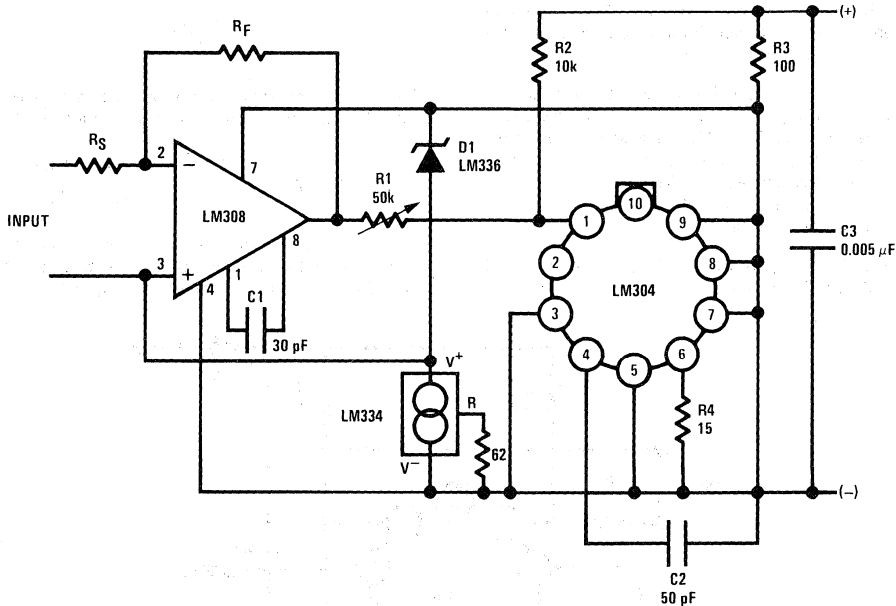


FIGURE 2. Current Transmitter With Amplifier



# Precision Reference Uses Only Ten Microamperes

National Semiconductor  
Linear Brief 41  
Carl Nelson  
June 1978



Increasing interest in battery-operated analog and digital circuitry in recent years has created the need for a micropower voltage reference. In particular, the reference should draw 10  $\mu\text{A}$  or less and operate from a single 5V supply. These requirements eliminate zener diodes which tend to have unpredictable temperature drift and are noisy at low currents and low voltages. One possibility is the LM103 series of punch-through diodes which have break-down voltages of 1.8V to 5.6V and operate well at 10  $\mu\text{A}$ . Unfortunately, these devices drift at  $-5 \text{ mV}/^\circ\text{C}$  and extra circuitry must be added to create a low-drift reference. Non-linearity in the drift characteristic limits usable drift compensation to about 50 ppm/ $^\circ\text{C}$ . Variations in slope from device to device can be up to  $\pm 0.5 \text{ mV}/^\circ\text{C}$ , so each reference must be individually corrected for temperature drift in an oven test.

The LM134 current source can provide an interesting solution to the low-power-drain reference problem. This device is a 3-terminal current source which has a compliance of 1V to 40V and is programmable over a current range of 1  $\mu\text{A}$  to 10 mA. Current is determined by an external resistor. With a zero drift resistor, the LM134 current is directly proportional to absolute temperature ( $^\circ\text{K}$ ). Untrimmed accuracy of the current is  $\pm 3\%$ , but the key to the success of the LM134 is that initial errors are gain errors which are trimmed to zero when the external resistor is adjusted. Independent of initial current, if the current is adjusted to 298  $\mu\text{A}$  at  $T = 25^\circ\text{C}$  (298 $^\circ\text{K}$ ), all devices will have a current dependence of  $1 \pm 0.01 \mu\text{A}/^\circ\text{C}$ .

A voltage reference can be made by combining the positive temperature coefficient of the LM134 with the negative TC of a forward-biased diode. The IC terminology for such a reference is "bandgap reference" because the total voltage of the reference is equal to the extrapolated (0 $^\circ\text{K}$ ) bandgap voltage of silicon. An important characteristic of bandgap references is that the zero TC voltage is independent of diode current even though the diode voltage and TC are not. This means that by adjusting the total voltage of the reference to a fixed value, T.C. will be adjusted to near zero at the same time. The zero TC voltage for most bandgap references falls between 1.20V and 1.28V.

The circuit in *Figure 1* is a micropower reference using the LM134 and an MPSA43 transistor connected as a

diode with collector-base shorted. A transistor is used in place of a diode because the transistor characteristics as a double-diffused structure are more consistent than a diode. In particular, the emitter-based voltage drift of wide-base high-voltage transistors connected as diodes is very linear with temperature.

In *Figure 1*, the LM134 controls the voltage between its R and  $V^-$  terminals to  $\approx 64 \text{ mV}$ . About 5.5% of the current out of the R terminal flows out of the  $V^-$  terminal. The total current flowing through R2 is then determined by  $67.7 \text{ mV}/R1$ . Output voltage is the sum of the diode voltage, plus the voltage across R2, plus 64 mV. The voltage TC across R2 and the 64 mV is positive and directly proportional to absolute temperature while the diode TC is negative. The overall TC of the output will be near zero ( $< 50 \text{ ppm}/^\circ\text{C}$ ) when the output is adjusted to 1.253V by trimming R2. To obtain this level of performance, R1 and R2 must track well over temperature. 1% metal film resistors are suggested.

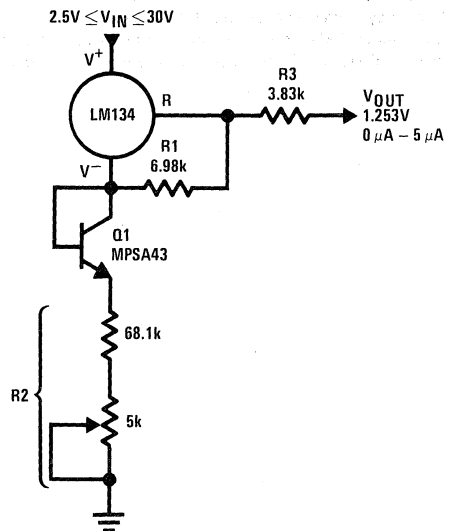


FIGURE 1

For optimum results with a single point adjustment of voltage and temperature coefficient, an additional error term must be accounted for. Internal to the LM134 are low  $I_{dss}$  FETs used for starting the control loop. This FET current adds directly to the  $V^-$  pin current and therefore creates an additional output voltage equal to  $(I_{dss})(R2)$ . Typical  $I_{dss}$  is 200 nA, causing  $V_{OUT}$  to be 14 mV high. Temperature coefficient of  $I_{dss}$  is low, typically 0.1%/°C. For best results in a single point adjustment,  $V_{OUT}$  should be adjusted to  $1.253V + I_{dss}(R2)$ .  $I_{dss}$  can be easily measured by open circuiting R1 and measuring the drop across R2. The resulting voltage must be divided by 2 due to an internal action which causes 2  $I_{dss}$  to flow when no current flows from the R pin. Example: with R1 open, 32 mV is measured across R2. Set  $V_{OUT}$  equal to  $1.253V + 32\text{ mV}/2 = 1.269V$ . Even lower TC can be obtained by measuring the output at 2 temperatures and using the following formula to calculate the exact zero TC output voltage for each reference.

$$V_{OUT} (0\text{ TC}) = V1 - \frac{T1(V2 - V1)}{T2 - T1}$$

Where:

V1 = Output voltage at T1  
 V2 = Output voltage at T2  
 T = Absolute temperature (°K)

The limitation on temperature drift after a 2 point calibration is non-linearity. This reference circuit has a non-reducible bow error of  $\approx 10\text{ ppm}/^\circ\text{C}$  over a temperature range of  $-25^\circ\text{C}$  to  $+100^\circ\text{C}$  and  $\approx 5\text{ ppm}/^\circ\text{C}$  from  $0^\circ\text{C}$  to  $+70^\circ\text{C}$ . At  $125^\circ\text{C}$ , leakage creates significant error, causing the output voltage to droop about 5 mV.

Noise of the reference consists primarily of theoretical shot noise current from the LM134. At the  $10\text{ }\mu\text{A}$  level, this is about  $6\text{ pA}/\sqrt{\text{Hz}}$  rms from 10 Hz to 10 kHz. Total output noise would be  $0.4\text{ }\mu\text{V}/\sqrt{\text{Hz}}$  rms over this frequency range, except that C1 bypasses most of the noise above 2 kHz. Measured output noise was  $25\text{ }\mu\text{V}$  rms over a 10 Hz to 10 kHz bandwidth with C1 = 1000 pF.

Larger values of C1 may be used if lower broadband noise is needed. Low frequency noise is about  $25\text{ }\mu\text{V}$  peak-to-peak from 0.1 Hz to 10 Hz.

The LM134 has a negative output resistance at the R pin when resistance is inserted in series with the  $V^-$  pin. The value of this negative resistance is approximately  $-R_x/19$ , where  $R_x$  is the equivalent resistance from  $V^-$  to ground. In this reference circuit  $R_x$  is 72 k $\Omega$ , yielding a negative output resistance of 3.8 k $\Omega$ . Resistor R2 sums with this resistance to give the reference a net zero output resistance ( $\pm 400\Omega$ ). Loading should be limited to about 5  $\mu\text{A}$ . Line regulation for the reference is typically less than 0.5 mV with an input voltage of  $5V \pm 2V$ . Minimum input voltage for a 2 mV drop in output voltage is 2.5V at  $-55^\circ\text{C}$ , 2.4V at  $25^\circ\text{C}$  and 2.3V at  $125^\circ\text{C}$ .

Although this reference was designed for ultra-low operating current, there is no reason that it cannot be used at higher current levels as well. All resistor values are simply scaled downward. Higher operating current will give lower output resistance, more drive capability, less sensitivity to FET  $I_{dss}$ , lower noise, and less droop at  $125^\circ\text{C}$ .

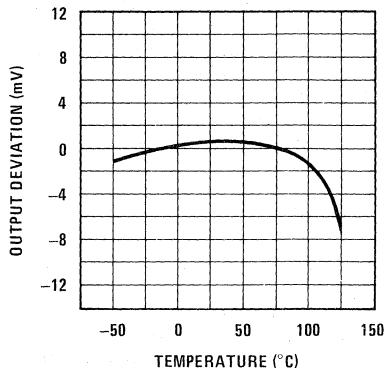


FIGURE 2. Output Voltage Drift

# Get Fast Stable Response From Improved Unity-Gain Followers

National Semiconductor  
Linear Brief 42  
Robert A. Pease  
August 1978



LB-42 Get Fast Stable Response From Improved Unity-Gain Followers

In many applications, a unity-gain follower (e.g. any operational amplifier with tight feedback to the inverting input) may oscillate or exhibit bad ringing when required to drive heavy load capacitance. For example, the LM110 follower will normally drive a 50 pF load capacitor, but will not drive 500 pF, because the open-loop output impedance is lagged by such a large capacitive load. The frequency at which this lag occurs is comparable to the gain-bandwidth product of the amplifier, and when the phase margin is decreased to zero, oscillation occurs.

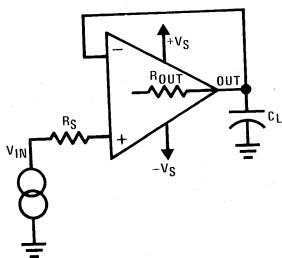


FIGURE 1. Unity-Gain Follower Attempting to Drive Capacitive Load

While the solution to this problem is not widely known, an analysis of the general problem shown in Figure 2 can lead to a useful approach. It is generally known that increasing the noise gain of an op amp's feedback network will improve tolerance of capacitive load. In Figure 2, adding a resistor  $R_2 \cong R_F/10$  will do this. (A moderate capacitor  $C_2$  is usually inserted in series with  $R_2$ , to prevent the DC noise gain from increasing also—to avoid degrading DC offset, drift and inaccuracy.) If the op amp has a 1 MHz gain bandwidth product, and  $R_1 = R_F$ , the closed-loop frequency response will be 1/2 MHz. Adding  $R_2 = R_F/10$  will drop the closed-loop frequency response to 90 kHz, where the amplifier can usually tolerate a much larger  $C_L$ :

$$\text{Noise Gain} = \frac{R_F}{R_1} + \frac{R_F}{R_2} + 1 \text{ (AC)}$$

$$\text{Noise Gain} = \frac{R_F}{R_1} + 1 \text{ (DC)}$$

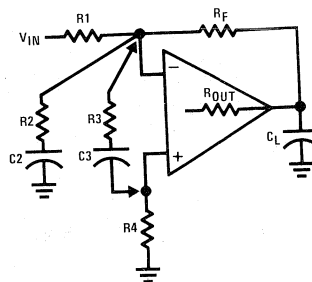


FIGURE 2. Stabilizing an Operational Amplifier for Capacitive Load

A similar result will occur if you install  $R_3$  and  $C_3$ , instead of  $R_2$ . Now the (AC) noise gain will be:

$$1 + \frac{R_4}{R_3} + \frac{R_F}{R_3} + \left( \frac{R_F}{R_1} \right) \left( \frac{R_3 + R_4}{R_3} \right)$$

As a simplification, if  $R_1$  is an open circuit, the AC noise gain will be:  $(R_4/R_3 + R_F/R_3 + 1)$ . Now it can be seen that noise gain can be raised by having a low value of  $R_3$  and a high value of  $R_4$  or  $R_F$  (or both).

In particular, where  $R_F$  is required to be  $0\Omega$ , as in a follower, the noise gain can be raised by adding a large  $R_4$  and a small  $R_5$ , as shown in Figure 3. If  $R_S$  is low, the AC noise gain will be  $R_4/R_5 + 1$ . (If  $R_S$  is large and constant,  $R_4$  may be unnecessary, and the noise gain would then be  $R_S/R_5 + 1$ .) For LM110/LM310's  $R_4 = 10 \text{ k}\Omega$  is recommended and when  $R_5 = 3.3 \text{ k}\Omega$ ,  $C_5 = 200 \text{ pF}$ , the LM110 will stably drive  $C_L$  up to 600 pF.

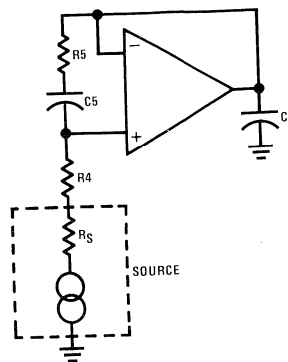


FIGURE 3. Stabilizing a Unity-Gain Follower for Capacitive Load

Another application of this technique is for making a fast follower with a high slew rate. An LF356 is specified as a follower, but an LF357 must be applied at an " $A_v = 5$ " minimum, because it has been "decompensated" with a smaller internal capacitor. Most people do not realize how easy it is to apply an LF357 as a follower. In *Figure 4*, an LF357 will have fast, stable response just like an LF356 does, when  $R_S$  is  $< 1 \text{ k}\Omega$ , but it will have a  $50\text{V}/\mu\text{s}$  slew rate (typical) vs.  $12\text{V}/\mu\text{s}$  for an LF356.

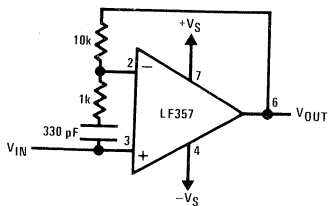


FIGURE 4. Unity-Gain Follower With Fast Slew Rate

Similarly, an LM349 is a fast decompensated quad op amp. Its bipolar input stage has a finite bias current, 200 nA max. For best results, the resistance which makes up the noise gain should be put equally in the **plus** and **minus** input circuits, as shown in *Figure 5*. The LM349 can slew at  $2\text{V}/\mu\text{s}$  typical, and is much faster for handling audio signals without distortion than the LM348 (which at  $0.5\text{V}/\mu\text{s}$  is only as fast as an ordinary LM741). The same approach can be used for an LM101 with a  $5 \text{ pF}$  damping capacitor. While these circuits give faster slewing, the bandwidth may degrade if the source impedance  $R_S$  increases. Also, when the AC noise gain is raised, the AC noise will also be increased. While most modern op amps have low noise, a noise gain of 10 may make a significant increase in output

noise, which the user should check to insure it is not objectionable.

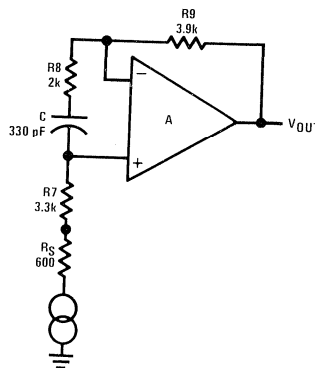


FIGURE 5. Application of Fast Follower With Balanced Resistors,  $R_9 = R_7 + R_S$ ,  $A = 1/4$  LM349 (or LM101 With  $5 \text{ pF}$  Capacitor)

If the series capacitor is much larger than necessary, noise will be increased more than necessary. In general, choose the  $C_5$  for *Figure 3*, (e.g.) per these guidelines: (where  $f_V$  = unity-gain bandwidth of op amp)

$$C_5 \text{ Min} = \frac{4 \cdot \left(1 + \frac{R_4}{R_5}\right)}{2\pi R_5 \cdot f_V} = \frac{R_4 + R_5}{\frac{\pi}{2} \cdot f_V \cdot (R_5)^2}$$

For best results, choose the design center value of  $C_5$  to be 2 or 3 times  $C_5 \text{ min}$ .


# Get More Power Out of Dual or Quad Op-Amps

National Semiconductor  
Linear Brief 44  
Bob Pease  
April 1979



Although simple brute-force paralleling of op-amps is a bad scheme for driving heavy loads, here is a good scheme for dual op-amps. It is fairly efficient, and will not overheat if the load is disconnected. It is *not* useful for driving active loads or nonlinear loads, however.

In *Figure 1*, an LF353N mini-DIP can drive a 600  $\Omega$  load to  $\pm 9V$  typical ( $\pm 6V$  min guaranteed) and will have only a 47°C temperature rise above free air. If the load R is removed, the chip temperature will rise to +50°C above free air. Note that A2's task is to drive half of the load. A1 could be applied as a unity-gain follower or inverter, or as a high-gain or low-gain amplifier, integrator, etc.

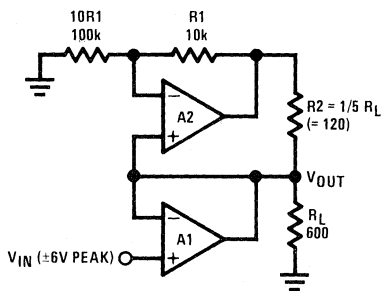

A1, A2 = 1/2 LM747 or 1/2 LF353 or any op-amp.

FIGURE 1. A1 and A2 Share the Load.

While *Figure 1* is suitable for sharing a load between 2 amplifiers, it is not suitable for 4 or more amplifiers, because the circuit would tend to go out of control and overheat if the load is disconnected.

Instead, *Figure 2* is generally recommended, as it is capable of driving large output currents into resistive, reactive, nonlinear, passive, or active loads. It is easily expandable to use as many as 2 or 4 or 8 or 20 or more op-amps, for driving heavier loads.

It operates, of course, on the principle that every op-amp has to put out the same current as A1, whether that current is plus, minus, or zero. Thus if the load is removed, all amplifiers will be unloaded together. A quad op-amp can drive 600  $\Omega$  to  $\pm 11$  or 12 volts. Two quads can put out  $\pm 40$  mA, but they get only a little warm. A series R-C damper of 15  $\Omega$  in series with 0.047  $\mu F$  is useful to prevent oscillations (although LM324's do not seem to need any R-C damper).

Of course, there is no requirement for the main amplifier to run only as a unity-gain amplifier. In the example shown in *Figure 3*, A1 amplifies a signal with a gain of +10. A2 helps it drive the load. Then A3 operates as a unity-gain inverter to provide  $V_2 = -V_1$ , and A4 helps it drive the load. This circuit can drive a floating 2000  $\Omega$  load to  $\pm 20V$ , accurately, using a slow LM324 or a quick LF347.

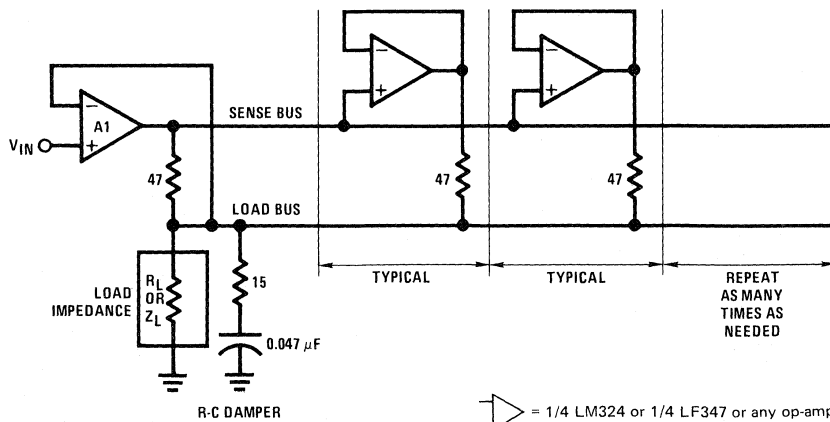


FIGURE 2. Improved Load-Sharing Circuit

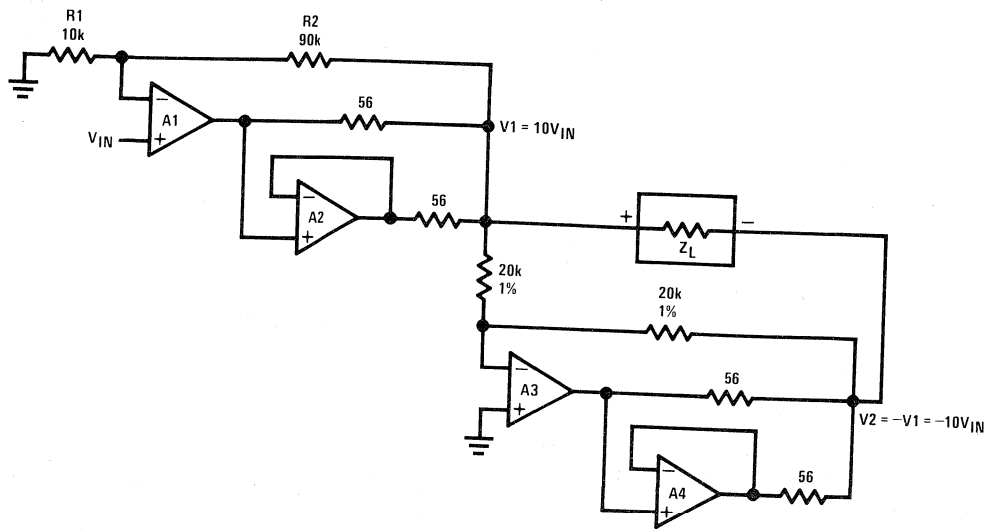


FIGURE 3. Typical Application of Load-Sharing

# Frequency-to-Voltage Converter uses Sample-and-Hold to Improve Response and Ripple

National Semiconductor  
 Linear Brief 45  
 Fran Terry  
 April 1979



Most frequency-to-voltage (F-to-V) converters suffer from the classical tradeoff of ripple versus speed of response. For example, the basic F-to-V converter shown below has 13 mVp-p of ripple, and a rather slow 0.6 second settling time, when C<sub>FILTER</sub> is 1 μF. If you want less ripple than that, the response time will be even slower. If you want quicker response, it is easy to decrease C<sub>FILTER</sub>, but the ripple will increase by the same factor.

such as LF398 can sample the F-to-V's output at the peak of its ripple, and hold it until the next cycle. The LF398 has fairly low output ripple (rms) but it does have some short duration noise spikes and glitches which can be removed easily with a simple output filter. The ripple at the output of the active filter V6 is smaller than 1 mV peak, but the settling time for a step change of input frequency is only 60 ms, or ten times quicker than the "basic" FVC with C<sub>FILTER</sub> = 1 μF.

The improved circuit in Figure 2 makes an end-run around these compromises. A low-cost sample-and-hold circuit

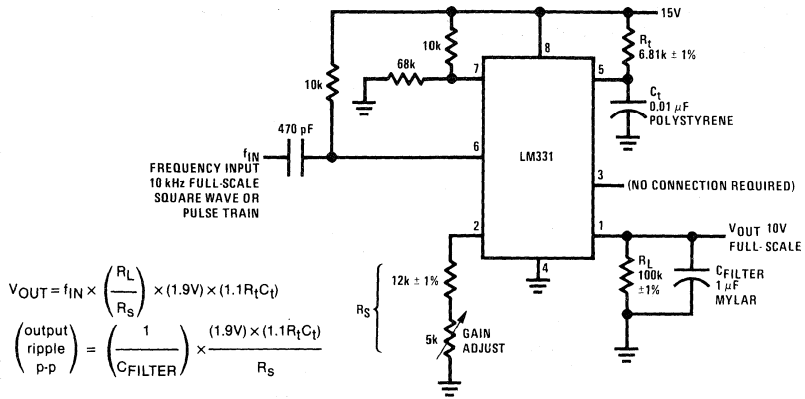


FIGURE 1. Basic Frequency-to-Voltage Converter

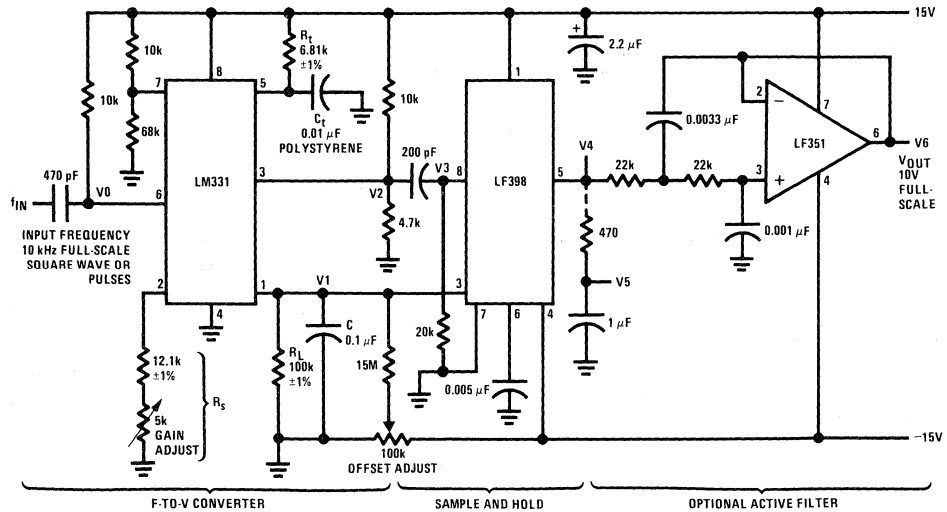


FIGURE 2. Improved F-to-V Converter Using Sample and Hold

### Details of Operation (Refer to Figure 3, Waveforms)

When the input frequency waveform has a negative-going transition, pin 6 of the LM331 is driven momentarily lower than the 13V threshold voltage at pin 7. This initiates a timing cycle controlled by the  $R_t$  and  $C_t$  at pin 5, and also causes a transition from +5V to 0V at pin 3, (the normal VFC logic output) which is usually left unused in F-to-V operation.

During the timing cycle ( $t = 1.1 \times R_t \times C_t = 75 \mu\text{s}$ , for the example shown) a precision current source  $i = 1.9\text{V}/R_s$  flows out of pin 1 of the LM331, and charges V1 up to a value slightly higher than the average DC value of V1. At the end of the timing cycle, V1 stops charging up, and also V2 rises. The 10 K $\Omega$  pull-up resistor is coupled (through the 200 pF capacitor) to V3, and causes the LF398 to *sample* for about 5  $\mu\text{s}$ . Then the LF398 goes back into *hold*. This entire operation is repeated at the same frequency as  $f_{IN}$ . The average voltage at V1 will be the same 10V full scale, according to the same formula as Figure 1. And the peak-to-peak ripple can be computed as 65 mV peak, 130 mVp-p, using the appropriate formula.

Now, the input to the sample and hold at pin 3 may have a 10.000V average DC value, but the output will be at 10.065V, because the sample occurs at the peak value of V1. Thus, to get an output with low offset, a 15 M $\Omega$  resistor is used to offset the V1 signal to a lower level. Trim the offset adjust pot to get  $V_{OUT} = 1\text{V}$  at 1 kHz, and trim the gain adjust pot to get  $V_{OUT} = 10\text{V}$  at 10 kHz (the interaction is minor), as measured at V4, V5, or V6. The rms value of the ripple at V4 is rather small, but the peak-to-peak ripple (spikes and glitches) may be excessive. A simple R-C filter can provide a filtered output at V5; or a simple active filter using an inexpensive LF351, will give submillivolt (peak) ripple at V6, with improved settling time and low output impedance.

This F-to-V converter will have a good linearity, better than 0.1%, but only from 10 kHz down to 500 Hz. Between 200 Hz and 20 Hz,  $V_{OUT}$  is not very proportional to  $f_{IN}$ . And at 0 Hz, the output will be indeterminate, because the sample and hold will never sample! However, there are many F-to-V applications where a 20:1 frequency range is adequate.

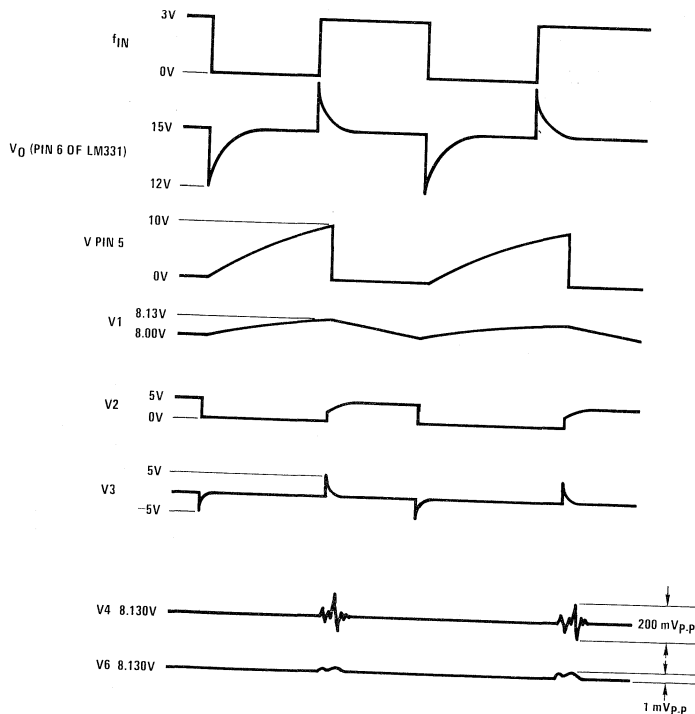


FIGURE 3. Waveforms, Improved F-to-V Converter



# A New Production Technique for Trimming Voltage Regulators

National Semiconductor  
 Linear Brief 46  
 Robert A. Pease  
 July 1979



LB-46 A New Production Technique for Trimming Voltage Regulators

Three-terminal adjustable voltage regulators such as the LM317 and LM337 are becoming popular for making regulated supplies in instruments and various other OEM applications. Because the regulated output voltage is easily programmed by two resistors, the designer can choose any voltage in a wide range such as 1.2V to 37V. In a typical example (Figure 1) the output voltage will be:

$$V_{OUT} = V_{REF} \left( \frac{R_2}{R_1} + 1 \right) + R_2 \cdot I_{ADJ}$$

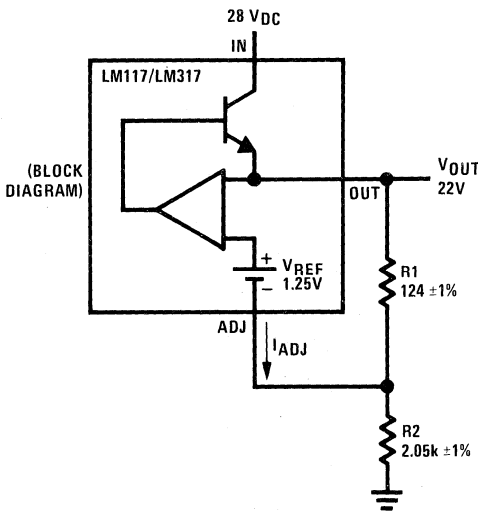


FIGURE 1. Basic Regulator

In many applications, when R1 and R2 are inexpensive  $\pm 1\%$  film resistors, and the room temperature accuracy of the LM117 is better than  $\pm 3\%$ , the overall accuracy of  $\pm 5\%$  will be acceptable. In other cases, a tighter tolerance such as  $\pm 1\%$  is required. Then a standard technique is to make up part of R2 with a small trim pot, as in Figure 2. The effective range of R2 is  $2.07k \pm 10\%$ , which is adequate to bring  $V_{OUT}$  to exactly 22.0V. (Note that a  $200\Omega$  rheostat in series with  $1.96k\Omega \pm 1\%$  would not necessarily give a  $\pm 5\%$  trim range, because the end resistance and wiper resistance could be as high as  $10\Omega$  or  $20\Omega$ ; and the maximum value of an inexpensive 10% or 20% tolerance trimmer might be as low as  $180\Omega$  or  $160\Omega$ .)

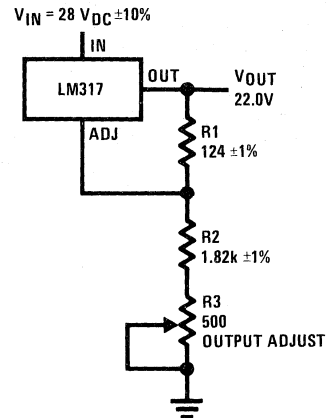


FIGURE 2. Regulator with Small Adjustment Range

In some designs, the engineering policy may frown on the use of such trim pots, for one or more of the following reasons:

- Good trim pots are more expensive.
- Inexpensive trim pots may be drift or unreliable.
- Any trim pot which can be adjusted can be *misadjusted*, sooner or later.

To get a tighter accuracy on a regulated supply, while avoiding these disadvantages of trim pots, consider the scheme in Figure 3.

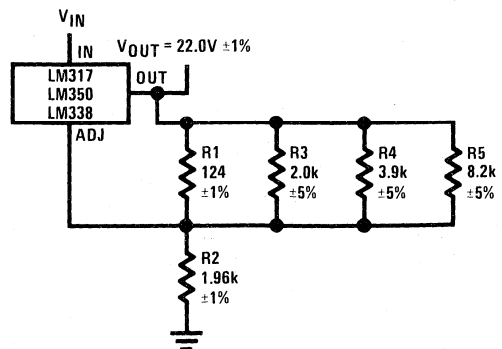


FIGURE 3. Regulator with Trimmable Output Voltage

When first tested,  $V_{OUT}$  will tend to be 4% to 6% higher than the 22.0V target. Then, while monitoring  $V_{OUT}$ , snip out R3, R4, and/or R5 as appropriate to bring  $V_{OUT}$  closer to 22.0V. This procedure will bring the tolerance inside  $\pm 1\%$ :

- If  $V_{OUT}$  is 23.08V or higher, cut out R3 (if lower, don't cut it out).
- Then if  $V_{OUT}$  is 22.47V or higher, cut out R4 (if lower, don't).
- Then if  $V_{OUT}$  is 22.16V or higher, cut out R5 (if lower, don't).

The entire production distribution will be brought inside 22.0V  $\pm 1\%$ , with a cost of 3 inexpensive carbon resistors, much lower than the cost of any pot. After the circuit is properly trimmed, it is relatively immune to being misadjusted by a screwdriver. Of course, the resistors' carcasses must be properly removed and disposed of, for full reliability to be maintained.


An alternate scheme shown in Figure 4 has R6, R7, and R8 all shorted out initially with a stitch or jumper of wire. The trim procedure is to open up a link to bring a resistor into effect. The advantage of this circuit is that  $V_{OUT}$  starts out lower than the target value, and never exceeds that voltage during trimming. In this scheme, note that a total "pot resistance" of 215 $\Omega$  is plenty for a 10% trim span, because the *minimum* resistance is always below

1 $\Omega$ , and the maximum resistance is always more than 200 $\Omega$ —it can cover a much wider range than a 200 $\Omega$  pot.

The circuit of Figure 5 shows a combination of these trims which provides a new advantage, if a  $\pm 2\%$  max tolerance is adequate. You may snip out R4, or link L1, or both, to accommodate the worst case tolerance, but in most cases, the output will be within spec without doing any trim work at all. This takes advantage of the fact that most  $\pm 1\%$  resistors are well within  $\pm \frac{1}{3}\%$ , and most LM337's output voltage tolerances are between  $-\frac{1}{2}\%$  and  $+1\frac{1}{2}\%$ , to cut the average trim labor to a minimum. Note that L1 could be made up of a 2.7 $\Omega$   $\pm 10\%$  resistor which may be easier to handle than a piece of wire.


In theory, a 10% total tolerance can be reduced by a factor of  $(2^n - 1)$  when  $n$  binary-weighted trims are used. In practice, the factor would be  $(1.8^n - 1)$  if  $\pm 10\%$  trim resistors are used, or  $(1.9^n - 1)$  if  $\pm 5\%$  resistors are used. For  $n=2$ , a 10% tolerance can be cut to 3.8% p-p or  $\pm 1.9\%$ . For  $n=3$ , the spread will be 1.7% p-p or  $\pm 0.85\%$ , and most units will be inside  $\pm 0.5\%$ , perfectly adequate for many regulator applications.

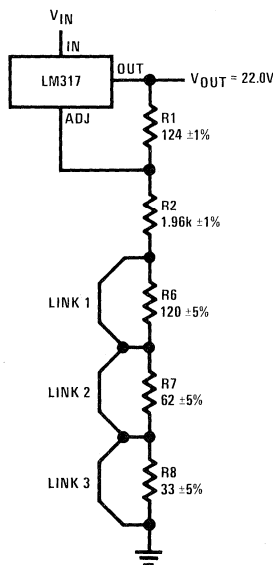National Semiconductor manufactures several families of adjustable regulators including LM117, LM150, LM138, LM117HV, LM137, and LM137HV, with output capabilities from 0.5A to 5A and from 1.2V to 57V. For complete specifications and characteristics, refer to the appropriate data sheet or the 1978 Linear Databook.



If  $V_{OUT}$  is lower than 20.90V, snip link 1 (if not, don't).  
 Then if  $V_{OUT}$  is lower than 21.55V, snip link 2 (if not, don't).  
 Then if  $V_{OUT}$  is lower than 21.82V, snip link 3 (if not, don't).

FIGURE 4. Alternate Trim Scheme

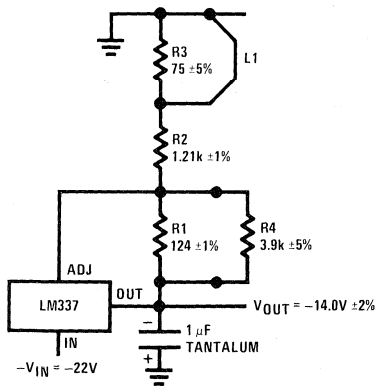

If  $|V_{OUT}|$  is smaller than 13.75V, snip L1 and it will get bigger by 6%.  
 Then if  $|V_{OUT}|$  is bigger than 14.20V, snip R4 and it will get smaller by 3%.

FIGURE 5. Circuit Which Usually Needs No Trim to Get  $V_{OUT}$  Within  $\pm 2\%$  Tolerance

# High Voltage Adjustable Power Supplies

National Semiconductor  
 Linear Brief 47  
 Michael Maida  
 March 1980



The floating-mode operation of adjustable three-terminal regulators such as the LM117 family make them ideal for high voltage operation. The regulator has no ground pin; instead, all the quiescent current (about 5 mA) flows to the output terminal. Since the regulator sees only the input-output differential, its voltage rating — 40V for the standard LM117 series and 60V for the high voltage LM117HV series — will not be exceeded for outputs of hundreds of volts. However, the IC may break down when the output is shorted unless special design approaches are used to protect against it.

Figure 1 shows how it's done. Zener diode D1 ensures that the LM317H sees only a 5V input-output differential over the entire range of output voltage from 1.2V to 160V. Since high-voltage transistors by necessity have a low  $\beta$ ,

a Darlington is used to stand off the high voltage. The zener impedance is low enough that no bypass capacitor is required directly at the LM317 input. (In fact, no capacitor should be used here if the circuit is to survive an output short!) R3 limits short circuit current to 50 mA. The RC network on the output improves transient response as does bypassing the ADJUST pin, while R4 and D2 protect the ADJUST pin during shorts.

Since Q2 may dissipate up to 5W normally or 10W during a short circuit, it should be well heat sunk. For higher output currents substitute a pass device in a TO-3 or TO-220 package in place of the TO-202 NSD134 and reduce R3. Of course, if the required output current is less than 25 mA, R3 can be increased to reduce the size of the heat sink needed.

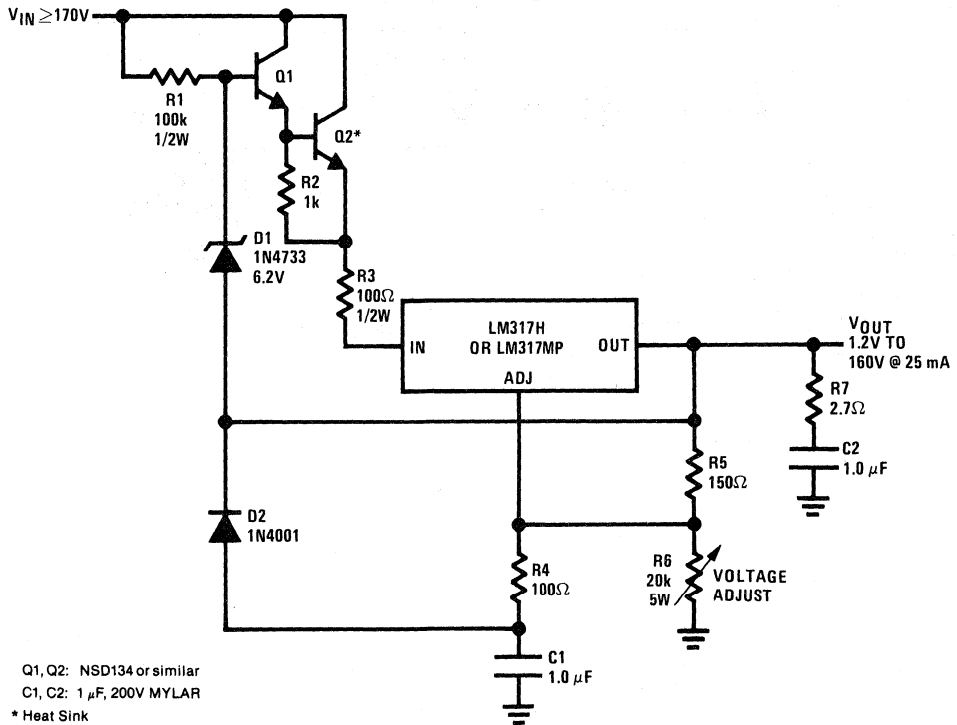


FIGURE 1. Basic High Voltage Regulator

An improved approach is shown in *Figure 2*. Here an LM329B 6.9V zener reference has been stacked in series with the LM317's internal reference. This both improves temperature stability, since the LM329B has a guaranteed TC of  $\pm 20$  ppm/ $^{\circ}\text{C}$ , and improves regulation, because more loop gain is available from the LM317.

These techniques can be extended for higher output voltages and/or currents by either using better high voltage transistors or cascoding or paralleling (with appropriate emitter ballasting resistors) several transistors. The output short circuit current, determined by R3, must be within Q2's safe area of operation so that secondary breakdown cannot occur.

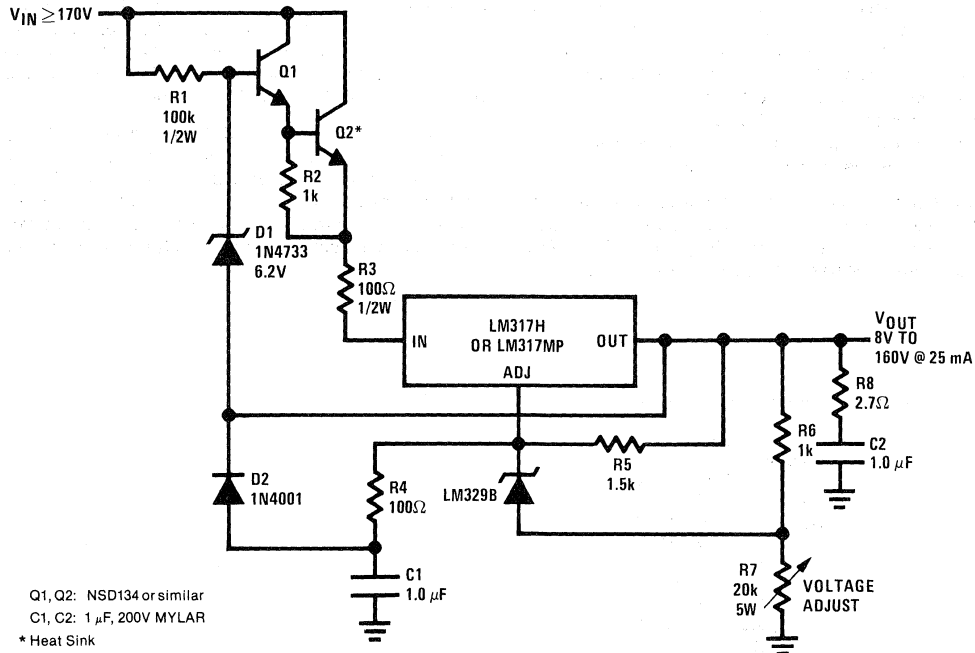


FIGURE 2. Precision High Voltage Regulator

# Simple Voltmeter Monitors TTL Supplies

National Semiconductor  
Linear Brief 48  
Michael Maida  
February 1980



Using a National Semiconductor LM3914 bar/dot display driver chip, a few resistors and some LEDs, a simple expanded-scale voltmeter is easily constructed. Furthermore, it runs from the same single  $5V \pm 10\%$  supply it monitors and can provide TTL-compatible undervoltage and overvoltage warning signals.

The complete circuit is shown in Figure 1. Resistors R1 and R2 attenuate  $V_{CC}$  by a factor of three at the LM3914 signal input, ensuring proper biasing of the IC with  $V_{CC}$  as low as 4V. The IC's internal reference sets the voltage across the series combination of R3, R4 and R5 at 1.25V, establishing a reference load current of about 1 mA. This current is joined by the small, constant current from the reference adjust pin ( $75 \mu A$ , typ) and flows to ground through R6 and R7, developing a voltage drop. Adjusting R6 varies this voltage drop and, consequently, the voltage at pin 7, nominally  $1.803V (= 5.41V/3)$ .

Pin 7 is connected to the top of the LM3914's internal ten-step voltage divider (pin 6). The bottom of this divider (pin 4) is connected to the center tap of potentiometer R4. By varying the pot setting this voltage can be set to 1.47V ( $= 4.41V/3$ ) without significantly affecting the potential

at pin 7. The optional diode D1 protects against damaging the IC by connecting the leads backwards.

In operation, the LM3914's ten internal voltage comparators compare the signal input,  $V_{CC}/3$ , to the reference voltage on the divider, lighting each successive LED for every 100 mV increase in  $V_{CC}$  above 4.5V as shown. The LM3914 regulates the LED currents at 10 times the reference load current, here about 10 mA, so external current-limiting resistors are not required. With pin 9 left open circuit, the LM3914 functions in Dot mode (only one LED on at a time). If desired, a Bar mode display could be obtained by connecting pin 9 to  $V_{CC}$ , but the dot display seems more suitable in this application.

To calibrate, set  $V_{CC}$  at 5.41V and adjust R6 until LED #9 and LED #10 are equally illuminated. (A built-in overlap of about 1 mV ensures all LEDs won't go out at a threshold point.) There's no need to vary the system supply voltage to perform this adjustment. Instead, disconnect R1 from  $V_{CC}$  and connect it to an accurate reference. Then, at 4.5V, adjust R4 until LED #1 just barely turns on. There is a slight interaction caused by the finite resistance (10k, typ) of the LM3914's voltage divider, so that repeating the above procedure once is advised.

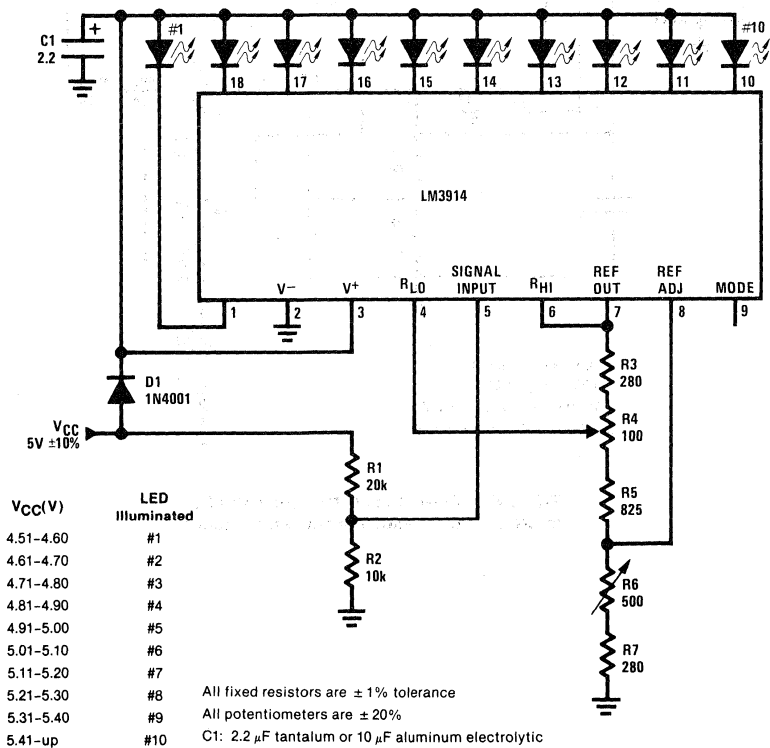


FIGURE 1: 5V Power Supply Monitor

The LED driver outputs can directly drive a TTL gate, so that the LED #1 and LED #10 outputs may be used for undervoltage and overvoltage warning signals. These may be used to initiate a soft shutdown or summon an operator, for example. The interfacing circuitry is shown in Figure 2. The 470Ω resistor R8 ensures that the LM3914 output will saturate to provide the proper TTL low level. Pull-up resistor R9 provides the logic high level.

In the previous circuit the undervoltage LED goes out when  $V_{CC}$  is less than 4.51V, a deficiency that is corrected here. Transistors Q1 and Q2 shut off LED #1 whenever any other LED is turned on by the LM3914. Q2's output will directly drive TTL.

Calibration procedure is the same as before. The LM3914 output thresholds have been shifted up by 100 mV and output #10 is or-tied with output #9. Other outputs may be wire-or'd together if 100 mV resolution is not necessary. If desired, the outputs can be color coded by making LED #1 and LED #10 red, LED #2 and LED #9 amber, and the rest of the LEDs green to ease interpretation.

This circuit is useful where quick and easy voltage adjustments must be made, such as in the field or on the production line. The circuit's low cost makes it feasible to incorporate it into the system, where the overvoltage and undervoltage warning signals provide an attractive extra. Of course, these techniques can be used to monitor any higher voltages, positive or negative.

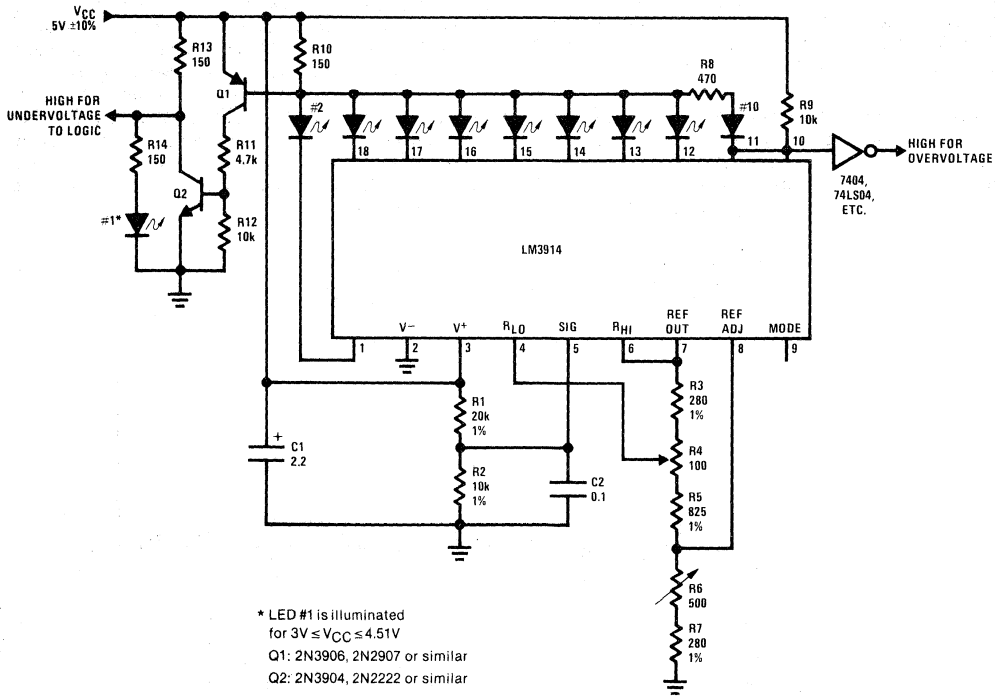


FIGURE 2. Power Supply Monitor with TTL Interface and Extended Undervoltage Range

# Programmable Power Regulators Help Check Out Computer System Operating Margins

National Semiconductor  
Linear Brief 49  
Robert A. Pease  
February 1980



It is a familiar situation that some computer systems which are functional with a 5.00V supply may run marginally at 5.10V but can show a solid failure at 5.3V (or, vice versa) even though all these voltages are within the system's specifications. The LM338 is an example of a monolithic voltage regulator which can be placed under computer control, and can trim the supply to a particular variation above (and below) the design-center voltage. Simultaneously the computer is exercised through a standard test sequence. Any deviation from correct functioning, at one supply voltage level or another, will serve as a warning of impending malfunction or failure. This test approach can be used for diagnostics, for troubleshooting, and for engineering evaluation. It can help detect skew, race conditions, timing problems, and noise and threshold problems.

## Here's How

During normal operation, the latch (IC 1) is programmed to have its Q1 and Q2 outputs HIGH, and its Q3 and Q4 LOW.

Then R4 and R5 are connected effectively in parallel with R6, and  $V_{OUT}$  is adjusted to 5.00V. If Q4 is commanded HIGH, the net conductance from the *adjust bus* to ground will decrease, and  $V_{OUT}$  will rise 3% to 5.151V. Conversely if Q1 is commanded LOW, the output voltage will fall 3.3% to 4.835V. The complete list of output voltages (in approximately 3.2% steps) is shown in Table I, covering a  $\pm 9.5\%$  total range.

The same basic function can be accomplished for  $-5.2V$  regulators (as are used for ECL) using LM337 negative adjustable regulators. If the command is from TTL latches, the circuit of Figure 2 will be suitable to interface between the (0V and 2.4V) logic levels and the saturated PNP collectors as shown. The resistors R101-R104 are switched by transistors Q101-Q104 in a similar way to Figure 1. Note that the resistors in Figure 2 are in a binary-weighted proportion. To decrease  $V_{OUT}$  by 2%, just change Q4 to LOW; but to increase  $V_{OUT}$  by 2%, set Q1 HIGH and Q2, Q3, Q4 all LOW, in a standard offset binary scheme.

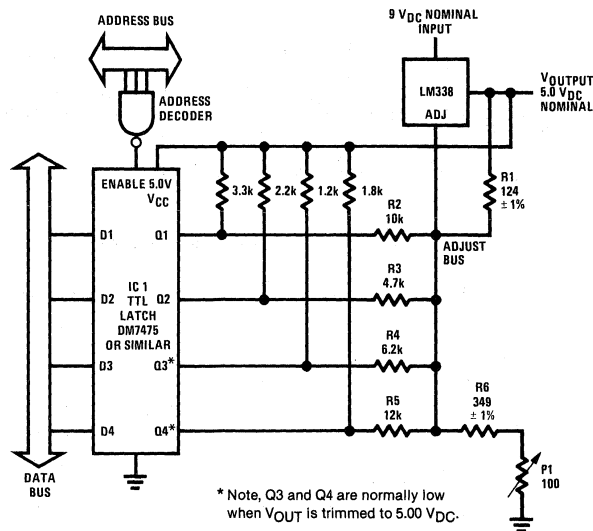


FIGURE 1. Programmable Power Supply

TABLE I. AVAILABLE TRIM RANGE

Q1	Q2	Q3	Q4	$V_{OUT}$	$\% \Delta V_{OUT}$
1	1	0	0	5.000V	(trimmed)
1	1	0	1	5.151V	+3.0%
1	1	1	0	5.299V	+6.0%
1	1	1	1	5.469V	+9.4%
0	1	0	0	4.835V	-3.3%
1	0	0	0	4.669V	-6.6%
0	0	0	0	4.526V	-9.5%

Figure 2 also provides another feature. If Q5 goes LOW, Q105 will saturate and pull the adjust bus to within 100 mV of ground, and the  $V_{OUT}$  will collapse to  $-1.35V$ . The negative supply will be effectively shut down, and the computer will draw substantially zero power.

In an extreme case of automation, the computer could trim the  $-5.2V$  supply to the "best" value, and the trimpot would be completely superfluous. The circuit of Figure 2 has a trim resolution of 3% steps, and can set  $V_{OUT}$  well within 2% of the ideal value, so long as some measurement has decided which voltage is "ideal".

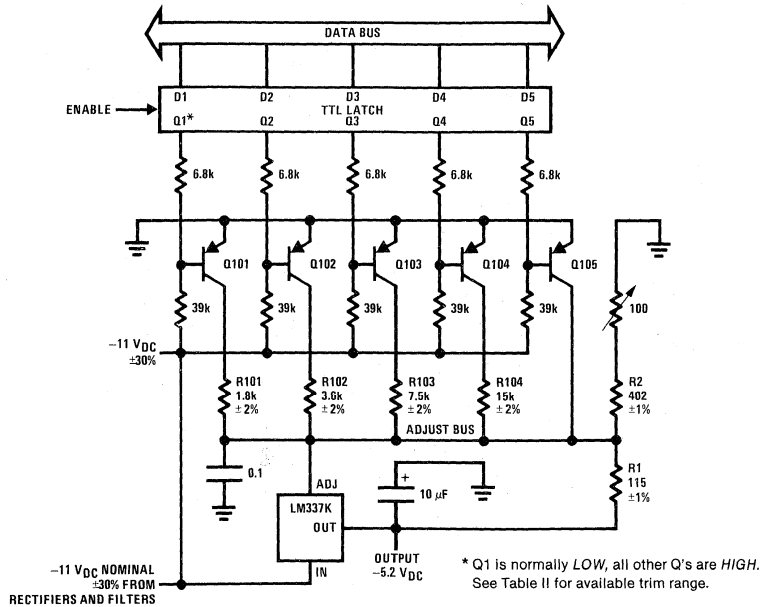


FIGURE 2. Programmable Negative Supply

TABLE II. AVAILABLE TRIM RANGE

Q1	Q2	Q3	Q4	$V_{OUT}$	$\% \Delta V_{OUT}$
0	1	1	1	5.200V	(trimmed)
0	1	1	0	5.110V	-1.7%
0	1	0	1	5.025V	-3.4%
0	1	0	0	4.944V	-4.9%
0	0	1	1	4.853V	-6.7%
0	0	1	0	4.779V	-8.1%
0	0	0	1	4.707V	-9.5%
0	0	0	0	4.638V	-10.8%
1	0	0	0	5.310V	+2.1%
1	0	0	1	5.409V	+4.0%
1	0	1	0	5.513V	+6.0%
1	0	1	1	5.622V	+8.1%
1	1	0	0	5.757V	+10.7%
1	1	0	1	5.880V	+13.1%
1	1	1	0	6.010V	+15.6%
1	1	1	1	6.147V	+18.2%



# Using the LM1524/LM3524 in Switching Servo Amplifier Applications

National Semiconductor  
Linear Brief 50  
Bruce J. Rogers  
June 1980



## ABSTRACT

The LM1524/LM3524 regulating pulse width modulator is a component designed to provide all the control circuitry necessary to implement switching regulators and DC-DC converters. This linear brief describes the application of this part in servo amplifiers.

## INTRODUCTION

Small AC and DC servo motors are used in a wide variety of applications. Typical of these are motors used in instrumentation such as X-Y plotters and chart recorders, positioning motors for numerical control of machine tools, and the 400 Hz servomotors used in a variety of military and commercial avionics equipment. Circuitry to drive these motors has usually been implemented as Class B linear amplifiers with large gains and large amounts of negative feedback to provide stability and minimize unit to unit variations. In AC applications the output stages are often powered with unfiltered DC to improve efficiency. Switching amplifiers have been used in applications where electrical efficiency was the prime design criterion and cost considerations were secondary as component counts are much higher. By using the LM3524 as the heart of a switching amplifier, efficiency is optimized while cost is held to a minimum.

## THEORY OF OPERATION

In a switching servo amplifier the output stages are run in a saturated switching mode instead of linearly. Therefore, the output devices are only dissipating a small amount of power. A high frequency linear ramp is compared with the input error signal in order to pulse width modulate the ON time of the output switching transistors. The net result is a high frequency rectangular waveform where the width of the individual pulses is modulated by the carrier. The output of the power switching stage is filtered to remove the high frequency components of the output signal. Therefore, the actual voltage appearing across the load is a faithful reproduction of the input signal.

## SYSTEM IMPLEMENTATION

In the principal system described in this brief a 400 Hz aircraft-type servomotor is driven.  $C_T$  and  $R_T$  are connected to the oscillator timing pins 6 and 7 to establish a switching rate around 100 kHz. A long period RC is used to integrate the ramp waveform and set the threshold of the control amplifier. This is connected to the non-inverting input, pin 2, and sets the quiescent duty cycle at 50%. The ratio of  $R_F$  to  $R_{IN}$  determines the system gain.  $C_{IN}$  decouples the DC component present on the input. Its value should be selected for a low impedance in comparison to  $R_{IN}$ . Various feedback and lag-lead compensation networks could be included around this control amplifier.

The output stage consists of four TO-92 + transistors connected as a complementary bridge switch. An additional PNP transistor is used to invert one of the outputs. The ground return of the output stage is through  $R_{SENSE}$ . This is connected to the negative input of the current limiter amplifier. A voltage derived from the internal reference regulator is connected to the positive input of the current limiter so that output current is limited to a safe value. As small AC servomotors are two phase motors, a series resonant capacitor C phase shift is connected to the variable phase input of the motor. Aside from providing 90° phase shift for the motor, this capacitor and winding reject the high frequency switching component of the amplifier.

## RESULTS

In tests run with a locked rotor on the servomotor, the motor provides rated output torque with no difficulty. The motor exhibits a rapid rise in temperature under these conditions, as might be expected. However, under these same conditions, the amplifier exhibits no appreciable temperature rise. No quantitative measurements of amplifier efficiency have been done at the time of writing. However, the lack of noticeable temperature rise on the TO-92+ output transistors is a good indication that efficiency is excellent. Various position servos have been implemented using synchros and potentiometers as control elements as well as a rate servo implemented with an AC tachometer generator. No noticeable differences were noted in comparison with more conventional linear circuits in implementing these designs.


## OTHER APPLICATIONS

A DC servo has been implemented using a low inertia ironless rotor servomotor such as those supplied by Microswitch or Hico-Maxon. A bifilar-wound choke was included to filter out the high frequency switching component in this application.


Some work has been done using a loudspeaker as a servo element in order to simulate voice coil servos such as those used in head positioning for disk drives. At the time of this writing I do not have a suitable position feedback element to fully explore these possibilities, however preliminary tests indicate this circuit makes a good 35W RMS audio amplifier with a suitable output filter.
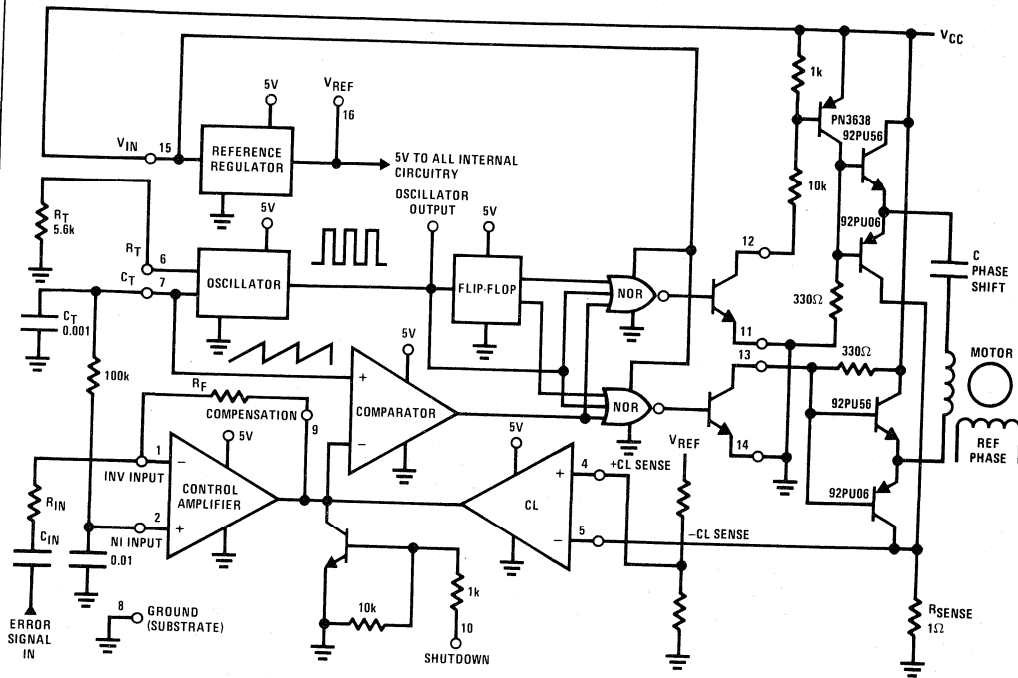
## CONCLUSION

It appears that the LM3524 is an optimum part to implement high efficiency servo amplifiers as well as the universal solution to the problem of controlling switching regulators.



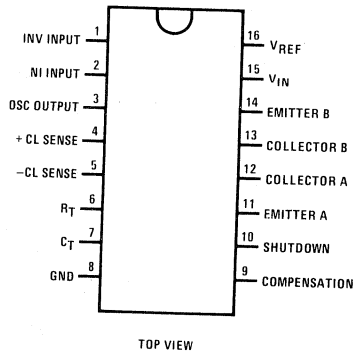**LM1524 Connection Diagram**  
Dual-In-Line Package



**Cavity Dual-In-Line Package (J)**  
Order Number LM1524J, LM2524J or LM3524J  
NS Package Number J16A

**Molded Dual-In-Line Package (N)**  
LM2524N or LM3524N  
NS Package Number N16A

# The Monolithic Operational Amplifier: A Tutorial Study

National Semiconductor  
Appendix A  
James E. Solomon  
December 1974



The Monolithic Operational Amplifier: A Tutorial Study

*Invited Paper—  
IEEE Journal of Solid-State Circuits, Vol. SC-9, No. 6*

**Abstract**—A study is made of the integrated circuit operational amplifier (IC op amp) to explain details of its behavior in a simplified and understandable manner. Included are analyses of thermal feedback effects on gain, basic relationships for bandwidth and slew rate, and a discussion of pole-splitting frequency compensation. Sources of second-order bandlimiting in the amplifier are also identified and some approaches to speed and bandwidth improvement are developed. Brief sections are included on new JFET-bipolar circuitry and die area reduction techniques using transconductance reduction.

## I. INTRODUCTION

THE integrated circuit operational amplifier (IC op amp) is the most widely used of all linear circuits in production today. Over one hundred million of the devices will be sold in 1974 alone, and production costs are falling low enough so that op amps find applications in virtually every analog area. Despite this wide usage, however, many of the basic performance characteristics of the op amp are poorly understood.

It is the intent of this study to develop an understanding for op amp behavior in as direct and intuitive a manner as possible. This is done by using a variety of simplified circuit models which can be analyzed in some cases by inspection, or in others by writing just a few equations. These simplified models are generally developed from the single representative op amp configuration shown in Figs. 1 and 2.

The rationale for starting with the particular circuit of Fig. 1 is based on the following: this circuit contains, in simplified form, all of the important elements of the most commonly used integrated op amps. It consists essentially of two voltage gain stages, an input differential amp and a common emitter second stage, followed by a class-AB output emitter follower which provides low impedance drive to the load. The two interstages are frequency compensated by a single small "pole-splitting" capacitor (see below) which is usually included on the op amp chip. In most respects this circuit is directly equivalent to the general purpose LM101 [1],  $\mu\text{A} 741$  [2], and the newer dual and quad op amps [3], so the results of our study relate directly to these devices. Even for more exotic designs, such as wide-band amps using feedforward [4], [5], or the new FET input circuits [6], the basic analysis approaches still apply, and performance details can be accurately predicted. It has also been found that a good understanding of the limita-

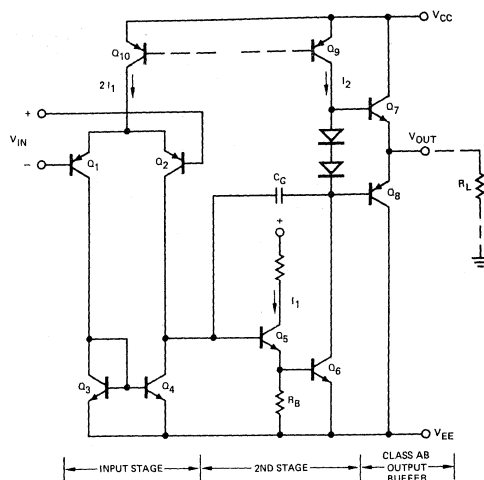


Fig. 1. Basic two-stage IC op amp used for study. Minimal modifications used in actual IC are shown in Fig. 2.


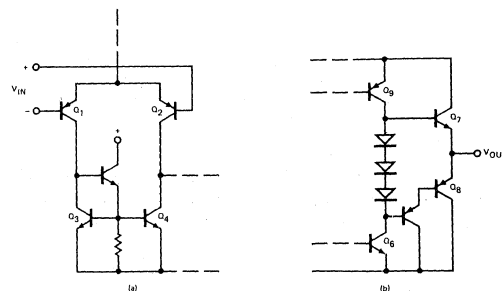


Fig. 2. (a) Modified current mirror used to reduce dc offset caused by base currents in  $Q_3$  and  $Q_4$  in Fig. 1. (b) Darlington p-n-p output stage needed to minimize gain fall-off when sinking large output currents. This is needed to offset the rapid  $\beta$  drop which occurs in IC p-n-p's.

tions of the circuit in Fig. 1 provides a reasonable starting point from which higher performance amplifiers can be developed.


The study begins in Section II, with an analysis of dc and low frequency gain. It is shown that the gain is typically limited by thermal feedback rather than elec-

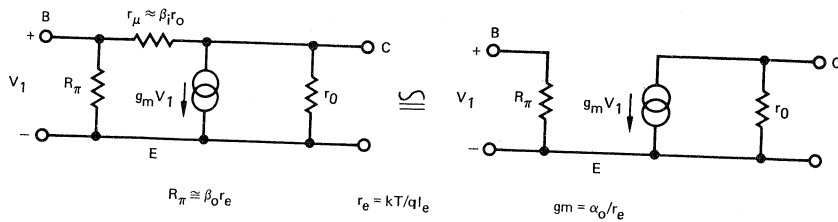Manuscript received July 1, 1974; revised August 8, 1974.  
The author is with the National Semiconductor Corporation, Santa Clara, Calif. 95051.



$r_o \cong 200/I_C$  MONOLITHIC NPN  
 $r_o \cong 80/I_C$  MONOLITHIC PNP

(a)

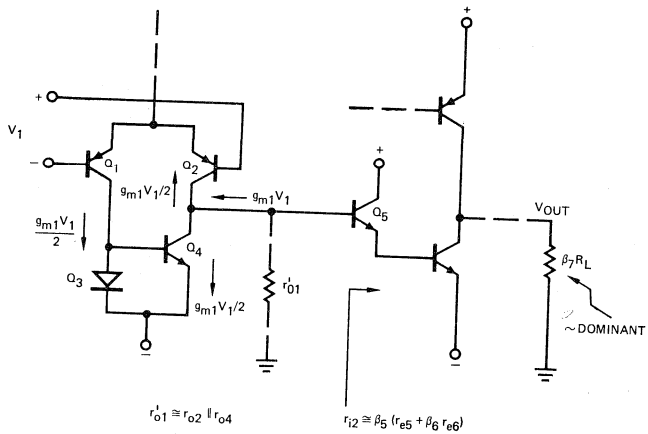

(b)

Fig. 3. (a) Approximate  $\pi$  model for CE transistor at dc. Feedback element  $r_{\mu} \cong \beta_f r_o$  is ignored since this greatly simplifies hand calculations. The error caused is usually less than 10 percent because  $\beta_f$ , the intrinsic  $\beta$  under the emitter, is quite large. Base resistance  $r_s$  is also ignored for simplicity. (b) Circuit illustrating calculation of electronic gain for op amp of Fig. 1. Consideration is given only to the fully loaded condition ( $R_L \cong 2 \text{ k}\Omega$ ) where  $\beta_7$  is falling (to about 50) due to high current density. Under this condition, the output resistance of  $Q_6$  and  $Q_9$  are nondominant.

trical characteristics. A highly simplified thermal analysis is made, resulting in a gain equation containing only the maximum output current of the op amp and a thermal feedback constant.

The next three sections apply first-order models to the calculation of small-signal high frequency and large-signal slewing characteristics. Results obtained include an accurate equation for gain-bandwidth product, a general expression for slew rate, some important relationships between slew rate and bandwidth, and a solution for voltage follower behavior in a slewing mode. Due to the simplicity of the results in these sections, they are very useful to designers in the development of new amplifier circuits.

Section VI applies more accurate models to the calculation of important second-order effects. An effort is made in this section to isolate all of the major contributors to bandlimiting in the modern amp.

In the final section, some techniques for reduction of op amp die size are considered. Transconductance reduction and layout techniques are discussed which lead to fabrication of an extremely compact op amp cell. An example yielding 8000 possible op amps per 3-in wafer is given.

## II. GAIN AT DC AND LOW FREQUENCIES

### A. The Electronic Gain

The electronic voltage gain will first be calculated at dc using the circuit of Fig. 1. This calculation becomes straightforward if we employ the simplified transistor model shown in Fig. 3(a). The resulting gain from Fig. 3(b) is

$$A_V(0) = \frac{v_{out}}{v_{in}} \cong \frac{g_m \beta_5 \beta_6 \beta_7 R_L}{1 + r_{i2}/r_{o1}} \quad (1)$$

where

$$r_{i2} \cong \beta_5(r_{e5} + \beta_6 r_{e6})$$

$$r_{o1}' \cong r_{o4}/r_{o2}.$$

It has been assumed that

$$\beta_7 R_L < r_{o6}/r_{o5}, g_{m1} = g_{m2}, \beta_7 = \beta_8.$$

The numerical subscripts relate parameters to transistor  $Q$  numbers (i.e.,  $r_{e5}$  is  $r_e$  of  $Q_5$ ,  $\beta_6$  is  $\beta_0$  of  $Q_6$ , etc.). It has also been assumed that the current mirror transistors  $Q_3$  and  $Q_4$  have  $\alpha$ 's of unity, and the usually small loading of  $R_B$  has been ignored. Despite the several assumptions made in obtaining this simple form for (1), its accuracy is quite adequate for our needs.

An examination of (1) confirms the way in which the amplifier operates: the input pair and current mirror convert the input voltage to a current  $g_{m1}v_{in}$  which drives the base of the second stage. Transistors  $Q_5$ ,  $Q_6$ , and  $Q_7$  simply multiply this current by  $\beta^3$  and supply it to the load  $R_L$ . The finite output resistance of the first stage causes some loss when compared with second stage input resistance, as indicated by the term  $1/(1 + r_{i2}/r_{o1}')$ . A numerical example will help our perspective: for the LM101A,  $I_1 \cong 10 \mu\text{A}$ ,  $I_2 \cong 300 \mu\text{A}$ ,  $\beta_5 = \beta_8 \cong 150$ , and  $\beta_7 \cong 50$ . From (1) and dc voltage gain with  $R_L = 2 \text{ k}\Omega$  is

$$A_V(0) \cong 625\,000. \quad (2)$$

The number predicted by (2) agrees well with that measured on a discrete breadboard of the LM101A, but is much higher than that observed on the integrated circuit. The reason for this is explained in the next section.

### B. Thermal Feedback Effects on Gain

The typical IC op amp is capable of delivering powers of 50–100 mW to a load. In the process of delivering this power, the output stage of the amp internally dissipates similar power levels, which causes the temperature of the IC chip to rise in proportion to the output dissipated power. The silicon chip and the package to which it is bonded are good thermal conductors, so the whole chip tends to rise to the same temperature as the output stage. Despite this, small temperature gradients from a few tenths to a few degrees centigrade develop across the chip with the output section being hotter than the rest. As illustrated in Fig. 4, these temperature gradients appear across the input components of the op amp and induce an input voltage which is proportional to the output dissipated power.

To a first order, it can be assumed that the temperature difference ( $T_2 - T_1$ ) across a pair of matched and closely spaced components is given simply by

$$(T_2 - T_1) \cong \pm K_T P_d \quad (3)$$

where

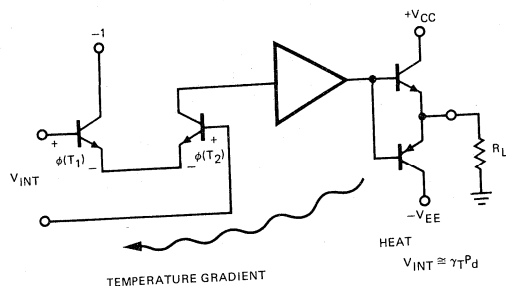


Fig. 4. Simple model illustrating thermal feedback in an IC op amp having a single dominant source of self-heat, the output stage. The constant  $\gamma_T \cong 0.6 \text{ mV/W}$  and  $P_d$  is power dissipated in the output. For simplicity, we ignore input drift due to uniform heating of the package. This effect can be significant if the input stage drift is not low, see [7].

$P_d$  power dissipated in the output circuit,  
 $K_T$  a constant with dimensions of  $^\circ\text{C/W}$ .

The plus/minus sign is needed because the direction of the thermal gradient is unknown. In fact, the sign may reverse polarity during the output swing as the dominant source of heat shifts from one transistor to another. If the dominant input components consist of the differential transistor pair of Fig. 4, the thermally induced input voltage  $V_{int}$  can be calculated as

$$V_{int} \cong \pm K_T P_d (2 \times 10^{-3}) \cong \pm \gamma_T P_d \quad (4)$$

where  $\gamma_T = K_T (2 \times 10^{-3}) \text{ V/W}$ , since the transistor emitter-base drops change about  $-2 \text{ mV}/^\circ\text{C}$ .

For a thermally well designed IC op amp, in which the power output devices are made to approximate either a point or a line source and the input components are placed on the resulting isothermal lines (see below and Fig. 8), typical values measured for  $K_T$  are

$$K_T \approx 0.3 \text{ }^\circ\text{C/W} \quad (5)$$

in a TO-5 package.

The dissipated power in the class-AB output stage  $P_d$  is written by inspection of Fig. 4:

$$P_d = \frac{V_o V_s - V_o^2}{R_L} \quad (6)$$

where

$$V_s = +V_{cc} \quad \text{when } V_o > 0$$

$$V_s = -V_{ee} \quad \text{when } V_o < 0.$$

A plot of (6) in Fig. 5 resembles the well-known class-AB dissipation characteristics, with zero dissipation occurring for  $V_o = 0$ ,  $+V_{cc}$ ,  $-V_{ee}$ . Dissipation peaks occur for  $V_o = +V_{cc}/2$  and  $-V_{ee}/2$ . Note also from (4) that the thermally induced input voltage  $V_{int}$  has this same double-humped shape since it is just equal to a constant times  $P_d$  at dc.

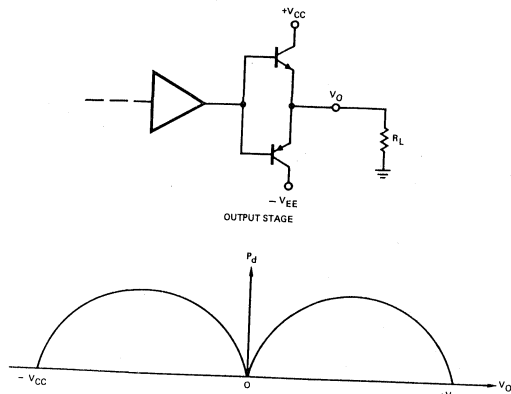


Fig. 5. Simple class-B output stage and plot of power dissipated in the stage,  $P_d$ , assuming device can swing to the power supplies. Equation (6) gives an expression for the plot.

Now examine Figs. 6(a) and (b) which are curves of open-loop  $V_o$  versus  $V_{in}$  for the IC op amp. Note first that the overall curve can be visualized to be made up of two components: a) a normal straight line electrical gain curve of the sort expected from (1) and b) a double-humped curve similar to that of Fig. 5. Further, note that the gain characteristic has either positive or negative slope depending on the value of output voltage. This means that the thermal feedback causes the open-loop gain of the feedback amplifier to change phase by  $180^\circ$ , apparently causing negative feedback to become positive feedback. If this is really true, the question arises: which input should be used as the inverting one for feedback? Further, is there any way to close the amplifier and be sure it will not find an unstable operating point and latch to one of the power supplies?

The answers to these questions can be found by studying a simple model of the op amp under closed-loop conditions, including the effects of thermal coupling. As shown in Fig. 7, the thermal coupling can be visualized as just an additional feedback path which acts in parallel with the normal electrical feedback. Noting that the electrical form of the thermal feedback factor is [see (4) and (6)]

$$\beta_T = \frac{\partial V_{int}}{\partial V_o} = \pm \frac{\gamma_T}{R_L} (V_s - 2V_o). \quad (7)$$

The closed-loop gain, including thermal feedback is

$$A_V(0) = \frac{\mu}{1 + \mu(\beta_e \pm \beta_T)} \quad (8)$$

where  $\mu$  is the open-loop gain in the absence of thermal feedback [(1)] and  $\beta_e$  is the applied electrical feedback as in Fig. 7. Inspection of (8) confirms that as long as there is sufficient electrical feedback to swamp the thermal feedback (i.e.,  $\beta_e > \beta_T$ ), the amplifier will behave as a normal closed-loop device with charac-

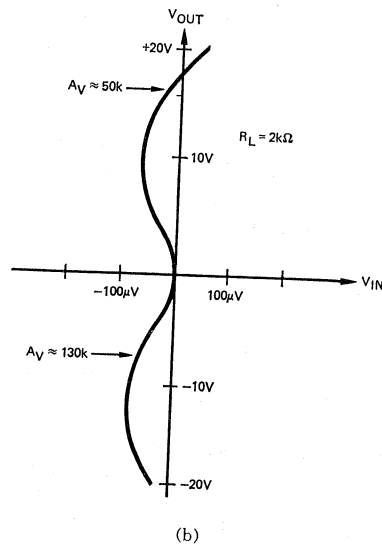
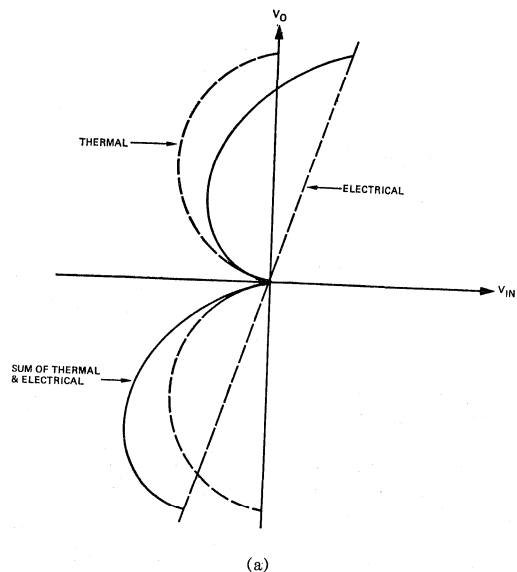


Fig. 6. (a) Idealized dc transfer curve for an IC op amp showing its electrical and thermal components. (b) Experimental open-loop transfer curve for a representative op amp (LM 101).

teristics determined principally by the electrical feedback (i.e.,  $A_V(0) \cong 1/\beta_e$ ). On the other hand, if  $\beta_e$  is small or nonexistent, the thermal term in (8) may dominate, giving an apparent open-loop gain characteristic determined by the thermal feedback factor  $\beta_T$ . Letting  $\beta_e = 0$  and combining (7) and (8),  $A_V(0)$  becomes

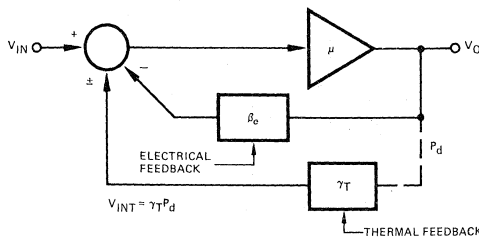


Fig. 7. Diagram used to calculate closed-loop gain with thermal feedback.

$$A_v(0) = \frac{\mu}{1 \pm \frac{\mu \gamma_T}{R_L} (V_s - 2V_o)} \quad (9)$$

Recalling from (6) that  $V_o$  ranges between 0 and  $V_s$ , we note that the incremental thermal feedback is greatest when  $V_o = 0$  or  $V_s$ , and it is at these points that the thermally limited gain is smallest. To use the amplifier in a predictable manner, one must always apply enough electrical feedback to reduce the gain below this minimum thermal gain. Thus, a *maximum usable gain* can be defined as that approximately equal to the value of (9) with  $V_o = 0$  or  $V_s$  which is

$$A_v(0)|_{\max} \cong \frac{R_L}{\gamma_T V_s} \quad (10)$$

or

$$A_v(0)|_{\max} \cong \frac{1}{\gamma_T I_{\max}} \quad (11)$$

It was assumed in (10) and (11) that thermal feedback dominates over the open-loop electrical gain,  $\mu$ . Finally, in (11) a maximum current was defined  $I_{\max} = V_s/R_L$  as the maximum current which would flow if the amplifier output could swing all the way to the supplies.

Equation (11) is a strikingly simple and quite general result which can be used to predict the expected maximum usable gain for an amplifier if we know only the maximum output current and the thermal feedback constant  $\gamma_T$ .

Recall that typically  $K_T \cong 0.3^\circ\text{C}/\text{W}$  and  $\gamma_T = (2 \times 10^{-3}) K_T \cong 0.6 \text{ mV}/\text{W}$ . Consider, as an example, the standard IC op amp operating with power supplies of  $V_s = \pm 15 \text{ V}$  and a minimum load of  $2 \text{ k}\Omega$ , which gives  $I_{\max} = 15 \text{ V}/2 \text{ k}\Omega = 7.5 \text{ mA}$ . Then, from (11), the maximum thermally limited gain is about:

$$\begin{aligned} A_v(0)|_{\max} &\cong 1/(0.6 \times 10^{-3})(7.5 \times 10^{-3}) \\ &\cong 220\,000. \end{aligned} \quad (12)$$

Comparing (2) and (12), it is apparent that the thermal characteristics dominate over the electrical ones if the minimum load resistor is used. For loads of  $6 \text{ k}\Omega$  or more, the electrical characteristics should begin to dominate

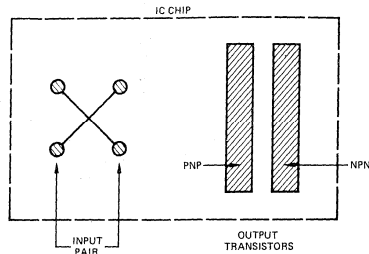


Fig. 8. One type layout in which a quad of input transistors is cross connected to reduce effect of nonuniform thermal gradients. The output transistors use distributed stripe geometries to generate predictable isothermal lines.

if thermal feedback from sources other than the output stage is negligible. It should be noted also that, in some high speed, high drain op amps, thermal feedback from the second stage dominates when there is no load.

As a second example, consider the so-called "power op amp" or high gain audio amp which suffers from the same thermal limitations just discussed. For a device which can deliver  $1 \text{ W}$  into a  $16\text{-}\Omega$  load, the peak output current and voltage are  $350 \text{ mA}$  and  $5.7 \text{ V}$ . Typically, a supply voltage of about  $16 \text{ V}$  is needed to allow for the swing loss in the IC output stage.  $I_{\max}$  is then  $8 \text{ V}/16 \Omega$  or  $0.5 \text{ A}$ . If the device is in a TO-5 package  $\gamma_T$  is approximately  $0.6 \text{ mV}/\text{W}$ , so from (11) the maximum usable dc gain is

$$A_v(0)|_{\max} \cong \frac{1}{(0.6 \times 10^{-3})(0.5)} \cong 3300. \quad (13)$$

This is quite low compared with electrical gains of, say,  $100\,000$  which are easily obtainable. The situation can be improved considerably by using a large die to separate the power devices from the inputs and carefully placing the inputs on constant temperature (isothermal) lines as illustrated in Fig. 8. If one also uses a power package with a heavy copper base,  $\gamma_T$ 's as low as  $50 \mu\text{V}/\text{W}$  have been observed. For example, a well-designed  $5\text{-W}$  amplifier driving an  $8\text{-}\Omega$  load and using a  $24\text{-V}$  supply, would have a maximum gain of  $13\,000$  in such a power package.

As a final comment, it should be pointed out that the most commonly observed effect of thermal feedback in high gain circuits is low frequency distortion due to the nonlinear transfer characteristic. Differential thermal coupling typically falls off at an initial rate of  $6 \text{ dB}/\text{octave}$  starting around  $100\text{--}200 \text{ Hz}$ , so higher frequencies are unaffected.

### III. SMALL-SIGNAL FREQUENCY RESPONSE

At higher frequencies where thermal effects can be ignored, the behavior of the op amp is dependent on purely electronic phenomena. Most of the important small and large signal performance characteristics of the classical IC op amp can be accurately predicted from

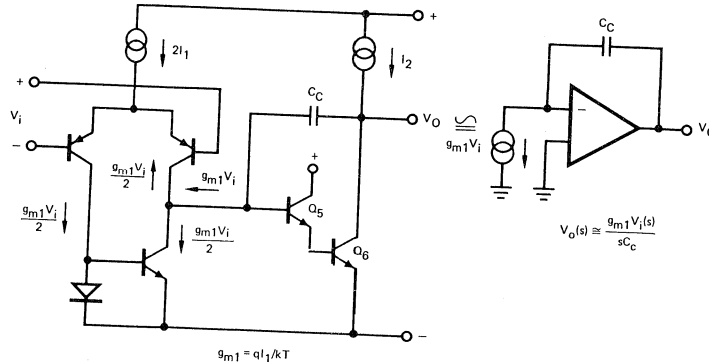


Fig. 9. First-order model of op amp used to calculate small signal high frequency gain. At frequencies of interest the input impedance of the second stage becomes low compared to first stage output impedance due to  $C_c$  feedback. Because of this, first stage output impedance can be assumed infinite, with no loss in accuracy.

very simple first-order models for the amplifier in Fig. 1 [8]. The small-signal model that is used assumes that the input differential amplifier and current mirror can be replaced by a frequency independent voltage controlled current source, see Fig. 9. The second stage consisting essentially of transistors  $Q_5$  and  $Q_6$ , and the current source load, is modeled as an ideal frequency independent amplifier block with a feedback or "integrating capacitor" identical to the compensation capacitor,  $C_c$ . The output stage is assumed to have unity voltage gain and is ignored in our calculations. From Fig. 9, the high frequency gain is calculated by inspection:

$$A_v(\omega) = \left| \frac{v_o}{v_i}(s) \right| = \left| \frac{g_{m1}}{sC_c} \right| = \frac{g_{m1}}{\omega C_c} \quad (14)$$

where dc and low frequency behavior have not been included since this was evaluated in the last section. Fig. 10 is a plot of the gain magnitude as predicted by (14). From this figure it is a simple matter to calculate the open-loop unity gain frequency  $\omega_u$ , which is also the gain-bandwidth product for the op amp under closed-loop conditions:

$$\omega_u = \frac{g_{m1}}{C_c} \quad (15)$$

In a practical amplifier,  $\omega_u$  is set to a low enough frequency (by choosing a large  $C_c$ ) so that negligible excess phase over the  $90^\circ$  due to  $C_c$  has built up. There are numerous contributors to excess phase including low  $f_t$  p-n-p's, stray capacitances, nondominant second stage poles, etc. These are discussed in more detail in a later section, but for now suffice it to say that, in the simple IC op amp,  $\omega_u/2\pi$  is limited to about 1 MHz. As a simple test of (15), the LM101 or the  $\mu A741$  has a first stage bias current  $I_1$  of 10  $\mu A$  per side, and a compensation capacitor for unity gain operation,  $C_c$ , of 30 pF. These amplifiers each have a first stage  $g_m$  which is half that

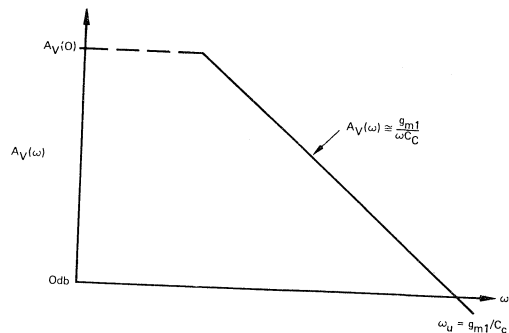


Fig. 10. Plot of open-loop gain calculated from model in Fig. 9. The dc and LF gain are given by (1), or (11) if thermal feedback dominates.

of the simple differential amplifier in Fig. 1 so  $g_{m1} = qI_1/2kT$ . Equation (15) then predicts a unity gain corner of

$$f_u = \frac{\omega_u}{2\pi} = \frac{g_{m1}}{2\pi C_c} = \frac{(0.192 \times 10^{-3})}{2\pi(30 \times 10^{-12})} = 1.02 \text{ MHz} \quad (16)$$

which agrees closely with the measured values.

#### IV. SLEW RATE AND SOME SPECIAL LIMITS

##### A. A General Limit on Slew Rate

If an op amp is overdriven by a large-signal pulse or square wave having a fast enough rise time, the output does not follow the input immediately. Instead, it ramps or "slews" at some limiting rate determined by internal currents and capacitances, as illustrated in Fig. 11. The magnitude of input voltage required to make the amplifier reach its maximum slew rate varies, depending on the type of input stage used. For an op amp with a



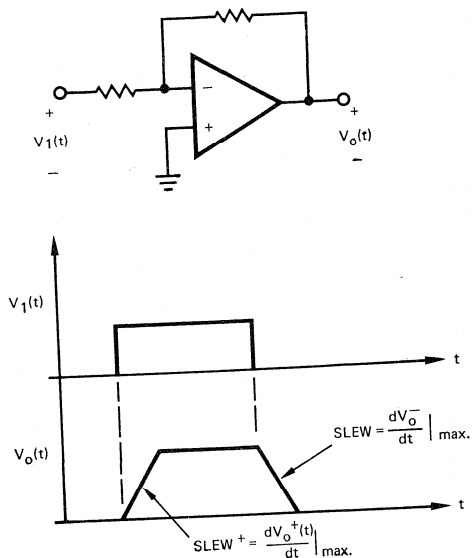


Fig. 11. Large signal "slewing" response observed if the input is overdriven.

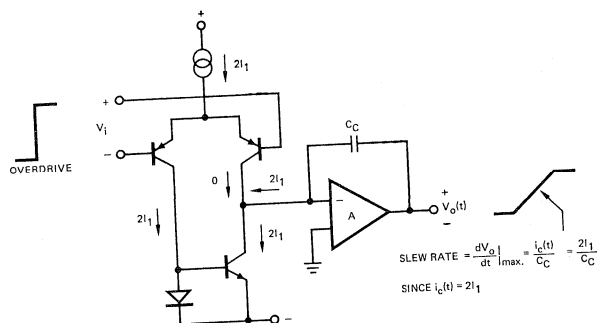


Fig. 12. Model used to calculate slew rate for the amp of Fig. 1 in the inverting mode. For simplicity, all transistor  $\alpha$ 's are assumed equal to unity, although results are essentially independent of  $\alpha$ . An identical slew rate can be calculated for a negative-going output, obtained if the applied input polarity is reversed.

simple input differential amp, an input of about 60 mV will cause the output to slew at 90 percent of its maximum rate, while a  $\mu A741$ , which has half the input  $g_m$ , requires 120 mV. High speed amplifiers such as the LM 118 or a FET-input circuit require much greater overdrive, with 1-3 V being common. The reasons for these overdrive requirements will become clear below.

An adequate model to calculate slew limits for the representative op amp in the inverting mode is shown in Fig. 12, where the only important assumption made is that  $I_2 \geq 2I_1$  in Fig. 1. This condition always holds in a well-designed op amp. (If one lets  $I_2$  be less than  $2I_1$ , the slew is limited by  $I_2$  rather than  $I_1$ , which results in lower

speed than is otherwise possible.) Fig. 12 requires some modification for noninverting operation, and we will study this later.

The limiting slew rate is now calculated from Fig. 12. Letting the input voltage be large enough to fully switch the input differential amp, we see that all of the first stage tail current  $2I_1$  is simply diverted into the integrator consisting of  $A$  and  $C_c$ . The resulting slew rate is then:

$$\text{slew rate} = \left. \frac{dv_o}{dt} \right|_{\text{max}} = \frac{i_c(t)}{C_c} \quad (17)$$

Noting that  $i_c(t)$  is a constant  $2I_1$ , this becomes

$$\left. \frac{dv_0}{dt} \right|_{\max} = \frac{2I_1}{C_c} \quad (18)$$

As a check of this result, recall that the  $\mu\text{A}741$  has  $I_1 = 10 \mu\text{A}$  and  $C_1 = 30 \text{ pF}$ , so we calculate:

$$\left. \frac{dv_0}{dt} \right|_{\max} = \frac{2 \times 10^{-5}}{30 \times 10^{-12}} = 0.67 \frac{\text{V}}{\mu\text{s}} \quad (19)$$

which agrees with measured values.

The large and small signal behavior of the op amp can be usefully related by combining (15) for  $\omega_u$  with (18). The slew rate becomes

$$\left. \frac{dv_0}{dt} \right|_{\max} = \frac{2\omega_u I_1}{g_{m1}} \quad (20)$$

Equation (20) is a general and very useful relationship. It shows that, for a given unity-gain frequency,  $\omega_u$ , the slew rate is determined entirely by just the ratio of first stage operating current to first stage transconductance,  $I_1/g_{m1}$ . Recall that  $\omega_u$  is set at the point where excess phase begins to build up, and this point is determined largely by technology rather than circuit limitations. Thus, the only effective means available to the circuit designer for increasing op amp slew rate is to *decrease* the ratio of first stage transconductance to operating current,  $g_{m1}/I_1$ .

### B. Slew Limiting for Simple Bipolar Input Stage

The significance of (20) is best seen by considering the specific case of a simple differential bipolar input as in Fig. 1. For this circuit, the first stage transconductance (for  $\alpha_1 = 1$ ) is<sup>1</sup>

$$g_{m1} = qI_1/kT \quad (21)$$

so that

$$\frac{g_{m1}}{I_1} = q/kT. \quad (22)$$

Using this in (20), the maximum bipolar slew rate is

$$\left. \frac{dv_0}{dt} \right|_{\max} = 2\omega_u \frac{kT}{q} \quad (23)$$

This provides us with the general (and somewhat dismal) conclusion that slew rate in an op amp with a simple bipolar input stage is dependent only upon the unity gain corner and fundamental constants. Slew rate can be increased only by increasing the unity gain corner, which we have noted is generally difficult to do. As a demonstration of the severity of this limit, imagine an op amp using highly advanced technology and clever design, which might have a stable unity gain frequency of 100 MHz. Equation (23) predicts that the slew rate for this advanced device is only

<sup>1</sup> Note that (21) applies only to the simple differential input stage of Fig. 12. For compound input stages as in the LM101 or  $\mu\text{A}741$ ,  $g_{m1}$  is half that in (21), and the slew rate in (23) is doubled.

$$\left. \frac{dv_0}{dt} \right|_{\max} = 33 \frac{\text{V}}{\mu\text{s}} \quad (24)$$

which is good, but hardly impressive when compared with the difficulty of building a 100-MHz op amp.<sup>2</sup> But, there are some ways to get around this limit as we shall see shortly.

### C. Power Bandwidth

Our intuition regarding slew rate will be enhanced somewhat if we relate it to a term called "power bandwidth." Power bandwidth is defined as the maximum frequency at which full output swing (usually 10 V peak) can be obtained without distortion. For a sinusoidal output voltage  $v_0(t) = V_p \sin \omega t$ , the rate of change of output, or slew rate, required to reproduce the output is

$$\frac{dv_0}{dt} = \omega V_p \cos \omega t. \quad (25)$$

This has a maximum when  $\cos \omega t = 1$  giving

$$\left. \frac{dv_0}{dt} \right|_{\max} = \omega V_p, \quad (26)$$

so the highest frequency that can be reproduced without slew limiting,  $\omega_{\max}$  (power bandwidth) is

$$\omega_{\max} = \frac{1}{V_p} \left. \frac{dv_0}{dt} \right|_{\max}. \quad (27)$$

Thus, power bandwidth and slew rate are directly related by the inverse of the peak of the sine wave  $V_p$ . Fig. 13 shows the severe distortion of the output sine wave which results if one attempts to amplify a sine wave of frequency  $\omega > \omega_{\max}$ .

Some numbers illustrate typical op amp limits. For a  $\mu\text{A}741$  or LM101 having a maximum slew rate of 0.67 V/ $\mu\text{s}$ , (27) gives a maximum frequency for an undistorted 10-V peak output of

$$f_{\max} = \frac{\omega_{\max}}{2\pi} = 10.7 \text{ kHz}, \quad (28)$$

which is a quite modest frequency considering the much higher frequency small signal capabilities of these devices. Even the highly advanced 100-MHz amplifier considered above has a 10-V power bandwidth of only 0.5 MHz, so it is apparent that a need exists for finding ways to improve slew rate.

### D. Techniques for Increasing Slew Rate

1) *Resistive Enhancement of the Bipolar Stage:* Equation (20) indicates that slew rate can be improved if we reduce first stage  $g_{m1}/I_1$ . One of the most effective ways

<sup>2</sup> We assume in all of these calculations that  $C_c$  is made large enough so that the amplifier has less than 180° phase lag at  $\omega_u$ , thus making the amplifier stable for unity closed-loop gain. For higher gains one can of course reduce  $C_c$  (if the IC allows external compensation) and increase the slew rate according to (18).

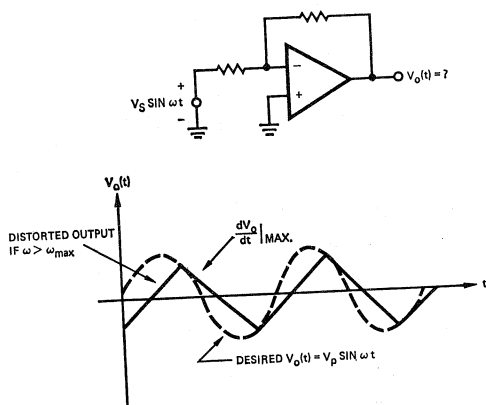


Fig. 13. Slew limiting effects on output sinewave that occur if frequency is greater than power bandwidth,  $\omega_{max}$ . The onset of slew limiting occurs very suddenly as  $\omega$  reaches  $\omega_{max}$ . No distortion occurs below  $\omega_{max}$ , while almost complete triangularization occurs at frequencies just slightly above  $\omega_{max}$ .

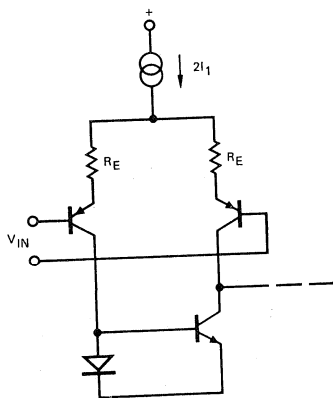


Fig. 14. Resistive degeneration used to provide slew rate enhancement according to (29).

of doing this is shown in Fig. 14, where simple resistive emitter degeneration has been added to the input differential amplifier [8]. With this change, the  $g_{m1}/I_1$  drops to

$$\frac{g_{m1}}{I_1} = \frac{38.5}{1 + R_E I_1 / 26 \text{ mV}} \quad (29)$$

at 25°C.

The quantity  $g_{m1}/I_1$  is seen to decrease rapidly with added  $R_E$  as soon as the voltage drop across  $R_E$  exceeds 26 mV. The LM118 is a good example of a bipolar amplifier which uses emitter degeneration to enhance slew rate [4]. This device uses emitter resistors to produce  $R_E I_1 = 500 \text{ mV}$ , and has a unity gain corner of 16

MHz. Equations (20) and (29) then predict a maximum inverting slew rate of

$$\left. \frac{dv_o}{dt} \right|_{\max} = 2\omega_u \frac{I_1}{g_{m1}} = \omega_u = 100 \frac{\text{V}}{\mu\text{s}} \quad (30)$$

which is a twenty-fold improvement over a similar amplifier without emitter resistors.

A penalty is paid in using resistive slew enhancement, however. The two added emitter resistors must match extremely well or they add voltage offset and drift to the input. In the LM118, for example, the added emitter  $R$ 's have values of 2.0 k $\Omega$  each and these contribute an input offset of 1 mV for each 4  $\Omega$  (0.2 percent) of mismatch. The thermal noise of the resistors also unavoidably degrades noise performance.

2) *Slew Rate in the FET Input Op Amp:* The FET (JFET or MOSFET) has a considerably lower transconductance than a bipolar device operating at the same current. While this is normally considered a drawback of the FET, we note that this "poor" behavior is in fact highly desirable in applications to fast amplifiers. To illustrate, the drain current for a JFET in the "current saturation" region can be approximated by

$$I_D \cong I_{DSS} (V_{GS} / V_T - 1)^2 \quad (31)$$

where

$$\begin{aligned} I_{DSS} & \text{ the drain current for } V_{GS} = 0, \\ V_{GS} & \text{ the gate source voltage having positive polarity} \\ & \text{ for forward gate-diode bias,} \\ V_T & \text{ the threshold voltage having negative polarity} \\ & \text{ for JFET's.} \end{aligned}$$

The small-signal transconductance is obtained from (31) as  $g_m = \partial I_D / \partial V_{GS}$ . Dividing by  $I_D$  and simplifying, the ratio  $g_m / I_D$  for a JFET is

$$\frac{g_m}{I_D} \cong \frac{2}{(V_{GS} - V_T)} = \frac{2}{-V_T} \left[ \frac{I_{DSS}}{I_D} \right]^{1/2} \quad (32)$$

Maximum amplifier slew rate occurs for minimum  $g_m / I_D$  and, from (32), this occurs when  $I_D$  (or  $V_{GS}$ ) is maximum. Normally it is impractical to forward bias the gate junction so a practical minimum occurs for (32) when  $V_{GS} \cong 0 \text{ V}$  and  $I_D \cong I_{DSS}$ . Then

$$\left. \frac{g_m}{I_D} \right|_{\min} \cong -\frac{2}{V_T} \quad (33)$$

Comparing (33) with the analogous bipolar expression, (22), we find from (20) that the JFET slew rate is greater than bipolar by the factor

$$\frac{\text{JFET slew}}{\text{bipolar slew}} \approx \frac{-V_T \omega_{uf}}{2kT/q \omega_{ub}} \quad (34)$$

where  $\omega_{uf}$  and  $\omega_{ub}$  are unity-gain bandwidths for JFET and bipolar amps, respectively. Typical JFET thresholds are around 2 V ( $V_T = -2 \text{ V}$ ), so for equal bandwidths (34) tells us that a JFET-input op amp is about forty times faster than a simple bipolar input. Further, if

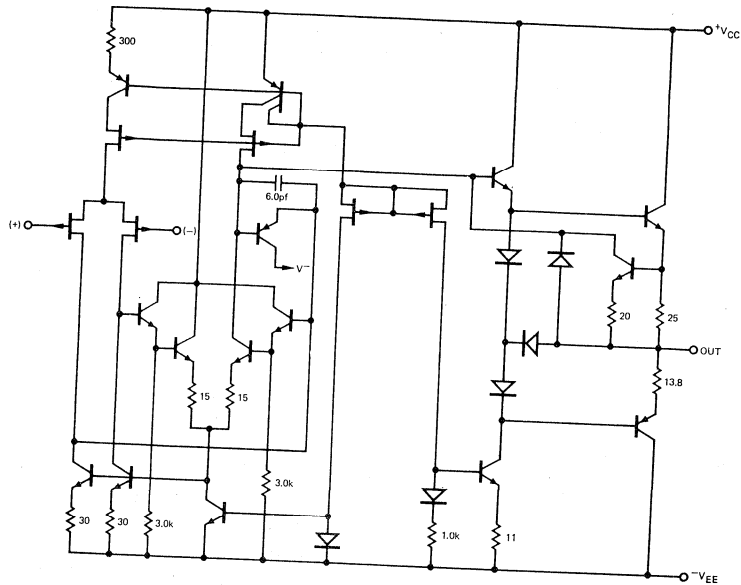


Fig. 15. Monolithic operational amplifier employing compatible p-channel JFET's on the same chip with normal bipolar components.

JFET's are properly substituted for the slow p-n-p's in a monolithic design, bandwidth improvements by at least a factor of ten are obtainable. JFET-input op amps, therefore, offer slew rate improvements by better than two orders of magnitude when compared with the conventional IC op amp. (Similar improvements are possible with MOSFET-input amplifiers.) This characteristic, coupled with picoamp input currents and reasonable offset and drift, make the JFET-input op amp a very desirable alternative to conventional bipolar designs.

As an example, Fig. 15, illustrates one design for an op amp employing compatible p-channel JFET's on the same chip with the normal bipolar components. This circuit exhibits a unity gain corner of 10 MHz, a 33 V/ $\mu$ s slew rate, an input current of 10 pA and an offset voltage and drift of 3 mV and 3  $\mu$ V/ $^{\circ}$ C [6]. Bandwidth and slew rate are thus improved over simple IC bipolar by factors of 10 and 100, respectively. At the same time input currents are smaller by about  $10^3$ , and offset voltages and drifts are comparable to or better than slew enhanced bipolar circuits.

#### V. SECOND-ORDER EFFECTS: VOLTAGE FOLLOWER SLEW BEHAVIOR

If the op amp is operated in the noninverting mode and driven by a large fast rising input, the output exhibits the characteristic waveform in Fig. 16. As shown, this waveform does not have the simple symmetrical slew characteristic of the inverter. In one direction, the output has a fast step (slew "enhancement") followed

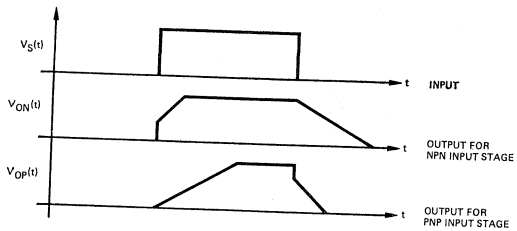
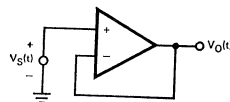


Fig. 16. Large signal response of the voltage follower. For an op amp with simple n-p-n input stage we get the waveform  $v_{op}(t)$ , which exhibits a step slew "enhancement" on the positive going output, and a slew "degradation" on the negative going output. (For a p-n-p input stage, these effects are reversed as shown by  $v_{op}(t)$ .)

by a "normal" inverter slewing response. In the other direction, it suffers a slew "degradation" or reduced slope when compared with the inverter slewing response.

We will first study slew degradation in the voltage follower connection, since this represents a worst case slewing condition for the op amp. A model which adequately represents the follower under large-signal conditions can be obtained from that in Fig. 12 by simply

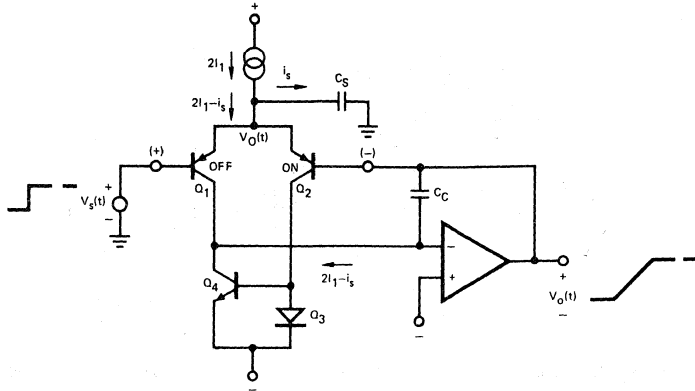


Fig. 17. Circuit used for calculation of slew "degradation" in the voltage follower. The degradation is caused by the capacitor  $C_s$ , which robs current from the tail,  $2I_1$ , thereby preventing the full  $2I_1$  from slewing  $C_c$ .

tying the output to the inverting input, and including a capacitor  $C_s$  to account for the presence of any capacitance at the output of the first stage (tail) current source, see Fig. 17. This "input tail" capacitance is important in the voltage follower because the input stage undergoes rapid large-signal excursions in this connection, and the charging currents in  $C_s$  can be quite large.

Circuit behavior can be understood by analyzing Fig. 17 as follows. The large-signal input step causes  $Q_1$  to turn OFF, leaving  $Q_2$  to operate as an emitter follower with its emitter tracking the variational output voltage,  $v_o(t)$ . It is seen that  $v_o(t)$  is essentially the voltage appearing across both  $C_s$  and  $C_c$  so we can write

$$\frac{dv_o}{dt} \cong \frac{i_c}{C_c} \cong \frac{i_s}{C_s}. \quad (35)$$

Noting that  $i_c \cong 2I_1 - i_s$  (unity  $\alpha$ 's assumed), (35) can be solved for  $i_s$ :

$$i_s \cong \frac{2I_1}{1 + C_s/C_c}, \quad (36)$$

which is seen to be constant with time. The degraded voltage follower slew rate is then obtained by substituting (36) into (35):

$$\left. \frac{dv_o}{dt} \right|_{\text{degr}} \cong \frac{i_s}{C_c} \cong \frac{2I_1}{C_c + C_s}. \quad (37)$$

Comparing (37) with the slew rate for the inverter, (18), it is seen that the slew rate is reduced by the simple factor  $1/(1 + C_s/C_c)$ . As long as the input tail capacitance  $C_s$  is small compared with the compensation capacitor  $C_c$ , little degradation occurs. In high speed amplifiers where  $C_c$  is small, degradation becomes quite noticeable, and one is encouraged to develop circuits with small  $C_s$ .

As an example, consider the relatively fast LM118

which has  $C_c \cong 5$  pF,  $C_s \cong 2$  pF,  $2I_1 = 500$   $\mu$ A. The calculated inverter slew rate is  $2I_1/C_c \cong 100$  V/ $\mu$ s, and the degraded voltage follower slew rate is found to be  $2I_1/(C_c + C_s) \cong 70$  V/ $\mu$ s. The slew degradation is seen to be about 30 percent, which is very significant. By contrast, a  $\mu$ A741 has  $C_c \cong 30$  pF and  $C_s \cong 4$  pF which results in a degradation of less than 12 percent.

The slew "enhanced" waveform can be similarly predicted from a simplified model. By reversing the polarity of the input and initially assuming a finite slope on the input step, the enhanced follower is analyzed, as shown in Fig. 18. Noting that  $Q_1$  is assumed to be turned on by the step input and  $Q_2$  is OFF, the output voltage becomes

$$v_o(t) \cong -\frac{1}{C_c} \int_0^t [2I_1 + i_s(t)] dt. \quad (38)$$

The voltage at the emitter of  $Q_1$  is essentially the same as the input voltage,  $v_i(t)$ , so the current in the "tail" capacitance  $C_s$  is

$$i_s(t) \cong C_s \frac{dv_i}{dt} \cong \frac{C_s V_{ip}}{t_1} \quad 0 < t < t_1. \quad (39)$$

Combining (38) and (39),  $v_o(t)$  is

$$-v_o(t) \cong \frac{1}{C_c} \int_0^t 2I_1 dt + \frac{1}{C_c} \int_0^{t_1} \frac{C_s V_{ip}}{t_1} dt \quad (40)$$

or

$$-v_o(t) \cong \frac{C_s}{C_c} V_{ip} + \frac{2I_1 t}{C_c}. \quad (41)$$

Equation (41) tells us that the output has an initial negative step which is the fraction  $C_s/C_c$  of the input voltage. This is followed by a normal slewing response, in which the slew rate is identical to that of the inverter, see (18). This response is illustrated in Fig. 18.

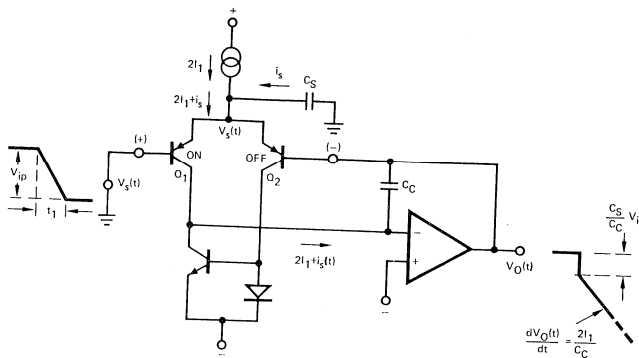


Fig. 18. Circuit used for calculation of slew "enhancement" in the voltage follower. The fast falling input causes a step output followed by a normal slew response as shown.

## VI. LIMITATIONS ON BANDWIDTH

In earlier sections, all bandlimiting effects were ignored except that of the compensation capacitor,  $C_c$ . The unity-gain frequency was set at a point sufficiently low so that negligible excess phase (over the  $90^\circ$  from the dominant pole) due to second-order (high frequency) poles had built up. In this section the major second-order poles which contribute to bandlimiting in the op amp are identified.

### A. The Input Stage: *p-n-p*'s, the Mirror Pole, and the Tail Pole

For many years it was popular to identify the lateral *p-n-p*'s (which have  $f_i$ 's  $\cong 3$  MHz) as the single dominant source of bandlimiting in the IC op amp. It is quite true that the *p-n-p*'s do contribute significant excess phase to the amplifier, but it is not true that they are the sole contributor to excess phase [9]. In the input stage, alone, there is at least one other important pole, as illustrated in Fig. 19(a). For the simple differential input stage driving a differential-to-single ended converter ("mirror" circuit), it is seen that the inverting signal (which is the feedback signal) follows two paths, one of which passes through the capacitance  $C_s$ , and the other through  $C_m$ . These capacitances combine with the dynamic resistances at their nodes to form poles designated the mirror pole at

$$p_m \cong \frac{I_1}{C_m kT/q}, \quad (42)$$

and the tail pole at

$$p_t \cong \frac{2I_1}{C_s kT/q}. \quad (43)$$

It can be seen that if one attempts to operate the first stage at too low a current, these poles will bandlimit the amplifier. If, for example, we choose  $I_1 = 1 \mu\text{A}$ , and assume  $C_m \cong 7$  pF (consisting of 4-pF isolation ca-

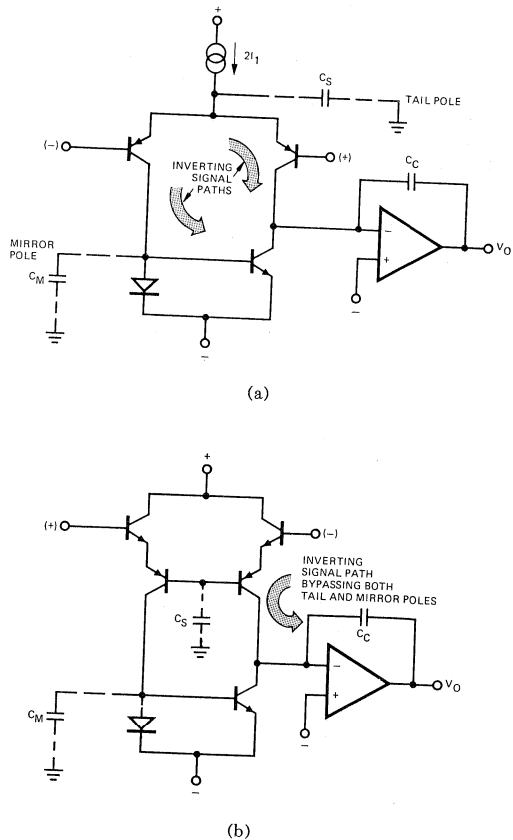


Fig. 19. (a) Circuit showing "mirror" pole due to  $C_m$  and "tail" pole due to  $C_s$ . One component of the signal due to an inverting input must pass through either the mirror or tail poles. (b) Alternate circuit to Fig. 19(a) (LM101,  $\mu\text{A}741$ ) which has less excess phase. Reason is that half the inverting signal path need not pass through the mirror pole or the tail pole.

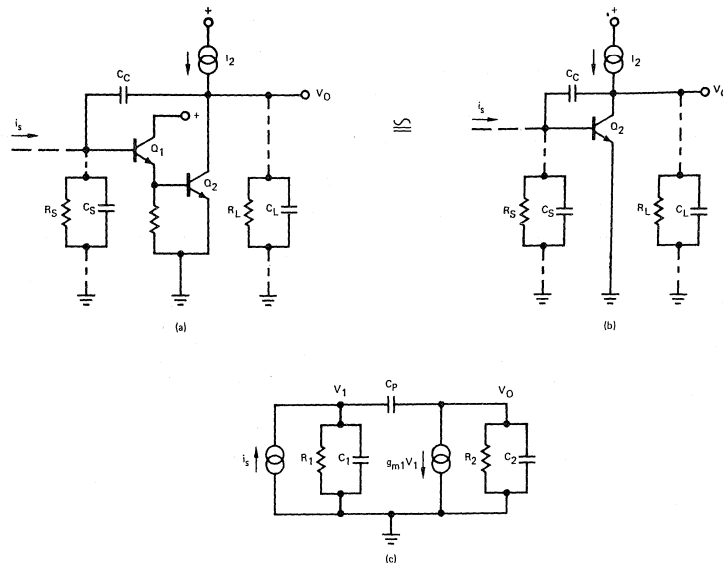


Fig. 20. Simplification of second stage used for pole-splitting analysis. (a) Complete second stage with input stage and output stage loading represented by  $R_s$ ,  $C_s$ , and  $R_L$ ,  $C_L$ , respectively. (b) Emitter follower ignored to simplify analysis. (c) Hybrid  $\pi$  model substituted for transistor in (b). Source and load impedances are absorbed into model with the total impedances represented by  $R_1$ ,  $C_1$ , and  $R_2$ ,  $C_2$ . Transistor base resistance is ignored and  $C_p$  includes both  $C_c$  and transistor collector-base capacitance.

capacitance and 3-pF emitter transition capacitance) and  $C_s \cong 4$  pF,<sup>3</sup>  $p_m/2\pi \cong 0.9$  MHz and  $p_l/2\pi \cong 3$  MHz either of which would seriously degrade the phase margin of a 1-MHz amplifier.

If a design is chosen in which either the tail pole or the mirror pole is absent (or unimportant), the remaining pole rolls off only half the signal, so the overall response contains a pole-zero pair separated by one octave. Such a pair generally has a small effect on amplifier response unless it occurs near  $\omega_u$ , where it can degrade phase margin by as much as 20°.

It is interesting to note that the compound input stage

### B. The Second Stage: Pole Splitting

The assumption was made in Section III that the second stage behaved as an ideal integrator having a single dominant pole response. In practice, one must take care in designing the second stage or second-order poles can cause significant deviation from the expected response. Considerable insight into the basic way in which the second stage operates can be obtained by performing a small-signal analysis on a simplified version of the circuit as shown in Fig. 20 [10]. A straightforward two-node analysis of Fig. 20(c) produces the following expression for  $v_{out}$ .

$$\frac{v_{out}}{i_s} = \frac{-g_m R_1 R_2 (1 - s C_p / g_m)}{1 + s[R_1(C_1 + C_p) + R_2(C_2 + C_p)] + g_m R_1 R_2 C_p + s^2 R_1 R_2 [C_1 C_2 + C_p(C_1 + C_2)]} \quad (44)$$

of the classical LM101 (and  $\mu A741$ ) has a distinct advantage over the simple differential stage, as seen in Fig. 19(b). This circuit is noninverting across each half, thus it provides a path in which half the feedback signal bypasses both the mirror and tail poles.

<sup>3</sup>  $C_s$  can have a wide range of values depending on circuit configuration. It is largest for n-p-n input differential amps since the current source has a collector-substrate capacitance ( $C_s \cong 3-4$  pF) at its output. For p-n-p input stages it can be as small as 1-2 pF.

The denominator of (44) can be approximately factored under conditions that its two poles are widely separated. Fortunately, the poles are, in fact, widely separated under most normal operating conditions. Therefore, one can assume that the denominator of (44) has the form

$$D(s) = (1 + s/p_1)(1 + s/p_2) \\ = 1 + s(1/p_1 + 1/p_2) + s^2/p_1 p_2 \quad (45)$$

With the assumption that  $p_1$  is the dominant pole and

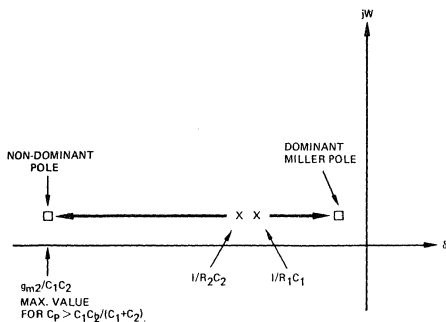


Fig. 21. Pole migration for second stage employing "pole-splitting" compensation. Plot is shown for increasing  $C_p$  and it is noted that the nondominant pole reaches a maximum value for large  $C_p$ .

$p_2$  is nondominant, i.e.,  $p_1 \ll p_2$ , (45) becomes

$$D(s) \cong 1 + s/p_1 + s^2/p_1 p_2. \quad (46)$$

Equating coefficients of  $s$  in (44) and (46), the dominant pole  $p_1$  is found directly:

$$p_1 \cong \frac{1}{R_1(C_1 + C_p) + R_2(C_2 + C_p) + g_m R_1 R_2 C_p} \quad (47)$$

$$\cong \frac{1}{g_m R_1 R_2 C_p}. \quad (48)$$

The latter approximation, (48), normally introduces little error, because the  $g_m$  term is much larger than the other two. We note at this point that  $p_1$ , which represents the dominant pole of the amplifier, is due simply to the familiar Miller-multiplied feedback capacitance  $g_m R_2 C_p$  combined with input node resistance,  $R_1$ . The nondominant pole  $p_2$  is found similarly by equating  $s^2$  coefficients in (44) and (46) to get  $p_1 p_2$ , and dividing by  $p_1$  from (48). The result is

$$p_2 \cong \frac{g_m C_p}{C_1 C_2 + C_p(C_1 + C_2)}. \quad (49)$$

Several interesting things can be seen in examining (48) and (49). First, we note that  $p_1$  is inversely proportional to  $g_m$  (and  $C_p$ ), while  $p_2$  is directly dependent on  $g_m$  (and  $C_p$ ). Thus, as either  $C_p$  or transistor gain are increased, the dominant pole decreases and the nondominant pole increases. The poles  $p_1$  and  $p_2$  are being "split-apart" by the increased coupling action in a kind of inverse root locus plot.

This *pole-splitting* action is shown in Fig. 21, where pole migration is plotted for  $C_p$  increasing from 0 to a large value. Fig. 22 further illustrates the action by giving specific pole positions for the  $\mu$ A741 op amp. It is seen that the initial poles (for  $C_p = 0$ ) are both in the tens of kilohertz region and these are predicted to reach 2.5 Hz ( $p_1/2\pi$ ) and 66 MHz ( $p_2/2\pi$ ) after compensation is applied. This result is, of course, highly satisfactory

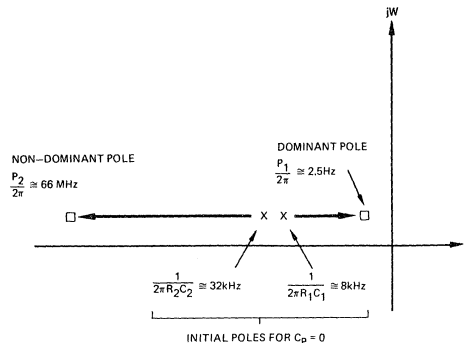


Fig. 22. Example of pole-splitting compensation in the  $\mu$ A741 op amp. Values used in (48) and (49) are:  $g_{m2} = 1/87 \Omega$ ,  $C_p = 30$  pF,  $C_1 = C_2 = 10$  pF,  $R_1 = 1.7$  M $\Omega$ ,  $R_2 = 100$  k $\Omega$ .

since the second stage now has a single dominant pole effective over a wide frequency band.

### C. Failure of Pole Splitting

There are several situations in which the application of pole-splitting compensation may not result in a single dominant pole response. One common case occurs in very wide-band op amps where the pole-splitting capacitor is small. In this situation the nondominant pole given by (49) may not become broadbanded sufficiently so that it can be ignored. To illustrate, suppose we attempt to minimize power dissipation by running the second stage of an LM118 (which has a small-signal bandwidth of 16 MHz) at 0.1 mA. For this op amp  $C_p = 5$  pF,  $C_1 \cong C_2 \cong 10$  pF. From (49), the nondominant pole is

$$\frac{p_2}{2\pi} \cong 16 \text{ MHz} \quad (50)$$

which lies right at the unity-gain frequency. This pole alone would degrade phase margin by  $45^\circ$ , so it is clear that we need to bias the second stage with a collector current greater than 0.1 mA to obtain adequate  $g_m$ . Insufficient pole-splitting can therefore occur; but the cure is usually a simple increase in second stage  $g_m$ .

A second type of pole-splitting failure can occur, and it is often much more difficult to cope with. If, for example, one gets over-zealous in his attempt to broadband the nondominant pole, he soon discovers that other poles exist within the second stage which can cause difficulties. Consider a more exact equivalent circuit for the second stage of Fig. 20(a) as shown in Fig. 23. If the follower is biased at low currents or if  $C_p$ ,  $Q_2 g_m$ , and/or  $r_x$  are high, the circuit can contain at least four important poles rather than the two considered in simple pole splitting. Under these conditions, we no longer have a response with just negative real poles as in Fig. 21, but observe a root locus of the sort shown in Fig. 24. It is seen in this case that the circuit contains a pair of com-



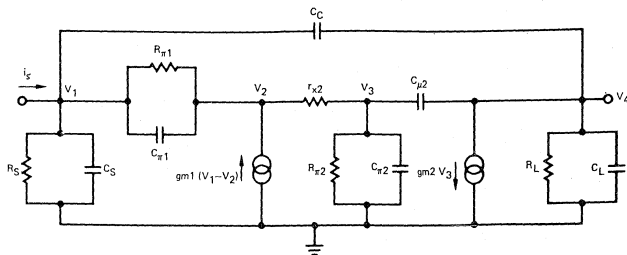


Fig. 23. More exact equivalent circuit for second stage of Fig. 20 (a) including a simplified  $\pi$  model for the emitter follower ( $R_{\pi 3}$ ,  $C_{\pi 3}$ ,  $g_{m1}$ ) and a complete  $\pi$  for  $Q_2$  ( $r_{\pi 2}$ ,  $R_{\pi 2}$ , etc.).

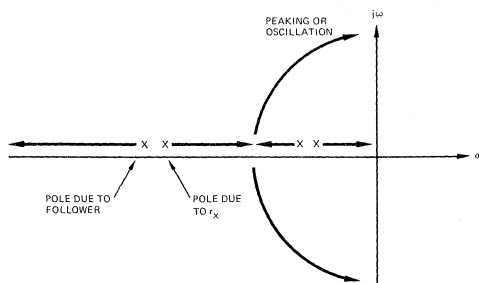


Fig. 24. Root locus for second stage illustrating failure of pole splitting due to high  $g_{m2}$ ,  $r_{\pi 2}$ ,  $C_p$ , and/or low bias current in the emitter follower.

plex, possibly underdamped poles which, of course, can cause peaking or even oscillation. This effect occurs so commonly in the development of wide-band pole-split amplifiers that it has been (not fondly) dubbed "the second stage bump."

There are numerous ways to eliminate the "bump," but no single cure has been found which is effective in all situations. A direct hand analysis of Fig. 23 is possible, but the results are difficult to interpret. Computer analysis seems the best approach for this level of complexity, and numerous specific analyses have been made. The following is a list of circuit modifications that have been found effective in reducing the bump in the various studies: 1) reduce  $g_{m2}$ ,  $r_{\pi 2}$ ,  $C_{\mu 2}$ ; 2) add capacitance or a series  $RC$  network from the stage input to ground—this reduces the high frequency local feedback due to  $C_p$ ; 3) pad capacitance at the output for similar reasons; 4) increase operating current of the follower; 5) reduce  $C_p$ ; 6) use a higher  $f_t$  process.

#### D. Troubles in The Output Stage

Of all the circuitry in the modern IC op amp, the class-AB output stage probably remains the most troublesome. None of the stages in use today behave as well as one might desire when stressed under worst case con-

ditions. To illustrate, one of the most commonly used output stages is shown in Fig. 2(b). The p-n-p's in this circuit are "substrate" p-n-p's having low current  $f_t$ 's of around 20 MHz. Unfortunately, both  $\beta_0$  and  $f_t$  begin to fall off rapidly at quite low current densities, so as one begins to sink just a few milliamps in the circuit, phase margin troubles can develop. The worst effect occurs when the amplifier is operated with a large capacitive load ( $>100$  pF) while sinking high currents. As shown in Fig. 25, the load capacitance on the output follower causes it to have negative input conductance, while the driver follower can have an inductive output impedance. These elements combine with the capacitance at the interstage to generate the equivalent of a one-port oscillator. In a carefully designed circuit, oscillation is suppressed, but peaking (the "output bump") can occur in most amplifiers under appropriate conditions.

One new type of output circuit which does not use p-n-p's is shown in Fig. 26 [6]. This circuit employs compatible JFET's (or MOSFET's, see similar circuit in [11]) in a FET/bipolar quasi-complementary output stage, which is insensitive to load capacitance. Unfortunately, this circuit is rather complex and employs extra process steps, so it does not appear to represent the cure for the very low cost op amps.

### VII. THE GAIN CELL: LINEAR LARGE-SCALE INTEGRATION

As the true limitations of the basic op amp are more fully understood, this knowledge can be applied to the development of more "optimum" amplifiers. There are, of course, many ways in which one might choose to optimize the device. We might, for example, attempt to maximize speed (bandwidth, slew rate, settling time) without sacrificing dc characteristics. The compatible JFET/bipolar amp of Fig. 15 represents such an effort. An alternate choice might be to design an amplifier having all of the performance features of the most widely used general purpose op amps (i.e.,  $\mu A741$ , LM107, etc.), but having minimum possible die area. Such a pursuit is parallel to the efforts of digital large-scale integration (LSI) designers in their development of minimum area

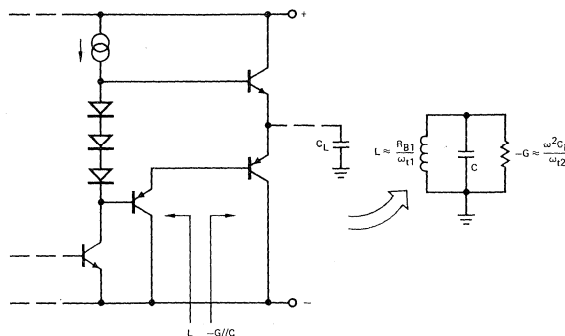


Fig. 25. Troubles in the conventional class-AB output stage of Fig. 2(b). The low  $f_c$  output p-n-p's interact with load capacitance to form the equivalent of a one-port oscillator.

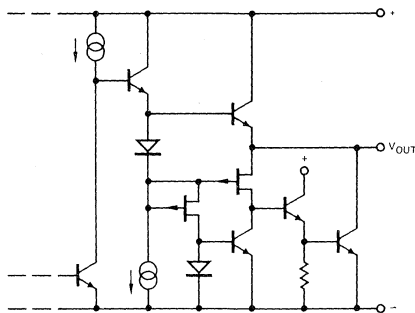


Fig. 26. The "BIFET" output stage employing JFET's and bipolar n-p-n's to eliminate sensitivity to load capacitance.

memory cells or gates. The object of such efforts, of course, is to develop lower cost devices which allow wide and highly economic usage.

In this section we briefly discuss certain aspects of the linear *gain cell*, a general purpose, internally compensated op amp having a die area which is significantly smaller than that of equivalent, present day, industry standard amplifiers.

#### A. Transconductance Reduction

The single largest area component in the internally compensated op amp is the compensation capacitor (about 30 pF, typically). A major interest in reducing amplifier die area, therefore, centers about finding ways in which this capacitor can be reduced in size. With this in mind, we find it useful to examine (15), which relates compensation capacitor size to two other parameters, unity gain corner frequency  $\omega_u$ , and first stage transconductance  $g_{m1}$ . It is immediately apparent that for a fixed, predetermined unity gain corner (about  $2\pi \times 1$  MHz in our case), there is only one change that can

be made to reduce the size of  $C_c$ : *the transconductance of the first stage must be reduced*. If we restrict our interest to simple bipolar input stages (for low cost), we recall the  $g_{m1} = qI_1/kT$ . Only by reducing  $I_1$  can  $g_{m1}$  be reduced, and we earlier found in Section VI-A and Fig. 19(a) and (b) that  $I_1$  cannot be reduced much without causing phase margin difficulties due to the mirror pole and the tail pole.

An alternate basic approach to  $g_m$  reduction is illustrated in Fig. 27 [12]. Here, a multiple collector p-n-p structure, which is easily fabricated in IC form, is used to split the collector current into two components, one component (the larger) of which is simply tied to ground, thereby "throwing away" a major portion of the transistor output current. The result is that the  $g_m$  of the transistor is reduced by the ratio of  $1/(1+n)$  (see Fig. 27), and the compensation capacitance can be reduced directly by the same factor. It might appear that the mirror pole would still cause difficulties since the current mirror becomes current starved in Fig. 27, but the effect is not as severe as might be expected. The

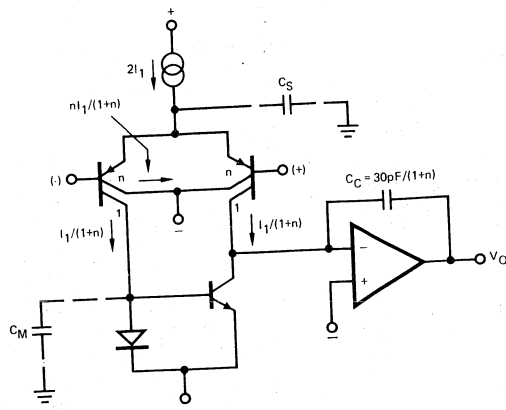


Fig. 27. Basic  $g_m$  reduction obtained by using split collector p-n-p's.  $C_c$  and area are reduced since  $C_c = g_m s / \omega_u$ .

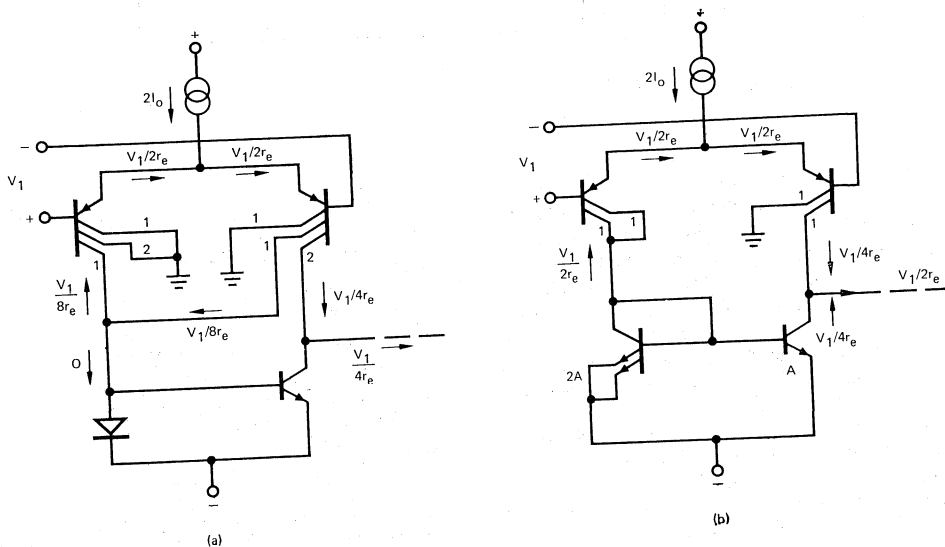


Fig. 28. Variations on  $g_m$  reduction. (a) Cross-coupled connection eliminates all ac current passing through the mirror, yet maintains dc balance. (b) This approach maintains high current on the diode side of the mirror, thereby broadbanding the mirror pole.

reason is that the inverting signal can now pass through the high current wide-band path, across the differential amp emitters and into the second stage, so at least half the signal current does not become bandlimited. This partial bandlimiting can be further reduced by using one of the circuits in Fig. 28(a) or (b).<sup>4</sup> In (a), the p-n-p collectors are cross coupled in such a way that the ac signal is cancelled in the mirror circuit, while dc remains completely balanced. Thus the mirror pole is virtually eliminated. The circuit does have a drawback, however, in that the uncorrelated noise currents coming from the two p-n-p's add rather than subtract at the input to the mirror, thereby degrading noise performance.

The circuit in Fig. 28(b) does not have this defect, but requires care in matching p-n-p collector ratios to n-p-n emitter areas. Otherwise offset and drift will degrade as one attempts to reduce  $g_m$  by large factors.

#### B. A Gain Cell Example

As one tries to make large reductions in die area for the gain cell, many factors must be considered in addition to novel circuit approaches. Of great importance are special layout/circuit techniques which combine a maximum number of components into minimum area.

<sup>4</sup> The circuit in Fig. 28(a) is due to R. W. Russell and the variation in Fig. 28(b) was developed by D. W. Zobel.

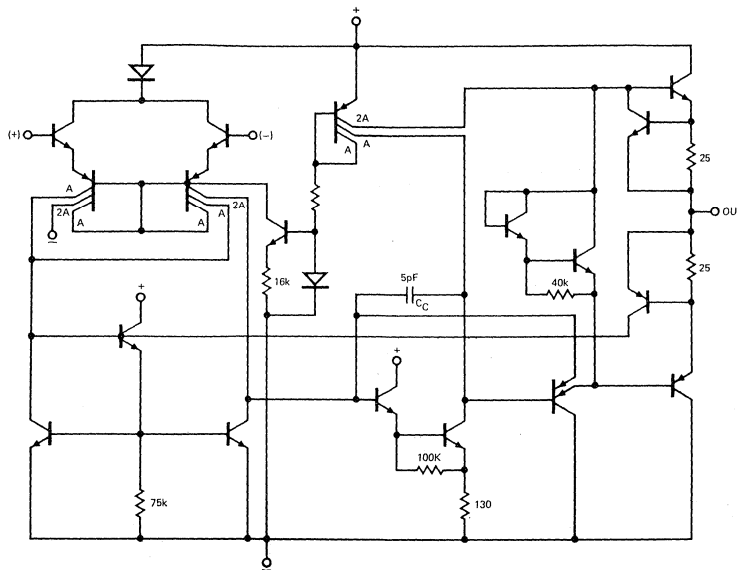


Fig. 29. Circuit for optimized gain cell which has been fabricated in one-fourth the die size of the equivalent  $\mu$ A741.

In a good layout, for example, all resistors are combined into islands with transistors. If this is not possible initially, circuit and device changes are made to allow it. The resulting device geometries within the islands are further modified in shape to allow maximum "packing" of the islands. That is, when the layout is complete, the islands should have shapes which fit together as in a picture puzzle, with no waste of space. Further area reductions can be had by modifying the isolation process to one having minimum spacing between the isolation diffusion and adjacent p-regions.

An example of a gain cell which employs both circuit and layout optimization is shown in Fig. 29. This circuit uses the  $g_m$  reduction technique of Fig. 28(a) which results in a compensation capacitor size of only 5 pF rather than the normal 30 pF. The device achieves a full 1-MHz bandwidth, a 0.67-V/ $\mu$ s slew rate, a gain greater than 100 000, typical offset voltages less than 1 mV, and other characteristics normally associated with an LM107 or  $\mu$ A741. In quad form each amplifier requires an area of only  $23 \times 35$  mils which is one-fourth the size of today's industry standard  $\mu$ A741 (typically  $56 \times 56$  mils). This allows over 8000 possible gain cells to be fabricated on a single 3-inch wafer. Further, it appears quite feasible to fabricate larger arrays of gain cells, with six or eight on a single chip. Only packaging and applications questions need be resolved before pursuing such a step.

#### ACKNOWLEDGMENT

Many important contributions were made in the gain cell and FET/bipolar op amp areas by R. W. Russell. The author gratefully acknowledges his very competent efforts.

#### REFERENCES

- [1] R. J. Widlar, "Monolithic op amp with simplified frequency compensation," *EEE*, vol. 15, pp. 58-63, July 1967. (Note that the LM 101, designed in 1967, by R. J. Widlar was the first op amp to employ what has become the classical topology of Fig. 1.)
- [2] D. Fullagar, "A new high performance monolithic operational amplifier," Fairchild Semiconductor Tech. Paper, 1968.
- [3] R. W. Russell and T. M. Frederiksen, "Automotive and industrial electronic building blocks," *IEEE J. Solid-State Circuits*, vol. SC-7, pp. 446-454, Dec. 1972.
- [4] R. C. Dobkin, "LM118 op amp slews 70 V/ $\mu$ s," *Linear Applications Handbook*, National Semiconductor, Santa Clara, Calif., 1974.
- [5] R. J. Apfel and P. R. Gray, "A monolithic fast settling feed-forward op amp using doublet compression techniques," in *ISSCC Dig. Tech. Papers*, 1974, pp. 134-155.
- [6] R. W. Russell and D. D. Culmer, "Ion implanted JFET-bipolar monolithic analog circuits," in *ISSCC Dig. Tech. Papers*, 1974, pp. 140-141.
- [7] P. R. Gray, "A 15-W monolithic power operational amplifier," *IEEE J. Solid-State Circuits*, vol. SC-7, pp. 474-480, Dec. 1972.
- [8] J. E. Solomon, W. R. Davis, and P. L. Lee, "A self-compensated monolithic op amp with low input current and high slew rate," in *ISSCC Dig. Tech. Papers*, 1969, pp. 14-15.
- [9] B. A. Wooley, S. Y. J. Wong, D. O. Pederson, "A computer-aided evaluation of the 741 amplifier," *IEEE J. Solid-State Circuits*, vol. SC-6, pp. 357-366, Dec. 1971.
- [10] J. E. Solomon and G. R. Wilson, "A highly desensitized, wide-band monolithic amplifier," *IEEE J. Solid-State Circuits*, vol. SC-1, pp. 19-28, Sept. 1966.
- [11] K. R. Stafford, R. A. Blanchard, and P. R. Gray, "A completely monolithic sample/hold amplifier using compatible bipolar and silicon gate FET devices," in *ISSCC Dig. Tech. Papers*, 1974, pp. 190-191.
- [12] J. E. Solomon and R. W. Russell, "Transconductance reduction using multiple collector PNP transistors in an operational amplifier," U.S. Patent 3801923, Mar. 1974. See also, as a general reference:
- [13] P. R. Gray and R. G. Meyer, "Recent advances in monolithic operational amplifier design," *IEEE Trans. Circuits and Syst.*, vol. CAS-21, pp. 317-327, May 1974.

# A Color TV Primer for the E. E.

National Semiconductor  
Appendix B  
Milt Wilcox  
October 1975



A Color TV Primer for the E. E.

## Section 1 – The Color TV Receiver

Let's look at a color TV in terms of signal flow, from antenna to picture tube.

Although the frequencies used will be for the American NTSC system (National Television System Committee), the basic theory also applies to the European PAL system (Phase Alternating Line). Only in the chroma section do the two systems differ significantly.

### RF AND IF SECTIONS

The first part is easy — all signal components received from the antenna pass through a tuner and IF amplifier to the video detector as shown in *Figure 1*.

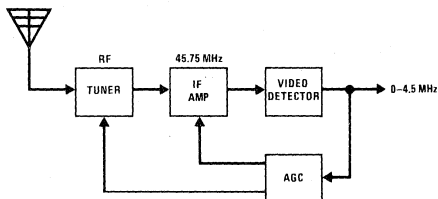


FIGURE 1

The RF signal received ranges in frequency from 55 MHz for channel 2 up to 885 MHz (tuned with the aid of a UHF converter) for channel 83! The tuner has the job of amplifying the desired channel frequency and converting it to an intermediate frequency (IF) of 45.75 MHz. It is then further amplified in the IF amplifier.

The 45.75 MHz signal being amplified is called the video carrier. It is amplitude-modulated (AM) with the picture information, so the video detector must strip this information from the carrier by using some form of envelope detection. So far we could be describing a basic AM radio, except for the signal being received — instead of having audio at the detector output, we have video.

The output level from the video detector is usually around 3 Vp-p. This level must be produced by as little as 10 $\mu$ Vrms on the antenna, which works out to 110 dB conversion gain for the three blocks shown in *Figure 1*. However, the catch is the same TV may have to receive antenna signals of up to 0.5 Vrms, and still produce the same 3 Vp-p at the video detector. For this reason, a TV has a very effective automatic gain control (AGC) system which detects increases in the peak amplitude of the composite video signal and automatically reduces the gain of the tuner and IF amplifier to compensate.

### SIGNAL INFORMATION

The picture you see on a color TV is actually formed by three electron beams, one each for red, blue and green being scanned horizontally and vertically over the screen. As these beams are scanned, their currents are changed to create the light and dark areas on the picture tube face which form the image you view. *Figure 2* shows the video detector output during the time that it takes the electron beams to make one horizontal scan across the screen. The output is actually a combination of four signal components which are required to form a color picture with sound. Let's look at them in turn:

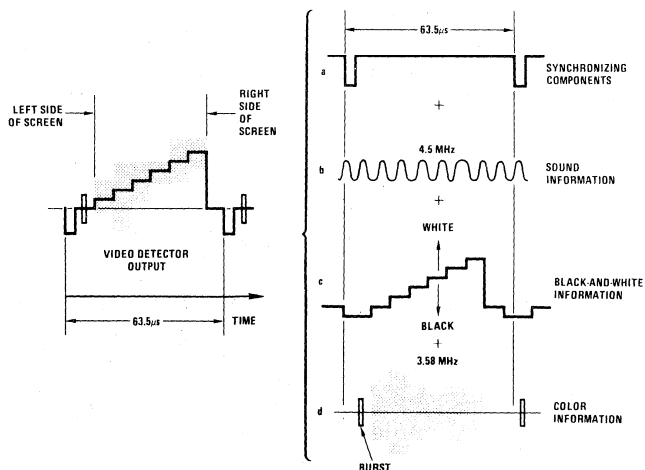


FIGURE 2

### a) Synchronizing Components

The synchronizing information is a series of pulses which tell the horizontal section when to return to the left of the screen to start a new *line*, and the vertical section when to return to the top of the screen to start a new *frame*. In the NTSC system each frame contains 525 lines. This is done by scanning the horizontal at approximately 15,750 lines per second, and the vertical at 30 frames per second (the vertical scan rate is actually 60 Hz, but it takes two trips down the screen to complete one frame). The process of returning to start a new scan is called retrace or flyback.

### b) Sound Information

The sound information is carried in the form of frequency-modulation (FM) of a 4.5 MHz carrier which in turn modulates the video carrier. (That makes the 4.5 MHz a "sub-carrier"). This sub-carrier is very similar to the IF signal in an FM radio. Although the sound sub-carrier is available at the video detector, a separate detector is often used to reduce crosstalk between signal components.

### c) Black-and-White Information (called luminance)

This information determines the instantaneous brightness of the electron beams as they are scanned over the screen. In fact, it is all that is used for the single electron beam in a black-and-white TV set. A negative going video detector detects a luminance signal in which the negative signal extremes correspond to dark areas of the picture and positive signal extremes correspond to bright areas of the picture. Thus the waveform shown in *Figure 2(c)* would produce vertical bars of increasing brightness from left to right. Note that the output is at black during retrace so the electron beams will not be seen. The luminance signal is designated by the letter Y.

### d) Color Information (called chrominance)

The color information (which is ignored in a black-and-white TV) is made up of the red, blue and green signals required to drive the picture tube, *minus* the luminance signal. These "color difference" signals, designated R-Y, B-Y and G-Y, modulate a second subcarrier which has a frequency of 3.58 MHz.

Although the type of modulation used on the sub-carrier is of a complex nature it boils down to a simple result:

1. The instantaneous *phase* of the 3.58 MHz signal determines *what* color will be displayed (called hue or tint).
2. The instantaneous *amplitude* of the 3.58 MHz signal determines *how much* color will be displayed (called saturation).

An obvious question is, the phase and amplitude of the 3.58 MHz signal relative to what? The answer is a short burst of 3.58 MHz (simply called the *burst*) which has constant phase and amplitude. The burst will be used to determine the tint and saturation of the color to be displayed. For the waveform shown in *Figure 2(d)* each bar would have a different saturation.

The four signal components are separated and sent to their respective sections in the TV according to the type of signal. Since the sync pulses are the negative peaks of the composite video signal, a peak-detector circuit called a *sync-separator* is used to separate them. The sound and chroma information is contained in sub-carriers which are separated with 4.5 MHz and 3.58 MHz tuned-circuits respectively. The luminance information combines frequency components from 0-4 MHz and therefore uses wideband dc-coupling.

## SIGNAL PROCESSING

The remaining sections of the Receiver will now be covered.

### Scanning and High Voltage

The sync section is shown in *Figure 3*.

The sync pulses separated in the sync-separator are divided into vertical and horizontal components according to their pulse widths, the vertical sync pulse being a string of wide horizontal sync pulses. When these wide pulses are fed through an integrator, they average to form the vertical sync pulse. The vertical oscillator is "injection-locked" by the vertical sync pulse to initiate vertical retrace at the correct time. The output stage then delivers a ramp of current to the vertical deflection coils to produce vertical scan.

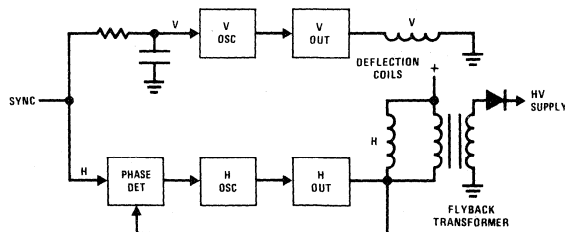


FIGURE 3

The horizontal section uses a different locking system, since horizontal retrace is started *before* the sync pulse is received in order to assure correct centering of the picture. This is done with a phase-locked loop (PLL) in which the oscillator is controlled by a phase detector to insure correct timing between the horizontal sync pulse and the flyback pulse produced by the output stage during horizontal retrace. The horizontal output stage does double duty — besides driving the horizontal deflection coils, it drives the flyback transformer for the picture tube anode high voltage supply. The 25–30 thousand volts dc required is generated either by directly rectifying or by tripling a hv flyback pulse derived from a large turns ratio on the flyback transformer.

#### The Sound Channel

The 4.5 MHz sound-subcarrier signal is amplified and limited in the sound IF to remove undesired amplitude information. The frequency modulation is then detected by an FM detector and applied to the audio amplifier.

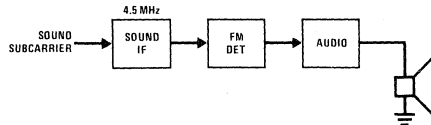


FIGURE 4

Limiting sensitivity for the sound section is typically  $100\mu\text{V}$  and the output power requirement is from 1W to 4W depending on receiver size.

#### Luma Processing

The luminance signal Y must be amplified and delayed some  $0.8\mu\text{s}$  on its way to the picture tube as shown in Figure 5. The delay is required to insure that the black and white information does not arrive at the picture tube before the color information, which is delayed by the comparatively narrow bandwidth of the 3.58 MHz chroma section.

The contrast and brightness controls are also located in the luminance amplifier. The *contrast* control changes the *peak-to-peak* amplitude of the signal, while the *brightness* control changes the *dc* level of the signal.

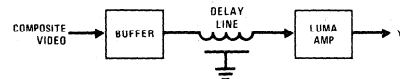


FIGURE 5

#### Chroma Processing

From the signal taken off the 3.58 MHz tuned circuit the chroma section must derive two signals:

- 1) The 3.58 MHz chroma sub-carrier signal of the correct amplitude and
- 2) A continuous 3.58 MHz chroma reference signal of the correct phase relative to the burst.

These two signals, when applied to the chroma demodulator, will produce the desired color difference signals R-Y, B-Y and G-Y. The chroma section is shown in Figure 6.

The first problem is that even though the AGC system holds the peak-to-peak video level constant, the chroma sub-carrier itself can vary in amplitude with transmission, antenna and fine-tuning changes, to name a few. Therefore, the chroma section requires an AGC loop of its own, which is called the Automatic Chroma Control stage, or ACC. This block compares the amplitude of the burst to a reference to keep the chroma output signal constant over a 20 dB input range.

The chroma signal is then gated into two components by a pulse derived from the horizontal section. The chroma sub-carrier (during horizontal scan) is sent to the chroma amplifier in which a gain control varies the saturation of the color picture. If *no* burst was present in the ACC stage, the output of the amplifier is “killed” completely for black and white reception.

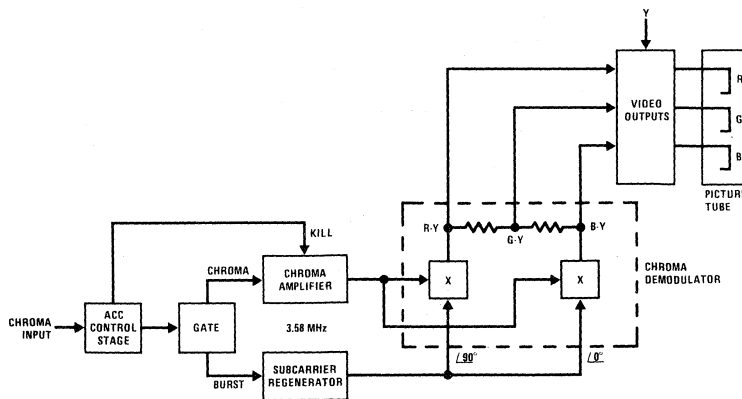


FIGURE 6

The burst (during horizontal retrace) is sent to the sub-carrier regenerator. This is actually a fancy name for a crystal-controlled 3.58 MHz oscillator which is locked to the frequency and phase of the incoming burst by either an injection-lock or phase-lock technique. This forms the reference output, which is passed through a variable phase-shift network to vary the tint of the color picture.

The outputs of the chroma amplifier and sub-carrier regenerator are the signals required by the chroma demodulator, which consists of two synchronous detectors operated in quadrature. What this means is that the reference phase applied to the B-Y detector makes it responsive only to chroma input phases corresponding to blue. The reference applied to the R-Y detector, which is 90° out of phase with the B-Y detector, makes it responsive only to red. The G-Y signal is derived by combining the R-Y and B-Y outputs in the correct ratios.

Finally, the luminance signal Y is added to the chroma difference signals R-Y, B-Y and G-Y to arrive at the desired red, blue and green signals. These signals are further amplified to 100 Vp-p in the video output stage and applied to the appropriate cathodes of the picture tube.

### CONVERGENCE

One other messy, but needed, function remains in a color TV receiver — color convergence. The need for convergence results from the origination of the three electron beams in different locations and the fact that they are being scanned over a flat, instead of round, surface. Therefore, the deflection of each beam must be modified separately such that it lands in the same location as the other beams over the entire face of the picture tube.

A complete block diagram of the color TV receiver is shown for reference in *Figure 7*.

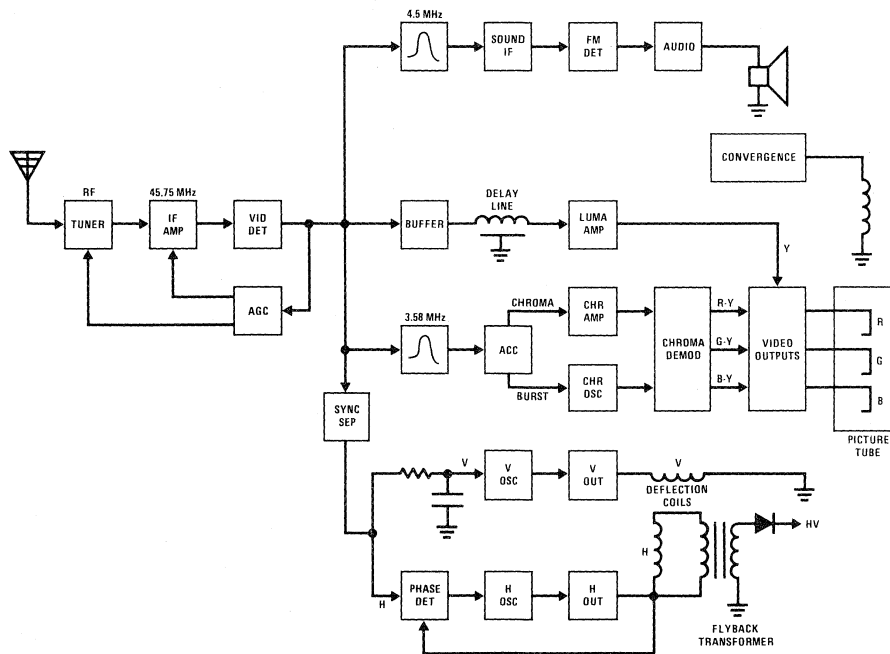


FIGURE 7



## Section 2 – Integrated Circuits in Television

Here we will look at the integrated circuits used in television including a glimpse inside TV ICs.

Every area of the television which does not have too high a frequency or voltage requirement has been integrated at least once, and many are on second and third generation IC's. The only areas that have been "off-limits" to date are the tuner, video outputs, and horizontal/HV output sections.

### RF AND IF SECTIONS

Monolithic circuits have been made to work very well at 45 MHz. The first IC IF systems used 2 chips: one for a 2-stage gain-controlled IF amplifier (Motorola MC1349, 52) and the second for a video detector with gain (Motorola MC1330). The major obstacle to combining these two chips into a single chip has been stability problems due to internal and/or external coupling output to input. However a one chip IF amplifier and video detector is now widely used in Europe (Telefunken TDA 440). The AGC system is also often included in these chips. Another IF function used in most color TV receivers today is automatic fine tuning (AFT) which keeps the tuner correctly tuned to the IF frequency (LM3064 type).

The first chip to incorporate all of the above functions into a single chip is the National LM1807. The chip uses a phase-locked loop to tune the tuner to the IF frequency set by a local oscillator on the chip. This concept is new to TV and is generating a lot of interest.

Rapid progress is also being made in periphery circuits to tuners. Present IC tuning systems control the voltage on a varactor in the tuner to tune the desired channel. However, new systems will actually "synthesize" the tuner local oscillator frequency for each channel.

### SCANNING

The deflection area is one of the last to be integrated. While only low-level horizontal circuits have been integrated, vertical drivers and even output stages have been attempted. Current IC's include the Motorola MC1391 or Philips TBA 920 for horizontal and the SGS TDS 1270 for vertical.

In the standard U.S. television system, the vertical and horizontal scanning frequencies are related by the formula  $f_v = 2f_h/525$ . The National DM8890 makes use of this fact by dividing down a horizontal signal to generate vertical timing, thus eliminating the need for a vertical hold control. Although previous combined vertical/horizontal chips have been unsuccessful, the digital approach holds much promise and TI has announced a combined chip using  $1^2L$ .

### THE SOUND CHANNEL

The LM3065 type sound IF/FM Detector is currently used in most TV receivers along with a class B discrete or IC audio amplifier. However, virtually every IC manufacturer has announced a one chip "sound system"

combining the IF, detector, and audio amplifier. National's entry is the LM1808 which has been well received.

### LUMA PROCESSING

Standard IC's have not been developed for the Luma area because of questionable economics. Instead, most of the efforts so far have been custom, with different IC's being used by Zenith, Sylvania and several European TV companies.

### CHROMA PROCESSING

The first IC in TV was the chroma demodulator. Today every color TV has one, usually an LM746 or LM1828 type. In one variation the luminance signal is added to the color difference outputs on the chip (Motorola MC1324).

The chroma amplifier and subcarrier regenerator sections have been integrated using a phase-locked loop system with two chips (LM3070 and LM3071 types) and an injection-locked system with one chip (Motorola MC1398). Both of these systems are widely used. Second generation systems which do the phase-locked system with one chip (RCA CA3126 or Motorola MC1399) are gaining acceptance. All of these systems can be used with the above-mentioned demodulators.

Thus, so far the chroma section takes a minimum of two chips, including the demodulator. When will the demodulator be combined with the rest of the system for a true one-chip chroma? Hitachi has just introduced the first practical attempt and others are sure to follow.

### WHAT'S A JUNGLE?

A "jungle" IC is a combination of miscellaneous TV functions on one chip. For example, the Zenith jungle (LM1845 type) does the sync-separator and AGC functions. The term is also sometimes applied to deflection IC's which include other functions.

### INSIDE TV IC's

Next to the basic differential amplifier, the most widely used linear circuits in TV IC's are probably the current-sharing gain control stage and the linear multiplier.

### Gain Control

The current-sharing gain control stage is so named because the input current is shared between two outputs depending on the dc control voltage  $V_C$ . For the circuit shown in *Figure 8*, the small signal gain at room temperature is given by:

$$A = \frac{\Delta V_{OUT}}{\Delta V_{IN}} \approx \frac{R_L/R_o}{1 + \exp\left(\frac{V_C \text{ in mV}}{26}\right)}$$

As  $V_C$  is increased, the circuit acts as a logarithmic attenuator, yielding a gain reduction of approximately 20 dB for each 60 mV of applied voltage. This same basic gain control stage is used in IF AGC and chroma ACC circuits, as well as for volume, contrast, and chroma controls.

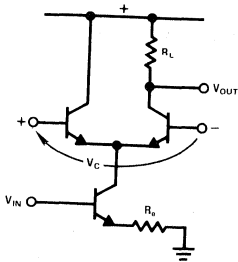


FIGURE 8

### Multiplier

The multiplier is widely used in television IC's for amplitude, phase, and frequency detection. Figure 9 shows a typical configuration in which the bottom pair is degenerated for linear operation while the top quad is switched. If  $V_a(t)$  is an amplitude modulated carrier  $F_m(t)\cos \omega t$  and  $v_b(t)$  is a square wave of the same frequency  $\omega$  and relative phase  $\phi$ , then the filtered output is given by:

$$V_{OUT} \cong \frac{2}{\pi} \frac{R_L}{R_E} F_m(t) \cos \phi$$

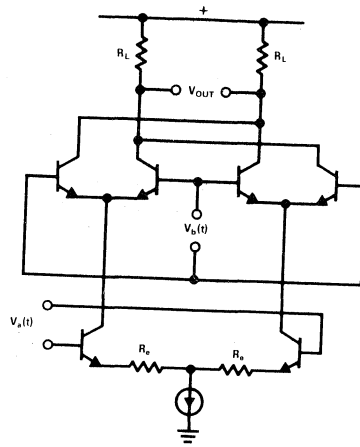


FIGURE 9

Thus the output depends on the amplitude of  $V_a$  and the relative phase  $\phi$  between  $V_a$  and  $V_b$ .

If  $\phi$  is made 0 degrees so  $\cos \phi$  is 1, then the multiplier acts as an amplitude detector and can be used to detect the video modulation on the IF carrier. Note that around 0 degrees  $\cos \phi$  changes very little with phase. To use the multiplier as a phase or frequency detector,  $V_a(t)$  is limited to remove amplitude information and  $\phi$  is centered at 90 degrees where  $\cos \phi$  produces the largest change in output for a given change in phase. This operation mode is used for chroma burst phase detectors and sound FM detectors. Both the amplitude and phase sensitive properties of the multiplier are used in chroma demodulators.

# V/F Converter ICs Handle Frequency-to-Voltage Needs

National Semiconductor  
Appendix C  
Robert A. Pease  
August 1980



V/F Converter ICs Handle Frequency-to-Voltage Needs

Simplify your F/V converter designs with versatile V/F ICs. Starting with a basic converter circuit, you can modify it to meet almost any application requirement. You can spare yourself some hard labor when designing frequency-to-voltage (F/V) converters by using a voltage-to-frequency IC in your designs. These ICs form the basis of a series of accurate, yet economical, F/V converters suiting a variety of applications.

Figure 1 shows an LM331 IC (or LM131 for the military temperature range) in a basic F/V converter configuration (sometimes termed a stand-alone converter because it requires no op amps or other active devices other than the IC). (Comparable V/F ICs, such as the RM4151, can take advantage of this and other circuits described in this article, although they might not always be pin-for-pin compatible.)

This circuit accepts a pulse-train or square wave input amplitude of 3V or greater. The 470 pF coupling capacitor suits negative-going input pulses between 80  $\mu$ s and 1.5  $\mu$ s, as well as accommodating square waves or positive-going pulses (so long as the interval between pulses is at least 10  $\mu$ s).

### IC Handles the Hard Part

The LM331 detects an input-signal change by sensing when pin 6 goes negative relative to the threshold voltage at pin 7, which is nominally biased 2V lower than the supply voltage. When a signal change occurs, the LM331's input comparator sets an internal latch and initiates a timing cycle. During this cycle, a current equal to  $V_{REF}/R_S$

flows out of pin 1 for a time  $t = 1.1 R_T C$ . The 1  $\mu$ F capacitor filters this pulsating current from pin 1, and the current's average value flows through load resistor  $R_L$ . As a result, for a 10 kHz input, the circuit outputs 10  $V_{DC}$  across  $R_L$  with good (0.06% typical) nonlinearity.

Two problems remain, however: the output at V1 includes about 13 mVp-p ripple, and it also lags 0.1 second behind an input frequency step change, settling to 0.1% of full-scale in about 0.6 second. This ripple and slow response represent an inherent tradeoff that applies to almost every F/V converter.

### The Art of Compromise

Increasing the filter capacitor's value reduces ripple but also increases response time. Conversely, lowering the filter capacitor's value improves response time at the expense of larger ripple. In some cases, adding an active filter results in faster response and less ripple for high input frequencies.

Although the circuit specifies a 15V power supply, you can use any regulated supply between 4  $V_{DC}$  and 40  $V_{DC}$ . The output voltage can extend to within 3  $V_{DC}$  of the supply voltage, so choose  $R_L$  to maintain that output range.

Adding a 200 k $\Omega$ /0.1  $\mu$ F postfilter to the circuit slows the response slightly, but it also reduces ripple to less than 1 mVp-p for frequencies from 200 Hz to 10 kHz. The reduction in ripple achieved by adding this passive filter, while not as good as that obtainable using an active filter, could suffice in some applications.

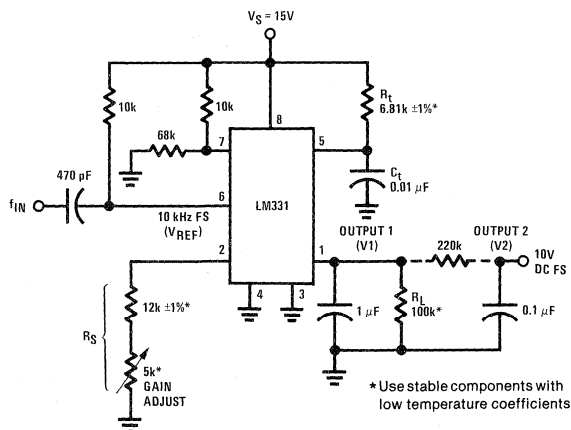


FIGURE 1. A Simple Stand-Alone F/V Converter Forms the Basis for Many Other Converter-Circuit Configurations




## Dealing with F/V Converter Ripple

Voltage ripple on the output of F/V converters can present a problem, and the chart shown in *Figure a* indicates exactly how big a problem it is. A simple, slow, RC filter exhibits low ripple at all frequencies. Two-pole filters offer the lowest ripple at high frequencies and provide a 30-times-faster step response than RC devices.

To reduce a circuit's ripple at moderate frequencies, however, you can cascade a second active-filter stage on the F/V converter's output. That circuit's response also appears in *Figure a* and shows a significant improvement in low-ripple bandwidth over the single-active-filter configuration, with only a 30% degradation of step response.

*Figures b* and *c* show filter circuits suitable for cascading. The inverting filter in *Figure b* requires closely matched resistors with a low TC over their temperature range for

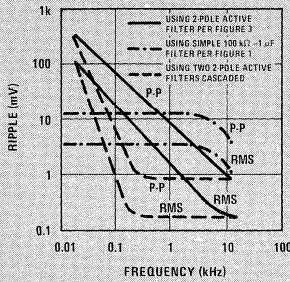

**FIGURE a.** Output-Ripple Performance of Several Different F/V Converter Configurations Illustrates the Effect of Voltage Ripple

best accuracy. For lowest DC error, choose  $R_5 = R_2 + (R_{IN} | R_F)$ . This circuit's response is

$$-V_{OUT}/V_{IN} = n/(1 + (R_F + R_2 + nR_2)C_4p + R_F R_2 C_3 C_4 p^2),$$


where  $n = \text{DC gain}$ . If  $R_{IN} = R_F$  and  $n = 1$ ,

$$-V_{OUT}/V_{IN} = 1/(1 + (R_F + 2R_2) C_4 p + R_F R_2 C_3 C_4 p^2).$$


The circuit shown in *Figure c* does not require precision passive components, but for best accuracy, choosing an A1 with a high CMRR is critical. An LM308A op amp's 96 dB minimum CMRR suits this circuit well, but an LM358B's 85 dB typical figure also proves adequate for many applications. Circuit response is

$$V_{OUT}/V_{IN} = 1/(1 + (R_1 + R_2) C_2 p + R_1 R_2 C_1 C_2 p^2).$$

For best results, choose  $R_3 = R_1 + R_2$ .

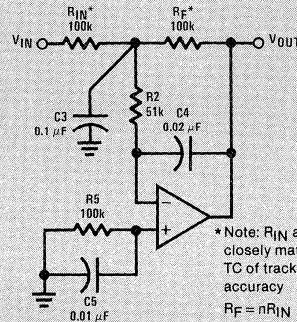

**FIGURE b.** You Can Cascade This 2-Pole Inverting Filter onto an F/V Converter's Output

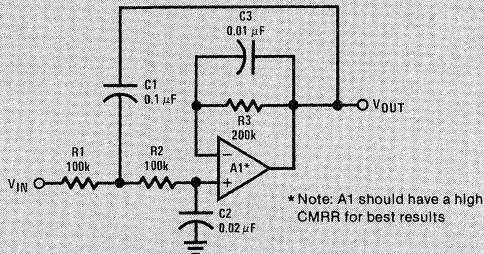

**FIGURE c.** This 2-Pole Noninverting Filter Suits Cascade Requirements on F/V Converter Outputs

## Components Determine Response

The specific response of the circuit in *Figure 3* is

$$V_{OUT}/I_{OUT} = R_L/(1 + (R_L + R_2)C_2p + R_L R_2 C_1 C_2 C_2 p^2).$$

Making C2 relatively large eliminates overshoot and sine peaking. Alternatively, making C2 a suitable fraction of C1 (as is done in *Figure 3*) produces both a sine response with 0 dB to 1 dB of peaking and a quick real-time response having only 10% to 30% overshoot for a step response. By maintaining *Figure 3*'s ratio of C1:C2 and R2:R<sub>L</sub>, you can adapt its 2-pole filter to a wide frequency range without tedious computations.

This filter settles to within 1% of a 5V step's final value in about 20 ms. By contrast, the circuit with the simple RC

filter shown in *Figure 1* takes about 900 ms to achieve the same response, yet offers no less ripple than *Figure 3*'s op amp approach.

As for the other components in the 2-pole filter, any capacitance between 100 pF and 0.05 μF suits C3 because it serves only as a bypass for the 200 kΩ resistor. C4 helps reduce output ripple in single positive power-supply systems when V<sub>OUT</sub> approaches so close to ground that the op amp's output impedance suffers. In this circuit, using a tantalum capacitor of between 0.1 μF and 2.2 μF for C4 usually helps keep the filter's output much quieter without degrading the op amp's stability.

## Avoid Low-Leakage Limitations


Note that in most ordinary applications, this 2-pole filter performs as well with 0.1  $\mu\text{F}$  and 0.02  $\mu\text{F}$  capacitors as the passive filter in *Figure 1* does with 1  $\mu\text{F}$ . Thus, if you require a 100 Hz F/V converter, the circuit in *Figure 3* furnishes good filtering with  $C_1 = 10 \mu\text{F}$  and  $C_2 = 2 \mu\text{F}$ , and eliminates the 100  $\mu\text{F}$  low-leakage capacitor needed in a passive filter.

## Compensating for Temperature Coefficients

F/V converters often encounter temperature-related problems usually resulting from the temperature coefficients of passive components. Following some simple design and manufacturing guidelines can help immunize your circuits against loss of accuracy when the temperature changes.

Capacitors fabricated from Teflon or polystyrene usually exhibit a TC of  $-110 \pm 30 \text{ ppm}/^\circ\text{C}$ . When you use such a component for the timing capacitor in an F/V converter (such as  $C_1$  in the *figure*) the circuit's output voltage—or the gain in terms of volts per kilohertz—also exhibits a  $-110 \text{ ppm}/^\circ\text{C}$  TC.

But the resistor-diode network ( $R_X$ , D1, D2) connected from pin 2 to ground in the *figure* can cancel the effect of the timing capacitor's large TC. When  $R_X = 240 \text{ k}\Omega$ , the current flowing through pin 1 will then have an overall TC of 110  $\text{ppm}/^\circ\text{C}$ , effectively canceling a polystyrene timing capacitor's TC to a first approximation. Thus, you needn't find a zero-TC capacitor for  $C_1$ , so long as its temperature coefficient is stable and well established. As an additional advantage, the resistor-diode network nearly compensates to zero the TC of the rest of the circuit.

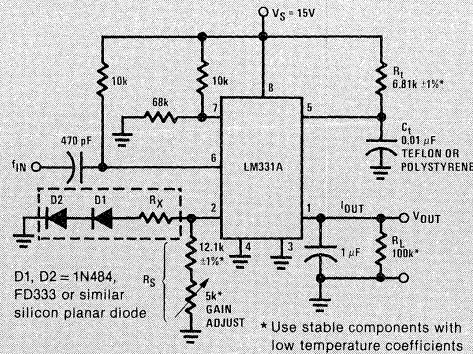

## Two Diodes and a Resistor Help Decrease an F/V Converter's Temperature Coefficient

### Bake it for a While

After the circuit has been built and checked out at room temperature, a brief oven test will indicate the sign and the size of the TC for the complete F/V converter. Then you can add resistance in series with  $R_X$ , or add conductance in parallel with it, to greatly diminish the TC previously observed and yield a complete circuit with a lower TC than you could obtain simply by buying low TC parts.

For example, if the circuit increases its full-scale output by 0.1% per  $30^\circ\text{C}$  (33  $\text{ppm}/^\circ\text{C}$ ) during the oven test, adding 120  $\text{k}\Omega$  in series with  $R_X = 240 \text{ k}\Omega$  cancels the temperature-caused deviation. Or, if the full-scale output decreases by  $-0.04\%$  per  $20^\circ\text{C}$  ( $-20 \text{ ppm}/^\circ\text{C}$ ), just add 1.2  $\text{M}\Omega$  in parallel with  $R_X$ .

Note also that because  $C_1$  always has zero DC voltage across it, you can use a tantalum or aluminum electrolytic capacitor for  $C_1$  with no leakage-related problems;  $C_2$ , however, must be a low-leakage type. At room temperature, typical 1  $\mu\text{F}$  tantalum components allow only a few nanoamperes of leakage, but leakage this low usually cannot be guaranteed.

Note that to allow trimming in both directions, you must start with a finite *fixed* TC (such as the  $-110 \text{ ppm}/^\circ\text{C}$  of  $C_1$ ), which then nominally cancels out by the addition of a finite *adjustable* TC. Only by using this procedure can you compensate for whatever polarity of TC is found by the oven test.

You can utilize this technique to obtain TCs as low as 20  $\text{ppm}/^\circ\text{C}$ , or perhaps even 10  $\text{ppm}/^\circ\text{C}$ , if you take a few passes to zero-in on the best value for  $R_X$ . For optimum results, consider the following guidelines:

- Use a good capacitor for  $C_1$ ; the cheapest polystyrene capacitors can shift value by 0.05% or more per temperature cycle. In that case, you would not be able to distinguish the actual temperature sensitivity from the hysteresis, and you would also never achieve a stable circuit.
- After soldering, bake or temperature-cycle the circuit (at a temperature not exceeding  $75^\circ\text{C}$  in the case of polystyrene) for a few hours to stabilize all components and to relieve the strains of soldering.
- Do not rush the trimming. Recheck the room temperature value before *and* after you take the high temperature data to ensure a reasonably low hysteresis per cycle.
- Do not expect a perfect TC at  $-25^\circ\text{C}$  if you trim for  $\pm 5 \text{ ppm}/^\circ\text{C}$  at temperatures from  $-25^\circ\text{C}$  to  $60^\circ\text{C}$ . None of the components in the *figure's* circuit offer linearity much better than 5  $\text{ppm}/^\circ\text{C}$  or 10  $\text{ppm}/^\circ\text{C}$  cold, if trimmed for a zero TC at warm temperatures. Even so, using these techniques you can obtain a data converter with better than 0.02% accuracy and 0.003% linearity, for a  $\pm 20^\circ\text{C}$  range around room temperature.
- Start out the trimming with  $R_X$  installed and its value near the design-center value (e.g., 240  $\text{k}\Omega$  or 270  $\text{k}\Omega$ ), so you will be reasonably close to zero TC; you will usually find the process slower if you start without any resistor, because the trimming converges more slowly.
- If you change  $R_X$  from 240  $\text{k}\Omega$  to 220  $\text{k}\Omega$ , do not pull out the 240  $\text{k}\Omega$  part and put in a new 220  $\text{k}\Omega$  resistor—you will get much more consistent results by adding a 2.4  $\text{M}\Omega$  resistor in parallel. The same admonition holds true for adding resistance in series with  $R_X$ .
- Use reasonably stable components. If you use an LM331A ( $\pm 50 \text{ ppm}/^\circ\text{C}$  maximum) and RN55D film resistors (each  $\pm 100 \text{ ppm}/^\circ\text{C}$ ) for  $R_L$ ,  $R_T$  and  $R_S$ , you probably won't be able to trim out the resulting  $\pm 350 \text{ ppm}/^\circ\text{C}$  worst-case TC. Resistors with a TC specification of 25  $\text{ppm}/^\circ\text{C}$  usually work well. Finally, use the same resistor value (e.g., 12.1  $\text{k}\Omega \pm 1\%$  for both  $R_S$  and  $R_T$ ) when these resistors come from the same manufacturer's batch, their TC tracking will usually rate at better than 20  $\text{ppm}/^\circ\text{C}$ .

Whenever an op amp is used as a buffer (as in *Figure 3*), its offset voltage and current ( $\pm 7.5$  mV maximum and  $\pm 100$  nA, respectively, for most inexpensive devices) can cause a  $\pm 17.5$  mV worst-case output offset. If both plus and minus supplies are available, however, you can easily provide a symmetrical offset adjustment. With only one supply, you can add a small positive current to each op amp input and also trim one of the inputs.

### Need a Negative Output?

If your F/V converter application requires a negative output voltage, the circuit shown in *Figure 4* provides a solution with excellent linearity ( $\pm 0.003\%$  typical,  $\pm 0.01\%$  maximum). And because pin 1 of the LM331 always remains at  $0 V_{DC}$ , this circuit needs no cascode transistor. (Note, however, that while the circuit's nonlinearity error is negligible, its ripple is not.)

The circuit in *Figure 4* offers a significant advantage over some other designs because the offset adjust voltage derives from the stable  $1.9 V_{DC}$  reference voltage at pin 2 of the LM331; thus any supply voltage shifts cause no output shifts. The offset pot can have any value between  $200$  k $\Omega$  and  $2$  M $\Omega$ .

An optional bypass capacitor (C2) connected from the op amp's positive input to ground prevents output noise arising from stray noise pickup at that point; the capacitance value is not critical.

### A Familiar Response

The circuit in *Figure 4* exhibits the same 2-pole response—with heavy output ripple attenuation—as the noninverting filter in *Figure 3*. Specifically,

$$V_{OUT}/I_{OUT} = R_F / (1 + (R_4 + R_F)C_4p + R_4R_F C_3C_4p^2).$$

Here also,  $R_5 = R_4 + R_F = 200$  k $\Omega$  provides the best bias current compensation.

The LM331 can handle frequencies up to  $100$  kHz by utilizing smaller-value capacitors as shown in *Figure 5*. This circuit increases the current at pin 2 to facilitate high-speed switching, but, despite these speed-ups, the LM331's  $500$  ppm/ $^{\circ}C$  TC at  $100$  kHz causes problems because of switching speed shifts resulting from temperature changes.

To compensate for the device's positive TC, the LM334 temperature sensor feeds pin 2 a current that decreases linearly with temperature and provides a low overall temperature coefficient. An  $R_y$  value of  $30$  k $\Omega$  provides first-order compensation, but you can trim it higher or lower if you need more precise TC correction.


### Detect Frequencies Accurately

Using an F/V converter combined with a comparator as a frequency detector is an obvious application for these devices. But when the F/V converter is utilized in this way, its output ripple hampers accurate frequency detection, and the slow filter frequency response causes delays.

If a quick response is not important, though, you can effectively utilize an LM331-based F/V converter to feed one or more comparators, as shown in *Figure 6*. For an input frequency drop from  $1.1$  kHz to  $0.5$  kHz, the converter's output responds within about  $20$  ms. When the input falls from  $9$  kHz to  $0.9$  kHz, however, the output responds only after a  $600$  ms lag, so utilize this circuit only in applications that can tolerate F/V circuits' inherent delays and ripples.

### Author's Biography

Bob Pease is a staff scientist in the Advanced Linear Integrated Circuit Group at National Semiconductor Corp., Santa Clara, CA. Holder of four patents, he earned a BSEE from MIT. Bob lists tracking abandoned railroad roadbeds and designing V/F converters as hobbies.

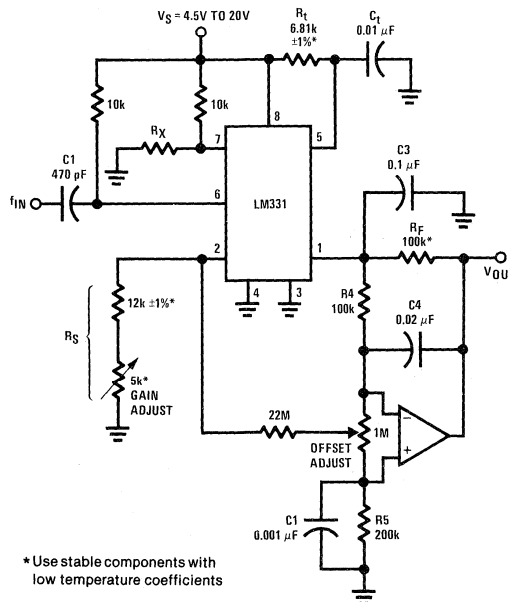

**FIGURE 4.** In This F/V Circuit, the Output-Buffer Op Amp Derives its Offset Voltage from the Precision Voltage Source at Pin 2 of the LM331

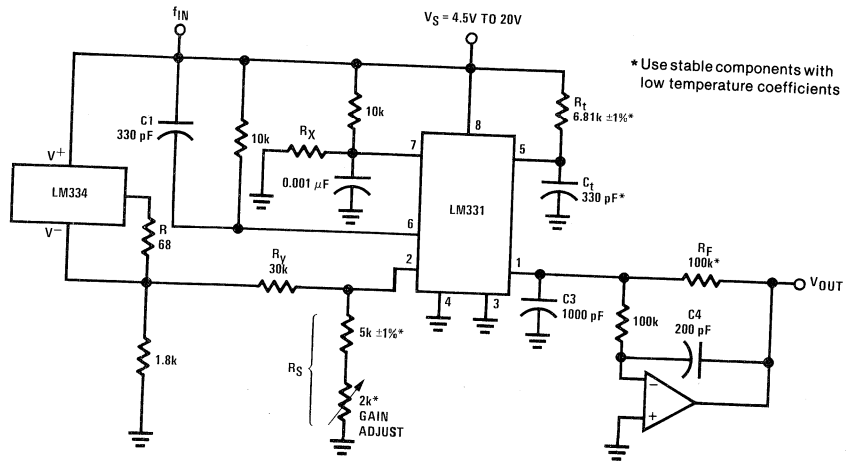


FIGURE 5. An LM334 Temperature Sensor Compensates for the F/V Circuit's Temperature Coefficient

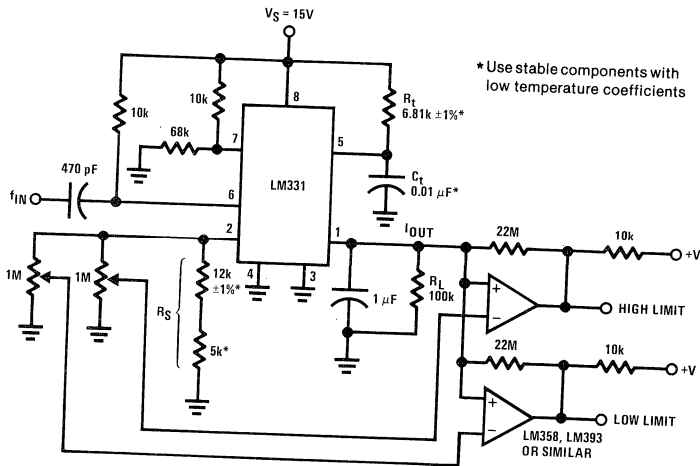


FIGURE 6. Combining a V/F IC with Two Comparators Produces a Slow-Response Frequency Detector



# Versatile Monolithic V/Fs Can Compute as Well as Convert with High Accuracy

National Semiconductor  
Appendix D  
Robert A. Pease  
August 1980



Versatile Monolithic V/Fs Can Compute as Well as Convert with High Accuracy

The best of the monolithic voltage-to-frequency (V/F) converters have performance that's so good it equals or exceeds that of modular types. Some of these ICs can be designed into quite a variety of circuits because they're notably versatile. Along with versatility and high performance come the advantages that are characteristic of all V/F converters, including good linearity, excellent resolution, wide dynamic range, and an output signal that's easy to transmit as well as couple through an isolator.

One of the recently introduced monolithic types, the LM131, has both high performance and a design that's rather flexible. For instance, it can compute and convert at the same time; the computation is a part of the conversion. Among other functions, it can provide the product, ratio and square root of analog inputs.

This IC has an internal reference for its conversion circuitry that's also brought out to a pin, so it's available to external circuits associated with the converter. Not surprisingly, it turns out that any deviations of the reference, due to process variations and temperature changes have equal and opposite effects on the scale factors of the converter and the external circuitry. (This presumes, of course, that the scale factor of the external circuitry is a linear function of voltage.)

## Precision Relaxation Oscillator


Before looking at some applications, quickly take a look at the basic circuit of an LM131 V/F converter (*Figure 1*). Basically, this IC, like any V/F converter, is a precision

relaxation oscillator that generates a frequency linearly proportional to the input voltage. As might be expected, the circuit has a capacitor,  $C_L$ , with a sawtooth voltage on it. Generally speaking, the circuit is a feedback loop that keeps this capacitor charged to a voltage very slightly higher than the input voltage,  $V_{IN}$ . If  $V_{IN}$  is high,  $C_L$  discharges relatively quickly through  $R_L$ , and the circuit generates a high frequency. If  $V_{IN}$  is low,  $C_L$  discharges slowly, and the converter puts out a low frequency.

When  $C_L$  discharges to a voltage equal to the input, the comparator triggers the one-shot. The one-shot closes the current switch and also turns on the output transistor. With the switch closed, current from the current source recharges  $C_L$  to a voltage somewhat higher than the input. Charging continues for a period determined by  $R_T$  and  $C_T$ . At the end of this period, the one-shot returns to its quiescent state and  $C_L$  resumes discharging.

Resistor  $R_S$  sets the amount of current put out by the current source. In fact, the current in pin 1, with the switch on, is identical to the current in pin 2. The latter pin is at a constant voltage (nominally 1.90V), so a given resistor value can set the operating currents. When connected to a high impedance buffer, this pin provides a stable reference for external circuits.


The open-collector output at pin 3 permits the output swing to be different from the converter's supply voltage, if the load circuit requires. The supplies don't have to be separate, however, and both the converter and its load can use the same voltage.

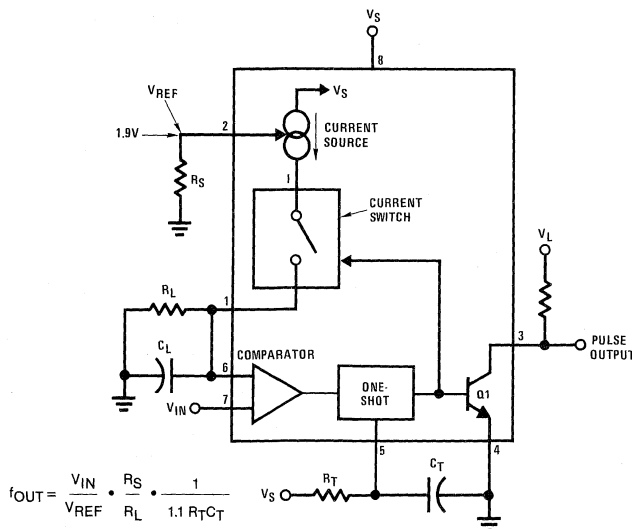

**FIGURE 1.** A voltage-to-frequency converter such as this is a relaxation oscillator with a frequency proportional to the input voltage. Current pulses keep  $C_L$ 's average voltage slightly greater than the input voltage.

## Steady as She Goes

By far the simplest of the circuits that make use of the reference output voltage from the LM131 is one that simply ties this output pin right back to the signal input. This connection is just a V/F converter with a constant input, which makes it a constant-frequency oscillator. Even with this simple circuit (Figure 2), variations in the reference voltage have two opposite effects that cancel each other out, so the circuit is particularly stable. In this type of circuit, the temperature-dependent internal delays tend to cancel as well, which isn't true of relaxation oscillators based on op amps or comparators.

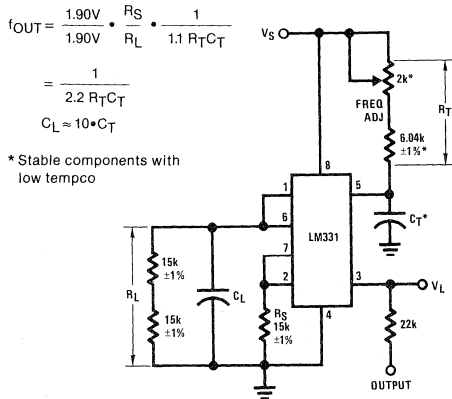

**FIGURE 2.** A V/F converter is a stable-frequency oscillator if its input is connected to its reference output. If the reference voltage changes, the effects of the change cancel out, so the frequency doesn't change. With low tempco components for  $R_T$  and  $C_T$ , frequency stability vs temperature can be as good as  $\pm 25$  ppm/°C.

Resistors  $R_L$  and  $R_S$  are best taken from the same batch. ( $R_L$  must be larger than  $R_S$ , so it's made up of two

resistors.) By doing this, the tempco tracking, which is the critical parameter, is five to ten times better than it would be if  $R_L$  were a single 30.1 kΩ resistor.

Although the reference output, pin 2, can't be loaded without affecting the converter's sensitivity, the comparator input, pin 7, has a high impedance so this connection does no harm.

Frequency stability is typically  $\pm 25$  ppm/°C, even with an LM331, which as a V/F converter is specified only to 150 ppm/°C maximum. From 20 Hz to 20 kHz, stability is excellent, and the circuit can generate frequencies up to 120 kHz.


Although the simplest way of using the reference output is to tie it back to the input, the reference can also be buffered and amplified to supply such external circuitry as a resistive transducer, which might be a strain gauge or a pot (Figure 3). As in the stable oscillator already described, deviations of the internal reference voltage from the ideal cause the transducer's and the converter's sensitivities to change equally in opposite directions, so the effects cancel.

In this circuit, op amp A2 buffers and amplifies the constant voltage at pin 2 of the converter to provide the 5V excitation for the strain gauge. Amplifier A1, connected as an instrumentation amplifier, raises the output of the strain gauge to a usable level while rejecting common-mode pickup.

A potentiometer-type transducer works just as well with this circuit. Its wiper output takes the place of A1's output as shown at the X.

The reference terminal is both a constant voltage output and a current programming input. So far, it's been shown simply with one or two resistors going to ground. It is, however, a full-fledged signal input that accepts a signal from a current source quite well.

This extra input is what enables the LM131 to compute while converting. For instance, it will convert the ratio of two voltages to a frequency proportional to the ratio

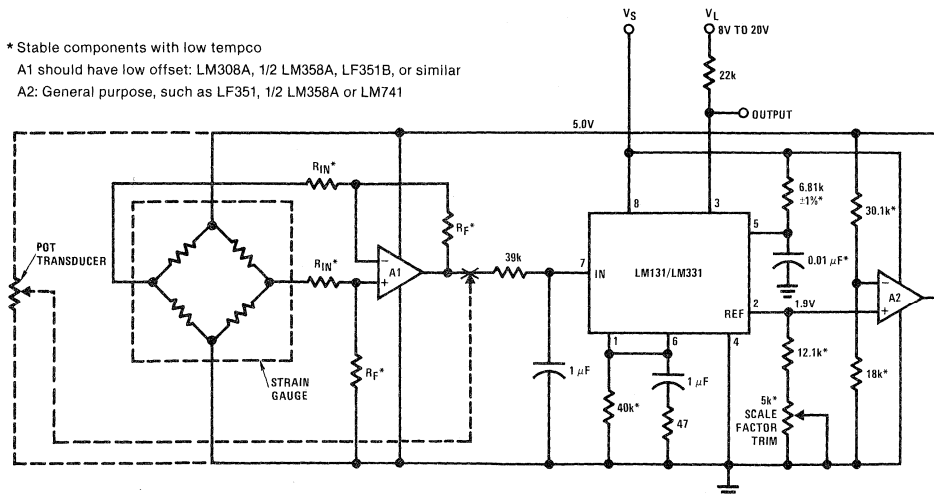


**FIGURE 3.** In this strain-to-frequency converter, the converter's reference excites the strain gauge (or the optional pot) through buffer amp A2. This makes the circuit insensitive to changes in the reference voltage.

(Figure 4). The circuit is still a V/F converter, but has two signal inputs, both of them going to rather unorthodox places at that. The inputs, shown as voltages, are converted to currents by two current pumps (voltage-to-current converters). Of course, if currents of the proper ranges are available, the current pumps aren't needed. The left current pump, which includes Q1 and A1, determines how fast capacitor  $C_L$  discharges between output pulses. The other pump sets the current in the reference circuit to control the amount of recharge current when the one-shot fires. Tying the comparator input, pin 7, to the reference pin sets the comparator's trip point at a constant voltage.

\* Stable components with low tempco


A1, A2 should have low offset and low bias current: LM351B, LM358A, LF353B, or similar  
Q1, Q2: 2N3565, 2N2484, or similar high  $\beta$

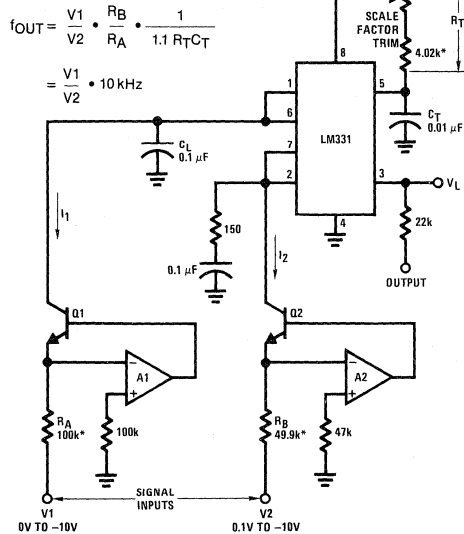


**FIGURE 4.** This circuit converts the ratio of two voltages to an equivalent frequency without a separate analog divider. Full-scale output is 15 kHz. The two op amp circuits convert the inputs to proportional currents.

To get an idea of how the circuit works, consider first the effect of, for instance, tripling the input voltage,  $V_1$ . This makes  $C_L$  discharge to the comparator trip point three times as fast, so the frequency triples. Next, consider a given change, such as doubling the voltage at the other input,  $V_2$ . This doubles the recharge current to  $C_L$  during the fixed-width output pulse, which means  $C_L$ 's voltage increases twice as much during recharging. Since the discharge into Q1 is linear (for  $V_1$  constant), it takes twice as long for  $C_L$  to discharge—the frequency becomes half of what it was before.

Although the current pumps in Figure 4 must have negative inputs, rearranging the op amps according to Figure 5 makes them accept positive inputs instead. Trimming out the offset in the op amp gives the ratio converter better linearity and accuracy. The trim circuit in Figure 5a needs stable positive and negative supplies for the offset trimmer, while the one in Figure 5b needs only a stable positive supply. Unmarked components in Figure 5b are the same as in Figure 5a.

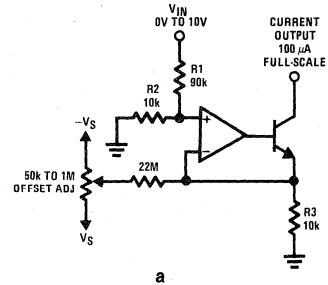


R1, R2, R3: Stable components with low tempco  
Q1:  $\beta \geq 330$

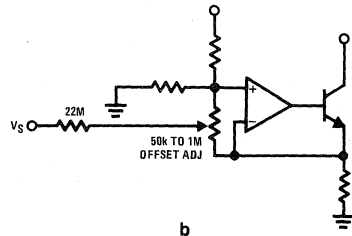

**FIGURE 5.** These current pumps adapt the converter circuits in Figures 4 and 6 to positive input voltages. Optional offset trimming improves linearity and accuracy, especially with input signals that have a wide dynamic range.
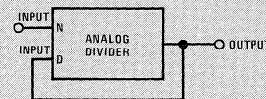
### Computing Square Roots Implicitly

An analog divider computes the square root of a signal when the signal is fed to the divider's numerator input, and the output is fed back to the divider's denominator input.




$$\text{OUT} = \frac{\text{IN}}{\text{OUT}}$$

$$\text{OUT}^2 = \text{IN}$$

$$\text{OUT} = \sqrt{\text{IN}}$$

This type of computation is called implicit, because the end result of the computation is only implied, not explicitly stated by the equation that defines the computation.

In the implicit square root computing loop described in the text, a V/F converter serves as a divider. Since it's a converter, its inputs are voltages (or currents), but its output is a frequency. To connect its output back to one of its inputs so it will compute a square root means that its output frequency must be converted back to a voltage. This is taken care of by the frequency-to-voltage converter.

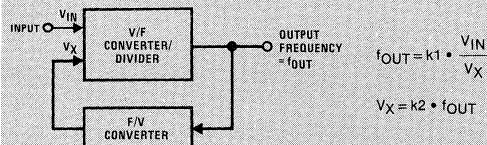

Doing some algebraic substitution shows that:

$$f_{\text{OUT}} = k_3 \cdot \sqrt{V_{\text{IN}}}$$

where

$$k_3 = \sqrt{k_1/k_2}$$

Note that the full-scale range of the current pumps can be changed by varying the value of the input resistor(s). If either of these pump circuits is used with a single positive supply, the op amp should be a type such as 1/2 LM358 or 1/4 LM324, which has a common-mode range that includes the negative-supply bus.

### It'll Take Reciprocals

Taking the ratio of two inputs—in other words, doing division—is only one of the mathematical operations that can be combined with converting. Another one is a special case of division, which is taking reciprocals. In this instance, the numerator ( $V_1$  in Figure 4) is held constant, and the denominator,  $V_2$ , changes over a wide range such as one or two decades. In this case, since the frequency is the reciprocal of the input, the period of the output is proportional to the input. When operated this way, the  $V_2$  current pump should have an offset trimmer. A constant current circuit is still needed to discharge capacitor  $C_L$ .

Nonlinearity (that is, deviation from the ideal law) with an LM331 is a little better than 1% for 10 kHz full-scale. Increasing  $C_T$  to 0.1  $\mu\text{F}$  reduces the nonlinearity to below 0.2% while decreasing full-scale output to 1 kHz.


Two inputs can also be multiplied while converting to a frequency. The multiplying converter circuit (Figure 6) that does this has a more elaborate current pump than the ratio circuit of Figure 4. This pump is really two cascaded circuits; it includes op amps A2 and A3 as well as transis-

tors Q2 and Q3. Current from this pump goes to pin 5 to control the one-shot's pulse width. (This current ranges from 13.3  $\mu\text{A}$  to 1.33 mA.)

As in the ratio circuit, the left current pump controls the discharge rate of  $C_L$ . The other pump, however, controls the one-shot's pulse width to vary the amount that  $C_L$  charges during the pulse. If the  $V_2$  input is close to zero, the current from the pump into pin 5 is small, and the one-shot develops a wide pulse. This allows  $C_L$  to charge quite a bit. It takes a relatively long time for  $C_L$  to discharge to the comparator threshold, so the resulting frequency is low. As  $V_2$  goes negative (a greater absolute magnitude), the output frequency rises. Op amp A3 must have a common-mode range that extends to the positive supply voltage, which the specified types do.

Multiplying, dividing and converting can all be done at the same time by combining the  $V_2$  input current pump of Figure 4 with the circuit of Figure 6. If a scale-factor trimmer is needed,  $R_4$  in Figure 6 is a good choice, better than input resistors such as  $R_1$  or  $R_2$ . Using the latter as trimmers would make the input impedance of the circuit change with trim setting.

Two V/F converter ICs along with some extra circuitry will take the square root of a voltage input. Square root functions are used mostly to simulate natural laws, but also to linearize functions that have a natural square-law relationship. One of the latter is converting differential pressure to flow, where flow is proportional to the square root of differential pressure.

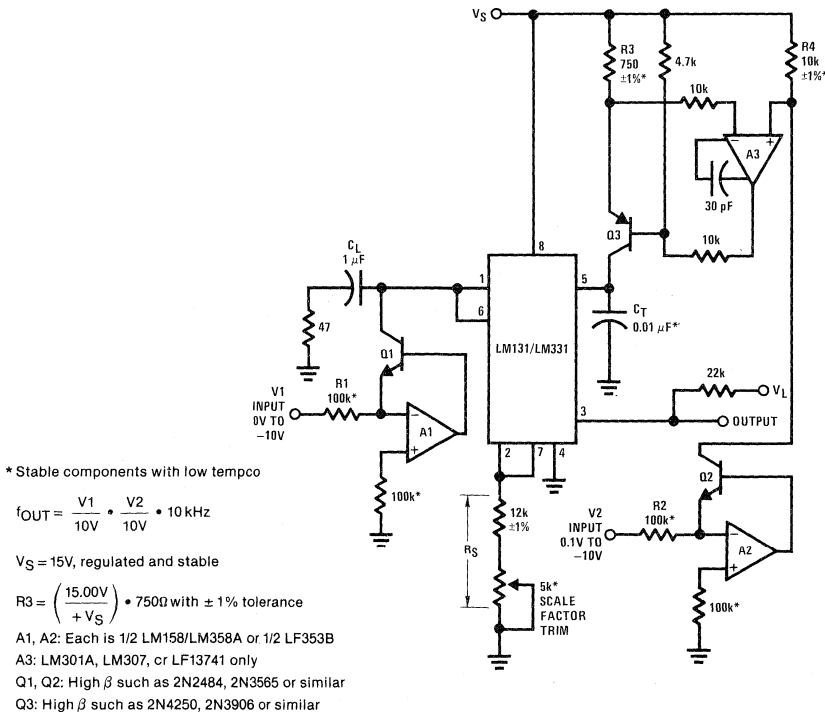

**FIGURE 6.** The product of two input voltages becomes an equivalent frequency in this converter. A current pump that includes op amps A2 and A3 controls the pulse duration of the converter's internal one-shot.

### Versatile Pin Functions Give Design Flexibility

Two features—the reference and the one-shot—of the LM131/LM331 V/F converter deserve a closer look because they are the key to its versatility. The simplified schematic of the chip, shown here along with a transducer and the components needed for a basic V/F converter, will help to illustrate how these features work.

The reference circuit, connected to pin 2, is both a constant voltage output and a current setting, scale-factor control input. The constant voltage can supply external circuitry, such as the transducer, that feeds the converter's input.

One great advantage of using the converter's internal reference to supply the external circuitry is that any variation in the reference voltage affects the sensitivities of the converter and the external circuitry by equal and opposite amounts, so the effects of the variation cancel.

While providing a constant voltage output, pin 2 also provides scale-factor, or sensitivity control for the converter. Current supplied to an external circuit by this terminal comes from the supply ( $V_S$ ) through the current mirror and the transistor. The op amp drives this transistor to hold pin 2 at a constant voltage equal to the internal reference, which is nominally 1.9V.


The current mirror provides a current to the switch that's essentially identical to that in pin 2. This means that a

resistor to ground or a signal from a current source will set the current that is switched to pin 1. In most circuits, a capacitor goes from pin 1 to ground, and the switched current from this pin recharges the capacitor during the pulse from the one-shot.

The one-shot circuit is somewhat like the well known 555 timer's circuit. In the quiescent state, the reset transistor is on and holds pin 5 near ground. When pin 7 becomes more positive than pin 6 (or pin 6 falls below pin 7), the input comparator sets the flip-flop in the one-shot.

The flip-flop turns on the current limited output transistor (pin 3) and switches the current coming from the current mirror to pin 1. The flip-flop also turns off the reset transistor, and the timing capacitor  $C_T$  starts to charge toward  $V_S$ . This charge is exponential, and  $C_T$ 's voltage reaches  $2/3$  of  $V_S$  in about  $1.1 R_T C_T$  time constants. (The quantity 1.1 is  $-1 \ln 0.333\dots$ ) When pin 5 reaches this voltage, the one-shot's comparator resets the flip-flop which turns off the current to pin 1, discharges  $C_T$ , and turns off the output transistor.

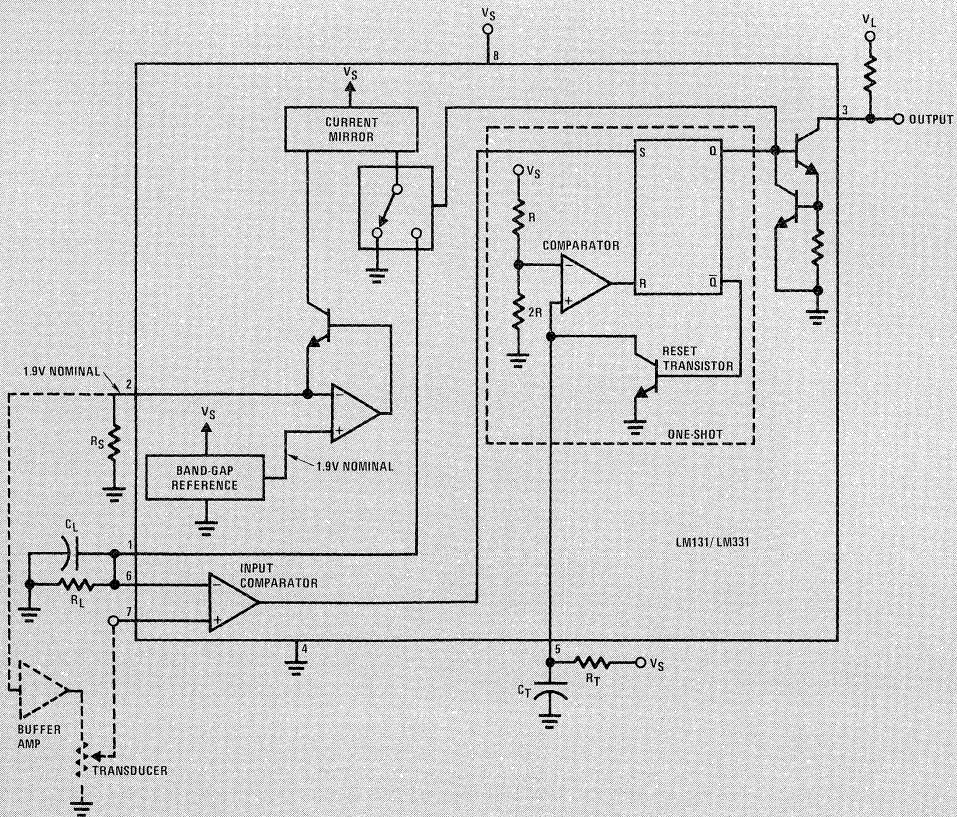If the voltages at pins 6 and 7 still call for setting the flip-flop after pin 5 has reached  $2/3 V_S$ , internal logic not shown in this simplified diagram overrides the reset signal from the one-shot's own comparator, and the flip-flop stays set. In this instance,  $C_T$  continues charging past  $2/3 V_S$ .



## Root Loop Computes

The circuit in Figure 7 is an implicit loop (see "Computing Square Roots Implicitly") that uses IC1 as a voltage-to-frequency converter and divider, and IC2 as a frequency-to-voltage converter. The F/V converter, IC2, and the current pump that includes A1 and the transistor return the output of IC1 to its denominator input. A relatively elaborate feedback circuit like this is needed to convert IC1's frequency output back to a current for its denominator input.

Looking at the circuit in more detail, IC1 puts out a frequency proportional to  $V_{IN}$  divided by the feedback voltage,  $V_X$ . The current  $I_1$  is generated by a current pump that has  $V_X$  as its input (Figure 5a). To develop the feedback IC2 converts the pulse output from IC1 into standard width precision current pulses that charge capacitor C1. This capacitor integrates them into the voltage  $V_X$ , thus closing the loop.

Op amp A2, serving as a comparator, ensures that the circuit will always start and continue running. If  $V_{IN}$  suddenly jumps to a higher voltage, one pulse from the one-shot in IC1 may not be enough to recharge  $C_1$  to a voltage higher than the input. In such a case, the IC's internal logic keeps its internal current switch turned on, and the voltage on  $C_1$  ramps up until it exceeds the input. During this time, however, IC1's output hasn't changed state. (Such a temporary hang-up isn't unique to this circuit, and equivalent things happen to other V/Fs besides the LM131/LM331.) What is worse here, though, is that the lack of pulses to IC2 means that  $V_X$  and  $I_1$  decay. The recharging current,  $I_2$ , is the same as  $I_1$ , so it not only becomes progressively harder for the voltage on  $C_1$  to catch up with the input, it may even fail to catch up entirely if  $(I_2 \cdot R_{L1})$  is less than the input voltage.


As a sign of this condition, when the converter hangs up, the one-shot's timing node, pin 5, continues to charge well beyond its normal peak of  $2/3 V_S$ . As soon as the comparator A2 detects this rise, it pulls up voltage  $V_X$ , current  $I_1$  increases, and the loop catches its breath again.

After all these nonlinear computations, this last circuit is about as linear as it can be. It's a precision, ultralinear V/F converter based on an LM331A (Figure 8) that has several detail refinements over previous V/F converter circuits. Choosing the proper components and trimming the tempo give less than 0.02% error and 0.003% nonlinearity for a  $\pm 20^\circ\text{C}$  range around room temperature.


This circuit has an active integrator, which includes the op amp and the integrating feedback capacitor,  $C_F$ . The integrator converts the input voltage, which is negative, into a positive-going ramp. When the ramp reaches the converter IC's comparator threshold, the one-shot fires and switches a pulse of current to the integrator's summing junction. This current makes the integrator's output ramp down quickly. When the one-shot times out, the cycle repeats.

There are several reasons this converter circuit gives high performance:

- A feedback limiter prevents the op amp from driving pin 7 of the LM331A negative. The limiter circuit arrangement bypasses the leakage through CR5 to ground via R5, so it won't reach the summing junction. Bypassing leakage this way is especially important at high temperatures.
- The offset trimming pot is connected to the stable 1.9V reference at pin 2 instead of to a power supply bus that might be unstable and noisy.

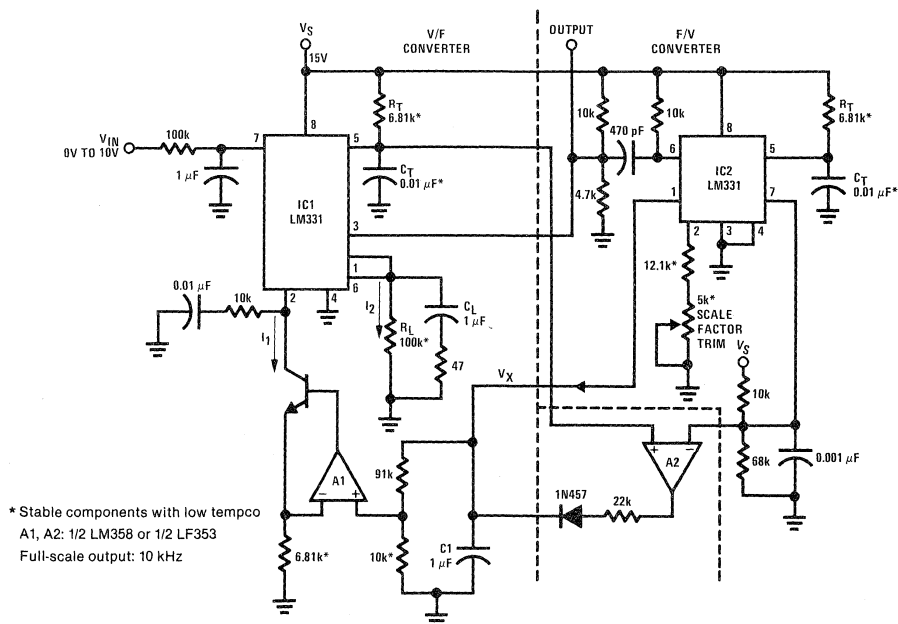

**FIGURE 7.** Two converter ICs generate an output frequency proportional to the square root of the input voltage. The circuit is an implicit loop in which IC1 serves as a divider and V/F converter. This IC's output goes back to its denominator input through F/V converter IC2 to make the circuit output equal the input's square root.

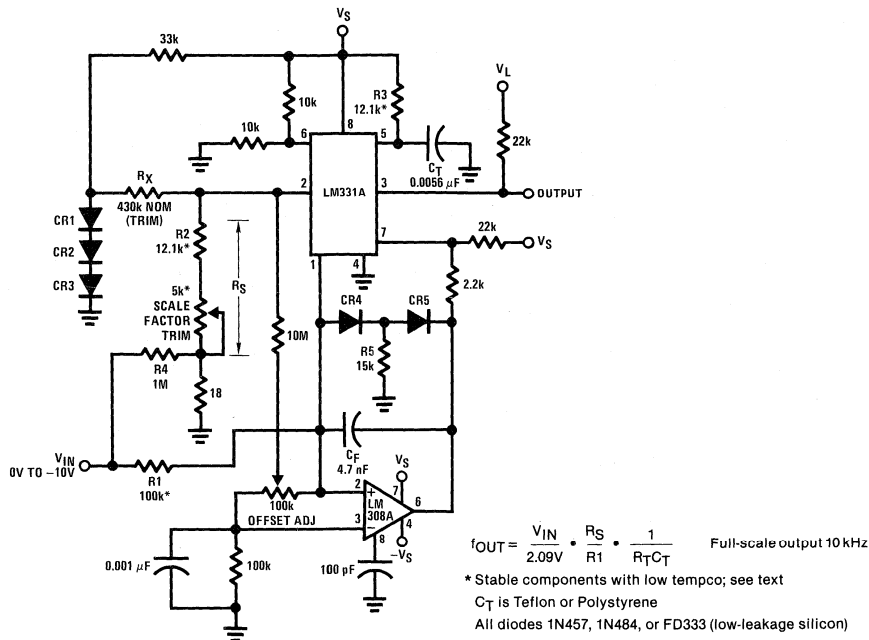

**FIGURE 8.** An ultraprecision V/F converter, capable of better than 0.02% error and 0.003% nonlinearity for a  $\pm 20^\circ\text{C}$  range about room temperature, augments the basic converter with an external integrator.

- A small fraction (180  $\mu\text{V}$ , full-scale) of the input voltage goes via R4 to the  $R_S$  network, which improves the non-linearity from 0.004% to 0.002%.
- Resistors R2 and R3 are the same value, so that resistors such as Allen-Bradley type CC metal-film types can provide excellent tempco tracking at low cost. (This tracking is very good when equal values come from the same batch.) Resistor R1 should be a low tempco metal-film or wirewound type, with a maximum tempco of  $\pm 10$  ppm/ $^\circ\text{C}$  or  $\pm 25$  ppm/ $^\circ\text{C}$ .

In addition,  $C_T$  should be a polystyrene or Teflon type. Polystyrene is rated to  $80^\circ\text{C}$ , while Teflon goes to  $150^\circ\text{C}$ . Both types can be obtained with a tempco of  $-110 \pm 30$  ppm/ $^\circ\text{C}$ . Choosing this tempco for  $C_T$  makes the tempco, due to  $C_T$ , of the full-scale output frequency 110 ppm/ $^\circ\text{C}$ .

Using tight tolerance components results in a total tempco between 0 ppm/ $^\circ\text{C}$  and 220 ppm/ $^\circ\text{C}$ , so the tempco will never be negative. The voltage at CR1 and  $R_X$  has a tempco of  $-6$  mV/ $^\circ\text{C}$ , which can be used to compensate the tempco of the rest of the circuit. Trimming  $R_X$  compensates for the tempco of the V/F IC, the capacitor, and all the resistors.

A good starting value for selecting  $R_X$  is 430 k $\Omega$ , which will give the 135  $\mu\text{A}$  flowing out of pin 2 a slope of 110 ppm/ $^\circ\text{C}$ . If the output frequency increases with temperature, a little more conductance should be added in parallel with  $R_X$ .

When doing a second round of trimming, though, note that a resistor of, say, 4.3 M $\Omega$ , has about the same effect on tempco when shunted across a 220 k $\Omega$  resistor that it does when shunted across one of 430 k $\Omega$ , namely,  $-11$  ppm/ $^\circ\text{C}$ . This technique can give tempcos below  $\pm 20$  ppm/ $^\circ\text{C}$  or even  $\pm 10$  ppm/ $^\circ\text{C}$ .

Some precautions help this procedure converge:

1. Use a good capacitor for  $C_T$ . The cheapest polystyrene capacitors will shift in value by 0.05% or more per temperature cycle. The actual temperature sensitivity would be indistinguishable from the hysteresis, and the circuit would never be stable.
2. After soldering, bake and/or temperature-cycle the circuit (at a temperature not exceeding  $75^\circ\text{C}$  if  $C_T$  is polystyrene) for a few hours, to stabilize all components and to relieve the strains from soldering.
3. Don't rush the trimming. Recheck the room temperature value, before and after the high temperature data are taken, to ensure that hysteresis per cycle is reasonably low.
4. Don't expect a perfect tempco at  $-25^\circ\text{C}$  if the circuit is trimmed for  $\pm 5$  ppm/ $^\circ\text{C}$  between  $25^\circ\text{C}$  and  $60^\circ\text{C}$ . If it's been trimmed for zero tempco while warm, none of its components will be linear to much better than 5 ppm/ $^\circ\text{C}$  or 10 ppm/ $^\circ\text{C}$  when it's cold.

The values shown in this circuit are generally optimum for  $\pm 12\text{V}$  to  $\pm 16\text{V}$  regulated supplies but any stable supplies between  $\pm 4\text{V}$  and  $\pm 22\text{V}$  would be usable, after changing a few component values.

