



## Generating a 1.2 V Voltage Supply using the NCP102 Voltage Regulator

Prepared by: Juan Carlos Pastrana  
ON Semiconductor

### INTRODUCTION

The NCP102 low dropout linear regulator controller contains all the control and protection features needed to implement a low voltage regulator. The required external N-Channel MOSFET allows the device to be used in applications across a broad range of voltage and power levels.

The NCP102 is the ideal choice for new generation low voltage supplies in computing motherboard and consumer applications thanks to the following features:

- **A dedicated enable input:** allows the controller to be remotely enabled or sequenced.
- **An extremely accurate 0.8 V (±2.0%) reference:** allows the implementation of sub 1 V voltage supplies.
- **Adjustable soft-start:** allows the system to turn on in a controlled manner eliminating output voltage overshoot.
- **Minimum drive capability of ±5 mA:** provides fast transient response. The drive current is internally limited to protect the controller in case of an external MOSFET failure.
- **Wide voltage supply operation:** allows the controller to be biased directly from existing voltage supplies without the need of external voltage limiting circuits.

### Linear Regulators

Linear regulators are a common topology for generating a lower voltage supply from a higher voltage. A linear regulator consists of a voltage reference ( $V_{REF}$ ), an error amplifier and a pass transistor as shown in Figure 1.

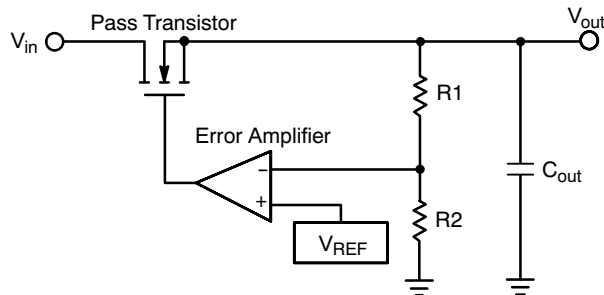


Figure 1. Simplified Linear Regulator Model

A fraction of the output voltage is compared to the internal reference voltage by means of resistor divider R1 and R2.

The minimum output voltage is limited by the voltage reference. The pass transistor is selected to achieve the desired input voltage and output current.

Stability of linear regulators is very critical as with any feedback system. The main contributors to the stability of a linear regulator are the error amplifier, the external pass transistor, the output capacitor(s) and load. Figure 2 shows a model of a linear regulator used to evaluate the frequency response of the regulator.

 


Figure 2. Frequency Model of a Linear Regulator

The overall system response,  $H(s)$ , is given by Equation 1.

$$H(s) = EA(s) \cdot G_{div}(s) \cdot T(s) \quad (\text{eq. 1})$$

The error amplifier ( $EA(s)$ ) usually has a dominant pole at a low frequency with additional poles or zeros at higher frequencies. Assuming its additional frequency components are above the frequency range of interest, the frequency response can be approximated to a single pole response as given by Equation 2.

$$EA(s) = \frac{K1}{(s + p1)} \quad (\text{eq. 2})$$

where  $K1$  is the dc gain and  $p1$  is the dominant pole. The resistor divider attenuates the system gain,  $G_{div}(s)$ , and its magnitude is given by Equation 3.

$$G_{div}(s) = 20 \cdot \log\left(\frac{R2}{R1 + R2}\right) \quad (\text{eq. 3})$$

The frequency response of the external components from  $V_{DRV}$  to  $V_{out}$  is a little more complicated. The response is determined by the output capacitors and the external pass transistor. If only one capacitor is considered the transfer response can be simplified as described in ON Semiconductor's application note AND8037.

$$T(s) = \frac{R_{out}(sC_{gs} + 1) \cdot (sR_{ESR1}C_{OUT1} + 1) \cdot (sR_{ESR2}C_{OUT2} + 1)}{D_4s^4 + D_3s^3 + D_2s^2 + D_1s + (1 + g_mR_{out})} \quad (\text{eq. 4})$$

where:

$$D_4 = C_{gs}R_{out}C_{gd}R_gR_X$$

$$D_3 = C_{gs}R_{out}C_{gd}R_gR_X + R_gR_XC_X + C_XR_{out}R_gR_{ESR2}C_{out2}C_{out1} + R_{out}R_gR_{ESR1}C_{out1}C_{out2}C_X + R_{out}R_X(R_gg_mC_{gd} + C_{gs})$$

$$D_2 = C_{gs}R_{out}C_{gd}R_g + R_gR_{ESR1}C_{out1}C_X + R_X + R_{ESR2}C_{out2}R_gC_X + C_{out1}R_{out}R_{ESR2}C_{out2} + C_{out1}R_{out}R_gC_X + C_{out2}R_{out}R_{ESR1}C_{out1} + C_{out2}R_{out}R_gC_X + g_mR_{out}R_X + g_mR_{out}R_gC_{gd}R_S + C_{gs}R_{out}R_S$$

$$D_1 = R_gC_X + R_S + R_{out}(C_{out1} + C_{out2} + C_{gs}) + g_mR_{out}(R_S + C_{gd}R_g)$$

$$R_X = R_{ESR1}C_{out1}R_{ESR2}C_{out2}$$

$$C_X = C_{gs} + C_{gd}$$

$$R_S = R_{ESR1}C_{out1} + R_{ESR2}C_{out2}$$

and  $g_m$  is the transconductance of the external transistor.

It is obvious that the overall transfer response is too complex for hand calculations. Even with several simplifications the roots of the transfer function to determine the poles of  $T(s)$  are too complex. A design tool is available for the NCP102 allowing the user to evaluate the system response. The design tool can be downloaded at [www.onsemi.com](http://www.onsemi.com).

### DESIGN EXAMPLE

The flexibility of the NCP102 is demonstrated by designing a 1.2 V/3.0 A voltage regulator using the NCP102 design tool. The input and supply voltages selected are typically found in computing mother board applications. The regulator specifications are listed in Table 1.

**Table 1. Design Specifications**

Parameter	Symbol	Min	Max
Input Voltage	$V_{in}$ (V)	1.8 ( $\pm 2\%$ )	
Output Voltage	$V_{out}$ (V)	1.2 ( $\pm 2\%$ )	
Output Current	$I_{out}$ (A)	0.3	3.0
Ambient Temperature	$T_A$ ( $^{\circ}\text{C}$ )	-	50
Supply Voltage	$V_{CC}$ (V)	5 V ( $\pm 5\%$ )	
Derating Factor	-	90 %	

### DESIGN PROCEDURE

#### External MOSFET:

The 1<sup>st</sup> step in the regulator design is to select the external pass transistor. The output and supply voltages as well as MOSFET gate-to-source threshold voltage,  $V_{th}$ , need to be considered. The MOSFET threshold voltage,  $V_{th}$ , should be less than  $V_{CC}$  minus  $V_{out}$  as given by Equation 5.

$$V_{th} \leq V_{CC} - V_{out} \quad (\text{eq. 5})$$

Solving 5 using the design specifications,  $V_{th}$  should be less than 3.8 V. The next step is to calculate the power

Each output capacitor contributes a zero due to its equivalent series resistance (ESR). In the case of two types of output capacitors (such as electrolytic and ceramic), zeros at different frequencies are generated. The external pass transistor contributes a zero and affects the poles of the system. The frequency response from  $V_{DRV}$  to  $V_{out}$  is given by Equation 4.

dissipation,  $P_D$ , of the external MOSFET. The power dissipation is calculated using Equation 6 and the maximum junction temperature,  $T_J$ , using Equation 7.

$$P_D = (V_{in} - V_{out}) \cdot I_{out} \quad (\text{eq. 6})$$

$$T_J = P_D \cdot R_{\theta JA} + T_A \quad (\text{eq. 7})$$

where,  $R_{\theta JA}$  is the junction to ambient thermal resistance (in  $^{\circ}\text{C}/\text{W}$ ) of the external MOSFET. The NCP102 design tool automatically calculates the power dissipation and junction temperature.

Using  $R_{\theta JA}$  doesn't always result in accurate junction temperature calculations as  $R_{\theta JA}$  depends on the board layout. Alternatively,  $T_J$  can be calculated using the junction to case thermal resistance,  $R_{\theta JC}$ , and measuring the case temperature ( $T_C$ ). Equation 8 relates the  $T_J$  to  $R_{\theta JC}$ .

$$T_J = P_D \cdot R_{\theta JC} + T_C \quad (\text{eq. 8})$$

ON Semiconductor's NTD40N03 is used in this design. It has a  $V_{th}$  of 2.0 V, an  $R_{\theta JA}$  of  $71.4^{\circ}\text{C}/\text{W}$  and an  $R_{\theta JC}$  of  $3^{\circ}\text{C}/\text{W}$ . Using  $R_{\theta JA}$  and the maximum ambient temperature a  $T_J$  of  $178^{\circ}\text{C}$  is calculated. That is slightly higher than the maximum junction temperature of the device and exceeds the derating factor. As  $R_{\theta JA}$  provided in the NTD40N03 datasheet is for a specific layout, we will evaluate the board at full load and use  $R_{\theta JC}$  to calculate  $T_J$ . It will be shown that the junction temperature meets the derating factor. This board provides a place holder for a parallel MOSFET (Q2) allowing the user to spread the power dissipation if needed.

Transconductance is the ratio of output current to the input voltage. In a MOSFET, it is the ratio of drain current ( $I_D$ ) to gate-to-source voltage ( $V_{GS}$ ) as given by Equation 9.

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}} \quad (\text{eq. 9})$$

Referring to the NTD40N03R datasheet, the transconductance is calculated using the On-Region

Characteristics Curve (Figure 1). Let's calculate the transconductance for a  $V_{DS}$  of 0.5 V with a  $V_{GS}$  variation from 2.8 V to 3 V. The drain current at 2.8 V is ~1.8 A and at 3 V it is approximately 3.8 A. Using these values a transconductance of 10 is calculated.

The gate-to-source,  $C_{GS}$ , and drain-to-source,  $C_{DS}$ , capacitances are needed for the frequency response analysis. The capacitances are calculated from the Capacitance Variation curve on the NTD40N03R datasheet.  $C_{RSS}$  is the gate-to-drain capacitance.  $C_{ISS}$  is the sum of  $C_{GS}$  and  $C_{GD}$ .  $C_{OSS}$  is the sum of  $C_{DS}$  and  $C_{GD}$ . Referring to the Capacitance Variation curve,  $C_{RSS}$  is approximately 150 pF,  $C_{ISS}$  is approximately 700 pF and  $C_{OSS}$  is approximately 600 pF at a  $V_{DS}$  of 0.5 V, resulting in a  $C_{DS}$  of 450 pF and a  $C_{GS}$  of 550 pF.

**Output Capacitor:**

The next step is to select the output capacitor. It is very common to use an electrolytic capacitor for bulk storage and a ceramic capacitor for high frequency bypass. However, the capacitors need to be carefully selected as they affect the stability of the system.

An electrolytic capacitor has high capacitance and high ESR resulting in a zero at a low frequency (typically below 1 kHz) and a dominant pole at a higher frequency. The ceramic capacitor has very low ESR placing a zero at a high frequency. If the ceramic capacitor capacitance is large (above 4.7  $\mu$ F) the resulting zero may be in the crossover frequency range and thus affect the stability of the system.

This design uses a 1000  $\mu$ F electrolytic capacitor with an ESR of 212 m $\Omega$  and a 4.7  $\mu$ F ceramic in parallel.

**Resistor Divider:**

The output voltage is sampled by resistor divider R1 and R2. The node between the resistors must equal the reference voltage (0.8 V) at the desired output voltage. Using the design tool, the user arbitrarily selects a value for R2 and the tool suggests a value for R1. The user can override the suggested R1 value. In this design, R2 is set at 20 k $\Omega$  and R1 at 10 k $\Omega$ .

**Frequency Response:**

The NCP102 design tool simplifies the frequency response analysis of the regulator. It is a good tool to evaluate the interaction between the components and approximate the cross over frequency. However, it does not take into account 2<sup>nd</sup> order effects such as transconductance variations with load current. The simulated frequency response of the regulator at minimum load is shown in Figure 3.

 


Figure 3. Simulated Frequency Response

The approximate crossover frequency is 50 kHz with a phase margin of 85°.

**Soft-Start:**

Soft-start slowly increases the regulator output voltage reducing stress during power up. The NCP102 implements soft-start by slowly charging the soft-start capacitor ( $C_{SOFT-S}$ ) with a fixed current source ( $I_{SOFT-S}$ ). The soft-start voltage is then used to control the dv-dt of the DRV pin. The soft-start period ends once the soft-start voltage reaches 0.8 V. Equation 10 is used to calculate the soft-start period.

$$t_{SOFT-S} = \frac{C_{SOFT-S} \cdot 0.8 V}{I_{SOFT-S}} \quad (\text{eq. 10})$$

The design tool calculates the soft-start capacitor based on the user provided soft-start period. The user can override the suggested soft-start capacitor value and the tool calculates the soft-start period based on the provided capacitor value. This design uses a 0.1  $\mu$ F soft-start capacitor for a 16 ms period.

**BOARD LAYOUT**

The regulator is built to validate the design using a 2 layer FR4 board having 1 oz copper plating. The board size is 3.5 in. x 3.2 in. Test points are provided for the Enable, DRV, Soft-Start, FB,  $V_{in}$ ,  $V_{out}$  signals.

During the layout process care was taken to:

1. Minimize trace length, especially for high current loops.
2. Use wide traces for high current connections.
3. Use a single ground connection.
4. Place decoupling capacitors close to the NCP102 and board terminals.
5. Sense output voltage at the output connector to improve load regulation.

The top layer is shown in Figure 4 and the bottom layer is shown in Figure 5. The top layer shows the component location.

 


Figure 4. Layer 1 (Top)

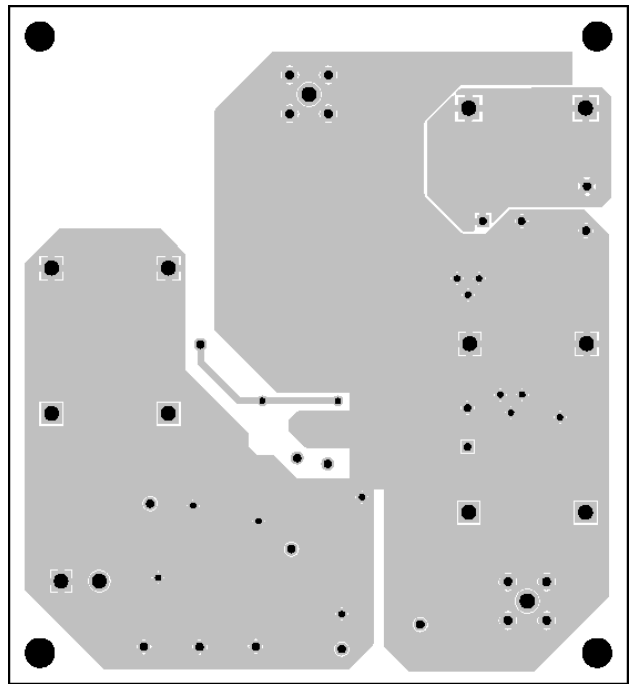


Figure 5. Layer 2 (Bottom)

The layout files may be available. Please contact your sales representative for availability.

**DESIGN VALIDATION**

The circuit schematic is shown in Figure 6 and the bill of materials is shown in Table 2.

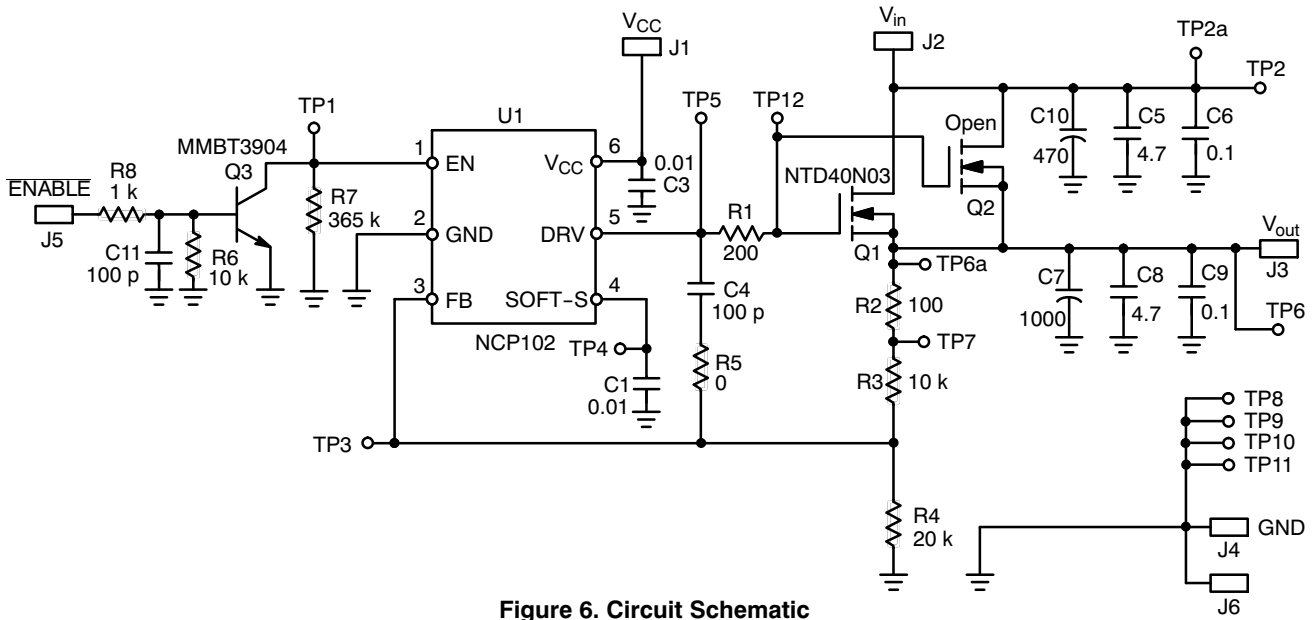


Figure 6. Circuit Schematic

# AND8303/D

**Table 2. Bill of Materials**

Reference	Value	Part	Vendor	Comments
C1, C3	0.01 $\mu$ F, 50 V (0.01 $\mu$ F, 25 V)	C1608X7R1H103K (VJ0603Y103KXXA)	TDK (Vishay)	Capacitor, Ceramic
C2	N/A	N/A	N/A	Not Used
C4, C11	100 pF, 50 V (100 pF, 25 V)	C1608CH1H1015 (VJ0603Y101KXXA)	TDK (Vishay)	Capacitor, Ceramic
C5, C8	4.7 $\mu$ F, 16 V	C3216X5R1C475K	TDK	Capacitor, Ceramic
C6, C9	0.1 $\mu$ F, 25 V	C3216CH1E104J (VJ1206Y104KXXA)	TDK (Vishay)	Capacitor, Ceramic
C7	1000 $\mu$ F, 25 V	ESMG250ELL102MJ20S	United-Chemicon	Capacitor, Aluminum Electrolytic
C10	470 $\mu$ F, 25 V	ESMG250ELL471MJC5S	United-Chemicon	Capacitor, Aluminum Electrolytic
Q1	45 A, 25 V	NTD40N03RG	ON Semiconductor	Power MOSFET, N-Channel
Q2	N/A	N/A	N/A	Not Used
Q3	200 mA, 40 V	MMBT3904LT1G	ON Semiconductor	Transistor, Sm Signal, NPN
R1	200 $\Omega$ , 0.25 W	CRCW1206200RF	Vishay	Resistor, Thick Film
R2	100 $\Omega$ , 0.25 W	CRCW1206100RF	Vishay	Resistor, Thick Film
R3	10 k $\Omega$ , 0.25 W	CRCW12061002F	Vishay	Resistor, Thick Film
R4	20 k $\Omega$ , 0.25 W	CRCW12062002F	Vishay	Resistor, Thick Film
R5	0 $\Omega$ , 0.1 W	CRCW06030R00F (*CRCW06030000Z0)	Vishay	Resistor, Thick Film
R6	10 k, 0.1 W	CRCW06031002F	Vishay	Resistor, Thick Film
R7	365 k $\Omega$ , 0.1 W	CRCW06033653F	Vishay	Resistor, Thick Film
R8	1 k $\Omega$ , 0.1 W	CRCW06031001F	Vishay	Resistor, Thick Film
U1		NCP102SNT1G	ON Semiconductor	Low Dropout Linear Regulator Controller
J2	10ADC	571-0500	Deltron Emcon	Banana Jack, 4 mm Socket, Red, Horizontal Mt.
J3	10ADC	571-0700	Deltron Emcon	Banana Jack, 4 mm Socket, Yellow, Horizontal Mt.
J4, J6	10ADC	571-0100	Deltron Emcon	Banana Jack, 4 mm Socket, Black, Horizontal Mt.
J5	300 V, 16 A	DigiKey ED1930-ND or equivalent		Terminal Block, 2 Pole, Side Entry
TP1		TP-015-01-01	Components Corporation	Test Point, Brown
TP2		TP-015-01-02	Components Corporation	Test Point, Red
TP3		TP-015-01-03	Components Corporation	Test Point, Orange
TP4		TP-015-01-04	Components Corporation	Test Point, Yellow
TP5		TP-015-01-05	Components Corporation	Test Point, Green
TP6		TP-015-01-06	Components Corporation	Test Point, Blue
TP7		TP-015-01-07	Components Corporation	Test Point, Violet
TP8 - TP11		TP-015-01-00	Components Corporation	Test Point, Black
TP12		TP-015-01-08	Components Corporation	Test Point, Gray
TP6a, TP2a		131-5031-00 (pkg of 25)	Tektronix	3.5 mm dia. Probe Adapter

\* Alternate

1. TDK components can be ordered at (847) 803-6100.
2. Vishay Components can be ordered at (402) 563-6866.

The final step is to verify the board performance. The evaluation criteria include step load and power up responses, load regulation, stability and power dissipation.

**Dynamic Response:**

The dynamic response of the regulator is evaluated stepping the load current from 10% to 100% and from 100% to 10% of the rated output current. The step load responses are shown in Figure 7.

 


Figure 7. Output Voltage Response to a Step Load from 0.3 A to 3.0 A to 0.3 A

The output voltage stays within the 2% tolerance limit. The initial drop on the output voltage as a higher load is applied is mostly dependent on the output capacitor and not on the loop response of the system. No ringing is observed, indicating an adequate phase margin.

 


Figure 8. Output Voltage During Power Up at Minimum Load

**Startup:**

The startup behavior of the regulator is evaluated at minimum and maximum load enabling the controller using the enable pin while  $V_{in}$  and  $V_{CC}$  are already high. The startup waveforms at minimum and maximum load are shown in Figure 8 and 9, respectively.

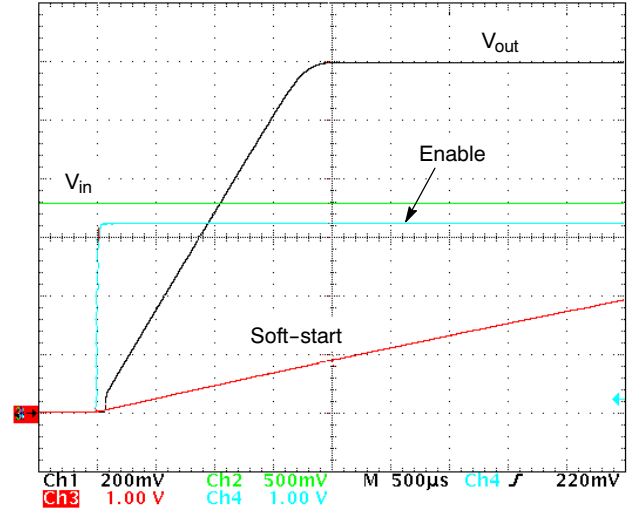


Figure 9. Output Voltage During Power Up at Maximum Load

**Line and Load Regulation:**

Line and load regulation are calculated using Equations 11 and 12, respectively. Line regulation is measured at 0.1% and load regulation is measured at 0.067%. The output voltage vs. input voltage and output load is shown in Figure 10.

$$Reg_{(line)} = \frac{\Delta V_{out}}{\Delta V_{in}} \quad (eq. 11)$$

$$Reg_{(load)} = \frac{V_{out(no\ load)} - V_{out(full\ load)}}{V_{out(no\ load)}} \quad (eq. 12)$$


 


Figure 10. Output Voltage Response to Input Voltage and Output Load Variations

**Frequency Response:**


The open loop response is measured by injecting an AC signal across R2 using a network analyzer and an isolation transformer. The measured and calculated open loop responses at minimum load are shown in Figure 11. The measured crossover frequency is 58 kHz with a phase margin of 70°. A good correlation is observed between simulated and calculated responses up to around 200 kHz.

 

**Figure 11. Measured and Calculated Open Loop Frequency Responses**

**Power Dissipation:**

This demo board is designed to operate with no airflow. However, in most desktop computing applications airflow will be present. The thermal performance of the board is evaluated using an infrared camera. Figure 12 shows the thermal image of the board at maximum output load.

 

**Figure 12. Thermal Image of the Board at Maximum Load**

As expected, the hottest component on the board is the external pass transistor. The case temperature is measured at 78.4°C at room temperature. Using Equation 8, the junction temperature is calculated at 84°C. The maximum junction temperature is calculated at 109°C assuming a 25°C temperature delta between room and maximum ambient temperatures. A junction temperature of 109°C meets our derating guidelines.

The thermal performance of the board can be optimized by using a heatsink, increasing the number of external pass transistors (Q1 & Q2) pad area, increasing the copper weight of the board or using an additional pass transistor.

**SUMMARY**

A 1.2 V regulator is designed and built using the NCP102. The regulator has excellent line and load regulation with better than ±2% output voltage regulation.

The regulator provides excellent transient response. Phase margin and crossover frequency are measured at 70° and 58 kHz, respectively.

**REFERENCES**

1. Tod Schiff, “Stability in High Speed Linear LDO Regulator,” AND8037/D, www.onsemi.com.
2. Low Dropout Linear Regulator Controller Datasheet NCP102, www.onsemi.com.
3. Power MOSFET 45 A, 25 V Datasheet NTD40N03R, www.onsemi.com

**ON Semiconductor** and **ON** are registered trademarks of Semiconductor Components Industries, LLC (SCILLC). SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. "Typical" parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that SCILLC was negligent regarding the design or manufacture of the part. SCILLC is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

## PUBLICATION ORDERING INFORMATION

### LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor  
P.O. Box 5163, Denver, Colorado 80217 USA  
**Phone:** 303-675-2175 or 800-344-3860 Toll Free USA/Canada  
**Fax:** 303-675-2176 or 800-344-3867 Toll Free USA/Canada  
**Email:** [orderlit@onsemi.com](mailto:orderlit@onsemi.com)

**N. American Technical Support:** 800-282-9855 Toll Free  
USA/Canada  
**Europe, Middle East and Africa Technical Support:**  
Phone: 421 33 790 2910  
**Japan Customer Focus Center**  
Phone: 81-3-5773-3850

**ON Semiconductor Website:** [www.onsemi.com](http://www.onsemi.com)  
**Order Literature:** <http://www.onsemi.com/orderlit>  
For additional information, please contact your local  
Sales Representative