AMIS-30663 - Loss of 3.3 V Digital I/O Supply



ON Semiconductor®

http://onsemi.com

APPLICATION NOTE

INTRODUCTION

This document describes the behavior of the AMIS-30663 high speed CAN transceiver in case the supply for the digital I/O is lost.

PROBLEM DESCRIPTION

When the supply of the digital I/O is lost this will have influence on the communication between the CAN controller and the AMIS–30663 CAN transceiver and on the communication on the bus. Two cases can be distinguished:

- V33 (Pin 8) is interrupted for the transceiver only (still Tx transmission from the controller)
- The common 3.3 V supply for CAN controller and transceiver is lost (no communication from controller)

CASE STUDY

Measurement Set-Up

All measurements were done on the set-up illustrated in Figure 1.

V33 is Interrupted for Transceiver Only

When the I/O supply of the transceiver is interrupted and the CAN controller is still supplied, there will still be a TxD transmission possible. RxD is a constant low (or dominant).

As a consequence, communication from the controller to the bus is still possible but communication from CAN-bus to controller is blocked (RxD = 0). See oscilloscope plots below.

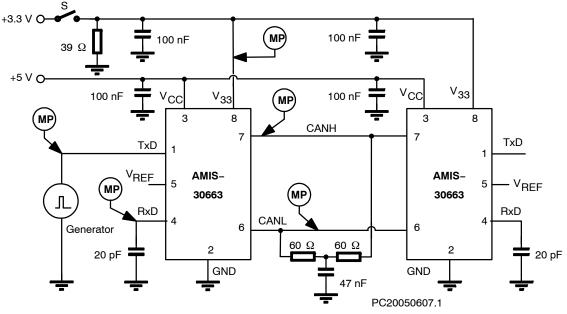


Figure 1. Measurement Set-Up

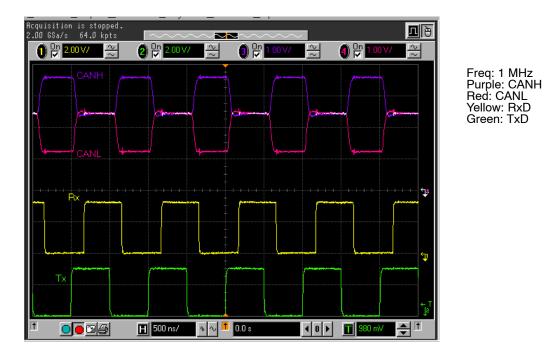


Figure 2. Normal Communication, S Closed V33 Present, Communication via TxD

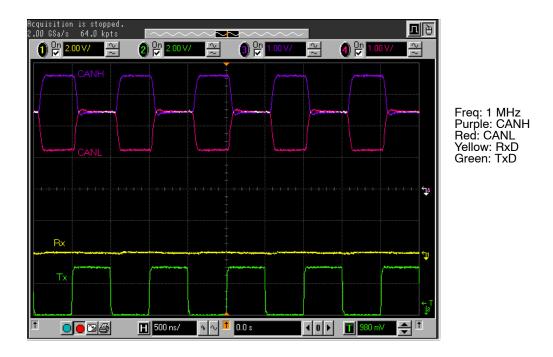


Figure 3. S is Open, V33 is Lost for Transceiver Only, Transmission is Still Possible

When the I/O supply of the transceiver is interrupted and the CAN controller is still supplied, there will still be a TxD transmission possible. Transients on the I/O supply will not have any influence on the communication on the bus, but enables the RxD driver. The oscilloscope plots below show the effect when V33 is switched on during dominant (TxD = 0) or recessive (TxD = 1) state.

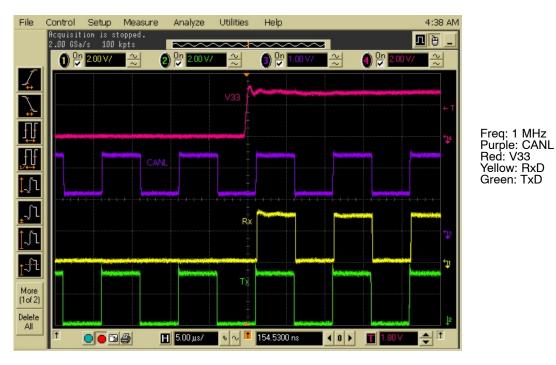


Figure 4. S is Closed \rightarrow V33 Transient at Dominant State (TxD = 0)

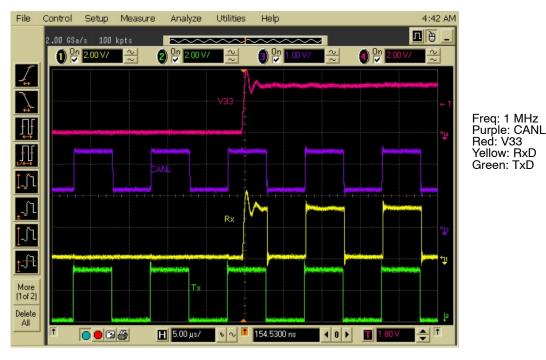


Figure 5. S is Close \rightarrow V33 Transient at Recessive State (TxD = 1)

V33 is Interrupted for Both Transceiver and CAN Controller

When the I/O supply of the transceiver is interrupted and the CAN controller is not supplied anymore, TxD transmission is possible. TxD will be 0 and the CAN bus becomes dominant. After the t_{dom} time-out (typically 450 µs) the CAN-bus becomes recessive. Further communication by other CAN nodes remains possible.

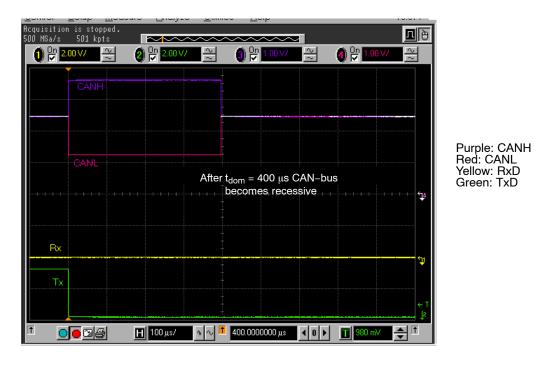


Figure 6. S = Open, V33 is Lost for Both Transceivers as Controller, After the Dominant Time–Out the CAN–Bus Becomes Recessive

CONCLUSION

When V33 I/O supply is lost in the AMIS–30663 transceiver only, transmission is still possible. The receiver output signal cannot propagate through the digital interface of the chip: RxD = 0 constantly. The CAN controller will see that the RxD is constant dominant although it sends data on the CAN bus. This will lead to an error state of this node which will, after several re–trials as defined by the CAN protocol, put itself to the "bus–off" state and will stop the transmission attempts. The CAN bus itself will then not be

affected and communication between other nodes on that bus will remain undisturbed.

When both V33 I/O supply of the AMIS–30663 and the 3.3 V CAN controller supply are lost, the CAN bus will be "decoupled" after a time–out of typically 450 μ s (CAN bus becomes recessive after t_{dom}). Again the CAN bus itself will not be affected and communication between other nodes on that bus will remain undisturbed.

ON Semiconductor and IIII are registered trademarks of Semiconductor Components Industries, LLC (SCILLC). SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other application in which the Folluce of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized to all applicable copyright laws and is not for reseal in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor P.O. Box 5163, Denver, Colorado 80217 USA Phone: 303–675–2175 or 800–344–3860 Toll Free USA/Canada Fax: 303–675–2176 or 800–344–3867 Toll Free USA/Canada Email: orderlit@onsemi.com N. American Technical Support: 800–282–9855 Toll Free USA/Canada Europe, Middle East and Africa Technical Support:

Phone: 421 33 790 2910 Japan Customer Focus Center Phone: 81–3–5773–3850 ON Semiconductor Website: www.onsemi.com

Order Literature: http://www.onsemi.com/orderlit

For additional information, please contact your local Sales Representative