

APPLICATION NOTE

**Application of the TEA1114A
Low voltage telephone transmission circuit
with dialler interface
and regulated strong supply**

AN98007



**TEA1114A transmission circuit with dialler
interface and regulated strong supply**

Application Note

Abstract

The TEA1114A is a bipolar transmission circuit for use in telephone sets. It is part of TEA111x family.

A detailed description of the circuit blocks of the TEA1114A and advices on adjustments are contained in this report.

APPLICATION NOTE

Application of the TEA1114A Low voltage telephone transmission circuit with dialler interface and regulated strong supply

AN98007

Authors:

B Arion, E Coenders, JM Malaurie

Keywords

Telecom
Demoboard
TEA1114A
 V_{DD}
Microphone
DTMF
Receive

Date: March 5th, 1998

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

Summary

A detailed description of the blocks of the TEA1114A is given. The possible settings to adjust the DC and transmission characteristics are explained.

The TEA1114A incorporates a microphone amplifier, a DTMF amplifier, a receive amplifier and an earpiece amplifier. It provides supplies for peripherals including a 3.3 V regulated.

An evaluation board for the TEA1114A is available.

Note:

The information **presented** in this document does not form part of any quotation or contract, is believed to be accurate and reliable and may be changed without notice. No liability will be accepted by the publisher for any consequence of its use. Publication thereof does not convey nor imply any licence under patent or other industrial property rights.

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

CONTENTS

1. INTRODUCTION	7
2. BLOCK DIAGRAMS AND PINNINGS	8
3. DESCRIPTION OF THE TEA1114A	10
3.1 DC characteristics and supply block	11
3.1.1 DC characteristics	11
3.1.2 Supplies for peripherals	15
3.2 Set impedance	19
3.3 Microphone amplifier	20
3.4 Receive amplifier block	24
3.5 Automatic gain control	27
3.6 DTMF amplifier	28
3.7 "MUTE" function	31
3.8 Anti-sidetone network	32
3.8.1 TEA111x family bridge	33
3.8.2 Wheatstone bridge	34
4. APPLICATION COOKBOOK	35
5. EXAMPLE OF APPLICATION	37
6. ELECTROMAGNETIC COMPATIBILITY	41
7. REFERENCES	42

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

LIST OF FIGURES

Fig. 1 TEA1114A block diagram.....	8
Fig. 2 TEA1114A pinning	9
Fig. 3 Basic application for measurements	10
Fig. 4 DC characteristics configuration	11
Fig. 5 I_{cc} versus VCC	12
Fig. 6 Main voltages versus line current	13
Fig. 7 Low voltage behavior in line powered condition	13
Fig. 8 Influence of the R_{va} resistor between REG and SLPE or between REG and LN	14
Fig. 9 Influence of R_{slpe} on the DC characteristics	15
Fig. 10 Configuration of the supplies	16
Fig. 11 VDD and V_{In} versus line current.....	18
Fig. 12 Current consumption on VDD.....	19
Fig. 13 Equivalent set impedance	20
Fig. 14 Microphone channel	21
Fig. 15 Microphone gain versus frequency: influence of temperature.....	22
Fig. 16 Distortion on line versus line signal (left) and versus microphone signal on TEA1114A	22
Fig. 17 Microphone noise versus line current	23
Fig. 18 Common mode rejection ratio on microphone.....	23
Fig. 19 Receive channel.....	24
Fig. 20 Receive gain versus frequency: influence of temperature	25
Fig. 21 Distortion on QR versus input signal on IR	26
Fig. 22 Distortion on QR versus level on 450 Ω and 150 Ω loads	26
Fig. 23 Noise on QR	27
Fig. 24 AGC on the microphone gain versus line current and R_{agc}	28
Fig. 25 DTMF channel of the TEA1114A.....	29
Fig. 26 DTMF gain versus frequency: influence of temperature	30
Fig. 27 Distortion of the DTMF signal on line versus input signal	30
Fig. 28 Microphone gain and MUTE/ input current versus MUTE/ input voltage.....	31
Fig. 29 Microphone and receive gain reduction in "mute" condition.....	32
Fig. 30 Wheatstone bridge (left) and TEA111x family anti-sidetone bridge (right)	32
Fig. 31 Equivalent average line impedance	33
Fig. 32 Basic application of the TEA1114A.....	38
Fig. 33 Circuit diagram of the demoboard.....	39
Fig. 34 Component placement diagram of the demoboard	40

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

1. INTRODUCTION

The TEA1114A offers all the microphone, receive and line interface functions required in telephone sets. It performs the interface between the line and the transducers of the handset.

The TEA1114A includes also a DTMF amplifier for dialling. The selection between the microphone amplifier and the DTMF amplifier is made with a "MUTE" function. The MUTE/ input switches-off both the microphone and the receive amplifiers and switches-on the DTMF amplifier.

Furthermore, a regulated 3.3 V supply is provided for the dialler or microcontroller.

The report is divided into two parts: the first part, up to chapter 3, gives a detailed description of the different circuit blocks of the TEA1114A including operating principles, settings of DC and transmission characteristics and performances of the different functions; the second part describes the consecutive steps to design and adjust applications using the TEA1114A and introduces the demoboard.

Note: the values of parameters given in this application note are as accurate as possible, but please, refer to the last product specification for final ones.

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

2. BLOCK DIAGRAMS AND PINNINGS

Fig. 1 shows the block diagram of the TEA1114A, the pinning is shown in fig. 2.

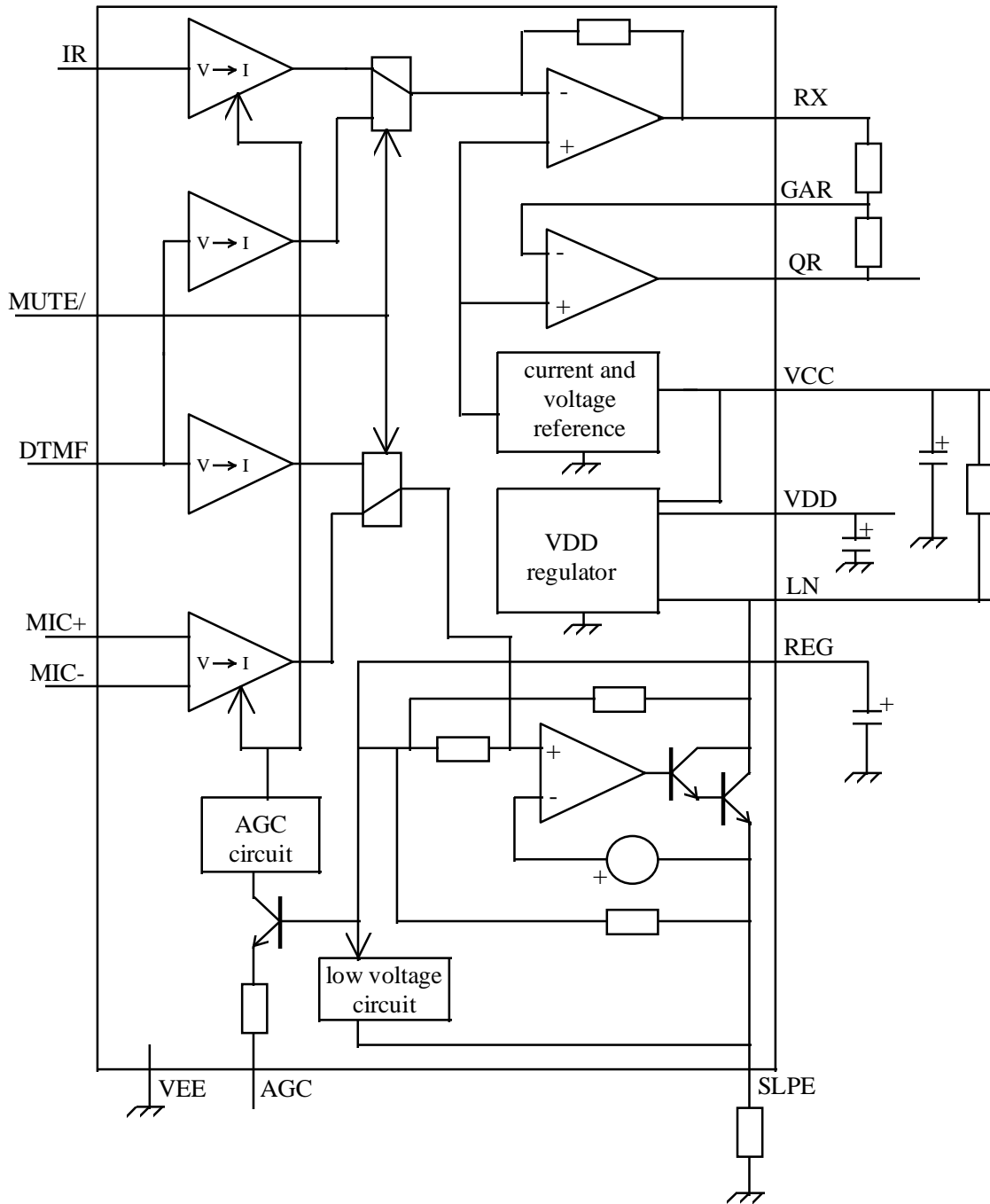


Fig. 1 TEA1114A block diagram

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

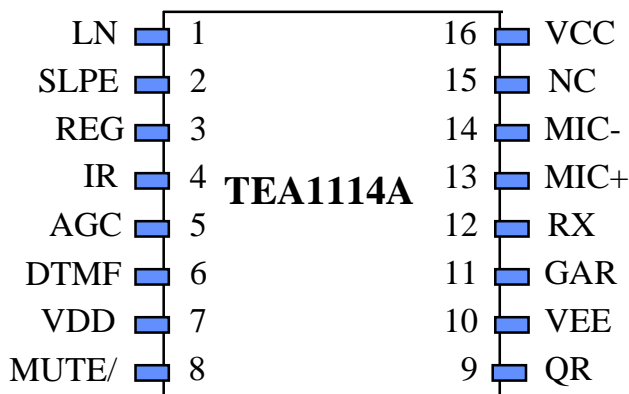


Fig. 2 TEA1114A pinning

TEA1114A PIN	NAME	DESCRIPTION
1	LN	Positive line terminal
2	SLPE	Slope adjustment
3	REG	Line voltage regulator decoupling
4	IR	Receive amplifier input
5	AGC	Automatic gain control
6	DTMF	DTMF input
7	V _{DD}	Regulated supply for peripherals
8	MUTE/	MUTE/ input
9	QR	Receive amplifier output
10	V _{EE}	Negative line terminal
11	GAR	Earpiece amplifier inverting input
12	RX	Receive amplifier output
13	MIC+	Non inverting microphone input
14	MIC-	Inverting microphone input
15	n.c.	Not connected
16	V _{CC}	Supply voltage for internal circuit

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

3. DESCRIPTION OF THE TEA1114A

All the curves shown in this section result from measurement of typical samples using the schematic shown in fig. 3.

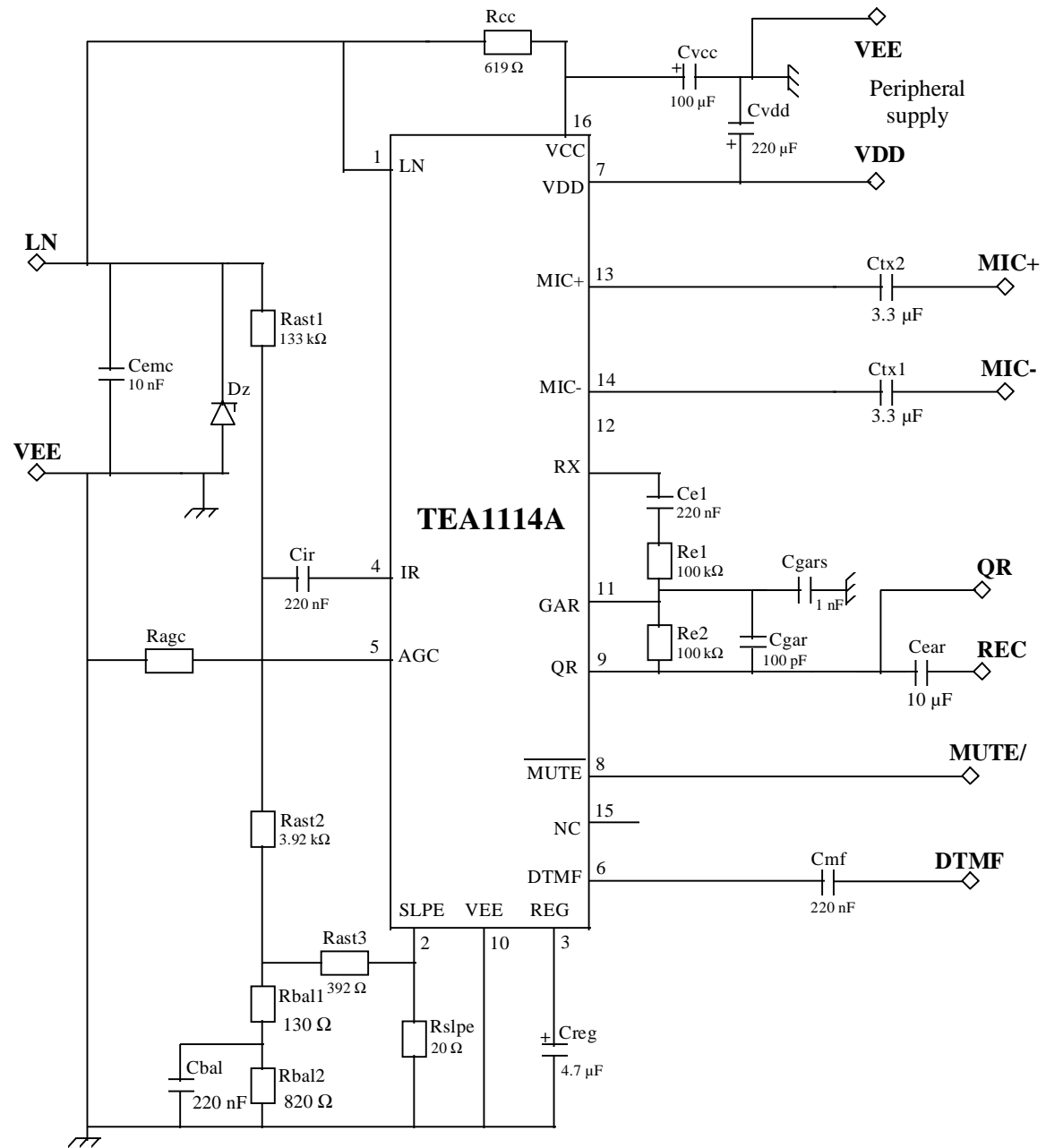


Fig. 3 Basic application for measurements

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

3.1 DC characteristics and supply block

3.1.1 DC characteristics

Principle of operation

The TEA1114A generates a stabilized voltage (called V_{ref}) between pins LN and SLPE. This reference voltage, typically 4.15 V, is temperature compensated. The voltage at pin REG is used by the internal regulator to generate the stabilized V_{ref} voltage and is decoupled by a capacitor C_{reg} connected to VEE.

For effective operation of the apparatus, the TEA1114A must have a low resistance to the DC current and a high impedance to speech signals. The C_{reg} capacitor, converted into an equivalent inductance (see “set impedance” section), realizes this impedance conversion from its DC value (R_{slpe}) to its AC value ($R_{cc} + R_z // C_z$ in the audio frequency range). The DC voltage at pin SLPE is proportional to the line current with an offset due to the VDD supply current.

This general configuration is shown in fig. 4.

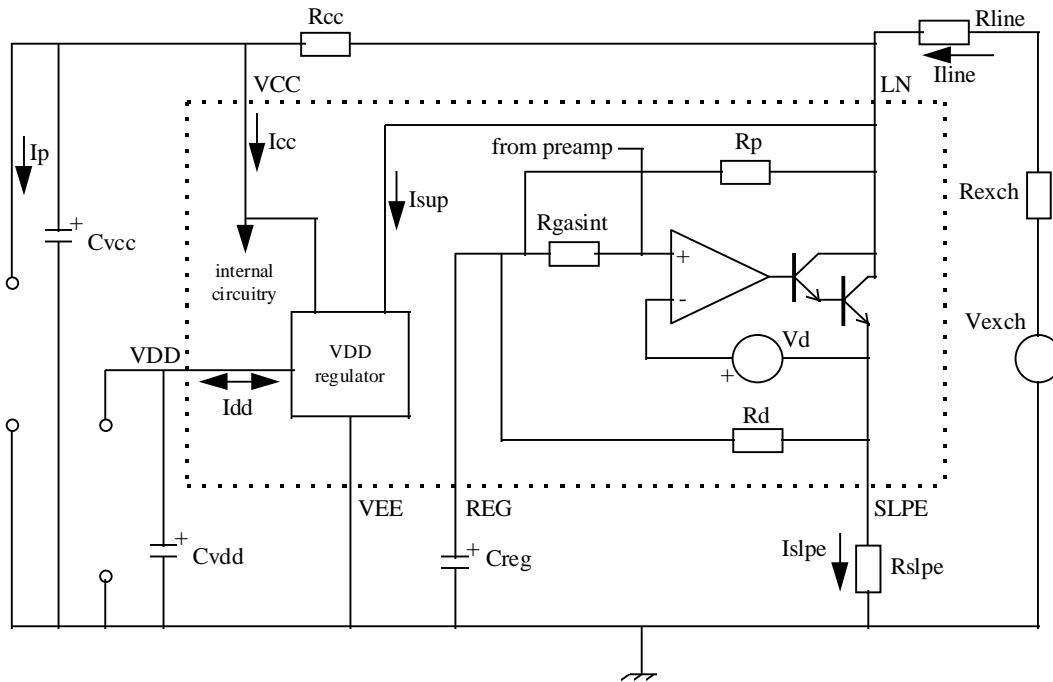


Fig. 4 DC characteristics configuration

The IC regulates the line voltage between pins LN and SLPE. the voltage on pin LN can be calculated as:

$$V_{ln} = V_{ref} + R_{slpe} \times I_{slpe}$$

$$I_{slpe} = I_{line} - I_{sup} - I_{cc} - I_p$$

I_{line} = line current

I_{cc} = current consumption of the IC

I_p = supply current for peripherals connected on VCC

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

I_{sup} = Current consumed between LN and VEE by the Vdd regulator

The DC line current I_{line} flowing into the apparatus is determined by the exchange supply voltage V_{exch} , the feeding bridge resistance R_{exch} , the DC resistance of the telephone line R_{line} and the voltage across the telephone set including diode bridge.

Below a threshold line current I_{th} (typically equal to 8 mA) the internal reference voltage (generating V_{ref}) is automatically adjusted to a lower value (down to an absolute minimum voltage of 1.6 V). This means that more sets can operate in parallel or that for a very low voltage feeding bridge the line current has a higher value. For line currents below this threshold current, the TEA1114A has reduced sending and receiving performances, moreover the voltage of Vdd and the current I_{sup} are reduced. This is called the low voltage area.

The internal circuitry of the TEA1114A is supplied from pin VCC. In line powered application, this voltage is derived from the line voltage by means of a resistor (R_{cc}) and must be decoupled by a capacitor (C_{vcc}). Fig. 5 shows the IC current consumption (I_{cc}) as a function of the VCC supply voltage.

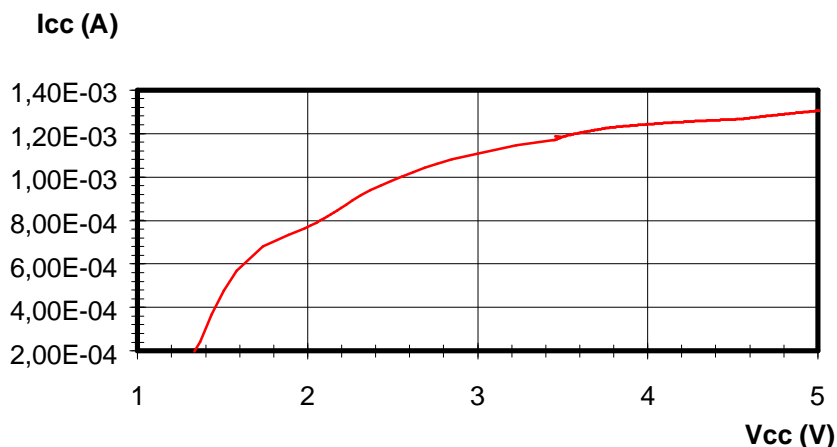


Fig. 5 Icc versus VCC

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

Fig. 6 shows the main voltages as a function of the line current.

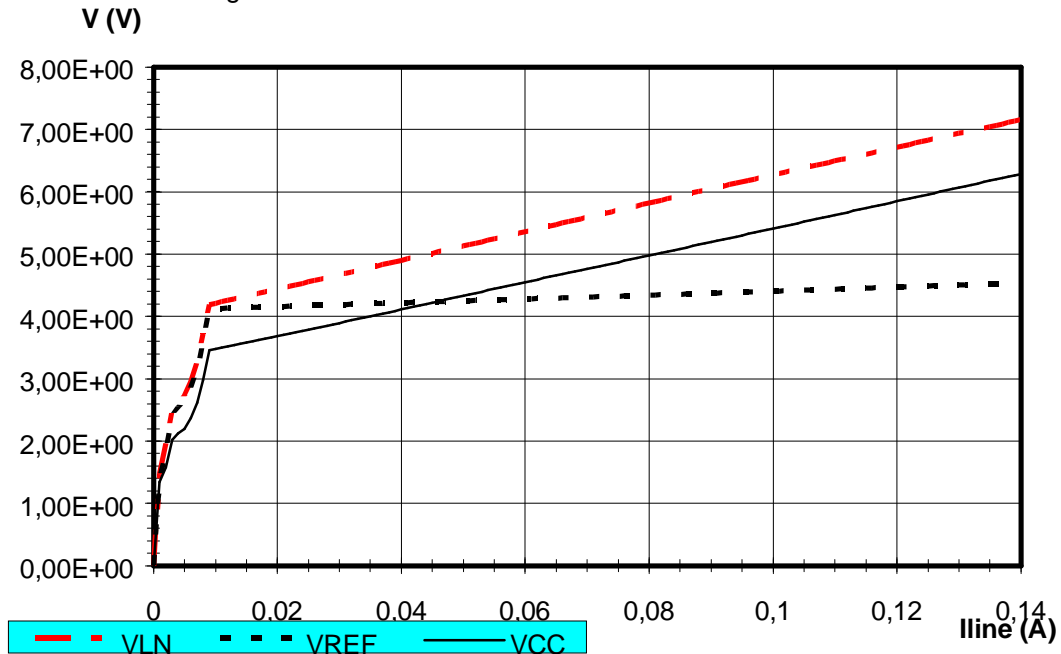


Fig. 6 Main voltages versus line current

Fig. 7 shows the behavior in the low voltage area in line powered condition.

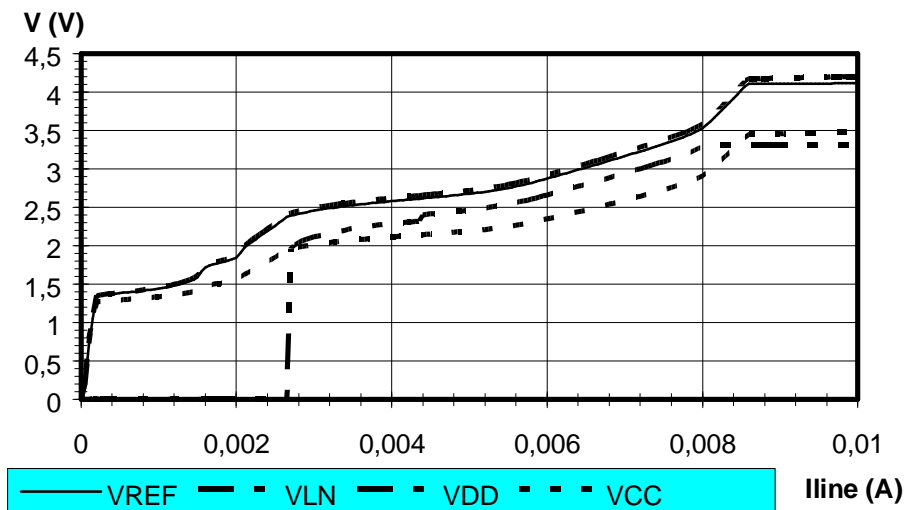


Fig. 7 Low voltage behavior in line powered condition

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

Adjustments and performances

The reference voltage, V_{ref} , can be adjusted by means of an external resistor R_{va} . It can be increased by connecting the R_{va} resistor between pins REG and SLPE, or decreased by connecting the R_{va} resistor between pins REG and LN (see fig. 8). In line powered application, using the voltage reduction reduces the peripheral supply capabilities: V_{In} must be at least 0.25 V higher than V_{dd} . To ensure correct operation, it is not advised to adjust V_{ref} at a value lower than 3 V or higher than 7 V (the maximum operating voltage of 12 V must be guaranteed by the application as well as the safe die operating temperature). These adjustments will slightly affect a few parameters: there will be a small change in the temperature coefficient of V_{ref} and a slight increase in the spread of this voltage reference due to matching between internal and external resistors. Furthermore, the R_{va} resistor connected between REG and LN will slightly affect the apparatus impedance (see section “set impedance”).

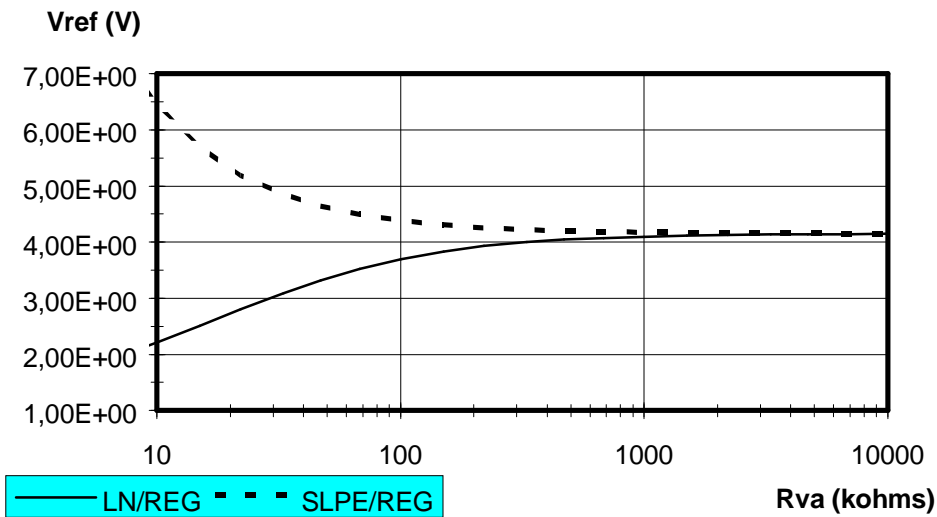


Fig. 8 Influence of the R_{va} resistor between REG and SLPE or between REG and LN

The DC slope of the voltage on pin LN is influenced by the R_{slpe} resistor as shown in fig. 9. The value of R_{slpe} may be slightly modified even if the preferred one is 20 Ω , changing this value will affect more than the DC characteristics, it also influences the gains, the AGC characteristics, the maximum output swing on the line and the low voltage threshold I_{th} .

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

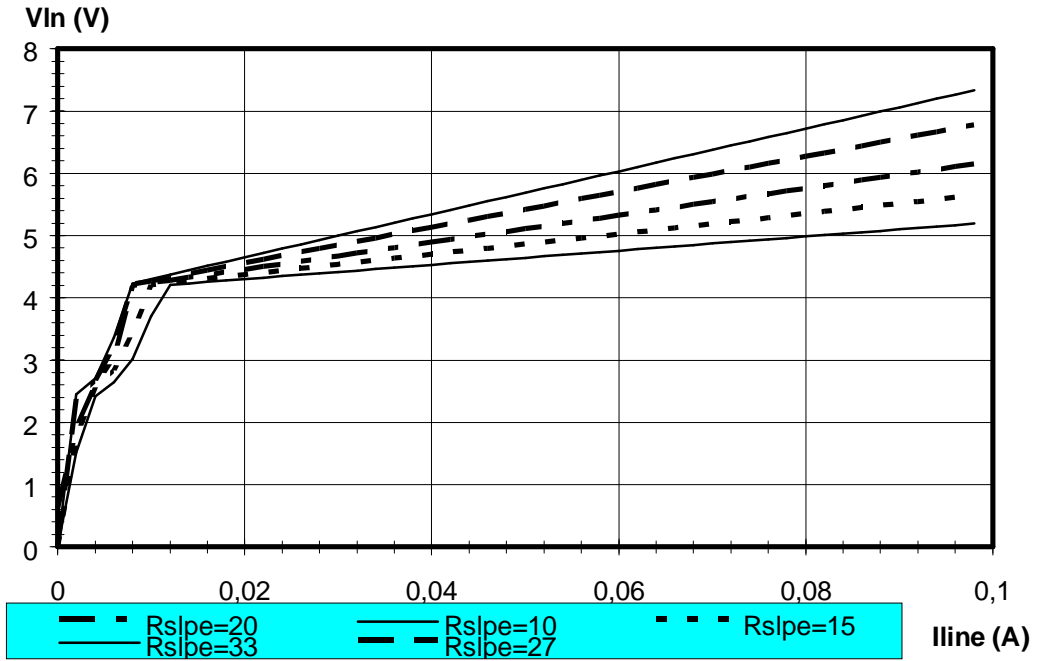


Fig. 9 Influence of Rslpe on the DC characteristics

3.1.2 Supplies for peripherals

Fig. 10 shows the architecture of the supply block.

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

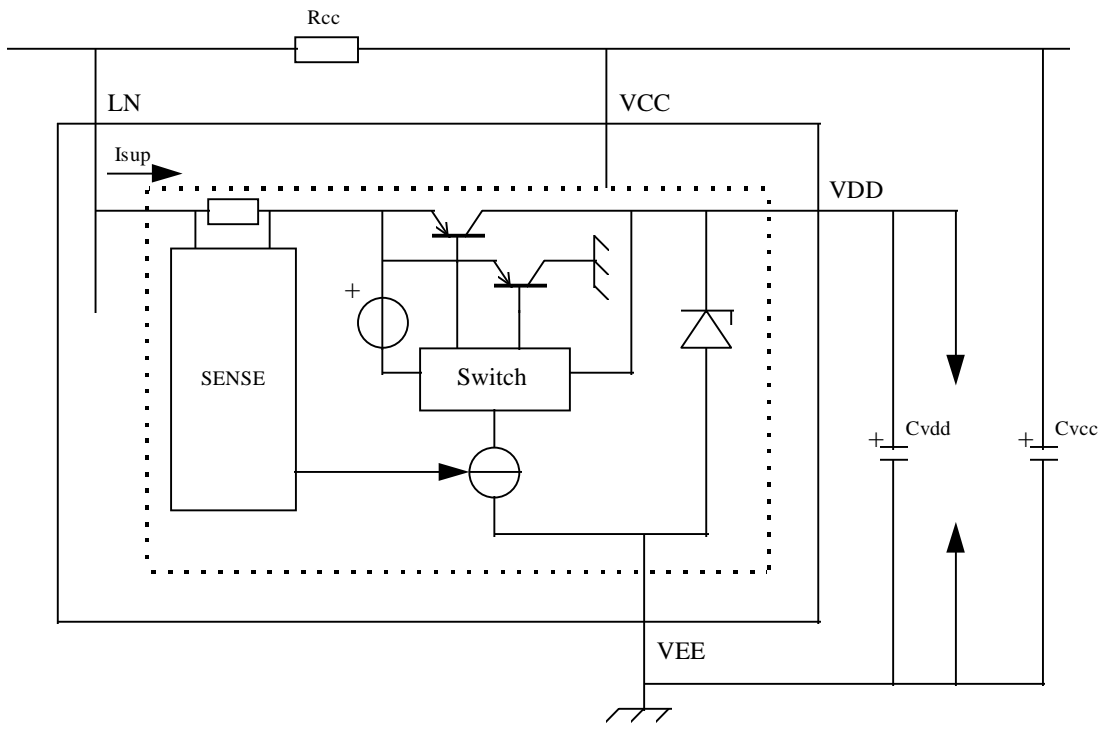


Fig. 10 Configuration of the supplies

3.1.2.1 Supply VCC

Principle of operation

The supply voltage at pin VCC is normally used to supply the internal circuitry of the TEA1114A. However, a small current can be drawn to supply peripheral circuits having VEE as ground reference. The VCC supply voltage depends on the current consumed by the IC and the peripheral circuits as shown by the following formula:

$$VCC = VCC0 - Rcc_{int} \times (I_{rec} + I_p)$$

$$VCC0 = V_{in} - Rcc \times I_{cc}$$

I_{rec} = internal current necessary to supply the receive output amplifier to realize an AC peak voltage V_{qr} across the earpiece impedance R_I

$$I_{rec} = V_{qr} / (\pi \times R_I)$$

Rcc_{int} = Rcc // internal equivalent impedance between VCC and VEE

Rcc_{int} is the output impedance of the voltage supply point. As can be seen from fig.5, the internal supply current I_{cc} depends on the voltage on the pin VCC, it means that the impedance of the internal circuitry connected between VCC and VEE is not infinite. While supplying a peripheral circuit on VCC, the I_p supply current flowing through the Rcc resistor decreases the value of the voltage on the pin VCC and then reduces the I_{cc} consumption. So, the impedance to use in combination with I_p and I_{rec} is not Rcc but Rcc_{int} which includes in parallel the impedance of the internal circuitry connected between VCC and VEE. For a line current equal to 15 mA and Rcc equal to 620 Ω , this Rcc_{int} impedance is approximately 550 Ω .

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

As VCC is limited to a minimum value to ensure correct operation, Ip will be limited to a maximum value. The limit is imposed by the requirement to maintain a minimum permitted voltage between VCC and SLPE which is called Vmin. So the maximum current available depends on the DC settings of the IC: Vref, Rcc(+Rz), Rslpe and the required AC signal level at the line and receive outputs. To simplify the calculation, we will use the worst case for Rccint, which is Rcc, it gives:

$$VCC = VIn - Rcc (Icc + Irec)$$

$$VCC = Vref + Rslpe (Iline - Icc - Irec) - Rcc (Icc + Irec)$$

$$VCCmin = Vmin + Rslpe (Iline - Icc - Irec - Ip)$$

$$Ipmax = (VCC - VCCmin) / Rcc$$

$$Ipmax = (Vref - Vmin) / (Rcc - Rslpe) - [Rcc (Icc + Irec)] / (Rcc - Rslpe)$$

$$Vmin = 1.7 V + VIn [Rslpe / (Zline // Rcc)]$$

Adjustments and performances

As the impedance connected between LN and VCC also determines the set impedance, the easiest way to increase the current capability of the supply point VCC is to increase the reference voltage Vref by connecting a resistor Rva between pins REG and SLPE (see 3.1.1).

3.1.2.2 Supply VDD

Principle of operation

VDD is a 3.3 V regulated supply for dialler or microcontroller. In speech mode, VDD is line powered while in trickle mode or in ringer mode it can be externally powered.

When VDD is line powered, it can provide at least 3 mA when VDD equals 3.3 V but its value is typically correlated with the value of the line voltage as follow:

- $VIn < 2.5 V$: $VDD = 0$
- $2.5 V < VIn < 3.55 V$: $VDD \cong VIn - 0.28 V$
- $VIn > 3.55 V$: $VDD = 3.3 V$

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

Fig. 11 shows VDD and VIn versus line current.

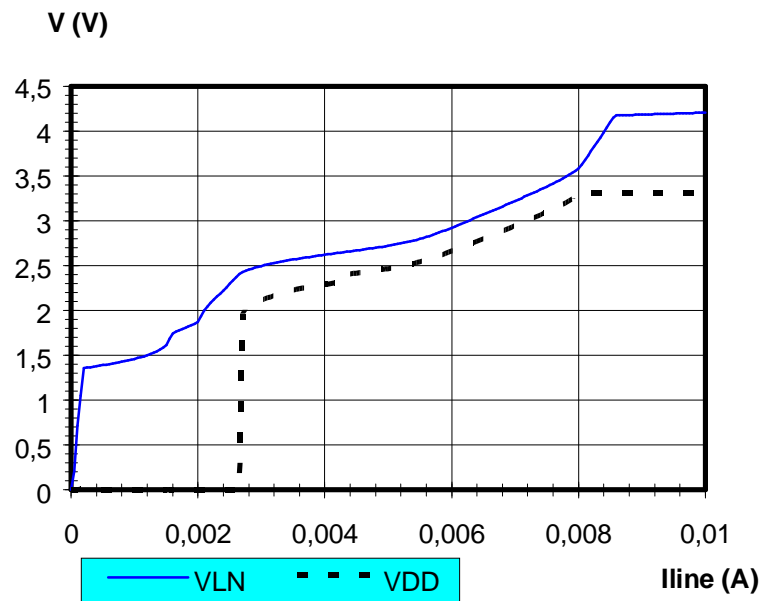


Fig. 11 VDD and VIn versus line current

The correlation between line voltage and VDD is done in order to get a voltage difference between VIn and VDD of at least 0.25 V. On the block diagram, two PNP transistors drive the line current either to VDD or to VEE: when the voltage on LN is higher than $VDD + 0.2$ V the current is driven to VDD, when the voltage on LN is lower than VDD the line current is driven to VEE, when the voltage on LN is between VDD and $VDD + 0.2$ V both transistors are conducting in order to minimize distortion.

When VDD equals 3.3 V, a constant current I_{sup} (4 mA typically) is sunk from LN. This constant current doesn't affect the return loss and its value is taken into account for the AGC characteristic. In this condition, the current I_{dd} available at the output VDD is at least 3 mA. When VDD is lower than 3.3 V, both currents I_{sup} and I_{dd} are reduced accordingly.

In trickle mode or in ringer mode, VDD works as a shunt regulator at 3.3 V. In trickle mode the current consumption of the shunt regulator is dramatically reduced in order to have typically 100 nA when VDD is lower than 1.2 V. In ringer mode, the shunt regulator is able to sink up to 75 mA between VDD and VEE. Fig. 12 shows the current consumptions on VDD.

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

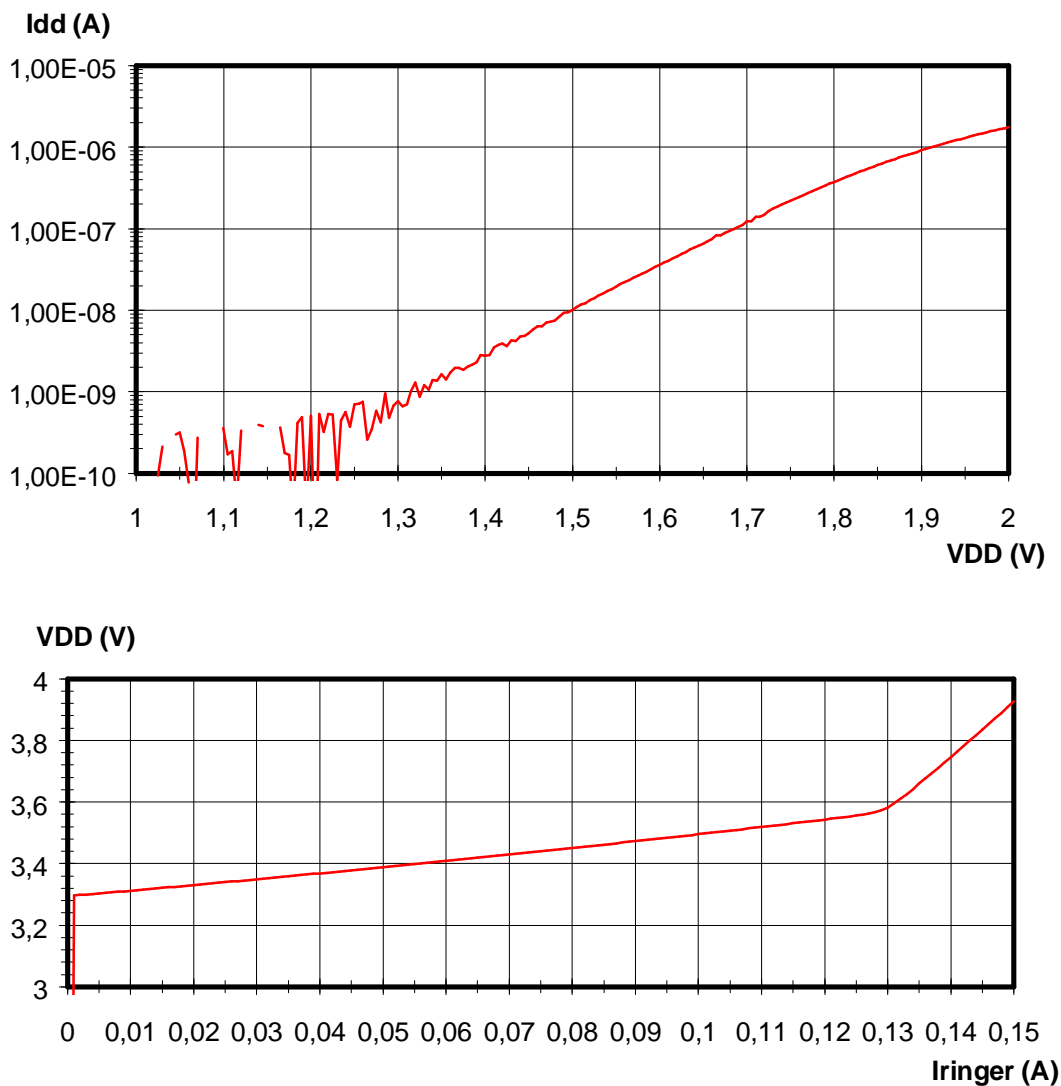


Fig. 12 Current consumption on VDD

NB: Due to this supply structure, the TEA1114A cannot be used in combination with the TEA1083/A, TEA1085/A, TEA1093 or OM5153. In this configuration, the stability may not be possible.

3.2 Set impedance

Principle of operation

The TEA1114A behaves like an equivalent inductance that presents a low impedance to DC (R_{slpe}) and a high impedance (R_p) to speech signals. R_p is an integrated resistance in the order of $17.5\text{ k}\Omega \pm 15\%$. It is in parallel with the external RC realized by R_{cc} and C_{vcc} . Thus, in the audio frequency range, the apparatus impedance

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

(called set impedance) is mainly determined by the Rcc resistor. Fig. 13 shows an equivalent schematic for the set impedance.

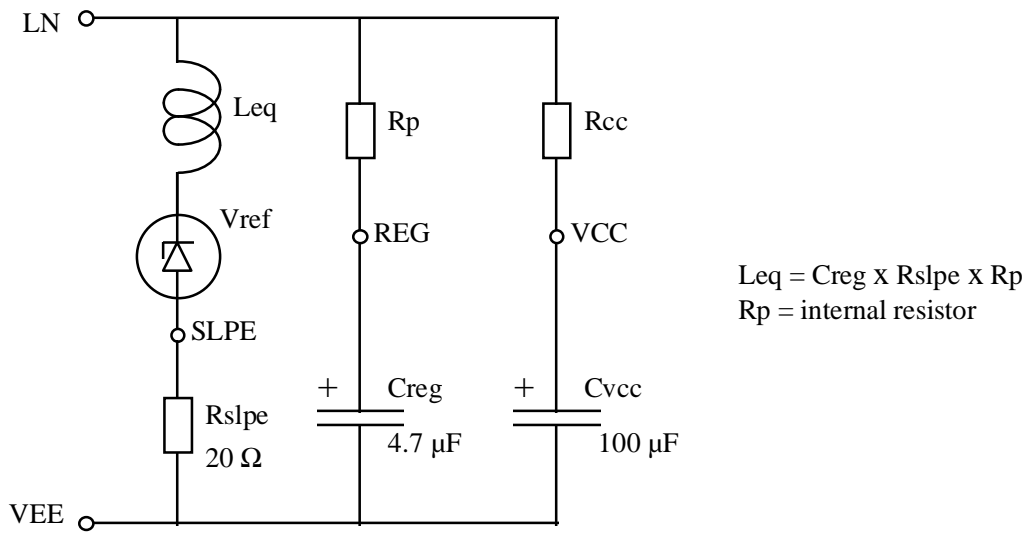


Fig. 13 Equivalent set impedance

Adjustments and performances

When decreasing the reference voltage $Vref$, a resistor is connected between LN and REG in parallel of Rp (see fig. 13) so, slightly modifying the impedance.

If complex set impedance is required, the Rcc resistor is replaced by a complex network (see fig. 32 : $Rcc + Rz // Cz$). The DC resistance which influences the value of VCC becomes $Rcc + Rz$.

3.3 Microphone amplifier

Principle of operation

In fig. 14, the block diagram of the microphone amplifier of the TEA1114A is depicted.

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

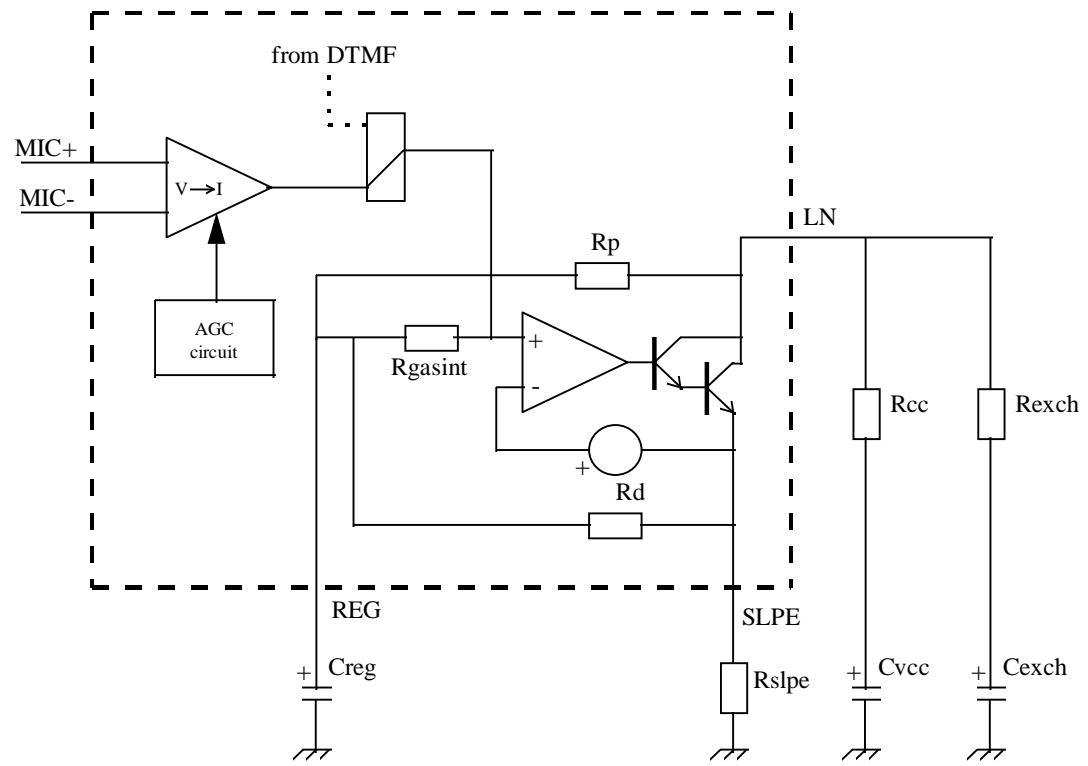


Fig. 14 Microphone channel

The microphone amplifier has symmetrical high input impedances (typically 64 kΩ - 2 times 32 kΩ- between pins MIC+ and MIC- with maximum tolerances of +/- 15%). The input of this microphone amplifier is able to handle AC signals up 18 mVrms with less than 2% total harmonic distortion.

As can be seen from fig. 14, the microphone amplifier itself is built up out of two parts: a preamplifier which realizes a voltage to current conversion, and an end-amplifier which realizes the current to voltage conversion. The overall gain (Gvtx) of the microphone amplifier from inputs MIC+/MIC- to output LN is given by the following equation:

$$G_{vtx} = 20 \times \log A_{vtx}$$

$$A_{vtx} = 2.6 \times (R_{gasint} / R_{refint}) \times (R_i // Z_{line} / R_{slpe}) \times \alpha$$

with:

- R_i = the AC apparatus impedance, R_{cc}//R_p (typically 620 Ω // 17.5 kΩ)
- R_{gasint} = internal resistor realizing the current to voltage conversion (typically 29.5 kΩ with a spread of +/-15%)
- R_{refint} = internal resistor determining the current of an internal current stabilizer (typically 7.25 kΩ with spread of +/- 15% correlated to the spread of R_{gasint})
- Z_{line} = load impedance of the line during the measurement
- α = gain control factor varying from 1 at I_{line} = 15 mA to 0.5 at I_{line} = 75 mA when AGC function is applied (see chapter 3.5 for details)

Using these typical values in the equation and assuming Z_{line} = 600 Ω, we find a gain equal to:

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

$$G_{vtx} = 20 \times \log A_{vtx} = 44 \text{ dB} \quad \text{at } I_{line} = 15 \text{ mA}$$

The different gain controls (AGC; MUTE/) act on the microphone preamplifier stage, modifying its transconductance.

Adjustments and performances

Fig 15 shows the typical frequency response and gain of the microphone amplifier of the TEA1114A.

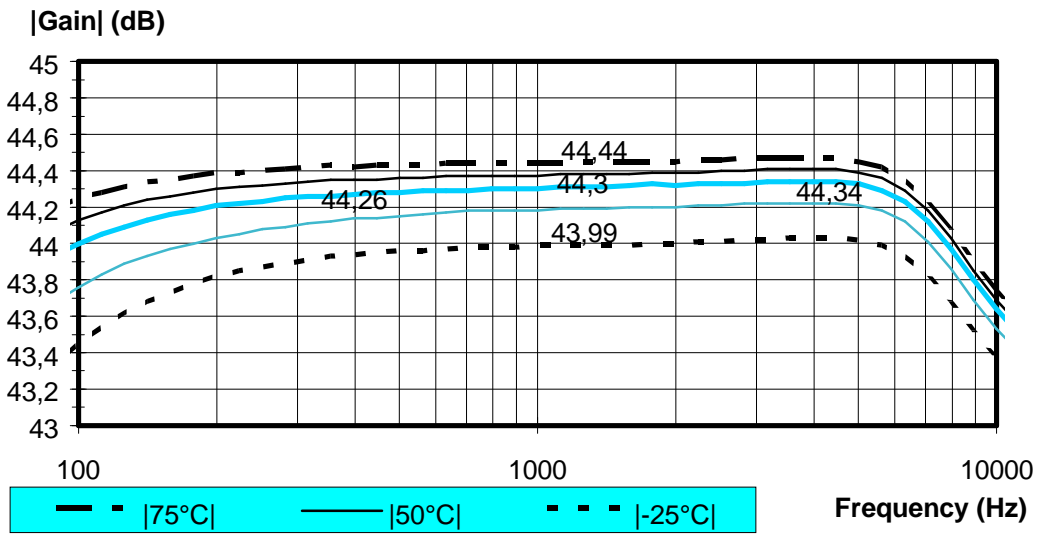


Fig. 15 Microphone gain versus frequency: influence of temperature

Fig 16 shows the distortion of the signal on the line as a function of the line signal at 4 mA, 15 mA and as a function of the microphone signal at 70 mA.

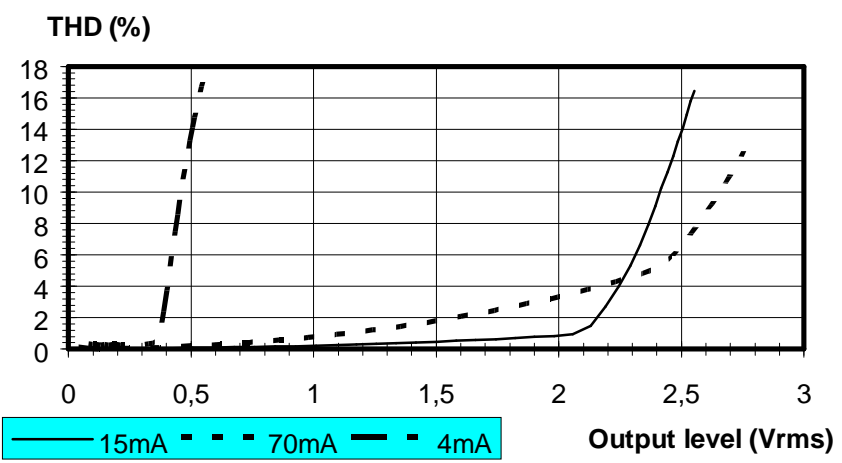


Fig. 16 Distortion on line versus line signal (left) and versus microphone signal on TEA1114A

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

Fig. 17 shows the microphone noise (psophometrically weighted: P53 curve) versus line current at nominal gain when a 200 Ω resistor is connected between the inputs MIC+ and MIC-.

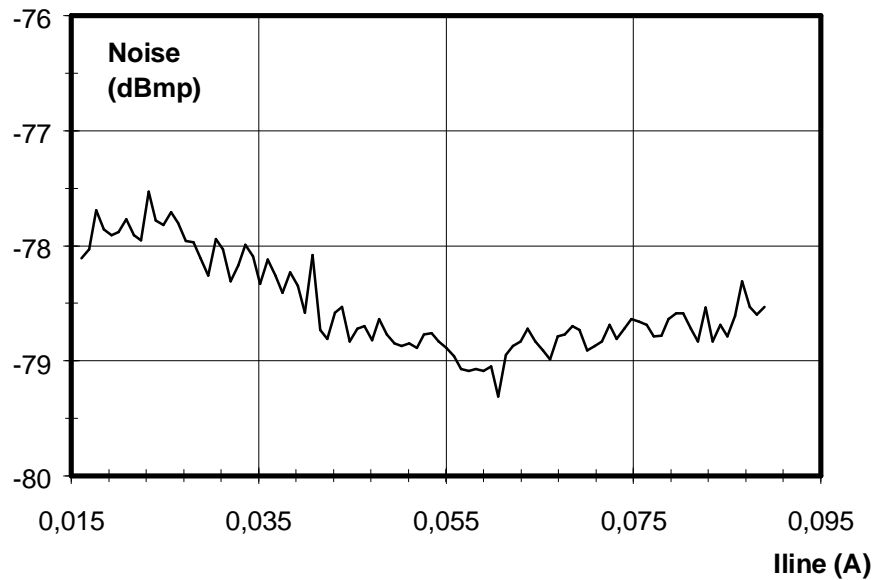


Fig. 17 Microphone noise versus line current

Fig. 18 shows the common mode rejection ratio at 15 mA. Two curves are present in this fig. 18, the first one is the spectrum of the signal on pin LN when a microphone signal is applied on pin MIC- while pin MIC+ is shorted to VEE, the second one is the spectrum of the signal on pin LN when a microphone signal is applied on pins MIC- and MIC+ shorted together. Both signals are at 1 kHz, the difference between the two curves gives the CMRR.

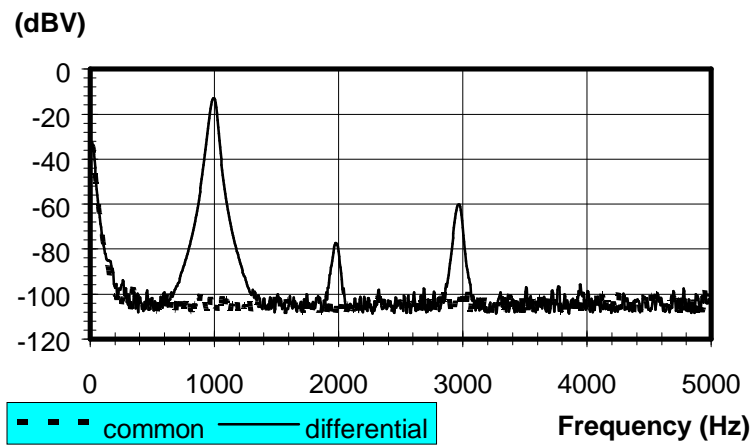


Fig. 18 Common mode rejection ratio on microphone

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

3.4 Receive amplifier block

Principle of operation

In fig. 19, the block diagram of the receive amplifier is depicted.

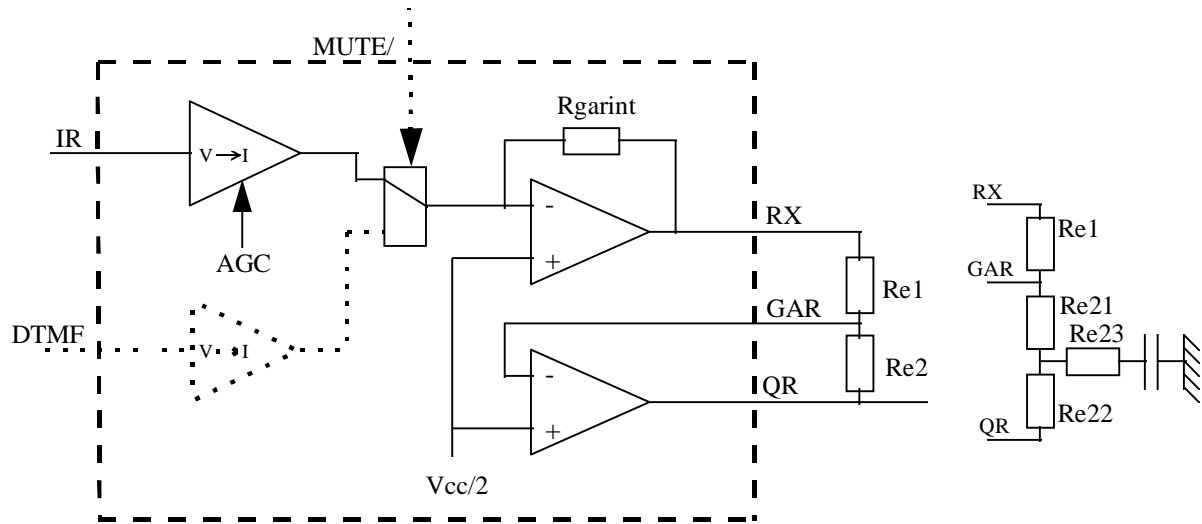


Fig. 19 Receive channel

As can be seen from fig. 19, the receive amplifier block is built up out of three parts: a preamplifier which realizes a voltage to current conversion followed by an end-amplifier which realizes the current to voltage conversion at RX and the earpiece amplifier itself with a gain externally determined. The preamplifier has an asymmetrical high input impedance between pins IR and VEE. It is equal to 20 kΩ with a maximum tolerance of +/-15%. The earpiece amplifier of the TEA1114A is able to drive loads down to an impedance of 150 Ω at QR while the receive amplifier can only drive loads down to 10 kΩ. The output capability is suitable for several kind of earpieces and can drive either dynamic, magnetic or piezo-electric earpieces. In case of magnetic or dynamic earpieces, a capacitor in series is required for decoupling. The overall gain Gvrx of the receive amplifier from input IR to output RX is given by the equation:

$$G_{vrx} = 20 \times \log A_{vrx}$$

$$A_{vrx} = 2.41 \times R_{garint}/R_{refint} \times \alpha$$

with:

Rgarint = internal resistor realizing the current to voltage conversion (typically 134 kΩ with a spread of +/-15%)

a Rrefint = internal resistor determining the current of an internal current stabilizer (typically 7.25 kΩ with spread of +/- 15% correlated to the spread of Rgarint)

α = gain control factor varying from 1 at Iline = 15 mA to 0.5 at Iline = 75 mA when AGC function is applied (see chapter 3.5 for details)

Using these typical values in the equation, we find a gain equal to:

$$G_{vrx} = 20 \times \log A_{vrx} = 33 \text{ dB} \quad \text{at } I_{line} = 15 \text{ mA}$$

The different gain controls (AGC; MUTE/) act on the receive preamplifier stage, modifying its transconductance.

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

Adjustments and performances

The gain of the earpiece amplifier is externally determined, it can be adjusted between -14 and +12 dB. For this purpose, fig. 19 shows two ways of setting this gain. 33 dB of gain between IR and RX compensates approximately the attenuation provided by the antisidetone network.

Two external capacitors C_{gar} (connected between GAR and QR) and C_{gars} (connected between GAR and VEE) ensure stability of the earpiece amplifier when the relationship $C_{gars} = 10 \times C_{gar}$ is fulfilled. The capacitor C_{gar} provides a first order low pass filter, which cut-off frequency is determined with R_{e2} , furthermore, if a high-pass filter is required a capacitor can be inserted in series with R_{e1} . Fig. 20 shows the frequency response and the typical gain of the receive amplifier from IR to RX at different temperatures.

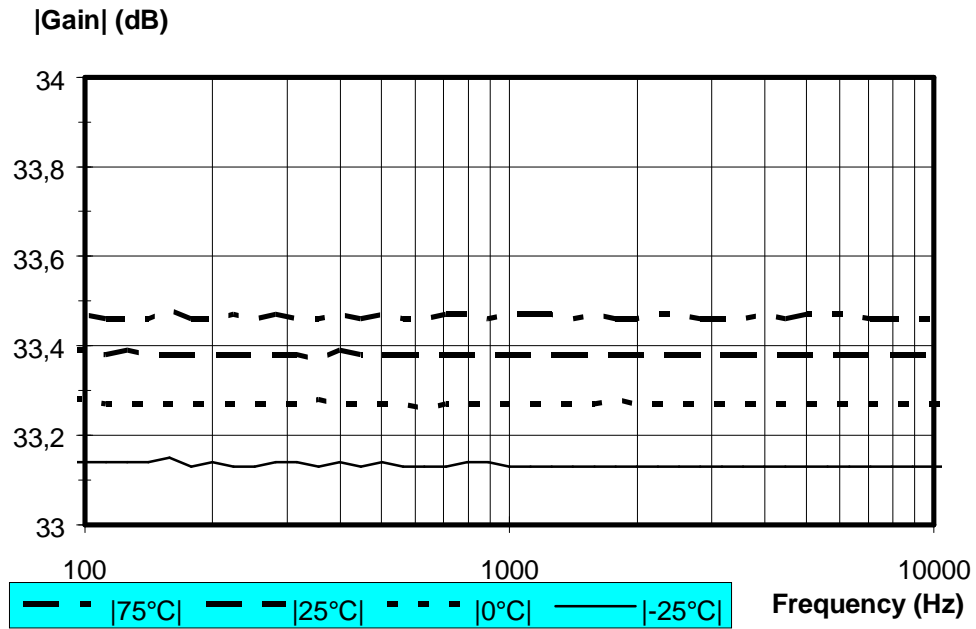


Fig. 20 Receive gain versus frequency: influence of temperature

The maximum output swing on QR depends on the DC line voltage, the R_{cc} resistor, the I_{cc} current consumption of the circuit, the I_p current consumption of the peripheral circuits and the load impedance on QR.

The receiving input IR can handle signals up to 18 mVrms with less than 2% THD. Fig. 21 shows the distortion on QR when the limitation is related to the input voltage for a line current equal to 75 mA with a gain of 0 dB on this amplifier. Fig. 22 shows the distortion of the signal on QR as a function of the rms signal on QR with loads of 450 Ω and 150 Ω at a line current of 15 mA and 0 dB of gain.

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

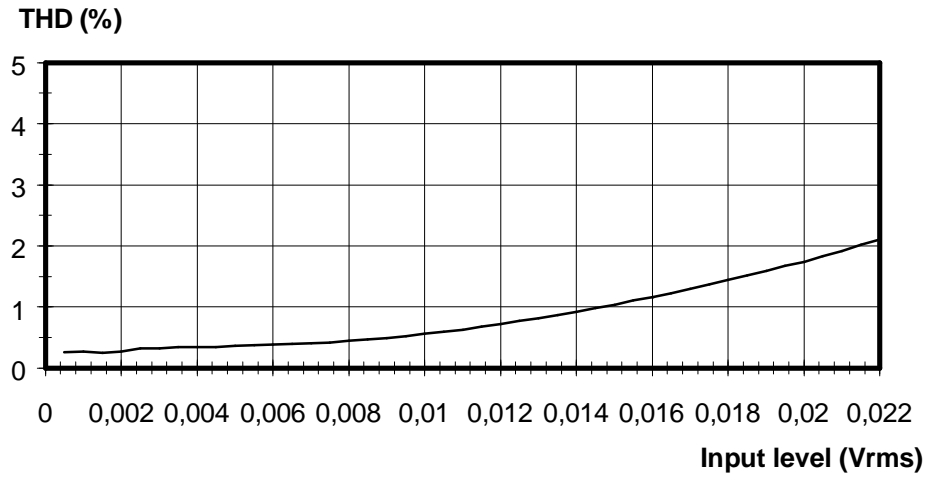


Fig. 21 Distortion on QR versus input signal on IR

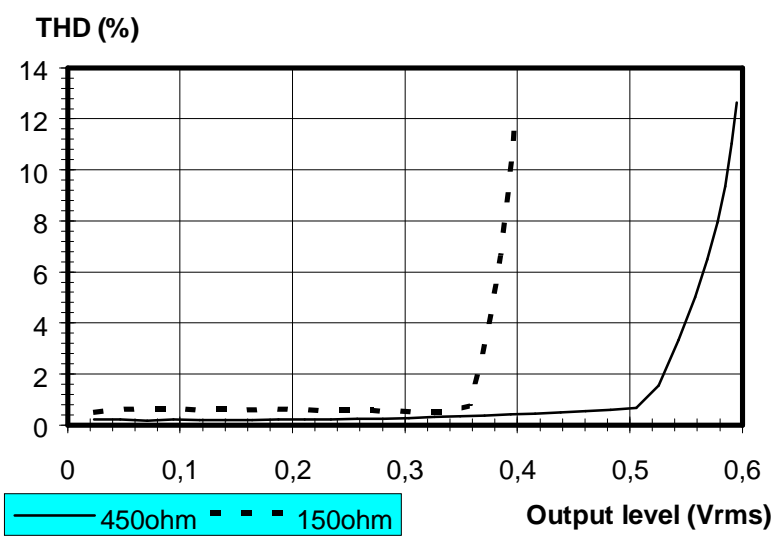


Fig. 22 Distortion on QR versus level on 450 Ω and 150 Ω loads

Fig. 23 shows the noise on QR loaded with 150 Ω (psophometrically weighted: P53 curve) as a function of the line current with a gain of 0 dB on this amplifier. This curve has been done with an open input IR. With the antisidetone network connected to the input IR, part of the microphone noise generated on the line will be added but, thanks to the low microphone noise value, the effect is almost negligible.

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

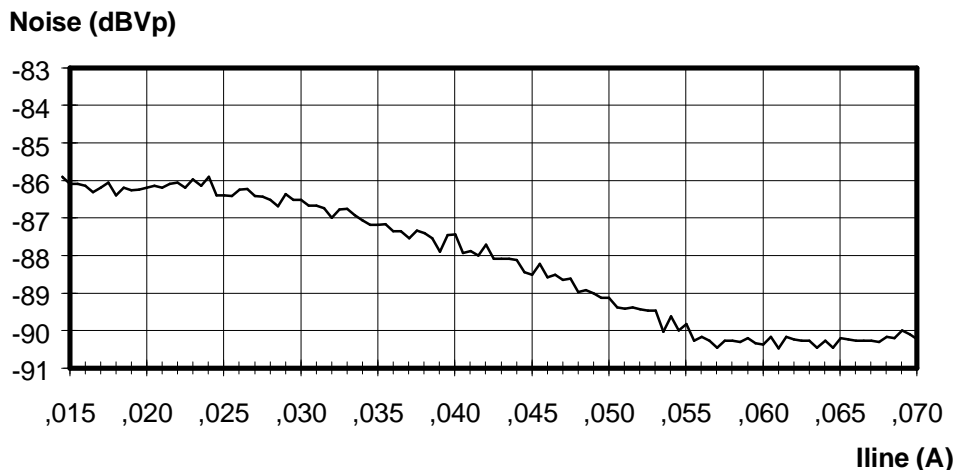


Fig. 23 Noise on QR

3.5 Automatic gain control

Principle of operation

The TEA1114A performs automatic line loss compensation. The automatic gain control varies the gain of the microphone and receive amplifiers in accordance with the DC line current. To enable this AGC function, the pin AGC must be connected to the pin VEE. For line currents below a current threshold, I_{start} (typically 23 mA), the gain control factor α is equal to 1, giving the maximum value to the gains G_{vtx} and G_{vr} . If this threshold current is exceeded, the gain control factor α is reduced and then the gains of the controlled microphone and receive amplifiers are also reduced. When the line current reaches an other threshold current, I_{stop} (typically 58 mA), the gain control factor α is limited to its minimum value equal to 0.5, giving the lower value to the microphone and receive controlled gains. The gain control range of both amplifiers is typically 6 dB, which corresponds approximately to a line length of 5 km (0.5 mm twisted pair copper) with an attenuation of 1.2 dB/km.

The attenuation is correlated to the current I_{agc} sunk at pin AGC: when this current is lower than typically 4.5 μA the gains are maximum, when this current is higher than typically 14 μA the gains are minimum. This current is proportional to the voltage between pins SLPE and VEE. There is an internal resistor which sets I_{start} and I_{stop} , adding one externally in series (between pins AGC and VEE) reduces I_{agc} and increases the values of I_{start} and I_{stop} .

Adjustments and performances

The AGC of the TEA1114A can be used with different exchange supply voltages and different feeding bridge resistances. For this purpose, a resistor R_{agc} , can be inserted between pins AGC and VEE. This R_{agc} resistor increases both threshold currents I_{start} and I_{stop} proportionally. Fig. 24 shows the control of the microphone gain versus the line current for different values of R_{agc} . When no AGC function is required, the AGC pin must be left open, then the control factor α equals to 1 and both controlled gains are at their maximum values.

When $R_{agc} = 0$ and the value of I_{start} is too high, increasing the value of R_{slpe} reduces proportionally I_{start} and shifts the AGC to lower currents. In this case, the value of I_{stop} is also reduced and the gains are modified. If the value of R_{slpe} has to be increased a lot, it is possible to restore the typical gains by connecting in parallel an RC series network which makes a total AC impedance of 20 Ω .

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

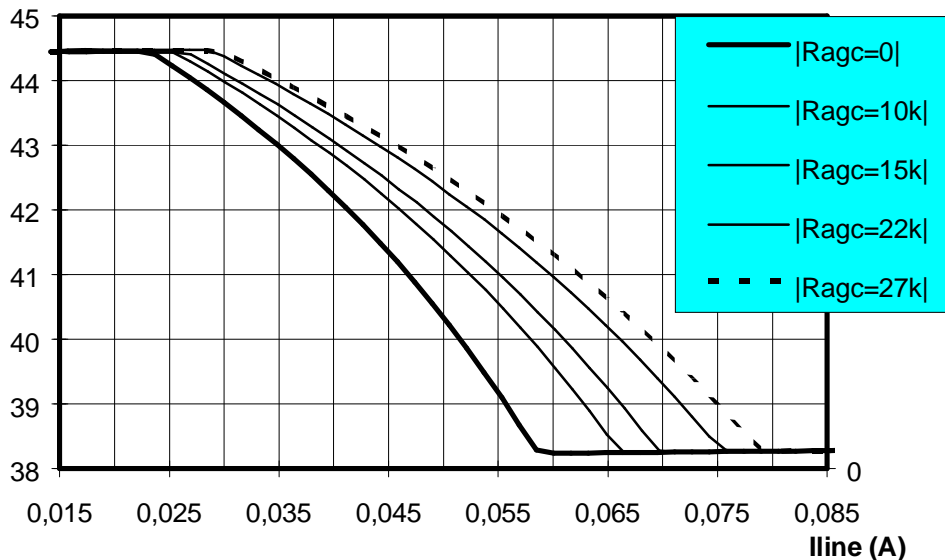


Fig. 24 AGC on the microphone gain versus line current and R_{agc}

3.6 DTMF amplifier

principle of operation

In fig.25, the block diagram of the DTMF channel of the TEA1114A is depicted.

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

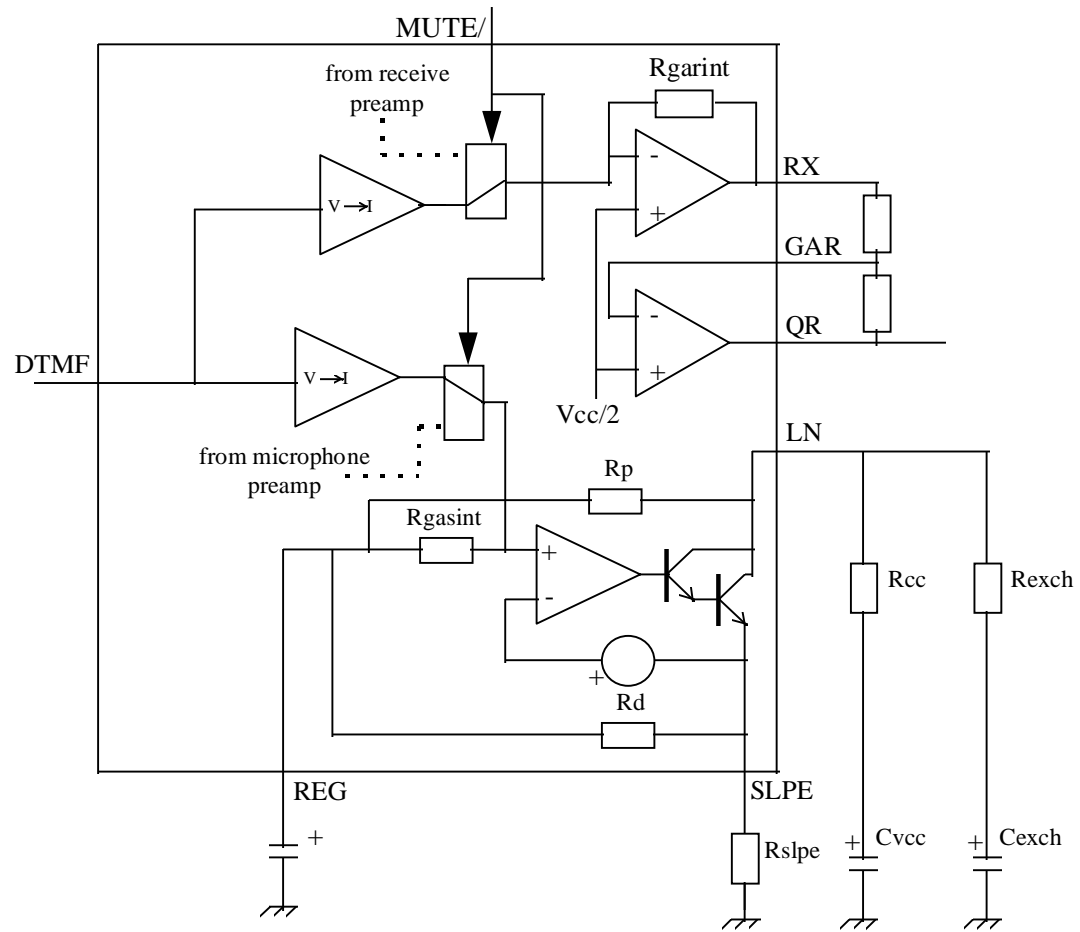


Fig. 25 DTMF channel of the TEA1114A

The DTMF amplifier has an a-symmetrical high input impedance of 20 kΩ between pins DTMF and VEE with a maximum spread of +/-15%. The input is biased at VEE, so when the input DTMF signal is polarized at VEE, the decoupling capacitor is not necessary. The DTMF amplifier is built up out of two parts: a preamplifier which realizes the voltage to current conversion and the same end-amplifier as the microphone amplifier. No AGC is applied to the DTMF channel. The overall gain (Gvmf) of the DTMF amplifier from input DTMF to output LN is given by the following equation:

$$G_{vmf} = 20 \times \log A_{vmf}$$

$$A_{vmf} = 0.246 \times (R_{gasint} / R_{refint}) \times (R_i // Z_{line} / R_{slpe})$$

with:

- R_i = the AC apparatus impedance, R_{cc}//R_p (typically 620 Ω // 17.5 kΩ)
- R_{gasint} = internal resistor realizing the current to voltage conversion (typically 29.5 kΩ with a spread of +/-15%)
- R_{refint} = internal resistor determining the current of an internal current stabilizer (typically 7.25 kΩ with spread of +/- 15% correlated to the spread of R_{gasint})

a

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

Z_{line} = load impedance of the line during the measurement

Using these typical values in the equation and assuming $Z_{line} = 600 \Omega$, we find a gain equal to:

$$G_{vmf} = 20 \times \log A_{vmf} = 26 \text{ dB}$$

Furthermore, the DTMF signal is attenuated and sent to RX and QR as confidence tone.

Fig. 26 shows the frequency response of the DTMF amplifier at 15 mA and different temperatures.

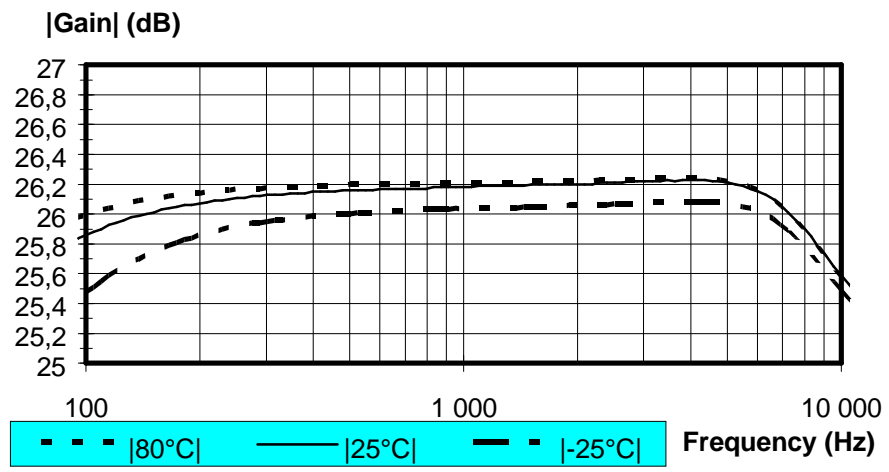


Fig. 26 DTMF gain versus frequency: influence of temperature

The input of the DTMF amplifier can handle signals up to 110 mVrms with less than 2% THD. Fig. 27 shows the distortion on line versus the rms input signal at $I_{line} = 15 \text{ mA}$.

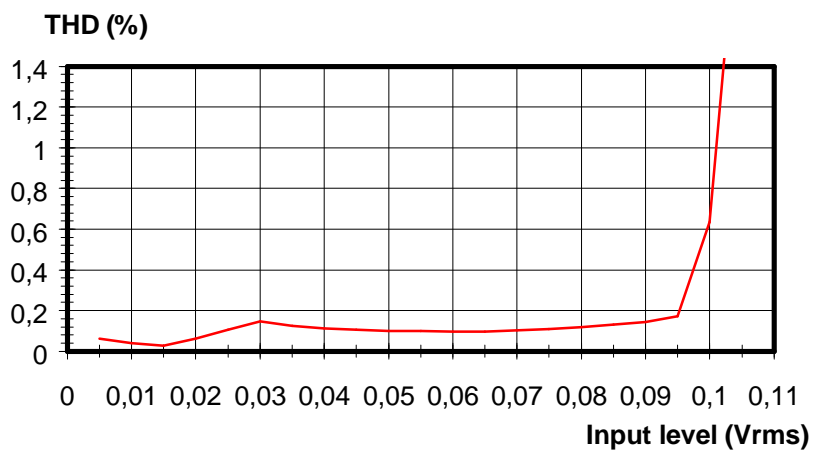


Fig. 27 Distortion of the DTMF signal on line versus input signal

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

3.7 “MUTE” function

Principle of operation

The “mute” realizes an electronic switching between the speech mode and the dialling mode. If a low level is applied to the MUTE/ input, both the microphone and the receive channels are disabled while the DTMF channel is enabled. By applying a high level or leaving pin MUTE/ open the microphone and the receive channels are enabled while the DTMF channel is disabled. The MUTE/ input has a pull-up structure to VCC, so it can be directly driven by an open drain output. Nevertheless, in case of I/O structure on the microcontroller side, a push-pull output structure is recommended to polarize properly the input of the microcontroller when VCC varies (no current will flow from VDD to VCC via this pin). The threshold voltage level is 0.65 V typically with a temperature coefficient of -2 mV/°C. Fig. 28 shows the microphone gain reduction and MUTE/ input current versus MUTE/ input voltage.

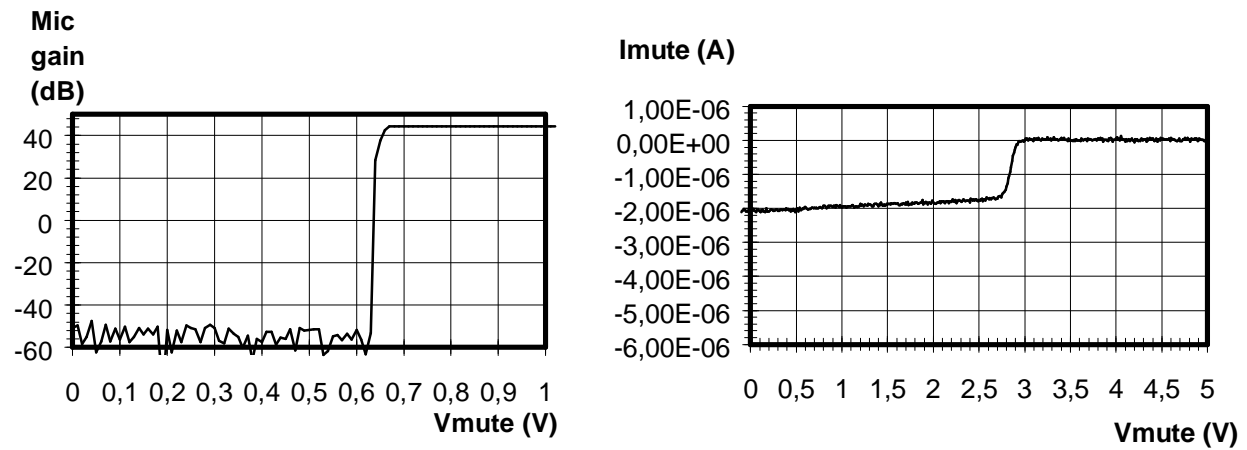


Fig. 28 Microphone gain and MUTE/ input current versus MUTE/ input voltage

Adjustments and performances

Fig. 29 shows the microphone and receive amplifier gain reduction at Iline = 15 mA for an input signal of 1 kHz. Two curves are present on these graphics, the first one shows the spectrum of the signal on the line (or on QR) when a signal is applied on the microphone inputs (or respectively on IR) and when MUTE/ is at a high level, the second one shows the same signal when pin MUTE/ is at a low level. The difference between the two curves at this frequency gives the gain reduction.

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

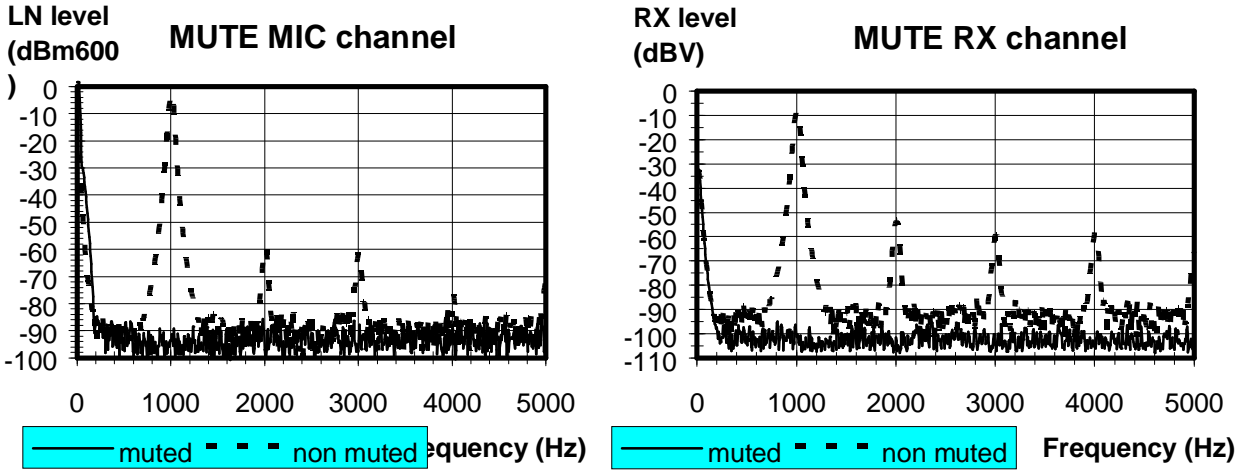


Fig. 29 Microphone and receive gain reduction in "mute" condition

The "mute" function works down to a voltage on VCC equal to about 1.65 V, below this threshold, the microphone and receive amplifiers remain always enabled independently of the MUTE/ input level. The maximum voltage allowed at the MUTE/ input is VCC + 0.4 V and the minimum is GND-0.4 V.

3.8 Anti-sidetone network

Principle of operation

To avoid the microphone signal to come back with a too high level in the receive channel, the anti-sidetone circuit uses the microphone signal from pin SLPE (which is in opposite phase) to cancel the microphone signal at the IR input of the receive amplifier. The anti-sidetone bridge already used for the TEA111x (or TEA106x) families or a conventional Wheatstone bridge as shown in fig. 30 may be used for the design of the anti-sidetone network.

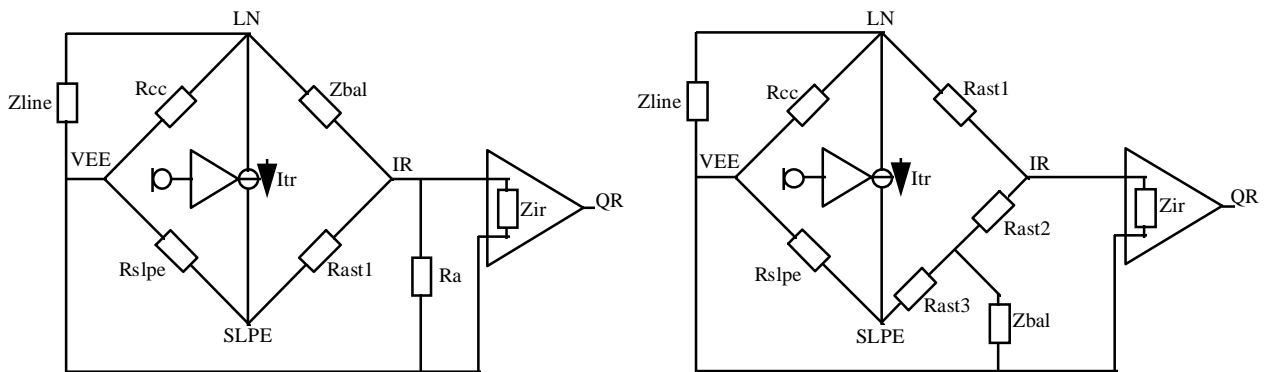


Fig. 30 Wheatstone bridge (left) and TEA111x family anti-sidetone bridge (right)

The TEA111x (or TEA106x) family anti-sidetone bridge has the advantage of a relative flat transfer function in the audio frequency range between the input IR and the output RX, both with real and complex set impedances. Furthermore, the attenuation of the bridge for the receive signal (between pins LN and IR) is independent of the

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

value chosen for Zbal after the set impedance has been fixed and the condition shown in equation (a) is fulfilled. Therefore, readjustment of the overall receive gain is not necessary in many cases.

Compare to the previous one, the Wheatstone bridge has the advantages of needing one resistor less and a smaller capacitor in Zbal. But the disadvantages include the dependence of the attenuation of the bridge on the value chosen for Zbal and the frequency dependence of that attenuation moreover, the input stage may introduce some distortion on high level signal. This requires some readjustment of the overall receive gain.

3.8.1 TEA111x family bridge

The anti-sidetone circuit is composed of: Rcc//Zline, Rast1, Rast2, Rast3, Rslpe and Zbal. Maximum compensation is obtained when the following conditions are fulfilled:

$$Rslpe \times Rast1 = Rcc \times (Rast2 + Rast3) \quad (a)$$

$$k = [Rast2 \times (Rast3 + Rslpe)] / (Rast1 \times Rslpe)$$

$$Zbal = k \times Zline$$

The scale factor k is chosen to meet the compatibility with a standard value of capacitor for Zbal.

In practice, Zline varies strongly with line length and line type. Consequently, the value for Zbal has to be chosen to fit with an average line length giving acceptable sidetone suppression with short and long lines. The suppression further depends on the accuracy with which Zbal equals this average line impedance.

Example

Let's optimize for a theoretical equivalent average line impedance shown in Fig. 31.

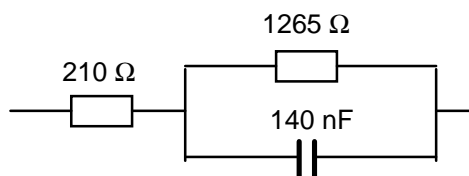


Fig. 31 Equivalent average line impedance

For compatibility of the capacitor value in Zbal with a standard capacitor value from the E6 series (220 nF):

$$k = 140 / 220 = \mathbf{0.636}$$

For Rast2, a value of 3.92 kΩ has been chosen. So, using the previous equations, we can calculate Zbal, Rast1, Rast3. We find Rast1 = 130 kΩ, Rast3 = 390 Ω, and for Zbal **130 Ω in series with 220 nF // 820 Ω**.

The attenuation of the receive line signal between LN and IR can be derived from the following equation:

$$V_{ir} / V_{ln} = (Z_{ir} // Rast2) / [Rast1 + (Z_{ir} // Rast2)]$$

If $Rast2 \gg (Rast3 // Zbal)$.

With the values used in this example, it gives 32 dB at 1 kHz.

Zir is the receive amplifier input impedance, typically 20 kΩ.

**TEA1114A transmission circuit with dialler
interface and regulated strong supply****Application Note**

3.8.2 Wheatstone bridge

The conditions for optimum suppression are given by:

$$Z_{bal} = (R_{ast1} / R_{slpe}) \times (R_{cc} // Z_{line})$$

Also, for this bridge type, a value for Z_{bal} has to be chosen that corresponds with an average line length.

The attenuation of the received line signal between LN and IR is given by:

$$V_{ir} / V_{in} = (Z_{ir} // R_{ast1} // R_a) / [Z_{bal} + (Z_{ir} // R_{ast1} // R_a)]$$

R_a is used to adjust the bridge attenuation; its value has no influence on the balance of the bridge.

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

4. APPLICATION COOKBOOK

In this chapter, the procedure for making a basic application is given. Referring to fig. 32, the design flow is given as a number of steps which should be made. As far as possible for every step, the components involved and their influence on every step are given.

Step	Adjustment
DC setting :	
Adjust the DC setting of the TEA1114A to the local PTT requirements.	
Voltage LN-VEE	This voltage can be adjusted by changing Vref: increased up to 7 V with the Rva resistor between pins REG and SLPE (or decreased down to 3 V with a resistor between REG and LN).
DC slope	The DC slope might be modified by changing the value of Rslpe (this is not advised: all gains are modified, AGC characteristic is modified).
Supply point VCC	In line powered applications, depends on the values of Vref and the resistive part of the impedance network ($R_{cc} + R_z$).
Artificial inductor	Its value can be adjusted by changing the value of Creg: a smaller value speeds-up the DC current shape during transients but decreases the value of the inductance and therefore affects the BRL at low frequencies.
Impedance and sidetone :	
After setting the required set impedance, the sidetone has to be optimized using the sidetone network in order to minimize the loop gain in all line conditions. AGC can be adjusted at that step.	
Application impedance	The BRL is adjusted with the impedance network connected between LN and VCC ($R_{cc} + R_z // C_z$).
Sidetone	Adjust Zbal (Rbal1, Rbal2, Cbal) according to the line characteristics.
AGC	Internally defined, the characteristics (Istart and Istop) can be shifted to higher line currents with an external Ragc resistor connected between AGC and VEE. In case it is necessary to shift Istart and Istop to lower current values, the value of Rslpe must be increased proportionally (see §3.5).

**TEA1114A transmission circuit with dialler
interface and regulated strong supply****Application Note**

Step**Adjustment**

TEA1114A microphone and receive gains

Microphone gain

The microphone gain of the application has to be adjusted before entering pins MIC+/MIC- of the TEA1114A. It can be reduced by using the resistor Rtx3 which forms a bridge attenuator with Rtx1 and Rtx2.

Ctx1, Ctx2 form a high-pass filter with Rtx1, Rtx2 in series with the input impedance at MIC+/MIC-. A capacitor Cmic forms a low-pass filter with the impedance of the microphone and the resistors Rmicp/Rmicm.

Earpiece gain

The earpiece gain of the application has to be adjusted by means of the resistors Re1 and Re2.

A capacitor in parallel with Re2 forms a low-pass filter, stability is ensured with capacitor $C_{gars} = 10 \times C_{gar}$ between pins GAR and VEE.

The gain between IR and RX is fixed at 33 dB.

TEA1114A DTMF gain

DTMF

The DTMF is selected with a low level on pin MUTE/. Its level on line must be adjusted before entering pin DTMF. The capacitor Cmf can be removed when the input signal is biased at VEE.

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

5. EXAMPLE OF APPLICATION

A demo board (OM5838) is available. As the TEA1114A may be used in various applications, this demoboard includes only the TEA1114A with its basic environment.

Fig. 32 gives the schematic of the basic application of the TEA1114A, fig. 33 gives the schematic of the demoboard while fig. 34 gives its component placement diagram. On these schematics, the capacitors connected with dotted lines and the resistors drawn with dotted lines are indicated for RFI immunity purpose.

According to the application, it is possible to connect the electret microphone to VDD instead of VCC. In this case, the current capability of VDD would be reduced by the electret consumption and the current capability of VCC would be increased by the same value (which would allow a slight increase of the earphone amplifier capability).

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

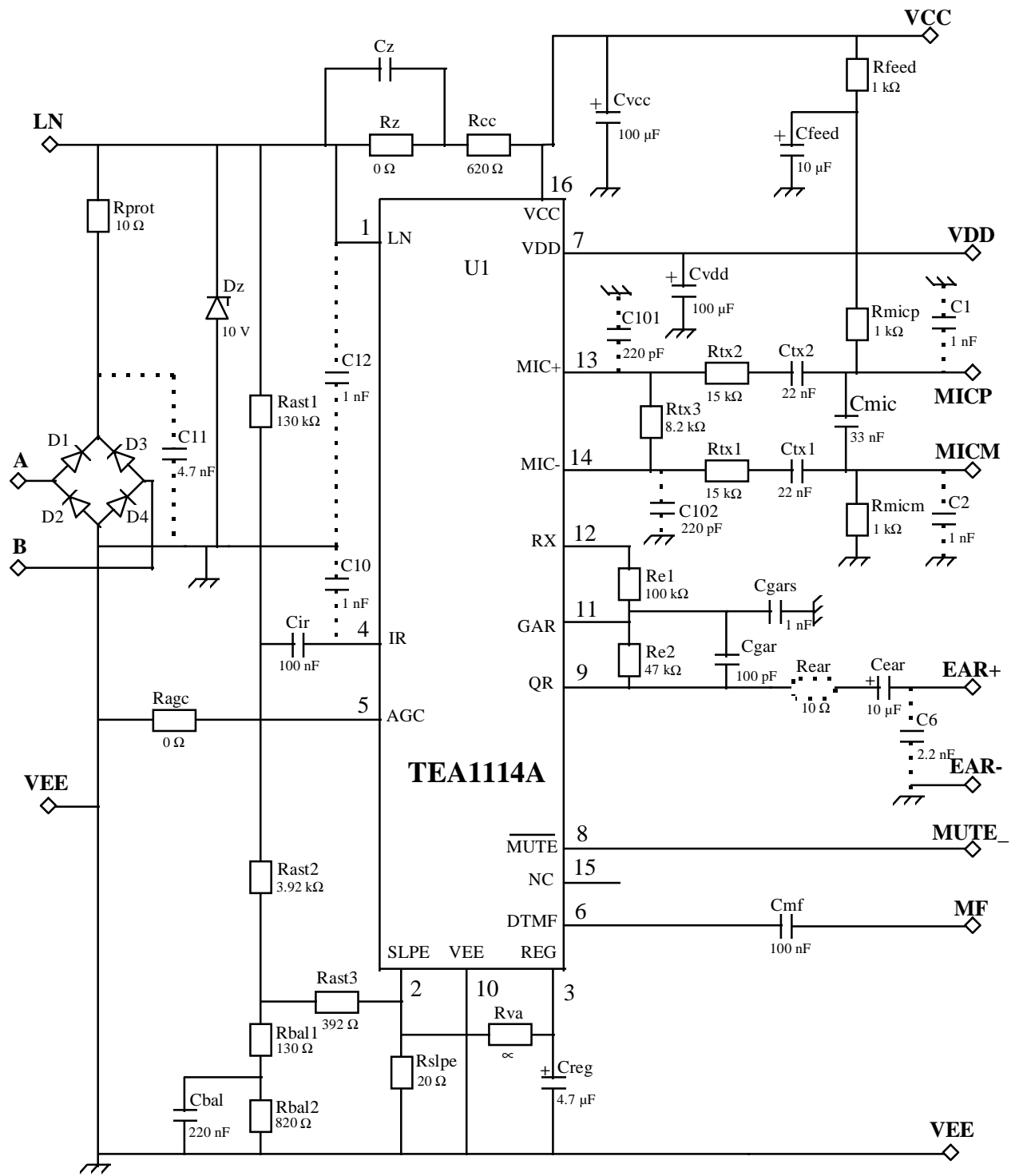


Fig. 32 Basic application of the TEA1114A

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

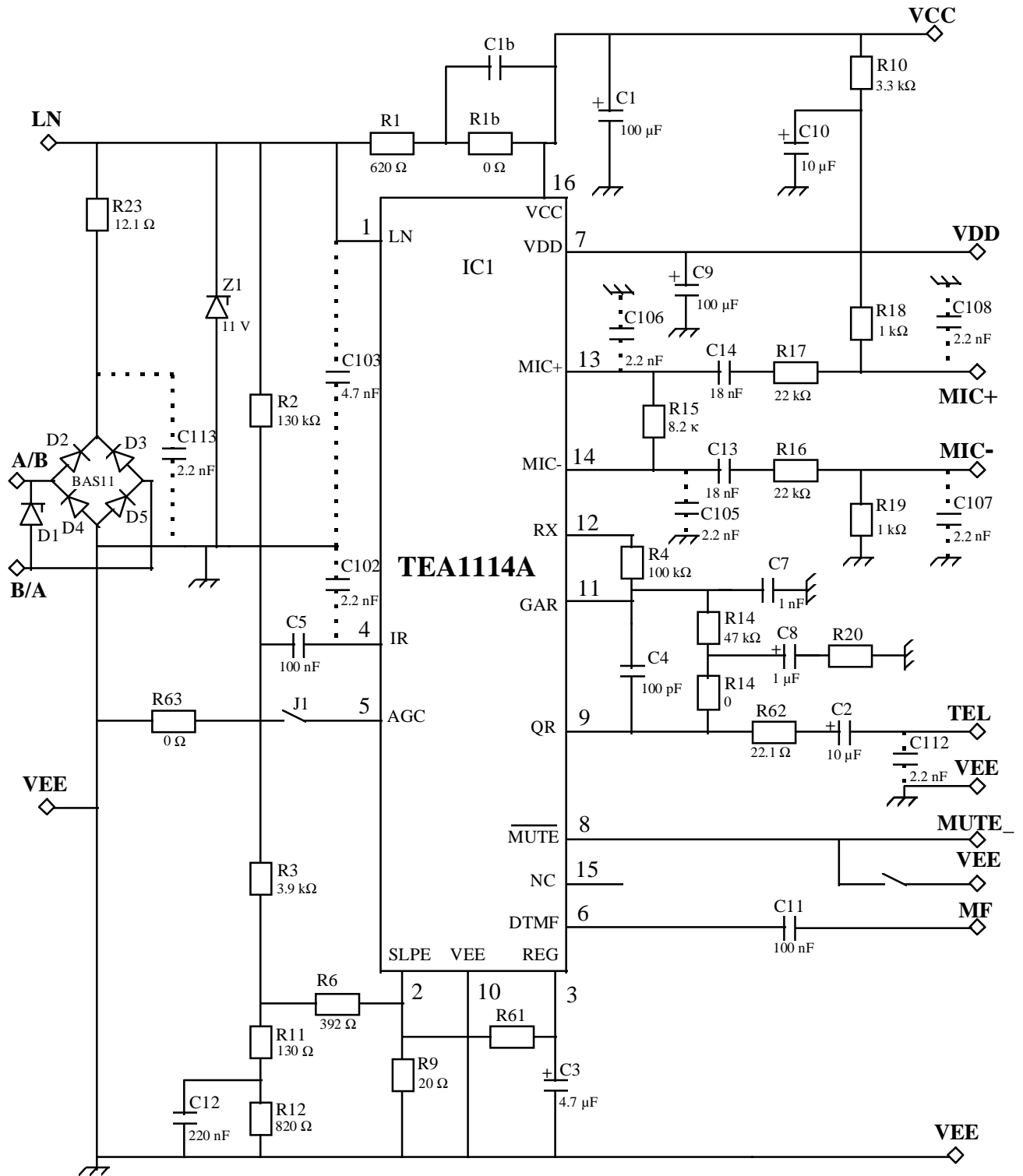


Fig. 33 Circuit diagram of the demoboard

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

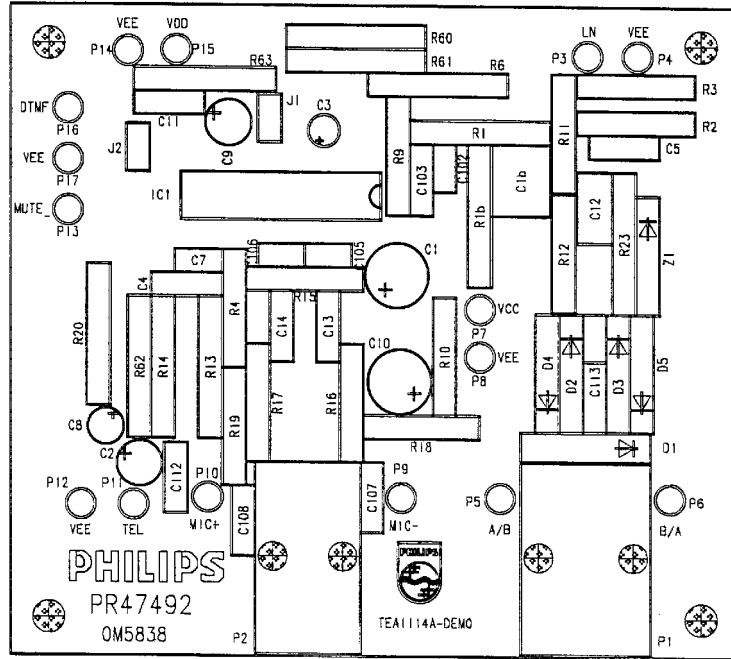


Fig. 34 Component placement diagram of the demoboard

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

6. ELECTROMAGNETIC COMPATIBILITY

As no common international specification exists for RFI immunity, and as different assembly methods may lead to different solutions, only some advices can be provided.

It is advisable to take care of the impedance of the GND, the smallest is always the best. This means that the Ground (VEE) trace must always be as large as possible, the best is to have a second layer dedicated to this purpose.

MIC+/MIC- inputs may also be sensitive (RF signals entering these pins would be amplified). Care has to be taken with the lay-out of the microphone amplifier, which is also helpful for the noise, providing a good decoupling to VEE. Capacitor of a few hundred pF forming low-pass RC filters to VEE may be added at the input of the amplifier (C101, C102).

Low impedance capacitors in parallel with the electrolytic one between VCC and VEE as well as in parallel with the Creg capacitor may help.

Usually a low impedance capacitor connected between LN and VEE (C12) helps for the conducted interferences, but this capacitor is in parallel with the impedance network of the apparatus, so, its value must be small enough.

In general when connections are coming from external environment (e.g. MICP, MICM, A, B on the demoboard), it is better to filter the RFI signal before it influences the close environment of the TEA1114A (e.g. action of C107, C108, C112, C113 on the demoboard).

NB: At very high frequencies (1 to 2 Ghz), the parasitic inductance of the RFI capacitors as well as the length of their connections (about 1 nH per mm) becomes a major concern and may inhibit the effect of these capacitors.

TEA1114A transmission circuit with dialler interface and regulated strong supply

Application Note

7. REFERENCES

- [1] TEA1114A Low voltage transmission circuit with dialler interface and regulated strong supply
Device specification

- [2] TEA1114A Line Interface Demonstration Board
User Manual of OM5838 TEA1114A Line Interface Demonstration Board (report n°: ETT/UM97001.1)

- [3] Philips Semiconductors
Semiconductors for Wired Telecom Systems
Data Handbook -IC03a -

- [4] Philips Semiconductors
Semiconductors for Wired Telecom Systems
Application Handbook -IC03b -

**TEA1114A transmission circuit with dialler
interface and regulated strong supply****Application Note**

APPENDIX LIST OF ABBREVIATIONS AND DEFINITIONS

A-B	Line terminals of application example
AGC	Automatic Gain Control: line loss compensation
BRL	Balance Return Loss: matching between the apparatus impedance and a reference
DTMF	Dual Tone Multi Frequency
EMC	ElectroMagnetic Compatibility
GAR	Earpiece amplifier gain adjustment pin of the TEA1114A
Gvmf	DTMF amplifier gain
Gvrx	Receive gain
Gvtx	Microphone gain
IC	Integrated circuit
Icc	Current consumption of the TEA1114A on VCC
Idd	Current in supply VDD
Iline	Line current
Ip	Current consumption of the peripherals on VCC
Irec	Internal current consumption (from VCC) of the receive amplifier
IR	Receive amplifier input pin of the TEA1114A
Islpe	Part of the line current flowing through SLPE pin
Istart	Start current of the AGC function
Istop	Stop current of the AGC function
Isup	Supply current of the voltage regulator
Ith	Threshold current of the low voltage part
k	Scale factor of anti-sidetone network
Leq	Artificial inductor of the voltage stabilizer
MUTE/	MUTE/ input of the TEA1114A
OM5838	Demoboard of the TEA1114A
QR	Earpiece amplifier output pin of the TEA1114A
Ra	Resistor to adjust the sidetone bridge attenuation
Rast	Antisidetone resistor
REG	Filter capacitor of the equivalent inductor connection pin of the TEA1114A
Rexch	Bridge resistance of exchange
RFI	Radio Frequency Interference

**TEA1114A transmission circuit with dialler
interface and regulated strong supply****Application Note**

Rgarint	Internal resistance (134 k Ω) which sets the receive gain
Rgasint	Internal resistance (29.5 k Ω) which sets the microphone gain
Rp	Internal resistance between LN and REG
Rva	Voltage adjustment resistor
RX	Receive output pin
SLPE	Slope input pin of the TEA1114A
THD	Total Harmonic Distortion (%)
MIC+/MIC-	Microphone amplifier input pins of the TEA1114A
VCC	Positive supply of the TEA1114A
VDD	Regulated supply
VEE	Ground reference of the TEA1114A
VIn	DC voltage between LN and VEE
Vref	Stabilized reference voltage between LN and SLPE
Vslpe	DC voltage level between SLPE and VEE
Zir	Input impedance of the receive amplifier of the TEA1114A
Zbal	Anti-sidetone network balance impedance
α	Gain control factor of the AGC