



# PHILIPS

Philips Semiconductors

---

## Application Note

# ***Ultra Low Noise Amplifiers for 900 and 2000 MHz with High IP3***

by Korné Vennema  
Philips Semiconductors  
Slatersville, RI

December 1996  
#KV96-157

This application note describes four Low Noise Amplifier designs with the BFG410W and the BFG425W, two devices from Philips Semiconductors' fifth generation wideband technology. The amplifier designs include measurement results and pcb layouts. The following designs are included:


- a) 900 Mhz LNA with BFG410W
- b) 2 GHz LNA with BFG410W
- c) 900 Mhz LNA with BFG425W
- d) 2 Ghz LNA with BFG425W

## Introduction

Today's wireless applications require Low Noise Amplifiers with a high third order intercept point (IP3) and a low noise figure (NF) at the same time. This is particularly interesting for 1900 MHz CDMA receiver front ends. This report describes four ultra low noise amplifiers for 900 MHz and 1900 MHz wireless applications, using Philips Semiconductors' fifth generation wideband technology. Philips' fifth generation die technology uses a double polysilicon process with a buried layer which results in transition frequencies ( $f_T$ ) higher than 20 GHz, gains in excess of 20 dB and Noise Figures as low as 1.2 dB. The amplifiers are designed for use at 2 Volt collector emitter voltage. A separate paragraph describes ways to improve IP3 in a LNA.


## The fifth generation

Philips' fifth generation double poly silicon wideband technology (see figure 1) uses a steep emitter doped profile resulting in transition frequencies over 20 GHz, and with poly base contacts a low base resistance is obtained. Via the buried layer, the collector contact is brought out at the top of the die.

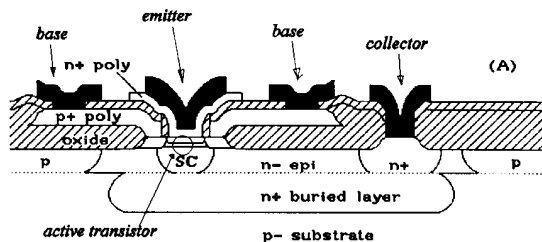

**Figure 1: Double polysilicon buried transistor**

The substrate is connected directly to the emitter package lead, resulting in improved thermal performance (see figure 2).

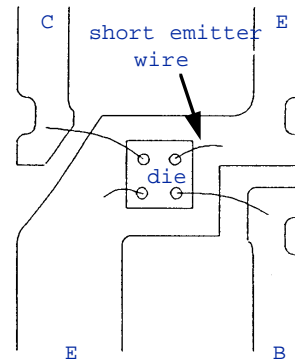

**Figure 2: Short emitter bonding wires reduce emitter inductance, which results in high gain. Heat flows through two emitter leads which lowers thermal resistance. Overall: Improved RF and thermal performance**


## The types of the fifth generation

The table below shows the three new types that use the fifth generation die technology.

| Type    | $I_E^{\wedge}$ (mA) | $f_T$ (GHz) | MSG (dB)        | NF (dB)         |
|---------|---------------------|-------------|-----------------|-----------------|
|         |                     |             | $f=2\text{GHz}$ | $f=2\text{GHz}$ |
| BFG403W | 3                   | 17          | 22              | 1.5             |
| BFG410W | 10                  | 22          | 23              | 1.3             |
| BFG425W | 25                  | 24          | 21              | 1.3             |


## IP3, using bypassing to improve it

Third order intercept point is usually determined by using a two tone test, i.e. two equal carriers with a small offset in frequency. Due to transistor non-linearities, these two carriers generate distortion products, both in-band and out of band (see figure 3). The product  $f_2-f_1$  is a low frequency product that is generated, which can modulate

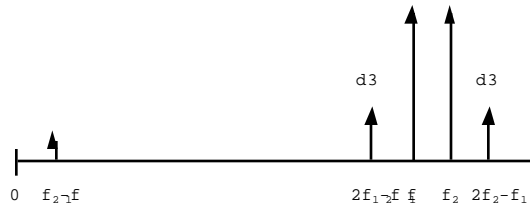

**Figure 3: Two tone test and generated intermodulation distortion products.  $f_2 - f_1$  is the low frequency product**


the base-emitter and collector-emitter voltages of a transistor used in an amplifier. This results in a fluctuating bias (base) voltage and supply (collector) voltage. For good linearity, a constant base and collector voltage are required. Lowering the collector voltage causes an amplifier to saturate earlier, thus decreasing linearity for a certain power level. The base voltage sets the quiescent current for the device, and thus the linearity (see also figure 4) . A fluctuating base voltage would change the linearity of the amplifier. Therefore it is important to apply proper bypassing at both collector and base.

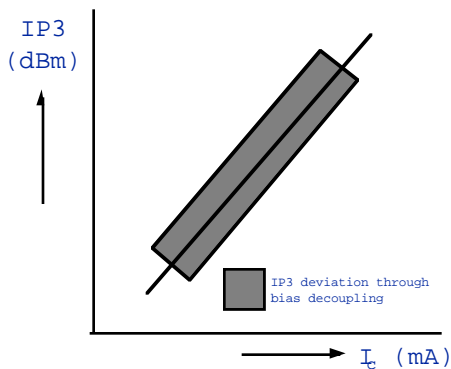

**Figure 4: IP3 in a Low Noise Amplifier is related to the collector current and also collector emitter voltage. As a rule of thumb for bipolar technology:  $IP_{3out} = 10 \log (V_{ce} * I_c * 5E3)$  in dBm**

Figure 5 shows the typical circuit diagram for a bipolar LNA. C is the bypassing capacitor for the working

frequency, i.e. either 900 or 1900 MHz. Adding additional bypassing by means

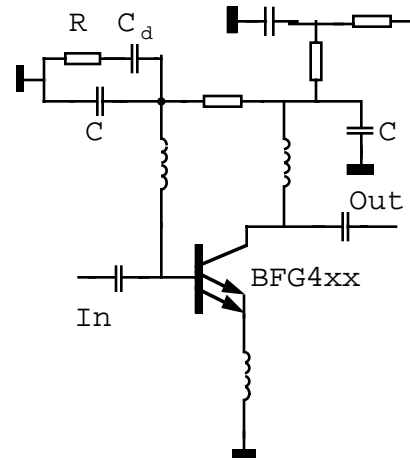

**Figure 5: Typical circuit diagram for a LNA.  $C_d$  is the additional bypassing for low frequencies. R is added to prevent low frequency instabilities. C is a short for the working frequency (27 pF at 900 MHz and 5.6 pF at 1900 MHz)**

of  $C_d$  improves the IP3 considerably. An improvement of 6 - 10 dB in IP3 can be expected. As a rule of thumb, the impedance of  $C_d$  should be smaller than 25 percent of the input impedance of the transistor at a particular carrier spacing. In case of a BFG520 (fourth generation wideband transistor) the following calculation is valid:

$$Z_{in} (25kHz) \approx h_{fe} / g_m = 120 / (40 * 0.0065) \approx 450 \Omega$$

$$C_d < 0.25 * 450 \approx 100 \Omega$$

At 25 kHz, the capacitor value equals:

$$C_d = 1 / (2 * \pi * f * 100) \approx 63 \text{ nF}$$


63 nF is the minimum recommended value. It is obvious that a higher capacitor value does a better job. Space constraints often don't allow the use of electrolytic (or even better tantalum) capacitors. In most cases, a 100 nF or 220 nF capacitor is sufficient. So far only base bypassing has been discussed. Similar effects can be

expected when collector bypassing is also applied; however, the effects are less dramatic.

**a) 900 MHz LNA with BFG410W**

This section describes a 900 MHz LNA with the BFG410W. The performance can be summarized as follows:

- $V_{ce}=2V, I_c=2mA, V_{SUP}\approx 3.3V$
- freq. = 900MHz
- $|S_{21}|^2 = 14 \text{ dB}$
- $|S_{12}|^2 = -26 \text{ dB}$
- NF = 1.4 dB
- $VSWR_i = 1 : 1.9$
- $VSWR_o = 1 : 2.3$
- $IP3_{in} = -9 \text{ dBm} (\Delta f=100 \text{ kHz})$

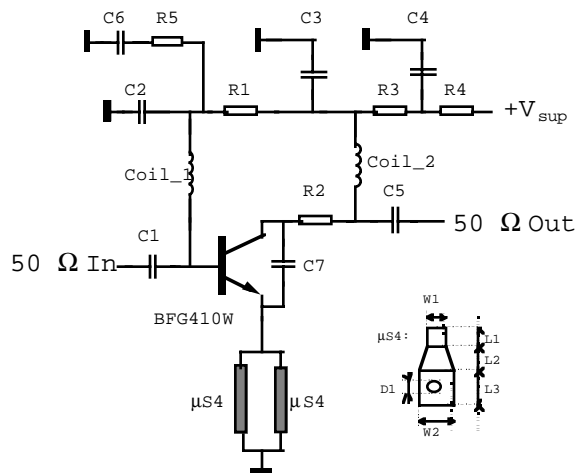

**Figure 6: Schematic diagram 900 MHz LNA with BFG410W.**

Input and output matching is realized with a LC combination. Additional emitter inductance on both emitter leads is used to improve the matching. All resistors and capacitors are 0603 or 0805 Philips SMD components. Coils are Coilcraft 0805. Board material is FR4.


| Comp.: | Value: | Comment: |
|--------|--------|----------|
| R1*    | 47 kΩ  | Bias.    |

|                                                   |            |                                     |
|---------------------------------------------------|------------|-------------------------------------|
| R2*                                               | 120 Ω      | Better RF-stability (K>1).          |
| R3*                                               | 22 Ω       | RF-block.                           |
| R4*                                               | 560 Ω      | Cancelling H <sub>FE</sub> -spread. |
| R5**                                              | 100 Ω      | To improve IP3-performance          |
| C1*                                               | 2.2 pF     | Input match.                        |
| C2*                                               | 27 pF      | 900MHz short.                       |
| C3*                                               | 27 pF      | 900MHz short.                       |
| C4*                                               | 1 nF       | RF-short                            |
| C5*                                               | 1.5 pF     | Output match.                       |
| C6**                                              | 100 nF     | To improve IP3-performance          |
| C7*                                               | 0.47 pF    | Better RF-stability (K>1).          |
| Coil_1                                            | 12 nH      | Input match.                        |
| Coil_2                                            | 15 nH      | Output match.                       |
| μS4                                               | next table | μ-stripline + via                   |
| Board FR4: ε <sub>r</sub> =4.6, h=0.5 mm, t=35 μm |            |                                     |
| * 0603 Philips                                    |            |                                     |
| ** 0805 Philips                                   |            |                                     |
| Coils: 0805CS Coilcraft                           |            |                                     |

**μS4 Emitter inductance (μ-stripline + via):**

|    |       |                                                                     |
|----|-------|---------------------------------------------------------------------|
| L1 | 2.0mm | μ-stripline Z <sub>0</sub> ~48Ω (PCB: ε <sub>r</sub> ~4.6, H=0.5mm) |
| L2 | 1.0mm |                                                                     |
| L3 | 1.0mm |                                                                     |
| W1 | 0.5mm | Emitter inductance: μ-stripline                                     |
| W2 | 1.0mm |                                                                     |
| D1 | 0.4mm | via-hde                                                             |

**Table 1: 900 MHz LNA with BFG410W, List of components.**

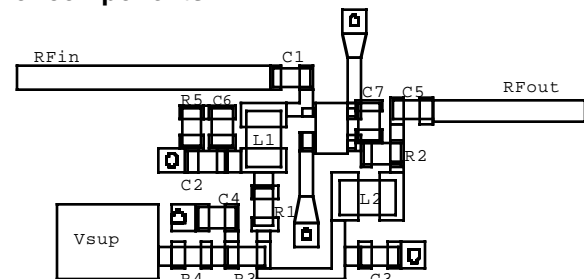

**Figure 7: PCB-layout 900 MHz LNA with BFG410W.**

### b) 2 GHz LNA with BFG410W

This paragraph describes a 2 GHz LNA with the BFG410W. The performance can be summarized as follows:

$$V_{ce}=2V, I_c=2mA, V_{SUP}\approx 3.3V$$

$$\text{freq.} = 2 \text{ GHz}$$

$$|S_{21}|^2 = 14.3 \text{ dB}$$

$$|S_{12}|^2 = -30 \text{ dB}$$

$$\text{NF} = 1.7 \text{ dB}$$

$$\text{VSWR}_i = 1 : 2.1$$

$$\text{VSWR}_o = 1 : 2.1$$

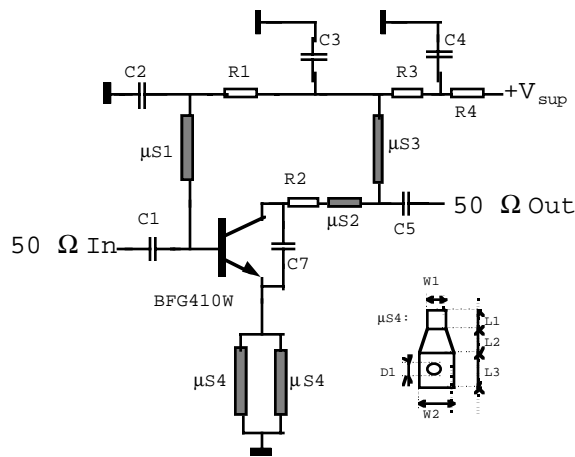


Figure 8: Schematic diagram 2 GHz LNA with BFG410W.

Input and output matching is realized with a microstrip-C combination. Additional emitter inductance on both emitter leads is used to improve the matching to 50 Ohm. All resistors and capacitors are 0603 Philips SMD components. Coils are Coilcraft 0805. Board material is FR4.

Please note that this amplifier is not optimized for noise and IP3 (extra bypassing is missing)

|                                                  |              |                                     |
|--------------------------------------------------|--------------|-------------------------------------|
| R1                                               | 47 KΩ        | Bias.                               |
| R2                                               | 10 Ω         | Better RF-stability (K>1).          |
| R3                                               | 22 Ω         | RF-block.                           |
| R4                                               | 560 Ω        | Cancelling H <sub>FE</sub> -spread. |
| C1                                               | 1 pF         | Input match.                        |
| C2                                               | 5.6 pF       | 2GHz short.                         |
| C3                                               | 5.6 pF       | 2GHz short.                         |
| C4                                               | 1 nF         | RF-short                            |
| C5                                               | 3.3 pF       | Output match.                       |
| C7                                               | 0.47 pF      | Better RF-stability (K>1).          |
| μs1                                              | W=0.25mm     | μ-stripline Z <sub>0</sub> ~95Ω     |
| μs2                                              | W=0.25mm     | μ-stripline Z <sub>0</sub> ~95Ω     |
| μs3                                              | W=0.25mm     | μ-stripline Z <sub>0</sub> ~95Ω     |
| μs4                                              | (next table) | μ-stripline + via                   |
| BoardFR4: ε <sub>r</sub> =4.6, h=0.5 mm, t=35 μm |              |                                     |
| All resistors and capacitors 0603 Philips        |              |                                     |

#### μS4 Emitter inductance (μ-stripline + via):

|    |       |                                 |
|----|-------|---------------------------------|
| L1 | 2.0mm | μ-stripline Z <sub>0</sub> ~48Ω |
| L2 | 1.0mm |                                 |
| L3 | 1.0mm |                                 |
| W1 | 0.5mm | Emitter inductance: μ-stripline |
| W2 | 1.0mm |                                 |
| D1 | 0.4mm | via-hde                         |

Table 2: 2 GHz LNA with BFG410W, List of components.

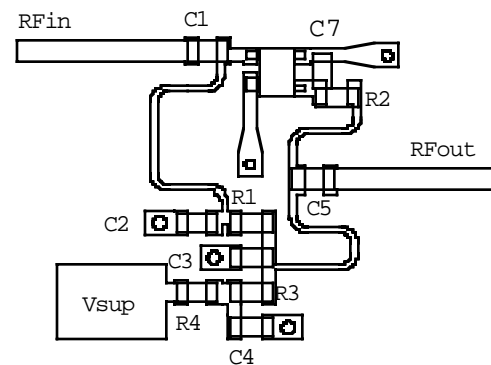


Figure 9: PCB-layout 2 GHz LNA with BFG410W.

### c) 900 MHz LNA with BFG425W

|      |        |          |
|------|--------|----------|
| Comp | Value: | Comment: |
|------|--------|----------|

This section describes a 900 MHz LNA with the BFG425W. The performance can be summarized as follows:

$V_{ce}=2V, I_c=10mA, V_{SUP}\approx 3.7V$   
 freq. = 900MHz  
 $|S_{21}|^2 = 17.3 \text{ dB}$   
 NF = 1.7 dB  
 $VSWR_i = 1 : 2.5$   
 $VSWR_o = 1 : 1.8$   
 $IP3_{in} = +3 \text{ dBm} (\Delta f=200 \text{ kHz})$

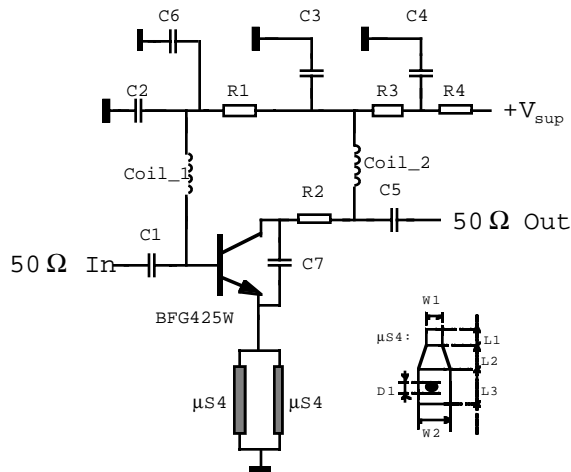


Figure 10: Schematic diagram 900 MHz LNA with BFG425W.

| Comp   | Value      | Purpose, comment               |
|--------|------------|--------------------------------|
| R1*    | 8.2 kΩ     | Bias (coll.-base)              |
| R2*    | 10 Ω       | better S22 and stability       |
| R3*    | 22 Ω       | RF blocking                    |
| R4*    | 150 Ω      | cancelling hFE spread          |
| C1*    | 8.2 pF     | Input match (input to base)    |
| C2*    | 27 pF      | 900 MHz short (L1 to ground)   |
| C3*    | 27 pF      | 900 MHz short (L2 to ground)   |
| C4**   | 100 nF     | RF decoupling collector bias   |
| C5*    | 22 pF      | Output match                   |
| C6**   | 100 nF     | To improve IP3                 |
| C7*    | 3.3 pF     | Output match, stability        |
| Coil_1 | 22 nH      | Input match (base-bias)        |
| Coil_2 | 12 nH      | Output match (collector-bias)  |
| μS4    | next table | μ-stripline Emitter-inductance |

Board FR4:  $\epsilon_r=4.6, h=0.5 \text{ mm}, t=35\mu\text{m}$   
 \* = 0603 Philips  
 \*\* = 0805 Philips  
 Coils: 0805CS Coilcraft

μS4 Emitter inductance of μ-stripline and via-hole

| Name | Dimension | Description                                     |
|------|-----------|-------------------------------------------------|
| L1   | 2.5mm     | length μ-stripline; $Z_0 \sim 48\Omega$         |
| L2   | 1.0mm     | length interconnect stripline and via-hole area |
| L3   | 1.0mm     | length via-hole area                            |

|    |       |                      |
|----|-------|----------------------|
| W1 | 0.5mm | width μ-stripline    |
| W2 | 1.0mm | width via-hole area  |
| D1 | 0.4mm | diameter of via-hole |

Table 3: 900 MHz LNA with BFG425W, List of components.

Input and output matching is realized with a microstrip-C combination. Additional emitter inductance on both emitter leads is used to improve the matching to 50 Ω. All resistors and capacitors are 0603 or 0805 Philips SMD components. Coils are Coilcraft 0805. Board material is FR4.

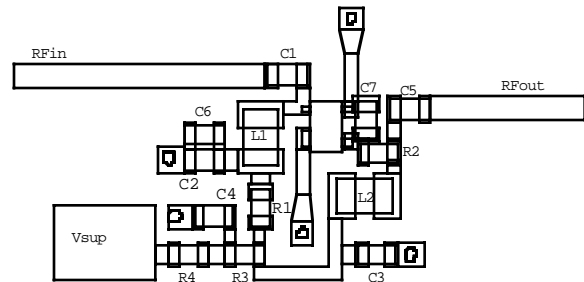


Figure 11: PCB-layout 900 MHz LNA with BFG425W.

### d) 2 GHz LNA with BFG425W

This section describes a 2 GHz LNA with the BFG425W. The performance, for different collector currents can be summarized as follows:

| $I_C$ [mA]         | $ S_{21} ^2$ [dB] | IP3_A [dBm] | IP3_B [dBm] | NF [dB] |
|--------------------|-------------------|-------------|-------------|---------|
| $V_{CE} \sim 2.5V$ | 2GHz              | input       | input       | 2 GHz   |
| 2                  | 14.4              | -10.9       | -2.3        | 1.5     |
| 3                  | 15.9              | -3.4        | -0.4        | 1.7     |
| 5                  | 16.3              | -0.9        | 1.8         | 1.8     |
| 6                  | 16.6              | 1.0         | 2.6         | 1.9     |
| 8                  | 16.9              | 3.9         | 5.6         | 2.1     |
| 10                 | 17.1              | 6.5         | 6.7         | 2.3     |

Table 4: Performance summary 2 GHz LNA with BFG425W

Input and Output VSWR is in all cases better than 1 : 2. IP3\_A is the third order intercept *without* R5 and C6. IP3\_B is the third order intercept *with* R5 and C6. It can be noticed that the IP3 improvement becomes less effective when the collector current increases.

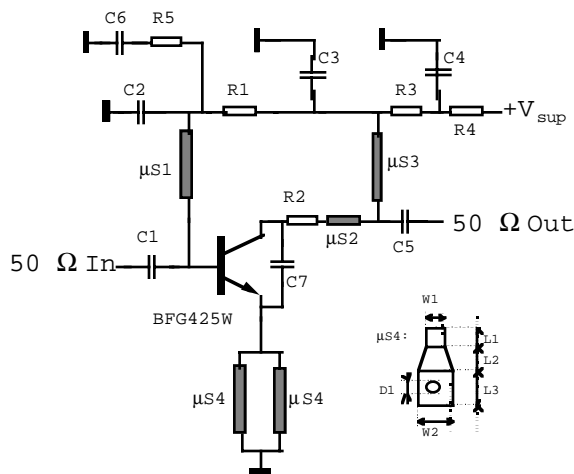


Figure 12: Schematic diagram 2 GHz LNA with BFG425W.

| Comp                                                  | Value:        | Comment:                             |
|-------------------------------------------------------|---------------|--------------------------------------|
| R1*                                                   | 15 K $\Omega$ | Bias.                                |
| R2*                                                   | 0 $\Omega$    | Omitted.                             |
| R3*                                                   | 22 $\Omega$   | RF-block.                            |
| R4*                                                   | 82 $\Omega$   | Cancelling H <sub>FE</sub> -spread.  |
| R5**                                                  | 100 $\Omega$  | To improve IP3-performance           |
| C1*                                                   | 4.7 pF        | Input match.                         |
| C2*                                                   | 5.6 pF        | 2GHz short.                          |
| C3*                                                   | 5.6 pF        | 2GHz short.                          |
| C4*                                                   | 1 nF          | RF-short                             |
| C5*                                                   | 2.7 pF        | Output match.                        |
| C6**                                                  | 100 nH        | To improve IP3-performance           |
| $\mu$ s1                                              | 8.9 x 0.25mm  | $\mu$ -stripline $Z_0 \sim 95\Omega$ |
| $\mu$ s2                                              | 3.9 x 0.25mm  | $\mu$ -stripline $Z_0 \sim 95\Omega$ |
| $\mu$ s3                                              | 6.6 x 0.25mm  | $\mu$ -stripline $Z_0 \sim 95\Omega$ |
| $\mu$ s4                                              | (next table)  | $\mu$ -stripline + via               |
| Board FR4: $\epsilon_r=4.6, h=0.5$ mm, $t=35$ $\mu$ m |               |                                      |
| * 0603 Philips                                        |               |                                      |
| ** 0805 Philips                                       |               |                                      |

$\mu$ S4 Emitter induction ( $\mu$ -stripline + via):

|    |       |                                      |
|----|-------|--------------------------------------|
| L1 | 1.0mm | $\mu$ -stripline $Z_0 \sim 48\Omega$ |
| L2 | 1.0mm |                                      |
| L3 | 1.0mm |                                      |
| W1 | 0.5mm | Emitter inductance $\mu$ -stripline  |
| W2 | 1.0mm |                                      |
| D1 | 0.4mm | via-hde                              |

Table 5: 2 GHz LNA with BFG425W, List of components.

Input and output matching is realized with a microstrip-C combination. Additional emitter inductance on both emitter leads is used to improve the matching to 50  $\Omega$ . All resistors and capacitors are 0603 or 0805 Philips SMD components. Coils are Coilcraft 0805. Board material is FR4.

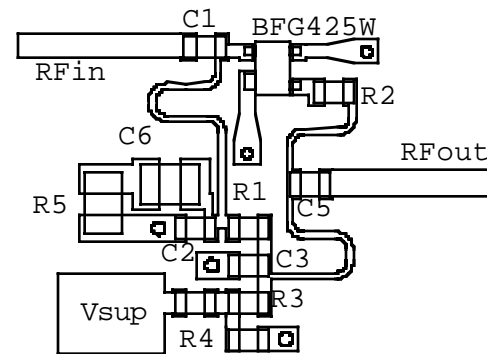


Figure 13: PCB-layout 2 GHz LNA with BFG425W.

### CONCLUSION

High performance small size LNAs, with a low supply voltage and current can be made with the new Philips BFG400W series double polysilicon transistors. IP3 can be optimized with extra components, and/or by increasing  $I_C$ . Increasing voltage also improves the IP3 point.

The LNAs presented in this brief application note are not the most optimized designs, nor are shown all possible circuit configurations by any means . They only show some possible LNA-designs with the BFG400W series double polysilicon transistors.