

Expanding A/D Resolution at the ST6 A/D Converter

P. MALUSARDI

INTRODUCTION

Occasionally the analog signal provided by external sensors require an Analog to Digital conversion with a resolution of greater than 8 bits. In order to extract the full information for subsequent data processing within the microcontroller a higher resolution Analog to Digital is thus required.


The solution described in this note enables this higher resolution with the on-chip 8-bit A/D converter of the ST62, using only an additional Operational Amplifier (OpAmp) and a few resistors.

1 OVERVIEW

The technique implemented is that of the Algebraic Adder, a full discussion of the principle of operation is included in this note.

A practical example of the external components used is shown in the following figure:

Figure 1. Example circuit

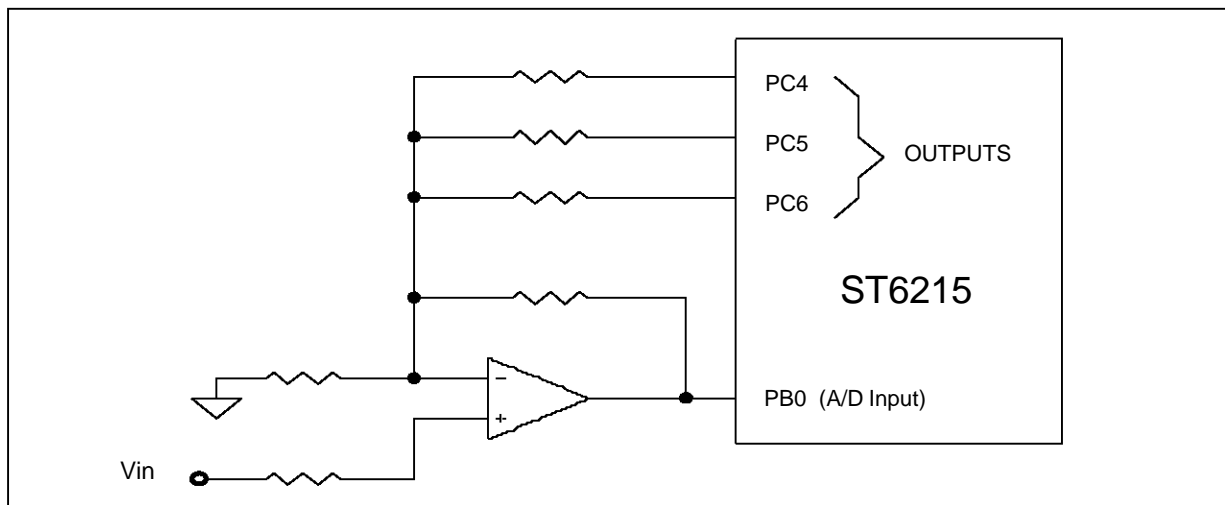


The resistances are selected by the ST62 I/O pins depending on the analog input voltage. The selection programmed modifies the output voltage of the OpAmp in such a way that the following A/D conversion is always made with the maximum input range of the converter.

This selection is made by software, therefore the total conversion time is increased versus a normal 8-Bit conversion, however the precision is increased and the input voltage range can be enlarged.

2 PRINCIPLE OF OPERATION OF AN ALGEBRAIC ADDER

Figure 2 represents the generic algebraic adder.

Figure 2. Generic algebraic adder

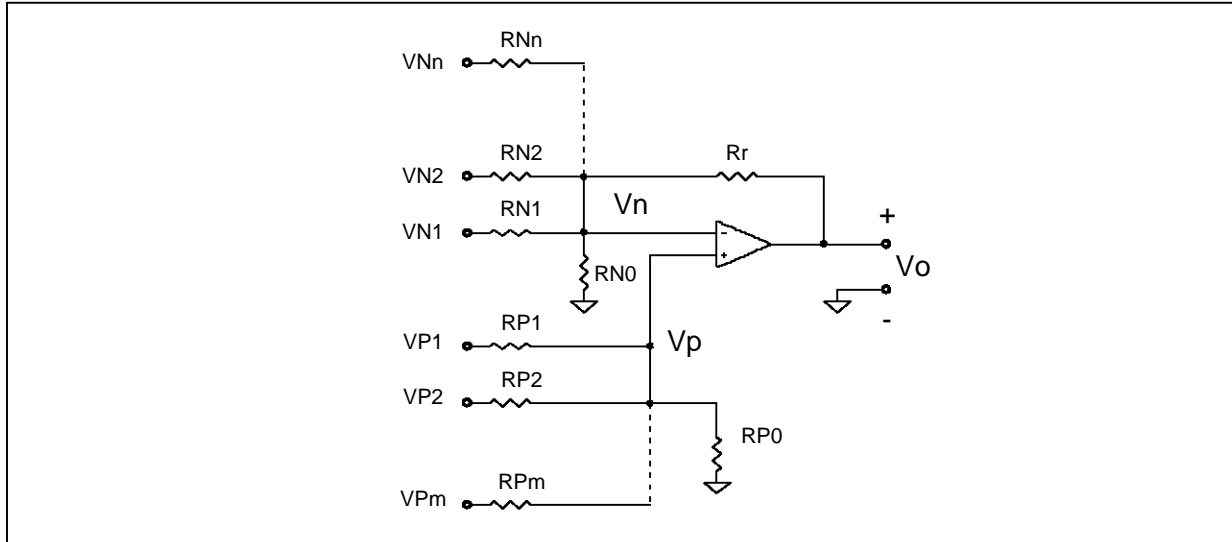

The circuit generates an output voltage equal to:

$$V_0 = \sum_{i=1}^m K_i \times V_{P_i} - \sum_{j=1}^n K_j \times V_{N_j} \tag{1}$$

To minimize the effects of the input polarizing currents, the total resistances seen from the two inputs of the OpAmp should be the same. Therefore:

$$\frac{1}{R_r} + \frac{1}{R_{N_0}} + \sum_{j=1}^n \frac{1}{R_{N_j}} = \frac{1}{R_{P_0}} + \sum_{i=1}^m \frac{1}{R_{P_i}} = \frac{1}{R_T} \tag{2}$$

The two resistances RP0 and RN0 are needed to satisfy the above relation. In general, only one of them will be needed.

To analyze the circuit, let us calculate the input voltages:

$$V_p = \frac{\sum_{i=1}^m G_{P_i} \times V_{P_i}}{G_{P_0} + \sum_{i=1}^m G_{P_i}} \text{ where } G_x = \frac{1}{R_x} \tag{3}$$

$$V_n = \frac{V_0 \times G_R + \sum_{j=1}^n G_{N_j}}{G_{N_0}} \tag{4}$$

Relation (2) becomes:

$$G_{N_0} + G_R + \sum_{j=1}^n G_{N_j} = G_{P_0} + \sum_{i=1}^m G_{P_i} = G_T$$

(5)

From 3, 4 and 5 we get:

$$V_0 = -\sum_{j=1}^n V_{N_j} \times \frac{R_r}{R_{N_j}} + \sum_{i=1}^m V_{P_i} \times \frac{R_r}{R_{P_i}}$$

(6)

Relation (6) is the relevant formula to be used. It also explains the name given to this circuit, since the output voltage is the 'algebraic sum' of the input voltages. To design the actual circuit, you chose one value of R_r (arbitrarily). The other resistances are then determined by the desired coefficients:

$$K_i = \frac{R_r}{R_{P_i}} \quad K_j = \frac{R_r}{R_{N_j}} \quad (7)$$

Finally, the values for R_{N_0} and R_{P_0} are chosen, based on (2).

3 EXAMPLE

Let us assume we have a voltage swing of 10 volts (0 to 10) that we want to convert with a 10-bit resolution. And let us assume we have a set of voltage sources V_{Nj} that we can switch between 0 to 5 volts under software control, and each one independently from the other.

Let us also assume we can 'cut' the 10 volt swing in 4 'pieces' of 2.5 volts each, and that every 'piece' can be converted with 8-bit resolution. The overall resolution will therefore be:

$$2^8_{\text{(ST6 A/D resolution)}} * 2^2_{\text{(# of 'pieces')}} = 2^{10}$$

Let us call V_{in} the actual value of the source to be converted. For instance, if $V_{in} \in [10, 7,5]$ volts, we could supply the ST6 A/D with the voltage:

$$(V_{in}-7.5\text{volt})\times 2 \Rightarrow \epsilon[0,5]\text{volt}$$

or, for (10,7.5) volts:

$$(V_{in}-1.5\times V_{N1})\times 2 = 2\times V_{in}-3\times V_{N1}$$

where V_{N1} is one of the V_{Nj} sources, either 0 or 5 volts. In similar fashion, for the other intervals, we could obtain:

(7.5, 5) volts

$$(V_{in}-V_{N2})\times 2 = 2\times V_{in}-2\times V_{N2}$$

(5, 2.5) volts

$$(V_{in}-0.5\times V_{N3})\times 2 = 2\times V_{in}-V_{N3}$$

(2.5, 0) volts


$$(V_{in}-0\times V_{N4})\times 2 = 2\times V_{in}$$

So, relation (6) becomes:

$$V_0 = 2\times V_{in}-3\times V_{N1}-2\times V_{N2}-V_{N3} \quad \text{where } V_{in} = V_{P1}$$

The software driving the conversion will therefore verify if, given a certain status of the V_{Nj} voltages, the conversion is far from being saturated. If so, another try will be performed with a different status of the V_{Nj} voltages. Figure 3 gives the flow chart of such software.

Figure 3 Conversion routine

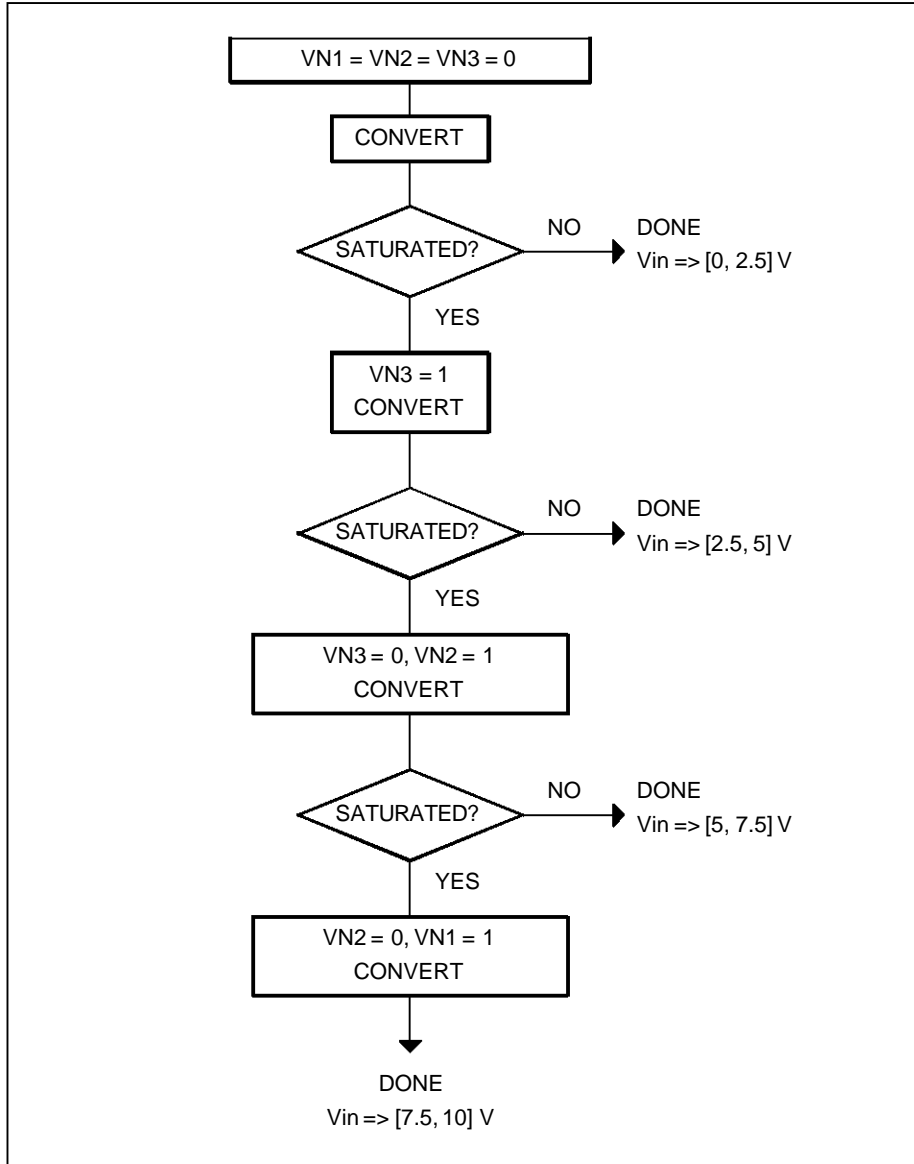

EXPANDING A/D RESOLUTION AT THE ST6 A/D CONVERTER

The actual circuit values are calculated as follows. With arbitrarily chosen R_r equal to 10 K Ω , the other resistor values are given by:

$$\frac{R_r}{R_{P1}} = 2 \Rightarrow R_{P1} = 5000\Omega$$

$$\frac{R_r}{R_{N1}} = 3 \Rightarrow R_{N1} = 3333\Omega$$

$$\frac{R_r}{R_{N2}} = 2 \Rightarrow R_{N2} = 5000\Omega$$

$$\frac{R_r}{R_{N3}} = 1 \Rightarrow R_{N3} = 10K\Omega$$

To satisfy relation (2), we obtain the following values, as indicated in Figure 4.

$$\frac{1}{R_r} + \frac{1}{R_{N0}} + \frac{1}{R_{N1}} + \frac{1}{R_{N2}} + \frac{1}{R_{N3}} + \frac{1}{R_{N0}} + 0.0007$$

$$\frac{1}{R_{P0}} + \frac{1}{R_{P1}} = \frac{1}{R_{P0}} + 0.0002$$


$$\frac{1}{R_{N0}} + 0.0007 = \frac{1}{R_{P0}} + 0.0002$$

Assuming $\frac{R}{R_{P0}} = \infty \Rightarrow R_{N0} = 2K\Omega$

4 APPLICATION EXAMPLE

An example ST62 software program follows on the next pages. It executes the program flow of Figure 3 in the application circuit of Figure 4.

Figure 4. Example circuit

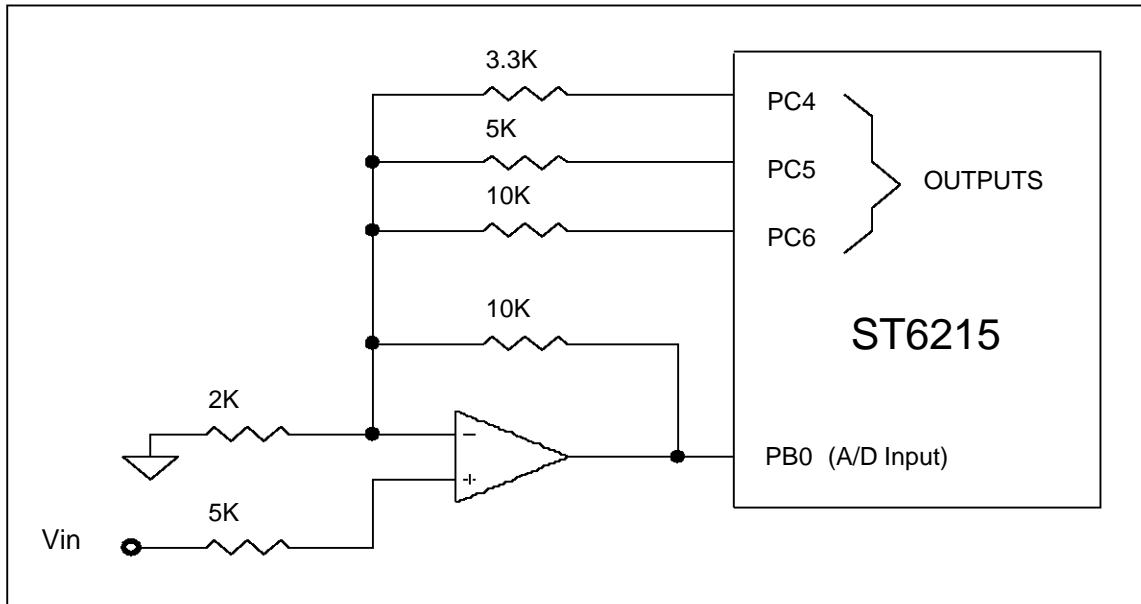

The ST6215 pin allocation is arbitrary. The three outputs can drive other identical circuits, when more the one 10-bit A/D channel is needed. Also, a different number of 'pieces' can be used to achieve a different resolution.

EXPANDING A/D RESOLUTION AT THE ST6 A/D CONVERTER

```
*****
;*      File name: HIRES_AD.ASM
;*
;*      ALGEBRAIC ADDER AND ST6 A/D CONVERTERS - Application note software
;*      This software is an example on how to increase the ST6 converter
;*      resolution. Please refer to the application note for further
;*      explanations.
;*
;*      Allocation of pins: PC4, PC5 and PC6 are, respectively, voltage sources
;*      VN1, VN2 and VN3. PB0 is an A/D input
;*
*****

        .input "6215_reg.asm"      ;ST6215 standard definitions file
VN1     .equ 4                      ;PC4 bit select
VN2     .equ 5                      ;PC5 bit select
VN3     .equ 6                      ;PC6 bit select
drchs   .def 0bfh,0ffh,0ffh        ;shadow register for Data Register C
Hres    .def 0bdh,0ffh,0ffh        ;MS 2 bits of conversion result, and ;conversion
flag
conv_f  .equ 7                      ;the MSB of Hres is the high resolution
                                ;end of conversion flag
c1      .equ 6                      ;conversion step flags
c2      .equ 5
c3      .equ 4
c4      .equ 3                      ;using Hres
Lres    .def 0beh,0ffh,0ffh        ;LSB of conversion result

*****                               N           O           T           E
*****
;register W is used to save the accumulator contents
;in standard interrupt routines
;*****
*

        .org 880h                  ;one module only. Do not use this
                                ;assembly directive if you organize
                                ;your software in linkable modules

init    ldi drb,1
        ldi orb,1                  ;PB0 is analog input
        ldi ddrc,070h              ;PC4..6 are open drain outputs
        ldi orc,070h              ;PC4..6 are push-pull outputs now
        ldi drchs,0               ;assume PC7 is input with pull-up,
                                ;no interrupt
        ldi ior,10h               ;enable interrupts
        ldi Hres,0
        reti                       ;initialize interrupt machine

conv    ;this is an endless loop converting
        ;PB0 input with 10-bit resolution
        ;the first time here after reset,
        ;VN1=VN2=VN3=0

        set conv_f,Hres
        set c1,Hres
        set 5,adcr                  ;start high resolution conversion
        jrs conv_f,Hres,$
        nop                        ;here the high resolution result is
                                ;available in Hres-Lres

        jp conv

adcint  ld w,a                      ;save accumulator
        ld a,adr                   ;in accumulator conversion result
        jrs c1,Hres,c1conv
        jrs c2,Hres,c2conv
```


EXPANDING A/D RESOLUTION AT THE ST6 A/D CONVERTER

```
        jrs c3,Hres,c3conv

c4conv  ldi Hres,3
        ld Lres,a
        ld a,drcs
        res VN1,a
        ld drcs,a
        ld drc,a           ;VN1=VN2=VN3=0
        jp convout

c1conv  pi a,0ffh
        jrnz c1c1
        lr Hres
        ld Lres,a
convout d a,w
        reti
c1c1    ld a,drcs
        set VN3,a
        ld drcs,a
        ld drc,a           ;VN1=VN2=0, VN3=1
        set 5,adcr         ;start conversion
        res c1,Hres
        set c2,Hres
        jp convout        ;exit interrupt

c2conv  cpi a,0ffh
        jrnz c2c1
        ldi Hres,1
        ld Lres,a
        jp convout
c2c1    ld a,drcs
        res VN3,a
        set VN2,a
        ld drcs,a
        ld drc,a           ;VN1=VN3=0, VN2=1
        set 5,adcr         ;start conversion
        res c2,Hres
        set c3,Hres
        jp convout        ;exit interrupt

c3conv  cpi a,0ffh
        jrnz c3c1
        ldi Hres,2
        ld Lres,a
        jp convout
c3c1    ld a,drcs
        res VN2,a
        set VN1,a
        ld drcs,a
        ld drc,a           ;VN2=VN3=0, VN1=1
        set 5,adcr         ;start conversion
        res c3,Hres
        set c4,Hres
        jp convout        ;exit interrupt

        .org 0ff0h
        jp adcint          ;A/D interrupt vector
        .org 0ffeh
        jp init           ;reset vector

        .end
```

EXPANDING A/D RESOLUTION AT THE ST6 A/D CONVERTER

THE SOFTWARE INCLUDED IN THIS NOTE IS FOR GUIDANCE ONLY. SGS-THOMSON SHALL NOT BE HELD LIABLE FOR ANY DIRECT, INDIRECT OR CONSEQUENTIAL DAMAGES WITH RESPECT TO ANY CLAIMS ARISING FROM USE OF THE SOFTWARE.

Information furnished is believed to be accurate and reliable. However, SGS-THOMSON Microelectronics assumes no responsibility for the consequences of use of such information nor for any infringement of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of SGS-THOMSON Microelectronics. Specifications mentioned in this publication are subject to change without notice. This publication supersedes and replaces all information previously supplied. SGS-THOMSON Microelectronics products are not authorized for use as critical components in life support devices or systems without the express written approval of SGS-THOMSON Microelectronics.

© 1994 SGS-THOMSON Microelectronics - All Rights Reserved

Purchase of I²C Components by SGS-THOMSON Microelectronics, conveys a license under the Philips I²C Patent. Rights to use these components in an I²C system, is granted provided that the system conforms to the I²C Standard Specifications as defined by Philips.

SGS-THOMSON Microelectronics GROUP OF COMPANIES

Australia - Brazil - France - Germany - Hong Kong - Italy - Japan - Korea - Malaysia - Malta - Morocco
The Netherlands - Singapore - Spain - Sweden - Switzerland - Taiwan - Thailand - United Kingdom - U.S.A.