

VOLTAGE TO CURRENT WAVEFORM CONVERSION
(Example Of The 10/700 μ s Surge)

A. Bremond

INTRODUCTION

CCITT members have generated a great deal of recommendations which have permitted national

administrations to publish local standards. In particular they have defined a 10/700 μ s surge waveform and its associated generator diagram (see fig.1).


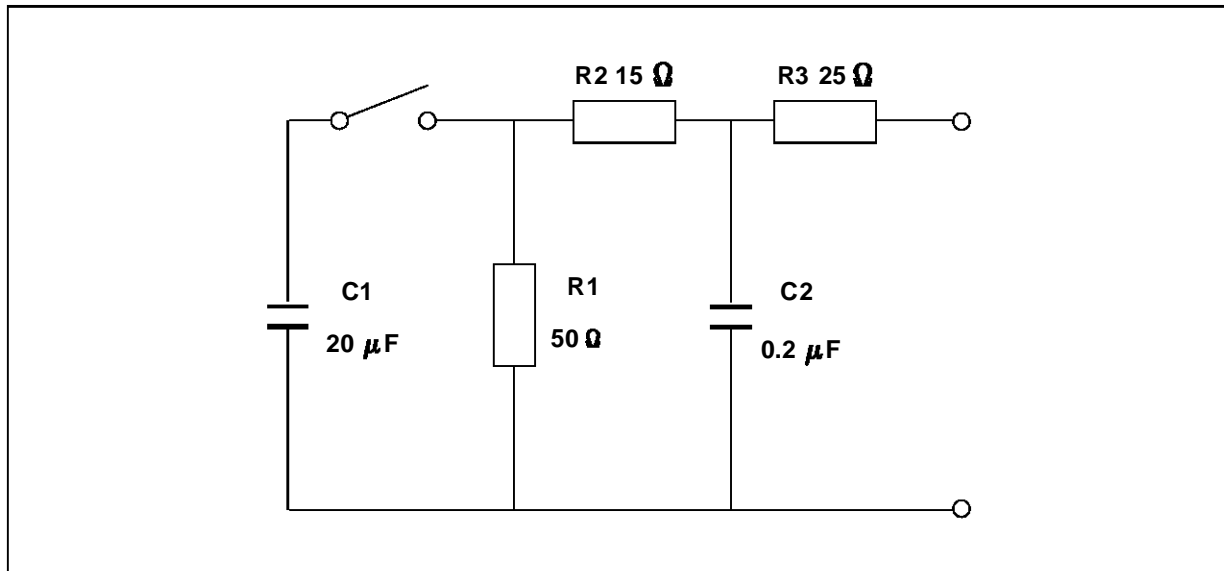


Figure 1 : CCITT 10/700 μ s Surge Definition

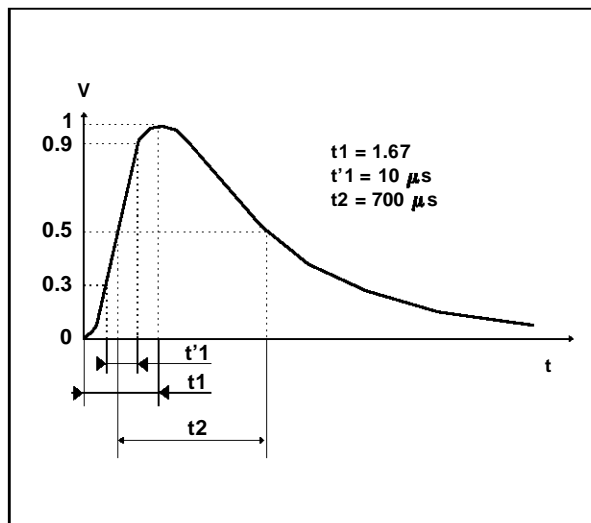


**GENERATOR DIAGRAM
OPEN OUTPUT SURGE WAVEFORM**

It is important to note that the given waveform is the generator output voltage without load. For a protection component user the most important parameter to take into account is the current waveform flowing through the surge suppressor. The goal of this paper is to give the current waveform parameters.

2 - WAVEFORM CALCULATION

2.1 : Generator output voltage without load.

Figure 2 : Voltage Rise time

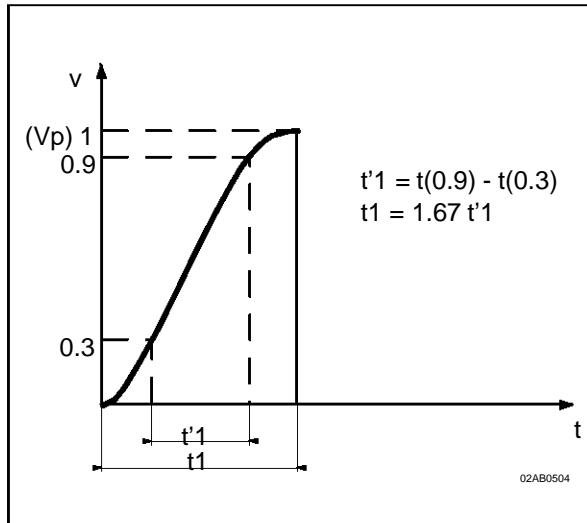

2.1.1 : Rise time

The equation of this curve is :

$$v(t) = V_p (1 - \exp(-t/T))$$

$$\Rightarrow t = -T \log_n (1 - (v(t)/V_p)) \quad (1)$$

In this case the time constant may be estimated as :

$$T = R_2 C_2$$

So \$t(0.3)\$ and \$t(0.9)\$ will be calculated respectively with \$v(t)/V_p = 0.3\$ and \$0.9\$


$$t(0.3) = 1 \mu s$$

$$t(0.9) = 6.9 \mu s$$

and then

$$t_1 = 1.67 (t(0.9) - t(0.1)) = 9.8 \mu s \approx \underline{\underline{10 \mu s}}$$

Figure 3 : Voltage duration

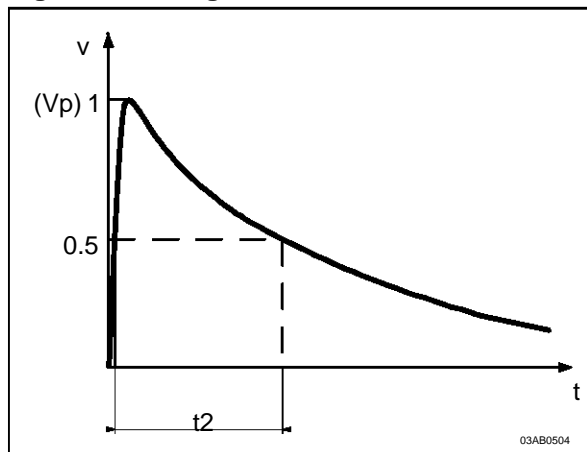

2.1.2 : Voltage surge duration

The equation of this curve is:

$$v(t) = V_p \exp(-t/T)$$

$$\Rightarrow t = - \log_n (v(t)/V_p) \quad (2)$$

with a time constant due essentially to \$R_1\$ and \$C_1\$

$$T = R_1 C_1$$


So \$t_2\$ may be calculated with \$v(t)/V_p = 0.5\$

$$\Rightarrow t_2 = 693 \mu s \approx \underline{\underline{700 \mu s}}$$

2.2 Generator short circuited output current.

In this chapter we will do the calculations with the generator output in short circuit (see fig.4), this is generally the case during the surge suppressor action (for example the Trisil technology devices from SGS THOMSON).

Figure 4 : CCITT 10/700 ms generator with output in short circuit

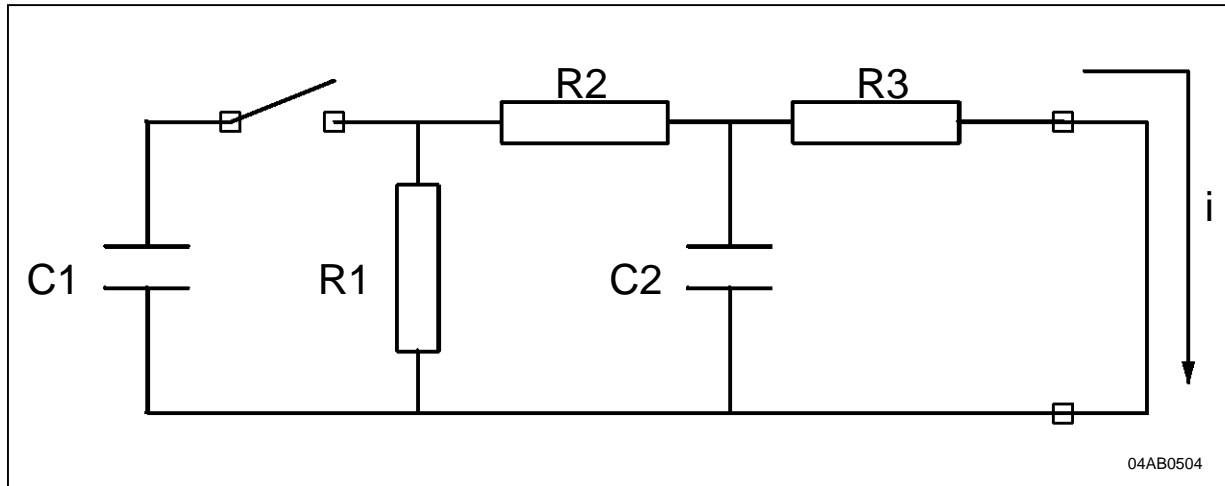

2.2.1 : Rise time

2.1.2 : Current surge duration.

Figure 5 : Current rise time


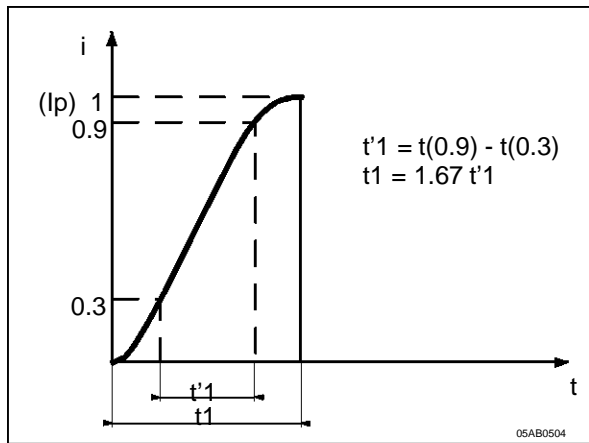


Figure 6 : Current duration

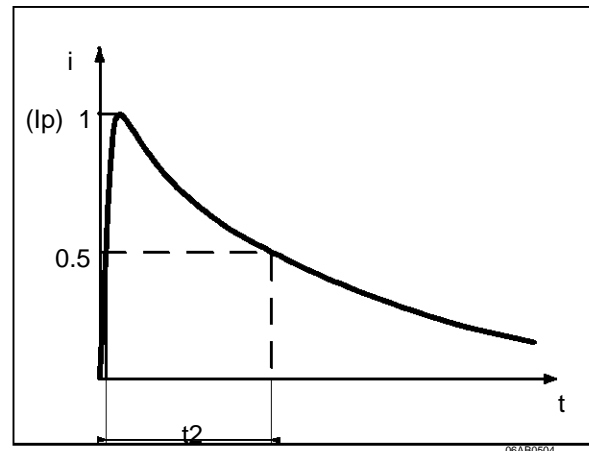

The formula (1) given in the chapter 2.1.1. remains true, but the time constant must take into account R_3 and may be estimated as :

$$T = (R_2 R_3 / (R_2 + R_3)) C_2$$

So $t_{(0.3)} = 0.67 \mu s$
 $t_{(0.9)} = 4.3 \mu s$

$$\Rightarrow t_1 = 1.67 (t_{(0.9)} - t_{(0.1)})$$

$$= 6 \mu s \approx \underline{\underline{5 \mu s}}$$

The formula (2) given in the chapter 2.1.2. remains true but the time constant is now due to the capacitor C_1 with the resistor R_1 in parallel with $R_2 + R_3$

$$T = (R_1 (R_2 + R_3) / (R_1 + R_2 + R_3)) C_1$$

$$\Rightarrow t_2 = 308 \mu s \approx \underline{\underline{310 \mu s}}$$

APPLICATION NOTE

3 - SUMMARY

The 10/700 μs surge waveform given by the CCITT recommendation is a voltage wave produced by the generator in open circuit. This curve is very important as a test reference for telecommunication equipment.

The protection function designers or users have to know the actual current waveform flowing through the protector in order to optimize it.

The 10/700 μs CCITT generator gives a 5/310 μs current wave when its outputs are in short circuit. (In the case of a crowbar device, for example Trisil).

For certain cases the resistor R3 is equal to zero and then the duration time becomes 160 μs .

Please note that in certain documents we find a 8/320 μs current wave which represents the same surge test.

Information furnished is believed to be accurate and reliable. However, SGS-THOMSON Microelectronics assumes no responsibility for the consequences of use of such information nor for any infringement of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of SGS-THOMSON Microelectronics. Specifications mentioned in this publication are subject to change without notice. This publication supersedes and replaces all information previously supplied.

SGS-THOMSON Microelectronics products are not authorized for use as critical components in life support devices or systems without express written approval of SGS-THOMSON Microelectronics.

© 1995 SGS-THOMSON Microelectronics - Printed in Italy - All rights reserved.

SGS-THOMSON Microelectronics GROUP OF COMPANIES

Australia - Brazil - France - Germany - Hong Kong - Italy - Japan - Korea - Malaysia - Malta - Morocco -
The Netherlands - Singapore - Spain - Sweden - Switzerland - Taiwan - Thailand - United Kingdom - U.S.A.