

## **APPLICATION NOTE**

## MAGNETIC SNUBBER FOR 200W PFC WITH UNIVERSAL MAINS

In high voltage continuous mode boost converters, a significant part of the power mosfet switching losses is related to the turn-on edge.

In fact, at turn on, the power mosfet has to sustain both the boost diode reverse recovery and the stray capacitances associated energies.

Moreover, the additional peak current due to the recovery of the diode can be significantly high, in particular at high temperature, thus increasing the high frequency noise, the E.M.I. filter requirements and reducing efficiency.

The turn on peak current, generating all the above mentioned problems, has been dramatically reduced by using the magnetic snubber we propose at Fig. 1b.

The concept of this snubber is to reduce (and control) the turn-on di/dt of the mosfet to the most convenient value, considering the voltages and switchingnfrequency applied to the system.

The values mentioned in the test circuit (Fig. 1b) are related to the application 200W/100kHz UNI-VERSAL MAIN "EVÁL4981A".



Figure 1a: Voltage Snubber.

Figure 1a shows the voltage snubber circuit used in the same evaluation board (EVALL4981A). The benefits of this magnetic snubber are re-

ported in the following table:

Vin	with voltage snubber		with current snubber		Pout
	Pin	η	Pin	η	
85	232	88.4	222	92.3	205
220	220	93.2	216	94.8	205
270	217	94.4	213	96.2	205

Analysing the table of results, it is possible to appreciate the much lower power dissipation. This additional benefit, at 85Vac input mains, corresponds to about 10W, where the most of this reduced power dissipation is located in the power mos.

## Figure 1b: Magnetic Snubber.



AN831/0795

Information furnished is believed to be accurate and reliable. However, SGS-THOMSON Microelectronics assumes no responsibility for the consequences of use of such information nor for any infringement of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of SGS-THOMSON Microelectronics. Specifications mentioned in this publication are subject to change without notice. This publication supersedes and replaces all information previously supplied. SGS-THOMSON Microelectronics products are not authorized for use as critical components in life support devices or systems without express written approval of SGS-THOMSON Microelectronics.

 $@ \$  1995 SGS-THOMSON Microelectronics - All Rights Reserved

SGS-THOMSON Microelectronics GROUP OF COMPANIES Australia - Brazil - France - Germany - Hong Kong - Italy - Japan - Korea - Malaysia - Malta - Morocco - The Netherlands - Singapore -Spain - Sweden - Switzerland - Taiwan - Thaliand - United Kingdom - U.S.A.

