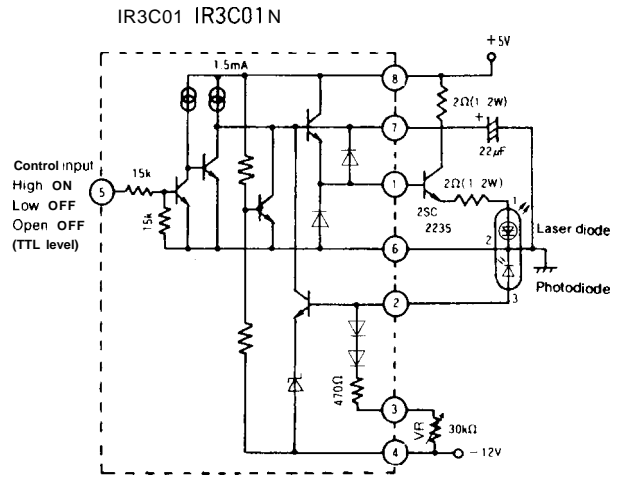


● **Typical Drive Circuits for LT090MD/MF (Using Driver IC)**

The operating current of LT090MD/MF is large, so when driving it with driver IC IR3C01 or IR3C01N, a transistor should be inserted between the output terminal of the IC and the laser diode as shown in Fig.31-1

Note See page 31 for power adjustment Instructions Because of the high optical power output of LT090M0/MF, extreme care must be taken to prevent the direct viewing of the beam by human eyes


Fig31-1 Typical Drive Circuit for LT090 Series



Typical Drive Circuits for P-type Laser Diodes

In the P-type laser diodes, the built-in PIN photodiode is reversed relative to Sharp's other models The same positive power voltage power supply that is used to drive the laser diode can be used to apply a reverse bias to the photodiode, as shown in Fig 31-2


Fig. 31 -2 Typical Drive Circuit for LT022PD Series

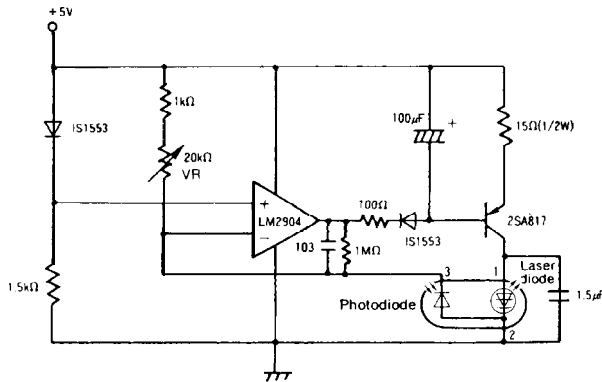

- Note 1) See page 30 for power adjustment instructions and precautions.
 2) If a thermal shut-off function is not required, remove R₁ and R₂, and use a TTL level input at Pin 5 to control the laser diode (high on, low off)

● **Circuits Using a Driver IC**

Fig. 31-3

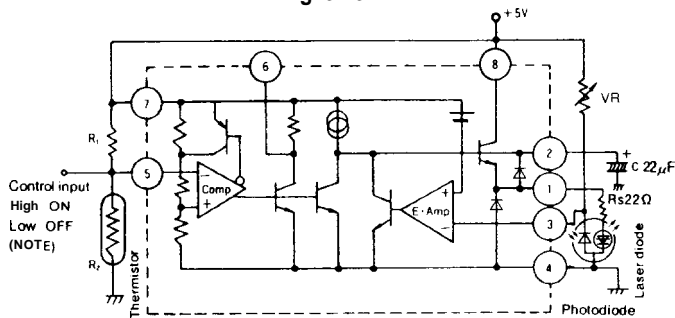

IR3C07/IR3C07N

The value of VR should be selected according to the following table

Model No.	VR Value
LT022PD, LT022WD	15kΩ
LT024ED, LT028GS	
LT022PS, LT022WS, LT023PS	35kΩ
LT023WS, LTO1 1 PS,	
LT028PS	
LT024PD, LT015PD, LT025PD	100kΩ

Pulse Drive Circuit

An important feature of laser diodes is their ability to respond to direct, high speed modulation.

In pulse drive operation, if the DC bias current, I_b , is less than the threshold current, I_{th} , a time delay will result between the drive current pulse and the optical power output pulse. Therefore, the DC bias current is normally set just above the threshold current to obtain quick response.

A typical drive circuit is shown in Fig. 32-2. The current flowing to the laser diode is used to obtain chopped pulse oscillation in a switching transistor. The transistor used must have good high speed response. The DC bias current is adjusted by R_b .

In this circuit, the APC function uses the average optical power output. Therefore, even if the frequency of the optical power output pulse is the same, a change in the duty ratio will cause the maximum optical power output to change. Care must be taken to avoid exceeding the absolute maximum rated output of the laser diode.

When the APC does not readily function because the duty ratio of the desired optical power output is small (less than 1/10) and the average output is low, use a circuit such as that shown in Fig. 32-3. This circuit holds the peak monitor current and feeds it back, so that the APC will function regardless of the duty ratio of the optical power output. The operational amplifier used in the peak hold circuit must have quick response and a large input impedance. Further, the time constant $t = RC$ of the peak hold circuit should be set sufficiently long in comparison with the drive pulse period f^{-1} .

The value of VR in the diagram should be selected according to the following table.

Model No.	VR Value
LT030 series, LT024 AD	15k Ω
LT022 series, LT023 series(9 ϕ)	
LT026 series, LT010 series	
LT022 series(5.6 ϕ), LT023 series(5.6 ϕ)	35k Ω
LT026 series(5.6 ϕ), LT011 series	
LT021 series, LT027 series	3k Ω
LT024 MD, LT015 series	100k Ω
LT017 series, LT025 MD	

In the case of pulse drive circuit shown in Fig 32-2, it is necessary to select the value of VR depending on the duty ratio.

Set the value of VR so that $VR \times$ duty ratio is equal to the value in the table. All Sharp laser diodes have a frequency response characteristic greater than 1 gigahertz and will more than meet the requirements of high speed optical communications (See Fig. 94-5)

Fig. 32-1 Principle of Direct Modulation



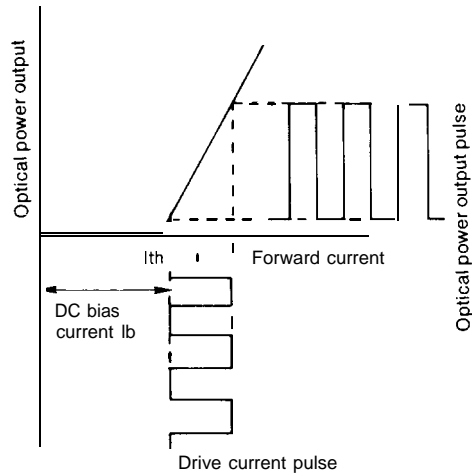


Fig. 32-2 Typical Pulse Drive Circuit I

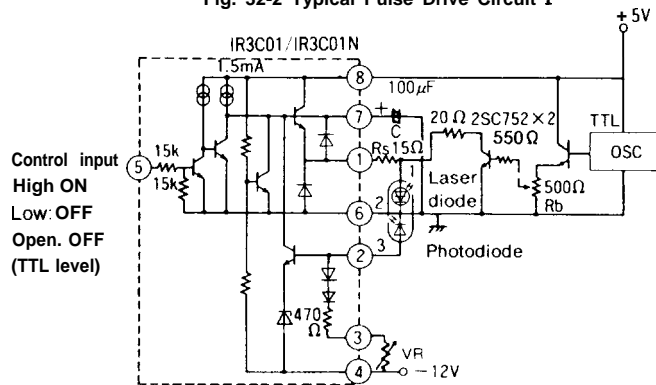

Note: See page 30 for power adjustment instructions.

Fig. 32-3 Typical Pulse Drive Circuit II

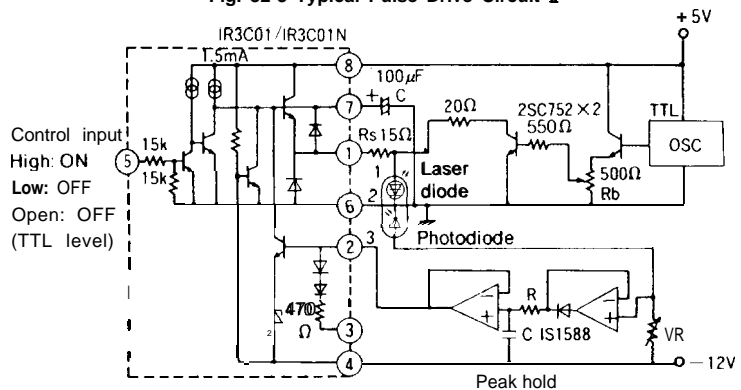

OP amplifier: CA3240 (1/2) X 2

Note See page 31 for power adjustment instructions

● **Pulse driver IC (IR3C08)**

An example of a pulse drive circuit is illustrated on the previous page, Sharp has developed the IR3C08 pulse driver IC for easy use in laser printers.


The IR3C08 controls the operating current level so that the optical power output of the laser diode will be constant. In addition, it is capable of switching the laser beam on and off at extremely high speeds. The IR3C08 consists of a control system 1 having the following functional blocks: Up/down counter 1, DA converter, and a control system 2 having the following functional blocks: Up/down counter 2, and DA counter 2. The operating current, I_O follows the following algebraic equation:

- $I_O = I_{F1} + I_{F2} + I_{OS}$
- I_{F1} - Set by control system 1
- I_{F2} - Set by control system 2
- I_{OS} - Constant offset current

I_{F1} and I_{F2} are set by an input signal. The method of setting the optical power output is as follows.


First, set one half of the desired optical power output P_o using I_{OS} and I_{F1} . Then, set optical power output with control system 2 by using I_{OS} , I_{F1} and I_{F2} . By using both control systems in this manner, the set quantizing error can be kept small.

Fig. 33-1 Timing Chart

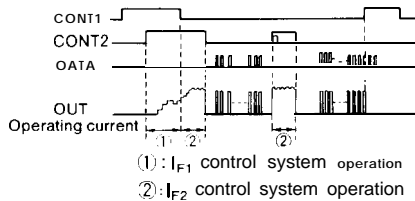

CONT 1	CONT 2	Up/down counter 1	Up/down counter 2	Operation
H	H	Count	Reset	I_{F1} current detection
H	L	Reset	Count	Reset (OUT = Low)
L	H	Hold	Count	I_{F2} current detection
L	L	Hold	Hold	Hold

Fig. 33-1 Block Diagram

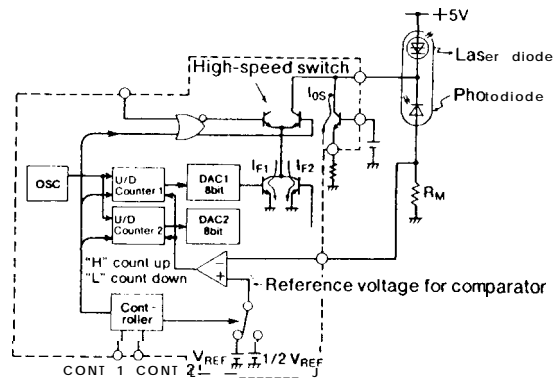

● **Optical Power Output Adjustment When Using Pulse Drive**

A pulse optical output of only a few microseconds cannot be measured directly using the SPD102 photodiode. The response of the SPD102 is too slow, and its output drops off as shown in Fig. 33-3b. The average optical power output can be measured by connecting a large capacity capacitor in parallel with the load resistance of the SPD102 and making the output direct current. This makes it possible to estimate the pulse optical power output from the average optical power output.

However, since fluctuations in the duty ratio and other factors will cause errors, it is recommended that a PIN photodiode be used to increase the accuracy of measurement of optical power output. Since the response of the PIN photodiode is extremely fast, the optical power output waveform can be measured directly as shown in Fig 33-3d. To accurately measure the absolute optical power output, a photodiode with a large photodetector surface should be used. The circuit used for measurement is illustrated in Fig 33-4. If the sensitivity of the photodiode is 0.5 mA/mW, and the lead used has a resistance of 50Ω then the value becomes 25mV/mW.

When measuring output power, bring the laser as close as possible to the Photodetector of the PIN photodiode. When measuring high power laser diodes such as the LT021/24/27/17/15 /90/ 91 series devices, place a neutral density (ND) filter in front of the detecting surface of the PIN photodiode to limit output

Fig. 33-3 Outputs of Photodiodes Receiving Pulse Optical Power Outputs


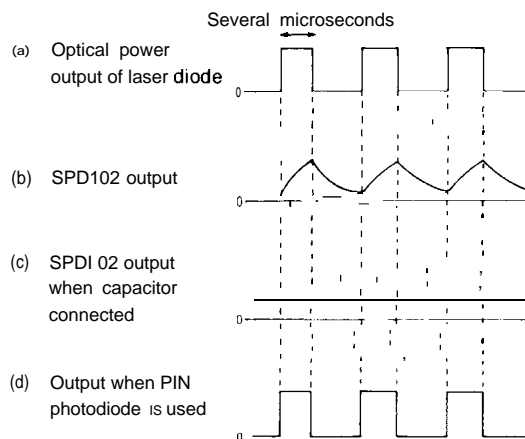


Fig. 33-4 Pulse Optical Power Output Measurement System

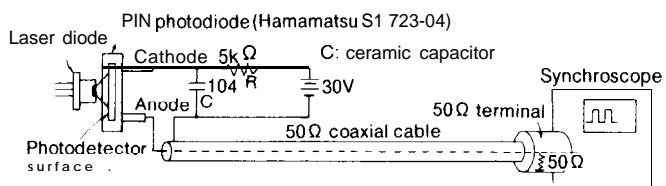

Note Connect the current limiter resistance R, coupling capacitor C and the end of the 50Ω coaxial cable near the photodiode