



# **Field Programmable Gate Array**

*European Applications  
Seminar*



# FPGA APPLICATIONS SEMINAR

*Easy Logic Integration*



**Texas Instruments**

# Agenda

---

- ***PLD/FPGA Architecture Analysis***
- ***How To Replace TTL With FPGA***
- ***How To Replace PLD With FPGA***
- ***Applications Benchmarks***
- ***FPGA Design With VHDL***
- ***FPGA Products And Development Systems***



# Agenda

---



- ***PLD/FPGA Architecture Analysis***
- ***How To Replace TTL With FPGA***
- ***How To Replace PLD With FPGA***
- ***Applications Benchmarks***
- ***FPGA Design With VHDL***
- ***FPGA Products And Development Systems***

# FPGA Application Examples

---

**COMPUTER:**

PC ADD-ON BOARD FOR NETWORKING

WORKSTATION PERIPHERALS (DMA, DRAM CONTROLLER)

**INDUSTRIAL:**

CONTROLLER FOR MACHINE TOOLS, CRANES, SCALES, PARKING TIMER, LIFTS

IMAGE PROCESSING (SCANNER, ROBOTS, ...)

**TELECOM:**

PABX, CENTRAL UNITS

LINE CARDS

**INSTRUMENTATION:**

MEDICAL EQUIPMENTS

SOPHISTICATED METERS

**AUTOMOTIVE:**

PROTOTYPING TWO WIRES BUS SYSTEM FOR CARS/TRUCKS

CONTROLLERS FOR WIPERS, LIGHTS

**CONSUMER:**

PROFESSIONAL VCR

**SPACE:**


AIRCRAFT CONTROLLER



**FPGA**

# PLD / FPGA Architectures

---

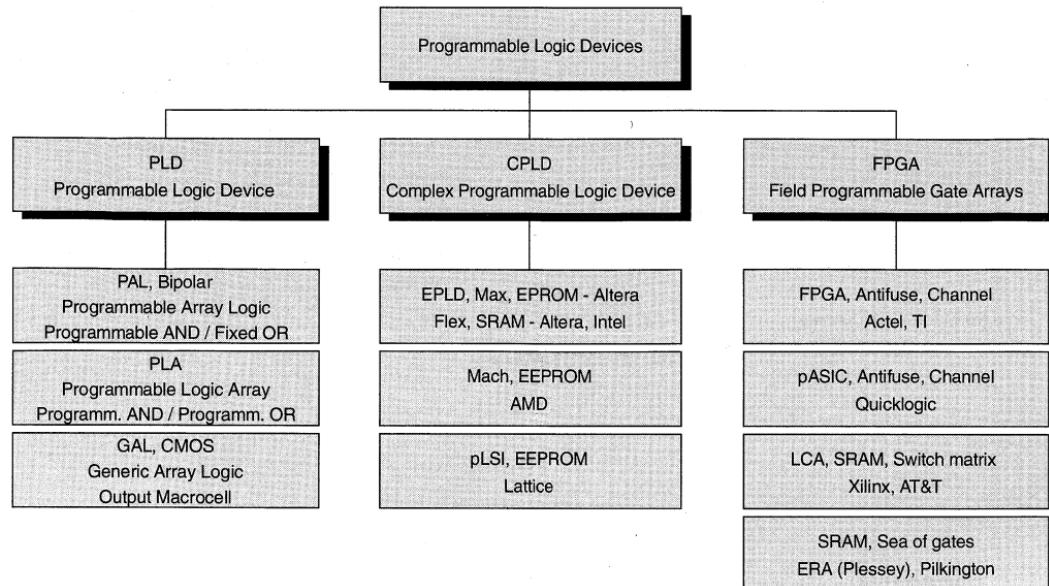


---

*Easy Logic Integration*




# PAL/PLA Evolution

PAL

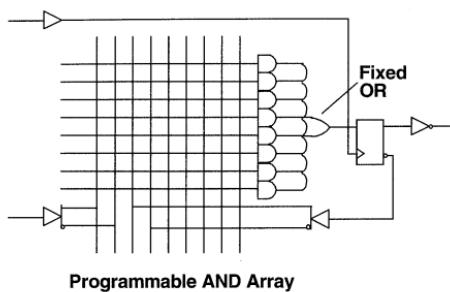

Programmable AND Array

PLA

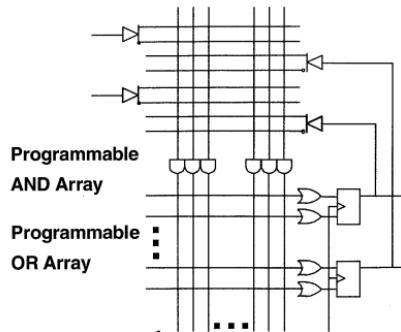


Programmable  
AND Array

Programmable  
OR Array

Multilevel Array

Programmable  
NAND Expander Array

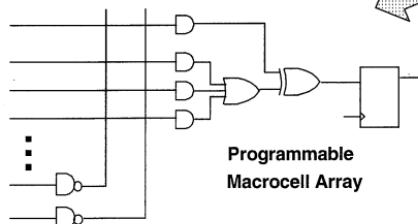


FPGA

*Easy Logic Integration*



# Macrocell Utilisation

---

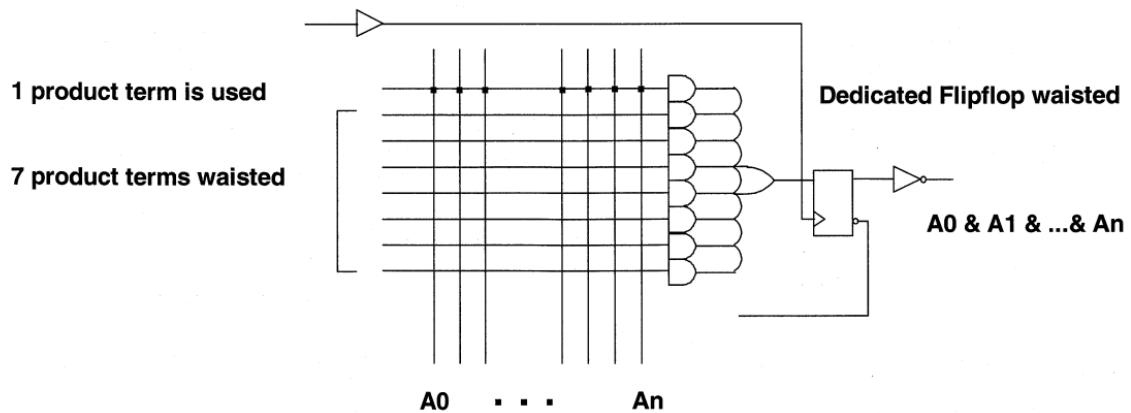

A typical address decoder

# LCA vs FPGA

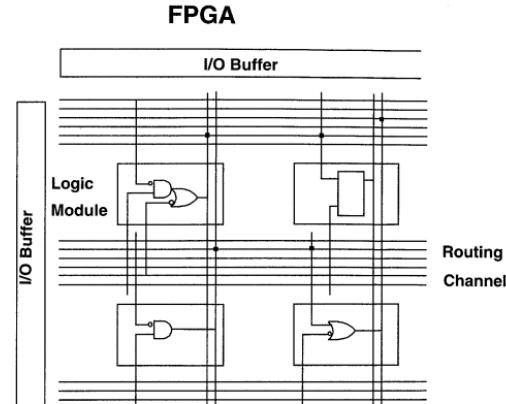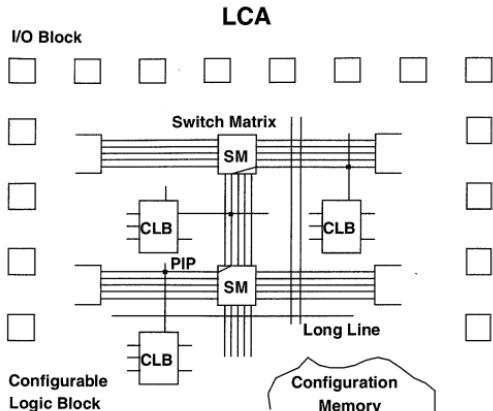


- **Volatile SRAM cells, 2-chip solution**
- **XC3090: 9000 nominal gates in 320 Configurable Logic Blocks, big building block**
- **Complex to use switch matrix**
- **Routing time in hours / days**

- **Non-volatile antifuses, 1-chip solution**
- **TPC1280: 8000 gates in 1232 logic modules, fine granularity**
- **Simple to use routing channels**
- **Routing time in minutes / one hour**


# Sea of Gates vs Channeled Architecture

Sea of Gates

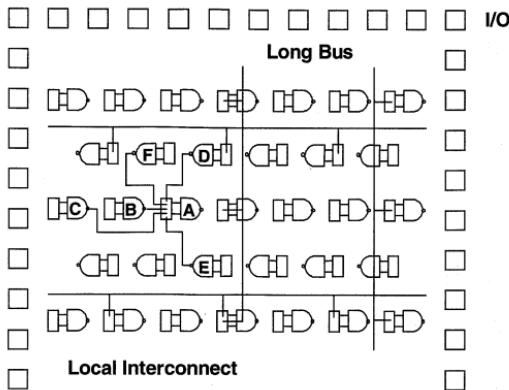

- High nominal but low usable gate count
- Limited and complex routing
- Low gate utilisation
- Difficult place & route

FPGA Channeled Gate Array

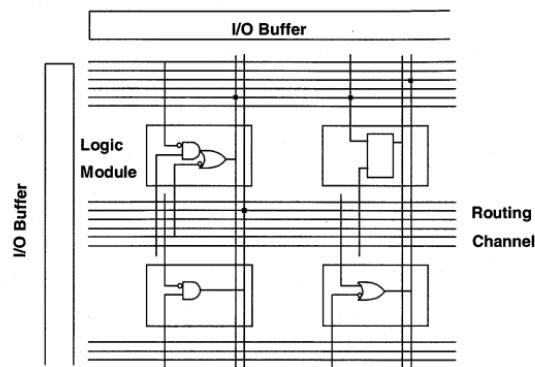

- Medium nominal but high usable gate count
- Efficient routing channels
- 85% - 95% gate utilisation
- Fast, automatic place & route

Easy Logic Integration




FPGA

# What is FPGA?

---

- A family of Field Programmable Gate Arrays which combines the complexity and flexibility of real gate arrays with the user programmability of PALs.
- A one chip solution using "Antifuses" as high-density, non-volatile and reliable programming elements.
- A channeled gate array architecture with efficient logic modules, simple and easy to use horizontal and vertical routing tracks.
- Allow 85-95% gate utilization, fast and 100% automatic Place & Route.
- FPGA "Actionprobe" allows in-circuit debug and 100% observability of all internal nodes.


# FPGA Architecture

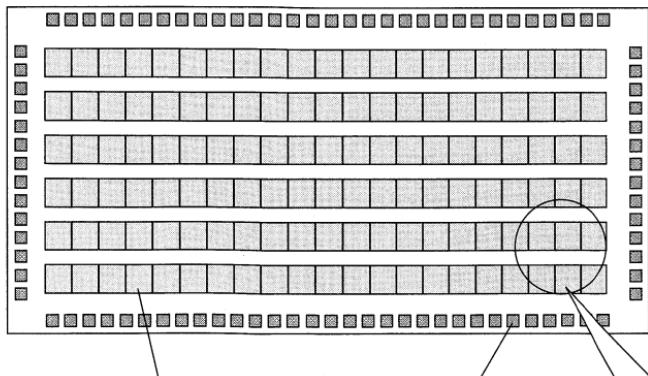

LogicModule

I/O Pad

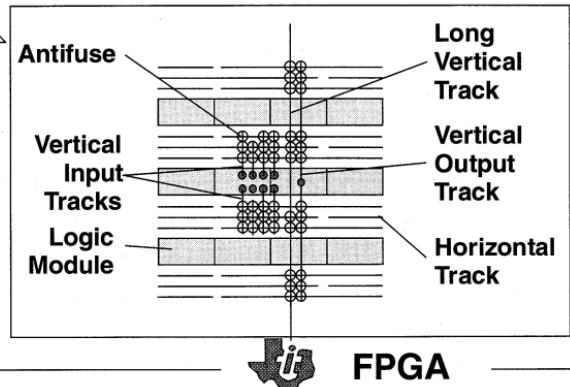- Array architecture similar to gate array
- Rows of logic modules interconnected by horizontal and vertical routing tracks
- I/O pads on periphery
- Programmable antifuse elements used to connect routing tracks




*Easy Logic Integration*



FPGA


# Antifuse

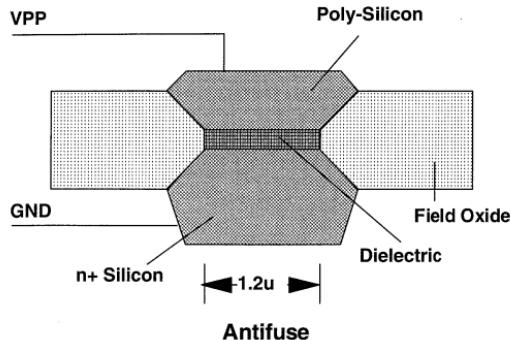

Parameter	Value
Programming Voltage VPP	21V
Programming Time	< 5ms
Programming Current	< 10mA
On Resistance	~ 500 Ohms
Off Resistance	> 100 MOhms
Geometrie	1.2μ x 1.6μ

- PAL fuses are normally connecting. FPGA Antifuses are non-connecting
- Antifuses consist of two conducting layers, separated from each other by a thin dielectric
- During programming, electrical pulses are applied across the antifuse that breaks down the dielectric and creates a conducting path
- The antifuse size is 1/20th the size of an SRAM size and 1/10 of an EPROM cell

# Routing Interconnects

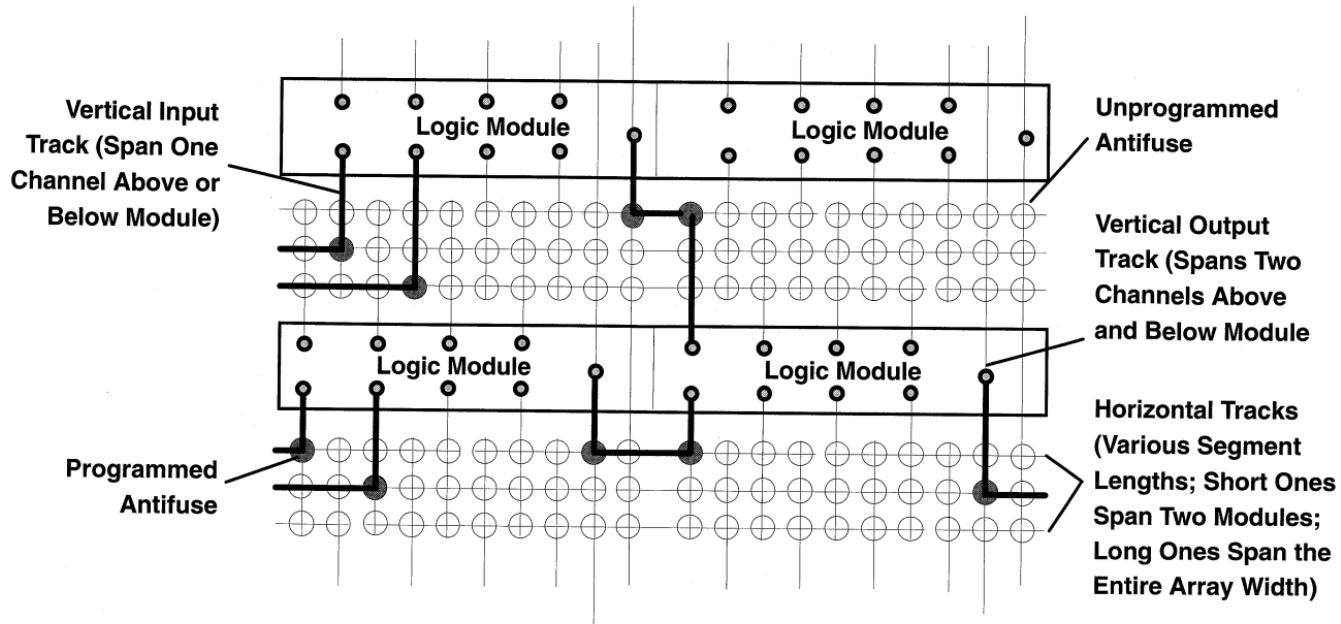


*Easy Logic Integration*



FPGA

# Architecture Summary

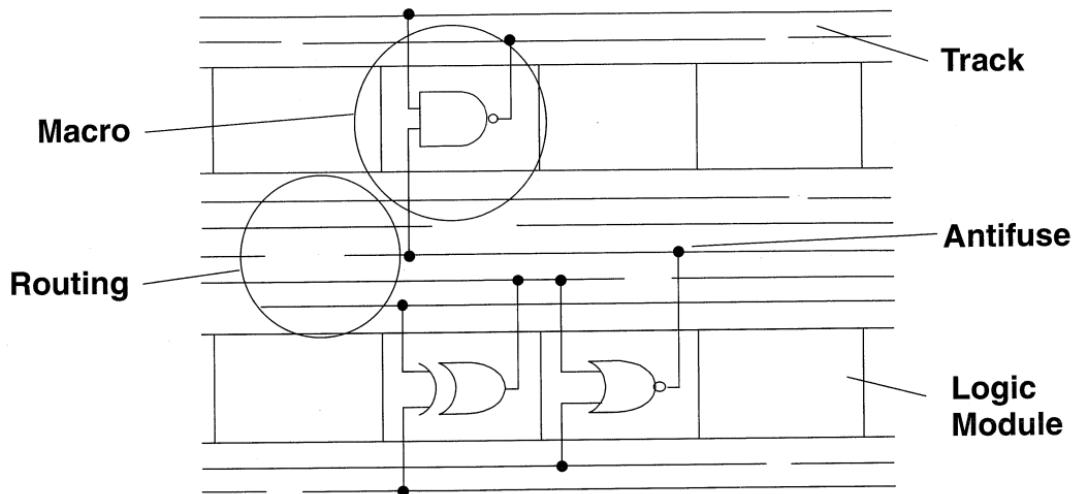


— *Easy Logic Integration* —




FPGA

# TPC10 Logic Module

**Block Diagram**

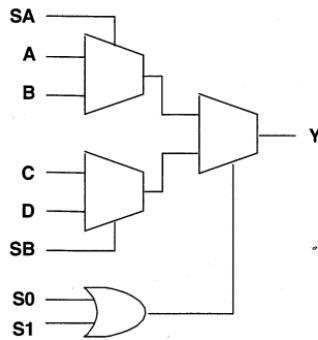

**Logic Diagram**

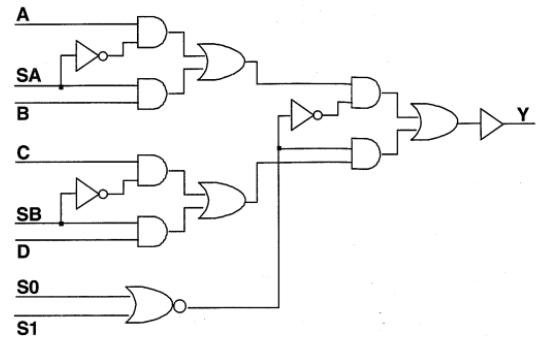

- TPC10 series has only combinatorial logic modules
- Every logic module consists of 8 inputs and one output
- Emulates the function of three 2-input multiplexors and one OR gate


Easy Logic Integration




FPGA

# TPC12 Logic Modules

Combinatorial Module

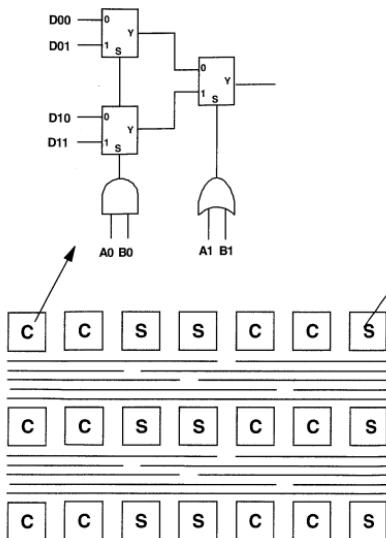

Sequential Module

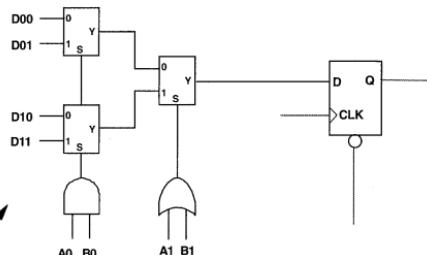


Easy Logic Integration



FPGA

# FPGA Hard Macros

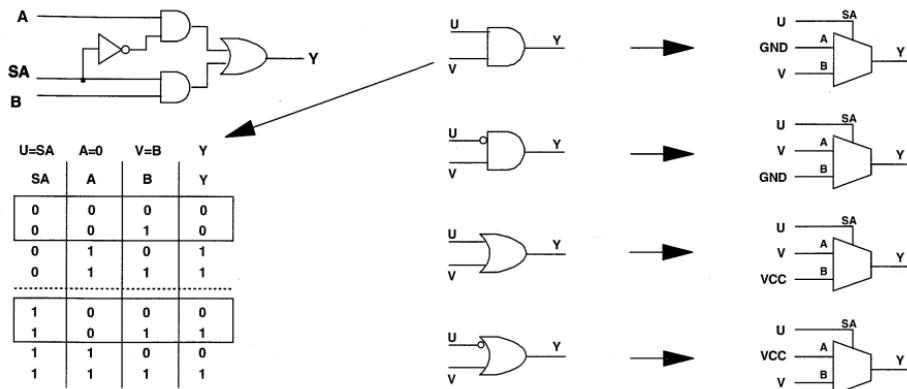


- FPGA hard macros are built from logic modules by programming the appropriate antifuses to connect the module inputs to GND or VCC
- The logic module architecture is capable of building complex gates or flip-flops with a minimum of resources

# FPGA Simplifies Logic


## Standard Logic

Example1: 5 Gates, 4 Nets

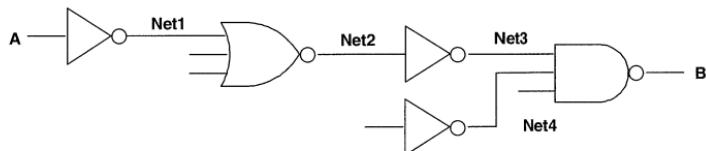


## Equivalent FPGA Logic


2 Gates, 1 Net

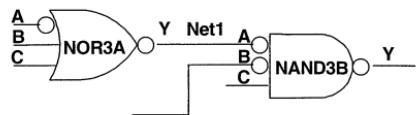

Example 2: 1 Gate + 1 Flipflop

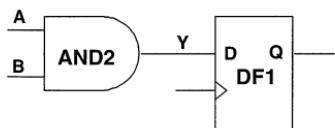

1 Multiplexed D-Flipflop

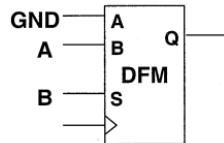




Easy Logic Integration



FPGA
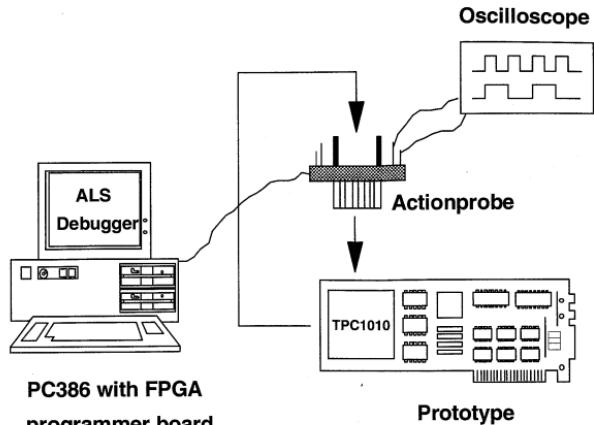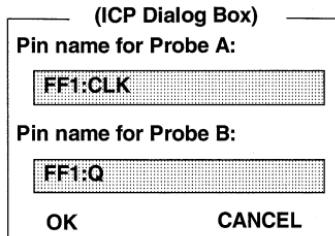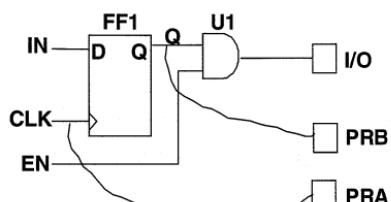
# In-Circuit Probe

Debugger  
Assign  
Low  
High  
Hi-Z  
FAssign  
Step  
Print  
FPrint  
Setup  
**ICP**  
View  
Exit  
Design




- 1) Remove FPGA from prototype
- 2) Plug FPGA in Actionprobe socket
- 3) Plug Actionprobe in FPGA socket on prototype




FPGA

# Actionprobe

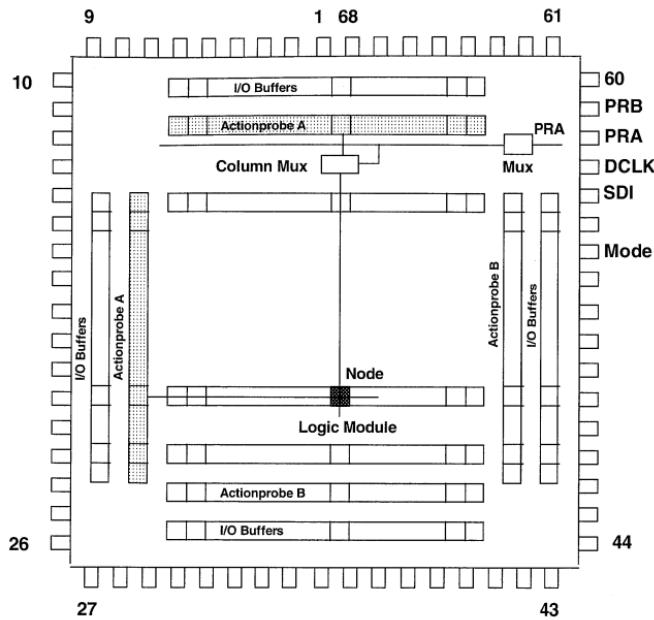

- Actionprobe allows 100% observability of any internal node in the array
- The device is switched into the Probe Mode (Mode)
- The node address is shifted to the device through the Serial Data Input (SDI) and loaded into the row and column registers
- The node is then connected to the pin PRA or PRB. DCLK is the Data Clock for SDI

# Product Roadmap

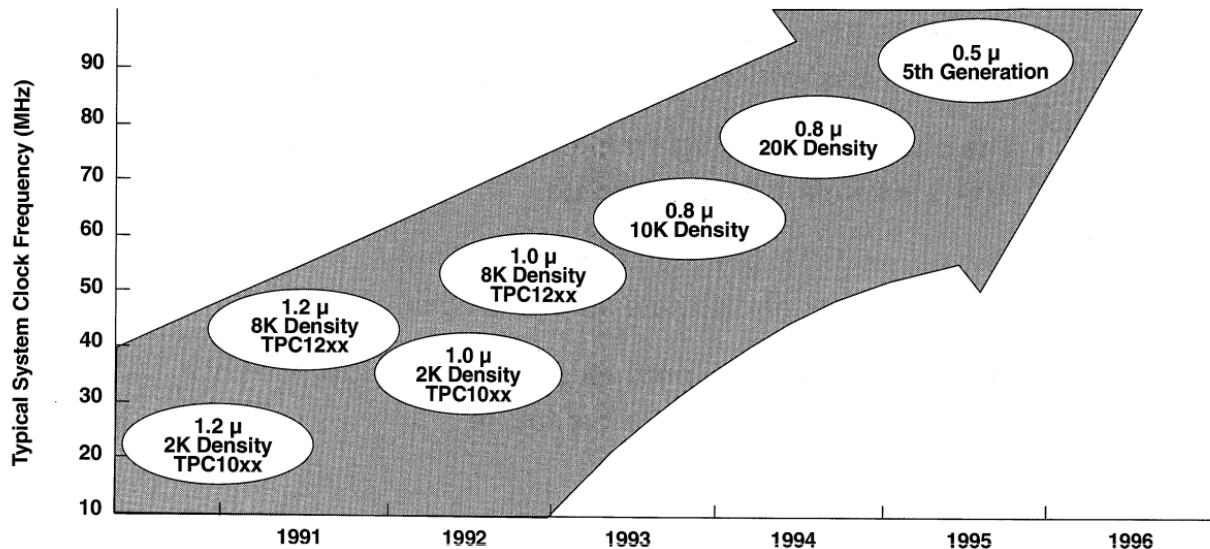

Easy Logic Integration



FPGA

# Summary

---

- TI FPGAs have fine grained logic modules which facilitate cost-efficient utilization of silicon resources.
- The channeled routing architecture allows fast and 100% automatic Place & Route.
- The non-volatile antifuses provide reliable interconnects and enable an one chip solution.
- The small size of the antifuses allows development of highest density FPGAs in the future .

# Agenda


---



- ***PLD/FPGA Architecture Analysis***
- ***How To Replace TTL With FPGA***
- ***How To Replace PLD With FPGA***
- ***Applications Benchmarks***
- ***FPGA Design With VHDL***
- ***FPGA Products And Development Systems***

# Why Use FPGA?

---

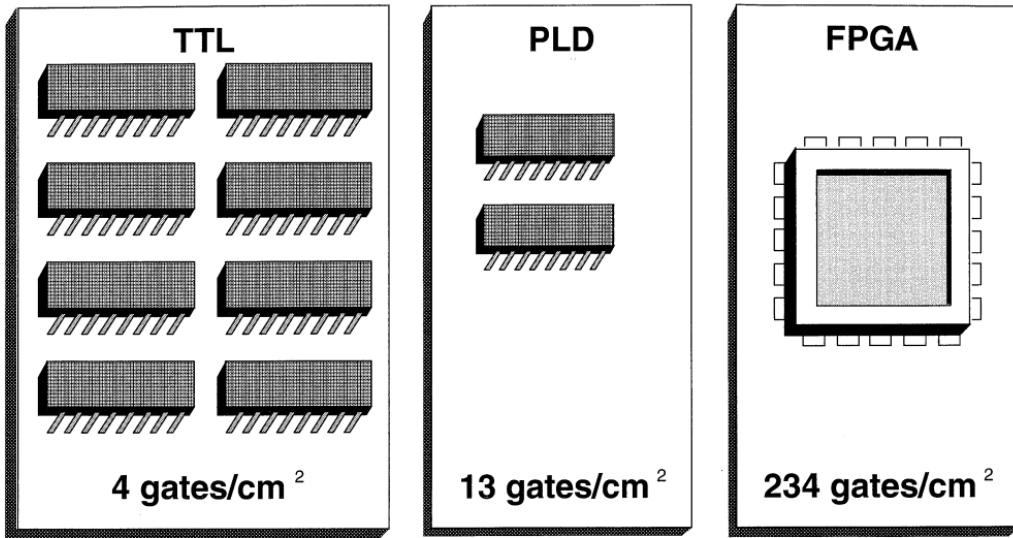

Source: In-Stat Forum, May 1990

---

*Easy Logic Integration*




**FPGA**

---

# A Case Study




---

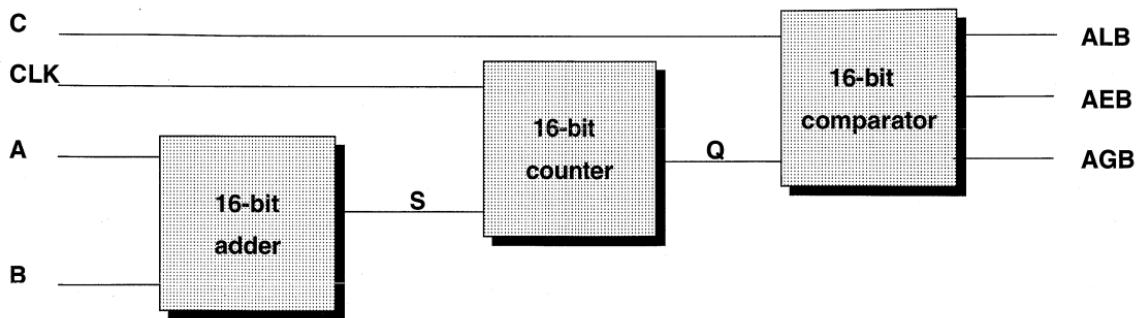


- Two 16-bit numbers A and B are added.
- The sum S is loaded to a preloadable 16-bit counter.
- A 16-bit comparator compares the count Q with a 16-bit number C.
- The outputs are ALB ( $A < B$ ), AEB ( $A = B$ ) and AGB ( $A > B$ ).

# A TTL Solution

---

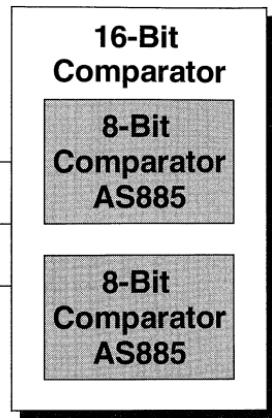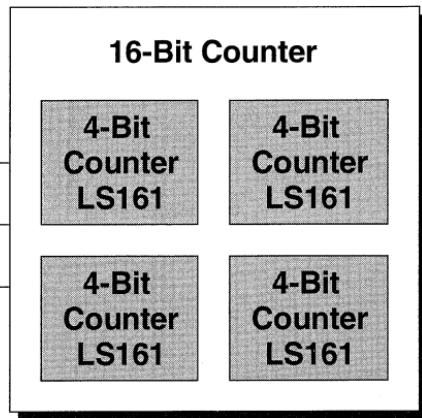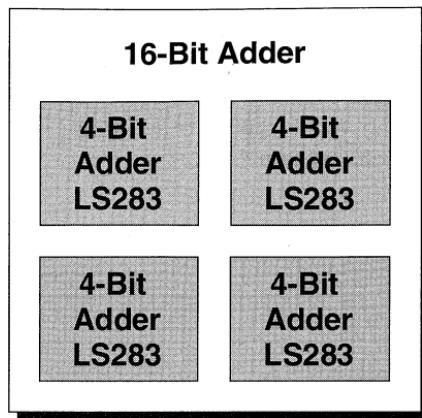

# FPGA Solution

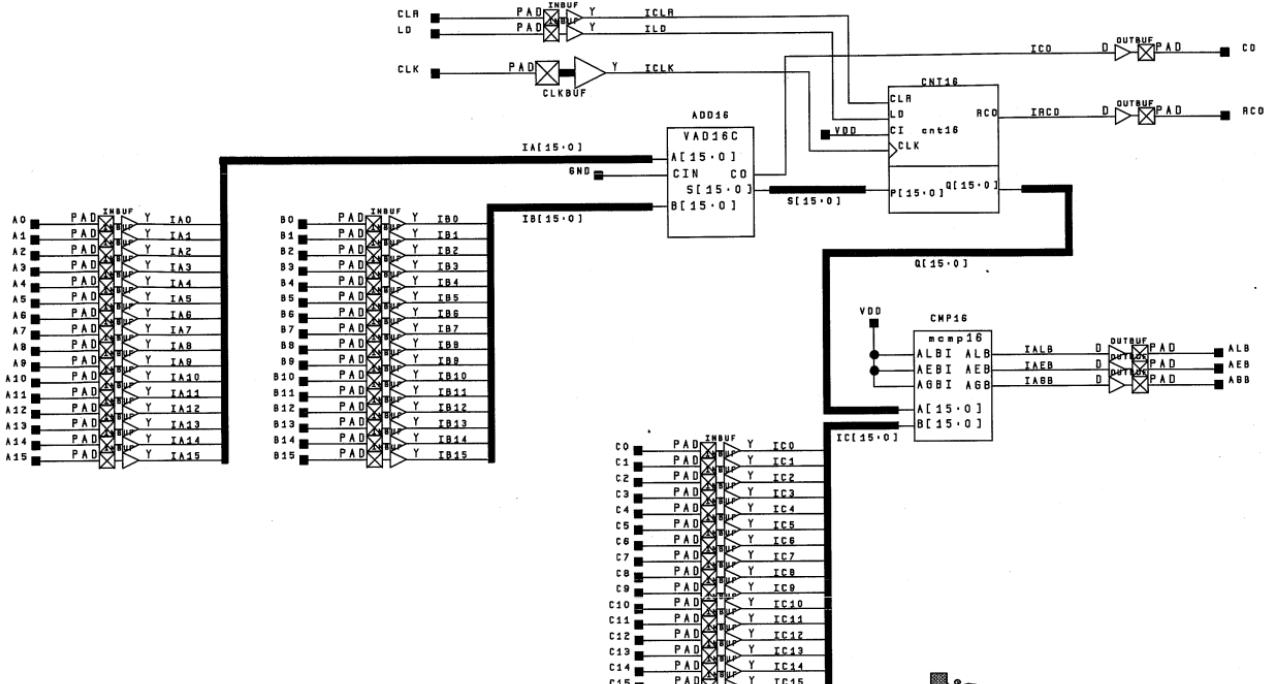

Easy Logic Integration



FPGA

# TTL versus FPGA Analysis

	TTL			TPC1225A			
	TTL Devices	tpd	Icc	% Device used	tpd	Icc	
16-Bit Adder	4xLS283	95 ns	130 mA	21%	64 ns	80 mA	
16-Bit Counter	4xLS161	130 ns	128 mA	16%	45 ns		
16-Bit Comparator	2xAS855	35 ns	420 mA	16%	114 ns		
Soldered Pins	176			85 (56 Used)			
Icc Total	687 mA			80 mA			
Device Cost	\$11.00 (10 Packages)			\$40.00 (1 Package) 53% used			
PCB Cost	\$20.00			\$5.00			
Total Cost	\$31.00			\$45.00			


- *Reduce board space*
- *Reduce power consumption*
- *Reduce test effort*
- *Improve reliability*
- *Reduce cost*

— Easy Logic Integration —




FPGA

# FPGA Design Flows

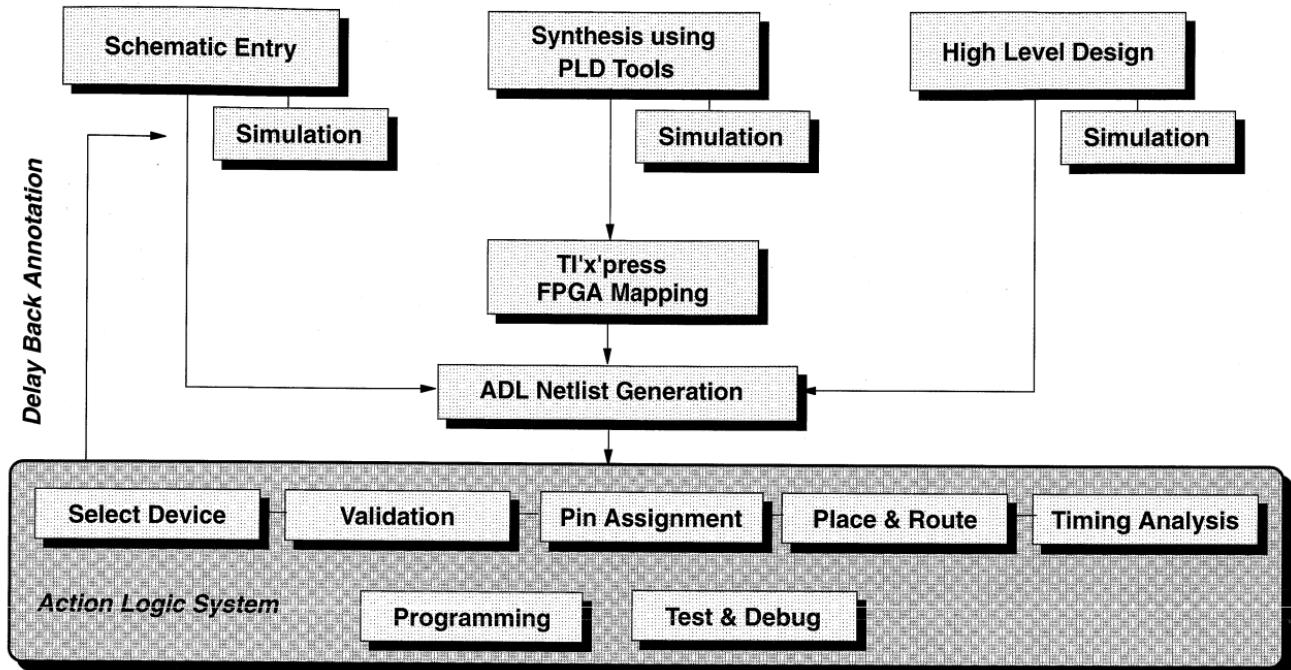

# Action Logic System

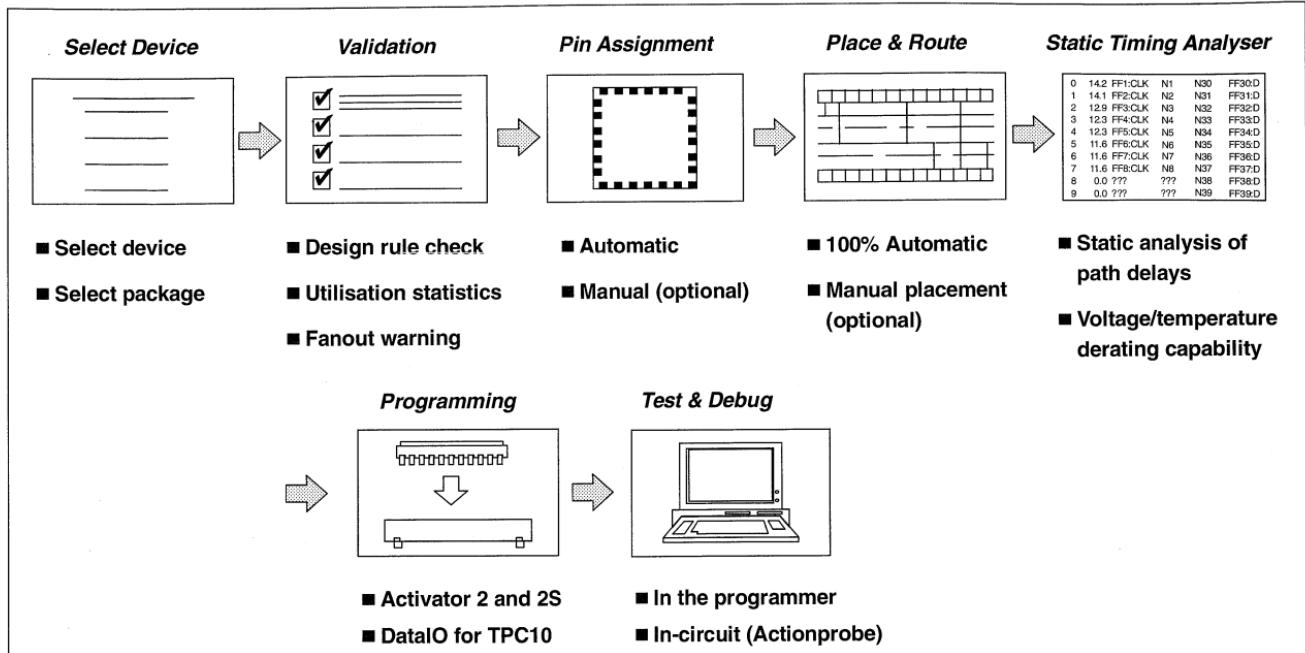

Easy Logic Integration




FPGA

# How To Replace TTL With FPGA

---

- Many TTL functions can be replaced directly by an equivalent soft macro from the library. For example, the TA161 is an equivalent soft macro for the TTL 4-bit counter 161.
- If there is no direct replacement, another soft macro may be used to realize the function:  
For example, the soft macros FADD16 (16-bit adder) or VADD16C (very fast 16-bit adder) can be used to replace four TTL 4-bit adders HC283.
- In other cases, users can create user macros using soft macros or hard macros from the library.  
For example, a 16-bit comparator can be built by cascading two 8-bit comparator soft macros MCMPC8.

# TTL To FPGA Design Flow

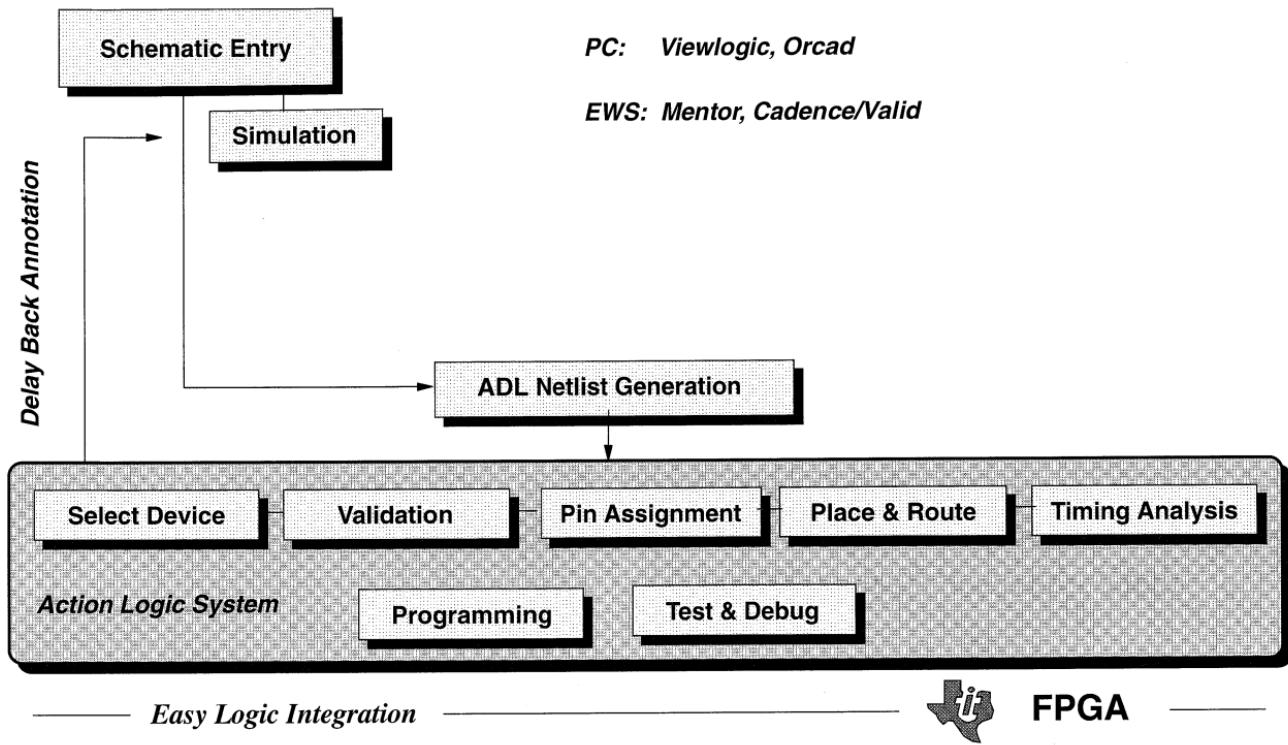

# TTL Soft Macros 1

Soft Macro	Function	Logic Levels	S-Module	C-Module
TA00	2-input NAND	1	0	1
TA02	2-input NOR	1	0	1
TA04	Inverter	1	0	1
TA07	Buffer	1	0	1
TA08	2-input AND	1	0	1
TA10	3-input NAND	1	0	1
TA11	3-input AND	1	0	1
TA20	4-input NAND	1	0	2
TA21	4-input AND	1	0	1
TA27	3-input NOR	1	0	1
TA32	2-input OR	1	0	1
TA40	4-input NAND	1	0	2
TA42	4 to 10 decoder	1	0	10
TA51	AND-OR-Invert	1	0	2
TA54	4-wide AND-OR-Invert	2	0	5
TA55	2-wide AND-OR-Invert	2	0	3
TA86	Quad 2-input XOR	1	0	1
TA138	3-to-8 decoder	2	0	12
TA139	Dual 2-to-4 decoder	1	0	4

# TTL Soft Macros 2

---

Soft Macro	Function	Logic Levels	S-Module	C-Module
TA150	16-to-1 multiplexor	3	0	6
TA151	8-to-1 multiplexor	3	0	5
TA153	4-to-1 multiplexor	2	0	2
TA154	4-to-16 decoder	2	0	22
TA157	2-to-1 multiplexor	1	0	1
TA160	4-bit decade counter	4	4	12
TA161	4-bit binary counter	3	4	10
TA164	8-bit shift register	1	8	0
TA169	4-bit updown counter	6	4	14
TA174	Hex D-flipflops	1	6	0
TA175	Quad D-flipflops	1	4	0
TA190	BCD updown counter	7	4	31
TA191	4-bit updown counter	7	4	30
TA194	4-bit shift register	1	4	4
TA195	4-bit shift register	1	4	1
TA269	8-bit updown counter	8	8	28
TA273	Octal register	1	8	0
TA280	Parity generator	4	0	9
TA377	Octal register	1	8	0
TA688	8-bit comparator	3	0	9

# Complex Soft Macros 1

Function	Description	Name	Logic Levels	S-Modules	C-Modules
Counters	4-bit counter	CNT4A	4	4	8
	4-bit counter (Cl, CO inverted)	CNT4B	4	4	7
	4-bit updown counter	UDCNT4A	5	4	13
	very fast 16-bit counter	VCNT16C	1	34	31
	2-bit down counter, prescaler	VCNT2CP	1	5	2
	2-bit down counter, MSB	VCNT2CU	1	2	3
	4-bit down counter, middle bits	VCNT4C	1	4	8
	4-bit down counter, LSB	VCNT4CL	1	4	7
Decoders	2-to-4 decoder	DEC2X4	1		4
	2-to-4 decoder, active low outputs	DEC2X4A	1		4
	3-to-8 decoder	DEC3X8	1		8
	3-to-8 decoder, active low outputs	DEC3X8A	1		8
	4-to-16 decoder	DEC4X16A	2		20
	2-to-4 decoder with enable	DECE2X4	1		4
	2-to-4 decoder, active low outputs	DECE2X4A	1		4
	3-to-8 decoder with enable	DECE3X8	2		11
	3-to-8 decoder, active low outputs	DECE3X8A	2		11

— Easy Logic Integration —



FPGA

# Complex Soft Macros 2

Function	Description	Macro Name	Logic Levels	S-Modules	C-Modules
Registers	octal latch	DLC8A	1	8	
	octal latch with enable	DLE8	1	8	
	octal latch with mux	DLM8	1	8	
	4-bit shift register	SREG4A	1	4	
	8-bit shift register	SREG8A	1	8	
Adders	8-bit adder	FADD8	3		44
	9-bit adder	FADD9	3		49
	10-bit adder	FADD10	3		56
	12-bit adder	FADD12	4		69
	16-bit adder	FADD16	5		97
	2-bit sum generator	SUMX1A	2		5
	very fast 16-bit adder	VADD16C	3		97
Comparators	4-bit identity comparator	ICMP4	2		5
	8-bit identity comparator	ICMP8	3		5
	2-bit magnitude comparator with enable	MCMPC2	3		9
	4-bit magnitude comparator with enable	MCMPC4	4		18
	8-bit magnitude comparator with enable	MCMPC8	6		36
Multiplexors	8-to-1 multiplexor	MX8	2		3
	8-to-1 multiplexor with active low outputs	MX8A	2		3
	16-to-1 multiplexor	MX16	2		5


# How To Create A User Soft Macro

---

To create a 16-bit user soft macro you do the following steps:


- Open a schematic window with your CAE tool (e.g. Viewdraw | Schematic)
- Use the 4-bit counter soft macro TA161 from the library to design a 16-bit counter as if you were designing with a LS161
- Write the file to create a netlist. Viewlogic saves this file under a /SCH sub-directory
- Open a symbol window (e.g. Viewdraw | Symbol) and draw a symbol for the 16-bit counter
- Write the symbol file with the same name as the schematic file name. Viewlogic saves this file under a /SYM sub-directory
- You can use your user soft macro in a similar way to a soft macro from the library

# 16-Bit Counter With 4 TA161

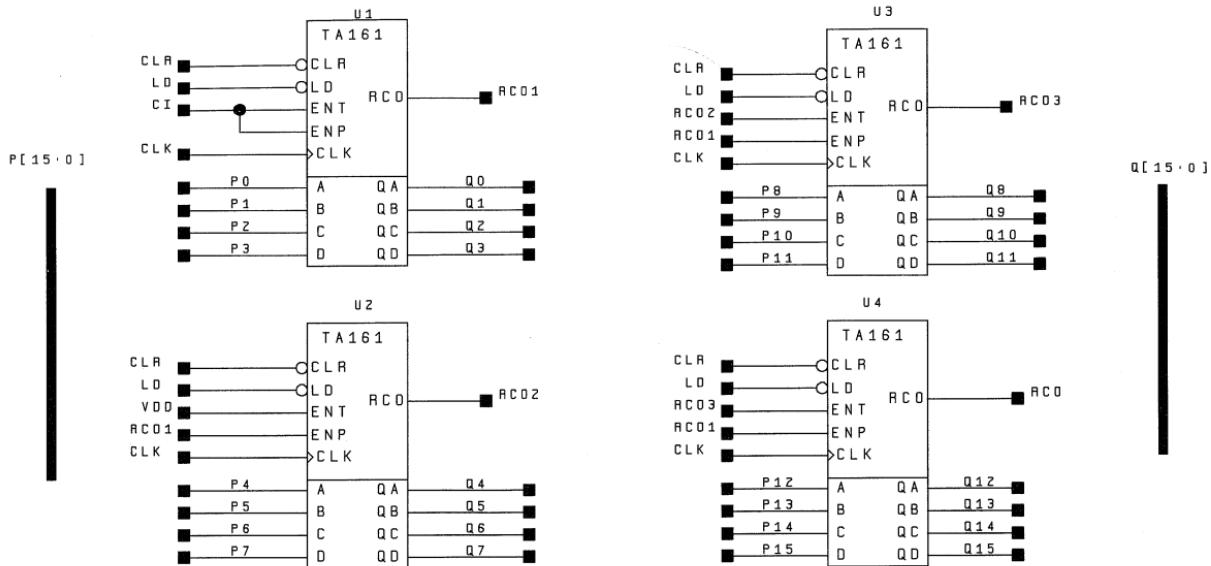

# 16-Bit Counter User Symbol

---

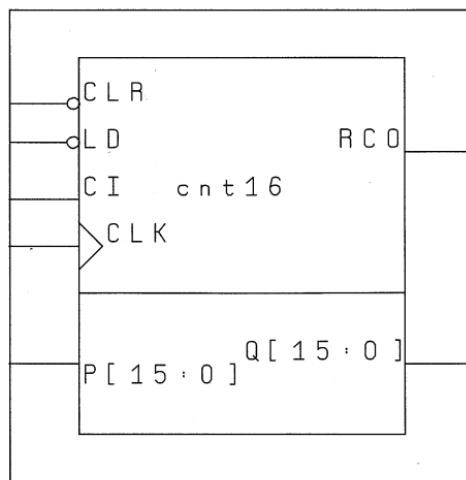


---

*Easy Logic Integration*



FPGA

# 16-Bit Adder Soft Macro

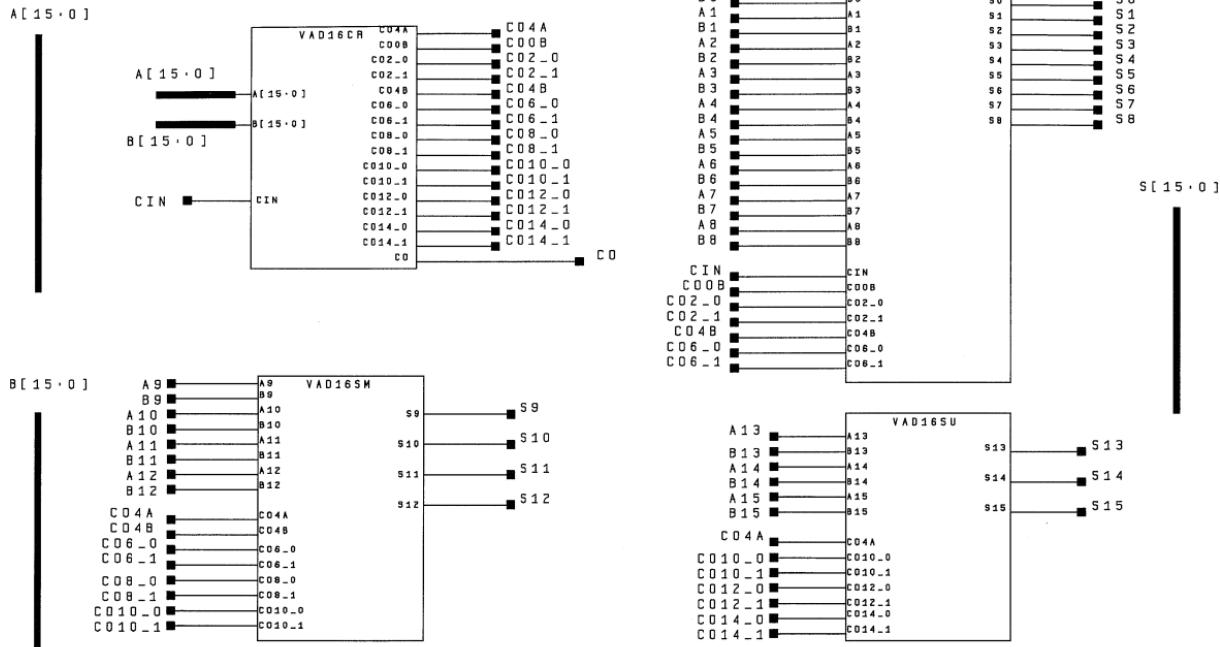


Easy Logic Integration



FPGA

# 16-Bit Comparator

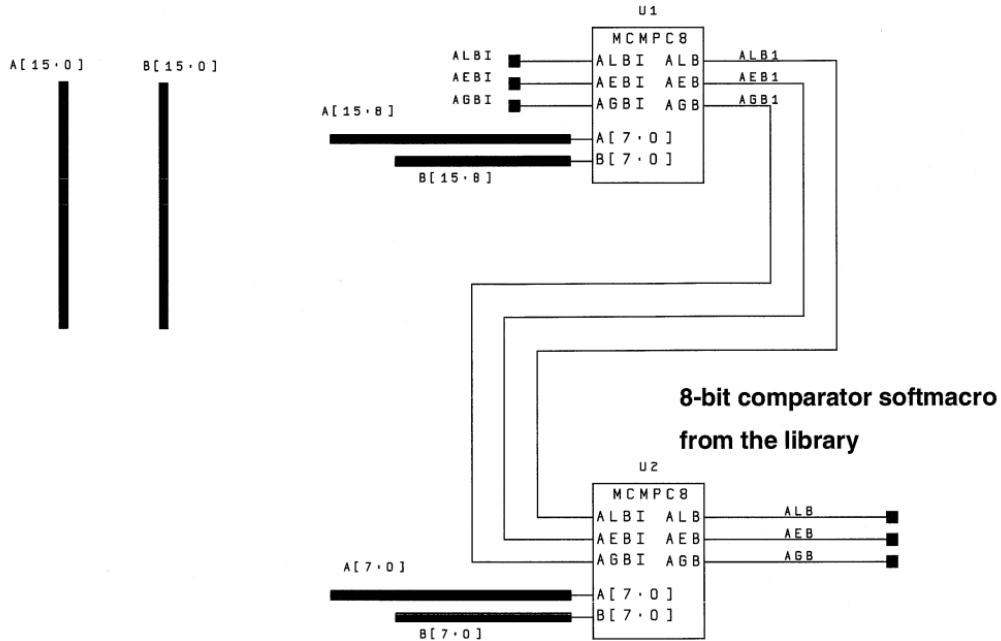


Easy Logic Integration



# FPGA Timing Analysis


---

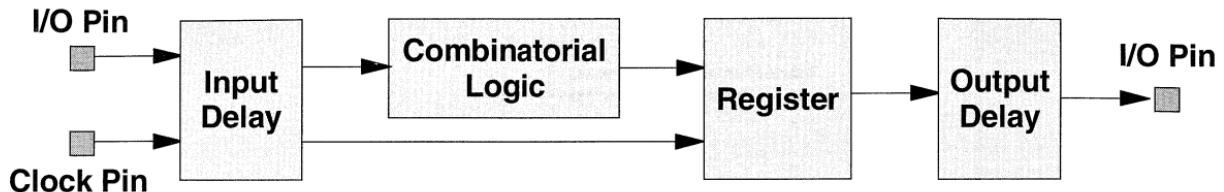

Propagation delay time (**tpd**) depends on:

- Levels of combinatorial logic
- Length of routing tracks used
- Number of antifuse elements used
- Number of logic modules being driven (FANOUT)

# Combinatorial Logic Timing

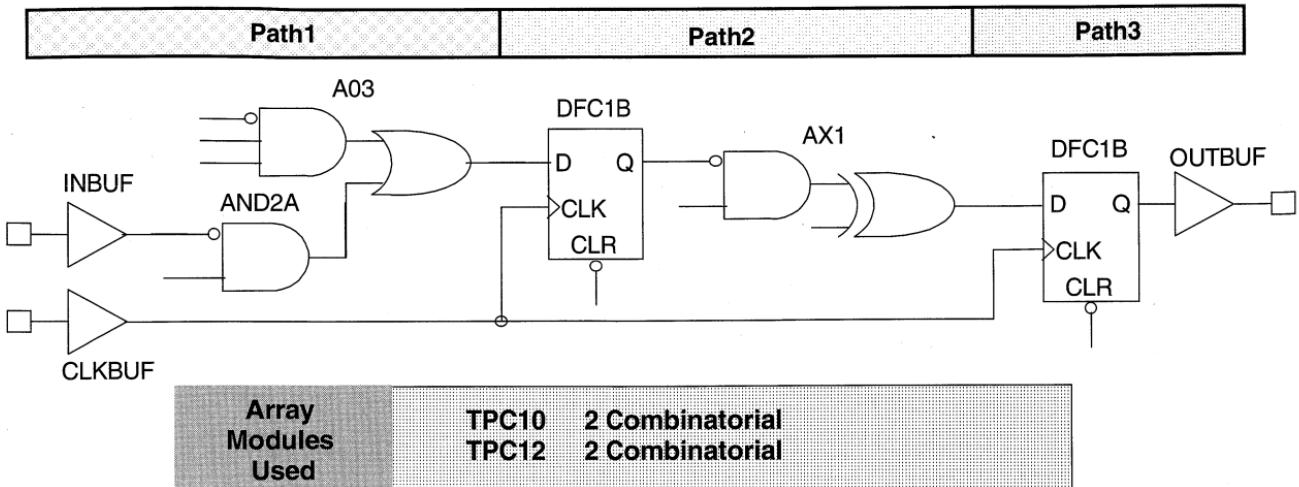


$$\begin{aligned} \text{Path 1 Delay} &= \text{INBUF} + \text{AND2A} + \text{A03} + \text{DFC1B}_{tsu} \\ \text{TPC10} &= 10.6 + 9.7 + 9.7 + 3.9 = 33.6 \text{ ns} \\ \text{TPC12} &= 9.2 + 8.0 + 0.0 + 0.4 = 17.6 \text{ ns} \end{aligned}$$

Easy Logic Integration



FPGA

# Sequential Logic Timing

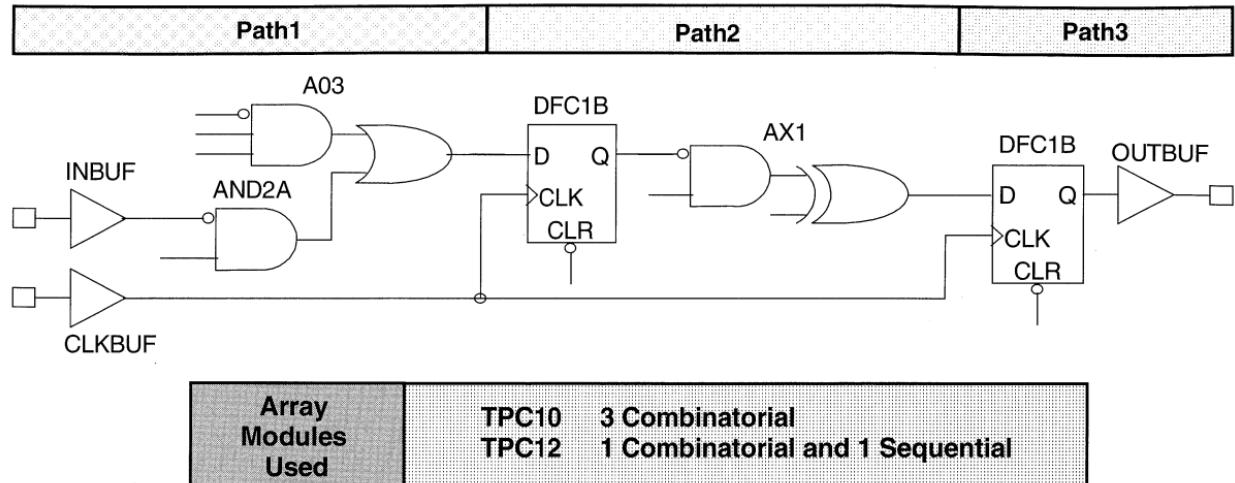


Path 2 Delay = DFC1B + AX1 + DFC1B<sub>tsu</sub>

$$\text{TPC10} = 9.7 + 9.7 + 3.9 = 23.3 \text{ ns}$$

$$\text{TPC12} = 8.0 + 8.0 + 0.4 = 16.4 \text{ ns}$$

# I/O Module Timing

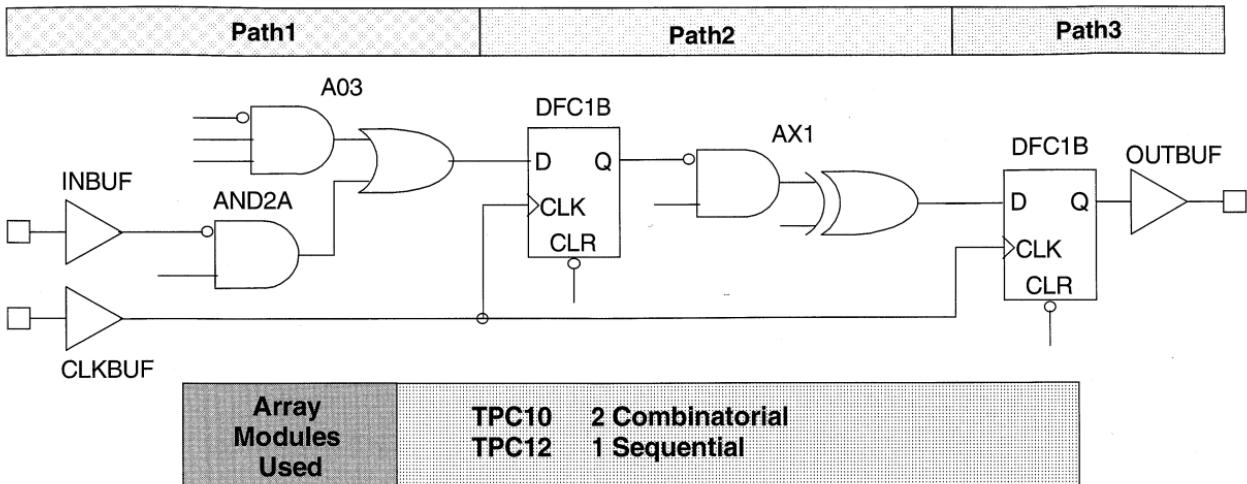


Path 3 Delay = DFC1B + OUTBUF

$$\text{TPC10} = 9.7 + 11.2 = 20.9 \text{ ns}$$

$$\text{TPC12} = 8.0 + 11.6 = 19.6 \text{ ns}$$

# Maximum Frequency

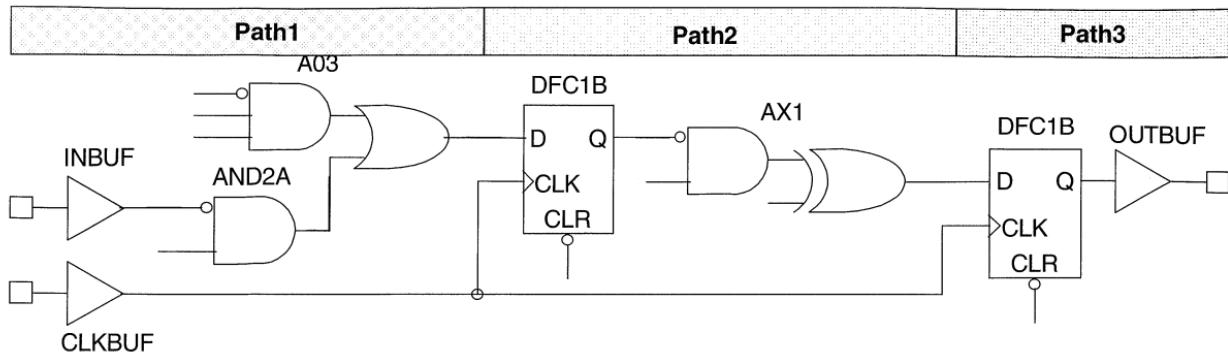

Total Array Modules Used	TPC10	7 Combinatorial
	TPC12	3 Combinatorial and 2 Sequential

Maximum Frequency

$$\text{TPC10} = 29.8 \text{ MHz}$$

$$\text{TPC12} = 51.0 \text{ MHz}$$




FPGA

# Timing Derating Factor


## Delay Time Factor vs Voltage

Delay Time Normalized to Value at 5V

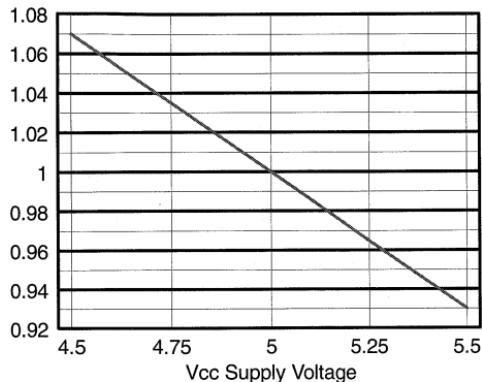

## Delay Time Factor vs Temperature


Delay Time Normalized to Value at 5V

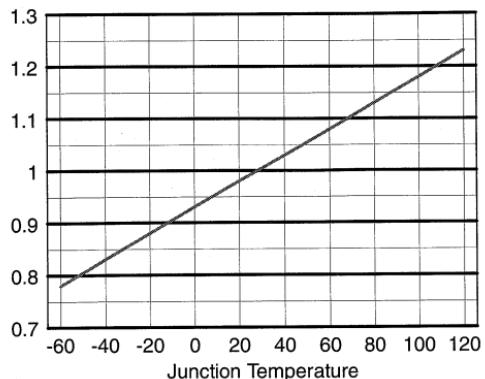

- Back-annotation timing simulation works with typical delays.
- Worst-case timing simulation can be made by using a delay derating factor.
- Worst case Timing Derating Factor (min voltage, max temperature, worst case process):  
C Suffix: 1.40      I Suffix: 1.50      M Suffix: 1.60

# Power Estimates TPC12 Series


---

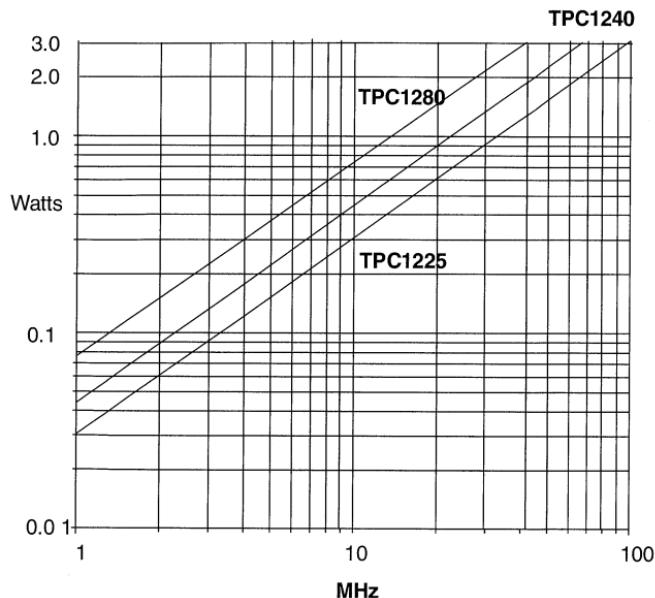

- Maximum static power for commercial device  
Static power =  $10\text{mA} \times 5.25\text{V} = 52.5\text{mW}$
- Active power depends on the frequency and the utilization of the modules
- The power graphs provide a simple guideline for estimating power

# FPGA Device Programming

---

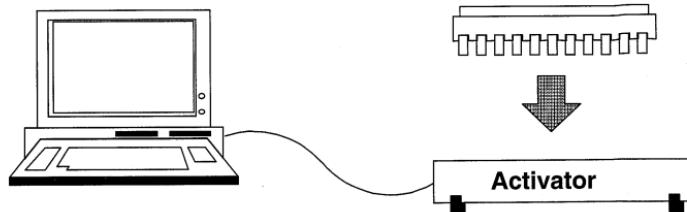

## ***Blank Check***

- Check for correct device
- Verifies each antifuse is unprogrammed
- Displays fuse checksum if programmed

## ***Device Programming***

- Programming pulses applied sequentially
- Programming time between 5 and 20 minutes
- Dynamically verifies each programmed fuse

## ***Design Protection***

- Security fuse
- Probe fuse

---

*Easy Logic Integration*




**FPGA**

---

# Test & Debug

---

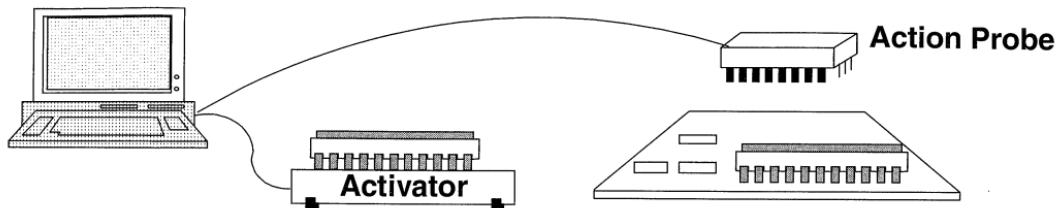

## *In the Activator:*

- Debug allows functional testing of the programmed FPGA by applying input test vectors and monitoring the outputs
- Allows testing of all internal nodes

## *In the prototype board:*

- Actionprobe adapter allows testing of the programmed FPGA under real operation (in-circuit-test)
- Allows display of all internal nodes on an oscilloscope or a logic analyzer

# Kit1e - FPGA Design Kit up to 2500 Gates

---

Description	Part Number
Viewlogic Viewdraw for schematic capture	TPC-ALS-VL-005
'Designer' ALS package for TPC10, TPC12, TPC14 series up to 2500 gates	TPC-ALS-DS-VL-PC
Viewlogic Viewsim simulator up to 3k gates	TPC-ALS-017
Single socket programmer for TPC10, TPC12, TPC12 (Activator 2S)	TPC-ALS-DS-P2S-PC

---

*Easy Logic Integration*



FPGA

# Summary

---

- Standard TTL functions can be replaced easily by FPGA soft macros. A TTL board can be converted and programmed into a FPGA in a week.
- FPGA's offer greater flexibility for design modification. TTL design iterations require a new PCB each time.
- FPGA's offer considerable power reduction
- FPGA's offer more logic integration at lower cost.




# Agenda

---

- ***PLD/FPGA Architecture Analysis***
- ***How To Replace TTL With FPGA***
-  ***How To Replace PLD With FPGA***
- ***Applications Benchmarks***
- ***FPGA Design With VHDL***
- ***FPGA Products And Development Systems***


# Consolidating PLD with FPGA

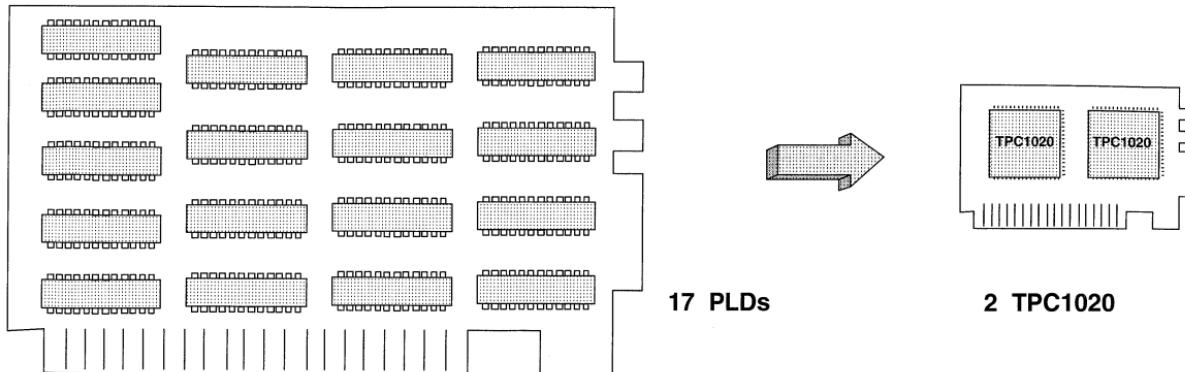


4	GAL16V8	1	PAL22V10	3	EP600
1	GAL18V10	1	PAL29MA16	4	ATV750
1	GAL20V8	1	PAL26V12		
1	GAL6001				



# PLD Solution

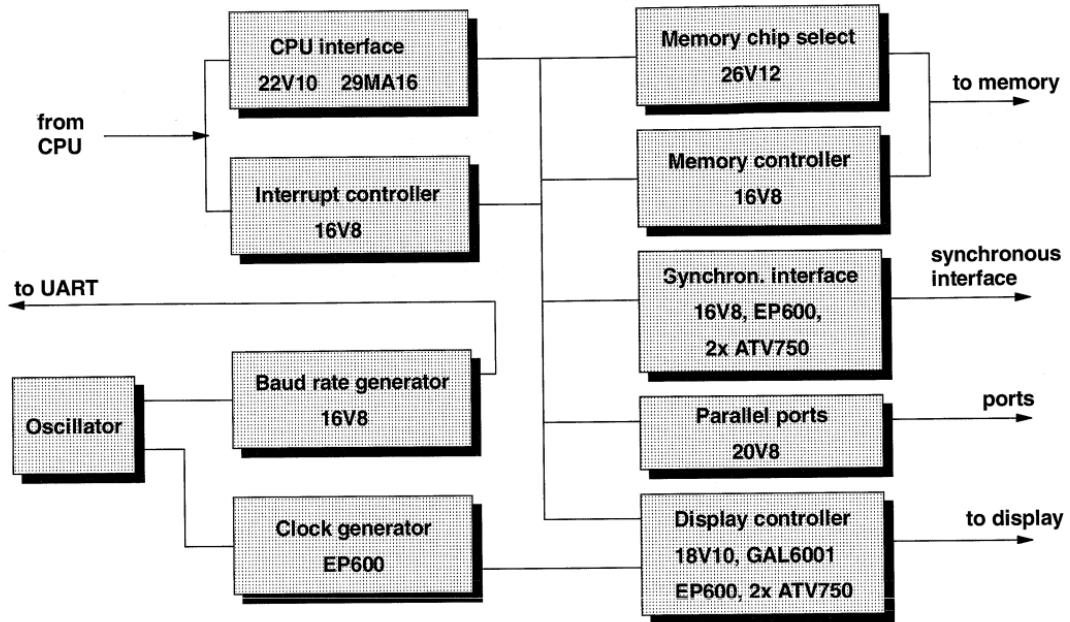

# FPGA Alternative

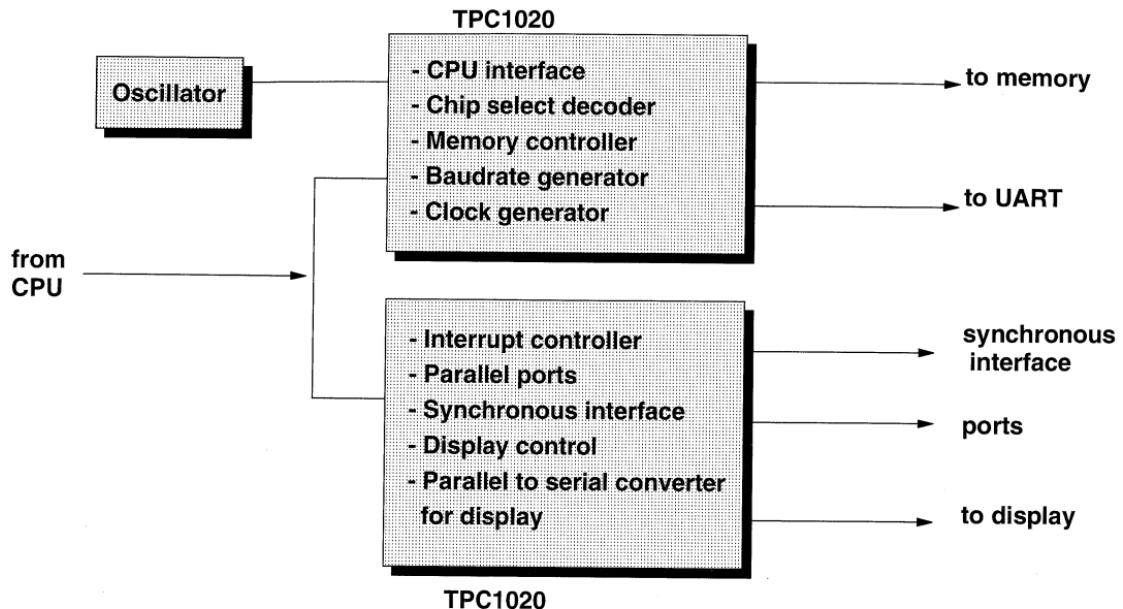

— *Easy Logic Integration* —



**FPGA**


# How To Replace PLD's With FPGA's

---

- PLD designs are normally described as Boolean equations, truth table or state machine using the syntax of a PLD design tool
- All PLD tools can generate reduced equations in PALASM2 format (.PDS)
- The reduced equations are optimized for the PAL AND-OR structure
- FPGA has architecturally-specific gates and flip-flops which yield efficient utilization of device resources
- The PLD equations are remapped and optimized for the FPGA hard macros with synthesis software




# PLD To FPGA Design Flow

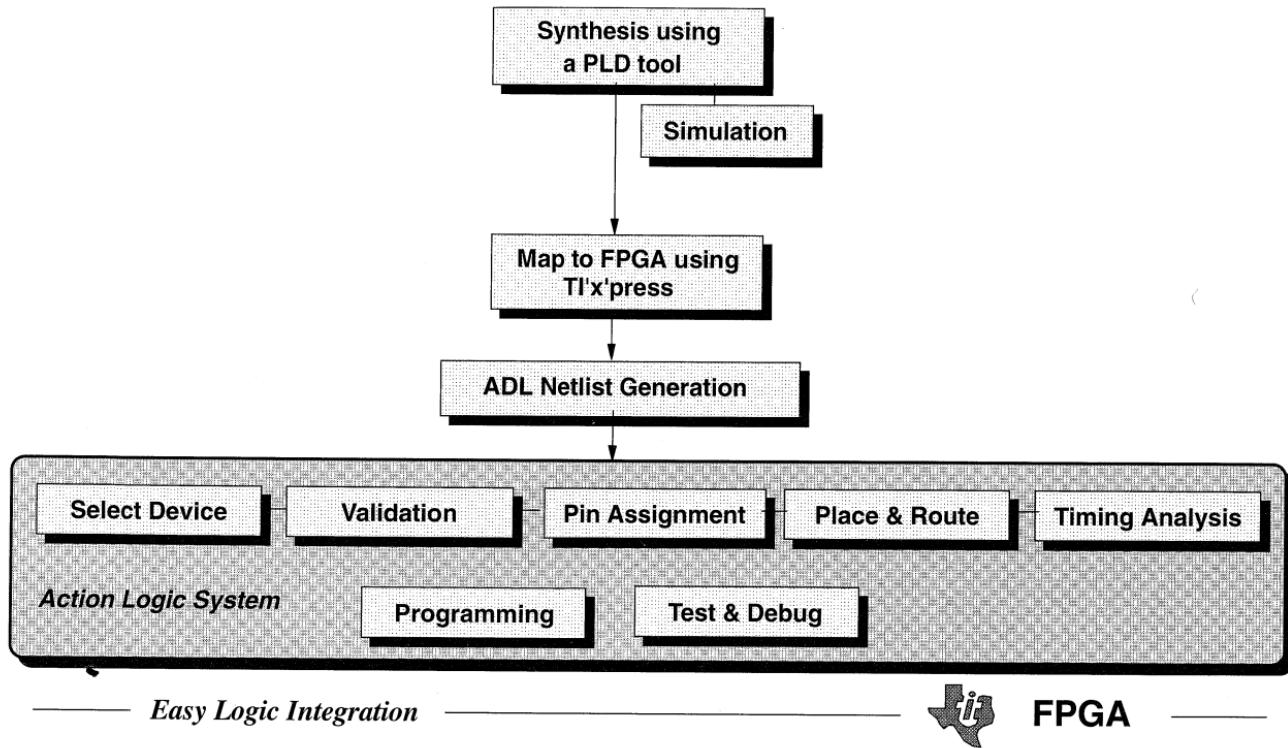

# PLD Synthesis Tools

---

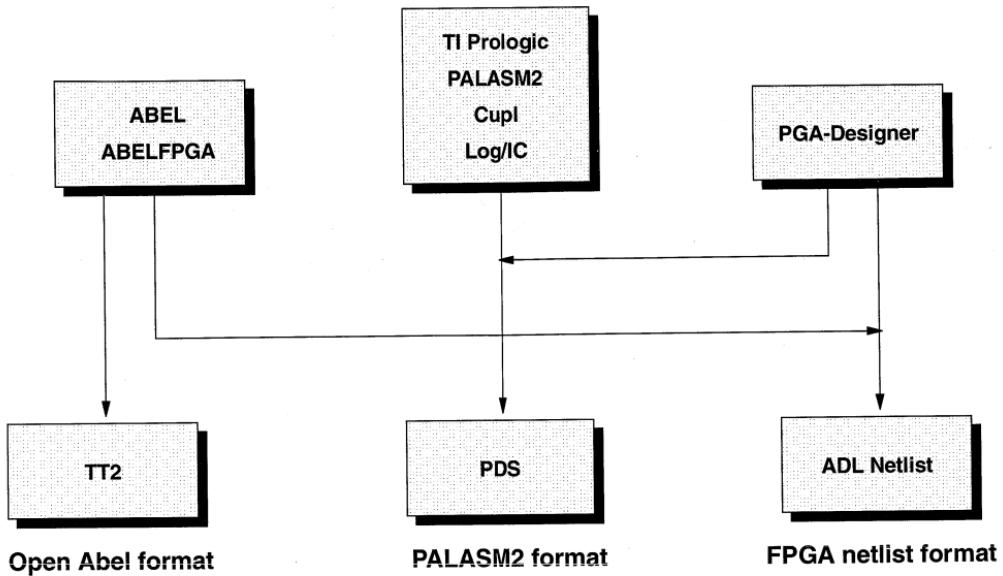


---

*Easy Logic Integration*



# TI Prologic - PLD Synthesis Tool

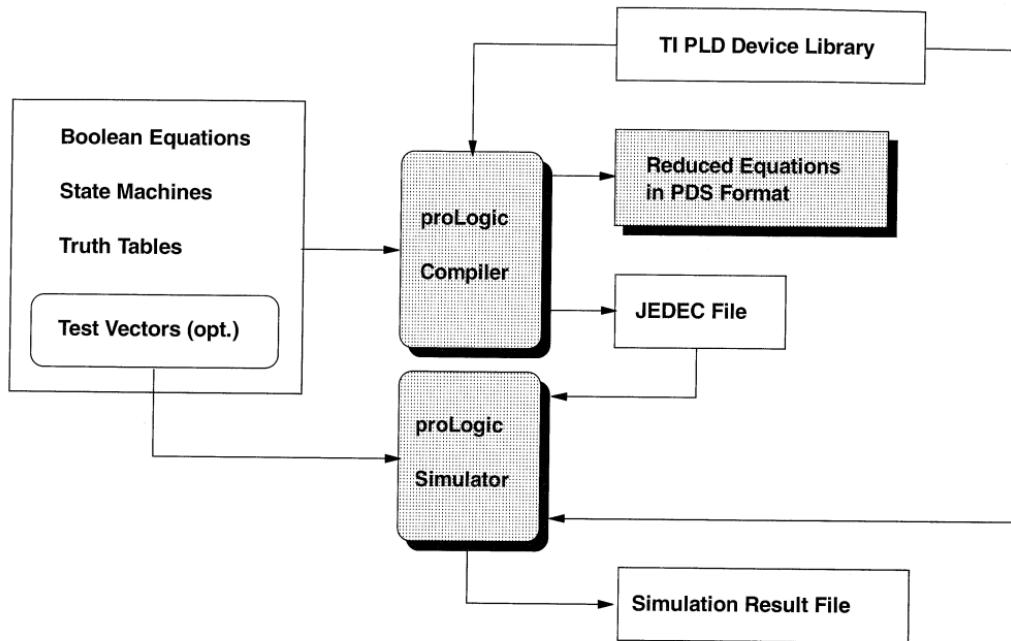


*Easy Logic Integration*



**FPGA**

# TI'x'press - FPGA Synthesis Tool

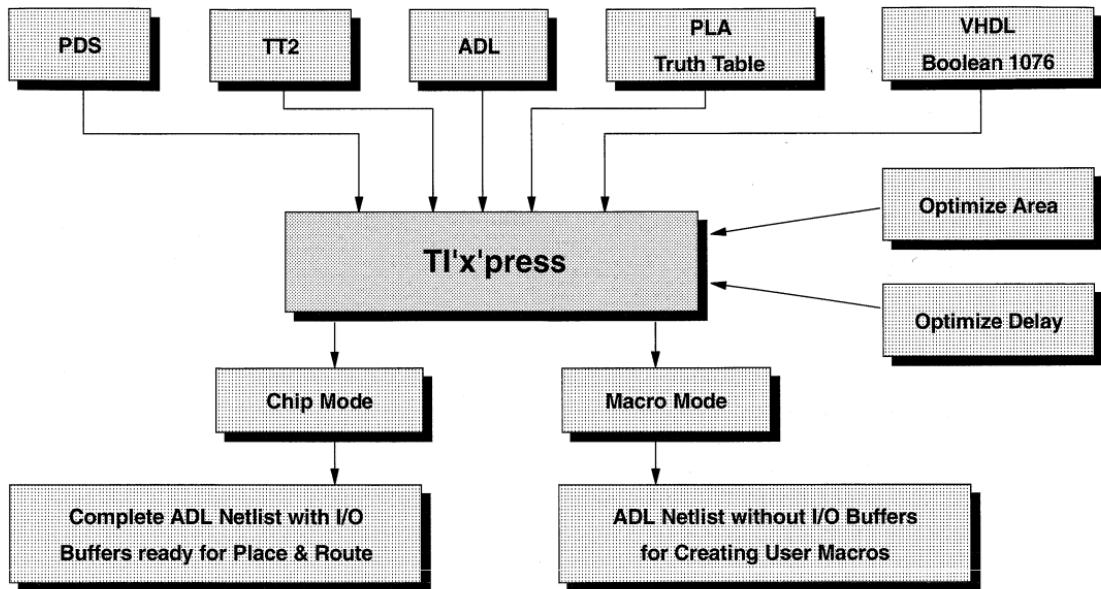

Easy Logic Integration



FPGA


# TI'x'press Features

---

- TI'x'press is a FPGA synthesis tool which can
  - use as inputs logic equations from ABEL, LOG/iC, PALASM, Cuple, PGADesigner, Prologic, or a FPGA netlist in ADL format ,
  - to optimize the logic for speed or area,
  - and map the logic to FPGA hard macros, and generate an ADL netlist.
- TI'x'press supports a subset of VHDL - the Boolean 1076 VHDL.
- TI'x'press allows two compilation modes
  - Chip mode synthesizes the whole design and adds input/output buffers in ADL netlist which can be used directly for Place & Route
  - Macro mode synthesizes portions of a design without input/output buffers which can be used in a CAD schematic capture environment as user soft macros (mixed mode entry.)
- TI'x'press integration language allows the interconnection of design blocks in text file without the need for a schematic editor.



# TI'x'press Synthesis Flow - Macro Mode

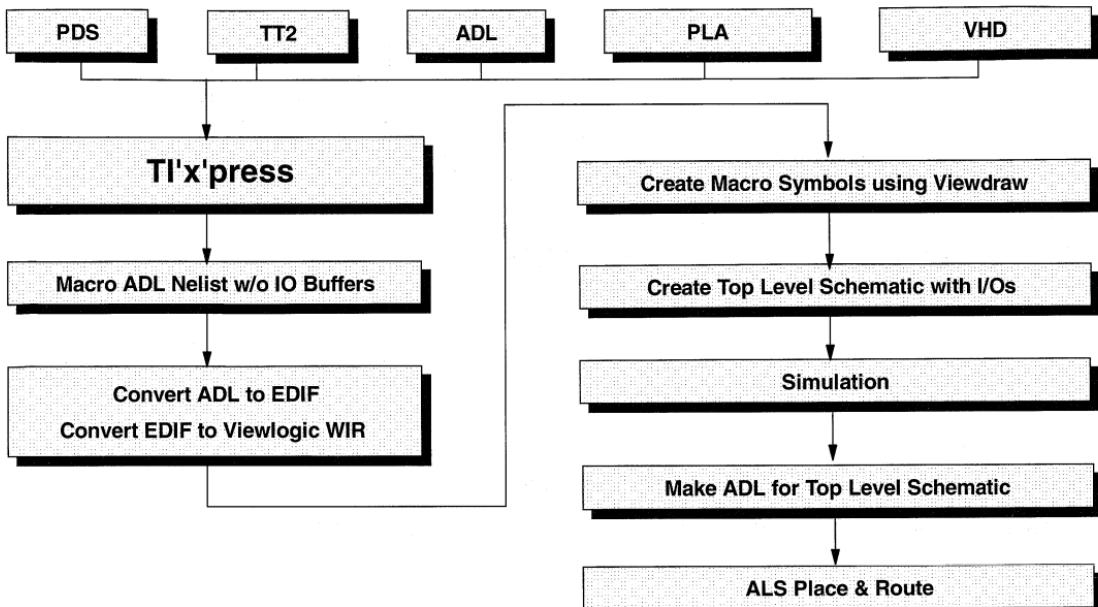


Easy Logic Integration



FPGA


# A Case Study

---

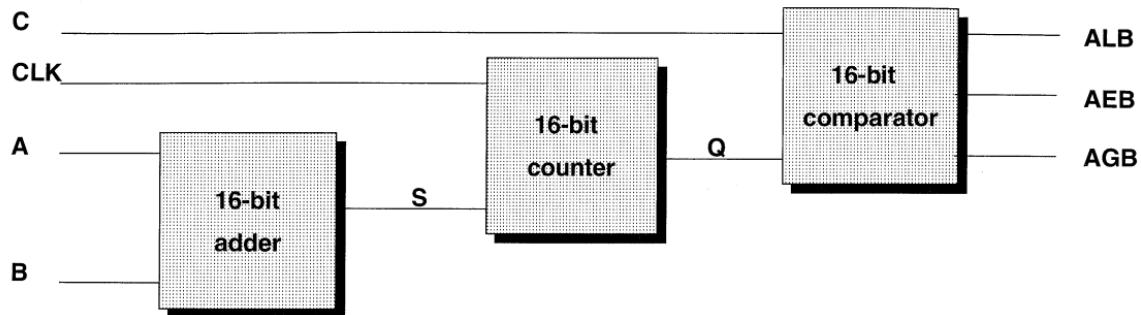

- Two 16-bit numbers A and B are added.
- The sum S is loaded to a preloadable 16-bit counter.
- A 16-bit comparator compares the count Q with a 16-bit number C.
- The outputs are ALB ( $A < B$ ), AEB ( $A = B$ ) and AGB ( $A > B$ ).

# Design Hierarchy

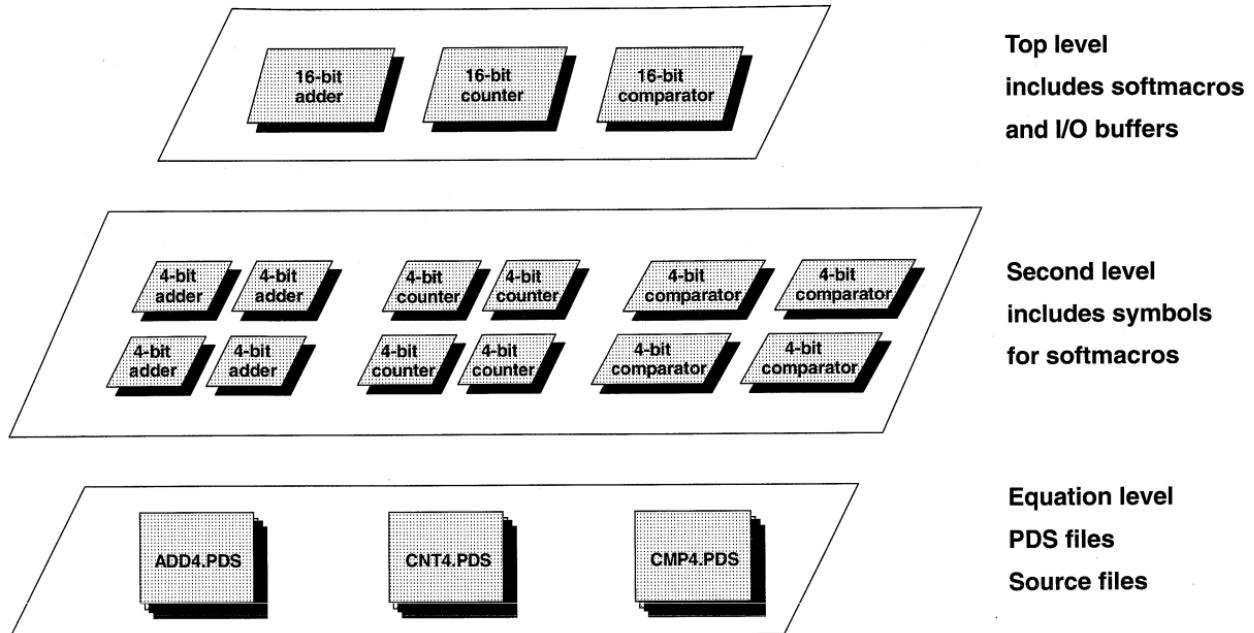

*Easy Logic Integration*



FPGA

# 4-Bit Counter (TA161) Prologic File

---

```
title { Filename: cnt161.pld
Function: 4-bit loadable counter with asynchronous
          clear, equivalent to TA161
Designer: Dung Tu
Date:    27.Dec.92
Note:   22V10 is specified as device to produce a PDS file and
        for simulation. The design is later converted to FPGA
        using ALES.
}
include p22v10;
include XOR.H;
define CLK = pin1;
define CLR = pin2; /* active low CLR */
define LD = pin3; /* active low LD */
define ENP = pin4; /* carry look ahead parallel input */
define ENT = pin5; /* carry look ahead serial input */
/* load inputs */
define P0 = pin6;
define P1 = pin7;
define P2 = pin8;
define P3 = pin9;

/* counter outputs */
define Q0 = pin14;
define Q1 = pin15;
define Q2 = pin16;
define Q3 = pin17;
define RCO = pin22; /* carry-out for cascading */
/* 4-bit counter equations */
Q0.d = !LD & P0 | LD & (Q0.q % (ENT & ENP));
Q1.d = !LD & P1 | LD & (Q1.q % (Q0.q & ENT & ENP));
Q2.d = !LD & P2 | LD & (Q2.q % (Q1.q & Q0.q & ENT & ENP));
Q3.d = !LD & P3 | LD & (Q3.q % (Q2.q & Q1.q & Q0.q & ENT & ENP));
RCO = Q3.q & Q2.q & Q1.q & Q0.q & ENT;
Q0.RSTF = !CLR;
Q1.RSTF = !CLR;
Q2.RSTF = !CLR;
Q3.RSTF = !CLR;
```

# 4-Bit Adder Prologic File

---

```
title { add4pl  4-bit full adder using Prologic syntax
Author: Dung Tu Texas Instruments
Date:  5.May.93'
}

include p22v10;
include xor.h;

define A3 = pin1;
define A2 = pin2;
define A1 = pin3;
define A0 = pin4;

define B3 = pin5;
define B2 = pin6;
define B1 = pin7;
define B0 = pin8;

define CIN = pin9;

define S3 = pin10;
define S2 = pin11;
define S1 = pin13;
define S0 = pin14;

define CO = pin15;

/* equations */
S0 = A0 % B0 % CIN;
S1 = A1 % B1 %
((A0 & B0)
 | (A0 | B0) & CIN);
S2 = A2 % B2 %
((A1 & B1)
 | (A1 | B1) & (A0 & B0)
 | (A1 | B1) & (A0 | B0) & CIN);
S3 = A3 % B3%
((A2 & B2)
 | (A2 | B2) & (A1 & B1)
 | (A2 | B2) & (A1 | B1) & (A0 & B0)
 | (A2 | B2) & (A1 | B1) & (A0 | B0) & CIN);
CO = (A3 & B3)
| (A3 | B3) & (A2 & B2)
| (A3 | B3) & (A2 | B2) & (A1 & B1)
| (A3 | B3) & (A2 | B2) & (A1 | B1) & (A0 & B0)
| (A3 | B3) & (A2 | B2) & (A1 | B1) & (A0 | B0) & CIN;
```



# 4-Bit Comparator Prologic File

---

```
title { Filename: lcmp4l.pld
  Function: 4-bit comparator
  Designer: Dung Tu
  Date: 5.May.93
  Note: 22v10 is specified as device to produce a
        PDS file and for simulation. The design is
        later converted to FPGA using ALES.
}

include p22v10;
include compare.h;

define A0 = pin1;
define A1 = pin2;
define A2 = pin3;
define A3 = pin4;

define B0 = pin9;
define B1 = pin10;
define B2 = pin11;
define B3 = pin13;

define AEBI = pin21;
define AGBI = pin22;
define ALBI = pin23;

define AEB = pin17;
define AGB = pin18;
define ALB = pin19;

define A = (A0, A1, A2, A3);
define B = (B0, B1, B2, B3);

AEB = (A == B) & AEBI;
AGB = (A > B) & AGBI;
ALB = (A < B) & ALBI;
•
```



# 4-Bit Adder - Sum Bit S3

$$\begin{aligned} S3 = & (A3 * /B3 * /B2 * /B1 * /B0 * /CIN \\ & + /A3 * B3 * /B2 * /B1 * /B0 * /CIN \\ & + A3 * /A2 * /B3 * /B1 * /B0 * /CIN \\ & + /A3 * /A2 * B3 * /B1 * /B0 * /CIN \\ & + A3 * /A1 * /B3 * /B2 * /B0 * /CIN \\ & + /A3 * /A1 * B3 * /B2 * /B0 * /CIN \\ & + A3 * /A2 * /A1 * /B3 * /B0 * /CIN \\ & + /A3 * /A2 * /A1 * B3 * /B0 * /CIN \\ & + A3 * /A0 * /B3 * /B2 * /B1 * /CIN \\ & + /A3 * /A0 * B3 * /B2 * /B1 * /CIN \\ & + A3 * /A2 * /A0 * /B3 * /B1 * /CIN \\ & + /A3 * /A2 * /A0 * B3 * /B1 * /CIN \\ & + A3 * /A1 * /A0 * /B3 * /B0 * /CIN \\ & + /A3 * /A1 * /A0 * B3 * /B0 * /CIN \\ & + A3 * /A2 * /A1 * /A0 * /B3 * /B0 * /CIN \\ & + /A3 * /A2 * /A1 * /A0 * B3 * /B0 * /CIN \\ & + A3 * /A1 * /A0 * /B3 * /B2 * /B0 * /CIN \\ & + /A3 * /A1 * /A0 * B3 * /B2 * /B0 * /CIN \\ & + A3 * /A2 * /A1 * /A0 * /B3 * /B2 * /B0 * /CIN \\ & + /A3 * /A2 * /A1 * /A0 * B3 * /B2 * /B0 * /CIN \\ & + A3 * /A1 * /A0 * /B3 * /B2 * B1 * B0 \\ & + /A3 * /A0 * B3 * B2 * B1 * B0 \\ & + A3 * A0 * B3 * B2 * B1 * B0 \\ & + /A3 * /A2 * A0 * /B3 * B1 * B0 \\ & + A3 * A2 * A0 * B3 * B1 * B0 \\ & + /A3 * /A1 * A0 * /B3 * B2 * B0 \\ & + A3 * A1 * A0 * B3 * B2 * B0 \\ & + /A3 * /A2 * /A1 * A0 * /B3 * B0 \\ & + A3 * /A2 * /A1 * A0 * B3 * B0 \\ & + /A3 * /A2 * A1 * A0 * /B3 * B0 \\ & + A3 * /A2 * A1 * A0 * B3 * B0 \\ & + /A3 * /A1 * /B3 * B2 * /B1 \\ & + A3 * /A1 * /B3 * B2 * /B1 \\ & + /A3 * /A2 * /A1 * /B3 * /B1 \\ & + A3 * /A2 * /A1 * B3 * /B1 \\ & + /A3 * /A1 * /B3 * B2 * B1 \\ & + A3 * A1 * B3 * B2 * B1 \\ & + /A3 * /A2 * A1 * /B3 * B1 \\ & + A3 * /A2 * A1 * B3 * B1 \\ & + /A3 * /A1 * /B3 * B2 \\ & + A3 * /A2 * /B3 * B2 \\ & + /A3 * /A2 * /B3 * B2); \end{aligned}$$



# Test Vector Block

---

```
test_vectors{ CLK CLR Q3 Q2 Q1 Q0 ; /* count */  
    C 0 L L L L ; /* clear */  
    C 1 L L L H ; /* 1 */  
    C 1 L L H H L ; /* 2 */  
    C 1 L L H H H ; /* 3 */  
    C 1 L H L L ; /* 4 */  
    C 1 L H L H ; /* 5 */  
    C 1 L H H L ; /* 6 */  
    C 1 L H H H ; /* 7 */  
    C 1 H L L L ; /* 8 */  
    C 1 H L L H ; /* 9 */  
    C 1 H L H L ; /* 10 */  
    C 1 H L H H ; /* 11 */  
    C 1 H H L L L ; /* 12 */  
    C 1 H H L H L ; /* 13 */  
    C 1 H H H L L ; /* 14 */  
    C 1 H H H H H ; /* 15 */  
    C 1 L L L L L ; /* 0 */  
}
```

- Test vectors are used by the proSim simulator to verify that the logic functions defined for the PLD are correct.

- Each test\_vectors block defines a sequence of input and output patterns which are used to test the logic function.

- The first line of the table defines the test variables:  
CLK CLR Q3 Q2 Q1 Q0;

- Each other line is a test vector:

C 0 L L L L;



FPGA

# proLogic Source File With Test Vectors

```
title {   Filename: CNT4L.pld
Function: Simple 4-bit binary counter
Designer: Dung Tu
Date: 1.Sep.92
Note: 22V10 is specified as device to produce a
PDS file and for simulation. The design is
later converted to FPGA using ALES.
}

include p22v10; /* Specify a PLD device type */
include XOR.H; /* To implement the "%" operator as Exclusive OR
*/
/* Input pins */
define CLK = pin1;
define CLR = pin2;

/* Output pins */
define Q0 = pin14;
define Q1 = pin15;
define Q2 = pin16;
define Q3 = pin17;

/* Specify register outputs of the 22V10 as active high
Q0 = q;      Q1 = q;      Q2 = q;      Q3 = q; */

/* The generic format for the n-th bit (Qn) of an n-bit counter is: */
/* Qn = Qn % (Qn-1 & Qn-2 & ... & Q0) */
/* proLogic uses "Q.d" for a flipflop input and "Q.q" for the output */
/* Equations for a 4-bit counter: */

Q0.d = !Q0.q & CLR;
Q1.d = (Q1.q % Q0.q) & CLR;
Q2.d = (Q2.q % (Q1.q & Q0.q)) & CLR;
Q3.d = (Q3.q % (Q2.q & Q1.q & Q0.q)) & CLR;
```

```
/* Test vectors for proLogic functional simulator */

test_vectors { CLK CLR Q3 Q2 Q1 Q0; /* count */
C 0 L L L L ; /* clear */
C 1 L L L H L ; /* 1 */
C 1 L L H L L ; /* 2 */
C 1 L L H H L ; /* 3 */
C 1 L H L L L ; /* 4 */
C 1 L H L H L ; /* 5 */
C 1 L H H L L ; /* 6 */
C 1 L H H H L ; /* 7 */
C 1 H L L L L ; /* 8 */
C 1 H L L H L ; /* 9 */
C 1 H L H L L ; /* 10 */
C 1 H L H H L ; /* 11 */
C 1 H H L L L ; /* 12 */
C 1 H H L H L ; /* 13 */
C 1 H H H L L ; /* 14 */
C 1 H H H H L ; /* 15 */
C 1 L L L L L ; /* 0 */
```



# Test Result File

---

proLogic Simulator  
Texas Instruments V2.0  
Copyright (C) 1991 Prologic Systems  
Architecture Description: \prologic\p22v10.lxa  
JEDEC Fuse Information: cnt4l.jed  
JEDEC Test Vectors: cnt4l.jed

V01 C0NN NNNN NNNN NLLL LNNN NNNN  
V02 C1NN NNNN NNNN NHLL LNNN NNNN  
V03 C1NN NNNN NNNN NLHL LNNN NNNN  
V04 C1NN NNNN NNNN NHHL LNNN NNNN  
V05 C1NN NNNN NNNN NLLH LNNN NNNN  
V06 C1NN NNNN NNNN NHLH LNNN NNNN  
V07 C1NN NNNN NNNN NLHH LNNN NNNN  
V08 C1NN NNNN NNNN NHHH LNNN NNNN  
V09 C1NN NNNN NNNN NLLL HNNN NNNN  
V10 C1NN NNNN NNNN NHLL HNNN NNNN  
V11 C1NN NNNN NNNN NLHL HNNN NNNN  
V12 C1NN NNNN NNNN NHHL HNNN NNNN  
V13 C1NN NNNN NNNN NLLH HNNN NNNN  
V14 C1NN NNNN NNNN NHLH HNNN NNNN  
V15 C1NN NNNN NNNN NLHH HNNN NNNN  
V16 C1NN NNNN NNNN NHHH HNNN NNNN  
V17 C1NN NNNN NNNN NLLL LNNN NNNN

No errors detected with 17 Test Vectors.

---


— *Easy Logic Integration* —



FPGA

---

# State Machine Synthesis With proLogic

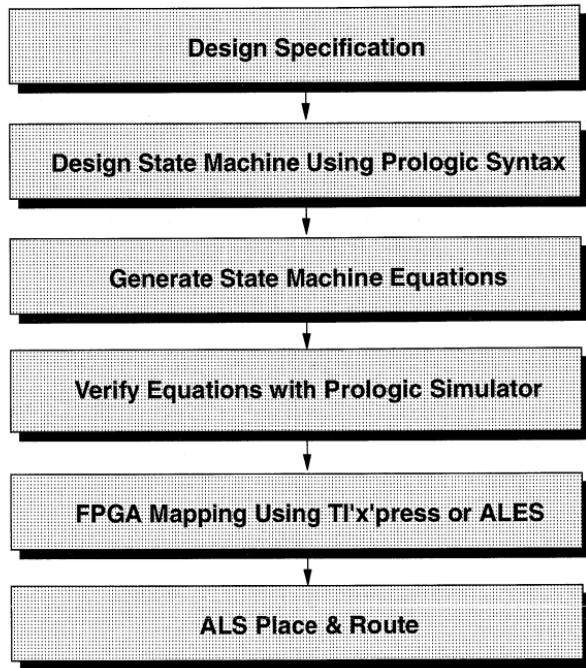


Easy Logic Integration




FPGA

# Bit Sequence Detector

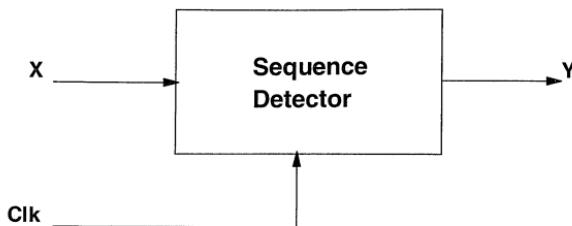


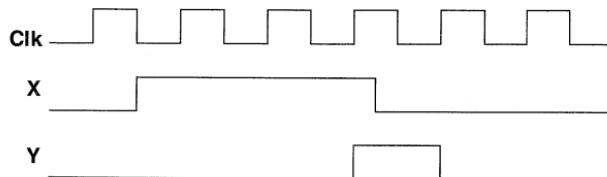A Bit-Sequence Detector monitors an input signal X and outputs a signal Y=1 when a defined sequence of bits has been transmitted through the input of the system.



In this example the output Y becomes High when the input bit sequence is 111.

# State Diagram: Graphical vs Syntax

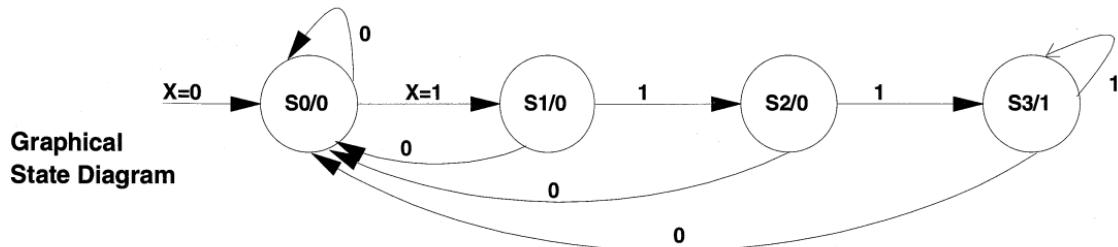

State Diagram in  
proLogic syntax

```
state_diagram Q1, Q0 {
    state s0 = 00 {
        Y = 0;
        if (X)     s1;
        else      s0;
    }
    state s1 = 01 {
        Y = 0;
        if (X)     s2;
        else      s0;
    }
}
state s2 = 10 {
    Y = 0;
    if (X)     s3;
    else      s0;
}
state s3 = 11 {
    Y = 1;
    if (X)     s3;
    else      s0;
}
```

# Moore vs Mealy State Machine


*Moore State Machine*



*Synchronous state machine*

- Outputs depend only on the state.
- Changes in inputs must first change the machine state before they can change the outputs.

*Mealy State Machine*

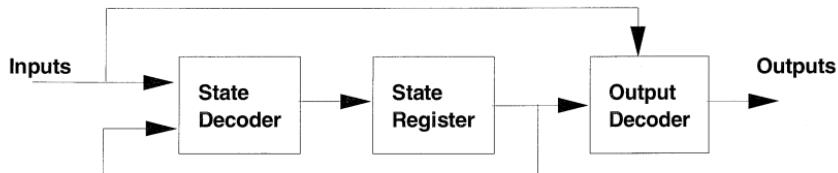

*Asynchronous state machine*

- Outputs depend on the state and the inputs.
- Changes in inputs affect the outputs immediately.



# Moore Sequence Detector

```
title { Filename: mooreseq.pld
Function: Sequence detector as Moore state machine
Designer: Dung Tu
Date: 8.Sep.92
Note: 22V10 is specified as device to produce a
PDS file and for simulation. The design is
later converted to FPGA using ALES.
}
include p22v10;
include dff;

/* Inputs */
define CLK = pin1;
define X = pin2;

/* State variables */
define Q0 = pin14;
define Q1 = pin15;

/* Output */
define Y = pin18;

/* Registers active high */
Q0 = q; Q1 = q;

state_diagram Q1, Q0 {
    state s0 = 00 {
        Y = 0;
        if (X) s1;
        else s0;
    }
    state s1 = 01 {
        Y = 0;
        if (X) s2;
        else s0;
    }
    state s2 = 10 {
        Y = 0;
        if (X) s3;
        else s0;
    }
    state s3 = 11 {
        Y = 1;
        if (X) s3;
        else s0;
    }
}
test_vectors { CLK X Y
;
    C 1 L;
    C 1 L;
    C 0 L;
    C 1 L;
    C 1 L;
    C 1 H;
    C 0 L;
}
```



FPGA

# Mealy Sequence Detector

---

```
title {     Filename:    mealyseq.pld
            Function:   Sequence detector as Mealy state machine
            Designer:  Dung Tu
            Date:      8.Sep.92
            Note:      22V10 is specified as device to produce a
                      PDS file and for simulation. The design is
                      later converted to FPGA using ALES.
}
include p22v10;
include dff;           /* for state machine synthesis */

/* Inputs */
define CLK = pin1;
define X = pin2;

/* State variables */
define Q0 = pin14;
define Q1 = pin15;

/* Output */
define Y = pin18;


/* Registers active high */
Q0 = q;  Q1 = q;
```

```
state_diagram Q1, Q0 {
    state s0 = 00
        if (X) { Y = 0;  s1; }
        else { Y = 0;  s0; }
    state s1 = 01
        if (X) { Y = 0;  s2; }
        else { Y = 0;  s0; }
    state s2 = 10
        if (X) { Y = 1;  s2; }
        else { Y = 0;  s0; }
    state s3 = 11
        s0;
}
test_vectors { CLK  X  Y;
    C  0  L;
    C  1  L;
    C  1  H;
    C  0  L;
    C  1  L;
    C  1  H;
    C  1  H;
    C  0  L;
}
```




# Waveform Mealy vs Moore

---

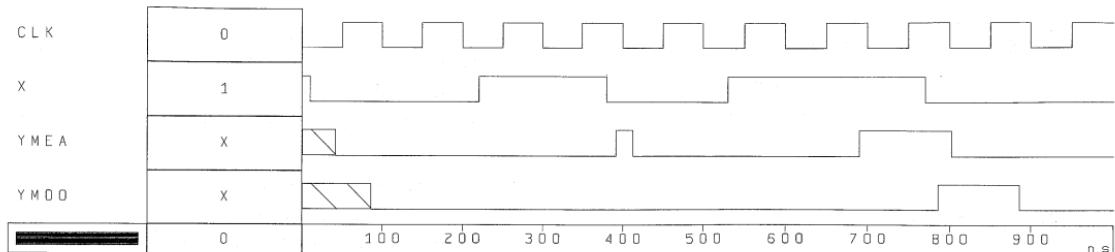


- Compared to the Moore machine, the output waveform of the Mealy machine is shifted to the left by one clock period.
- The falling edge of the output pulse is triggered by the falling edge of the input signal and not by the clock edge.
- To build a synchronous system, the input of a Mealy machine must be synchronized with a flip-flop.
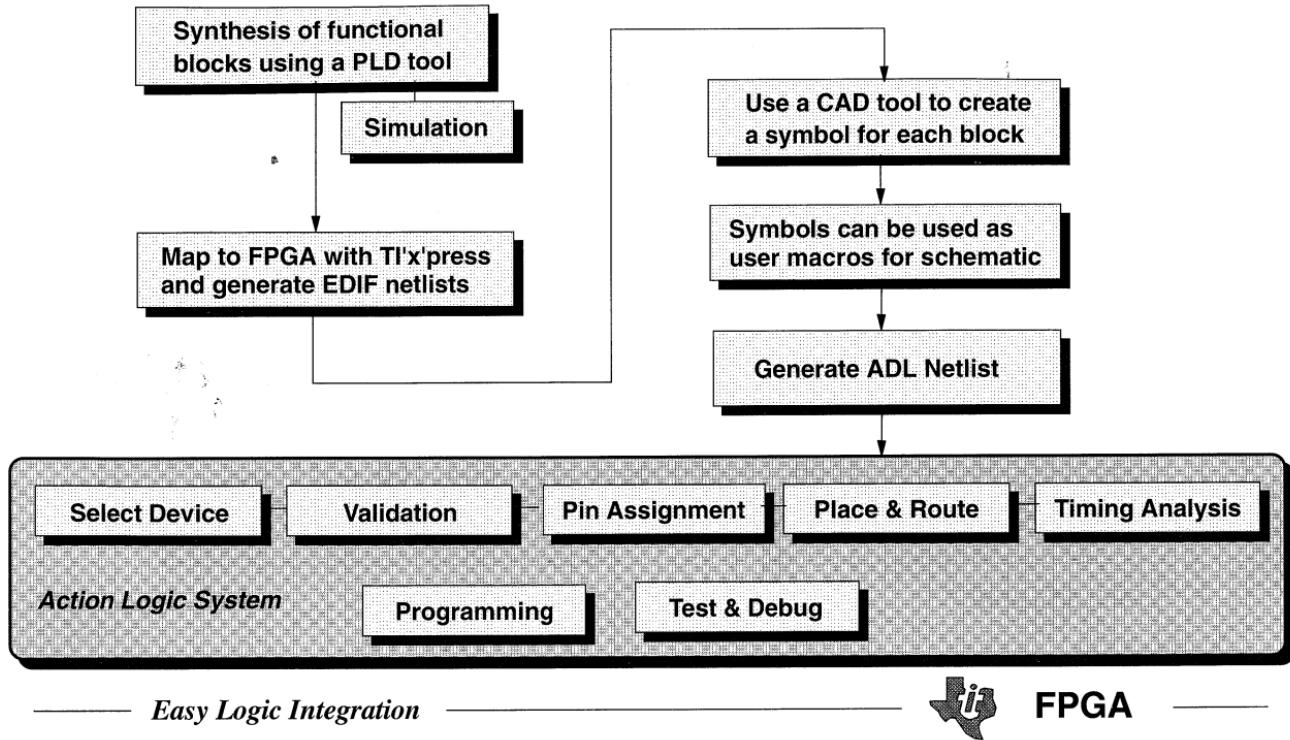
# Equations And Schematic Mixed Mode Entry



# Combine Logic Synthesis With Schematic

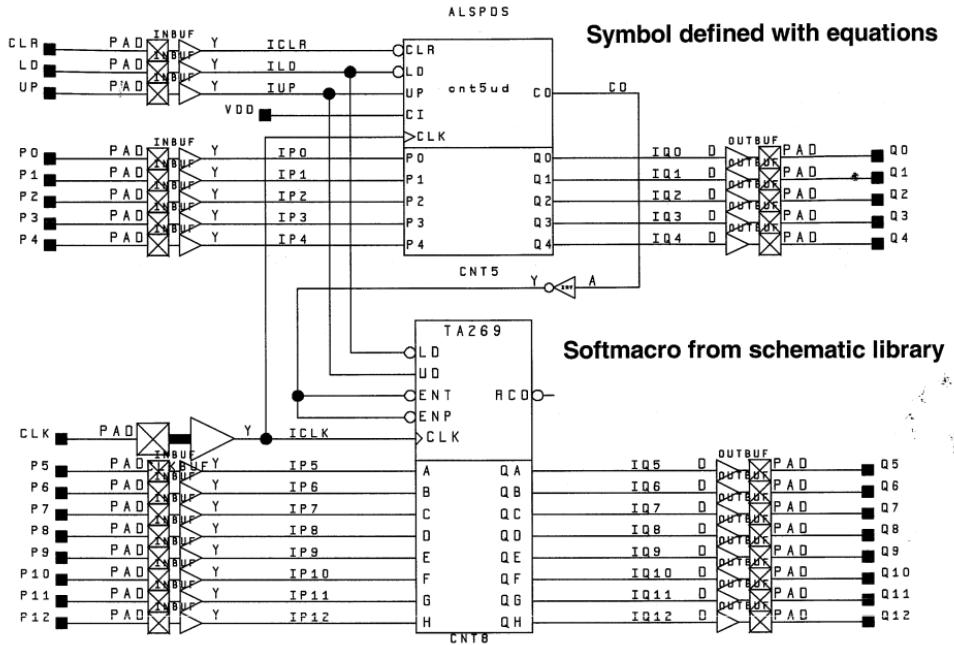

Easy Logic Integration



FPGA

# Summary

---

- **FPGA architecture enables better use of silicon resource compared to GAL's and macrocell-based complex PLD's.**
- **Structure allows implementation of a wider range of functions.**
- **Synthesis enables designers to use familiar PLD design entry techniques to target TI FPGA's.**
- **PLD consolidation saves space, power and cost.**

# Agenda

---

- ***PLD/FPGA Architecture Analysis***
- ***How To Replace TTL With FPGA***
- ***How To Replace PLD With FPGA***
-  ***Applications Benchmarks***
- ***FPGA Design With VHDL***
- ***FPGA Products And Development Systems***

# PREP

---

- PREP (Programmable Electronics Performance Corporation) is a non-profit consortium of 13 vendors of programmable logic hardware and software.
- PREP develops standard benchmarks which allow a fair analysis and comparison of the performance and functional abilities of programmable logic devices.
- The first PREP Benchmark Suite Version 1.2 which was announced on March 29, 1993 in Santa Clara is composed of nine commonly used applications which are neutral to all architectures and vendors.

# PREP Benchmarks

---

## 1. Data Path

Eight 4-to-1 multiplexers drive an 8-bit register. This register drives a parallel load 8-bit shift register.

## 2. Timer / Counter

Two 8-bit words from a common data bus drive a 2-to-1 multiplexer whose output loads an 8-bit binary counter. The counter outputs are compared against an 8-bit register which is loaded from the data bus.

## 3. Small State Machine

A state machine with 8 states, whose outputs are a function of the current state and the 8 input data bits.

## 4. Large State Machine

A state machine with 16 states, 40 transitions and 8 inputs.

## 5. Arithmetic

A 4-by-4 unsigned multiplier drives an 8-bit accumulator. The accumulator has a control input that passes either the multiplier data to the accumulator register or the accumulator's adder data to the register.

## 6. 16-bit accumulator

## 7. 16-bit loadable binary counter


## 8. 16-bit pre-scaled binary counter

## 9. Memory map

The map decodes address spaces ranging in size from 4k down to one. Addresses that do not correspond to any space assert a bus error.

# Benchmark #1 : Data Path

---

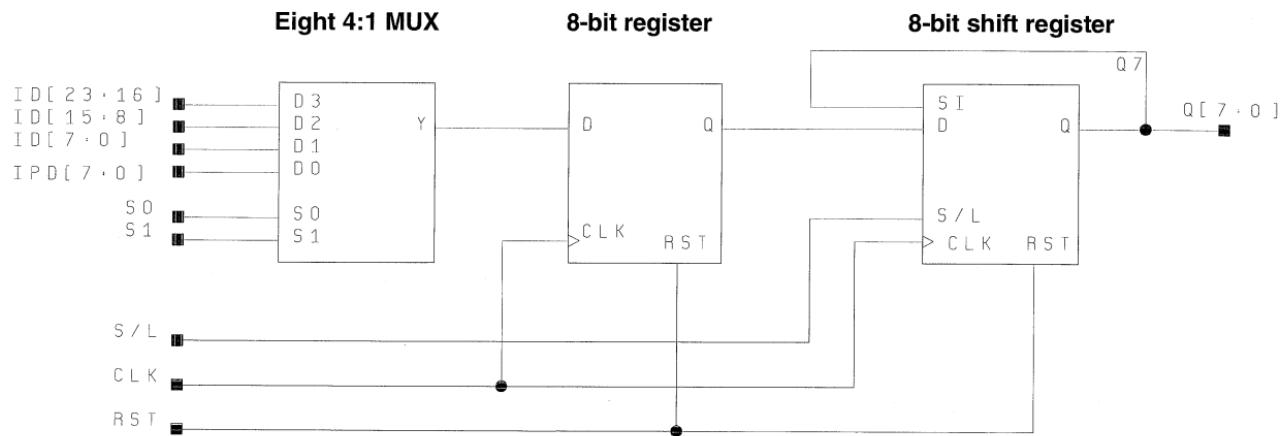


# Data Path - Capacity / Performance

---

Device	Number of circuits	Worst-case speed (MHz)	Optimized for capacity	Optimized for speed
TPC1280-1	48	29	X	
TPC1280-1	39	55		X
TPC1240	21	66		X
TPC1240A-2	27	49	X	
TPC1240	27	37	X	
TPC1240A-2	21	95		X
TPC1225-1	18	44	X	
TPC1225-1	14	85		X

# Benchmark #2 : Timer / Counter

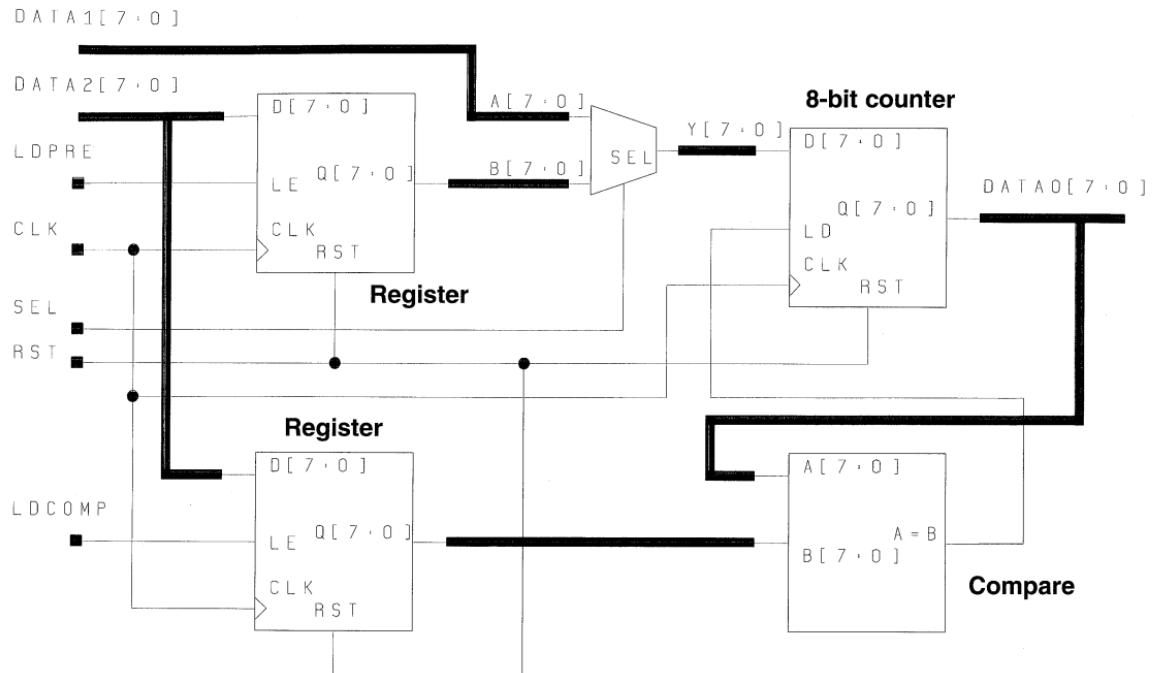

Easy Logic Integration



FPGA

# Timer / Counter : Capacity / Performance

---

Device	Number of circuits	Worst-case speed [MHz]
TPC1225-1	9	28
TPC1240A-2	14	35
TPC1240	14	26
TPC1280-1	20	19

# Benchmark #3 : Small State Machine

---

Current State	Next State	IN[7:0] hex	OUT[7:0] hex
START	SA	3C	82
START	START	/3C	00
SA	SC	2A	40
SA	SB	1F	20
SA	SA	/1F * /2A	04
SB	SE	AA	11
SB	SF	/AA	30
SC	SD	XX	08
SD	SG	XX	80
SE	START	XX	40
SF	SG	XX	02
SG	START	XX	01

# Small State Machine : Capacity / Performance

---

Device	Number of circuits	Worst-case speed [MHz]
TPC1225-1	15	32
TPC1240	23	28
TPC1240A-2	23	37
TPC1280-1	42	26

# Benchmark #4 : Large State Machine

---


- 16 states
- 40 transitions
- 10 inputs
- 8 outputs

Device	Number of circuits	Worst-case speed [MHz]
TPC1225-1	6	21
TPC1240	10	17
TPC1240A-2	10	22
TPC1280-1	18	16



FPGA

# Benchmark #5 : Arithmetic Circuit

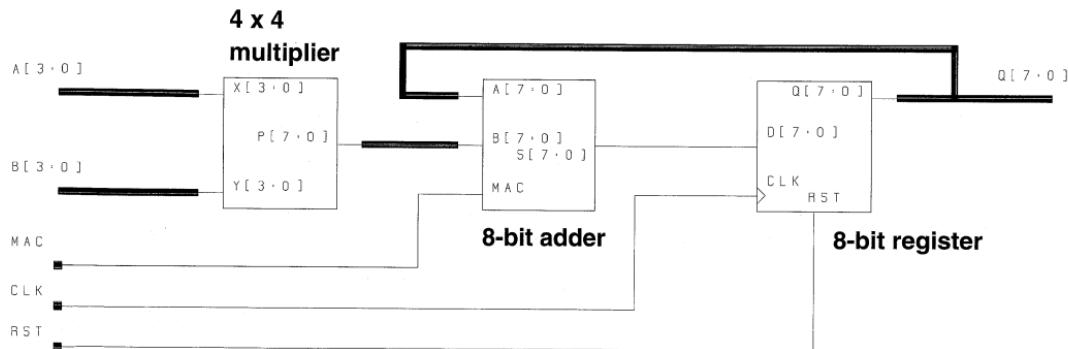


Device	Number of circuits	Worst case speed [MHz]
TPC1225-1	6	13
TPC1240A-2	9	14
TPC1240	9	11
TPC1280-1	16	11

Easy Logic Integration



FPGA

# Benchmark #6 : 16-Bit Accumulator

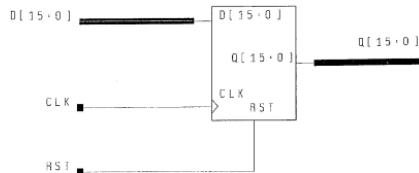


Device	Number of circuits	Worst-case speed [MHz]	Optimized for capacity	Optimized for speed
TPC1225-1	5	23	X	
TPC1240	8	21	X	
TPC1240A-2	8	27	X	
TPC1280-1	15	18	X	
TPC1225-1	4	32		X
TPC1240	7	24		X
TPC1240A-2	7	32		X
TPC1280-1	13	21		X



FPGA


# Benchmark #7 : 16-Bit Up-Counter

---

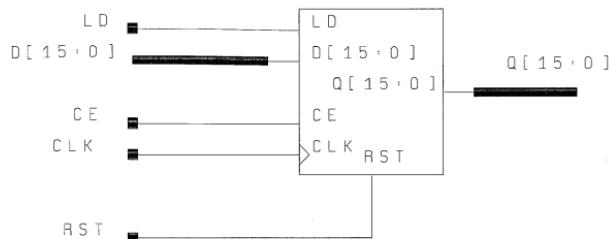


Device	Number of circuits	Worst-case speed [MHz]
TPC1225-1	9	46
TPC1240	13	39
TPC1240A-2	13	52
TPC1280-1	25	33
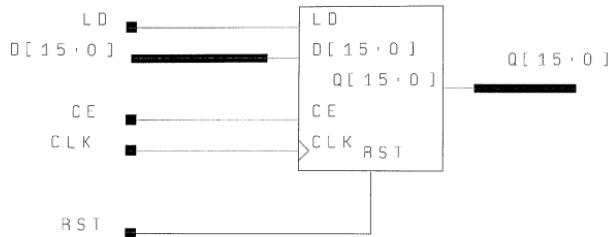
# Benchmark #8 : 16-Bit Prescaled Counter



Device	Number of circuits	Worst-case speed [MHz]
TPC1225-1	6	85
TPC1240	10	66
TPC1240A-2	10	95
TPC1280-1	18	75


# Benchmark #9 : Memory Map

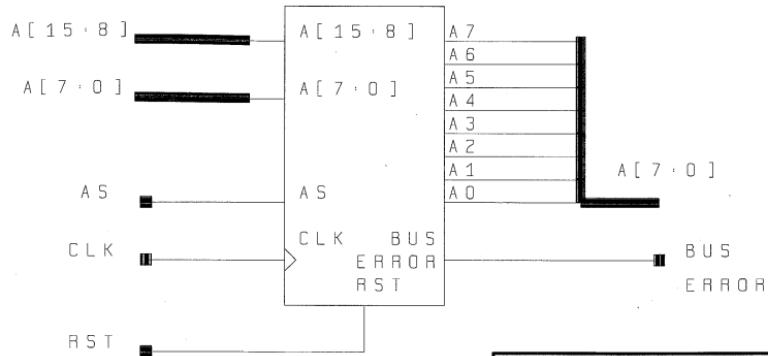

Device	Number of circuits	Worst-case speed [MHz]
TPC1225-1	20	33
TPC1240	31	37
TPC1240A-2	31	37
TPC1280-1	56	26

# FPGA Performance vs Cost

Average performance [MHz]

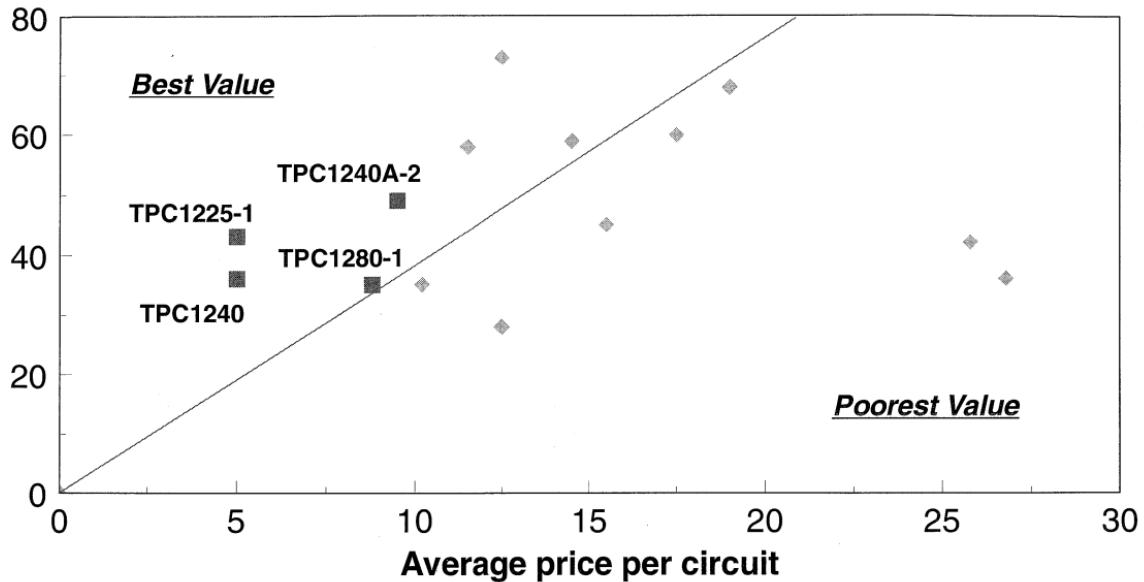

Easy Logic Integration



FPGA

# Summary

---

- PREP Benchmarks are useful for understanding and comparing the performance and functional abilities of programmable logic products.
- The best product for a user is the product which fits the application in terms of performance, density, power consumption and cost.
- Antifuse based FPGAs from Texas Instruments are production proven and offer an excellent cost / performance benefit for many applications.




# Agenda

---

- ***PLD/FPGA Architecture Analysis***
- ***How To Replace TTL With FPGA***
- ***How To Replace PLD With FPGA***
- ***Applications Benchmarks***
-  ***FPGA Design With VHDL***
- ***FPGA Products And Development Systems***

# Success Factors

---

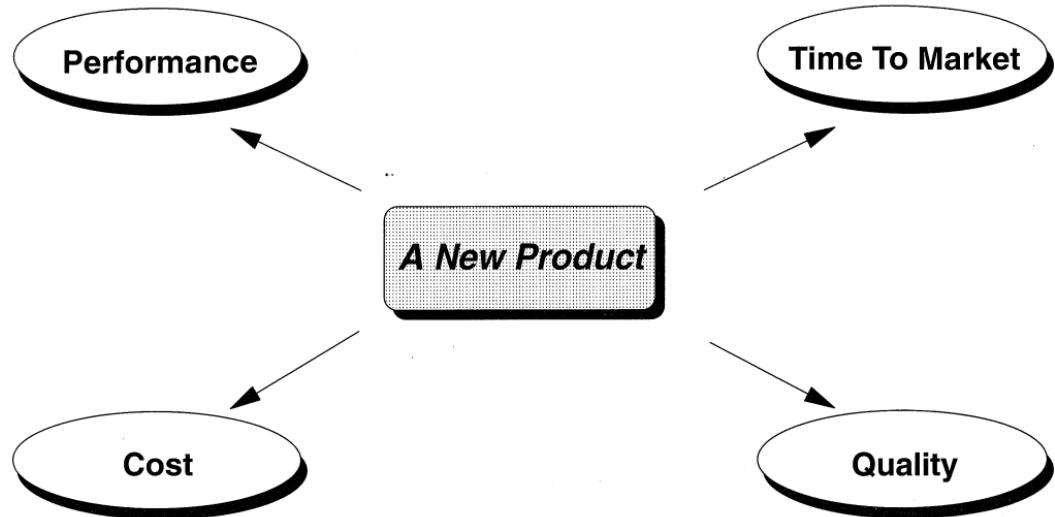

---

— *Easy Logic Integration* —



**FPGA**

---

# The Designer's Pressures

---

- Decreasing product life cycle.
- Increasing time-to-market pressure .
- Increasing design complexity and performance.
- Increasing product differentiation pressure.
- Increasing cost pressure.
- Increasing quality / reliability pressure.
- Increasing global competition.



# Design Methodology Trends

---

- Trend to high complexity application specific products.
- Trend to high level design languages to master the complexity and reduce the development time.
- Trend to technology independent design methodology to use the best appropriate silicon for each phase of the product.
- Trend to automatic test synthesis to reduce the development time and improve the quality.
- Trend to board and system level simulation.


---

*Easy Logic Integration*



FPGA

# Why Technology Independent?

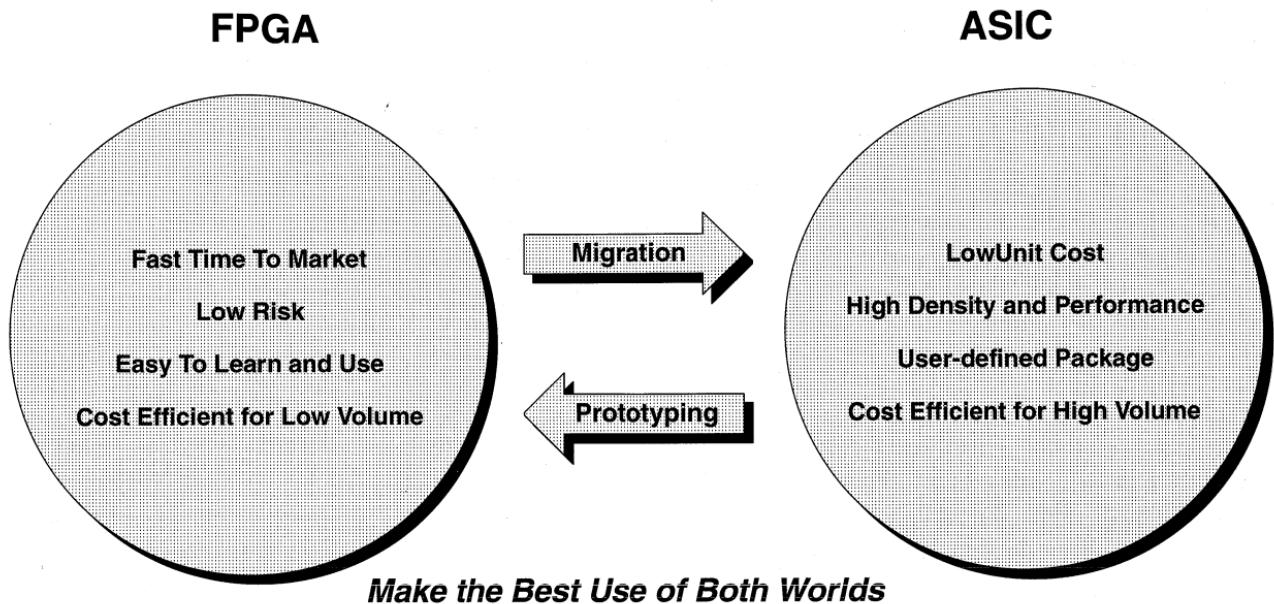


— *Easy Logic Integration* —




FPGA

# Migration Options

## *Low Level Netlist Migration*

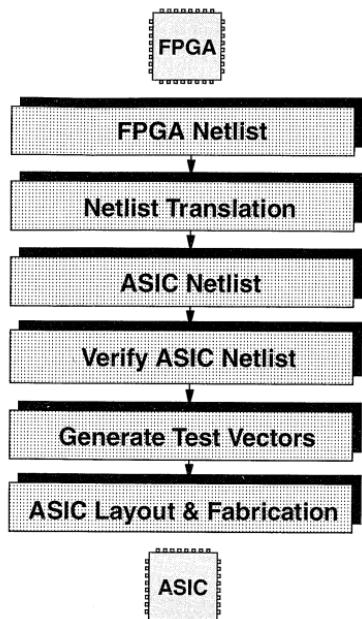

## *High Level Design Migration*

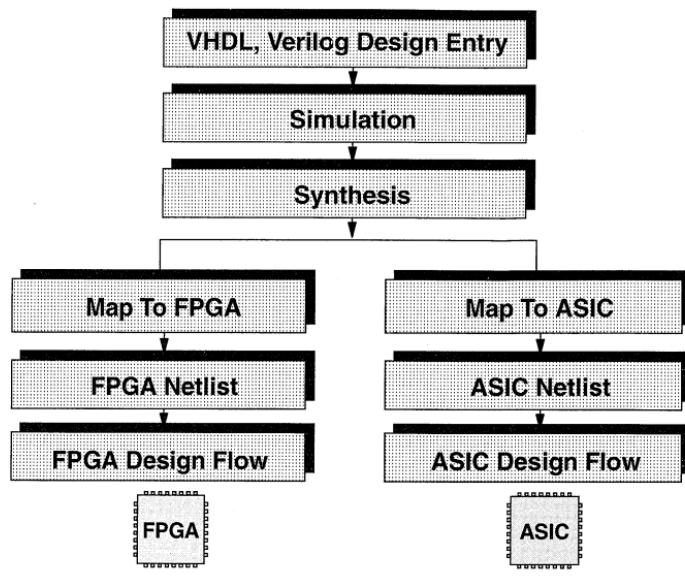


*Easy Logic Integration*



**FPGA**

# Low Level Netlist Migration

## *Low Level Netlist Migration*

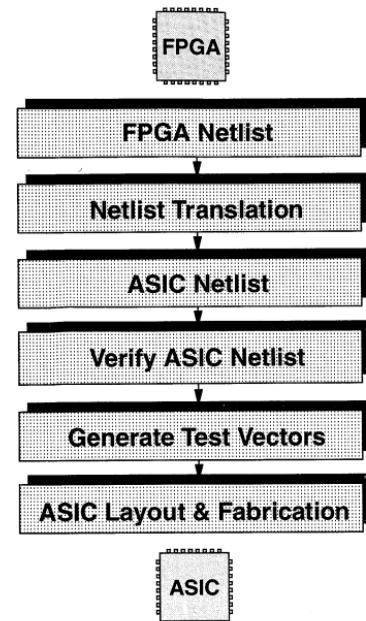

### **Advantages:**

- Straight forward FPGA implementation (without bothering about the ASIC)
- Low cost FPGA tool
- Familiar schematic entry approach

### **Disadvantages:**

- Could cause timing problem with the ASIC (asynchronous signals)
- Potential testability problem with the ASIC

# Designing for Migration

---

- Rule for automatic scan chain insertion:
  - Design should be synchronous as possible
  - Clock should not be divided or gated with other signals
  - All asynchronous preset and clear signals should be controllable from external pins
  - All register or latches should be sensitive to the same clock edge
- TI Migration Checklist:
  - Address testability issues to ensure high fault coverage



**Always keep ASIC testability issues in mind**


# What is VHDL?

---

- Very High Speed IC (VHSIC) Hardware Description Language.
- A design language, a simulation language, a documentation language.
- Supports all levels of abstraction: behavioural, RTL, gate, switch.
- Initiated 1985 by Intermetrics, IBM and Texas Instruments.
- Standardized 1987 by IEEE-1076 and revised 1992.
- Widely supported by EDA vendors and ASIC suppliers.
- Strongly typed language with a wide set of constructs.

# High Level Migration

## *High Level Design Migration*

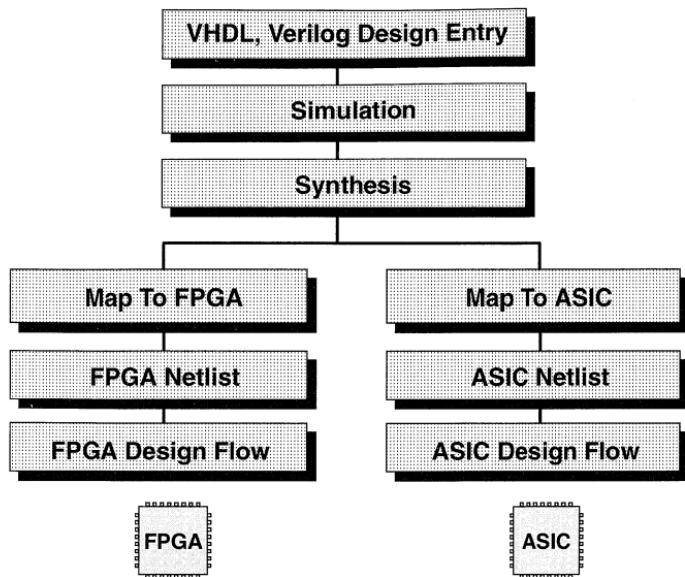

### **Advantages:**

- When learned - increased design productivity
- Fast design modification
- Synthesis tool optimizes utilization of silicon resources
- Automatic test pattern generation with test synthesis tool

### **Disadvantages:**

- Expensive synthesis tools
- High level design is new to designers


*Easy Logic Integration*



**FPGA**

# Why Automatic Test Synthesis?

---

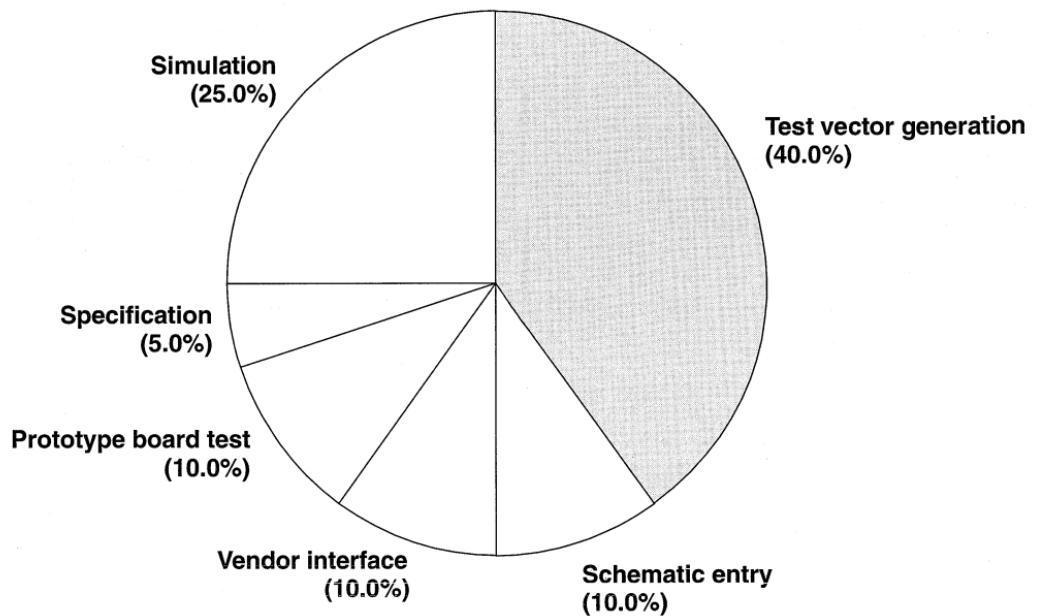

Source: Dataweek

---

*Easy Logic Integration*

---




FPGA


---

# Scan Cell - Scan Path

Synchronous Model

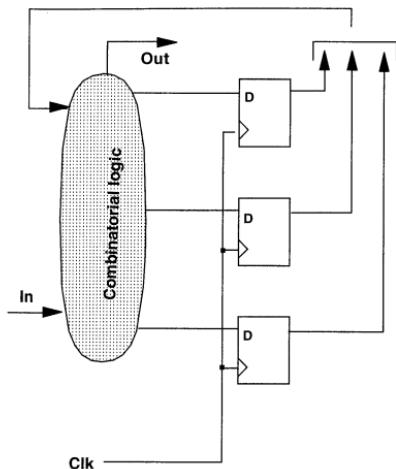

With Scan Path

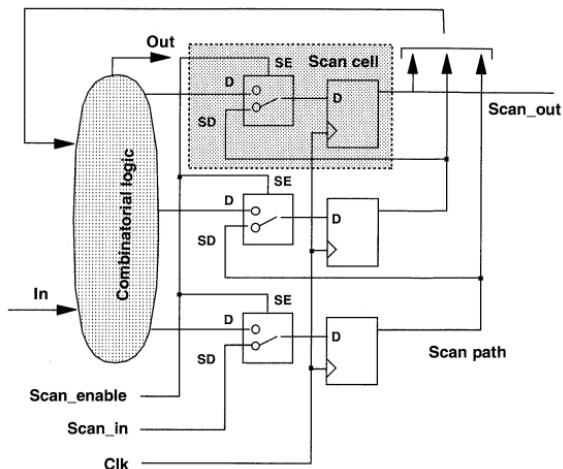

Scan\_enable=H -> Test mode


Scan\_enable=L -> Normal mode

Easy Logic Integration



FPGA

# Circuit Without Test Scan

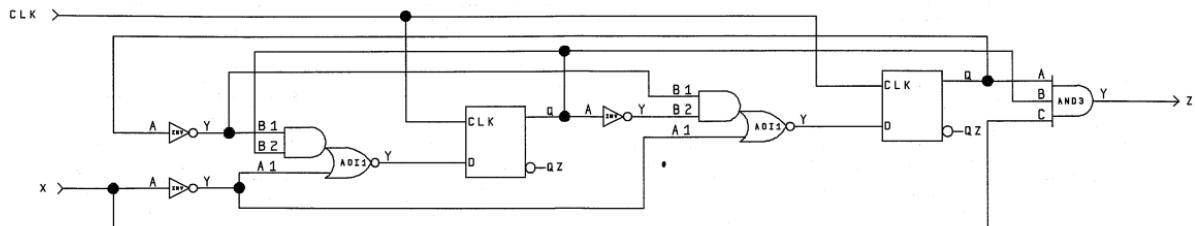


design: MEASEQ	designer: Dung Tu	date: 9/18/91
technology: TGC100.db	company: Texas Instruments	sheet: 1 of 1

Easy Logic Integration



FPGA

# TGC100 Schematic With Test Scan

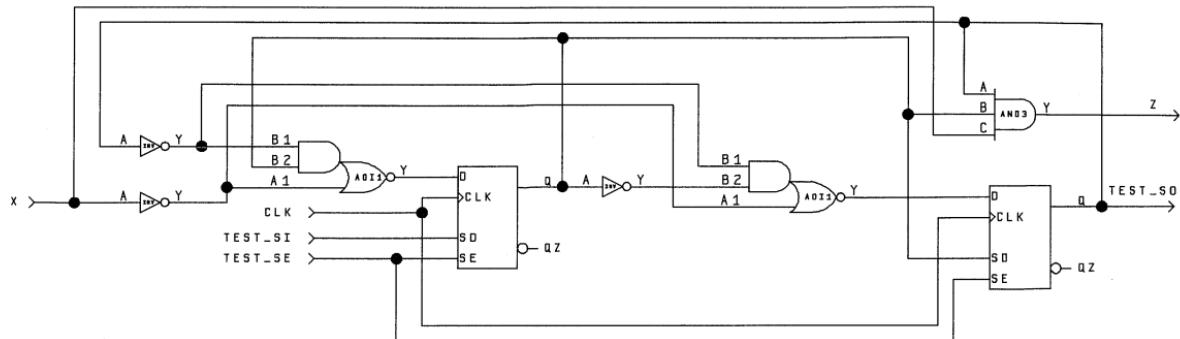

design: MEASEQ	designer: Dung Tu	date: 9/18/91
technology: TGC100.db	company: Texas Instruments	sheet: 1 of 1

— Easy Logic Integration —



FPGA

# ATPG Test Patterns

## SIGNAL DEFINITION

### 1. Signal Names:

```
test_se      # scan_mode_control port
CLK          # system clock ; active rising-edge
test_si      # scan_in port
test_so      # scan_out port
X            # primary input
Z            # primary output
```

### 2. Signal Sets:

Set 1: SS1

```
test_se      1 I # scan_mode_control port
CLK          2 I # system clock ; active rising-edge
test_si      3 I # scan_in port
test_so      4 O # scan_out port
X            5 I # primary input
Z            6 O # primary output
```

Set 2: SS2

```
CLK          1 I # system clock ; active rising-edge
test_si      2 I # scan_in port
```

Set 3: SS3

```
CLK          1 I # system clock ; active rising-edge
test_so      2 O # scan_out port
```

Set 4: SS4

```
CLK          1 I # system clock ; active rising-edge
test_si      2 I # scan_in port
test_so      3 O # scan_out port
```

## TEST VECTORS

0.0 U D U X U X SS1	10900.0 D D U X U X SS1
500.0 U U U X U X SS1	11000.0 D D U X U L SS1
1000.0 D D SS2	11100.0 D U U X U X SS1
1500.0 U D SS2	11600.0 U D U L U X SS1
2000.0 U D N H U X SS1	12100.0 U U U X U X SS1
2500.0 U U N X U X SS1	12600.0 D U H SS4
3000.0 D L SS3	13100.0 U U X SS4

3500.0 U D U X U X SS1	13600.0 D D U X D X SS1
4000.0 U U U X U X SS1	13700.0 D D U X D L SS1
4500.0 D U SS2	13800.0 D U U X D X SS1
5000.0 U U SS2	14300.0 U D D L D X SS1
5500.0 D D U X U X SS1	14800.0 U U D X D X SS1
5600.0 D D U X U H SS1	15300.0 D U L SS4
5700.0 D U U X U X SS1	15800.0 U U X SS4
6200.0 U D U H U X SS1	
6700.0 U U U X U X SS1	
7200.0 D D H SS4	
7700.0 U D X SS4	

8200.0 D D D X U X SS1	16300.0 D D U X U X SS1
8300.0 D D D X U L SS1	16400.0 D D U X U L SS1
8400.0 D U D X U X SS1	16500.0 D U U X U X SS1
8900.0 U D D H U X SS1	17000.0 U D N H U X SS1
9400.0 U U D X U X SS1	17500.0 U U N X U X SS1
9900.0 D D H SS4	18000.0 D L SS3


8400.0 D U D X U X SS1
8900.0 U D D H U X SS1
9400.0 U U D X U X SS1
9900.0 D D H SS4
10400.0 U D X SS4



FPGA

# A Case Study

---

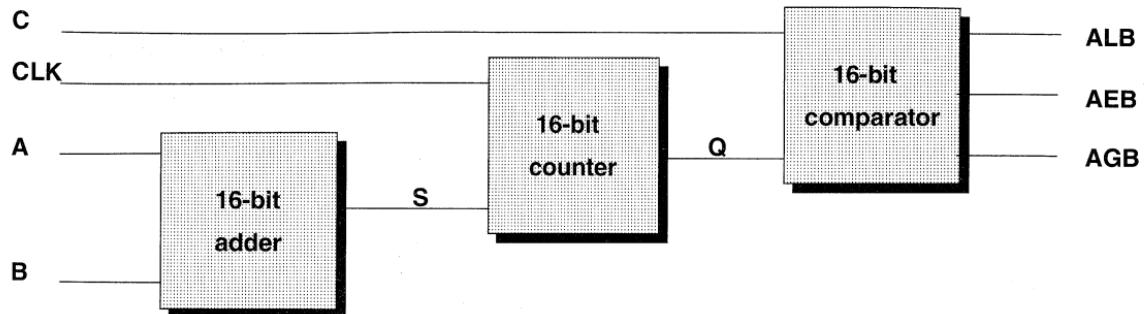

- Two 16-bit numbers A and B are added.
- The sum S is loaded to a preloadable 16-bit counter.
- A 16-bit comparator compares the count Q with a 16-bit number C.
- The outputs are ALB ( $A < B$ ), AEB ( $A = B$ ) and AGB ( $A > B$ ).

# 16-Bit Comparator VHDL Code

```
entity CMP is
    port( A, B           : in INTEGER range 0 to 255;
          ALBI, AEBI, AGBI : in BOOLEAN;
          ALB, AEB, AGB    : out BOOLEAN
        );
end CMP;

architecture BEHAVIOR of CMP is
begin
    ALB <= ALBI and (A < B);
    AEB <= AEBI and (A = B);
    AGB <= AGBI and (A > B);
end BEHAVIOR;
```

**entity**  
*defined the interface between  
a design and its environment*

**architecture**  
*describes the operation of a design  
defines the relationship between  
inputs and outputs*

# 16-Bit Counter VHDL Code

---

```
entity COUNT is
  port( Q      : buffer INTEGER range 0 to 65535;
        P      : in  INTEGER range 0 to 65535;
        RCO   : out BIT;
        CLK   : in  BIT;
        CLR   : in  BIT;
        CI    : in  BIT;
        LD    : in  BIT );
end COUNT;
```

```
architecture BEHAVIOR of COUNT is
begin
  process ( CLK, CLR, LD, CI, P, Q )
  begin
    if Q = 65535 then
      RCO <= '1';
    else
      RCO <= '0';
    end if;
    if CLR = '0' then
      Q <= 0;
    elsif (CLK'event and CLK = '1') then
      if LD = '0' then
        Q <= P;
      elsif CI = '1' then
        if Q = 65535 then
          Q <= 0;
        else
          Q <= Q + 1;
        end if;
      end if;
    end if;
  end process;
end;
```

# 16-Bit Adder VHDL Code

---

```
entity ADD is
    port( A, B : in INTEGER range 0 to 65535;
          S      : buffer INTEGER range 0 to 65535;
          CO     : out BIT);
end ADD;

architecture BEHAVIOR of ADD is
begin
    process (A, B, S)
    begin
        S <= A + B;
        if (S >= 65535) then
            CO <= '1';
        else
            CO <= '0';
        end if;
    end process;
end BEHAVIOR;
```



# VHDL Design Integration

---

```
use work.SYNOPSYS.all;
use work.ATTRIBUTES.all;
entity DEMO is
port( CLK, CLR, LD : in BIT;
      A, B, C : in INTEGER range 0 to 65535;
      ALB, AEB, AGB : out BOOLEAN;
      RCO, CO : out BIT);
end DEMO;
architecture STRUCTURAL of DEMO is
component ADD
port( A, B : in INTEGER range 0 to 65535;
      S : buffer INTEGER range 0 to 65535;
      CO : out BIT);
end component;
component CMP
port( A, B : in INTEGER range 0 to 65535;
      ALBI, AEBI, AGBI : in BOOLEAN;
      ALB, AEB, AGB : out BOOLEAN );
end component;
component COUNT
port( Q : buffer INTEGER range 0 to 65535;
      P : in INTEGER range 0 to 65535;
      CLK, CLR, CI, LD : in BIT;
      RCO : out BIT);
end component;
signal SI : INTEGER range 0 to 65535;
signal QI : INTEGER range 0 to 65535;
signal VDDTIE : BIT;
signal VDDTIEBOOL : BOOLEAN ;
signal N1, N2 : BIT;
signal N3, N4, N5 : BOOLEAN;
begin
  VDDTIE <='1';
  VDDTIEBOOL <= TRUE;
  ADD16 : ADD port map (A, B, SI, N1);
  CNT16 : COUNT port map (QI, SI, CLK, CLR, VDDTIE, LD, N2);
  CMP16 : CMP port map (QI, C, VDDTIEBOOL, VDDTIEBOOL, VDDTIEBOOL, N3,
N4, N5);
  CO <= N1;
  RCO <= N2;
  ALB <= N3;
  AEB <= N4;
  AGB <= N5;
end STRUCTURAL;
```

---

*Easy Logic Integration*

---



FPGA

---

# Recommended Reference Books

---

**VHDL : Douglas Perry**  
**McGraw Hill : \$39.95**

**VHDL : Hardware Description and Design : Roger Lipsett, Carl Schaefer & Carl Ussary**  
**Kluwer Academic Publishers : \$59.95**

**Chip-Level Modelling with VHDL : James Armstrong**  
**Prentice Hall : \$39.00**

**Hardware Design and Simulation : Larry Augustin, David Luckham and Benoit Gennart**  
**Kluwer Academic Publishers : \$69.95**

**The VHDL Handbook : David Coelho**  
**Kluwer Academic Publishers : \$70.00**

**IEEE Standard VHDL Language Reference Manual**



# Summary

---

- VHDL is becoming a useful tool for hardware design and simulation.
- VHDL synthesis tools for FPGAs are now available for PC as well as workstations.
- Designing with high level language enables a seamless migration from one technology to another.
- High level languages increase productivity and design quality.
- TI is one major supplier for both FPGAs and ASICs.

# Agenda

---

- ***PLD/FPGA Architecture Analysis***
- ***How To Replace TTL With FPGA***
- ***How To Replace PLD With FPGA***
- ***Applications Benchmarks***
- ***FPGA Design With VHDL***
- ***FPGA Products And Development Systems***



# TPC10 Devices

---

Device	TPC1010A	TPC1020A	TPC1010B	TPC1020B
Gate array equivalent gates	1200	2000	1200	2000
TTL equivalent packages	34	53	34	53
CMOS Process	1.2um	1.2um	1.0um	1.0um
Logic Modules	295	547	295	547
Flip-Flops (maximum)	130	273	130	273
Antifuse	112k	186k	112k	186k
User I/Os (maximum)	57	69	57	69
Speed grade -1 : 15 %faster -2 : 25% faster	-1	-1	-1 -2	-1 -2
Packages	44 PLCC 68 PLCC 100 PQFP	44 PLCC 68 PLCC 84 PLCC 100 PQFP	44 PLCC 68 PLCC 100 PQFP	44 PLCC 68 PLCC 84 PLCC 100 PQFP

---

Easy Logic Integration



FPGA

---

# TPC12 Devices

Device	TPC1225A	TPC1240	TPC1240A	TPC1280	TPC1280A
Gate array equivalent gates	2500	4000	4000	8000	8000
TTL equivalent packages	70	105	105	210	210
CMOS Process	1.0um	1.2um	1.0um	1.2um	1.0um
Logic Modules	451	684	684	1232	1232
Flip-Flops (maximum)	382	565	565	998	998
Antifuse	250k	400k	400K	750k	750k
Signal I/Os (maximum)	82	104	104	140	140
Speed grade -1 : 15% faster -2 : 25% faster	-1	-1	-1 -2	-1	-1 -2
Packages	84 PLCC 100 PQFP	132 CPGA 144 PQFP	84 PLCC 132 CPGA 144 PQFP	176 CPGA 160 PQFP	176 CPGA 160 PQFP


— Easy Logic Integration —



FPGA

# TPC Product Nomenclature


## *Commercial and Industrial*

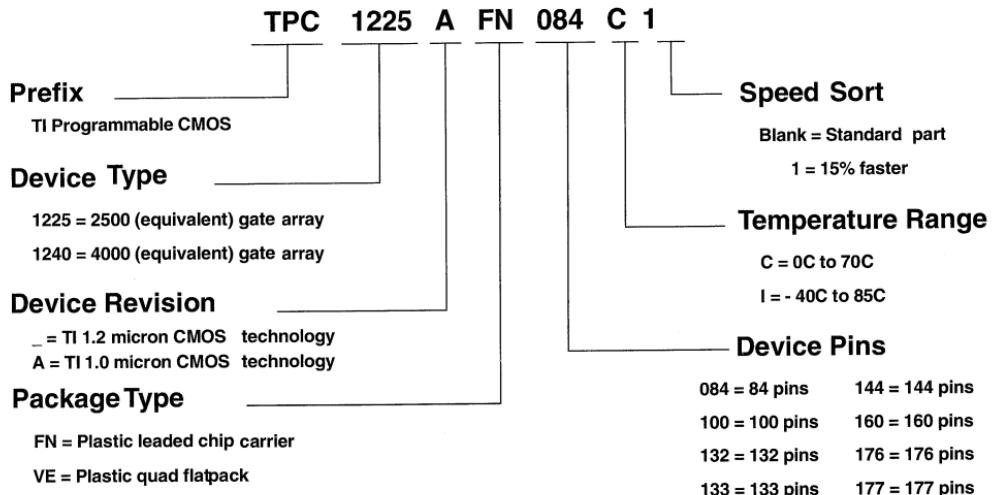

**FPGA**

*Easy Logic Integration*

# FPGA Design Flows

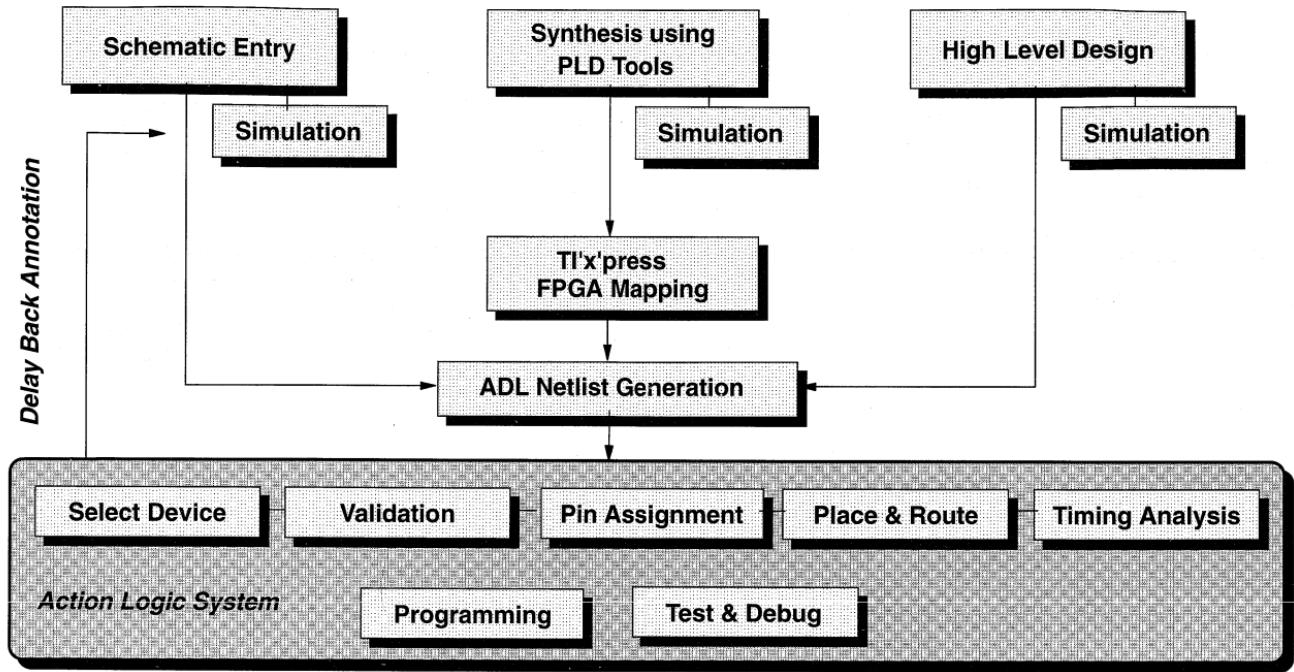


*Easy Logic Integration*



FPGA

# Action Logic System

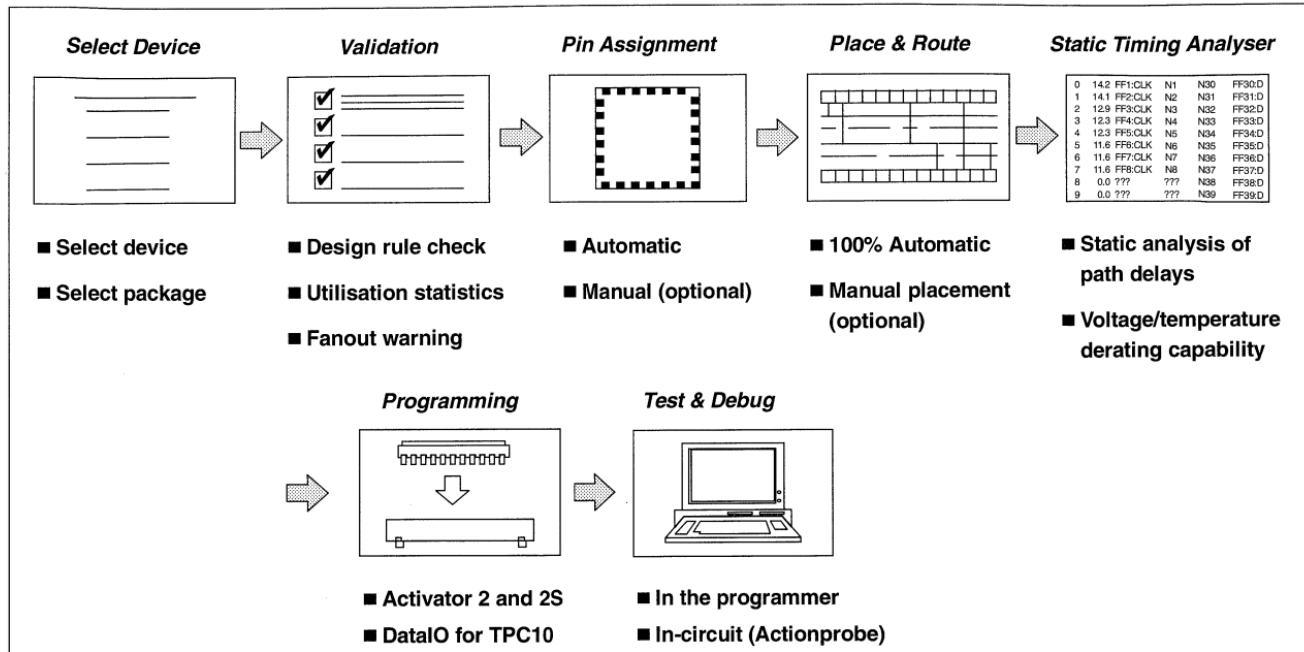

— Easy Logic Integration —



FPGA

# TI-ALS System Options

---

**TPC- ALS-DS Series : for devices up to 2500 gates**

**TPC-ALS-DA Series : for devices greater than 2500 gates**

# TI-ALS CAE Platforms

Hardware Platform	Library/CAE Host Environment	Max Density 2500 gates	Max Density 10000 gates	Part Number
PC	Viewlogic	X		TPC-ALS-DS-PC-VL
PC	Viewlogic		X	TPC-ALS-DA-PC-VL
PC	Orcad	X		TPC-ALS-DS-PC-OR
PC	Orcad		X	TPC-ALS-DA-PC-OR
Sun	Cadence		X	TPC-ALS-DA-SN-CD
Sun	Mentor 8.2		X	TPC-ALS-DA-SN-MG
Sun	Valid		X	TPC-ALS-245
Sun	Viewlogic		X	TPC-ALS-DA-SN-VL
HP700	Mentor 8.2		X	TPC-ALS-DA-HP7-MG
DN4000/HP400	Mentor 7.0		X	TPC-ALS-235

**Note:** To get the Part Number for the annual maintenance, please add a -SP suffix to the Part Number of the corresponding software packages



# TI-ALS Programming Configurations

Hardware Platform	CAE Host Environment	Programmer for One Device	Programmer for Four Devices	Part Number
PC	Viewlogic/Orcad	X		TPC-ALS-DS-P2S-PC
PC	Viewlogic/Orcad		X	TPC-ALS-219
Sun	Cadence/Mentor/Valid/Viewlogic	X		TPC-ALS-DS-P2S-SN
Sun	Cadence/Mentor/Valid/Viewlogic		X	TPC-ALS-249
HP700	Mentor	X		TPC-ALS-DS-P2S-HP7
HP700	Mentor		X	TPC-ALS-DS-P2-HP7
HP400	Mentor	X		TPC-ALS-DS-P2S-HP4
HP400	Mentor		X	TPC-ALS-DS-P2-HP4
DN Series	Mentor		X	TPC-ALS-239

**Note:** Programming units are compatible with both high (10000 gates) and low (2500 gates) density systems



# Software Options

Hardware Platform	Library/CAE Environment	Description	Part Number
PC	Viewlogic	High Density Viewsim Simulator	TPC-ALS-016
PC	Viewlogic	Low Density Viewsim Simulator	TPC-ALS-017
PC	Viewlogic	Schematic Capture, Viewdraw	TPC-ALS-VL-005
PC	Viewlogic	Schematic Generation, Viewgen	TPC-ALS-VL-001
PC	TI'x'press	Boolean Synthesis and FPGA Optimization	TPC-ALS-PLDSYN
PC	TI	Universal Actionprobe for Test & Debug	TPC-ALS-218
Sun	Synopsys	TI-Synopsys Libraries fro Design Compiler	TPC-ALS-SYN-S4
Sun	TI	Universal Actionprobe for Test & Debug	TPC-ALS-218
HP700	Synopsys	TI-Synopsys Libraries fro Design Compiler	TPC-ALS-SYN-HP
HP700	TI	Universal Actionprobe for Test & Debug	TPC-ALS-218
DN4000/HP400	Synopsys	TI-Synopsys Libraries fro Design Compiler	TPC-ALS-SYN-DN
DN4000/HP400	TI	Universal Actionprobe for Test & Debug	TPC-ALS-218

— Easy Logic Integration —



FPGA

# TI FPGA Integrator Series

---

- ✓ **Schematic Capture - Viewlogic Viewdraw**
- ✓ **Simulation - Viewlogic Viewsim**
- ✓ **PLD Equation Entry - TI Prologic**
- ✓ **Logic Synthesis - TI'x'press**
- ✓ **Device Implementation - TI-ALS-DS**
- ✓ **Floorplanning - TI Module Mover**
- ✓ **Logic Technology Selector - TI Logic Integration Software**
- ✓ **Programmer - Activator 2S**

# TI FPGA Integrator Series

	FPGA DELUXE KIT	PLD PLUS KIT	PLD KIT	TI FPGA STARTER KIT
Schematic Capture	✓			
Simulation	✓			
PLD Equation Entry	✓	✓	✓	
Logic Synthesis	✓	✓	✓	
Device Implementation:				
- Place & Route				
- Viewlogic or OrCAD Libraries	✓	✓	✓	✓
- Timing Analysis				
- Programming Software				
Floorplanning	✓	✓	✓	✓
Logic Selector Software	✓	✓	✓	✓
Single Socket Programmer	✓	✓		
\$1000 Credit Towards Exemplar VHDL Upgrade	✓	✓	✓	
1 Year Maintenance	✓	✓	✓	✓
	\$4,495	\$1,995	\$1,295	\$ 695

— Easy Logic Integration —



FPGA

# TI FPGA Integrator Series

FPGA Deluxe Kit	PLD Plus Kit	PLD Kit	FPGA Starter Kit
TPC-ALS-INT-FPGA-DX	TPC-ALS-INT-PLDP-VL	TPC-ALS-INT-PLD-VL	TPC-ALS-INT-START-VL
Viewlogic Schematic Capture (TPC-ALS-VL-005)			
Viewlogic 3k Gates Simulator (TPC-ALS-017)			
Prologic - PLD Equation Entry	Prologic - PLD Equation Entry	Prologic - PLD Equation Entry	
TI'xPRESS - Logic Synthesis (TPC-ALS-PLDSYN)	TI'xPRESS - Logic Synthesis (TPC-ALS-PLDSYN)	TI'xPRESS - Logic Synthesis (TPC-ALS-PLDSYN)	
TI-ALS with Viewlogic Libraries (TPC-ALS-DS-PC-VL)			
TI Module Mover	TI Module Mover	TI Module Mover	TI Module Mover
TI Logic Integration Software			
Programmer Activator 2S (TPC-ALS-DS-P2S-PC)	Programmer Activator 2S (TPC-ALS-DS-P2S-PC)		
\$ 1000 Credit towards Exemplar VHDL Upgrade	\$ 1000 Credit towards Exemplar VHDL Upgrade	\$ 1000 Credit towards Exemplar VHDL Upgrade	
1 Year Maintenance	1 Year Maintenance	1 Year Maintenance	1 Year Maintenance
<b>\$ 4,495</b>	<b>\$ 1,995</b>	<b>\$ 1,295</b>	<b>\$ 695</b>

— *Easy Logic Integration* —



**FPGA**





