



DIGITAL

DESIGN

SEMINAR

look to the future

1997
REFERENCE MANUAL



IMPORTANT NOTICE

Texas Instruments (TI) reserves the right to make changes to its products or to discontinue any semiconductor product or service without notice, and advises its customers to obtain the latest version of relevant information to verify, before placing orders, that the information being relied on is current.

TI warrants performance of its semiconductor products and related software to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilised to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

Certain applications using semiconductor products may involve potential risks of death, personal injury, or severe property or environmental damage ("Critical Applications").

TI SEMICONDUCTOR PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORISED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT APPLICATIONS, DEVICES OR OTHER CRITICAL APPLICATIONS.

Inclusion of TI products in such application is understood to be fully at the risk of the customer. Use of TI products in such applications requires the written approval of an appropriate TI officer. Questions concerning potential risk applications should be directed to TI through a local SC sales office.

In order to minimise risks associated with the customer's applications, adequate design and operating safeguards should be provided by the customer to minimise inherent or procedural hazards.

TI assumes no liability for applications assistance, customer product design, software performance, or infringement of patents or services described herein. Nor does TI warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such semiconductor products or services might be or are used.

Copyright ©1997, Texas Instruments Incorporated.

1997

Digital Design Seminar

contributions by : Georg Becke
Peter Forstner
Eilhard Haseloff
Johannes Huchzermeier



Digital Design Seminar

Digital Design Seminar

Agenda

- ★ Introduction
- ★ Basics and Practical Examples of Transmission
- ★ Logic Families
- ★ Metastability
- ★ System Design Criteria
- ★ Bus Systems
- ★ Advanced Logic Trends

DDSAgcnprob.ppt Jan97




Digital Design Seminar

Design Problem 1

★ The arrangement above is found on a computer module.

★ Problem: Microprocessor 2 fails at reduced temperature or at increased supply voltage.

WDSVAgcprob.ppt Jan97 



The above example shows a multi-processor system. Both processors get the same clock signal and are running synchronously. The designer builds up the system and finds that at reduced temperature or increased supply voltage Microprocessor 2 fails.

After replacing Microprocessor 2 with a new device, the system still fails. Processor 1 and 2 are exchanged; now Processor 1 fails in socket 2, while Processor 2 works perfectly in socket 1.

Obviously there is a problem with socket 2, but the designer doesn't know what to do.

At the end of the section "Bus Systems", the solution of this problem is found.

Design Problem 2

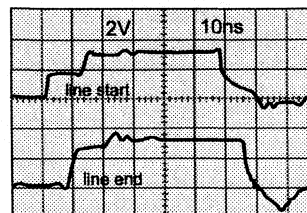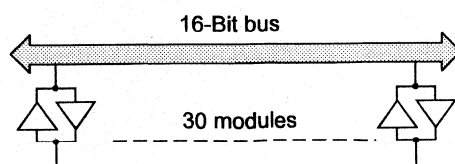

★ Signal distortion limits the data rate to 20 MByte/s (10 Mbit/line).

★ Transmission reliability is poor.

★ System power dissipation is extremely high

2 x F245 transmitting	$I_{CC} = 200 \text{ mA}$
2 x F245 receiving	$I_{CC} = 200 \text{ mA}$
56 x F245 3-State	$I_{CC} = 6160 \text{ mA}$
total	$I_{CC} = 6560 \text{ mA}$

★ Use of Advanced CMOS reduces the power dissipation, but worsens signal distortion.



A 16-bit backplane bus with 30 modules plugged into it has to be developed. Because the designer was successful using F245 transceiver in the past, these circuits are chosen to drive the backplane.

A look at the waveforms on this bus with a oscilloscope shows bad signal quality. At the driver output, stairs in the rising edge are observed and at the end of each signal trace there is an undershoot in the range of -1.5V. On the other hand the 60 bus-transceiver has a huge power-consumption. A theoretical calculation shows a worse case supply current of 6.5A for the bus functions only.

The aim is to reduce the power consumption and improve the signal quality. The first idea is to use CMOS circuits, well known for their low power consumption. Replacing the F245 transceiver with AC245 devices reduces power consumption, but the signal quality becomes even worse. The designer had no idea how to improve the bus-system at this point.

To see the solution of this problem, please look at the end of the section "Bus Systems".

Digital Design Seminar

Design Problem 3

Computer-module 1 f_1

Computer-module 2 f_2

VME-Bus

- ★ The computer system exhibits sporadic failures (mean time between errors < 1 day).
- ★ After an extensive EMC hardening (improved layout of printed circuit boards, better shielding, filtering of I/O lines etc.), the communication between the two modules did not show improved reliability.
- ★ The MTBF was satisfactory after Module 2's clock rate had been reduced by 10%.

UDSVAgenprob.ppt Jan97

A multiprocessor system, connected through the VME-bus, was designed and running well. After 12 hours, processor module 2 fails; a system reset solves the problem. But again after a further 14 hours, processor module 2 fails again.

Now the designer made a lot of improvements regarding EMC-behaviour, thinking EMC to be the root cause of the problem (introduction of a main-line-filter, new board layout, new metal cabinet, etc. But the improvement was negligible.

Now the designer was desperate and tried this and that. During these experiments he found out that a reduction of f_2 by 10% seemed to solve the problem. But the system requirement was 100% f_2 and not 90% f_2 and so the root cause of failure still needed to be found.

The solution of this problem can be found at the end of the section "Bus Systems".

..... Digital Design Seminar

**Basics
and
Practical Examples
of Transmission**

..... FOPE \DDSTransmis.ppt Jan97



Digital Design Seminar

Circuit Diagram of a Transmission Line

L' Characteristic Inductance per Unit Length nH/cm
C' Characteristic Capacitance per Unit Length pF/cm
R' Characteristic Resistance per Unit Length Ω/cm
G' Characteristic Conductance per Unit Length S/cm

Line Impedance $\vec{Z}_0 = \sqrt{\frac{j\omega L' + R'}{j\omega C' + G'}}$

FOPE ADMS\Transmis.ppt Jun07

Circuit diagram of a Transmission Line

The equivalent circuit of a transmission line consists of an inductance L' representing the inductance of the transmission line, a resistor R' representing the ohmic resistance of the line, a capacitance C' representing the capacitance of the line and the conductance G' representing the losses in the capacitance of the line. All these values are length dependent and are therefore specified in unit/length, e.g.: nH/cm, pF/cm, Ω/cm, and S/cm. By setting up differential equations, one can calculate the impedance of a transmission line:

$$\vec{Z}_0 = \sqrt{\frac{j\omega L' + R'}{j\omega C' + G'}}$$

In practice this equation is difficult to handle. First, the line impedance results in a complex number which makes the required calculations time consuming. Second the line impedance is frequency dependent. This becomes uncomfortable in digital circuits, where one has to consider many frequencies simultaneously.

Digital Design Seminar

Loss-free Transmission Lines

At high frequencies the transmission line losses on printed circuit boards in digital systems can be neglected.

With $R' \ll j\omega L'$ and $G' \ll j\omega C'$:

Line impedance	$Z_0 = \sqrt{\frac{L'}{C'}}$	(real number !)
Propagation time	$\tau = \sqrt{L' \times C'}$	
Cut-off-frequency	$f_0 = \frac{1}{2\pi \sqrt{L' \times C'}}$	with $L', C' \rightarrow 0 \Rightarrow f_0 = \infty$

FOPE_ADDSI/Trancus ppt Jan97

Loss-Free Transmission Lines

In digital circuits low frequencies are not generally of concern. At higher frequencies (above some 10 kHz) the impedance of the inductance $j\omega L'$ becomes large compared to the resistance R' of the wire. The admittance $j\omega C'$ is also much greater than the corresponding conductance G' . Under this assumption R' and G' can be neglected. The impedance of the transmission line can now be calculated by the simple formula

$$Z_0 = \sqrt{\frac{L'}{C'}}$$

The impedance is now a real number which can be handled like an ohmic resistor. A further advantage is Z_0 is now independent of the frequency.


An important parameter in data transmission circuits is the propagation time t_p of the signal on a transmission line. This time is also determined by the parameters of the line:

$$t_p = \sqrt{L' \cdot C'}$$

On typical cables used in transmission circuits (coaxial cable, twisted pair cable) the propagation time becomes $t_p = 5 \text{ ns/m}$. This reflects a propagation speed $v = 200\,000 \text{ km/s}$ (about 60 % of the speed of light).

Digital Design Seminar

Transmission Line

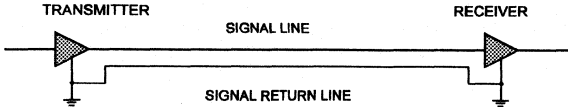


A transmitter and a receiver are connected by two parallel lines. The top line is labeled 'SIGNAL LINE' and the bottom line is labeled 'SIGNAL RETURN LINE'. Both lines are grounded at both ends.

A transmission line consists of

- a signal line, which carries the signal current
- a signal return line (mostly GND) which carries a return current of the same magnitude.

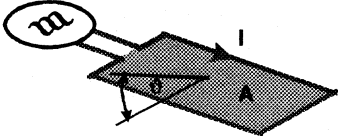Any DC interconnect between the GND terminals of the two circuits (e.g. safety earth) will not provide a signal return path according to transmission line theory.




The diagram shows a rectangular loop of two parallel wires. An arrow labeled 'I' indicates current flow in the top wire. The area between the wires is labeled 'A'. A distance 'r' is shown from the center of the loop to a point. A magnetic field symbol 'm' is shown above the loop.

$$E = k \times I \times A \frac{1}{r} \times \sin \theta$$

The area between the signal line and the return lines determines the capability of the circuit to radiate RF and also its susceptibility to EMI.

FOPE \DDSTransmit.ppt Jan97



Transmission Line

The designer has to keep in mind that a transmission system always has two conductors: the signal line and the signal return line. Both lines have to be designed carefully to ensure the required quality of the interface circuit. A random signal return path (e.g. via the protective ground wire) is not an adequate signal return line.

Both wires - the signal wire and the signal return wire - act as an antenna which influences the electromagnetic compatibility of the interface circuit. The larger the area between these wires, the larger will be the probability that electromagnetic energy is radiated, which may affect neighbouring equipment. Similarly the area between these wires also determines the electromagnetic susceptibility of the interface circuit.

Digital Design Seminar

Transmission Line Theory

Rule of Thumb:

Transmission line theory has to be applied, when the rise time of the signal is shorter than twice the propagation time.

Example 1 : Twisted pair cable; $\tau = 5 \text{ ns/m}$; $t_r = 2 \text{ ns}$

$$L = \frac{t_r}{2 \times \tau} = \frac{2 \text{ ns}}{2 \times 5 \text{ ns/m}} = 0.2 \text{ m}$$

Example 2 : Bus Line; $t = 20 \text{ ns/m}$; $t_r = 2 \text{ ns}$

$$L = \frac{t_r}{2 \times \tau} = \frac{2 \text{ ns}}{2 \times 20 \text{ ns/m}} = 0.05 \text{ m}$$

With shorter signal lines all line reflections occur during the rise/fall time of the signal. In this case it is allowed to use the simplified capacitive load line model.

FOPE \DDSI\Transmis.ppt Jan97




Transmission line theory

Transmission lines have to be treated as lines in accordance with transmission line theory when twice the signal propagation time becomes longer than the rise time of the signal - i.e.: when the line reflections no longer fall into the rise time interval. For a given rise time $t_r = 5 \text{ ns}$ and a typical propagation time of the signal $t_p = 5 \text{ ns/m}$, the critical line length in $l_{\text{max}} = 1 \text{ m}$. In applications where the propagation time of the signal is much longer - e.g. bus lines - the critical line length is even shorter.

Digital Design Seminar

Typical Line Impedances

	L' (nH/cm)	C' (pF/cm)	Z (Ω)	τ (ns/m)
Single Wire (far away from GND)	20	0.06	600	≈ 4
Space	μ_0	ϵ_0	370	3.3
Twisted pair cable	5 - 10	0.5 - 1	80 - 120	5
Flat cable	5 - 10	0.5 - 1	80 - 120	5
Wire on PC board	5 - 10	0.5 - 1.5	70 - 100	≈ 5
Coax cable	2.5	1.0	50	5
Bus line	5 - 10	10 - 30	20 - 40	10 - 20




FOPE_MDSVTransmis.ppt Jan07

Typical Line Impedances

The table shows typical Inductive and Capacitive Layers (L', C') of various signal traces. The last two columns display the corresponding impedance and propagation delay time along the wire calculated from L' and C'.

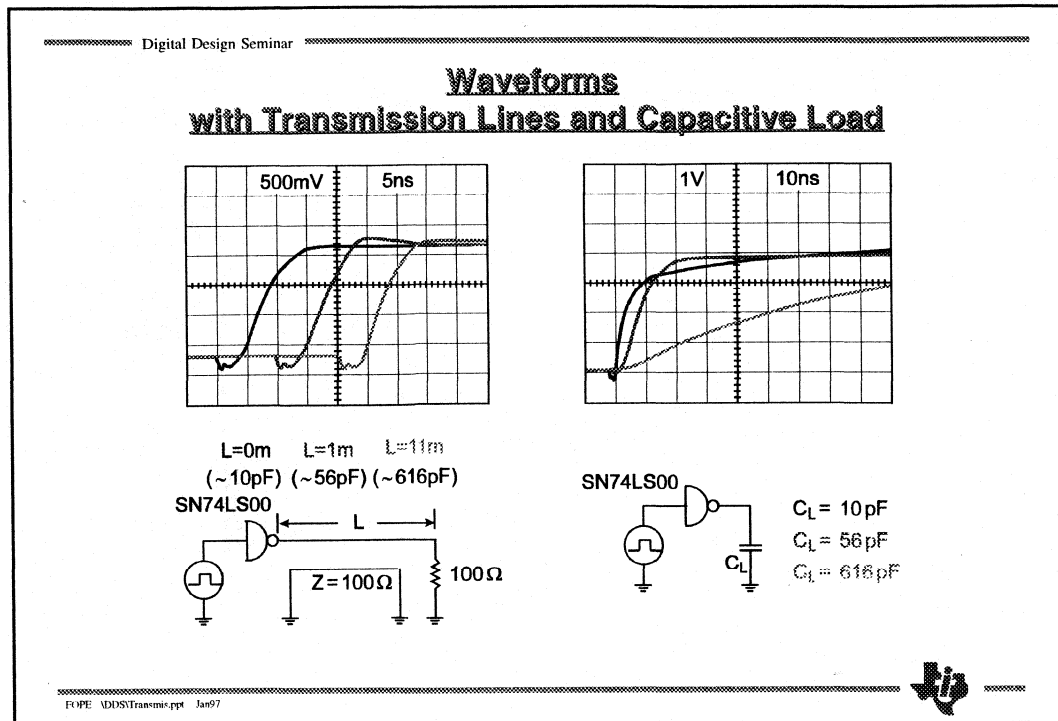
Common signal traces show an impedance in the range of 20 Ω to 120 Ω and propagation delay times of 4ns/m to 20ns/m.



Wave-forms with Transmission line and Capacitance Loads


Transmission line theory says that the line impedance is independent of the line length. As a consequence, the loading of the integrated circuit connected to a transmission line must be independent of the line length. The oscillogram above shows the signal wave-forms measured at the output of an integrated circuit (SN74LS00) when terminated transmission lines of various lengths ($l = 0\text{ m}$, $l = 1\text{ m}$, $l = 11\text{ m}$) are connected to the output of the circuit (the line termination is required to avoid line reflections). The three signals measured are displayed with a time offset for visibility. In all cases the rise time of the signal - and that means also the propagation delay time of the integrated circuit - is not influenced by the line length - say: by the capacitance of the line. The designer however has to consider the propagation time of the signal on the transmission line: a line length $l = 11\text{ m}$ results in signal propagation time $t_p = 55\text{ ns}$.

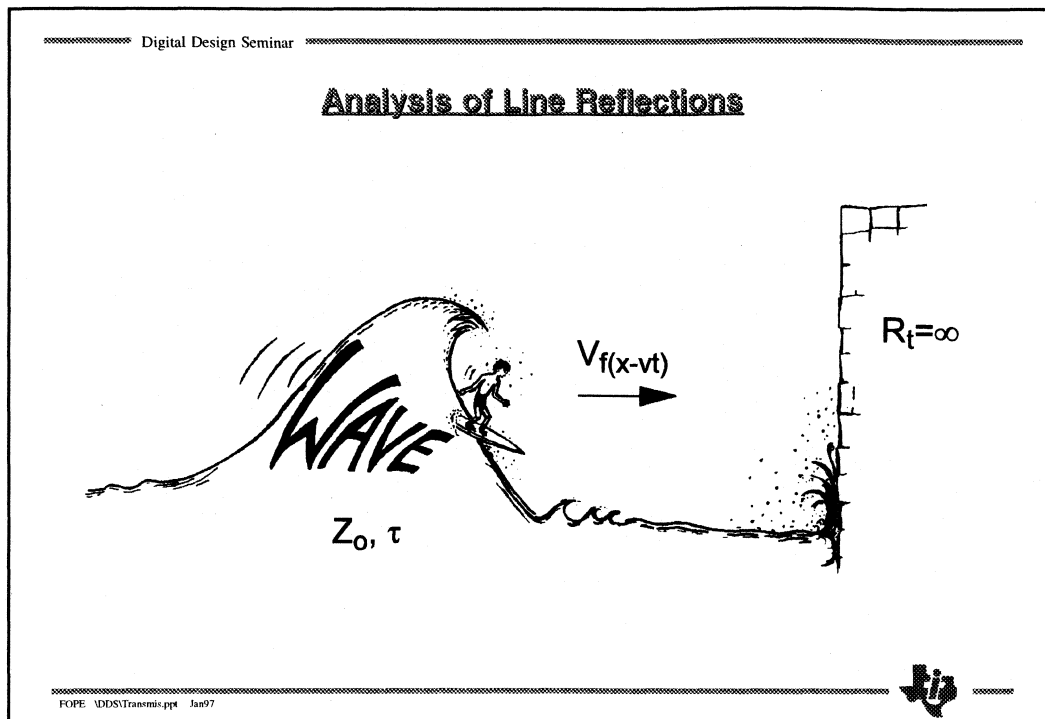A simple capacitive load caused a high input capacitance of the following circuit - e.g. when driving the gate of a MOS power transistor (Miller effect) - in conjunction with the output impedance of the gate ($R \approx 150\ \Omega$ for a SN74LS00) generates a low-pass filter, which increases the propagation delay time of the circuit.



Analysis of Line Reflections

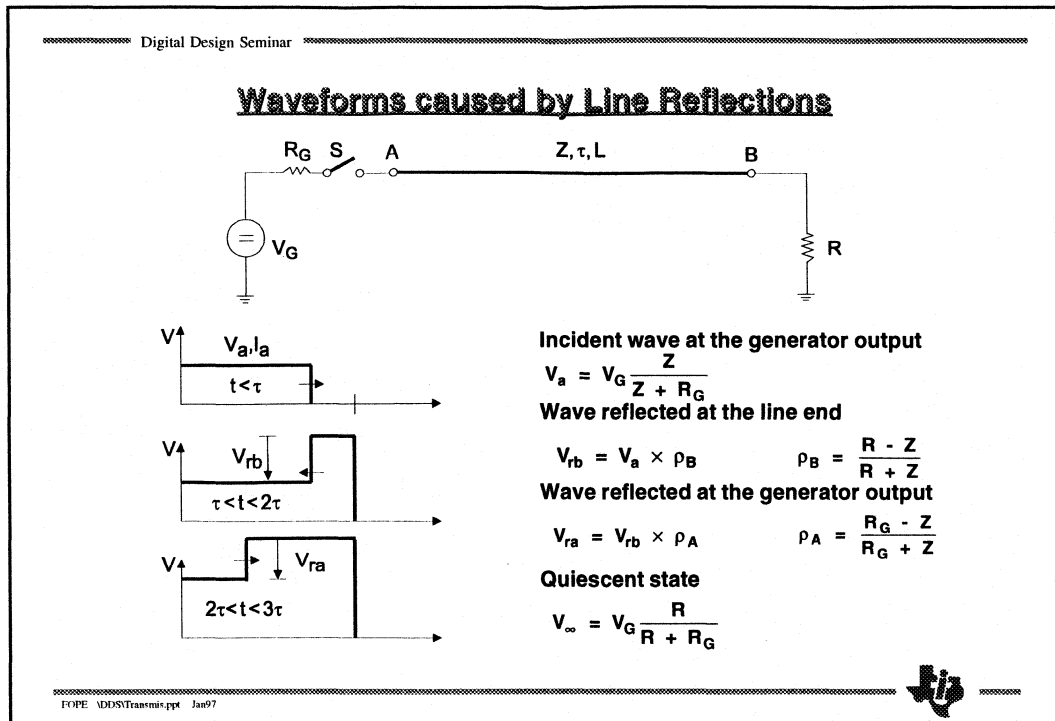In data transmission systems the designer has to take care of line reflections caused by improperly terminated lines. These line reflections may lead to an additional signal distortion which cause incorrect detection of the value of the signal at the line end (receiver input). This may result in an false operation of the system.



Wave-Forms Caused by Line Reflections

The circuit above shows a simple arrangement to analyse the wave-form in transmission circuits. At the time the switch at the output of the voltage source (generator) is closed, the effective generator load is the impedance of the transmission line alone. The voltage of the incident wave $V_{a(t=0)}$ can be calculated by using the simple voltage divider formula:

$$V_{a(t=0)} = V_o \frac{Z_o}{Z_o + R_o}$$

When the wave with this amplitude arrives at the line end, the energy not absorbed in the termination resistor - assuming that the line is not terminated correctly ($R_t \neq Z_o$) - will be reflected back to the generator. The amplitude of the reflected wave at that point is calculated:


$$V_{r1} = V_a \cdot \rho_B = V_a \frac{R_t - Z_o}{R_t + Z_o}$$

When this reflected wave arrives again at the generator output and the output impedance of the generator is not equal to the line impedance ($R_o \neq Z_o$), again a reflection occurs, where the amplitude of the reflected wave has to be calculated:

$$V_{r2} = V_{r1} \cdot \rho_A = V_a \frac{R_o - Z_o}{R_o + Z_o}$$

This process is continued until the energy of the wave is absorbed by the losses of the circuit (termination resistor R_t at the line end, and output resistor of the generator R_o). The final steady-state condition is calculated by the simple voltage divider:

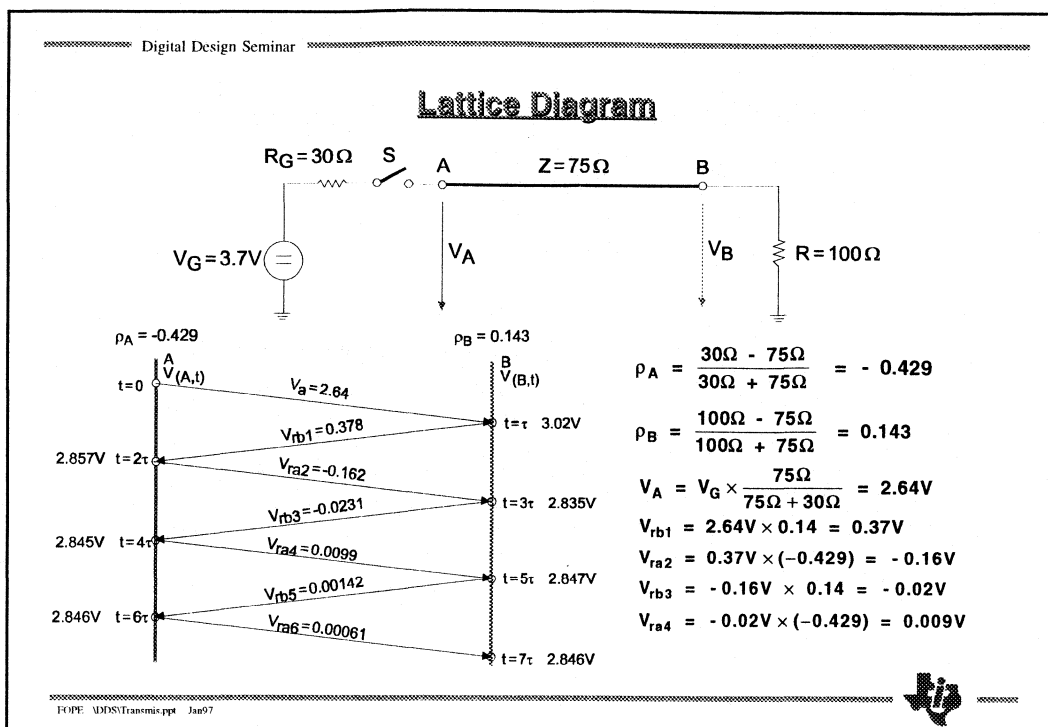
$$V_{t=\infty} = V_o \frac{R_t}{R_o + R_t}$$



Lattice Diagram


This example shows the analysis of an actual circuit. The generator with an open loop voltage $V_O = 3.7V$ and an output impedance $R_O = 30\Omega$ represents the simplified equivalent circuit of a SN74F00 in the high state. The line with an impedance $Z_O = 75\Omega$ may be a coax cable or a printed wire on multi-layer printed circuit board. As one can see, the amplitude of the reflected wave drops very fast. In most application the calculation of the various reflected waves can be stopped after the third reflection since the amplitude of the reflected wave is now so small that it can be neglected (in this example $V_{rb3} = 0.02V$).

The Lattice Diagram is a useful tool to simplify handling the many numbers to be considered when analysing line reflections. In this simple example the diagram consists of two time scales, each representing the situation at the beginning and at the end of the line. A change of voltage at the generator output is found at every even multiple of the propagation time, at the end of the line at every odd multiple of the propagation time. These points are now connected by lines which represent the forward and backward travelling waves. To each of these lines the corresponding voltage is assigned. The final task left is to add these voltages at the left side of the diagram (beginning of line) or the right side (end of line) to calculate the voltage in the system at a specific time.

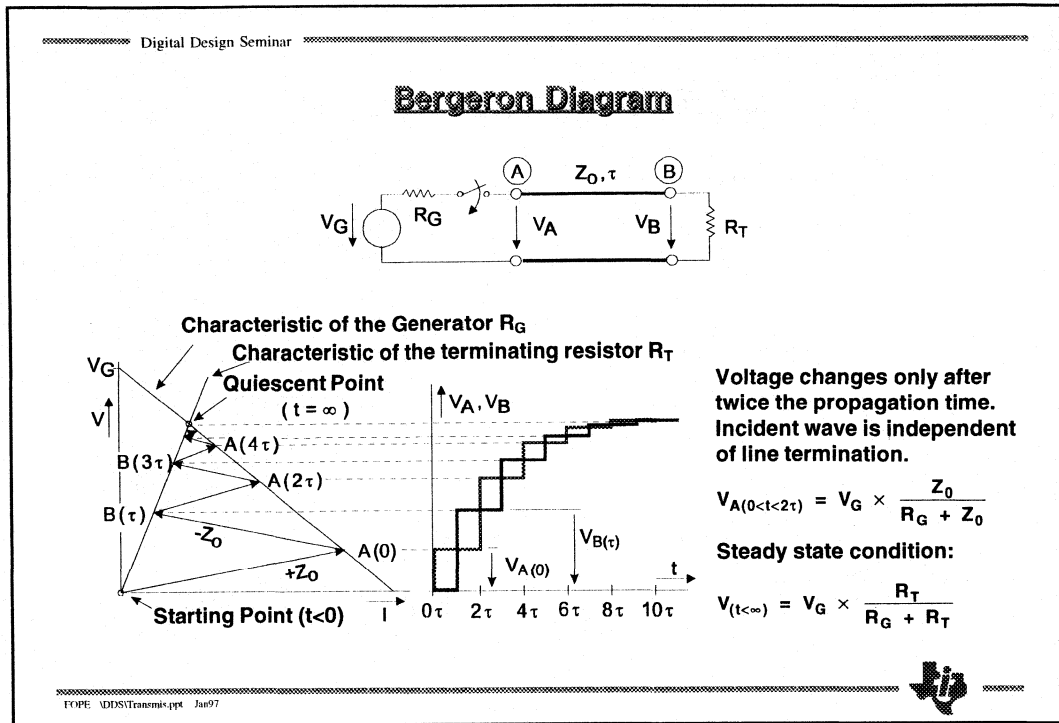

Bergeron Diagram

The Bergeron Diagram is a simple tool to analyse line reflections in circuits which show non-linear characteristics e.g. semiconductor components. For the analysis one has to draw a voltage/current diagram. Into this diagram the output characteristic of the generator R_0 (in this example a linear resistor) as well as the characteristic of the termination at the line end R_t has to be drawn. The point of intersection of these two lines provides the first result: the steady state voltage. The steady-state condition on the line before the switch has been closed ($V_{t=0} = 0 \text{ V}$, $I_{t=0} = 0 \text{ mA}$) is the starting point for the construction of the wave-form. Through this point (in this example the origin of the diagram) a line with the slope of the line impedance Z_0 ($\text{tg } \alpha = Z_0$) is drawn. Where this line hits the line which represents the output characteristic of the generator $A(0)$, one gets the voltage of the incident wave. By drawing a line with the negative slope ($\text{tg } \alpha = -Z_0$) through the point just constructed, the point of intersection (B_{tp}) with the line representing the termination characteristic R_t provides the voltage at the line end, when the wave arrives there the first time. By further drawing lines with alternating slopes ($Z_0, -Z_0$) one finds the voltages in the circuit during the following build-up. Finally the wave-forms at the beginning and the end of the line can be constructed by using the voltages found during the previous construction.

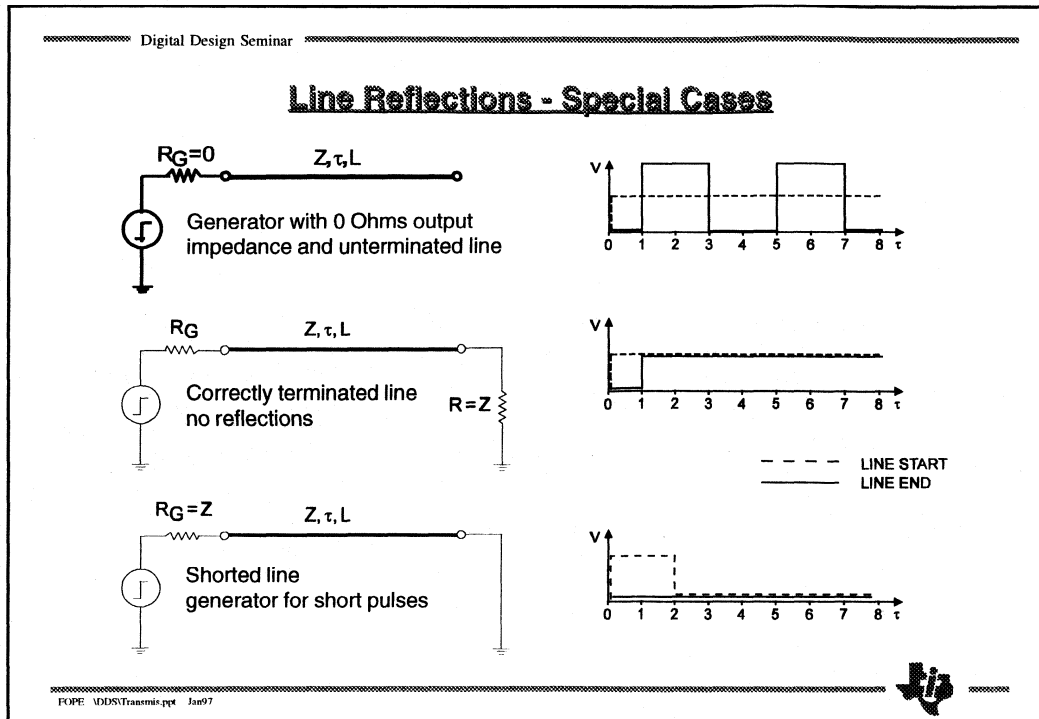


Line Reflections - Special Cases

This picture shows various extreme situations in transmission circuits. In the first circuit a generator with zero Ohm output impedance ($R_O = 0\Omega$) drives a loss-free transmission line, with an open circuit at the line end ($R_t = \infty$). The open circuit may represent the input impedance of integrated circuits, which mostly have an input impedance of several kilo-ohms - large compared with typical line impedance. The reflection factor $\rho = -1$ at the generator output and $\rho = 1$ at the line end leads to an undamped oscillation at the end of the line. This causes a receiver to switch many times, but not once only as desired.

The next circuit shows an interface terminated correctly at the line end. Under this condition one finds an undistorted signal (no line reflections)

The last circuit shows an interface shorted at the line end. For simpler understanding the output impedance of the generator has been chosen equal to line impedance ($R_O = Z_0$). When the switch is closed, an incident wave with an amplitude of $0.5 \times V_O$ travels to the line end and is reflected there with the inverted amplitude ($\rho = -1$). When the reflected wave arrives at the generator output again the steady-state is achieved. This circuit is a pulse generator which provides a pulse width equal to twice the propagation time of the wave on the transmission line. Such a circuit can be used advantageously when pulses with a length of a few nanoseconds only have to be generated.

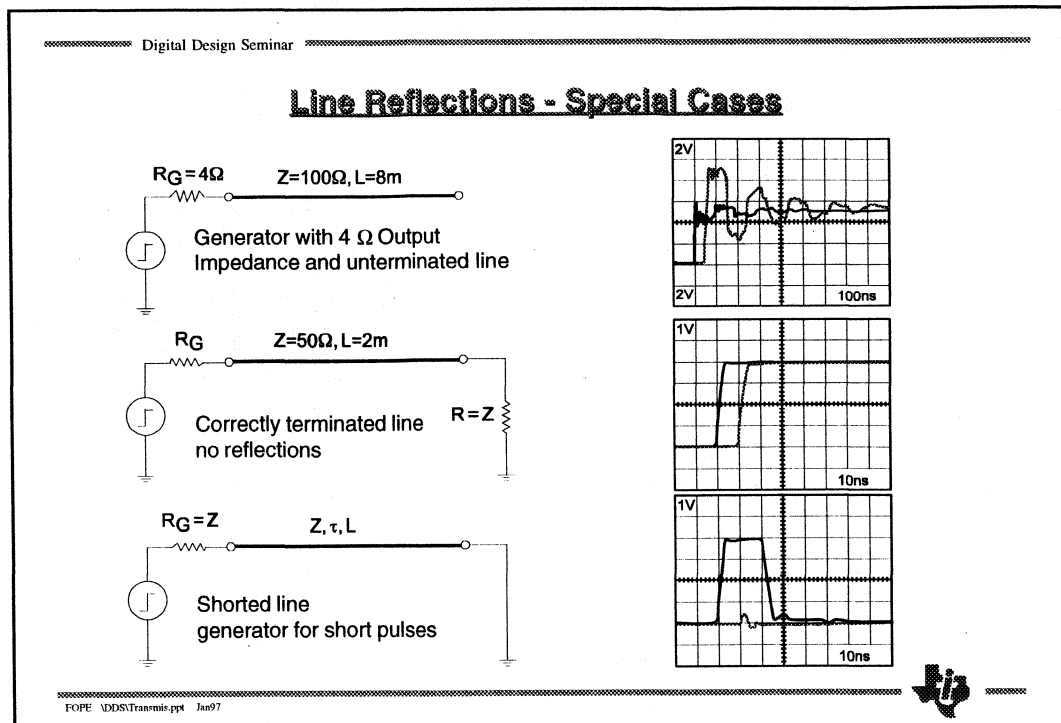

Line Reflections - Special Cases

The circuits described before have been built up to vary the behaviour. It is not as easy to design an generator with an output impedance of 0Ω . Therefore an Advanced CMOS circuit has been used as the generator. Its output impedance $R_O = 8\Omega$ leads to a damped oscillation, where the first undershoot at the line may still be capable of reaching the threshold voltage of the receiver to cause a false triggering.

The correctly terminated line shows no signal distortion.

In the interface shorted at the end, a coax cable with a propagation time $t_p = 5\text{ ns/m}$ and a length $l = 2\text{ m}$ has been used. This circuit generates a pulse with a width $t_d = 2 \times 5\text{ ns/m} \times 2\text{ m} = 20\text{ ns}$.

Digital Design Seminar

Measurement of the Line Impedance

Pulse Generator
 $R_G = 50\Omega, t_r < 1\text{ ns}$

Oscilloscope

50Ω Termination

Printed Circuit Board

$$Z_o = \frac{R_o}{V_o/V_a - 1}$$

$$\tau \times Z_o = L'$$

$$\tau / Z_o = C'$$

*) Note: $R_o = 50\Omega // 50\Omega = 25\Omega$

FOPE_ADDS\Transmis.ppt Jan97

Measurement of the Line Impedance

For correct design of an interface (selection of the generator, termination of the transmission line), knowledge of the impedance of the transmission line in use is necessary. One way to determine the line impedance is by means of a L/C bridge where one measures the inductance of a transmission line shorted at the end (short circuit impedance \approx inductive layer L') and capacitance with the line open at the end (open circuit impedance \approx capacitive layer C'). This method however mostly requires expensive equipment which often is not available.

A simpler method is shown on the picture above, where one needs a fast pulse generator and an oscilloscope only. By applying this method one measures the amplitude of the incident wave V_a caused by the voltage divider 'output impedance of the generator / line impedance' (in this example a signal and a ground wire in parallel on a printed circuit board) as well as the steady-state voltage V_o . By using the following equation (the voltage divider formula solved to Z_o) one gets the line impedance Z_o :

$$Z_o = \frac{R_o}{\frac{V_o}{V_a} - 1}$$


where R_o is output impedance of the generator. In this measurement set up the output impedance is made by the two coax cables in parallel, therefore $R_o = 25\Omega$.

By measuring the propagation time t_p one can also determine the inductance and the capacitance per unit length:


$$L' = t_p \cdot Z_o \qquad C' = \frac{t_p}{Z_o}$$

..... Digital Design Seminar


Line Reflections Open Circuit

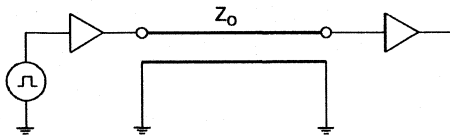

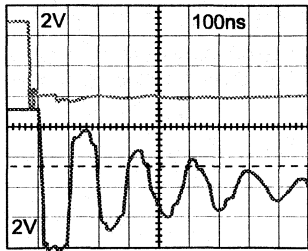An open circuit at the line end causes under- and overshoots which may exceed the maximum rated input voltage of the receiving circuit.



The following over- and undershoots may cross the threshold voltage of the receiver several times and may generate system errors.

..... 


FOPE_ADDSVTransmission.ppt Jan97

Line Reflections - Open Circuit

Driving an unterminated transmission line with a low-impedance output generates a good signal quality at the beginning of the line, while at the end of the line oscillation can be observed. This corresponds to the first example of our "Special Cases".

Digital Design Seminar


Line Reflections Terminated Line

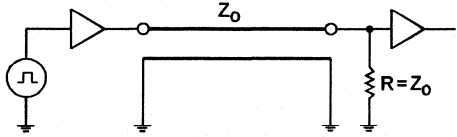


Line reflections are eliminated by correct line termination.

A mismatch up to 50% is acceptable.

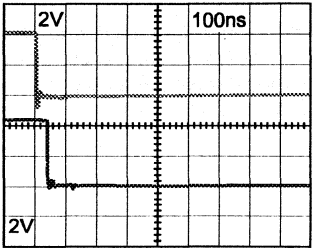Note: - Increased Power Dissipation
- High drive Capability required.




FOPE_VDSSTransmis.ppt Jan97



Line Reflections - Parallel-Terminated Line

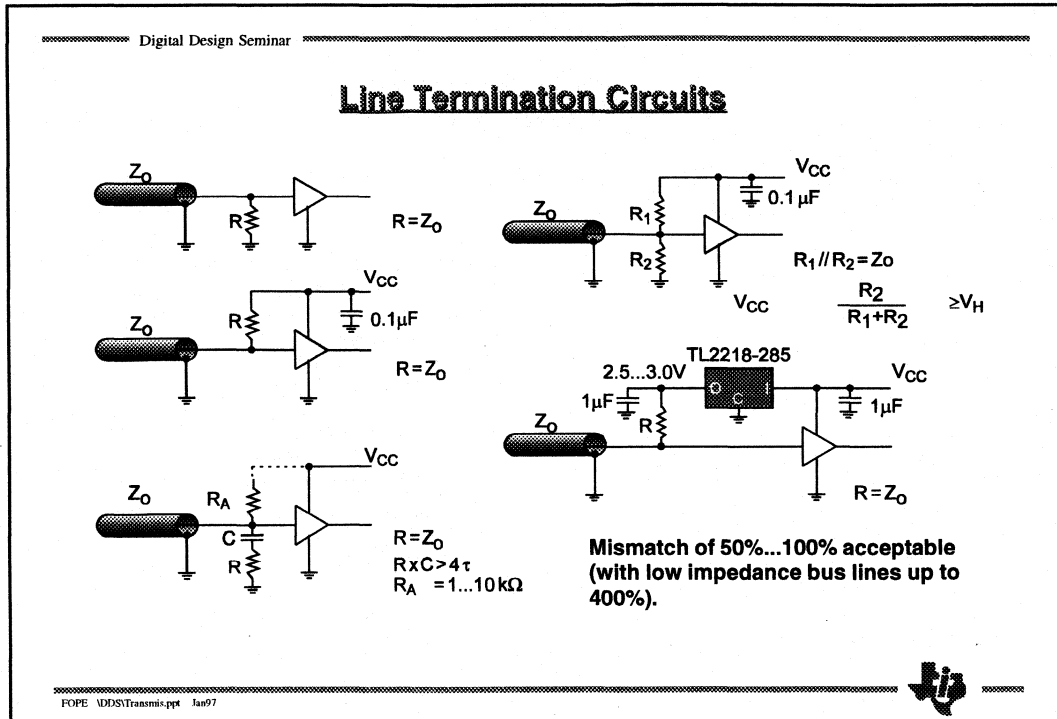Transmission lines are parallel-terminated at the line end by a resistor between the signal line and the signal return line. If the termination resistor is chosen equal to the line impedance ($R_t = Z_0$) no line reflections are found. In many applications, a mismatch of up to 50 % is acceptable. Under this condition the resulting reflection factor will be $\rho = 0.2$.



Parallel Line Termination Circuits

Single-ended or unbalanced transmission lines are usually terminated by a resistor between the line end and signal ground. If the drive capability of the generator in high state is not sufficient - e.g. open collector or open drain outputs - the termination resistor can also be placed between the line and the positive supply rail. This rail for low frequencies is shorted to ground via the power supply and for high frequencies via the decoupling capacitor (typical 0.1 μ F).

Particularly in CMOS applications, the designer does not like the continuous current in the termination resistor. This current increases the power dissipation. The current can be blocked by placing a capacitor C_b in series to the termination resistor R_t . When the time constant $R_t \times C_b$ is about 4 times the propagation time of the interface circuit, the line is almost sufficiently terminated.



In TTL systems, a resistor divider is often found at the line end (split resistor or Thevenin termination). This circuit is adapted ideally to the drive capability of TTL circuit and performs well in terms of eliminating line reflections. However the disadvantage of this arrangement is the large DC current through the resistor divider.

In advanced interfaces therefore often a circuit is used, which is called Active Termination. Here the termination resistor is placed between the line end and the output of an additional power supply, which provides an output voltage of 2.5 ... 3 V. Since on average 50 % of its active time the line is in the high state, the supply current is reduced by this amount. This termination technique is also used in bus applications, where much of the operating time all bus drivers are in inactive mode (3-state). In this situation the supply current becomes zero. Last but not least, the pull-up resistor avoids the line floating when all bus drivers are in the 3-state.

..... Digital Design Seminar

Line Reflections


Matching of Generator Impedance

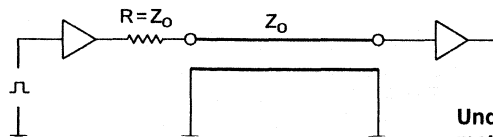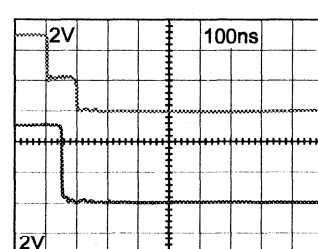Under- and overshoots are avoided by matching the output impedance of the line driver to the line impedance by means of a series resistor. Power dissipation is not increased (recommended in CMOS systems).

Note: Undefined logic levels along the transmission line for up to twice the propagation time.

Circuits with built-in serial termination (25Ω to 30Ω):
 8 Bit: SN74ABT2244
 16 Bit: SN74ABT162244
 18 Bit: SN74ABT162501


FOPE UMDSVTransmis.ppt Jan07 

Line Reflections - Matching of Generator Impedance


An elegant method to avoid under and overshoots at the line end is to match the output impedance of the driver circuit to the line impedance by placing a resistor in series with the output. A different output impedance of the driver in the low and the high state mostly does not allow correct matching. As long as the output impedance of the circuit in question is chosen to be 60 % to 100 % of the line impedance, a reasonable signal quality can be expected at the line end (receiver input). This technique is applicable in uni- and bi-directional point-to- point interfaces. In multi-point applications, where several stations are located along the transmission line, this technique is not recommended due to the long settling time of the signal (up to twice the propagation time).

Digital Design Seminar

Line Reflections Clamping Diodes

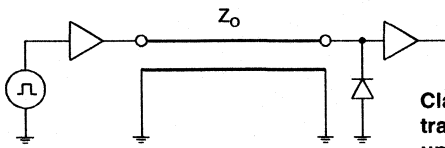

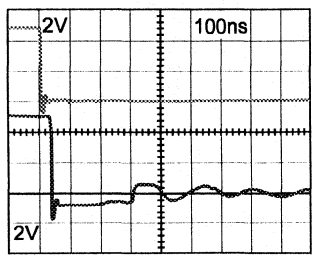
Clamping diodes at the end of the transmission line absorb the energy of under- and overshoots and ensure a clean signal waveform. Input circuits of logic ICs contain these clamping diodes.



Note: The clamping diodes of VLSI circuits often cannot handle the high currents generated by line reflections (parasitic transistors!). Provide additional Schottky clamping diodes!

Schottky Diode Arrays:
SN74S1050, SN74S1051, SN74S1052, SN74S1053,
SN74S1056, SN74F1056, SN74F1016, SN74F1018



FOPE: UDSSTransmis.ppt Jan97

Line Reflections - Clamping Diodes

An effective method to avoid excessive under- and overshoot at the line end is to limit this by means of clamping diodes. As the picture shows, a negative transition at the begin of the transmission line causes a negative undershoot at the line end which amplitude is limited to the forward voltage of the clamping diode at the line end ($\approx 0.7V$). The energy stored in the transmission line is not absorbed totally. Therefore one can observe several waves travelling forward and backward on the line. However their amplitude is a few 100 mV only.

Due to the positive influence of these diodes, clamping diodes are integrated into all logic circuits. TTL circuits contain at their inputs clamping diodes to the ground terminal to limit negative undershoots. In a CMOS environment, where owing to the higher voltage swing the positive overshoots are also of concern, additional clamping diodes between the input and the positive supply rail are often incorporated.

..... Digital Design Seminar

Bus Termination Arrays

Released Functions :

- SN74S1050 12-Bit Schottky Diode Array
- SN74S1051 12-Bit Schottky Diode Network
- SN74S1052 16-Bit Schottky Diode Array
- SN74S1053 16-Bit Schottky Diode Network
- SN74S1056 8-Bit Schottky Diode Array
- SN74F1056 9-Bit Schottky Diode Array
- SN74F1016 16-Bit Schottky Diode
R-C Bus Termination Array
- SN74F1018 18-Bit Schottky Diode
R-C Bus Termination Array

Applications :


- ★ Arrays in TTL systems
- ★ Networks in CMOS systems (positive overshoots)
- ★ Small buses, e.g. Memory Arrays
- ★ System bus in personal computers

FOPE AD5S1Tranemic.ppt Jan97

Line Reflections - Bus Termination Arrays

To reduce the number of required components, Texas Instruments offers the Bus Termination Arrays:

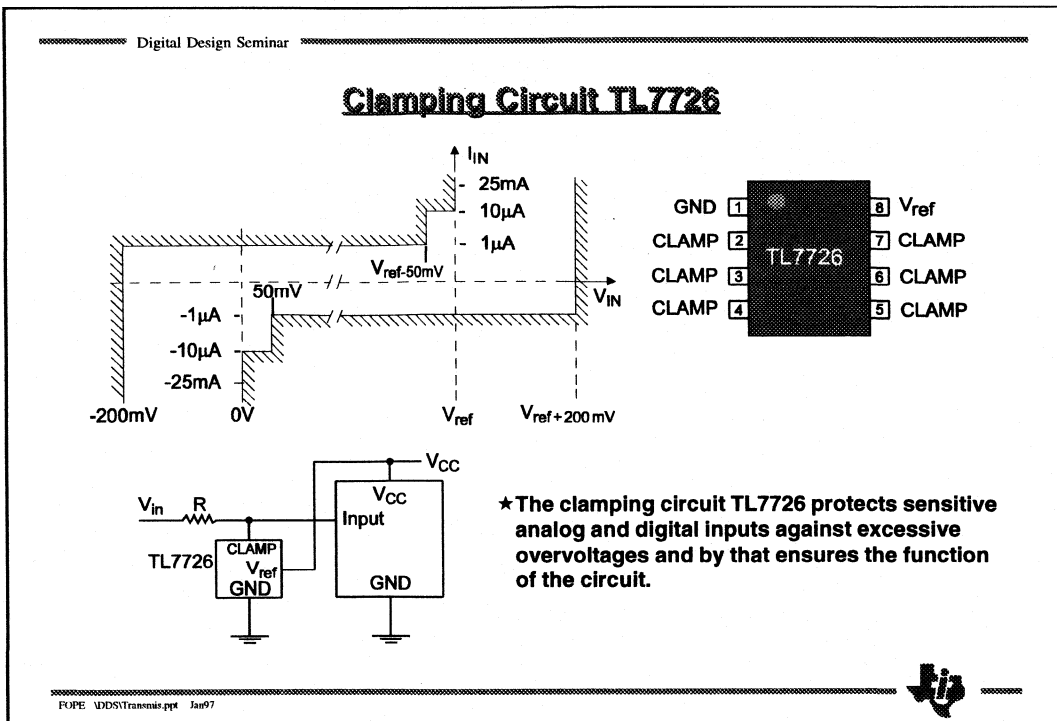These circuits include clamping diodes for 8- to 16-Bit circuits. Depending on the device type, the designer can select between clamping diodes to GND only or two rows of clamping diodes, one to VCC and one to GND.



Line Reflections - Clamping Circuit TL 7726


The clamping circuit TL7726 protects sensitive analog and digital inputs against excessive overvoltages and thus ensures the function of the circuit. It limits the over- and under-shoots to a maximum of $\pm 200\text{mV}$ by sourcing up to 25mA of clamping current.

..... Digital Design Seminar

Logic Families

.....
HUC1-DDS1-LogicFam.ppt Aug96



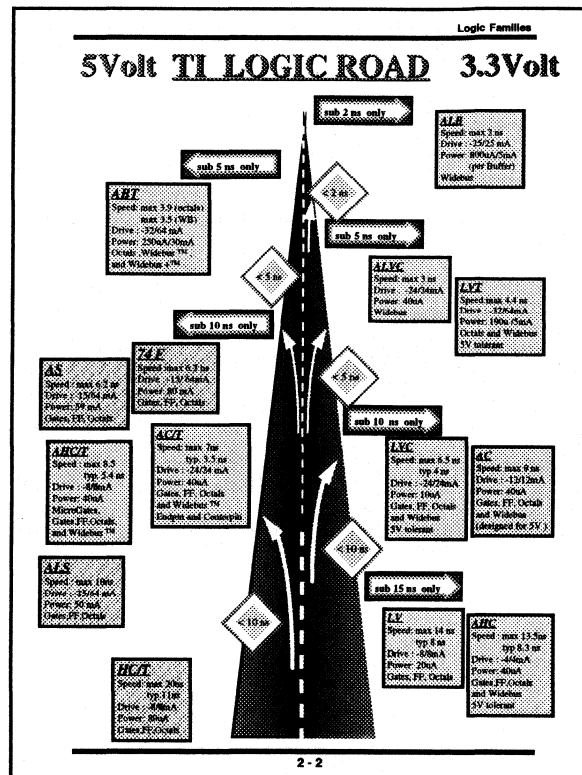

You always drive well with TI - on the ASL road.

This road shows different Logicfamilies, selected by speed .

The right side comprises TI's 3.3V Logoc families, while the left side shows the 5V Logic families.

One can see that there are only a few bipolar families mentioned on this foil:


AS,74F and the ALS family. This are families which are still in a sold in a huge volume.

This shows where TI wants to go : TI goes CMOS.

The performance data for each family is shown in the box.

Also one can see that there are some families specified at different voltages:

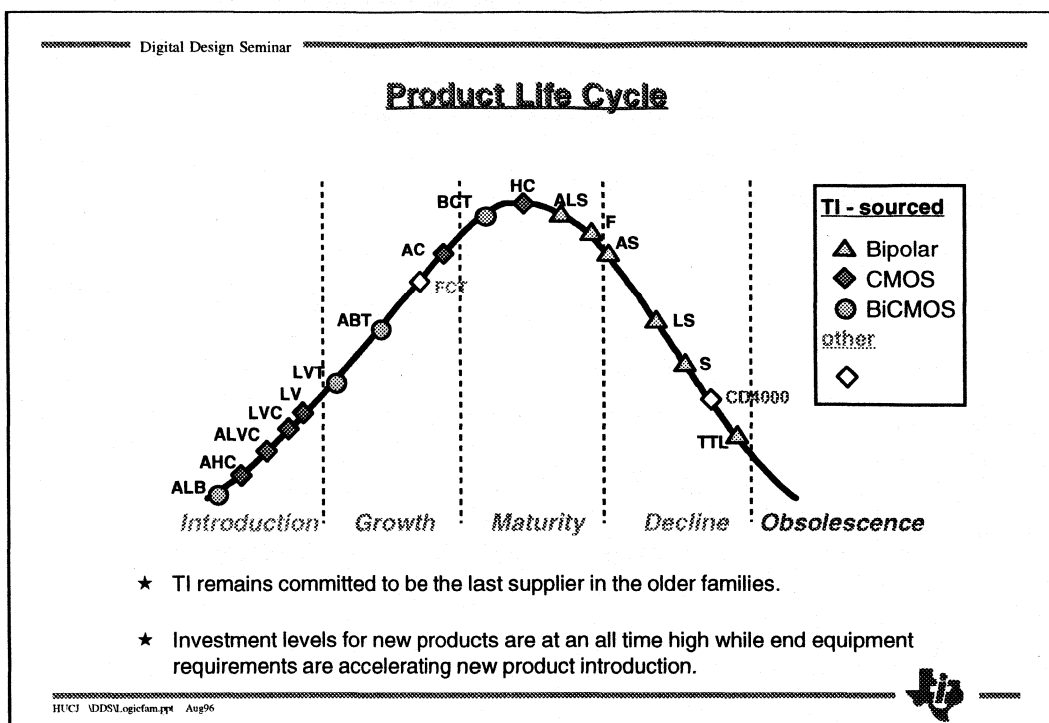The AC family and the AHC family have an additional specification at 3.3V, but were designed originally for 5V.



The Product Life Cycle curve shows all available logic families from TI.

This cycle is divided into 5 sections, beginning on the left side with the introduction phase and ending on the right side with obsolescence.

One can find that all bipolar families are in the decline phase. Those are not recommended to be used in new designs.


Today's system trends, such as increased packaging density, higher operating frequencies and reduced heat generation (e.g. no need for a cooling fan), lead to a strong need to reduce the power consumption or to change to low power technologies. This limits the use of mature technologies like LS and F. Even for HCMOS there is an improved version available: AHC Advanced HCMOS.

With the development of BiCMOS, a combination of Bipolar and CMOS technologies, the high drive capability and low noise characteristic of bipolar technology and the low power consumption of CMOS technology have been combined.

TI has true second source agreements with Philips Semiconductor and Hitachi Semiconductor for the Advanced BiCMOS Technology (ABT) family as well as for the low-voltage families (LV, LVC, LVT, ALVC). The agreement with Philips has recently been extended to also cover ALVT and AHC.

Investments for new products are at an all time high while end equipment requirements are accelerating new product introduction.

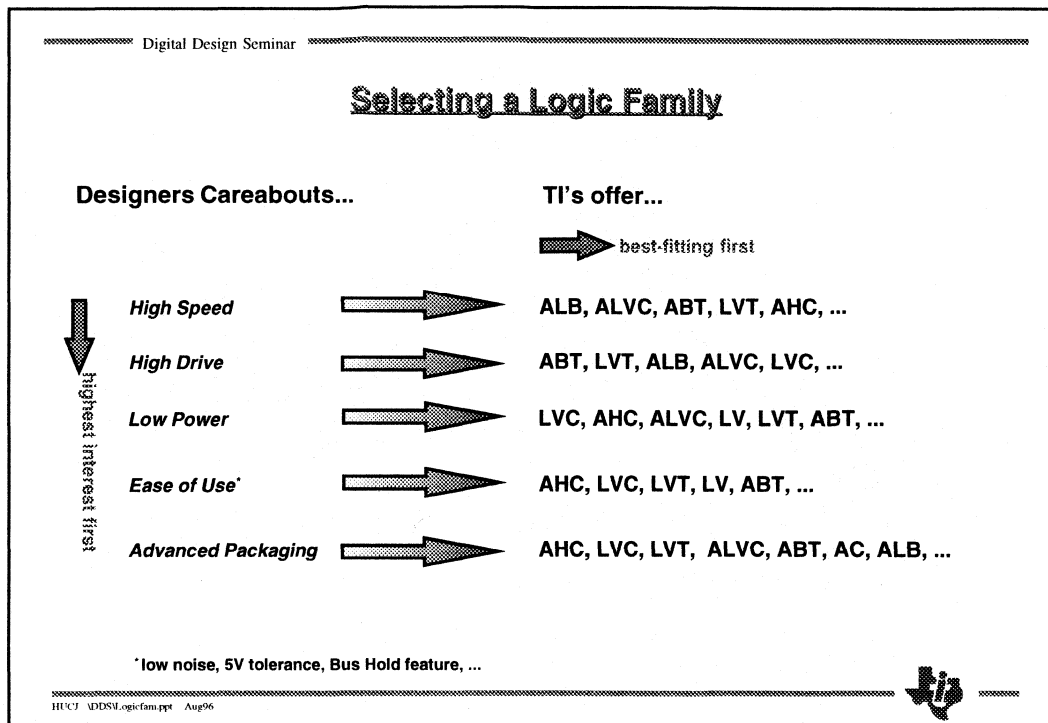On the other side, TI remains committed to be the last supplier in the older families.



Customer careabouts for selecting the optimum logic family are diverse depending on application needs and targeted end-equipments. From a survey, recently conducted by TI, the ranking of customer careabouts are as shown above.


According to this survey the careabouts have been sorted by importance from top to bottom.

The logic families have been sorted from left to right with regard to the most suitable family for a given criteria.

For example: you are looking for the fastest logic family ?

Choose the row 'High Speed' and look for the first family in 'TI's offer': ALB

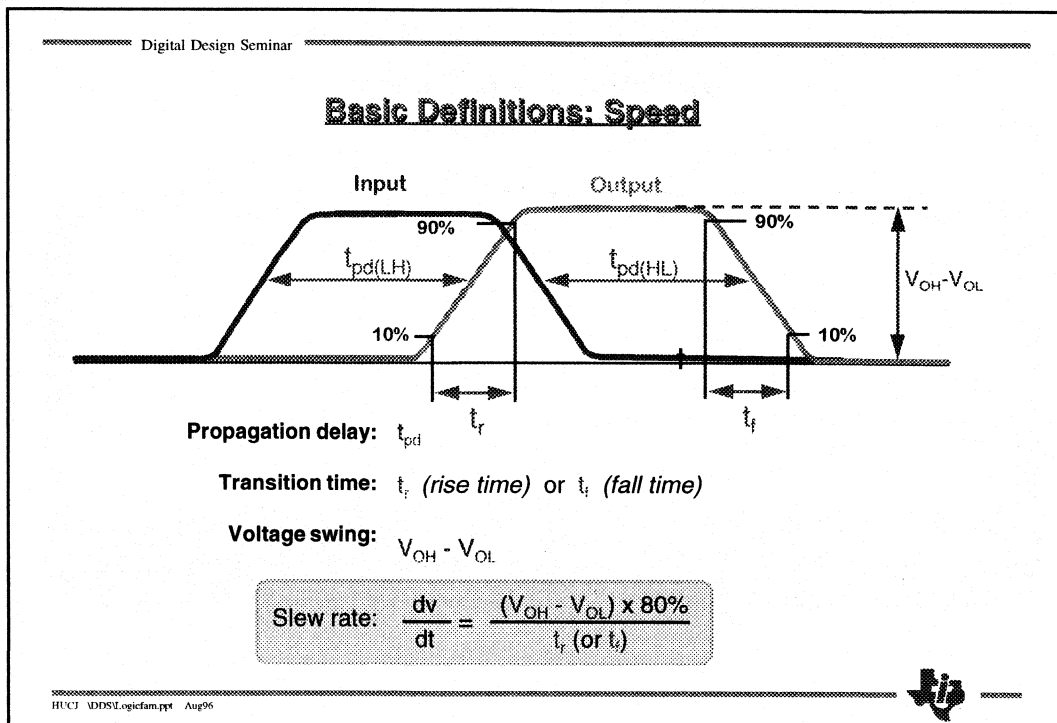It doesn't matter which focus you have; TI offers always the optimum logic family for your application.




There are two parameters a designer may have in mind when mentioning “speed”. The more frequently used refers to the circuit’s propagation delay, t_{pd} .

The shorter the t_{pd} , the higher the speed.

Some engineers, however, also refer to “circuit speed” in the context of a device’s signal slew rate. As can be seen from the formula, a circuit’s slew rate corresponds to the transition (rise or fall) time of the output signal.

The shorter the rise or fall time, the higher the slew rate.

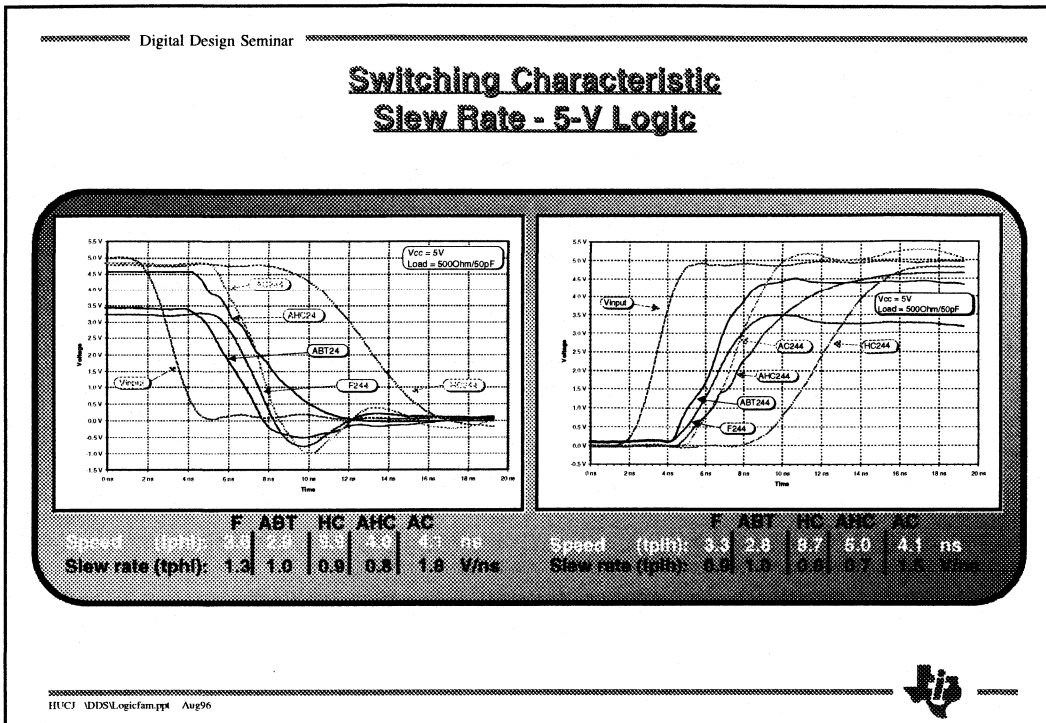As will be shown on the next page, propagation delay and slew rate are not necessarily proportional.




This and the next page show propagation delays (t_{pd}), voltage swing ($V_{OH} - V_{OL}$) and slew rates (dv/dt) for selected 5V and 3V logic families.

F, ABT, HC, AHC and AC are operating from a 5V supply voltage, while LVT, ALVC, LVC, AHC and LV have a 3.3V supply (next page).

The data may indicate that t_{pd} and dv/dt show common trends, but a closer look points out that there is no direct link between the two parameters. For example, the fastest family (ABT) is not the one with the highest slew rate. Another example is AHC, which is characterised by a three-fold speed improvement over HCMOS, but shows lower slew rates.

As will be discussed later in this section, high slew rates are often unfavourable, as this leads to high noise levels generated by the components. The worst technology in this respect is 5V AC, while AHC gives very positive results.

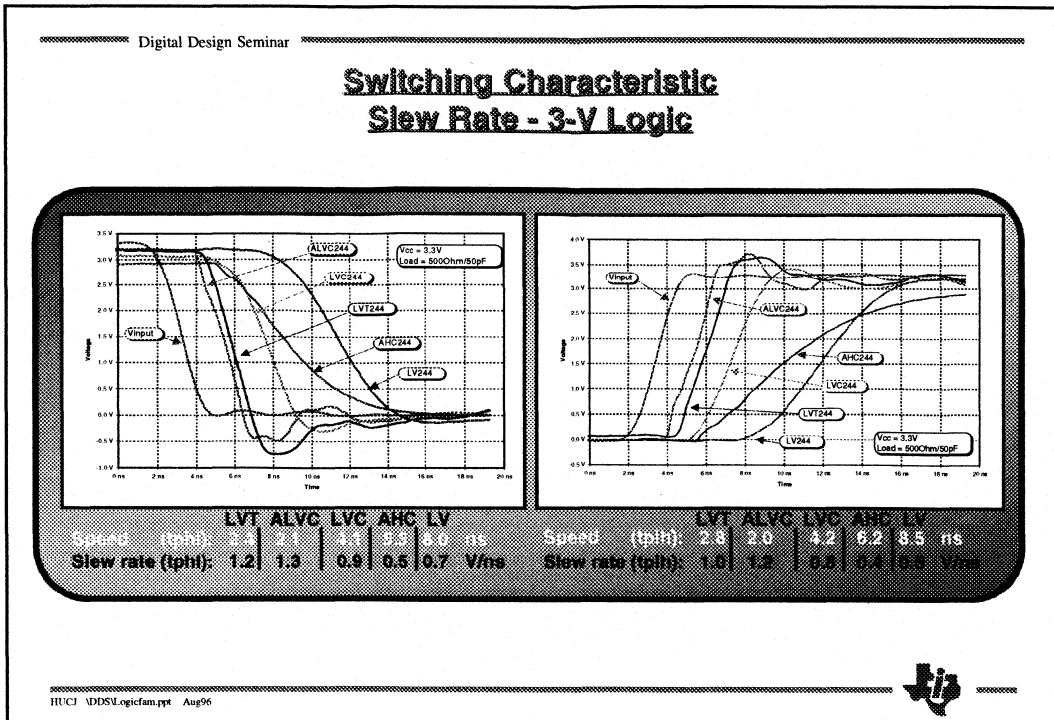Slew rates must be considered especially when designing high speed systems.



These graphs show propagation delays (t_{pd}), voltage swing ($V_{OH} - V_{OL}$) and slew rates (dv/dt) for selected 3V logic families (LVT, ALVC, LVC and LV) and AHC operated at $V_{cc}=3.3V$ (as specified in the datasheet).

In comparison to 5V logic, all of the low voltage technologies have somewhat lower signal slew rates.

It should be especially noted that ALVC, the fastest of all technologies shown, exhibits an uncritically low slew rate.

Circuit design techniques and the use of SSOP or TSSOP packages makes this favourable characteristic available.

Digital Design Seminar

Simultaneous Switching and Ground Bounce

$$V = L \times \frac{di}{dt}$$

dt = Change in time
 di = Change in current
 L = Packages inductance
 V = Amplitude of noise voltage

8 x 50 pF

HU03 0D5VL logicfam.ppt Aug96

A widely accepted method of measuring ground bounce is to switch (N-1) device outputs, while keeping the Nth input at a Low level.

The outputs of the drivers which are switching react with a certain delay to the changes at the inputs, whilst the unswitched output should remain undisturbed at "L" level. But, crosstalk from the neighbouring pins, a brief dip in the supply voltage and a brief rise of the groundlevel (resulting from the inductance of the Vcc and ground connections) automatically cause a reaction at the corresponding output.

The best results are achieved by the 48 pin Widebus package. This is primarily because of the 8 distributed GND pins for the 16 integrated drivers. The traditional 8 bit 'corner pin' devices are provided with only one GND pin and therefore show poor behaviour.


It is also necessary to mention that the measured values of noise level depend on the process technology used.

Whereas with BiCMOS and bipolar devices the threshold level will normally not be exceeded, with fast CMOS logic 2V or more may be reached as a result of the steeper pulse slope of CMOS signals, and consequently higher effect on the lead inductance.

Package Inductance drives Noise Voltage

- ★ Noise levels depend on package inductance and current slew rates (di/dt)
- ★ Noise voltages induced in switching outputs will be cross-coupled into quiet output(s)
- ★ Packages with multiple V_{CC}/GND pins (e.g. Widebus™) typically show much lower noise
- ★ Slew rate control helps reduce noise

DIP			SOP			SSOP		
Capacitance to GND	Pin Inductance	Coupling Factor	Capacitance to GND	Pin Inductance	Coupling Factor	Capacitance to GND	Pin Inductance	Coupling Factor
1.49 pF	13.7 nH	0.3	0.85 pF	5.8 nH	0.1	0.47 pF	5.0 nH	0.40
1.29 pF	11.1 nH	0.5	0.75 pF	4.8 nH	0.4	0.45 pF	4.1 nH	0.25
0.90 pF	8.8 nH	0.4	0.60 pF	3.8 nH	0.4	0.30 pF	2.7 nH	0.47
0.72 pF	8.0 nH	0.4	0.54 pF	3.3 nH	0.4	0.30 pF	2.8 nH	0.46
0.53 pF	3.4 nH	0.3	0.48 pF	3.0 nH	0.4	0.30 pF	2.8 nH	0.46
0.53 pF	3.4 nH	0.4	0.46 pF	3.0 nH	0.4	0.30 pF	2.8 nH	0.46
0.72 pF	6.0 nH	0.4	0.54 pF	3.3 nH	0.4	0.30 pF	2.8 nH	0.46
0.90 pF	8.8 nH	0.5	0.60 pF	3.8 nH	0.4	0.30 pF	2.7 nH	0.47
1.29 pF	11.1 nH	0.5	0.75 pF	4.8 nH	0.4	0.45 pF	4.1 nH	0.25
1.49 pF	13.7 nH	0.5	0.85 pF	5.8 nH	0.4	0.47 pF	5.0 nH	0.40

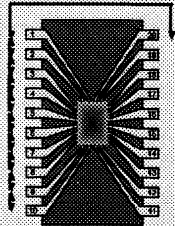


There are three factors which determine the electrical characteristics of a package:

- 1) the capacitance of a pin to ground
- 2) the inductance of a pin
- 3) the coupling factors of the pins to each other

In particular, the supply voltage pin should have a low inductance, and all signal lines of a good package should have as low as possible of all these three parameters.

The table above shows capacitance, inductance and coupling factor of each two neighbouring pins. These parameters are determined by:

- the length of the connections to the pin within the package,
- the spacing between these connections,
- the length of the wirebonds.

A DIP package has significantly longer internal connections than SOP or SSOP (and TSSOP). A long connection results in a high inductance and a high coupling factor; the increased area caused by the long connections also results in a high capacitance.

However, the reduction in coupling factor achieved by the short connections is partly offset by the smaller spacing between them.

..... Digital Design Seminar

Output Edge Control Circuitry (OEC™)

- ★ Gradual turn-on of output transistors by splitting the output in multiple stages
- ★ Dynamic smoothing circuit by softening the turn-on to obtain gradual takeover of current (di/dt control)

The result is that ground bounce is almost independent of the load!

OEC is a trademark of Texas Instruments Incorporated

.....

HUCJ_VDDSLogicfam.ppt Aug96

Signal slew rate improvements seen in Advanced Logic circuits have mainly been achieved by designing the circuits' output stages such that the change in output current (di/dt) and correspondingly the change in output voltage (dv/dt), are under control.


For this purpose, Texas Instruments has developed a technique called

Output Edge Control (OEC™)

The use of parallel output transistors that are turned on one after the other limits the signal slew rate.

A side effect is that the output noise levels are almost independent of the circuit load.

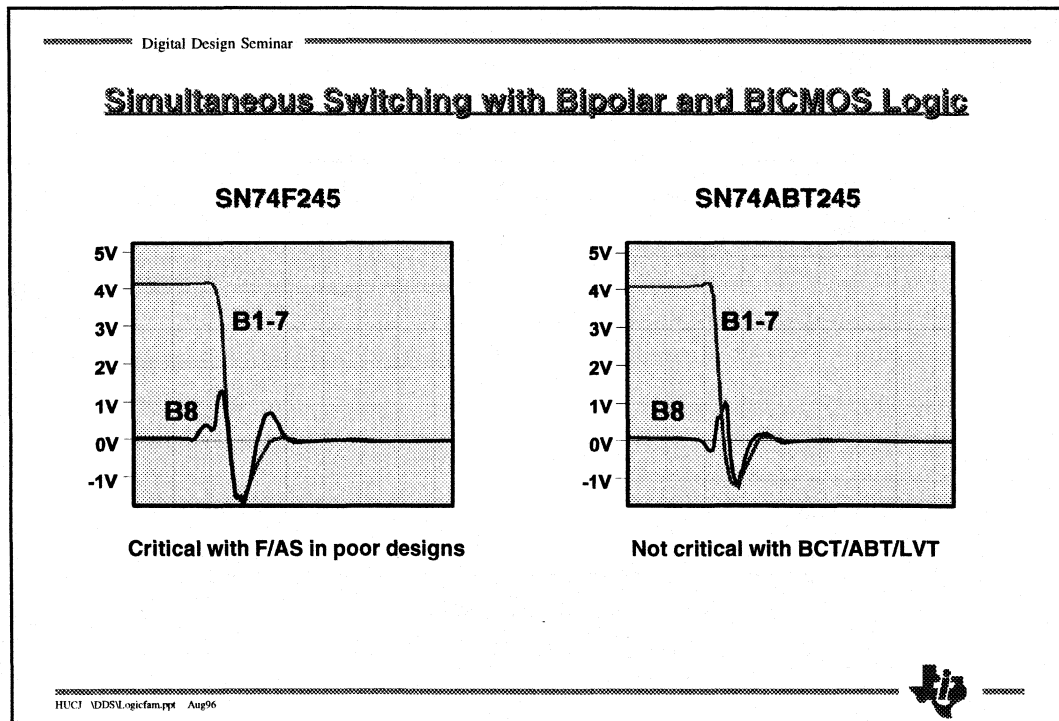
OEC has been implemented in AC, LVC and LVT.



Comparing ABT with 74F logic on simultaneous switching noise, one can recognize that the device of the F-family shows a more critical behaviour than the ABT device.

The maximum undershoot of the F device is greater than -1.5 V, while the ABT devices show a maximum value of about -800mV only.

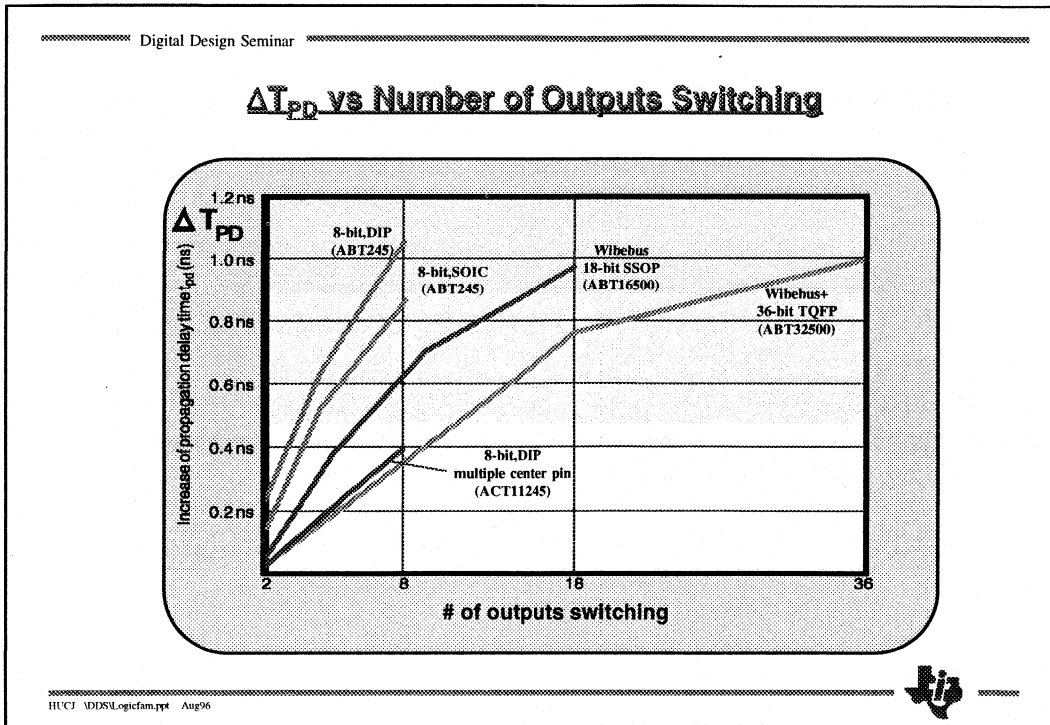Ground bounce behaviour must be taken into account very carefully for the design of digital systems using fast bipolar and CMOS technology families such as F/AS or AC/FCT.



The propagation delay of the component also depends on the number of simultaneously switched outputs.

The reason is that the inductance of the supply leads acts as a "current brake".


For devices in conventional packages (DIP and SOP) an additional delay of 150 to 200 ps for each output switched needs to be taken into account.

For example, an SN74F244 will have a maximum delay $t_{pHL} = 7.5$ to 8 ns, if all eight outputs switch simultaneously.

In this respect, the multiple V_{CC} leads in Widebus™ circuits are of advantage. They may not eliminate the effect, but at least they insure that the loss of speed is no greater than in octal bus drivers, even though twice as many outputs are switched.


..... Digital Design Seminar

Widebus™ Devices
Reduce Component Count



- ➔ Significant noise improvement
- ➔ More than 50% PCB space savings
- ➔ Significant speed improvement

..... Widebus is a trademark of Texas Instruments Incorporated

HUCJ VDSM logicfam.ppt Aug'96 

Widebus™ circuits offer designer substantial advantages, when it comes to designing advanced systems.

With the growing performance demands that are being made of computer systems, one has to expand the width of bus systems to 16 or 32 bits, so that high data throughput can be achieved. As the available space for a circuit is limited, this can only be implemented with components like Widebus™, which support wide bus architectures at an attractive cost.

As circuits become faster, the electrical characteristic of the package becomes more and more the focal point. Besides the unavoidable capacitances of the leads, it is primarily their inductances that determine the response of fast digital circuits and which, in some cases, limit their usage.


In addition, doubling the transfer channels in the new circuits reduces the component count by 50%.

Each of these new components is no bigger than a conventional 24-pin SO package, as the new circuit uses only 50% of the area previously used.

Digital Design Seminar

WIDEBUS / Widebus+™

	16 Bits				18 Bits				20+bits		
ABT	16240	H16245	16543	16833	16500B	162601	16843	H16646	16260	H16504A	32245
Advanced	16241	16373A	16623	16953	162500	16823	16863		162260	162827	32316
BiCMOS	16244A	16374A	16640	16952	16801	H16823	16245A		16460	16841	32318
Technology	162244	16470	16646		162501	162823	H16502A		162460	162841	32501
	16245A	16540	16852		16800	16825	H16504A		16821		32543
	162245	16541	16657		16801	162825	16640		16827		
AC/T	16240	16374	16623	16833			16472		16821		
Advanced	16241	16470	16640	16952			16474		16827		
CMOS	16244	16540	16646				16475		16841		
	16245	16541	16648				16823		16861		
	16254	16543	16651				16825				
	16255	16544	16852				16863				
	16373	16620	16657				16864				
AHC/T	16244	16245	16373	16374							
Advanced											
High-Speed											
CMOS											
LVC	16240A	162244	16374A	16543							
Low	16241A	16245A	16540	16646							
Voltage	16244A	16373A	16541A	16652							
CMOS											
ALVC	H16240	164245	H16827		H16524	H16835	H16601		16260	H16344	H162520
Advanced	16244A	H16254			H16525	H16863	H162601		H162260	H16721	16821
Low	H16244	H16373			H162525	H16901			H162268	H162721	16827
Voltage	H162245	H16374			H16821	H16500			16269	HR162409	162827
CMOS	H16245	H16543			H16825	H16501			HR162269	H16409	H162721
	HR162245	H16646			H16823	H16500			16270	H16828	H16841
LVT	16244A	16373	16952		16500	162502			16504		
Low	162244	16374			16501				162504		
Voltage	16245A	16543			16835						
Technology	162245	16646			16502						



HUCJ \DDSVLogicfa.ppt Aug96

TI offers more than 160 Widebus™ functions.

The excellent electrical behaviour of Widebus™ packaging is used for devices operating from 5V and 3V supply voltage.

For 5V families TI offers ABT and AC as well as some functions in the new AHC family.

For 3.3V supply voltage Widebus™ is available for LVC, ALVC and LVT.

Widebus+™ supports up to 36 bits within one single package.

Nomenclature:

8

SN74 FAM H R 16 2 xxx A DL.

18

32

FAM = Logic family

H (optional) - BusHold- feature,

8 - Octal device with JTAG functionality

16 - Widebus™

18 - Widebus™ with JTAG functionality

32 - Widebus+™

2 - Series damping resistor B-Port

R,2 - Series damping resistor A- and B- port

xxx - function

A - Die Revision

DL - Package (here SSOP)

Digital Design Seminar

Universal Bus Transceivers

A flexible Bus Interface Concept

- ★ UBTs can replace nearly all common bus interface logic parts ('245, '543, '2952, etc.)
- ★ Clocked storage "out" Latched or Transparent "in"
- ★ Shortens time to market with common t_{su} , t_h and min delay times

Device	UBT™ Part Types *
'ALVC16409	9-bit 4-Port
'ABT/'LVT16500	18-bit, Neg Clock
'ALVC16500	
'ABT/'ALVC16600	18-bit, Neg Clock w/CLKEN
'ABT/'LVT16501	18-bit, POS Clock
'ALVC16501	
'ABT/'ALVC16601	18-bit, POS Clock w/CLKEN
'ALVC16901	18-bit, w/parity generator/checkers
'ABT32501	36-bit, POS Clock w/CLKEN
'ABT32316	16-bit, Tri-Port
'ABT32318	18-bit, Tri-Port

* Series damping memory driver options available

UBT is a trademark of Texas Instruments Incorporated


HUC7 UDSU.ogicfa.ppt Aug96

Many high performance applications require more than one mode for accessing their system bus, because different parts of the system have different data access and processing speeds. While some may be able to work in transparent mode (fully synchronous to the data source), others will require data to be latched, to meet setup and hold time requirements. When designing CPU access to the bus, clocked storage is the easiest method.

UBT™s are bi-directional transceivers that can be configured as

- ★transparent,
- ★data-flow-through transceivers (e.g. '245 function),
- ★latch-enabled transceivers (e.g '543 function) ,
- ★clocked registered transceivers (e.g. '646 function),
- ★and clock-enabled registered transceivers (e.g. '952 function).

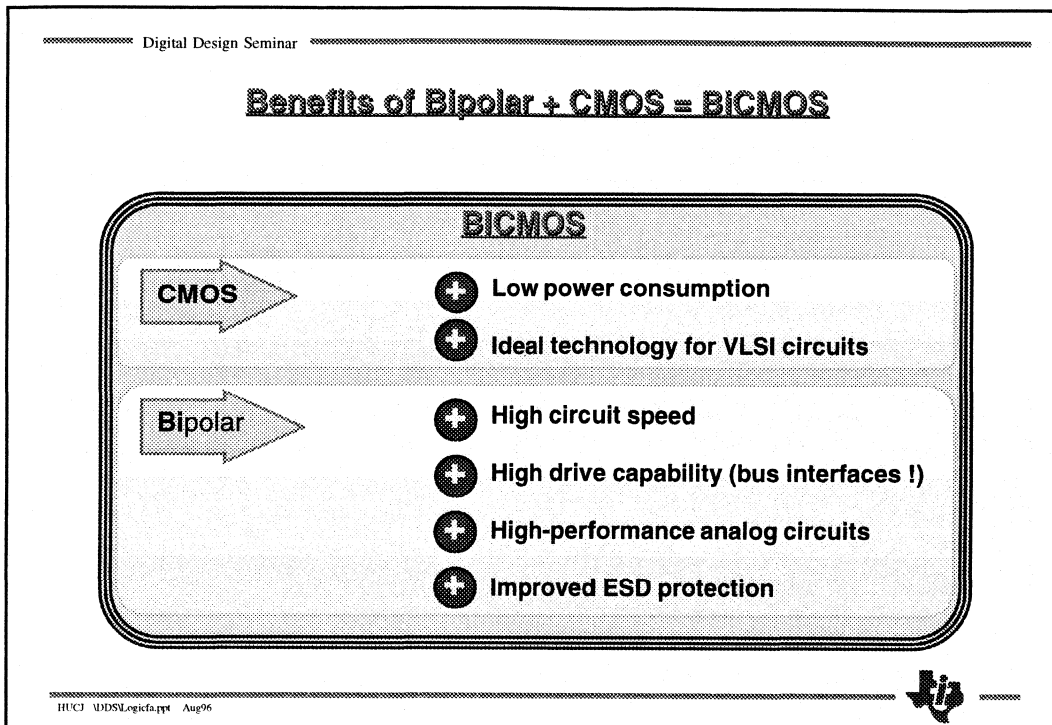Designed specifically for workstation bus-interface applications, the UBT™ is perfect as an interface to many different microprocessor architectures and system backplane specifications available. It may also be cost effective in low volumes as an alternative to several different interface functions.



Advanced BiCMOS technology (ABT) is available from Texas Instruments, to help designers develop high performance bus systems.

It was designed to provide speeds equivalent to existing advanced bipolar solutions with 90% less power consumption.

ABT employs a submicron 0.8 μ m process technology.


It combines elements of both bipolar and CMOS circuits on a single silicon chip.

ABT is based on a CMOS core-circuit structure with an NPN bipolar output transistor module.

From a power (current) consumption standpoint, the use of bipolar in the output stage is advantageous for two reasons:

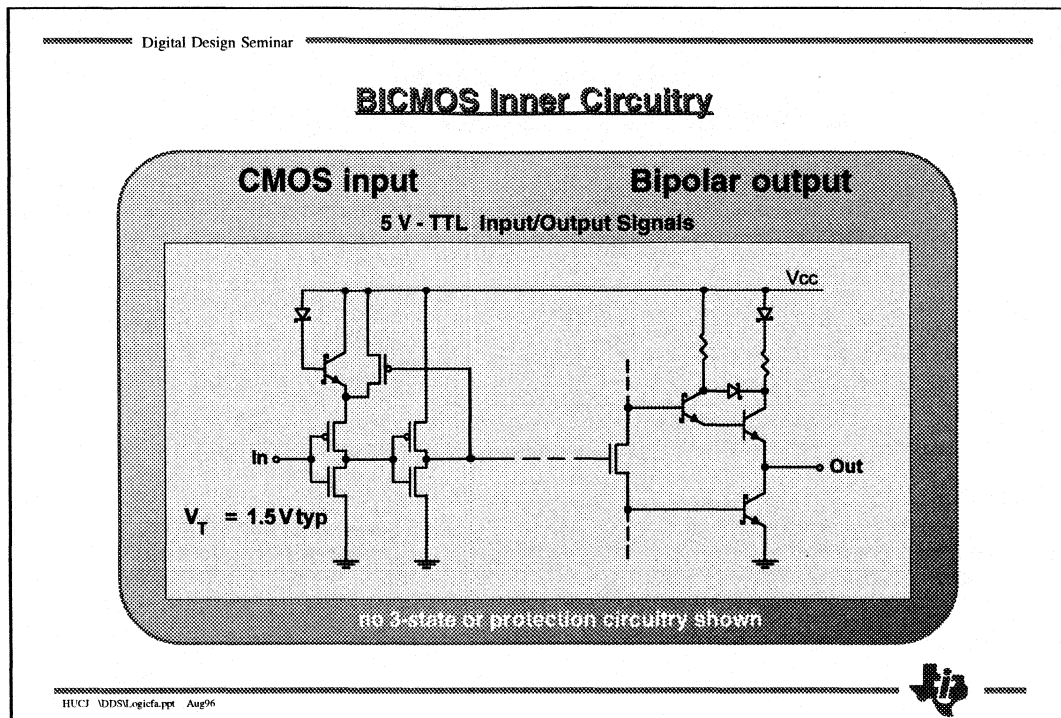- 1) the voltage swing is less than that of a CMOS output. The power consumed when charging or discharging internal circuit capacitances and the external load capacitance is reduced.
- 2) the bipolar transistors are capable of turning off more efficiently than CMOS transistors. The wasteful flow of current from V_{cc} to GND is reduced.

Although bipolar tends to have a high static power consumption, its lower dynamic power consumption allows for better overall power performance at high frequencies than either pure bipolar or CMOS as the dynamic power makes up the majority of a device's overall power consumption.



Simplified input and output stages of an ABT transceiver are shown on this slide.


The inputs are designed to offer TTL- compatible levels with guaranteed switching between a V_{IH} minimum of 2V and a V_{IL} maximum of 0.8V.

As these inputs are implemented in CMOS circuitry they offer high impedance for low leakage and low capacitance for minimal bus loading.

(The CMOS supply voltage of the input stage is dropped by diode D1 and transistor Q1, centering the threshold around 1.5V).

ABT outputs utilizes bipolar circuitry to provide the speed and drive necessary for a bus interface. A major advantage of bipolar circuitry in the output stage is the reduced voltage swing, which lowers ground noise, improves signal integrity and reduces dynamic power consumption.

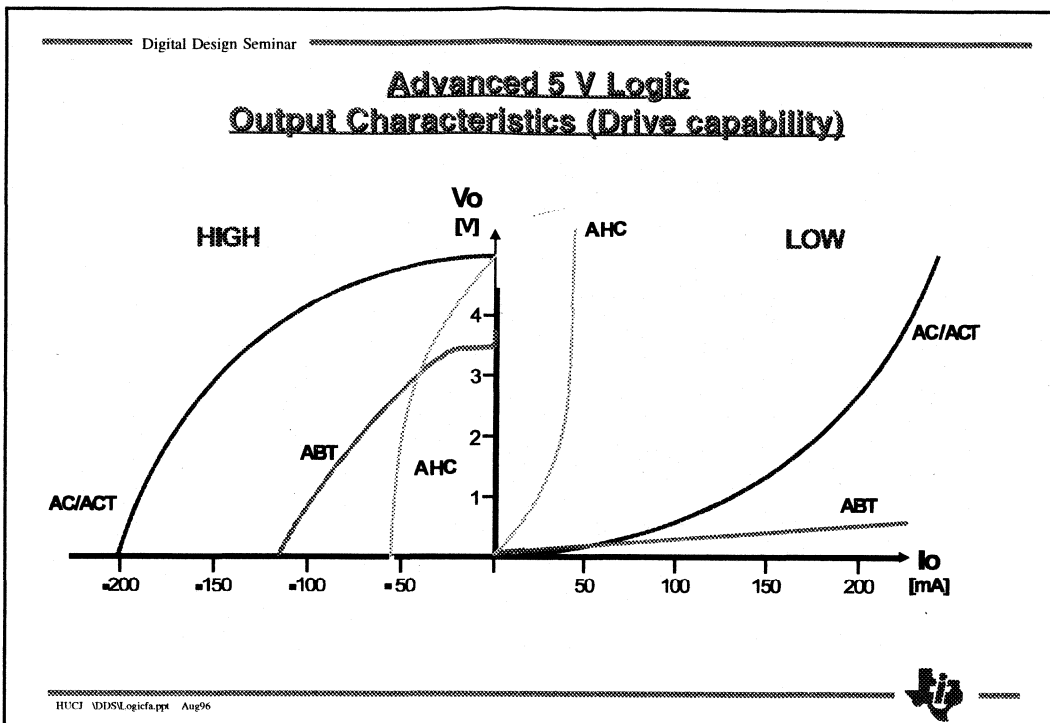Because of its small process geometry, tight metal pitch and shallow junctions, ABT can provide for strong output drive currents (sink current 64mA, source current 32mA) and low capacitances. As a result of these enhancements, internal propagation delay are very fast and show good behaviour regarding noise.



The curves show the drive capability in the logic 'high' and 'low' - states for various logic families.


The steeper the H- (L-) curve, the higher the drive capability.

To be noticed: ABT is a BICMOS family and delivers TTL levels at their outputs (typical output high: 3.6 V).

These curves can be taken as base for the graphical calculation of over- and undershoots of a certain family.

For the Bergeron method, as mentioned earlier, two more parameters are necessary: the **line impedance** and the value of the **line termination resistor**.

An example is given on the next page.

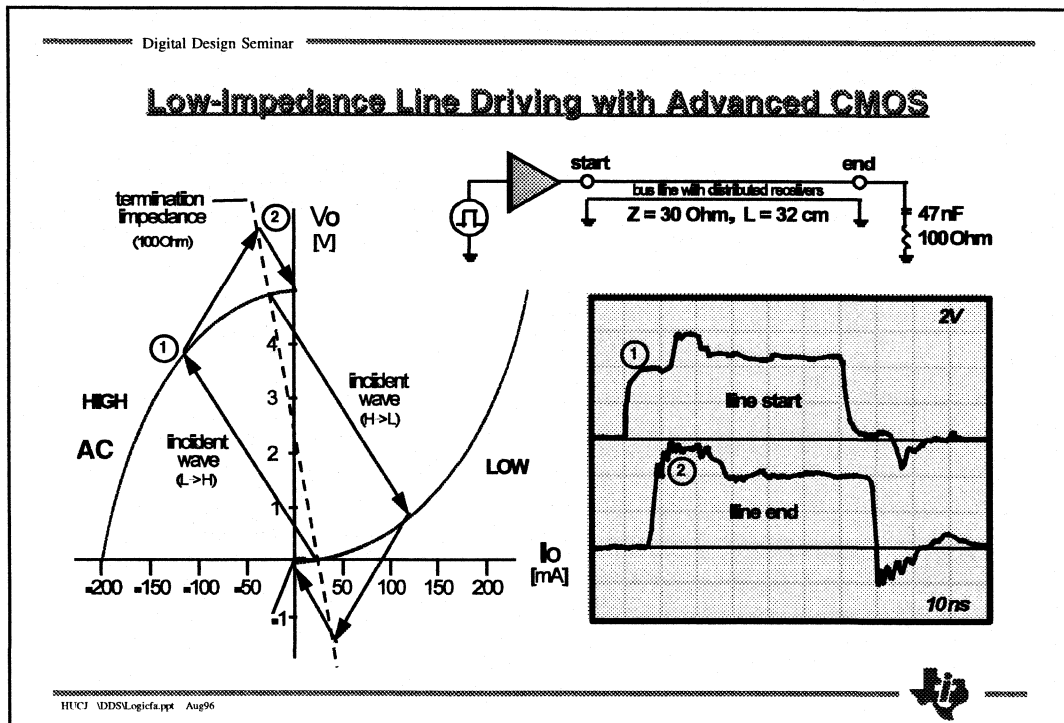

As an example of the graphical Bergeron method, a low impedance line is evaluated.


The set up is as follows: A line driver AC is connected to a line which impedance is $Z_0 = 30 \text{ Ohm}$, the length of the line is 32 cm. The line is terminated with 47nF in series with 100 Ohm. The generator delivers a digital signal, duty cycle 50%.

The first step to solve this problem graphically is to choose the output characteristics of the AC driver.

The termination resistor of the setup together with the duty cycle (50%) results in the dashed straight line. The line impedance (Z_0) results in the steepness of the progressing waves (solid arrows).


Each crossing of Output characteristic and the solid arrow can be recognized as voltage value at the begin of the line (Output driver).

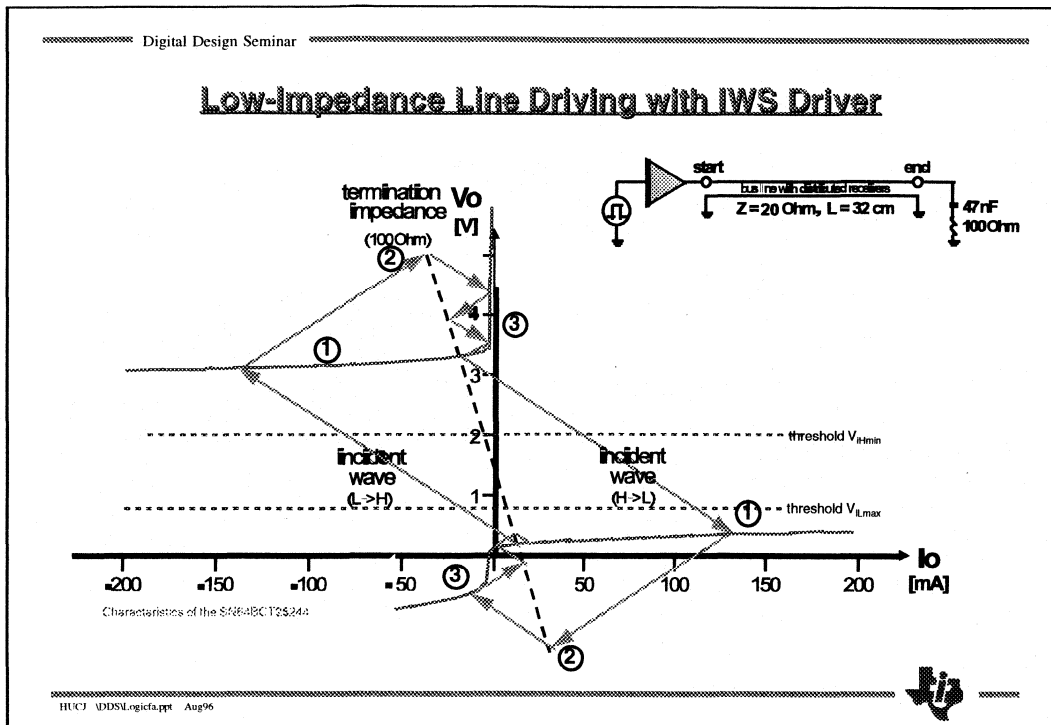Each crossing of termination curve and the solid arrow can be recognized as voltage value at the end of the line (termination resistor)



For the same set-up as before, but with the line impedance changed down to 20 Ohms, the Bergeron method is applied, using an BCT25244, an Incident Wave Switching (IWS) driver instead of the AC driver.

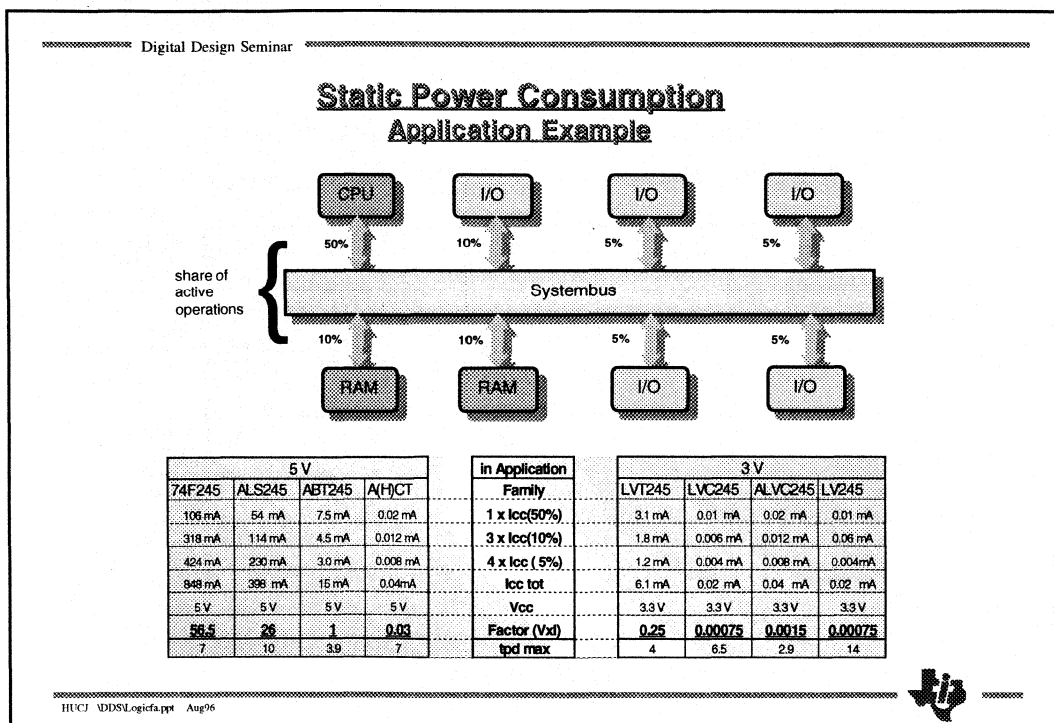The graph shows that again with the 1.wave a change of the logic level is ensured, which would not be achieved by using the AC driver earlier.




This foil shows an application example in a computer system.

CPU, RAM and I/O ports are connected via a bus. The percentage value shows the share of activity on the bus (e.g. the CPU uses the bus for 50% of the time). If we assume that all components used for this application are taken from the same family and we set up four identical systems, we can compare the performance.

The 74F family uses the highest power consumption for the application. This family is made in bipolar technology and consumes in tristate the same current as during active operation. Also the propagation delay time is the slowest with 7 ns.

ABT has improved performance in both power consumption and speed. ABT devices are made in BiCMOS Technology. During tristate-mode the power consumption is decreased down to 190 microamps. The speed is increased by 44% against the 74 F family.

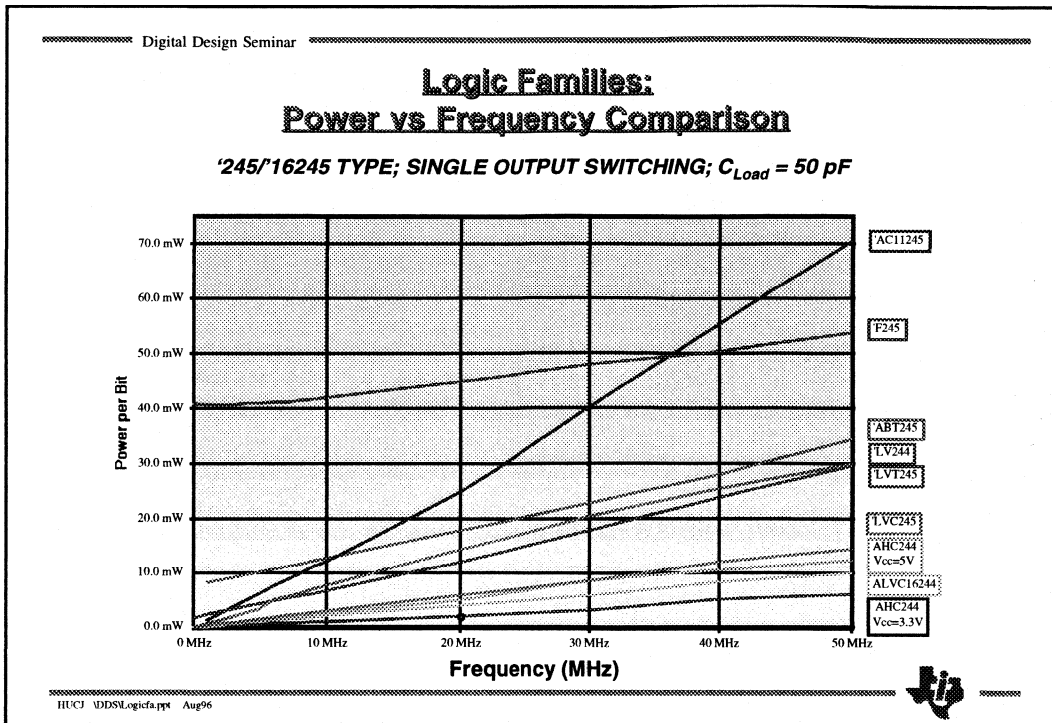A comparison with ALVC shows that only 0.15% of the ABT power consumption is used by ALVC. Also the propagation delay is improved to a value of $T_{pd}=2.9$ ns.



This foil shows the dynamic power consumption of different 5V and 3.3V Logic families.

Digital Design Seminar

Why 3.3 V ?

$$P_{TOT} = V_{CC} \times \left(I_{CC} + \frac{V_{CC}}{f_i} \times \left(\frac{I_{CC}}{V_{CC}} - C_L \times N_{SW} \times f_o \right) \times f_i \times N_{SW} + \sum_{n=1}^{N_{sw}} (C_{Ln} + f_{On}) \right)$$

where :

V_{CC} = Supply voltage	C_L = External Load Capacitance
f_i = Input frequency	N_{SW} = Total Number of Outputs switching
	f_o = Output frequency

Theoretically :	5V 3.3 V	$P_{TOT} = - 34 \% ^1)$
Practically :	5V 3.3 V	$P_{TOT} = - 50-70 \% ^2)$

¹⁾ assume that Output-Level V_{OL} and V_{OH} are maintained
²⁾ assume that Output-Level V_{OH} is changing to 3.3 V

HUCJ_ADBSI_logica.ppt Aug96

The answer to the question : "Why 3.3V" is given by the formula for determination of the power consumption related to logic circuits, here as example the formula for CMOS devices (CMOS level inputs) .

A logic circuit's total power consumption, P_{TOT} , is strongly influenced by a number of parameters. If we investigate this formula, we can split this into two parts:


- 1) V_{CC}
- 2) the 'rest' , which is determined by various parameters such as number of outputs, frequency, etc.

Some are inherent to the technology, like the static I_{CC} currents and the so-called "current spike" (I_{SP}), that flows across the output during circuit switching. Others depend on load conditions, operating frequency, and so on.

However, the parameter with the most significant effect on the overall power consumption, is V_{CC} .

The theoretical saving of power dissipation is 34%, if you reduce the voltage from 5V down to 3.3V.

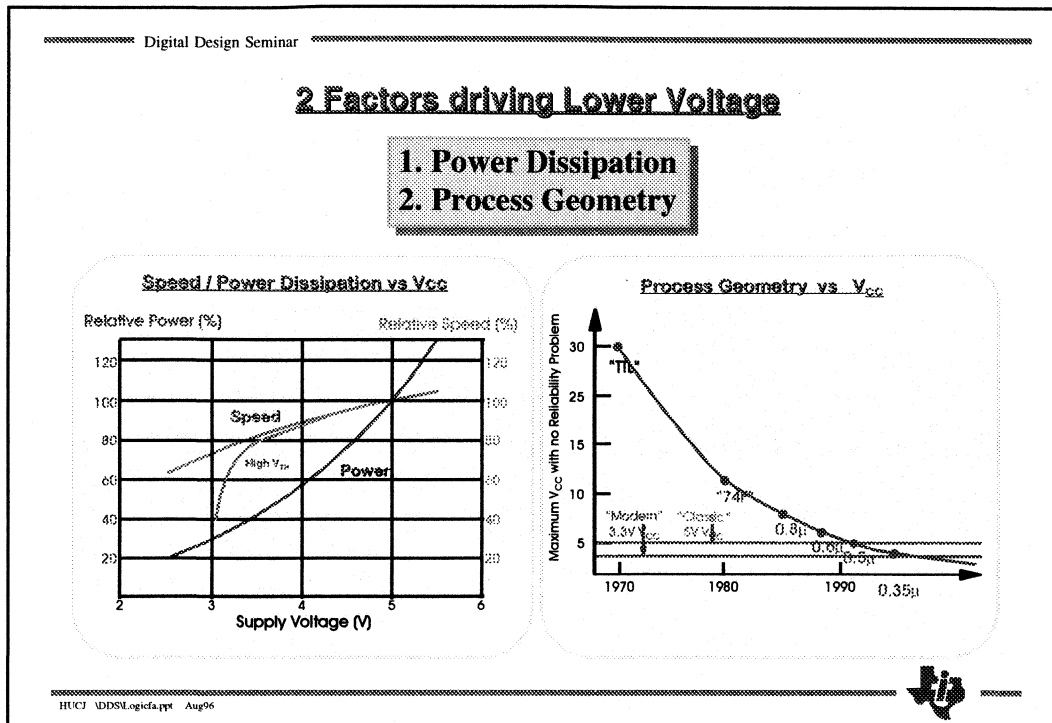Practically, the power saving will be about 50-70%, because other parameters are also improved by reducing the supply voltage.




Changing a system's V_{CC} from 5V to 3.3V by reducing a circuit's supply voltage will worsen its speed. However, as the figure on the left shows, the relative loss of speed is much less than the improvement in power consumption.

Practically, most system designs do not allow for any speed degradation. The way out for suppliers is to use process technologies with smaller feature sizes that (often even over-) compensate the speed loss. This results in the availability of 3.3V logic families that offer the same or higher speeds than the 5V families they replace, in combination with a drastic reduction of the power consumed.

The significant improvement in power consumption is only one reason why there is such a strong momentum in the industry to migrate towards reduced supply voltages.

Another strong push to reduce V_{CC} is driven by the accelerated use of small process geometries. Advanced microprocessors or ASICs sometimes employ several millions of transistors. This demands process feature sizes of 0.5 micron and below. Unfortunately, such small process geometries start to show reliability problems, if operated with a 5V supply voltage. Some types of equipment, e.g. industrial control systems, are therefore frequently forced to change their V_{CC} to 3.3V, although their operating environment would still allow for the high power consumption of 5V designs.

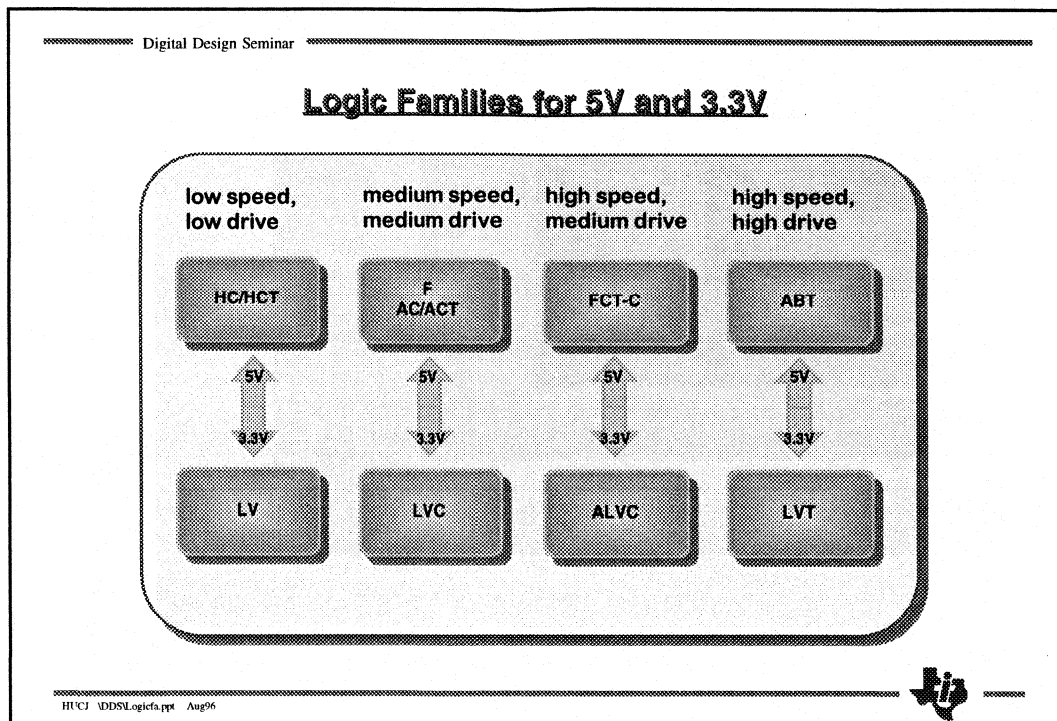

Texas Instruments' Low Voltage Logic families have been designed to provide a performance that is at least equivalent to, but usually even better than, that of commonly used 5V devices.

If you are in the situation to design a new application with 3.3V logic, but are only familiar with the performances of the 5V logic families, this foil will help you.

LV is somewhat comparable to the well-known LS and HC/HCT families, but features improved speed.

LVC addresses the medium performance range, where families like F or AC are predominant in 5V applications.

Two different solutions are available for high performance 3.3V system design:

ALVC combines medium output drive with very high speed performance (unmatched by any other 3.3V logic family).

LVT, which is the 3.3V equivalent to the 5V ABT family of bus interface devices, combines speed with a drive capability that is high enough for reliable operation of large backplanes.

Digital Design Seminar

LVT / LVC / ALVC / LV Comparison

Product Family	SN74LVT	SN74LVC	SN74ALVC	SN74LV
Speed [245 type]	tpd(typ) = 2.4ns tpd(max) = 4.0ns	tpd(typ) = 4.0ns tpd(max) = 6.5ns	tpd(typ) = 2.1ns tpd(max) = 2.9ns	tpd(typ) = 8.0ns tpd(max) = 14.0ns
Drive	IOH = -32mA IOL = 64mA	IOH = -24mA IOL = 24mA	IOH = -24mA IOL = 24mA	IOH = -8mA IOL = 8mA
Current consumption	ICCH/Z = 190µA ICCL = 5mA	ICCH/Z = 10µA	ICCH/Z = 40µA	ICCH/Z = 20µA
Vcc range	← Vcc = 2.7 - 3.6 V →			
Temperature range	← -40 ... +85 degrees Celcius →			
Switching noise	← Ground-Bounce less than 800 mV →			
Package	SOIC / SSOP / TSSOP	SOIC / SSOP / TSSOP	SSOP / TSSOP	SOIC / SSOP / TSSOP
Price Similarity	-ABT	-AC	-FCT	-HC
Special user benefit	<ul style="list-style-type: none"> * Bus hold cells * High impedance at power down * Very low noise * 5V tol. I/O 	<ul style="list-style-type: none"> * Very low noise * 5V tol. I/O * Broad product spectrum incl. Gates/FF/MSI... 	<ul style="list-style-type: none"> * Bus hold cells * Very low noise * pure 3.3 V 	<ul style="list-style-type: none"> * Very low noise * Specification at Vcc=5V available

HUCJ MDSVLlogicfa.ppt Aug'96

These four families of 3.3 V logic devices can be used for portable applications from electronic games up to high performance engineering workstations.

The LVT family is the only low voltage family using BiCMOS technology.


LV, ALVC and LVC families are manufactured in CMOS technology.

The LVC and the LV families are designed for low cost 3V Systems such as consumer equipment, portable computers, electronic games, toys, portable telecom equipment that require medium performance at low cost.

The ALVC family, with a typical propagation delay time of 2 ns has been designed to meet the requirements of high speed systems including engineering workstations and interfaces to SDRAM-modules.

The LVT family, with its high drive capability, can be used for Backplane/Bus Driving applications, high-performance engineering workstations, desktop-PC's and telecom transmission/switching equipments.

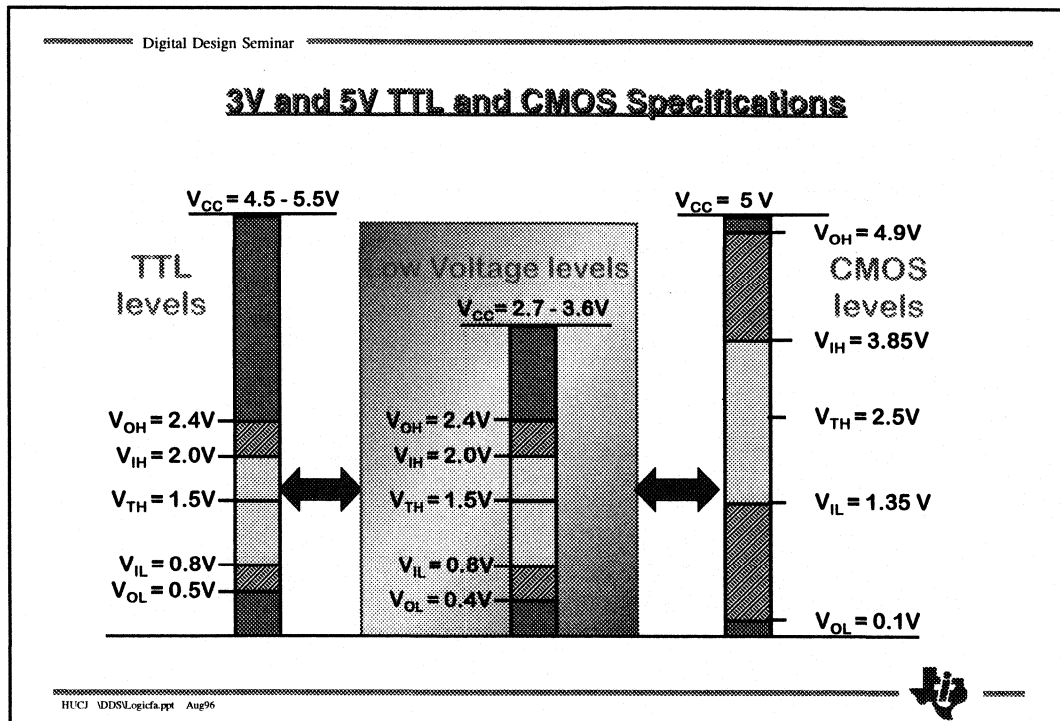TI has second source agreements with Philips and Hitachi for all of these four Low Voltage Logic families. The agreement with Philips has recently been extended to cover other new logic families like ALVT and AHC.



Before discussing the special requirements of mixed mode designs (i.e. systems, where there is a need to interface between the 5V and the 3.3V part), we would like to briefly discuss the different voltage level specifications used in both environments.

During the development of the 3.3V specification in JEDEC, there were basically two "interest groups" endorsing slightly different proposals.


The LV-CMOS proposal was mainly targeted to mobile applications, where battery operation requires a V_{CC} min of 2.7V.

This proposal favoured a concept that basically copied the 5V CMOS one, i.e. an output voltage swing that almost equals V_{CC} , where $V_{OL} \sim 0V$ and $V_{OH} \sim V_{CC}$. This would allow the proper operation of existing 5V CMOS devices from 3.3V ("Scaled CMOS").

On the other hand, the LV-TTL proposal favoured V_O/V_I specifications that are identical with 5V TTL, so that interfacing the two worlds is greatly eased.

Fortunately, the final 3.3V specification agreed upon by JEDEC covers both proposals.

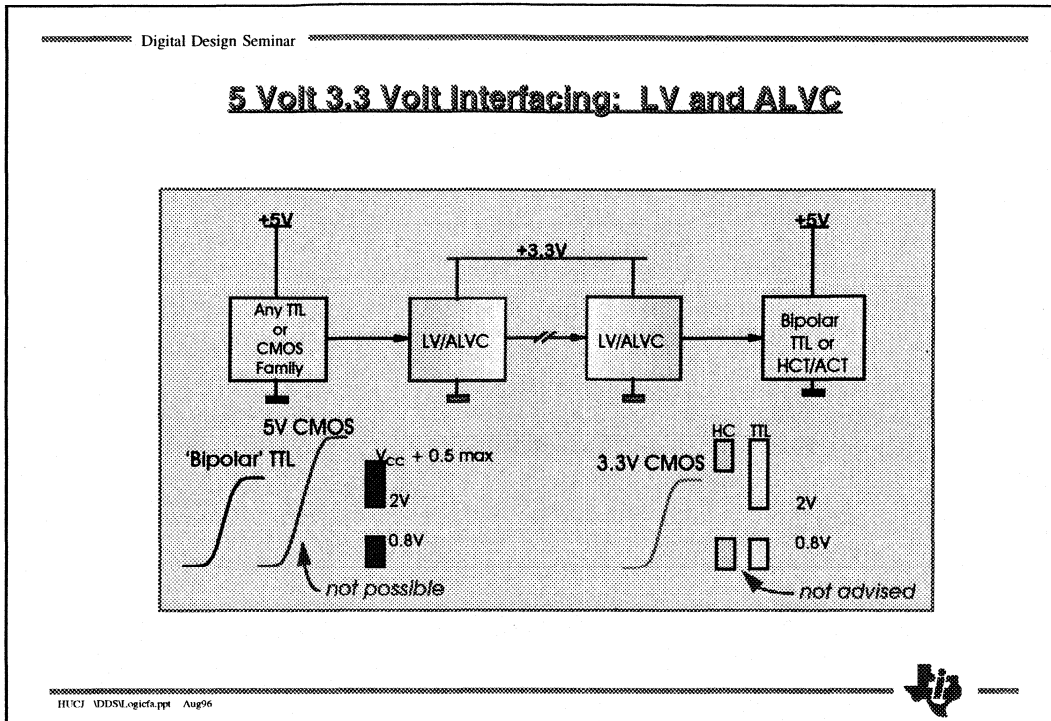It specifies a 2.7-3.6V V_{CC} range, in which the max/min values of the logic input levels are identical with the 5V TTL spec (0.8/2.0V) and max/min values of the logic output levels match the CMOS spec.



As has been explained on the previous page, both LV and ALVC do not allow input voltages higher than $V_{CC} + 0.5V$.


However, this does not necessarily mean that these technologies are unable to interface with 5V signals.

If a 5V TTL signal is applied, its High level will typically be about 3.2V. This does not violate the LV or ALVC inputs specifications. One will have to make sure, however, that no overshoots can occur on the line which might again cause trouble.

On the output side, both LV and ALVC can directly drive 5V inputs that are TTL-compatible. No additional provisions will have to be made.

If the 5V receiver expects to see CMOS levels a special 'Level-Shifter' is required.

5 Volt 3.3 Volt Interfacing: LVT and LVC

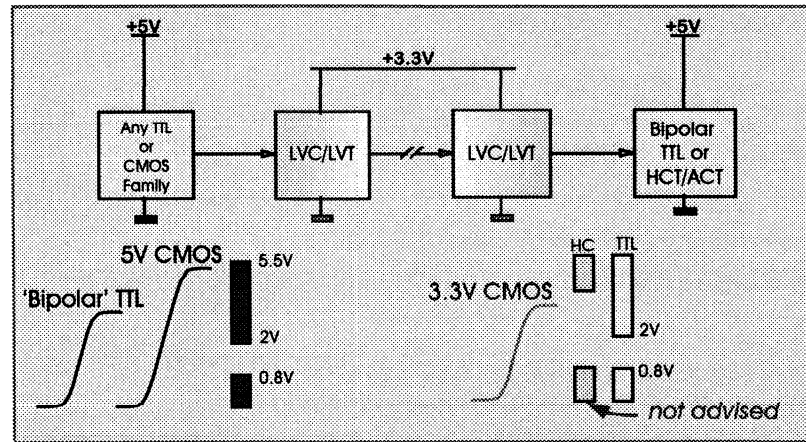

- * LVCxxxA and LVT devices allow direct interface from 5V TTL- and 5V CMOS - devices
- * The direct interfacing to 5 V CMOS is not advised



Both LVC and LVT allow input voltages to go up to 6.5V.

It means that these technologies can interface directly to 5V signals. Care needs to be taken, however, when driving the inputs from a 5V CMOS device, as possible overshoots may lead to the maximum LVC/LVT input voltage being exceeded.

On the output side, LVC and LVT can again (like LV and ALVC) directly drive 5V inputs that are TTL-compatible. No additional provisions will have to be made.

If the 5V receiver expects to see CMOS levels a special 'Level-Shifter' is required.

Digital Design Seminar

Special Level Shifters: 'LVC4245 and 'ALVC164245

'4245 pinning

'245 pinning

The dual V_{CC} level shifters ALVC164245 and LVC4245 have 3.3V and 5V V_{CC} pins (dual V_{CC})

In this way, a full mixed mode system can be designed.

This solution is compatible with a 3.3V-only system: Both can be replaced later with 3.3V parts without PCB redesign

'164245

HUCJ_MDSLogicfa.ppt Aug96


Certain applications will require a 'Level-Shifter' between 3.3V and 5V that can provide 5V output signals. Examples are:

- 1) interfaces to 5V CMOS-level devices which, as shown on the previous page, cannot be operated reliably from 3.3V outputs, or
- 2) 5V memory modules that should be connected to 3.3V components.

In the latter case a designer might want to provide a true 5V input signal to the memory, even if it has a TTL-type input, as the memory circuit's current consumption will otherwise be increased.

In these cases a dual V_{CC} level shifter will be required. This is a device that is connected both to the 5V and the 3.3V supply voltages such that it can independently access to and interface between both sides.

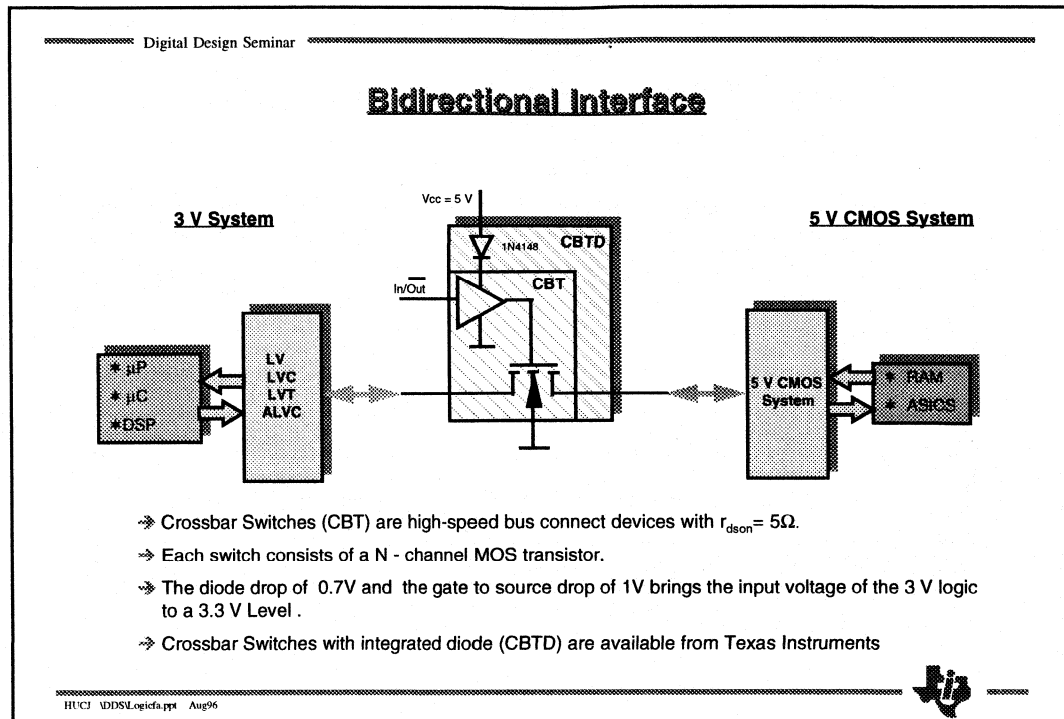Here are two level shifter examples. The LVC4245 is an 8-bit version and the ALVC164245 is a 16-bit version, both with true 5V ↔ 3.3V level translation. Both devices are, or will be, offered by Texas Instruments.



If a device with the capability to switch bus signals on or off is needed, then TI's CBT devices can be used to support easy bus communication.

CBT devices serve a number of unique applications in PC, Workstation, Bus Board, Telecom, Industry and Hard Drive end-equipment markets.

A CBT switch consists of simple n-channel MOS transistors. When the switch is open, it provides isolation (3-state) for the bus line. When the switch is closed, it imposes a near-zero propagation delay on the line (250 ps).

In multiprocessor systems, CBT can be used for extremely fast bus connections, bus exchanges in crossbar systems, memory interleaving, bus byte-swapping and a variety of other switching functions. CBT switches also serve as 5-V to 3.3-V bus translators, helping designers to mix devices of different voltage levels in the same system.

Crossbar Switches with integrated diode (CBTD) are available from Texas Instruments.

Extremely low propagation delays of 250 ps make CBT devices an effective replacement for drivers and receivers in high-speed systems, where signal buffering is not required.


In addition, low power consumption helps to improve battery life in portable systems. Small foot-print packages save board space.

Digital Design Seminar

5 Volt ↔ 3.3 Volt Interfacing Capability

to \ from	SN74LVT	SN74LVC	SN74ALVC	SN74LV	5V CMOS (CMOS levels)	5V TTL, ACT/ HCT/AHCT
SN74LVT	✓	✓	✓	✓	use pull-up resistor to 5V	✓
SN74LVC	✓	✓	✓	✓	use pull-up resistor to 5V	✓
SN74ALVC	✓	✓	✓	✓	use Levelshifter '4245 or 164245	✓
SN74LV	✓	✓	✓	✓	use Levelshifter '4245 or 164245	✓ *
5V CMOS (HC/AC/AHC/.)	✓	✓	use input voltage divider	use input voltage divider	✓	✓ *
5V TTL (ALS/F/AS/.)	✓	✓	✓	✓	use pull-up resistor to 5V	✓
ACT/HCT	✓	✓	use input voltage divider	use input voltage divider	✓	✓ *

* limited by output drive capability of HC(T), AHC(T), LV



HUJ DDSLgrcfa.ppt Aug'96

Four different signal level constellations may have to be addressed in mixed mode design:

- 5V TTL → 3.3V TTL
- 3.3V TTL → 5V TTL
- 5V CMOS → 3.3V TTL
- 3.3V TTL → 5V CMOS

While the first two are very easy to address, the last two are difficult, as a certain technology may not support their requirements. LVC and LVT have I/Os that are 5V CMOS-tolerant. Interfacing a 3.3V part to a 5V system that expects CMOS levels, however, usually requires a dedicated level shifter. CMOS levels are specified as follows:

$$V_{IL} = 0.3 \times V_{CC}$$

$$V_{IH} = 0.7 \times V_{CC}$$

The driver should at least be able to deliver:

$$V_{OL} < 0.3 \times V_{CCmin} = 1.35V \text{ (with } V_{CCmin} = 4.5V)$$


$$V_{OH} > 0.7 \times V_{CCmax} = 3.85V \text{ (with } V_{CCmax} = 5.5V)$$

This also implies that a standard 3.3V output does not deliver a high enough output voltage to reliably drive 5V CMOS inputs.

Even with a pull-up resistor

$$V_{Omax} = V_{CCmin} + 0.7V \text{ (diode)} = 3.7V < 3.85V$$

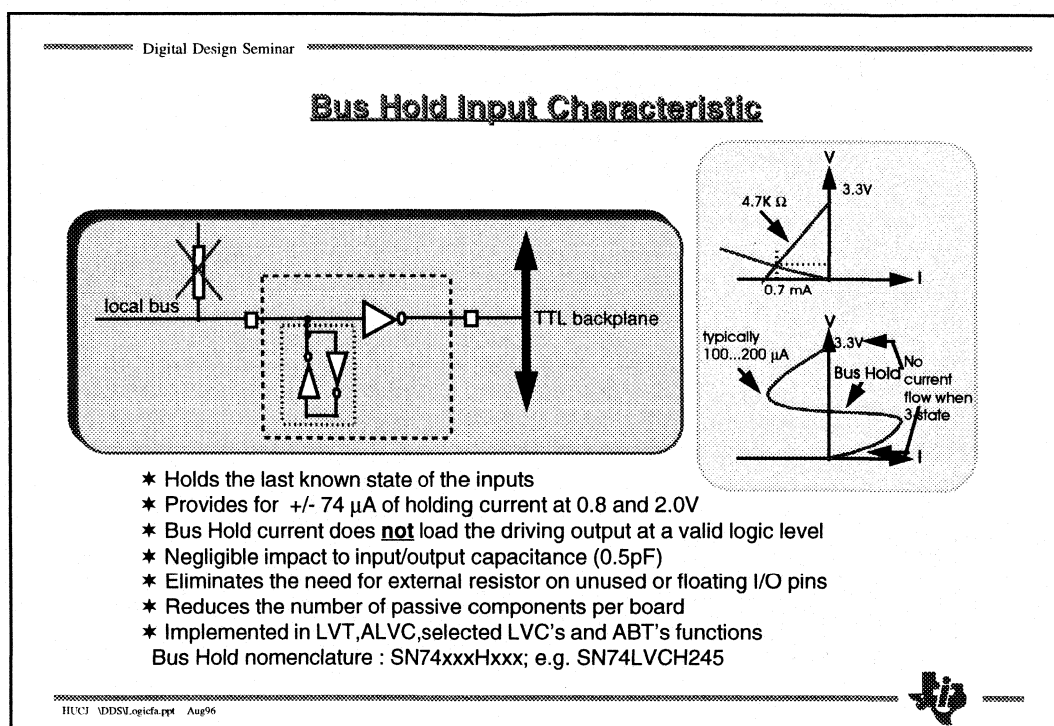the result is the following: a special 'Level-Shifter' is required.



TI has addressed many important design issues including testability, memory driving, bus termination, low skew requirements, and low-impedance line driving with specialized, advanced logic devices that improve overall system performance.

This figure shows the typical V-I characteristics of a bus line with pull-up resistors versus a bus line using a bus interface device with integrated bus hold. The bus hold circuit basically consists of a non-inverting driver that will drive a small current (typically peak value is about 100-200 μA) back into the bus, to pull it back to proper signal levels, if the bus is floating.

As can be seen, the pull-up solution causes a constant current to flow on both ends. The bus hold circuit, on the other hand, not only consumes much less current, but also does not represent any static loading to the bus. This means that it will not consume any current, as long as the bus is at a proper Low or High level.

The Bus Hold feature has been implemented in the LVT and ALVC family as well as in selected LVC and ABT functions.

Look for the 'H' within a device nomenclature.

Series Termination - Devices

- * Series Resistor at Outputstage
- * Short propagation delays & low power consumption
- * Supports highest system performance and use of slower memories
- * Reduces component count, board space, mounting costs

Function	Description	Family				Function	Description	Family			
		ABT	LVTH	ALVC	LVC			ABT	LVTH	ALVC	LVC
'2240	8-bit mem. drv.	✓				'162374	16-bit D-flip-flop		✓	✓ ¹	
'2241	8-bit mem. drv.	✓				'R162409	9-bit, 4-port bus exchr.				✓
'2244	8-bit mem. drv.	✓			✓	'162460	4 to 1 bit mem. drv/mux.	✓			
'2245	8-bit mem. drv.	✓			✓	'162500	18-bit memory UBT™	✓			
'5400	11-bit mem. drv.	✓				'162501	18-bit memory UBT™	✓			
'5401	11-bit mem. drv.	✓				'162525	18-bit reg. bus trans.				✓
'5402	12-bit mem. drv.	✓				'162540	16-bit buffer drv.		✓ ¹	✓ ¹	
'5403	12-bit mem. drv.	✓				'162541	16-bit buffer drv.		✓ ¹	✓ ¹	
'162240	16-bit mem. drv.			✓ ¹⁾		'162601	18-bit memory UBT™	✓	✓ ¹		✓
'162241	16-bit mem. drv.		✓ ¹			'162721	20-bit D-fl. clk enable				✓
'162244	16-bit mem. drv.	✓	✓	✓	✓	'162820	10-bit FF w dual Output	✓			✓
'(R)162245	16-bit mem. drv.	✓	✓	✓	✓	'162823	18-bit Bus Interf. FF	✓			
'162260	12 to 24-bit mem. drv/mux.	✓				'162825	18-bit mem. drv.	✓			✓ ¹
'162268	12 to 24-bit reg. bus exchr.			✓		'162827	20-bit mem. drv.	✓			✓
'R162269	12 to 24-bit reg. bus exchr.			✓		'162830	1-2 addr. drv.				✓ ¹
'162344	8-bit 1:4 addr. line drv.			✓ ¹⁾		'162831	1-4 addr. drv.				✓ ¹
'162373	16-bit transp. latch		✓	✓ ¹⁾							

¹⁾planned



One line termination technique, which was already mentioned earlier is the so-called Series Termination.

As opposed to most other termination techniques (where the lines are terminated at the end), here the driver output impedance is matched with the line impedance by adding a series resistor. This means that no reflection will occur on the driver side.

It is thus a very efficient method for a point-to-point connection, or for a line driving a concentrated load. This technique is especially useful when driving memory array address lines as it suppresses signal under- and overshoots which may otherwise lead to data loss.

Several 5-V and 3.3-V logic devices are available with an integrated output resistor. The resistor value is typically around 25Ω, leading to an effective output resistance of about 33Ω.


As a certain impedance mismatch is acceptable, these circuits will be feasible for line impedances up to approximately 75Ω.

..... Digital Design Seminar

Texas Instruments IEEE 1149.1 Products

Boundary scan products allow easy test of high-density boards

- * SCOPE™ bus drivers support most applications demanding boundary scan functions
- * Path support functions allow easy handling of scan path's in large systems

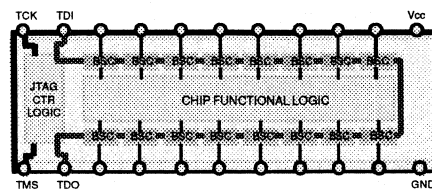

IEEE1149.1 was developed by the Joint Test Action Group (JTAG)

SCOPE (System Controllability Observability Partitioning Environment)
is a trademark of Texas Instruments Incorporated

Benefits using IEEE1149.1

- * Test node access on high-density board
- * Inexpensive test adapters
- * Std interface for ICs, boards, systems
- * Easy to implement in ASICs
- * Broad spectrum of bus driver functions
- * 3.3-volt drivers already on the market
- * Support from IC and ATE vendors

Product features

- * State-of-the-art techniques used
- * Popular bus driver functions available
- * 3.3-volt versions
- * Universal-Bus-Transceivers available
- * Functions available for large systems

..... HUCJ \DDSL\Logicfa.ppt Aug96



Scope™ products from Texas Instruments comply with the IEEE1149.1 specification. Scope products are offered in BICMOS technology (ABT and LVT) and Advanced CMOS (ACT).

The nomenclature includes an '8' to express its testability feature (e.g SN74ABT8245, which is a '245 function additionally supporting testability (IEEE1149.1).

The widebus devices including this feature can be recognized with '18' instead of '16' (e.g SN74.LVT18502).

The generic IEEE1149.1 function:

Between each IC pin (input and output) and the chip functional logic there is a boundary scan cell (BSC).


All BSCs are connected to a serial scan path with the function of a shift register.

The BSCs are to be controlled via 4 control pins: TCK (test clock), TMS (test mode select), TDI (test data input), TDO (test data output).

The BSC allows capturing data from and providing data to the chip data path.

Potential Problems in Live Insertion Applications

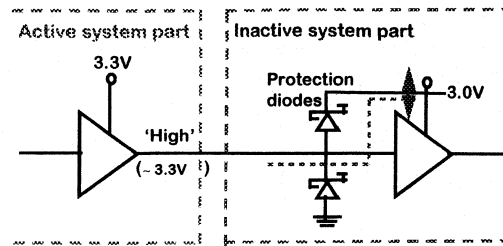- ◆ Unexpected device behaviour during power up or power down causes malfunction
- ◆ Input signals start sourcing circuitry through input protection diodes



Along with the power reduction trend that drove the transition to 3.3V, live insertion has become of much more interest in system design. Also, so-called “partial power down” is being applied more frequently, where the supply voltage V_{CC} will be switched off in certain parts of the system, while these are not in use.

In both cases (live insertion and partial power down), there are two potential problems that need to be addressed. First, there is a risk of unexpected device behaviour during the power transition. All logic circuits available in the market have specifications that guarantee proper circuit operation only within a certain V_{CC} range. During power up or power down, the circuit will be operated outside this range, which may lead to an unpredictable device response. For example, the output may start sinking large currents or, worst case, even start oscillating.

Second, the block diagram shows a constellation, where an active device output is connected to a device, whose V_{CC} has been switched off. In this special case, the inactive circuit uses protection diodes as its inputs. This method is being used in many CMOS circuits for ESD protection. Unfortunately, a high signal applied to this input will be fed to the circuit's V_{CC} connection via the protection diode. The V_{CC} level of the inactive circuit will be about 3.0V, which is high enough to activate this circuit and (via the V_{CC} path) the remaining devices in the inactive system part. This may result in all kinds of unexpected system behaviour.

Live Insertion Support Aspects of Logic Families

	HC/ HCT	AC/ ACT	ALS/ F/AS	ABT	LV	LVC/ ALVC	LVT
Diode connects Inputs to V_{CC} if $V_{CC}=0V$	X	X	---	---	X	---	---
Diode connects Outputs to V_{CC} if $V_{CC}=0V$	X	X	---	---	X	---	---
V_{CC} above which the circuit will typically work*	1.5V	2V	3.5V	2.5V	1.5V	2V	1.8V
Outputs will be tri-stated below this limit				✓			✓


* Circuit will be functional but may still be outside AC specifications



This table illustrates the feasibility of using certain logic families for live insertion applications.

As can be seen, the 5V families HC/HCT and AC/ACT, as well as the 3.3V family LV, will be difficult to use in any live insertion applications. This is mainly, because they all use protection diodes that connect the inputs and outputs to V_{CC} .

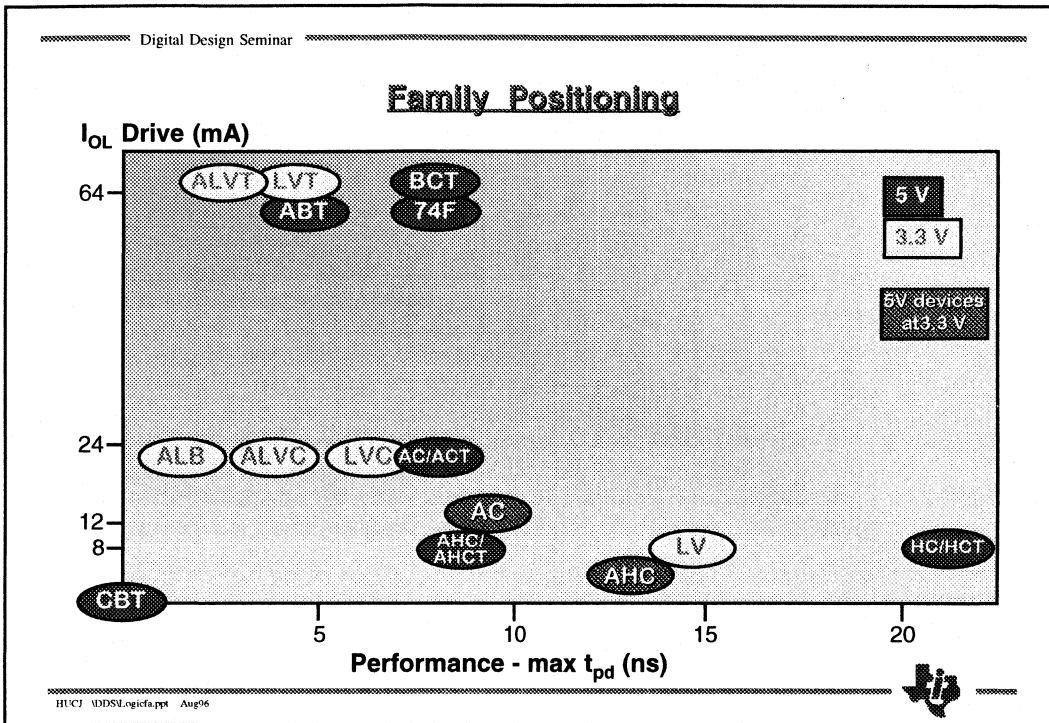Those families that do not use protection diodes to V_{CC} will be easier to design with. However, only 5V ABT and 3.3V LVT circuits feature full live insertion support, as they also comprise a "power-up 3-state" circuitry that will 3-state the device outputs, if V_{CC} is below a certain limit. A system designer can thus easily design interfaces that allow reliable power-down operation.



Plotting I_{OL} vs t_{pd} we see that the 3.3V families (ALB, LV, LVC, ALVC, LVT and ALVT) and the 5V logic families (ABT, AC/T, AHC/T and CBT) cover the whole range of required performance nodes.

For reference, some 5-V families (AHC and AC) are also shown with their performance parameters, when operated with 3.3V.

..... Digital Design Seminar

Metastability

..... FOPE \DDS\Metastab.ppt Jan07



Digital Design Seminar

The Synchronization Problem

The diagram shows a box labeled 'DATA SOURCE' on the left and a box labeled 'MICROPROCESSOR SYSTEM' on the right. Two arrows labeled 'DATA' and 'STROBE' point from the 'DATA SOURCE' to the 'MICROPROCESSOR SYSTEM'. Inside the 'MICROPROCESSOR SYSTEM' box, there is a flip-flop symbol with 'D' and 'Q' inputs and 'SYSTEM CLOCK' and 'Q' outputs.

- ★ **Microprocessors are synchronous systems.**
- ★ **Data sources (peripheral devices, memories, etc.) provide data mostly asynchronously with respect to the microprocessor.**
- ★ **Therefore the control signals of the data source have to be synchronized to the system clock.**
- ★ **In synchronization circuits the timing requirements of flip-flops (t_{su} , t_h) are violated.**

FOPE \DDSMetastab.ppt Jan97


Standard microprocessor systems are synchronous systems, which means that there is a common clock signal that feeds the clock inputs of all flip-flops in the system. Under these circumstances it's easy to fulfill the set-up and hold-time requirements of all flip-flops.

It's a common situation that external data has to be transferred into a microprocessor system and mostly the external equipment is running asynchronously to the clock of the microprocessor system. In this situation it's usual to put the new data-word onto the data-lines and use a separate strobe line to indicate the presence of the new data. Anywhere within the microprocessor this strobe signal will be stored in a flip-flop, whose clock is synchronous to the microprocessor clock.

Under these circumstances the designer can not ensure that the set-up or hold-time requirements of this flip-flop will be fulfilled. If a violation of the set-up or hold-time takes place, the manufacturer of the flip-flop will no longer guarantee proper function and the system may malfunction.

Digital Design Seminar

Metastable behaviour

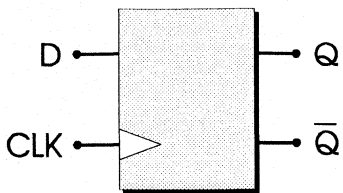


Critical time window $t_d = 10... 150 \text{ ps}$

$$MTBF = \frac{1}{f_{in} \times f_{CLK} \times t_d}$$

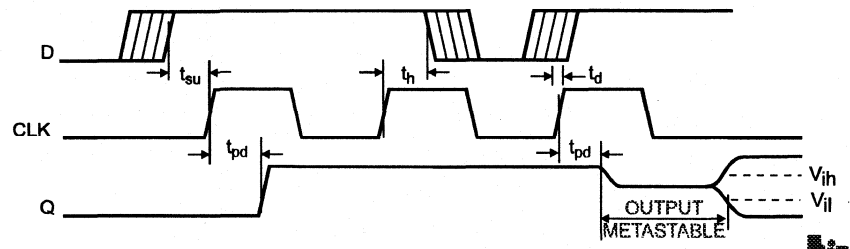Example:

$$MTBF = \frac{1}{1 \text{ kHz} \times 1 \text{ MHz} \times 30 \text{ ps}} = 33.3 \text{ s}$$



FOPE UDSM:Metastab.ppt Jan97

Every flip-flop data-sheet specifies a set-up and a hold time. The set-up and hold-time define a time window around the active (mostly rising) edge of the clock signal, where it is not allowed to change the signal at the D-input. If the signal at the D-input changes within the forbidden set-up and hold-time window, one of two reactions of the flip-flop can be observed:

- 1) The flip-flop works perfectly with no special behaviour
- 2) The output of the flip-flop becomes metastable


If the output of a flip-flop is metastable, the voltage value V_O is higher than the V_{il} low-level-limit, but lower than the high-level-limit V_{ih} . It is in the forbidden area between low and high. This situation can last less than 1ns, but could also last longer than 30ns. This normally is a major problem for the input of the circuit that gets its signal from this metastable flip-flop.

Because it's not possible to avoid this situation by design, the only way to deal with it is statistically. The value used here is MTBF (Meantime between failure) and can be calculated using the following formula:

$$MTBF = \frac{1}{f_{in} \times f_{CLK} \times t_d}$$

- with f_{in} : Data rate at D-input
 f_{CLK} : Clock frequency
 t_d : Critical time window

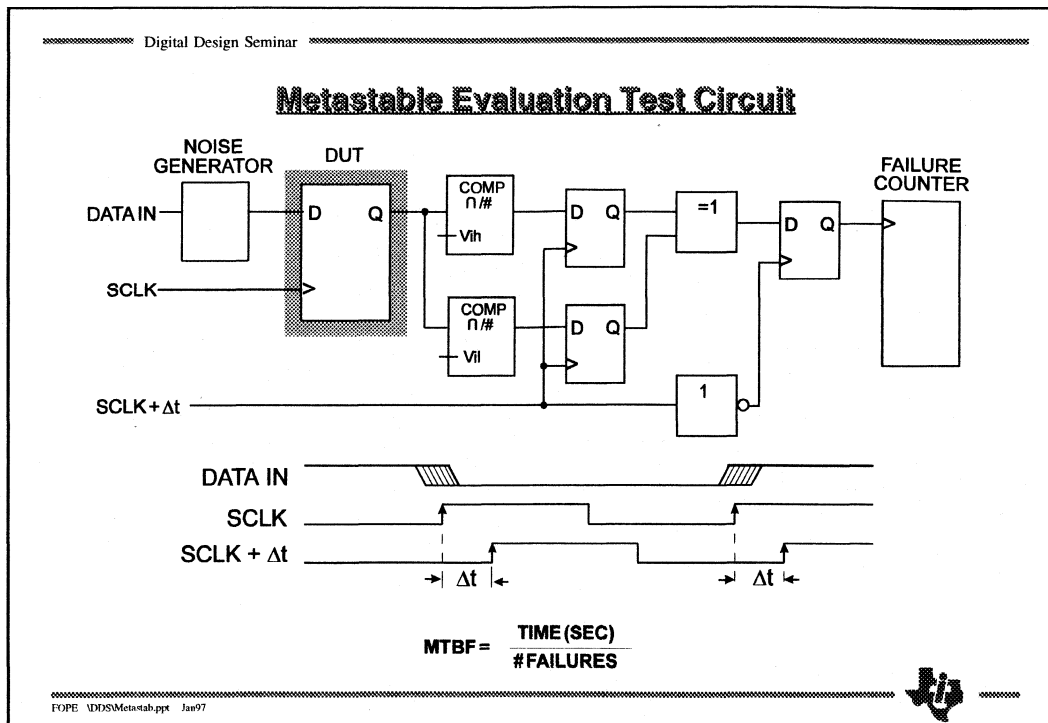The set-up and hold-time window is a time window guaranteed by the manufacturer of the flip-flop, guaranteed over the temperature range, supply voltage range and production variations. If the signal at the D-input changes within the critical time windows t_d , then the flip-flop will become metastable. The above example with $MTBF = 33.3\text{s}$ shows a unacceptable situation.




To find out the metastable behaviour of the flip-flops from Texas Instruments, the applications lab has made measurements with the above setup:

The flip-flop under test (DUT) gets a stable clock signal and a data signal with some jitter. The output of the flip-flop is connected to two comparators, one for the comparison against a valid logic high level V_{ih} and one for the valid logic low level V_{il} . The result of this comparison is stored in two flip-flops, whose clock signal is the delayed clock of the tested flip-flop (DUT). The following EXOR gate filters the errors and sends them to a ordinary counter.

With the amount of delay that is added to the clock signal of the two comparators flip-flops, we give some time to the tested flip-flop to make the decision between a logic high- and low-level. If the flip-flop wasn't able to make this decision within the specified time-frame, and the output of the flip-flop is still within the forbidden voltage area, a metastable state will be counted with the failure counter.

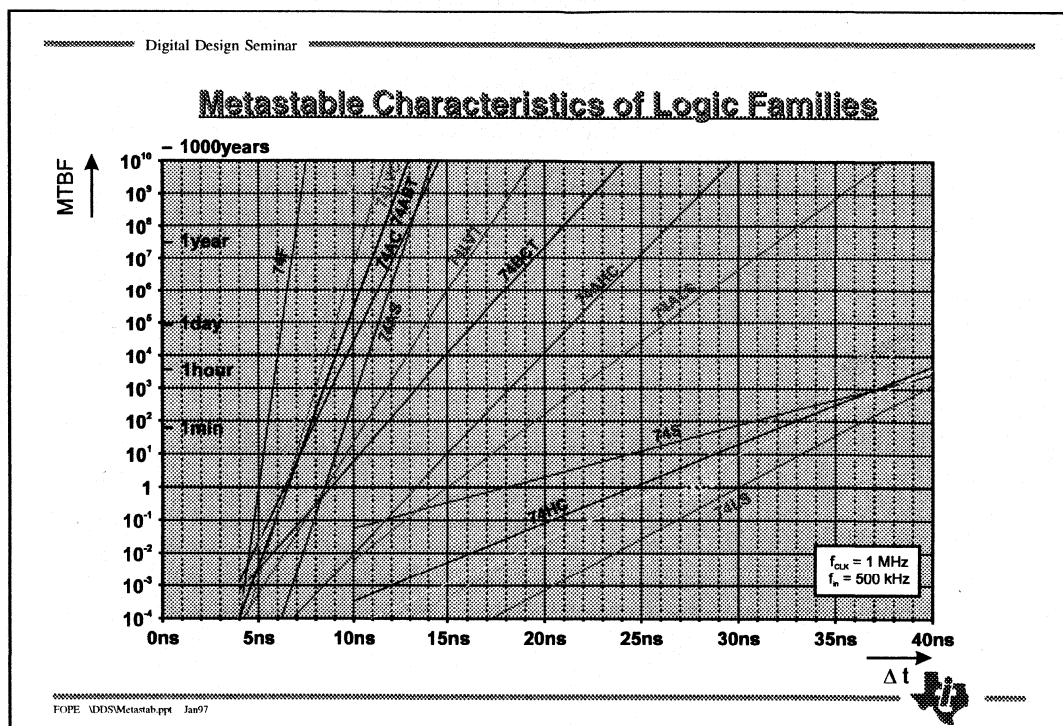Some of these tests have to be running over several days to find a reasonable number of metastable conditions.



The Applications Lab of Texas Instruments measured the flip-flop of all available product families with the test set-up described one page before. The result of these measurements can be seen in the above diagram.

In X-direction the diagram shows Δt , the time-frame the flip-flop gets to make a decision for high or low, and the Y-axis applies to the resulting meantime between failure (MTBF) rate.

These curves have been measured with a clock frequency of 1MHz and an input data rate of 500 kHz.

Mean Time between Failures of a Synchronizer

$$MTBF = \frac{e^{(T \times \Delta t)}}{f_{in} \times f_{CLK} \times T_0}$$

- ★ There is no way to avoid metastable states in synchronization circuits.
- ★ Fast Logic Circuits return quicker from a metastable to a stable state.
- ★ The probability of system failures is greatly reduced by a delayed test of the synchronization circuit.

	T [ns ⁻¹]	T ₀ [s]
74STD	0.74	2.9E-4
74LS	0.72	4.8E-3
74S	0.36	1.3E-9
74ALS	1.02	8.8E-6
74AS	4.03	1.4E3
74F	9.20	1.9E8
74BCT	1.51	1.14E-6
47ABT	3.61	0.033
74HC	0.55	1.48E-6
74AHC	1.41	2.9E-4
74AC	2.80	1.1E-4
74LV	0.60	1.38E-5
74LVC	4.40	4.008
74ALVC	4.60	1.047
74LVT	2.13	1.52E-4



The following equation is the mathematical representation of the graphs on the previous page:

$$MTBF = \frac{e^{(T \times \Delta t)}}{f_{in} \times f_{CLK} \times T_0}$$

- with f_{in} : Data rate at D-input
 f_{CLK} : Clock frequency
 T and T_0 : Constants describing the device family characteristics
 Δt : time for the flip-flop to decide between high or low

With this equation it's possible to calculate the MTBF rate of a specific circuit design.

Digital Design Seminar

Calculation of System Reliability

```

graph LR
    LM[LOCAL MEMORY] <--> CPU[CPU]
    CPU <--> GM[GLOBAL MEMORY]
    subgraph Synchronous
        LM
    end
    subgraph Asynchronous
        GM
    end
  
```

Assumptions: System clock rate 10 MHz
Average access rate to the global memory 100 kHz
Logic family SN74ALS

Required: Mean time between failure > 100 years


$$100 \text{ years} = 3.2 \times 10^9 \text{ s} = \frac{e^{(1.02 \text{ ns}^{-1} \times \Delta t)}}{100 \text{ kHz} \times 10 \text{ Mhz} \times 8.8 \times 10^{-6} \text{ s}}$$

$\Delta t = 37 \text{ ns}$

To meet the required system reliability, the test of the synchronization circuit output signal has to be delayed by 37 ns.


FOPE \DDSMetastab.ppt Jan97

In the above example a CPU, running with 10MHz clock frequency, accesses a external global memory with an average data-rate of 100kHz. The designer wants to use a SN74ALS flip-flop and needs a meantime between failure rate of 100 years. Using the equation of the page before, Δt can be calculated to be 37 ns. This means, that if the CPU waits 37ns after the active clock edge before it looks at the output of the SN74ALS flip-flop, an MTBF rate of 100 years is achieved.

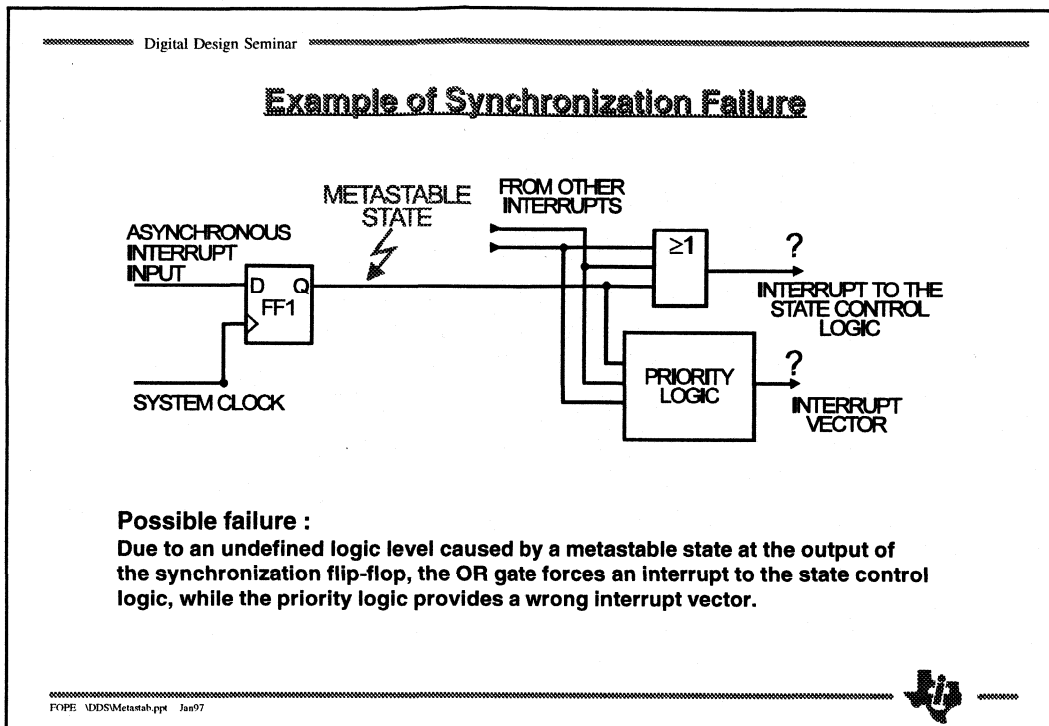

In the first example (page 3-2) the metastable states could be supervised by intelligent software: The CPU looks at the STROBE signal twice before it accepts the logic state.


The example above shows a situation where metastability must be solved by hardware. Assume the output of the interrupt flip-flop is metastable and correspondingly the logic level is undefined. The gate that sends the interrupt to the CPU can detect a valid interrupt while the priority logic takes the same signal and decides that there is actually no interrupt. Therefore an interrupt occurs, but no interrupt (or a wrong) vector is sent to the CPU. In this case the CPU will jump to a no existing interrupt service routine and a system crash will be the result.

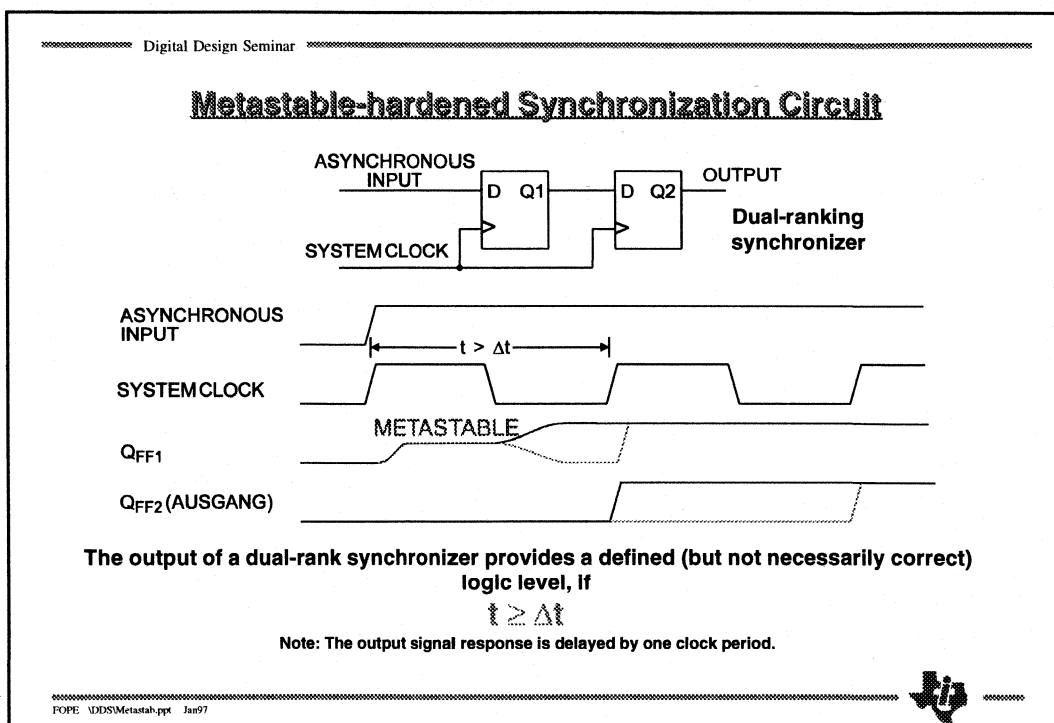

To increase the MTBF rate a further circuit design method is available: The Dual-Rank Synchronizer. Here we take two flip-flops and connect them as a shift-register. In this case the output of the second flip-flop will be less often in a metastable condition than the output of the first flip-flop. Three situations can occur when flip-flop 1 is in metastable state:

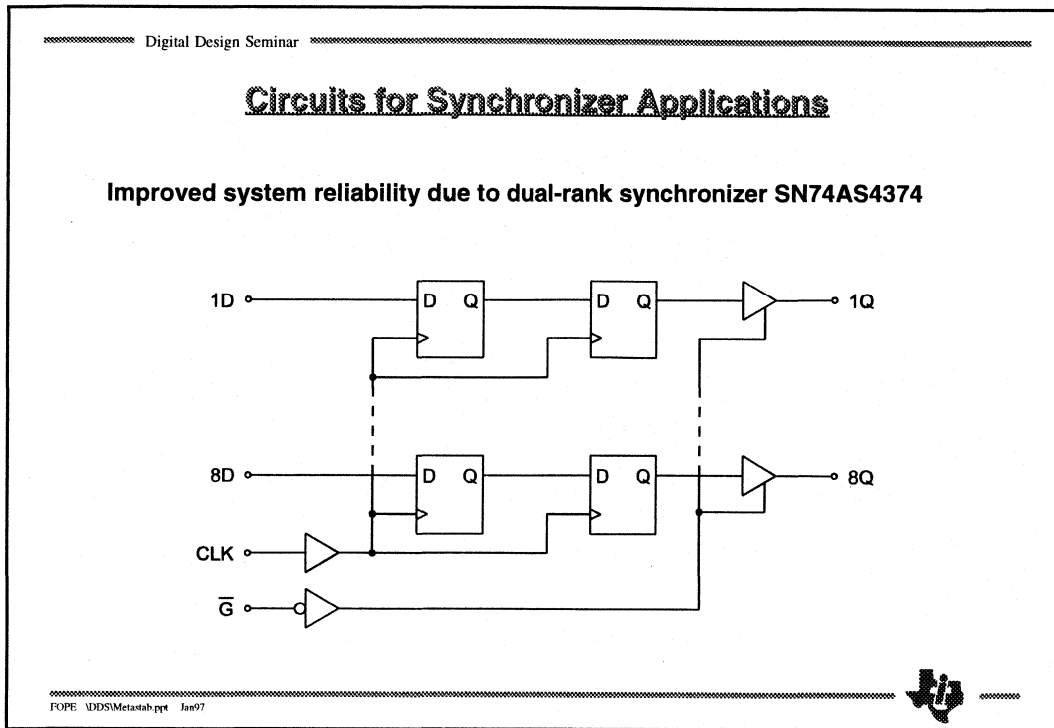- 1) The metastable state of the first flip-flop is short enough, so at the next rising edge of the clock signal the second flip-flop already gets a good signal at its D-input.
- 2) The metastable state of the first flip-flop lasts longer than one clock period, but the second flip-flop accepts the undefined signal as a valid high or low state.
- 3) The metastable state of the first flip-flop lasts longer than one clock period and the second flip-flop becomes metastable, too.

In the first two cases the output of the second flip-flop is not metastable, while the first one is metastable. This shows the reduction of metastable states with this circuit.



Because dual-rank synchronizers are a common way to reduce the occurrence of metastable states, Texas Instruments invented the SN74AS4374. This circuit has nearly the same function as the well known octal flip-flop SN74AS374, with the only difference that there is a dual-rank synchronizer instead of a single flip-flop in each data-path. Here no extra board space and no redesign is necessary to upgrade a single flip-flop synchronizer to a dual-rank synchronizer.

Digital Design Seminar

Mean Time between Failure of a Dual-rank Synchronizer

$$MTBF(2) = \frac{e^{(T \times \Delta t)}}{f_{in(2)} \times f_{CLK} \times T_0}$$

$$f_{in(2)} = \frac{1}{MTBF(1)}$$

$$= \frac{f_{in(1)} \times f_{CLK} \times T_0}{e^{(T \times 1/f_{CLK})}}$$

$$MTBF(2) = \frac{e^{(T \times t)} \times e^{(T \times 1/f_{CLK})}}{f_{in(1)} \times f_{CLK}^2 \times T_0^2}$$

Note: The flip-flop (2) will only fall into a metastable state, if the output of flip-flop (1) violates the timing requirements at the input of flip-flop (2)

FOPE \DDSMetastab.ppt Jan97

To calculate the MTBF rate of a dual rank synchronizer only the metastability of the second flip-flop is of interest. Here we use the previously discussed formula:

$$MTBF = \frac{e^{(T \times \Delta t)}}{f_{in} \times f_{CLK} \times T_0}$$

It's not possible to generate a metastable state at the output of the second flip-flop if the first flip-flop is working well. To drive the second flip-flop into metastable condition a metastable state of the first flip-flop is necessary. Hence the input data of flip-flop two that is of interest regarding metastability is only the situation where the first flip-flop is metastable. So the reciprocal MTBF value of the first flip-flop can be used as input data rate of the second flip-flop.


$$f_{in(2)} = \frac{1}{MTBF(1)} = \frac{f_{in(1)} \times f_{CLK} \times T_0}{e^{(T \times 1/f_{CLK})}}$$

Now the final formula can be calculated:



$$MTBF(2) = \frac{e^{(T \times t)} \times e^{(T \times 1/f_{CLK})}}{f_{in(1)} \times f_{CLK}^2 \times T_0^2}$$

Reliability of Clocked FIFOs

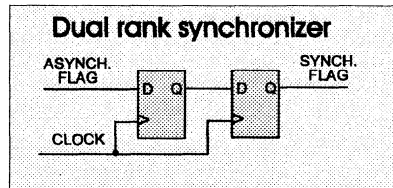Multi-Stage Flag Synchronization reduces the Probability of Metastable States



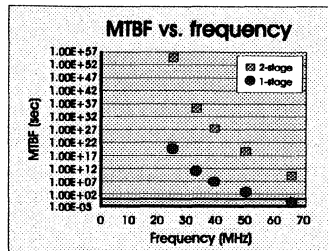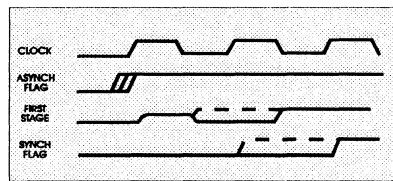Second flip-flop stage filters metastable events from first stage, increasing the MTBF by several orders of magnitude.



Texas Instruments offers FIFO (first-in-first-out) memories. One key feature here is the possibility of asynchronous write and read operations. This is a product where metastability is a major issue and Texas Instruments uses at least dual-rank synchronizers to avoid metastable conditions at the outputs.

During the design phase investigations took place to find out the MTBF rate of FIFOs with and without dual-rank synchronizers. The result of these investigations can be seen in above diagram. For example at a clock frequency of 50 MHz the single flip-flop synchronizer shows a MTBF rate in the range of several minutes, while the dual-rank synchronizer is in the range of 10^{19} seconds or 3.17×10^{11} years.


This example shows the tremendous improvement this type of circuit design can achieve regarding metastable behaviour.

..... Digital Design Seminar

System Design Criteria

.....
GEBE \DDS\Criteria.ppt Feb97



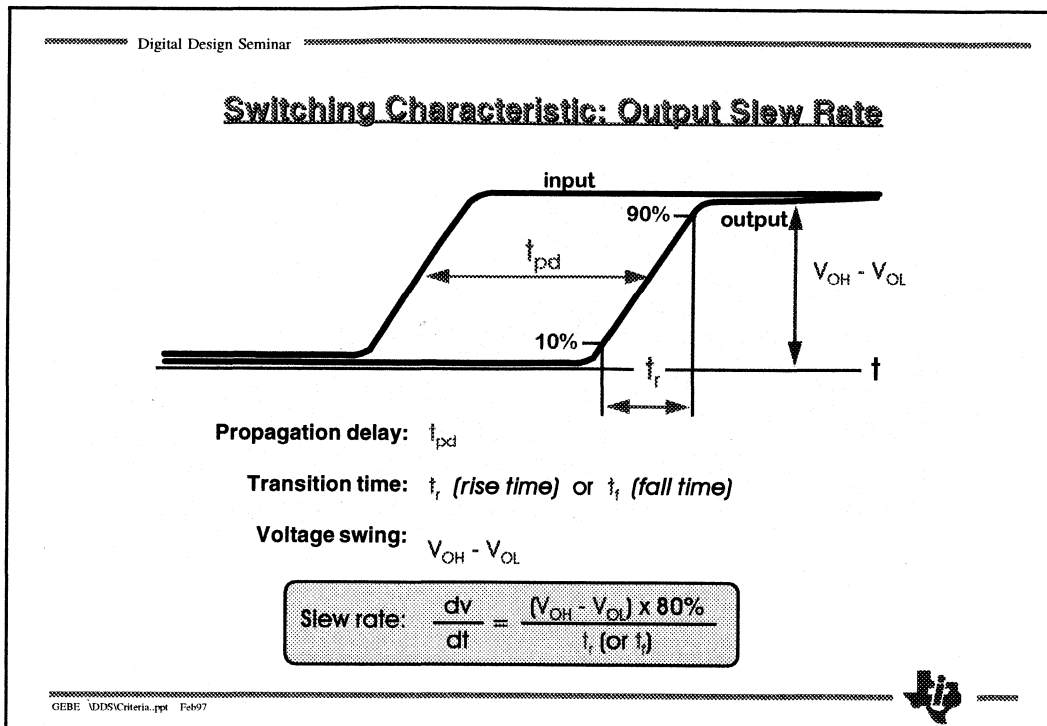

Noise in digital logic systems arises from different sources:

- External noise radiated into the system
- Power-line noise coupled through the AC and DC power distribution system
- Cross talk induced into signal lines from adjacent signal lines
- Signal- and supply-current spikes caused by switching several loads
- Transmission-line reflection from unterminated transmission lines.

A major noise source is the integrated circuit, simply because of its high-speed switching.

As can be seen from the formula, a circuit's slew rate corresponds to the transition (rise or fall) time of the output signal. The shorter the rise or fall time, the higher the slew rate.

Knowing about the slew rate is a good way to get a rough estimation on the noise potential of the device in use. However, keep in mind that propagation delay and slew rate are not necessarily proportional.


Digital Design Seminar

Switching Characteristic
Slew Rate - 5-V and 3.3-V Logic

	F	ALS	ABT	AC	HC	AHC	AHC	LVT	ALVC	LVC	LV	
Propagation delay	4	6	2.7	5	13	5.5	8.3	2.4	2.0	4.5	10	ns
Voltage Swing	3	3	3	4.8	4.8	4.8	3	3	3	3	3	V
Slew Rate	1.3	1.0	1.0	2.0	0.9	0.8	0.5	1.2	1.3	0.9	0.7	V/ns
	V _{cc} = 5 V						V _{cc} = 3.3 V					

◆ Example: '244 function ('16244 in case of ALVC), outputs loaded with 500 Ω/50 pF; all values are typical

◆ Slew rate values shown are the higher ones of rising and falling edge of output signal



GEBE VDS/Criteria.ppt Feb97


This table shows the propagation delay, t_{pd} , voltage swing, ($V_{OH} - V_{OL}$), slew rate, and dv/dt for selected logic families. HC, AHC, ALS, AC, F and ABT operate from a 5V supply voltage, while AHC, LV, LVC, LVT and ALVC have a 3.3V supply. The data indicates that t_{pd} and dv/dt show common trends (the shorter the propagation delay, the higher the slew rate). However, there is no direct link between the two parameters. In particular, the fastest family is not the one with the highest slew rate.

This must be considered especially when designing high speed systems. As will be discussed later in this section, high slew rates are very unfavorable as they design in high noise levels generated by the components. The worst technology in this respect is 5V AC. All of the low voltage technologies have somewhat lower signal slew rates.


It should be especially noted that ALVC, the fastest of all technologies shown, exhibits a comparably low slew rate. This is due to appropriate circuit design techniques and the SSOP/TSSOP package technology used for these 16- to 20-bit bus interface functions.


Digital Design Seminar

Slow Input Signals (1)

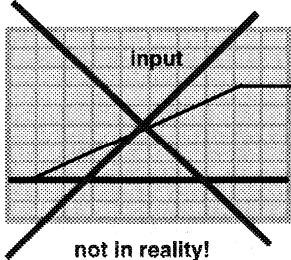


not in reality!

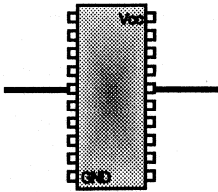

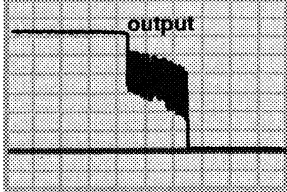

Slow input signals can cause oscillations both on the output and input side because of induced chip-internal noise.

With an input voltage hysteresis, this effect will only occur, if very slow input signals are applied.



GEBE \DDSCriteria.ppt Feb97

A problem often overlooked in system design is the floating (or slow) input. When using CMOS inputs especially (i.e. with all CMOS and BiCMOS logic devices), leaving an input floating may sometimes lead to very high supply currents, I_{CC} , or to subsequent oscillations on the circuit's output side.


The reason for this is that in each state - high or low - only one transistor conducts. In transition, however, some current flows in both transistors.

If the voltage at the input rises slowly and if it reaches the value of the threshold voltage, the output then switches rapidly from high to low, as a result of the high voltage amplification, and discharges the load capacitor. The discharge results in a voltage drop at the internal ground potential of the IC. This causes a reduction of the potential difference between the input and the internal ground potential, which has the effect of reducing the input voltage, and as a result causes the output to switch to the opposite direction. The process repeats, but with reversed polarities. This continues periodically, with the duration of the period determined by the delay time of the circuit.

As these oscillations mean high energy moving back and forth between the output and the load, they drastically increase the overall power and heat dissipation. Worst case, the circuit may be destroyed after some time.

Digital Design Seminar


Slow Input Signals (2)

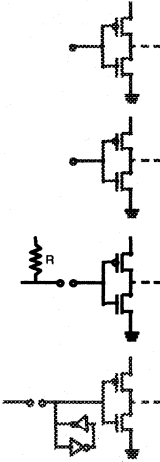

1. Do nothing - - - feel lucky?
2. Do nothing, if duration of 3-state is $< 2\mu\text{s}$
3. Use a pull-up resistor
Downside: extra components
bus parasitics
high power dissipation
4. Use a device with integrated bus hold cell
 - LVT
 - LVT16 (Widebus™)
 - LVCH*
 - LVCH16* (Widebus)
 - ALVCH16 (Widebus)
 - ABTH16* (Widebus)

* Selected functions only

GEBE IDDSCriteria.ppt Feb97



A few options are available to the system designer, to address the problem of floating (or slow) inputs. Obviously, one can choose to ignore it and, depending on the load conditions along the floating line, may even be lucky that the increase in power consumption remains uncritical. However, Murphy's famous law unfortunately also applies to electronic design: whatever CAN go wrong, WILL probably go wrong.

The problem can be ignored, though, if the duration of 3-states, i.e. the time period(s) during which the line may start to float, is shorter than 2 microseconds. In this case, the line level will only change gradually.

In all other cases, there are two options left: one can use a pull-up (or pull-down) resistor to ensure proper signal levels, if all circuits are 3-stated. This is a reliable, but power consuming method. It also changes the line's impedance unfavourably.

The other option is to use so-called bus hold cells, to ensure proper signal levels along the line. Separate ICs are being offered by some manufacturers to provide this function. The best method, however, is to use devices with integrated bus hold cells. Most of Texas Instruments' LVC, ALVC and LVT devices feature integrated bus hold cells.

Digital Design Seminar

Slow Input Signals (3)
Recommended Input Slew Rate Limits

Series	V _{cc} [V]	V _{il,max} [V]	V _{ih,min} [V]	V _i [V]	T _{r,max} [ns/V]
SN74	4.74-5.25	0.8	2.0	1.4	100
SN74LS	4.74-5.25	0.8	2.0	1.0	50
SN74S	4.74-5.25	0.8	2.0	1.4	50
SN74ALS	4.5-5.5	0.8	2.0	1.4	15
SN74AS	4.5-5.5	0.8	2.0	1.4	8
SN74F	4.5-5.5	0.8	2.0	1.4	8


SN74HC	2.0	0.3	1.5	1.0	625
	4.5	0.9	3.15	2.25	110
	6.0	1.2	4.2	3.0	80
SN74HCT	4.5-5.5	0.8	2.0	1.4	125
SN74AHC	3.3	0.9	2.1	1.5	100
	5.5	1.65	3.85	2.75	20
SN74AHCT	4.5-5.5	0.8	2.0	1.4	20
SN74LV	2.7-3.6	0.8	2.0	1.5	100
74AC	3.0	0.9	2.1	1.5	10
	4.5	1.35	3.15	2.25	10
	5.5	1.65	3.85	2.75	10
74ACT	4.5-5.5	0.8	2.0	1.5	10
SN74LVC	2.7-3.6	0.8	2.0	1.5	10
SN74ALVC	2.3-3.6	0.8	2.0	1.5	10

SN74BCT	4.5-5.5	0.8	2.0	1.5	10
SN74ABT	4.5-5.5	0.8	2.0	1.5	5/10
SN74LVT	2.7-3.6	0.8	2.0	1.5	10

TI

CEBE \DDSV\criteria.ppt Feb97

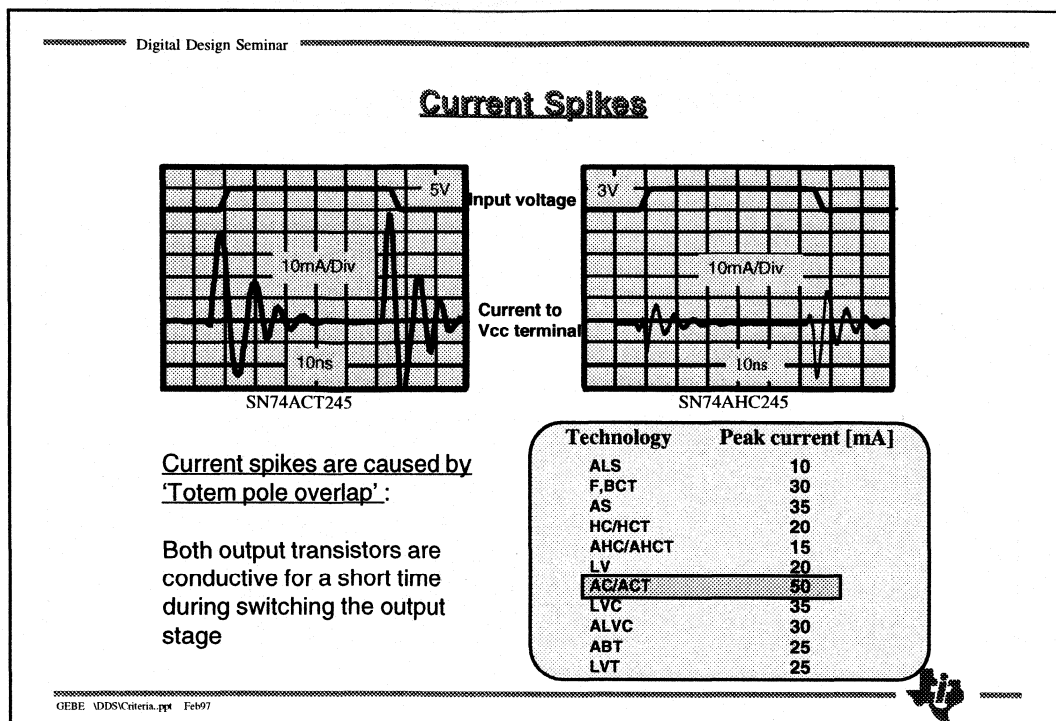The table above gives an overview of Texas Instruments' logic families with respect to the maximum input transition rise or fall rate. There is a direct correlation between speed and the parameter for rise and fall time. The faster the family, the higher the rise or fall time and more critical the slew rate.



This foil explains the current peaks which occur always during switching.


A characteristic common to all Totem-Pole and 3-State output stages is an additional current transient, when the output changes from a logic low to high and vice versa.

The internal output circuitry of the devices consists of two alternately conducting transistors. At every transition from logic high - state to logic low - state both output transistors are - for a very short time - conductive. This is called 'Totem pole overlap'.

The total supply-current spike is a combination of three major effects:

- the difference in high-level and low-level supply current
- the charging of load capacitance
- the conduction overlap.

The charging of load capacitance in most cases overshadows the other two effects with respect to noise produced on the supply voltage lines by switching current transients. However, to keep the current spike as low as possible, it is important to maintain low impedance of the power lines, use a decoupling capacitor (bypass capacitor) at the devices' supply pins and keep the area covered by the power traces small.

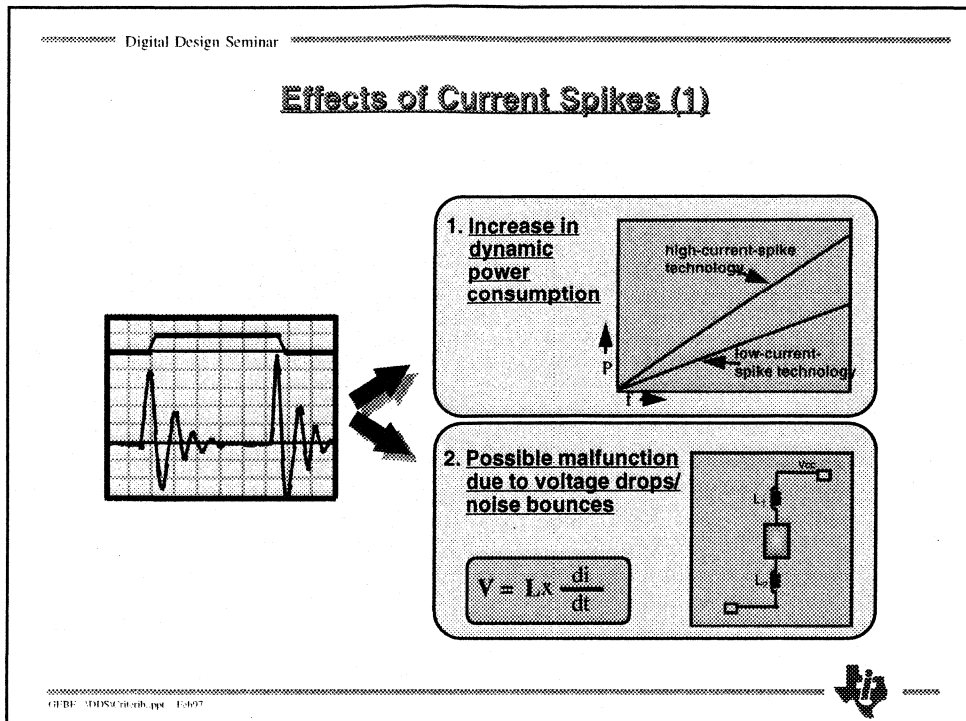


The current spikes at the Vcc terminal lead to a higher power dissipation, the power consumption increases proportional to the operational frequency.

The possible malfunctions can be forced by high current deltas on the supply lines related to the given formula.


Digital Design Seminar

Effects of Current Spikes (2)

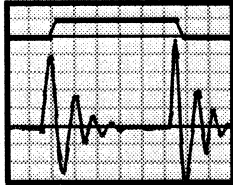


3. Increase in EMI noise generation

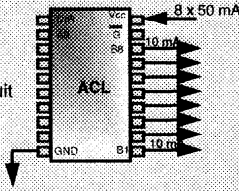Example:
Advanced CMOS circuit at typical output load conditions (all outputs active)



$$E = \text{Const} \times [I \times A \times \frac{1}{r} \times \sin(\theta)]$$
(at a given frequency)

CFE: 11/24/04 revb.ppt E:107


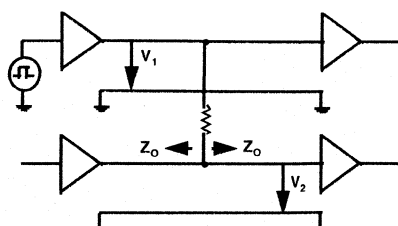
The formula shows that the current peaks are the chief device parameter in the formula of the EMI radiation. All other parameters are either constants or parameters which the designer may consider in PCB layout.

(See details in the EMI section).

Digital Design Seminar


Crosstalk

On long transmission lines ($2\tau > t$) the Crosstalk can be calculated as follows :



Z_0 = Line Impedance
 Z_c = Coupling Impedance

Crosstalk :

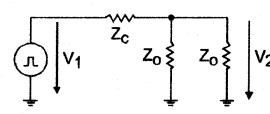

$$C = \frac{V_2}{V_1} \times 100 \%$$

$$= \frac{0.5 Z_0}{0.5 Z_0 + Z_c} \times 100 \% = \frac{1}{1 + 2Z_c / Z_0} \times 100 \%$$

Note: At the end of an unterminated line Crosstalk is twice as high (Reflection Factor $\rho = 1$) !

G:\EE\405SCH06b.ppt 12/07

When currents and voltages are impressed on a connecting line in a system, it is impossible for adjacent lines to remain unaffected. Static and magnetic fields interact and opposing ground currents flow, creating linked magnetic and capacitive fields. These cross-coupling effects are lumped together and called crosstalk.

The coupling from the sending line to the receiving line can be represented by taking coupling impedance Z_c into account. The voltage at the sending line is the voltage source V_1 . V_1 is then coupled to the receiving line via the coupling capacitance Z_c , where the impedance looking into the line is line impedance in both directions.

The voltage impressed on the receiving line (V_2) then propagates along the receiving line to the input of the receiver, which - in case of an unterminated line - can be considered as an open-line and voltage doubling occurs.




The term V_2/V_1 can be defined as the cross-talk coupling constant.

The worst-case for signal line cross talk occurs when sending and receiving lines are close together, but widely separated from a ground return path. The lines then have a high characteristic impedance and a low coupling impedance (as lower the coupling impedance, as higher the cross talk constant!).

The next page shows some cross talk examples of typical lines used in digital systems.


..... Digital Design Seminar

**Crosstalk on Printed Circuit Boards
(typical Values)**

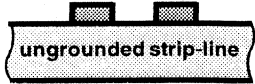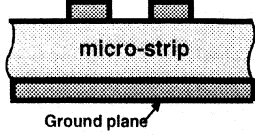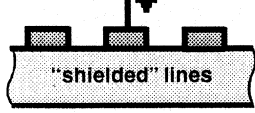	Line Impedance Z_0 [Ω]	Coupling Impedance Z_c [Ω]	Crosstalk [%]
 <p>ungrounded strip-line</p>	200	100	50
 <p>micro-strip</p> <p>Ground plane</p>	80	125	25
 <p>"shielded" lines</p>	100	400	11

Note: line width = line distance

..... QFBE 0005a v10eb.qpt 1-107




Crosstalk on a printed circuit board is a function of the mutual reactances (Z_c) and the line parameters which define the line impedance (Z_0). Therefore the coupling constant will vary with the type of transmission-line used.

The use of ungrounded strip-lines (see figure in the top) is a simple and low cost method, but it is also the poorest for noise rejection.


A microstrip line as well as a strip line with an adjacent ground line (figures in the middle and bottom) is, by definition, a conductor placed relatively close to a ground plane/line. Because of the low line impedance and shielding characteristic of the ground plane/line, its crosstalk is minimal and not a problem with most logic families.

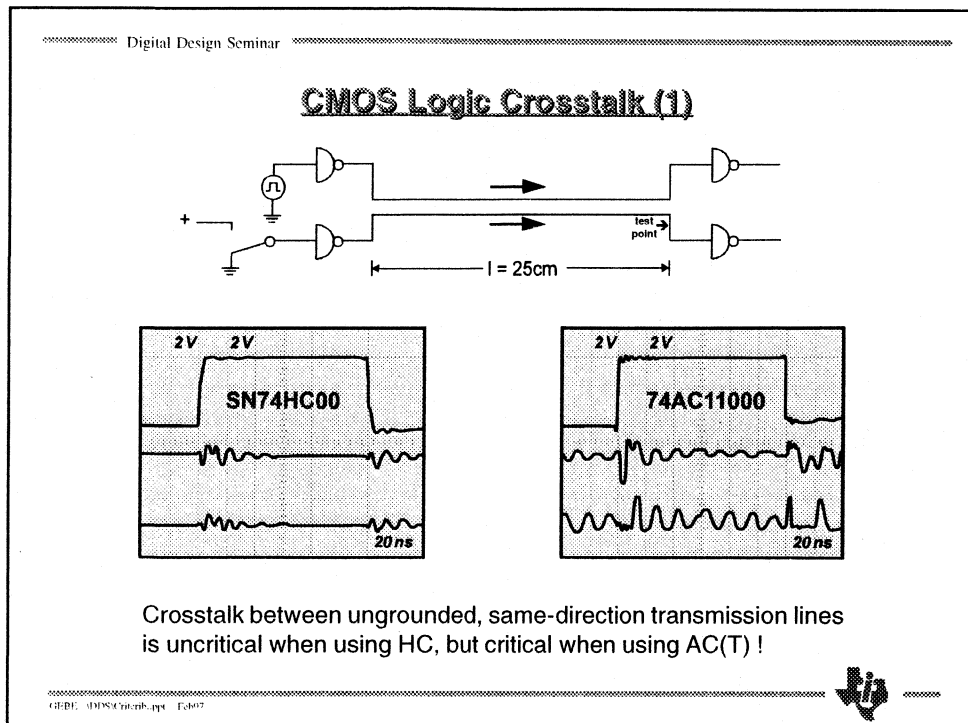The data shown above can be used to estimate the typical crosstalk effect in digital systems.




This and the next 4 pages show some practical examples of cross-coupling effects. As a test vehicle we used the High-Speed CMOS (HC) and Advanced CMOS (ACL) technology. ACL with its high slew rate is a good example to demonstrate crosstalk problems in digital systems.

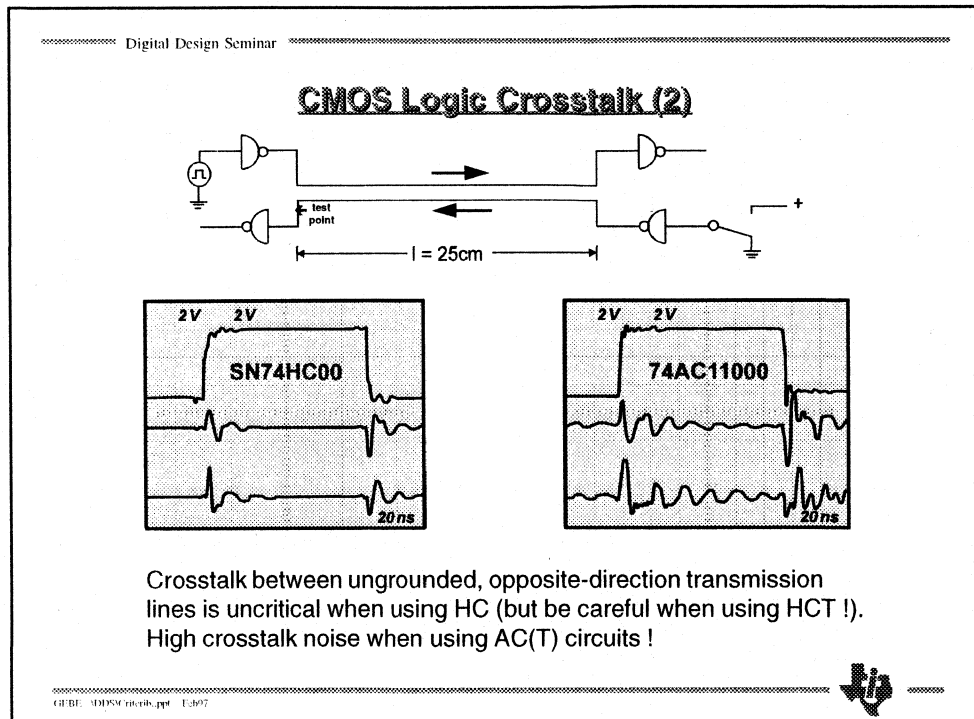This foil shows the crosstalk between two ungrounded strip-lines of 25 cm in length with data transmission in the same direction! Crosstalk between same-direction transmission lines is uncritical, when using HC or AHC (as well as all bipolar, BiCMOS and low-voltage technologies), but is critical, when using Advanced CMOS technologies, e.g. such as AC(T)!



This foil shows the crosstalk between two ungrounded strip-lines of 25 cm in length. It is important to notice that now the lines use the opposite transmission direction. Opposite-direction transmission is worse than same-direction transmission!

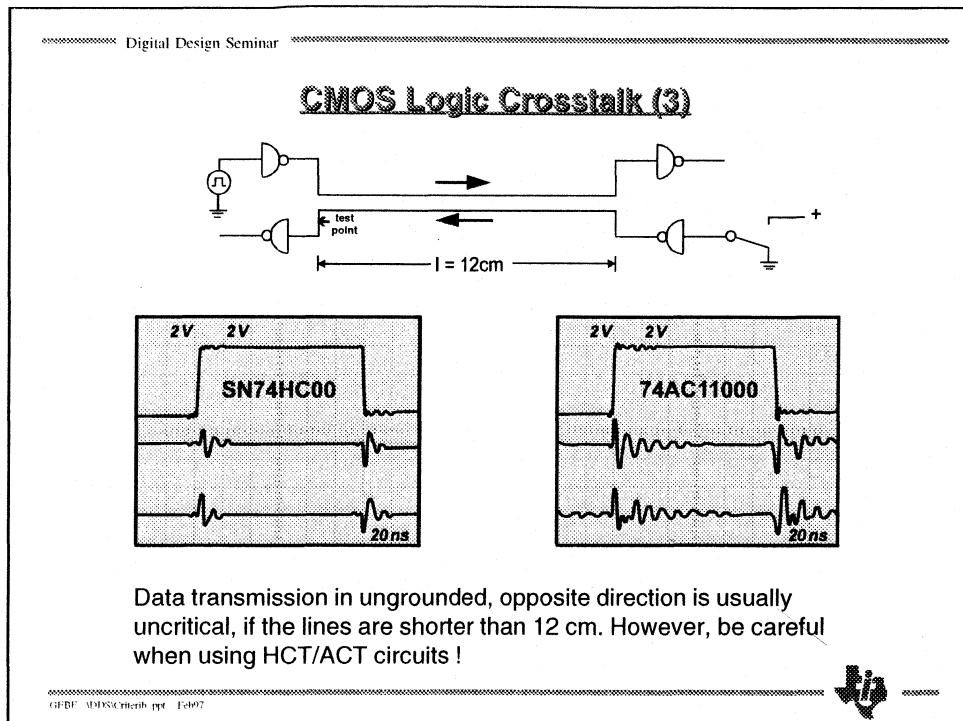Crosstalk between opposite-direction transmission lines is uncritical, when using HC or AHC (and most bipolar, BiCMOS and low-voltage technologies), but be careful, when using HCT! Very high crosstalk noise is caused, when using AC(T)!




Crosstalk can be reduced by shortening the length of the adjacent lines.

This foil shows the crosstalk of two ungrounded strip-lines of 12 cm in length. Again, to reflect the worse-case situation, both lines use the opposite transmission direction!

If the lines are shorter than 12 cm, data transmission in opposite direction is usually uncritical. However, be careful, when using 5V CMOS circuits with TTL compatible inputs, such as HCT, AHCT and ACT!

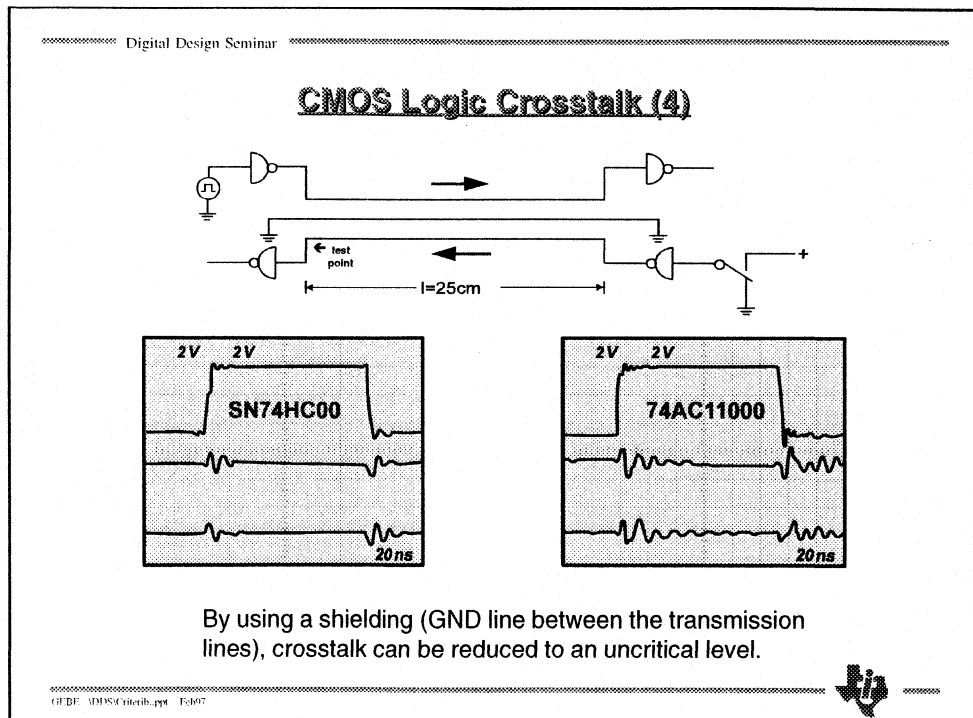
The same improvement can be seen, if we increase the space between both lines. However, either shortening the line length or increasing the space between the lines, is not very effective to reduce crosstalk noise, because that means changing the layout or even the hardware.



A more effective method to minimize crosstalk noise is to use a shielding line (ground line) between the adjacent strip-lines.

This foil shows the crosstalk of two strip-lines of 25 cm in length with a shielding line in between. Also here, to show the worse-case situation, both lines use the opposite transmission direction!

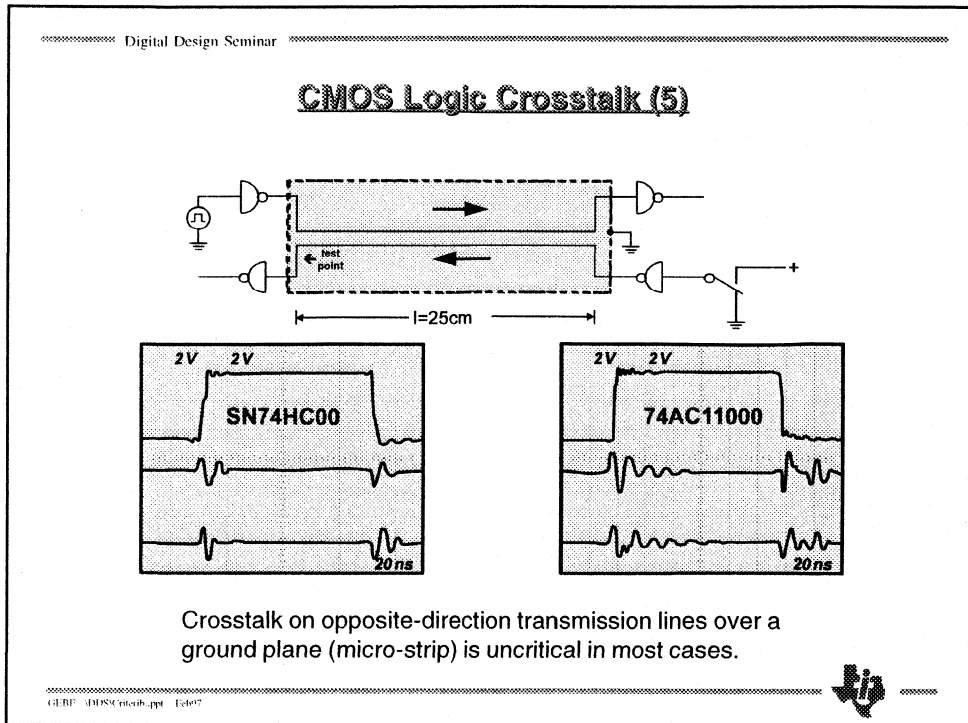By using a shielding line (grounding on both sides is advised), crosstalk for all logic families can be reduced to an uncritical level - even with 5V CMOS circuits with TTL compatible inputs (HCT, AHCT and ACT).



The same improvement demonstrated with the shielding line can be seen, if we use a ground plane underneath the adjacent signal lines. Even if the crosstalk constant is slightly worse than with the shielding line, it effectively eliminates crosstalk in most cases.

Digital Design Seminar


Circuit Speed vs Slew Rate: Overview

	HC	AHC	AC	F	ABT	LVT	LVC	LV	ALVC
Propagation Delay [ns]	13	6.5	5	4	2.5	2.4	4	8	2
Voltage Swing [V]	4.8	4.8	4.8	3	3	3	3	3	3
Slew Rate [V/ns]	0.9	0.8	1.8	1.3	1.2	1.2	0.9	0.7	1.3
Crosstalk Noise	medium	medium	high	medium	medium	medium	medium	low	medium
Recommended PCB	2-layer	2-layer	multilayer	multilayer	multilayer	multilayer	multilayer	2-layer	multilayer
Current Spike [mA]	20	15	50	30	25	25	35	20	30
Number of ICs per Gate	n=4	n=4	n=1	n=2	-	-	n=2	n=4	-
Blocking Capacitor Bus Drive	n=2	n=2	n=1	n=1	n=1	n=1	n=1	n=2	n=1

n = number of devices per decoupling capacitor

1. Data adapted to 5V supply

- ★ Example: '244 function ('16244 in case of ALVC), outputs loaded with 50 pF; all values are typical
- ★ Slew rate values shown are the higher ones of rising and falling edge of output signal



GEBE - DDS/Chalk.ppt - E-07

This table summarizes different noise types, noise sources and some methods of controlling them for selected logic families.

Critical noise sources are the propagation delay, t_{pd} , voltage swing, $(V_{OH} - V_{OL})$, slew rate, dv/dt and current spikes. HC, AHC, AC, F and ABT are operating from a 5V supply voltage, while LV, LVC, LVT and ALVC have a 3.3V supply.

The data indicate that t_{pd} and dv/dt show common trends (the shorter the propagation delay, the higher the slew rate). However, there is no direct link between the two parameters. In particular, the fastest family (ALVC) is not the one with the highest slew rate.

Crosstalk will be worse in case of opposite-direction transmission lines. Remedies are shielding lines or the use of separate ground and V_{CC} planes with multilayer boards. In the latter case it should be noted that crosstalk may still in some cases be critical with ACT or other fast TTL-compatible CMOS parts.

Current spikes are one of those effects which apply to more or less all digital circuits. While the supply voltage drop effects can be addressed by appropriate design measure (e.g. by using a GND and V_{cc} plane and a bypass or a decoupling capacitor), both the increased dynamic power consumption and the increased EMI noise energy are device-related effects. Therefore a system designer's only option is to choose appropriate technologies that have low current spikes.

..... Digital Design Seminar

Decoupling Guidelines

- ★ Capacitance can be calculated

$$I = C \times dv/dt,$$
 from the amount of current needed, how long the current is needed, and what change in voltage is allowable.
- ★ Choose a capacitor whose resonant frequency is at least as high as the corresponding edge rates of the switching signals, where frequency response @ $1 / (3.5 \times t_{rise,fall})$.

$$f_{res(LVC)} = \frac{1}{(3.5 \times 2 \text{ ns})} = 143 \text{ MHz}$$

- ★ Place the capacitors as close to the switching device as possible. In the case of a transceiver place the capacitance between the VCC and Ground planes at the part. In the case of termination place the capacitance from the supply voltage to Ground at the termination resistor.


..... DDCS Criteria CR-1 Feb97

While the slew rate and the corresponding ground bounce noise mainly depend on the technology chosen, a system designer will have to decide on the decoupling method used to prevent voltage drops and ringing on the power supply lines. This is somewhat more critical in 3.3V systems than in 5V environments, where sometimes larger voltage drops are still acceptable.

A bypass (decoupling) capacitor stores an electrical charge that is released to the power line, whenever a transient voltage spike occurs. It provides a low impedance supply, thereby minimizing the noise generated by the switching outputs of the device.

Bypassing a power line (or plane) from the device internal noise requires capacitors with very small inductances. That is why the multilayer ceramic chip capacitors (MLC) are more favourable than others for bypassing power lines (or planes). They exhibit negligible internal inductance, thereby allowing the charge to flow easily, when needed, without degradation. For TTL and CMOS systems, a good guideline is 0.01 μF per device.

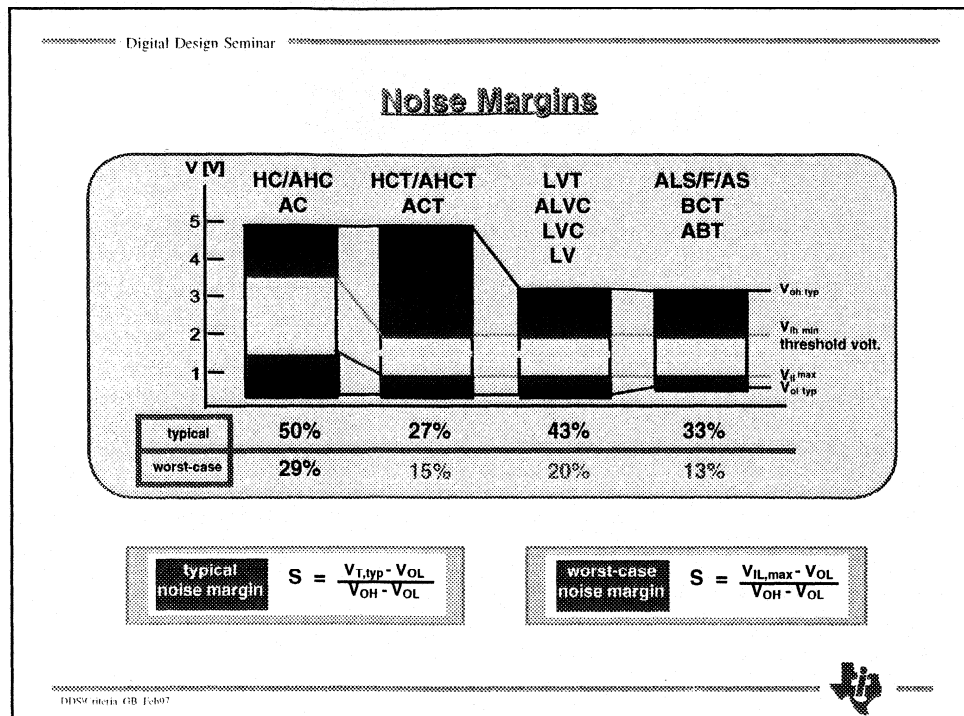For effective decoupling on printed circuit boards the most desirable arrangement is a multilayer board with solid GND and V_{CC} plane. In addition it is highly recommended that the bypass capacitor is placed as close as possible between the power pins of the device.



Noise margin is a voltage specification that ensures the static DC immunity of a circuit to adverse operating conditions. The noise margin is defined as the difference between the worst-case input logic level and the worst-case output logic level.

The usefulness of noise margins at the system design level is the ability of a device to be resistant to noise spikes at the input.

The above comparison shows the noise margin for selected logic families. The 5V CMOS families - HC, AHC and ACL - have a typical noise margin of 50% and even in the worst-case condition a remarkable noise margin of 29%. In comparison, the TTL-compatible Bipolar and BiCMOS families have only 13% in the worst-cast condition. But if we have a look at the low-voltage families, all 3.3V devices have an improved noise margin of 20% in the worst-case, which makes this families even more attractive for new designs.

The improved noise immunity of 5V CMOS and 3.3V families over bipolar and BiCMOS devices is due to the rail-to-rail (Vcc to GND) output voltage swing. This noise immunity makes them ideal for high noise environments. However, keep in mind that TTL-compatible 5V CMOS devices, such as HCT, AHCT and ACT, have similar noise margins to bipolar and BiCMOS.


Digital Design Seminar

Bipolar / BICMOS / CMOS Comparison Electromagnetic Interference

		Bipolar/ BICMOS	3-V logic	5-V CMOS
voltage swing		3 V	3 V	5 V
slew rate	dV/dT	X	0.9 X	1.5 X
output current	I	X	1.2 X	1.5-2.0 X
relative EMI power	(dV/dT) x I	X²	~X²	2.2-3.0X²

5-V CMOS slew rate and output current are 50% greater than 3-V - CMOS or bipolar, for equal speeds.

Thus electromagnetic interference for 5-V - CMOS is more than twice as great.



DMS-C001 GR 15M7

Like line-reflection, crosstalk or simultaneous switching, noise from Electro-magnetic Interference (EMI) depends on the integrated circuits switching characteristic.

The three major factors affecting EMI are the output voltage swing, the devices' slew rate and the output current. However, all three factors can be addressed to minimized switching noise:

- Output Edge Control™ (OEC) reduces high-frequency components (implemented in all new logic families at TI)
- lower output voltage swing - this reduces critical slew rate (e.g. use 3.3V logic)
- reduce package inductance (SOICs better than DIPs)
- minimize output drive (e.g. use AHC instead of ACL)


As a result from above calculation, the EMI noise from 5V CMOS is more than twice that of bipolar or 3.3V devices.

..... Digital Design Seminar

Technology Comparison Ease of Design

	Bipolar/ BiCMOS	5-V CMOS CMOS compatible	5-V CMOS TTL compatible	3V Logic
Noise Margin worst case	X (13%)	2.2 X (29%)	1.1X (15%)	1.5 X (20%)
Noise Energy (du/dt x I)	X ²	2.2-3.0 X ²	2.2-3.0 X ²	~X ²

Reducing V_{cc} (e.g. to 3.3 V) will not improve switching noise, but will give a better noise margin.

..... 

DSSCriteria GB Feb97

A general technology comparison between bipolar, BiCMOS, 5V CMOS and 3.3V CMOS circuits will only make sense, by looking at both the device-related noise energies and the noise margins that are dictated by the input and output signal level specifications.

Considering these two parameters, one finds that bipolar or BiCMOS circuits show about the same 'ease of design' level as CMOS parts working at CMOS levels (ie with a V_{cc}/2 input threshold voltage).


Looking at the 3.3V technologies you actually see the best ratio in noise energy vs noise margin, which in addition makes 3.3V devices very attractive for new designs.


The **most critical combination**, however, is CMOS process technology and bipolar-like TTL-level specifications. Because of high noise levels of CMOS and the lower noise margins of TTL-level systems sometimes a crucial obstacle is encountered, whilst developing reliable systems.

----- Digital Design Seminar -----

EMI PCB Design Guidelines: Overview

- ★ Since January 1996, a new EC (European Community) directive regarding electromagnetic compatibility (EMC) came into effect.
- ★ The EMC regulation affects many aspects of circuit and system design.
- ★ Electromagnetic Interference (EMI) is switching noise that is radiated or conducted via electric and magnetic field.
- ★ As manufacturer of electronic components, Texas Instruments are committed to minimize both the emissions from and susceptibility to electromagnetic interference.

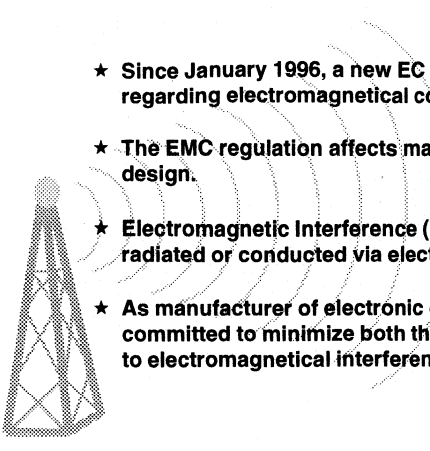


----- DDSCriteria GB Feb97 ----- 

The EC (European Community) regulations regarding EMC will affect many aspects of circuit and system design. However, there are many considerations that can be applied generally to reduce both the emission from and susceptibility to EMI.

Electromagnetic interference (EMI) often seems like a mysterious phenomenon. EMI can be difficult to control, and even the results of EMI testing can vary from day to day and from test facility to test facility. At times, the act of controlling EMI has been called "black magic" or "voodoo". However, EMI has been researched for many years, and guidelines have been established that can improve the electromagnetic compatibility of a system to which they are applied.

Designing for low EMI from the start of a project results in much easier and less expensive solutions than attempting to fix EMI problems, after a design has reached the testing phase of development. Consequently, following a few guidelines for printed circuit board (PCB) design at the beginning of a project can help to minimize the systems' EMI while adding little or no cost to the system.

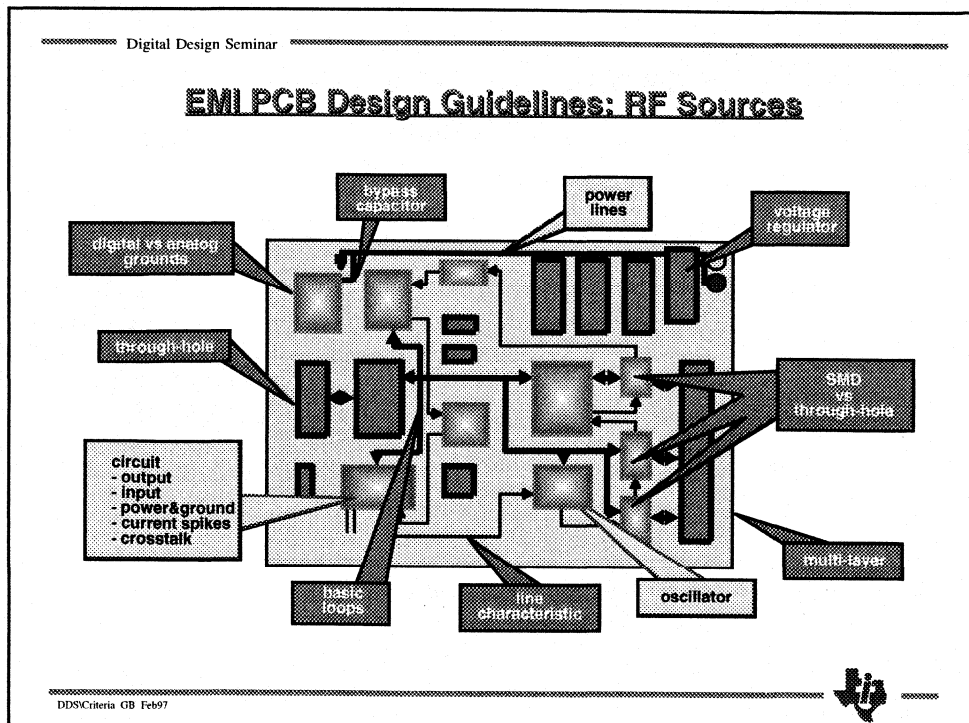This chapter will give some tips and recommendations for low-noise design.



Let us start looking at typical digital PCB with a quick look at the most EMI critical areas on the PCB.

There are three important contributors of RF noise.






The number one problem is noise from the IC I/O pins, simply because the area covered by traces connected to them on the PCB makes large antenna (basic loops!).


The second most important contributor is the power supply system which includes the voltage regulation, the bypassing capacitor and the supply lines. These 'components' are the source and the sink of all RF energy in the system.

The number three noise source is the oscillator circuit, where the oscillator swings rail to rail. In addition to the fundamental frequency, harmonics are introduced on the output side.

..... Digital Design Seminar

EMI PCB Design Guidelines:
Definition

RF-Source:	Trace bound (RF-voltage/current) and radiated interface (RF- noise), e.g. active components like diodes, transistors, integrated circuits, etc.	
RF-Channel:	Signal lines; power lines; boards; modules; systems	
RF-Sink:	Receiver of RF-noise (e.g. IC input, IC supply-pins)	
RF-Noise:	Caused by voltage, current or field effects --> important factors are amplitude and period	
RF-Effects:	Reflection; cross talk; current spikes; simultaneous switching; coupling of signals; etc.	




..... DDS/Criteria GB Feb97

EMI requires a source, a path and a receiver. In today's electronics, integrated circuits (IC) often supply the source and the printed circuit board, as well as the associated cabling and wire harness, acts as the conductive and radiating part of the path, otherwise called the antenna. The receiver simply can be a IC's input, a sensitive electronic module, such as a radio, or it can be a loop at the PCB, accidentally designed to receive electromagnetic noise.

EMI generation is a function of RF-source, RF-channel and RF-sink. All three 'components' are involved in EMI generation in a system, as they source, transmit and feed the current required in switching.

The two major factors affecting RF energy are the amplitude and period of the switching signal: Switching frequency, duty cycle, edge rate, noise content and voltage levels.

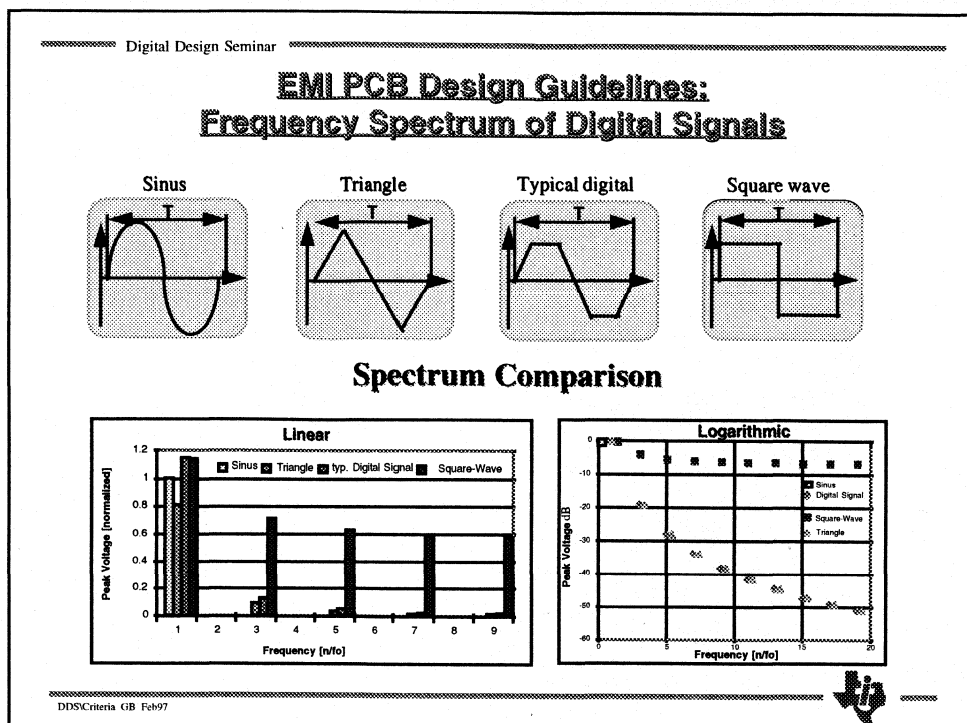Noise is generated and coupled out through many different possible mechanisms: line reflection, crosstalk, current spikes, simultaneous switching, etc.




To get a better understanding of EMI, it is important to know the frequency spectrum of the waveform used in digital systems.

The upper curves represent some basic signal waveforms which could be found in today's electronic systems. In digital systems, however, the trapezoidal (square) signal dominates. Beside the sine waveform, all others include beside the fundamental frequency also harmonics of the fundamental frequency.

The fundamental frequency and its harmonics, as well as any noise (ringing) on the signal, will influence the frequency envelope in which EMI generation may be expected.

The lower curve illustrates the theoretical spectrum lines of the upper signals.

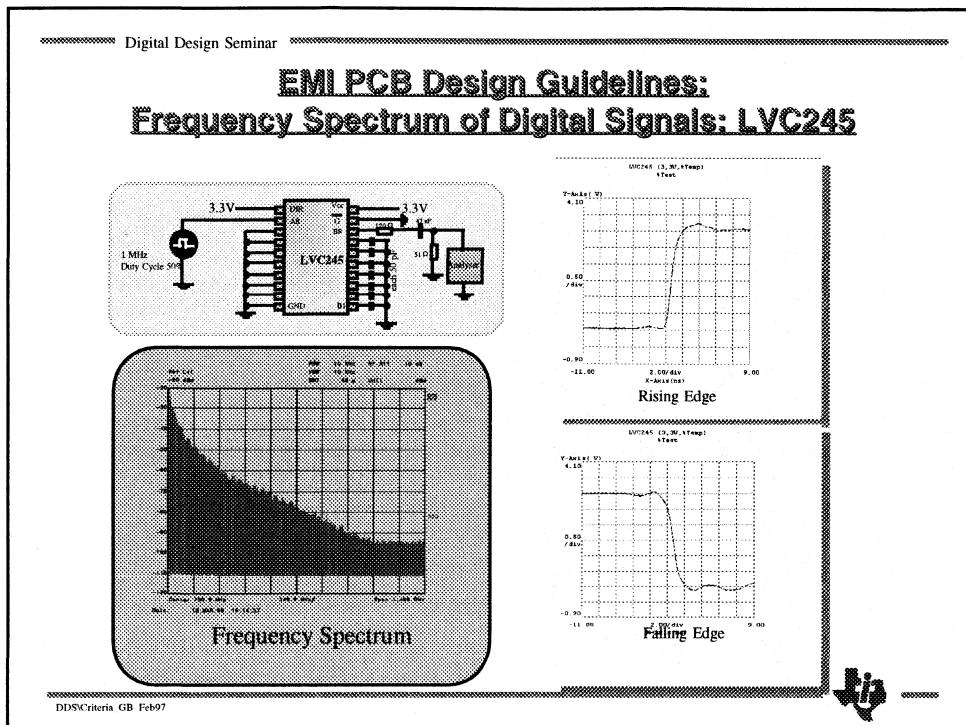The sine curve consists of only one spectrum line, whereas the square wave includes a lot of high frequency harmonics. The right-hand figure illustrates the logarithmic spectral content in dB.



The above slide illustrates a lab measurement of output spectral content for SN74LVC245.

The measurement setup represents a typical bus line with about 150 Ohm resistance and 47 pF capacitance.

The spectrum of the digital signal was measured with a spectrum analyser at the end of the artificial bus line.

The shape of the spectrum envelope shows good conformity to the theory. At this point you should not forget that the spectrum is given in dB (20 dB are equal to factor 10 !)

The figure on the right-hand side shows the output signal of the SN74LVC245.


The slew rate with this test condition is about 1.5V/ns and the rising and falling edges are very symmetrical.

..... Digital Design Seminar

EML PCB Design Guidelines: **IC-I/O Pin Noise**


★ The number one problem is RF-noise from the IC - I/O pins

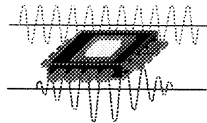- ↳ signal/power traces connected to the pins on the PCB make a large antenna



★ Noise from a pin is a function of the chip and package

- ↳ minimize output voltage swing → e.g. 3.3V logic
- ↳ reduce package inductance → SOICs are better than through-hole devices
- ↳ smooth output waveform edge → use devices with Output Edge Control™
- ↳ minimize capacitive loading → reduces current loading per part
- ↳ eliminate switching noise → use bypass capacitor, advanced packages, avoid undefined inputs voltages
- ↳ minimize output drive → e.g. use AHC instead ACL

..... DDS/Criteria GB Feb97 

We are going to be concerned with the RF noise from the device. That noise is generated internally in the device and is coupled out through many different possible mechanisms.

The noise will be present on all outputs, inputs, and power and ground, at all times. Basically, every pin on the device could be a problem.

The most critical pins are the IC I/O pins, simply because the area covered by traces connected to them on the PCB makes a large antenna. The noise from clock switching internally to the IC, simultaneous switching, internal crosstalk or current spikes, appears as noise spikes on outputs, inputs as well as power/ground pins.

On the chip and package level several design improvements have improved signal quality. Additional circuitries like Output Edge Control™ (OEC), Power-On-Demand (POD), Bus Hold (BH) and package improvements like a split ground lead frame, (thin small-outline packages), Widebus™ packages and flow-through pinout, help to minimize device-generated noise.

Digital Design Seminar

EMI PCB Design Guidelines: Basic Loops

- ★ Every signal sent out from the IC to another chip returns on the *return path* back to the IC (e.g. via ground)
 - ★ it travels in a loop back to where it originates
 - ★ loops are antennas which radiate RF energy

power supply voltage regulator ambient field loops oscillator loops

bypassing loops shield cable loops connector loops signal loops

TIA

DDSCriteria GB Feb97

The amount of radiation produced by an electronic system is to a large extent proportional to the efficiency of its radiating antennas - or basic loops. Antennas or loops on a PCB include all traces, components, component leads, connectors and wiring harnesses.

Every edge transition that is sent out from the μP to another chip, is actually a current pulse. It goes to the receiving device and actually exits through that device's ground pin. It then returns, via ground traces, back to the ground pin of the μP . It travels in a loop back to where it originates.

Loops exist everywhere. Any noise voltage and its associated current will travel the path(s) of lowest impedance back to the place where it was generated.

A loop can be a signal and its return path, the bypassing loop between power and ground and the active device inside the μP , the oscillator crystal as well as the loops from power supply or voltage regulator to bypassing caps. Other more difficult loops are actually ambient field loops. For example, the crystal itself radiates and can be coupled into a wire running nearby. Then the wire contains noise that is going to try to get back to the crystal loop. That may mean a very long convoluted path, which of course serves as another antenna for the crystal noise.

The understanding what loops are is a very powerful concept, because it allows us to track all signals on the board, to avoid unknown return paths (flying leads) and to change noise propagation by controlling the shape and impedance of the return path.


Digital Design Seminar

EMI PCB Design Guidelines: Antenna radiates RF noise

★ Loops and dipoles are antennas. Their radiating efficiency increases up to 1/4 wavelength of the frequency of interest,

★ at

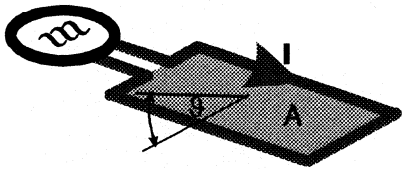- ⇒ 1MHz, $\lambda/4=75$ meters *)
- ⇒ 300MHz, $\lambda/4=25$ cm *)




★ Normally, trace length becomes important when greater than

- ⇒ $\lambda/10$: FCC Limits
- ⇒ $\lambda/20$: Automotive
- ⇒ $\lambda/40$: Mil Std

$$E = k \cdot I \cdot A \cdot \frac{1}{r} \cdot \sin \vartheta$$

*) vacuum; effective length of the antenna is determined by μ , and ϵ , (PCB $\epsilon_r=5$)

DDSCriteria GB Feb97



Loop areas can be the most serious EMI threat. A loop can transmit as well as receive electromagnetic energy. Thus, the loop areas associated with a PCB directly affect the emissions and immunity of the system.


Loops and dipoles are antennas. As the size of a loop increases, so does the efficiency of the loop as a radiator. The radiating efficiency increases up to 1/4 wavelength of the frequency of interest. Geometrically, that means, in case of a loop, that the larger the laid-out area of the loop, the stronger the radiation. This is true until one or both legs of a loop reach 1/4 wavelength.

Thus to minimize radiated and received EMI, loops must be made as small as possible.

Digital Design Seminar

EMI PCB Design Guidelines: Power & Grounds (1)

- ★ **The power supply system is often the most important contributor of RF noise (Current spike)**
- ★ **Ground & Power should have as low an inductance as possible**
 - 2-layer board: length to width ratio should not exceed 3:1 (bypass capacitor)
 - power and ground should be run directly over each other (Z ; loop area)
- ★ **A 2-layer board can achieve 95% of the effectiveness of a multilayer board, if you:**
 - route the ground underneath power
 - grid the power and ground
 - route return path directly under/parallel the signal trace (gridding; ground plane)
 - build a solid plane for ground under the IC

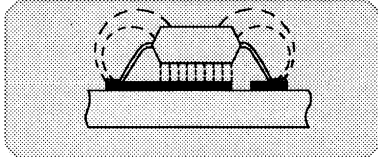

EIA

DDSCriteria GB Feb97

Proper power routing is of fundamental importance to achieve electromagnetic compatibility. The only non-DC current that should flow in the power lines of the PCB is the current for the bypassing capacitor. High frequency current used inside the IC should come from the bypass capacitor, not the power supply!

Since a "ground" is really a current return path in most cases, the goal of any trace carrying RF energy is to provide the lowest impedance current path possible without generating additional noise. A ground (power) plane will best accomplish this task. However, also a ground grid for digital circuitry can provide low-impedance signal return paths on a two-layer board and does not require the additional cost of a ground plane.

Power should be routed over (under) or next to the ground, whenever possible. The power lines typically contain the most high-frequency noise in a digital system. Therefore routing power directly over ground results in a path with low inductance and minimized radiating loop area. Routing power and ground next to each other is the next best alternative.


Additionally, series filters, such as ferrites or inductors, often prove helpful for reducing noise on power supply routes. A π configuration can be used on the V_{CC} pin. Also, the ferrite should be located very close to the pin of the IC, in order to keep the noise off the PCB trace.

A solid ground area under the IC becomes a ground island for the RF noise made by the IC. It provides a low inductance path and minimized radiating loop area. The ground should be connected to IC ground and the bypassing capacitor ground.

..... Digital Design Seminar


EMI - PCB Design Guidelines: Power & Grounds (2)

★ Multilayer board

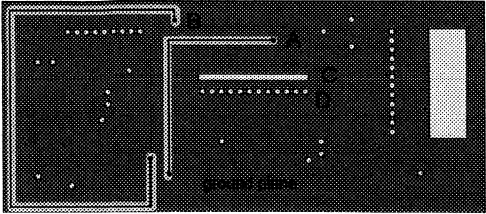

A: Poor - buried trace cuts ground plane into two parts **C: Poor** - Slot cuts up ground plane, focuses slot antenna radiation into that connection

B: Better - buried trace around the perimeter; best is no trace at all in the ground plane **D: Better** - Ground plane extends between 100 mil centers

..... 

DDSCriteria GB Feb97


The closest approximation to having a ground plane in a 2 layer board comes from gridding the ground. The following guidelines are meant to maintain the advantages gained with a ground plane or ground gridding:

- Pay utmost attention to how the holes and cutouts on planes are done. They break up the plane and therefore cause increases in loop areas.
- Avoid buried traces in the ground plane. If you have to use them, put them in the upper side of PCB. See A and B in above figure.
- When making through-holes for sockets or connectors in the plane, place a small trace between each pin. Breaking up a plane with a row of holes is much, much better than having a long slot. See C and D in above figure.
- When splitting the ground plane up to make, say a digital and power ground, make sure that the signals connected to the IC are still located entirely over the digital ground. Extending signals over the power ground hurt, because the power ground does not work to reduce the loop area for digital noise signals.


Digital Design Seminar

EMI - PCB Design Guidelines: Power & Grounds (3)


★ Power Distribution

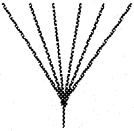

star point

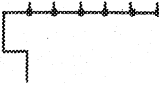


multiple point

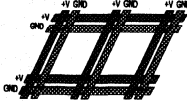

gridding

		star point	multiple point	gridding
power lines	digital analog	fair *	poor	fair
signal lines	digital analog	poor fair	poor	fair poor

*short traces



DDSCriteria GB Feb97

In a mixed-signal environment digital and analog parts should be separated from each other and connected only at a low-impedance ground node. This configuration will reduce coupling of digital noise onto sensitive analog circuitry.

Digital grounds should be designed to return high frequencies through a low impedance path, and analog grounds should normally be designed to return low frequency current or DC to its origin through a low-resistance path.


For digital signals, a ground plane or alternatively a ground grid can provide a low-impedance signal return path for high-frequency noise. Contrary to the star point scheme, the ground grid (plane) is best in order to reduced RF noise and overall costs.

For analog circuitry a star-point grounding scheme is often better, in order to avoid the presence of ground loops. The star point (parallel connection) or the multi-point (series connection) provides the cleanest current return path for analog signals. Star point connection is best, in order to avoid ground loops, but more expensive to design on PCB. Multi-point is less desirable, but easier to design. Thus, a star point should be used for the most sensitive analog signals, and multipoint can be used for less sensitive analog devices. Star point grounding is also preferred for noisy or high-power circuitry.


Digital Design Seminar

EMI - PCB Design Guidelines: Board Zoning

- ★ Place high-speed ICs close to power supply, with slower components located further away, and analog components even further still;
- ★ Place oscillator tank loops away from analog circuits, low-speed signals and connectors;
- ★ Build a gridded or solid ground between the IC, volt. reg and Vcc input, and tie the shield in at that point;
- ★ Locate the IC next to the volt. reg and the volt. reg next to where Vcc comes on the board;
- ★ Don't design in cable assemblies that fold over oscillators or high-speed devices.

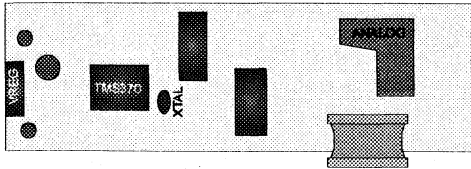

DDSCriteria GB Feb97



Board zoning (or floor-planning) a PCB is the first step towards designing EMC. Board zoning consists of creating zones on the PCB for analog, digital and noisy components and providing proper space for grounding. Also, devices should be arranged to minimize routing distances of EMI-critical signals, such as clocks, power, cabling and control signals.


High-speed ICs are placed close to the power supply, with slower components located further away, and analog components even further still. In this way the high-speed logic has less chance to pollute other signal traces.

Of special note, oscillator tank loops should be placed away from analog circuits, low speed signals and connectors.

..... Digital Design Seminar

EMI - PCB Design Guidelines:
Cable & Connectors

- ★ **At the system level RF noise is radiated via cables interconnecting the PCBs**
- ★ **RF energy becomes critical if return path has high RF impedance**
 - reduce RF impedance in the ground wire
 - use several ground wires
- ★ **Crosstalk in cables is the same as in PCBs - therefore run clocking or other high-speed wires twisted with their own separate return**
- ★ **As for number of returns:**
 - best is to run 1 ground return for each signal in the cable, as twisted pair
 - never run less than 1 ground for every 9 signal lines
 - cables over 30 cm long should be 1/4 ground lines
 - whenever possible, use a solid metal bracket soldered between the two boards

..... 

DDSCriteria GB Feb97

The problem at the system level becomes the radiation due to cables interconnecting the PCB with any off board support function or other processor or display or keypad PCBs. Since there is usually only one ground wire between boards, this one inductive wire has to return all of the RF energy carried into the second PCB by the other (signal) wires.

If there is any impedance in the one ground wire (e.g. connector), a portion of the RF energy will not return to the IC's PCB via the ground wire, but rather through a radiated path. It will radiate off the second board and couple back to the first, but during that process that radiation can add noise in other locations in the system.

The key corrective action is to insure the conducted path for the return has a very low RF impedance. For low speed data transmission it is common practice to have at least 1 ground for every 9 signal lines in a cable or harness. The number is moving towards 1:5 with higher speeds. The best is to run 1 ground return for each signal line in cable, as twisted pair.

Whenever possible, there should be a solid metal bracket, used as a mechanical brace, soldered between the two boards that serves both as a mounting brackets and as a robust RF ground return.

..... Digital Design Seminar

Bus Systems

FOPE UDSBusSys.ppt Jan07



Digital Design Seminar

Bus Lines

LINE PARAMETER		
	UNLOADED	LOADED WITH LUMPED CAPACITANCE
L_o	6 nH/cm	6 nH/cm
C_o	0,6 pF/cm	0,6 pF/cm
C_L	-	20 pF/2 cm
Z	100 Ω	25 Ω
τ	6 ns/m	25 ns/m

CAPACITANCE OF THE CONNECTOR CONTACT ~ 5pF

CAPACITANCE OF THE PRINTED WIRE ~ 5pF

CAPACITANCE OF THE TRANSCEIVER (I/O) ~ 10pF

LUMPED CAPACITANCE C_L ~ 20pF

FOPE_ADDSBuSys97.ppt Jan97

A signal line on a backplane bus compared to a signal line on a board is just the same wire with the same capacitive-layer (0.6pF/cm) and inductive layer (5nH/cm) with the only difference, that on a bus-line every 2 cm an additional capacitance adds to the capacitive-layer:

- a connector with a capacitance of 5pF
- a stub line on the plug-in-board (5pF) and
- the I/O-pin of a transceiver (10pF).



This 20pF additional capacitance, added every 2 cm, dramatically increases the capacitive layer from 0.6pF/cm to 20.6pF/cm. If we look at the basic equations

$$Z_0 = \sqrt{\frac{L'}{C'}}$$

$$\tau_0 = \sqrt{L' \times C'}$$

we can calculate an extreme decrease of the characteristic impedance from 100 Ω to 25 Ω and a massive increase of the signal propagation delay time from 6ns/m to 25ns/m.

Transmission Line Parameter

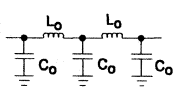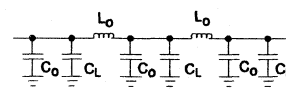		UNLOADED	LUMPED LOADING
			
INDUCTANCE	nH/cm	L_0	L_0
CAPACITANCE	pF/cm	C_0	$C_0 + C_L$
LINE IMPEDANCE	Ω	$Z_0 = \sqrt{\frac{L_0}{C_0}}$	$Z = \sqrt{\frac{L_0}{C_0 + C_L}} = Z_0 \sqrt{\frac{1}{1 + C_L/C_0}}$
PROPAGATION TIME	ns/m	$\tau_0 = \sqrt{L_0 C_0}$	$\tau = \sqrt{L_0 (C_0 + C_L)} = \tau_0 \sqrt{1 + C_L/C_0}$
CUT OFF FREQUENCY	Hz	$f_0 = \infty$	$f_0 = \frac{1}{2\pi \sqrt{L_0 (C_0 + C_L)}}$



This table is an overview of the basic formulae of transmission line theory. It compares unloaded signal traces and loaded bus-lines.

Digital Design Seminar

Line Driver SN74ALSxxx

Line driver SN74ALS245 ($I_{OL} = 24\text{mA}$)
 $Z_O = 30\ \Omega$; $\tau = 8\ \text{ns}$; $L = 32\ \text{cm}$
 No line termination
 Output impedance of the driver $\approx Z_O$
 (impedance matching)

A: Signal at driver output
 B: Signal at line end

- ★ No incident wave switching
- ★ valid logic levels after $2 \times \tau$
- ★ owing to matching of driver output impedance and line impedance, no undershoots
- ★ not applicable in fast systems with long bus lines

FOPE: \DMS\Bussyst.ppt Jan97

The output impedance of an SN74ALS245 pull-up transistor is in the range of $35\ \Omega$ and is therefore higher than the impedance of the bus line ($30\ \Omega$). The incident wave of the rising edge, which is calculated from the resistor divider, output impedance of the driver and line impedance, therefore is about

$$V_{\text{Incident}} = V_{OL} + (V_G \frac{30\ \Omega}{30\ \Omega + 35\ \Omega}) = 0.3\text{V} + (3.3\text{V} \times 0.46) = 1.8\text{V}$$

For the falling edge the situation is not much better. The pull-down transistor has a output impedance in the range of the line impedance and so the incident wave on the falling edge is again slightly below 2V.



Because of this physical situation, valid logic levels on the bus-line are available after the reflected wave comes back from the end of the line ($2 \times \tau$).

This type of bus-driver is not applicable for fast systems with long bus lines.

Digital Design Seminar

TTL-Bus

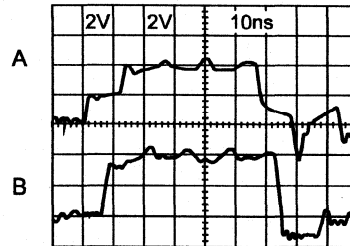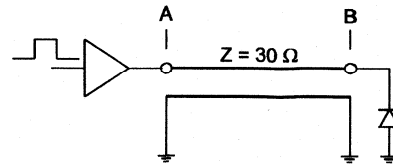SN74ABT240, No Line Termination, only Clamping Diode



- ★ The driver output reaches high level (>2 Volts) only after twice the propagation time
- ★ Negative undershoot at the line end is limited by the clamping diode


FOPE \DDSBusyst.ppt Jan97



If we take a driver of the latest BiCMOS technology for 5V supply voltage, the SN74ABT240, the output drive capability at the low level is higher than for the SN74ALS240 and hence the incident wave at the falling edge reaches a value of about 1V. But with the advantage of incident wave switching at the falling edge comes the disadvantage of a tremendous undershoot at the end of the signal line. In this situation we need at least a clamping diode at the line-end to limit the undershoot to about -0.7V.

The higher output impedance of the pull-up transistor still generates a incident wave below 2V at the rising edge and thus no incident wave switching is possible here.

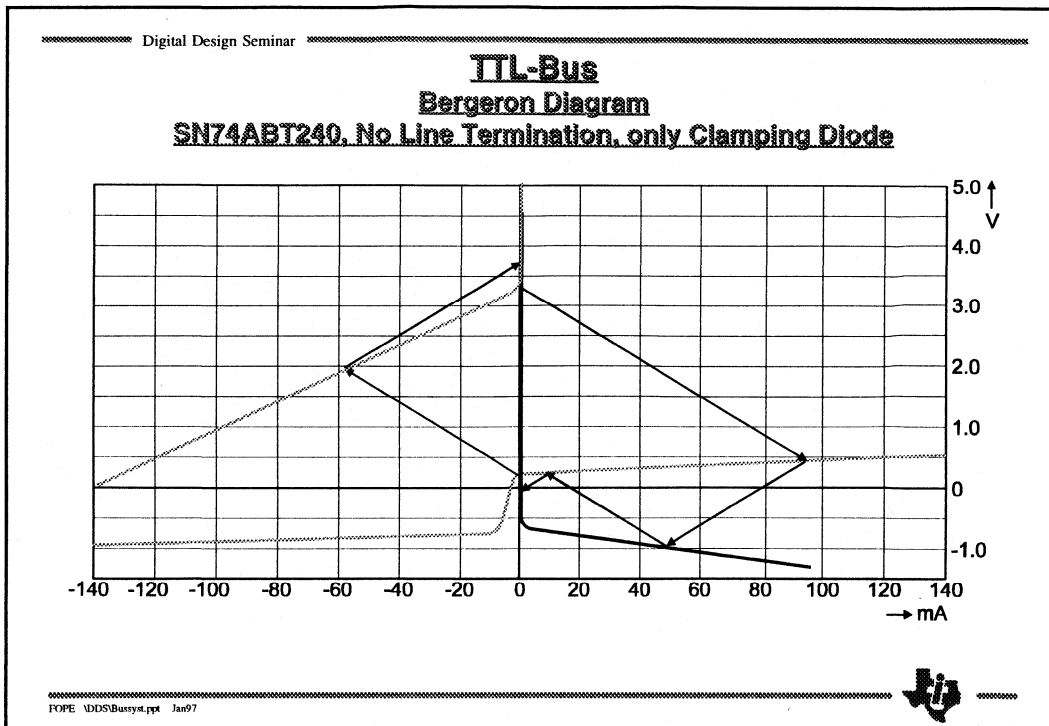For a fast system with a long bus this modern technology still is not able to switch all slopes with the incident wave.



The Bergeron Diagram shows the behaviour of an SN74ABT240 which is driving a transmission line of 30Ω with a clamping diode at the end of the transmission line. A comparison between the measurement on the page before and the theoretical discussion here shows good correspondence.

Digital Design Seminar

TTL-Bus


SN74ABT240, Line Termination with Thevenin Network

The diagram shows a circuit for line termination. On the left, a square wave pulse is applied to the input of an SN74ABT240 buffer. The output of the buffer is labeled 'A' and is connected to a transmission line with impedance $Z = 30\Omega$. The other end of the transmission line is labeled 'B'. At node B, there is a pull-up network consisting of a 180Ω resistor connected to a $+5V$ supply and a 220Ω resistor connected to ground. The output of the buffer at node B is also connected to a diode (likely a Schottky diode) which is connected to ground. To the right of the circuit is an oscilloscope showing two waveforms, A and B. The vertical scale is $2V$ and the horizontal scale is $10ns$. Waveform A shows a rising edge that is significantly higher than the $2V$ level, and waveform B shows a similar rising edge. Both waveforms show a sharp falling edge.

- ★ Incident positive wave has an amplitude >2 Volts
- ★ Line reflections are sufficiently dampened by a 100Ω termination

FOPE \DDSB\buscy4.ppt Jan07



An additional Thevenin termination network of 180Ω to V_{cc} and 220Ω to GND at the end of the transmission line reduces the output impedance of the pull-up driver, a combination of the ABT240 and termination network, and thus helps us at the rising edge. This lifts the incident wave of the rising edge above the $2V$ hurdle and now we are able to switch the rising and falling edge with the incident wave.

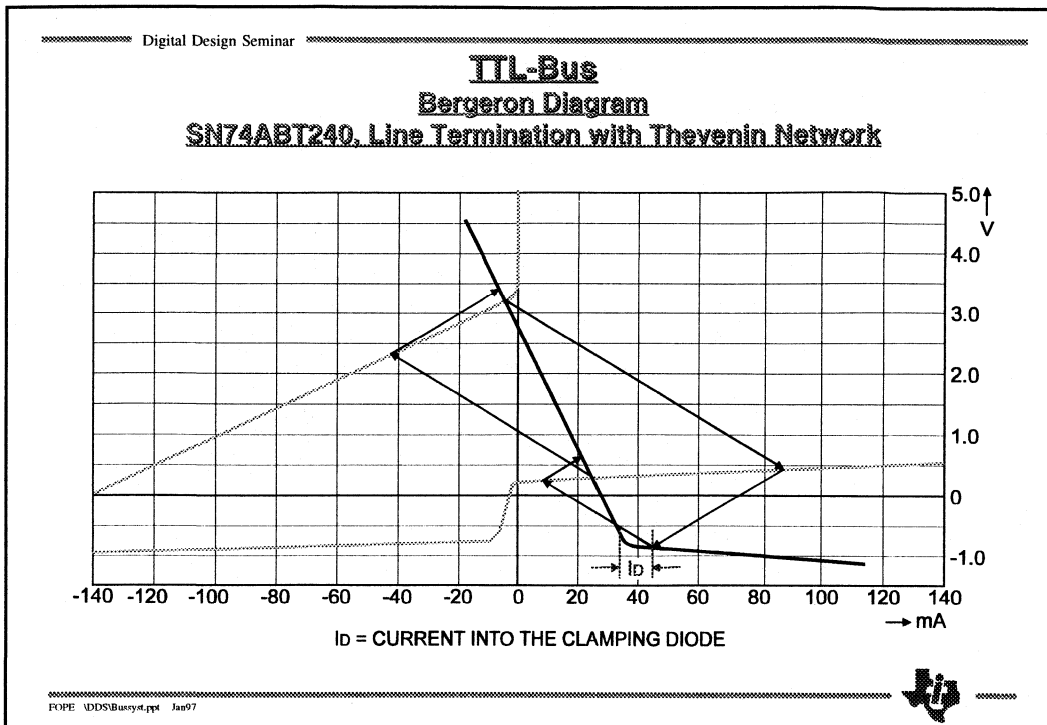

The Bergeron Diagram shows the behaviour of an SN74ABT240 driving a transmission line of 30Ω with a Thevenin termination network of 180Ω to V_{cc} and 220Ω to GND and a clamping diode at the end of the transmission line. A comparison between the measurement on the page before and the theoretical discussion here shows good correspondence.

..... Digital Design Seminar

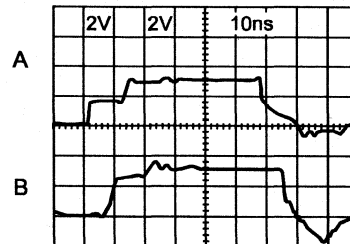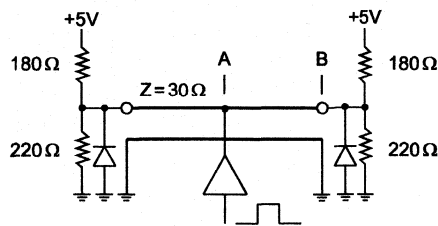TTL-Bus
SN74ABT240, Driver in the Middle of the Bus, Thevenin Termination



- ★ Effective load = 15 Ω
- ★ Driver output reaches high level only after the reflected wave is returned from the line end
- ★ Line reflections are dampened sufficiently by the termination network


FOPE ADUS\Busysyst.ppt Jan97



In the examples on the previous pages the bus-driver had to drive a transmission line with a impedance of 30Ω. But in real bus application only two drivers sit at the ends of the signal line and most of the bus-drivers are located in the middle of line. These drivers in the middle of the line now have to drive a 30Ω line to the left and a 30Ω line to the right side with an overall impedance of 30Ω || 30Ω = 15Ω.

Although we are using Thevenin termination networks and clamping diodes on both ends of the signal line, the SN74ABT240 in this situation is not able the switch the bus-level with the incident wave from low to high or vice versa. The output impedance of the driver is too high to generate a reasonable output voltage. For the calculation we need the resistor divider of the driver's output-impedance R_G and line impedance Z_0 :

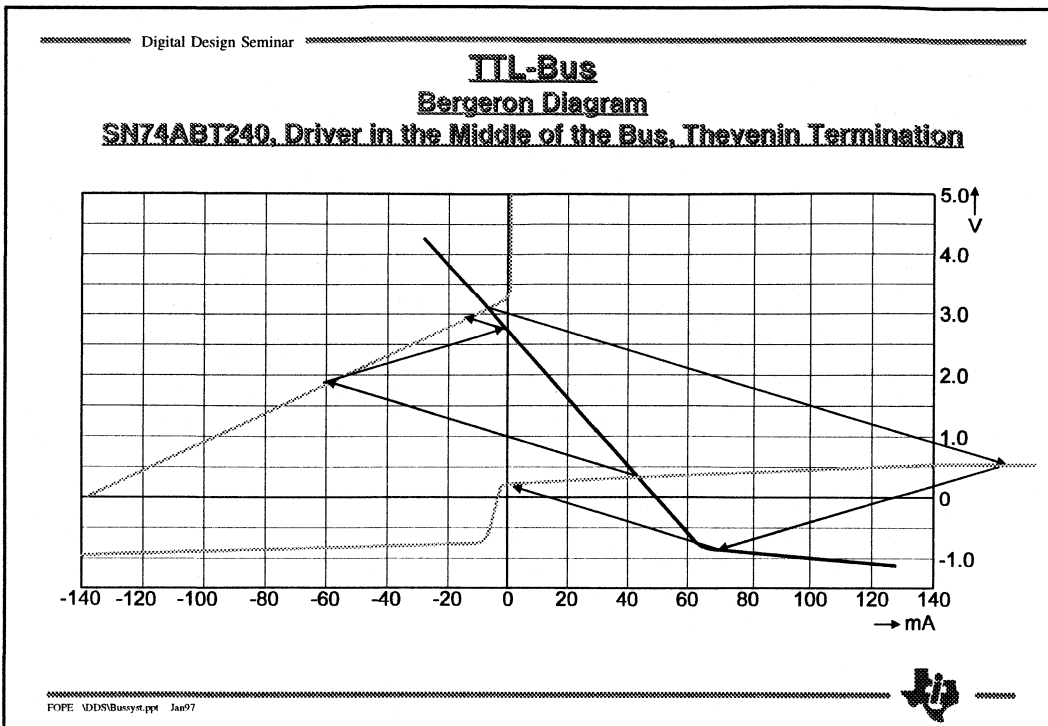
$$V_{\text{Incident}} = V_G \frac{Z_0}{Z_0 + R_G}$$




This Bergeron Diagram shows the behaviour of an SN74ABT240 driving two transmission lines of 30Ω equivalent to one 15Ω -line with a Thevenin termination network of 180Ω to V_{CC} and 220Ω to GND, and a clamping diode at both ends of the transmission line. A comparison between the measurement on the page before and the theoretical discussion here shows good correspondence.

..... Digital Design Seminar

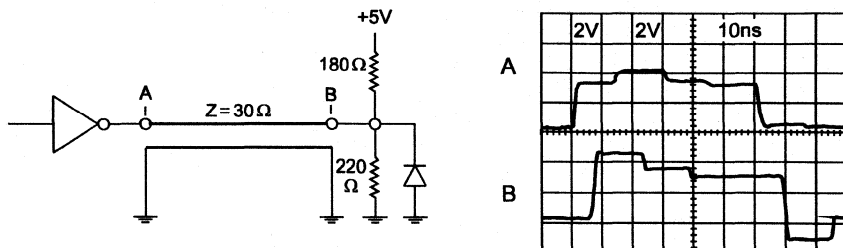TTL-Bus
'IWS'-Line Driver SN74ABT25xxx
IWS Driver, Thevenin Termination




- ★ IWS (= Incident Wave Switching) drivers have a greatly improved drive capability in the high state
- ★ High level at the driver output is achieved with the incident wave

FOPE \DDSBussyst.ppt Jan97 

The main reason for the low amplitude of the incident waves is the impedance of the driver-output which is too high compared with the low impedance (30Ω) of a bus-line. Often a driver is sitting in the middle of a bus and has to drive two 30Ω lines in parallel. As a result of this physical situation we need a driver with an extremely low output impedance to be able to switch a bus line with the incident wave.

The Texas Instrument IWS drives family (SN74ABT25xxx) has a guaranteed high level DC output current $I_{OH} = -80\text{mA}$ and low level DC output current $I_{OL} = 188\text{mA}$. This is possible only, because the output impedance for low and high level is below 2Ω . Such a low impedance driver easily generates incident waves above 3.3V at the rising edge and below 0.5V at the falling edge when driving a 30Ω line. If the load is 15Ω , it still reaches more that 3.2V and less than 0.6V with the incident wave.

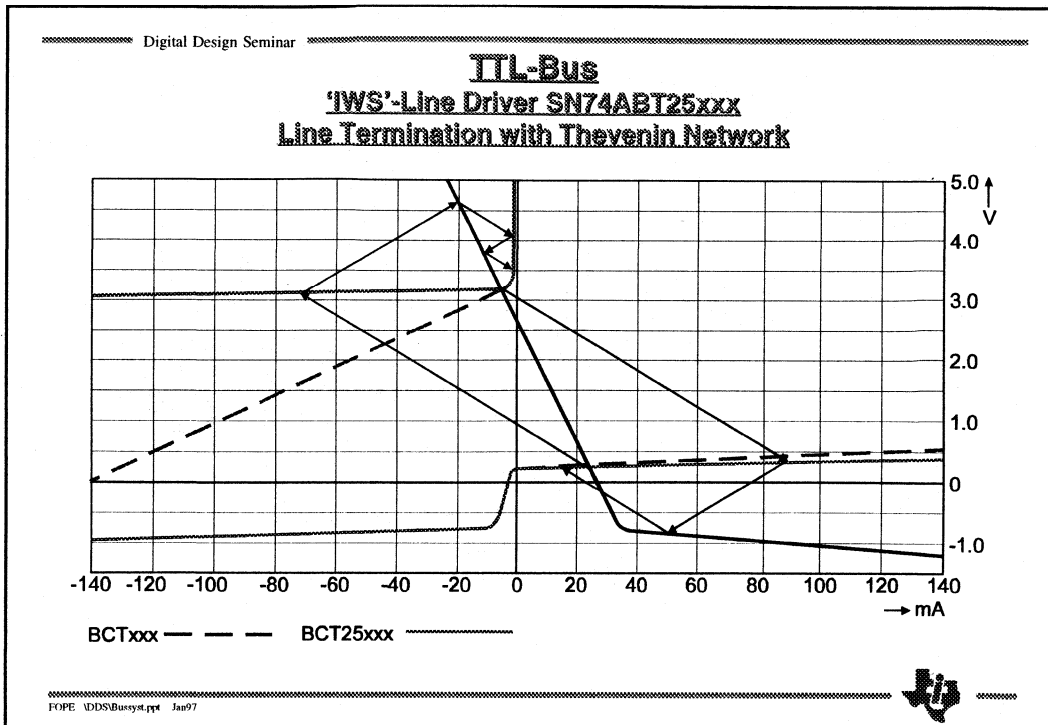The IWS-line drivers SN74ABT25xxx are the ideal solution for fast, TTL-compatible systems with long bus-lines.



Here the Bergeron Diagram shows the behaviour of an SN74ABT25240 IWS-line-driver driving a transmission line of 30Ω with a Thevenin termination network of 180Ω to V_{cc} and 220Ω to GND and a clamping diode at the end of the transmission line. A comparison between the measurement on the page before and the theoretical discussion here shows good correspondence.

Digital Design Seminar

Enhanced Transceiver Logic - ETL

Benefits:

- ★ Extends life of TTL characteristic bus
- ★ Enhanced noise margin
- ★ Supports live insertion
- ★ Lower part-to-part skew
- ★ Higher driver capability

Characteristics:

- ★ Tighter input threshold (1.4 ... 1.6 V)
- ★ Input circuit is current mode switch (compensates for temperature, voltage, process)
- ★ Precharge function (to 1.5 V) added to minimize capacitive discharge to active backplane
- ★ VCC-BIAS used to control high impedance state during live insertion

Products:
SN74ABTE16245, SN74ABTE16246

The chart shows voltage levels in Volts (V) on the y-axis (0 to 2.8). For ETL, V_{OH} is approximately 2.4V, V_{IH} is approximately 1.6V, V_{IL} is approximately 1.2V, and V_{OL} is approximately 0.4V. For TTL, V_{OH} is approximately 2.4V, V_{IH} is approximately 2.0V, V_{IL} is approximately 0.8V, and V_{OL} is approximately 0.4V. The circuit diagram shows a differential amplifier with a +1.5V precharge source connected to the inputs. The inputs are labeled 'LOCAL BUS' and 'VME BUS'. A 'LIVE INSERT' signal is connected to the precharge circuit.


FOPE \DDSBusyst.ppt Jan97

To increase the speed of the VME-bus the new VME-64 has been defined. The physical layer of this VME-64 is called the Enhanced Transceiver Logic (ETL).

Here the standardization committee found another way to speed up the bus system and still keep backwards compatibility to the older TTL-compatible VME-bus. With differential amplifiers at the inputs, the threshold (1.5V) is better defined than with the common TTL-inputs and so V_{IL} can be defined to be below 1.4V (TTL: $V_{IL} < 0.8V$) and V_{OH} above 1.6V (TTL: $V_{OH} > 2V$). With this modification we gain room for the incident waves at the inputs which now have to jump above 1.6V instead of 2V and below 1.4V instead of 0.8V for standard TTL devices.

The specification also includes the precharge feature for live insertion. Each pin has an overall capacitance of about 20pF. If a card is inserted while the system is running, the precharge feature charges the 20pF capacitance of each signal-pin to the threshold (1.5V) before the pins are connected to the bus-lines. This makes sure that the voltage spike, which is generated by changing the capacitance of the pins to a valid logic high or low level, never exceeds the threshold.

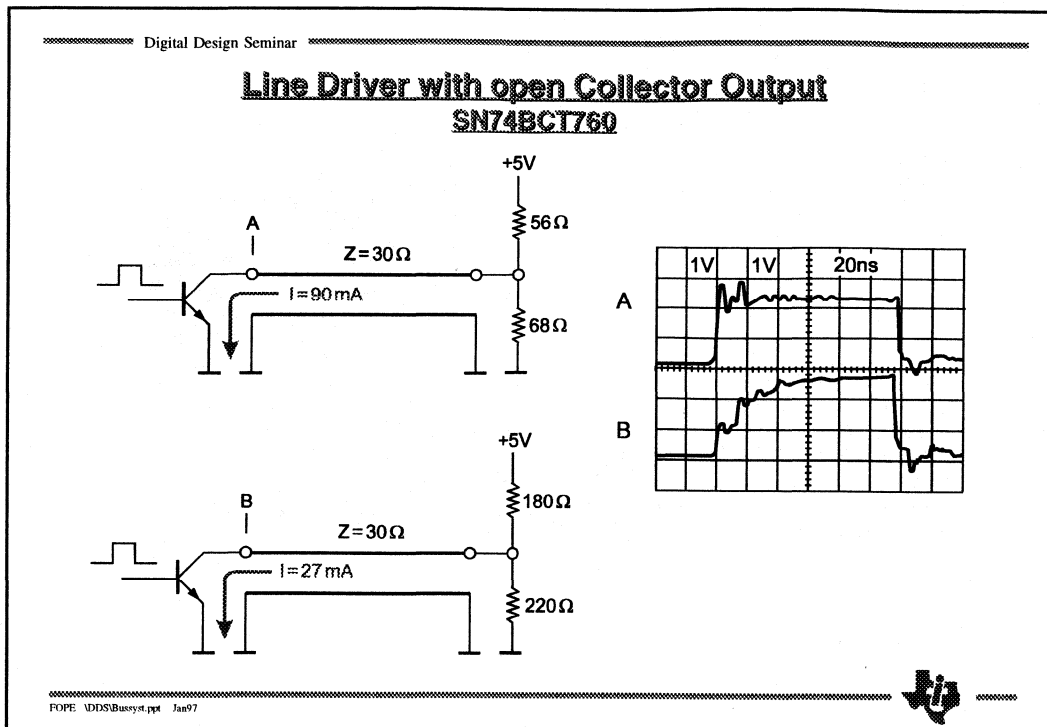SN74ABTE16245 and SN74ABTE16246 are TI's offer of bus transceivers to the ETL specification.




Always some bus-signals are carried out in open collector or open drain mode. In these cases, the falling edge is actively generated by the driver, and knowledge about TTL-drivers on bus systems shown previously is also valid here: Only a low impedance driver can switch the bus with the incident wave.

The rising edge is generated by the passive pull-up-network. If we choose a pull-up-network with a output impedance like the impedance of the bus-line, then we see a excellent rising edge at the driver output with the disadvantage of a tremendous low-level-current of 90mA for one signal-trace.


Because this current is not acceptable we change the output impedance of the pull-up-network to about 100Ω . Now for the rising edge, a driver with 100Ω tries to pull-up a transmission line of 30Ω with the result that we have to wait for several reflections of the bus-signal until we reach a valid logic high level.

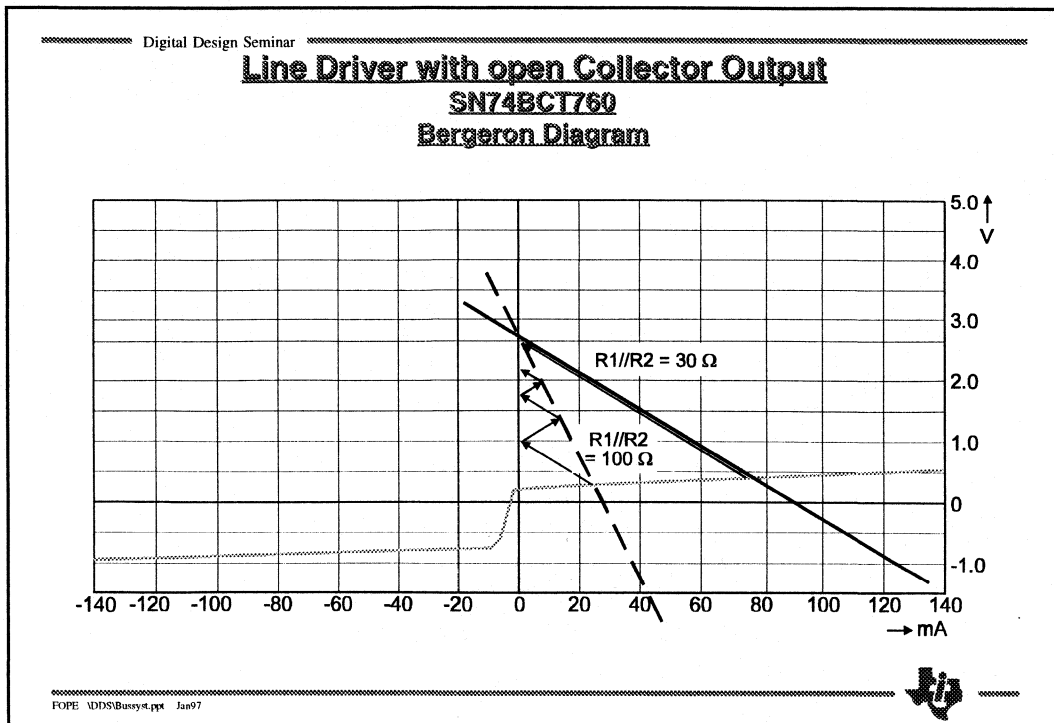Remember: Rising edges on open-collector bus-lines are always slow ... and there is no generally valid work around.



This Bergeron Diagram shows the behaviour of the rising edge of a open collector bus-line. A pull-up-network with an impedance of 100Ω compared to a 30Ω network is driving a transmission line of 30Ω. A comparison between the measurement on the page before and the theoretical discussion here shows good correspondence.

CMOS-Bus SN74HCxxx/SN74AHCxxx

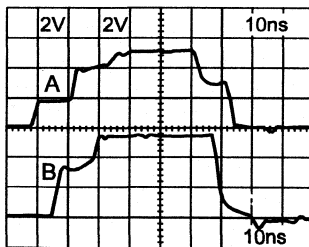

Bus driver SN74HC245

$Z_0 = 30 \Omega$; $\tau = 8 \text{ ns}$; $L = 32 \text{ cm}$

Output impedance of the driver $> Z_0$

No line termination

A: Signal at driver output

B: Signal at line end

- ★ No incident wave switching
- ★ Valid logic level after $2 \times \tau$,
in worst case only after $4 \times \tau$
- ★ Due to the high output impedance of
the driver no termination necessary
- ★ Not applicable with long bus lines



After a detailed look at the behaviour of bipolar outputs connected to a backplane-bus, we now look at CMOS outputs driving a backplane bus.

The low drive capability, and therefore high output impedance, ($\approx 25\Omega..35\Omega$) of HCMOS devices and AHC devices makes it impossible to switch bus lines with the incident wave. Under worst case situations the signal settles after four times the propagation delay time of the signal on the bus line. For short buses and/or slow systems HC or AHC could be an acceptable solution.

Digital Design Seminar

CMOS-Bus SN74ACxxx


Bus driver 74AC245
 $Z_o = 30 \Omega$; $\tau = 8 \text{ ns}$; $L = 32 \text{ cm}$
Output impedance of the driver $> 10 \Omega$
Line termination $R = 100 \Omega$ and diodes
A: Signal at driver output
B: Signal at line end

- ★ Low Signal distortion and low reflections due to line termination and clamping diodes
- ★ Incident wave switching capability sufficient for TTL compatible circuits

FOPE \DDSI\BusSys.st.ppt Jan97

Advanced CMOS (SN74ACxxx) drivers have, with an output impedance of about 10Ω , the highest drive capability and lowest output impedance of all CMOS outputs. Because of this, incident wave switching is possible, especially for TTL compatible circuits (SN74ACTxxx). The high voltage swing of 5V and the low output impedance make the presence of line termination and clamping diodes necessary.

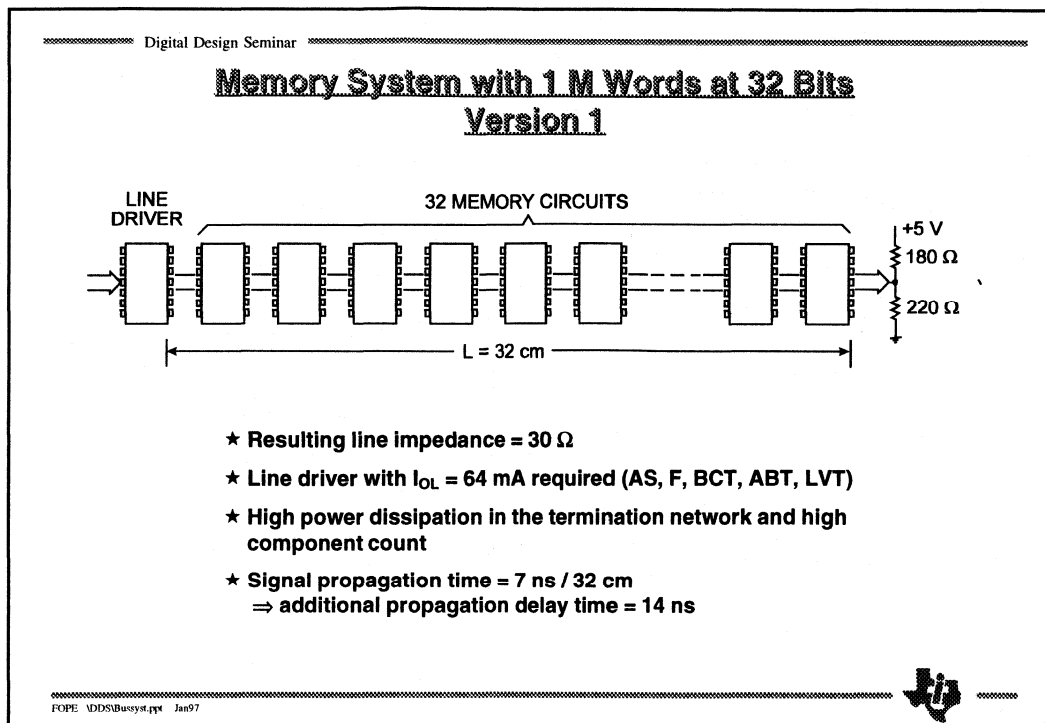
Advanced CMOS drivers generate a high current spike at the supply current because of the high voltage swing and the fast rise/fall times. These current spikes generate a lot of electromagnetic noise (EMC) and so Advanced CMOS is not the first choice in big backplane systems.



Besides huge backplane busses there are also smaller busses in computer systems: e.g. a memory bus on a processor board. These memory busses add, for each 2 cm length, the capacitance of one I/O pin (10pF) to the capacitive layer of the signal trace. So the capacitive layer changes from 0.6pF/cm to 10.6pF/cm, exactly the same value we see on backplane busses with 20pF connected each 2cm. As a result the impedance of the signal trace is about 30Ω and the propagation delay time of the trace about 20ns/m.

In the example above, 32 memory chips are placed in one row and this leads to a line length of about 32cm and a signal delay time of 7ns along the bus-line. When a memory read takes place we have to add two times the propagation delay time of the trace ($2 * 7\text{ns} = 14\text{ns}$) to the RAM access time. This additional delay time comes only from the wire on the boards, and not from the delay time of active electronics like the bus transceiver.

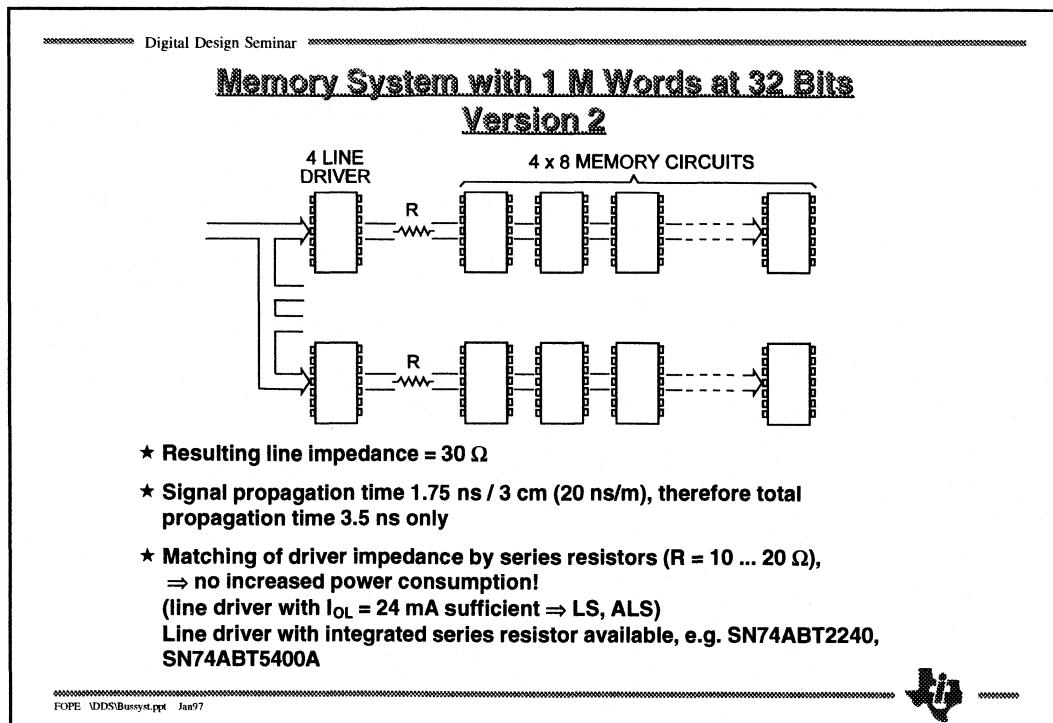
Because of the 7ns delay on the signal line is longer than the rise-/fall-time of the signal, the designer has to terminate the line in parallel to avoid signal reflection, which would increase the settling time of the signal on the trace beyond the delay time of 7ns. DC-current through the termination network is the result.



Here the design of the previous page has been modified to speed up the RAM access. Now the 32 RAM chips are located in 4 rows of 8 memory devices. In this case the length of the bus trace is only 8 cm, and the propagation delay time along this line is 1.75ns.

The calculation of the access time shows now 3.5ns for the wire, which has to be added to the RAM access time. With 3.5ns compared to 14ns of the previous example, the RAM access has been improved by more than 10ns. Now the designer can choose RAMs with an access time which are 10ns slower. The cost of cheaper RAM circuits more than offsets the increased cost of the four instead of one bus-transceiver.

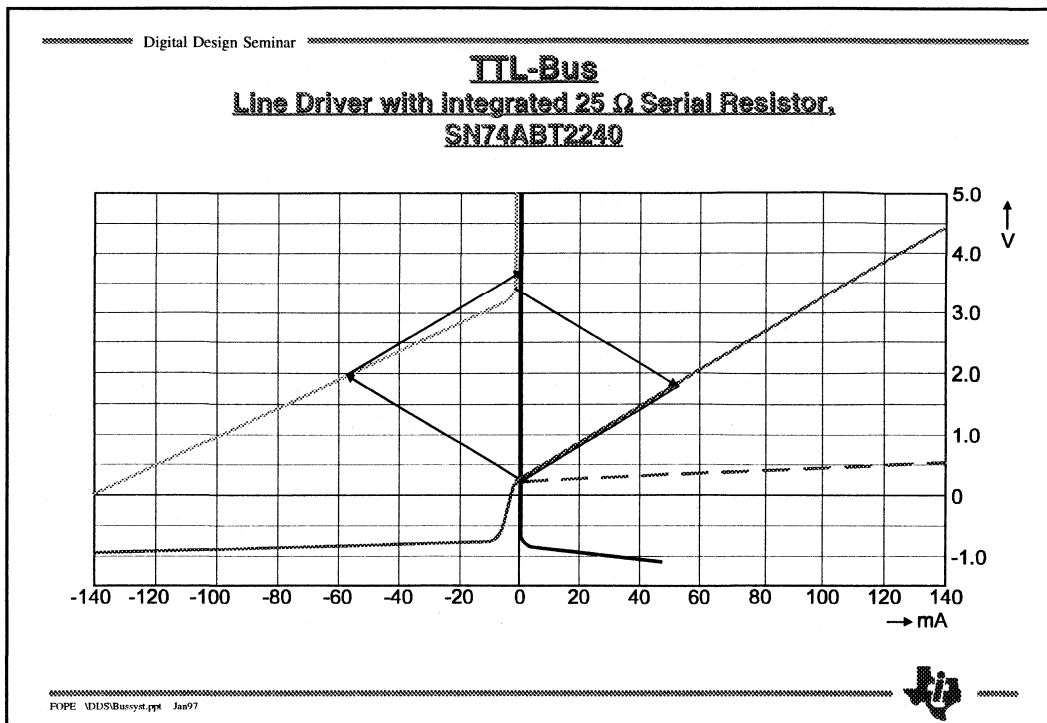Now twice the signal delay time (3.5ns) is in the range of the rise/fall time of a typical digital signal and hence parallel termination is no longer necessary. Serial termination has been selected to avoid undershoots that could lead to malfunction of the RAM circuits.



This Bergeron Diagram shows the behaviour of the rising and falling edge of a memory driver circuit with an output impedance of 30Ω driving a memory-bus line with an impedance of 30Ω . A comparison between the measurement on the page before and the theoretical discussion here shows good correspondence.

Digital Design Seminar

Backplane Transceiver Logic - BTL

- ★ Reduced voltage swing: $V_L = 1V$; $V_H = 2.1V$
- ★ High drive capability: $I_{OL,max} = 100\text{ mA} \Rightarrow$ Incident wave switching down to 10Ω or $2 \parallel 20\Omega$ line impedance
- ★ Correct line termination by a pull-up resistor at the line end avoids line reflections
- ★ Decoupling diode reduces output capacitance to $< 5\text{ pF} \Rightarrow$ increased line impedance
- ★ Maximum output edge rate $2\text{ ns} \Rightarrow$ Trapezoidal wave-form reduces system noise
- ★ Supports live insertion/withdrawal \Rightarrow Output high impedance when $V_{CC}=0V$
 \Rightarrow Power-up 3-state control at outputs
 \Rightarrow BIAS V_{CC} pin to pre-charge BTL outputs
- ★ Differential amplifier guarantees stable threshold voltage of the receiver


FOPE_ADDS\Bussyst.ppt Jan97

One of the problems of TTL or CMOS circuits driving bus lines come from the high voltage swing: no correct termination is possible and big ICC current spikes are necessary to enable incident wave switching. A bus system with reduced voltage swing could solve a lot of problems.

The physical layer of the Future-Bus is called Backplane Transceiver Logic (BTL) and works with a voltage swing of 1.1V only. The bus system is open collector. The low level of 1V is generated by the saturation voltage of the pull-down transistor and the forward voltage of the serially connected diode. The high level of 2.1V comes from the termination resistor connected to a termination voltage of 2.1V. The value of the termination resistor is equal to the impedance of the bus-line and therefore the bus-line is terminated correctly. For safe detection of the logic levels, the inputs are designed with differential amplifiers and a threshold at 1.55V, exactly in the middle of the voltage swing.

To reduce ICC current spikes, the fall-time is defined to be at least 2ns. The rise time is not generated by active electronics, but by the pull-up resistor.

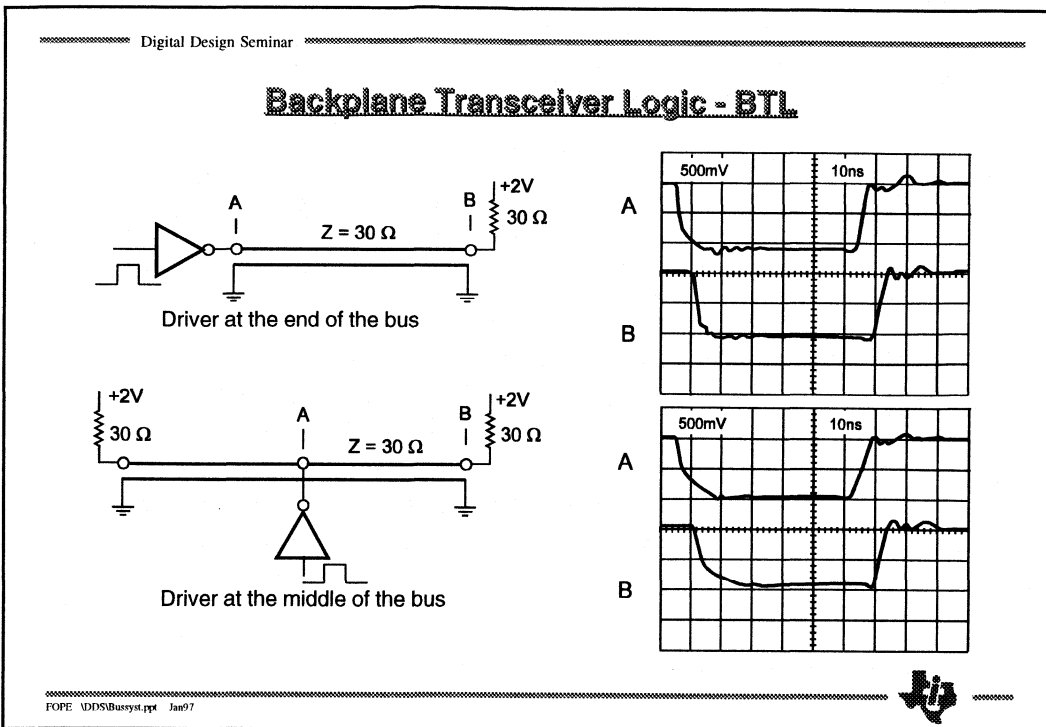All necessary features for live insertion and withdrawal have been included: The outputs are in high impedance when $V_{CC}=0V$ and during power up/down (Power-up 3-state). The pre-charge feature reduces voltage spikes when the I/O connects to the bus-line (see ETL logic).



Measurements of BTL circuits driving 30Ω bus-lines show excellent wave forms. In the upper example a BTL output drives a point-to-point connection with a characteristic impedance of 30Ω and a termination resistor of 30Ω at the end of the line. In the second example the BTL driver is sitting in the middle of the bus-line, driving two signal traces of 30Ω. Both lines are correctly parallel terminated with 30Ω pull-up resistors.

***** Digital Design Seminar *****

Backplane Transceiver Logic - BTL

- ★ TI offers BTL to TTL converter
- ★ Bus width from 7-bits to 18 bits
- ★ Transceivers with and without registers or latches are available

SN74FB1650	100-PIN SQFP	18-Bit Universal Storage Transceiver
SN74FB1651	100-PIN SQFP	18-Bit Universal Storage Transceiver
SN74FB2031	52-PIN PQFP	9-Bit Address/Data Transceiver
SN74FB2032	52-PIN PQFP	9-Bit Competition Transceiver
SN74FB2033	52-PIN PQFP	8-Bit Registered Transceiver
SN74FB2040	52-PIN PQFP	8-Bit Noninverting Transceiver
SN74FB2041	52-PIN PQFP	7-Bit Noninverting Transceiver

FOPE \DDSB\Busyst.ppt Jan97



All the circuits TI offers are bi-directional BTL to TTL converters. The designer can choose from 7 to 18-bit bus-width and gets bus functions with and without registers and/or transparent latches.

Digital Design Seminar

Gunning Transceiver Logic - GTL

- ★ Reduced voltage swing: $V_L = 0.4V$; $V_H = 1.2V$
- ★ Low drive capability: $I_{OL,max} = 40\text{ mA} \Rightarrow$ Incident wave switching down to 20Ω or $2 \parallel 40\Omega$ line impedance \Rightarrow Low power dissipation ($0.4V \times 40mA$ per output)
- ★ Correct line termination by a pull-up resistor at the line end avoids line reflections
- ★ High data rates ($> 100\text{ MBit/s}$)
- ★ Integration of line driver and receiver into ASICs possible
- ★ Doesn't support live insertion/withdrawal \Rightarrow Output high impedance when $V_{CC}=0V$
- ★ Differential amplifier guarantees stable threshold voltage of the receiver

FOPE UDS/Busysyst.ppt Jan97

The basic concept of a GTL bus is very similar to a BTL system.

Because of the missing diode in the open collector/drain outputs the low level is 0.4V. With a chosen high level of 1.2V the voltage swing is reduced to 0.8V only. Again the threshold is in the middle of the voltage swing at 0.8V.

The drive capability of GTL outputs is defined to be 40mA, which enables a output to drive one termination resistor of $0.8V / 40mA = 20\Omega$. If the bus line is terminated correctly, the lowest impedance that can be driven by a GTL driver in the middle of a bus now is 40Ω (in both directions: $40\Omega \parallel 40\Omega = 20\Omega$).

On the previous pages, the heavily loaded backplane-bus always had a line impedance of 25Ω to 30Ω . Here we see that a 40Ω bus is not heavily loaded and GTL was designed for a smaller bus on a board, e.g. between a processor and it's memory. Because the target application for GTL is not a backplane bus, but a bus on a board, no requirements for live insertion/withdrawal have been included into the specification.

As a result of the 0.8V swing and the 40mA I_{OL} the maximum power dissipation of one output is 16mW. It is thus possible to integrate these low power drivers into ASICs.

..... Digital Design Seminar

Gunning Transceiver Logic - GTL

- ★ TI offers GTL and GTL/GTL+ to TTL converter
- ★ Bus width from 7-bits to 18 bits
- ★ Transceivers with and without registers or latches are available

Released:

SN74GTL16612	56-PIN SSOP/TSSOP	18-Bit Universal Storage Transceiver
SN74GTL16616	56-PIN SSOP/TSSOP	17-Bit Universal Storage Transceiver with buffered clock output
SN74GTL16622	64-PIN TSSOP	18-Bit GTL/GTL+ Registered Transceiver


Planned:

SN74GTL16922	64-PIN TSSOP	18-Bit GTL/GTL+ Registered Transceiver accepts TTL-compatible CMOS signals (0V/5V) at TTL-inputs.
---------------------	---------------------	--

..... FOPE \DUS\Busyst4.ppt Jan97



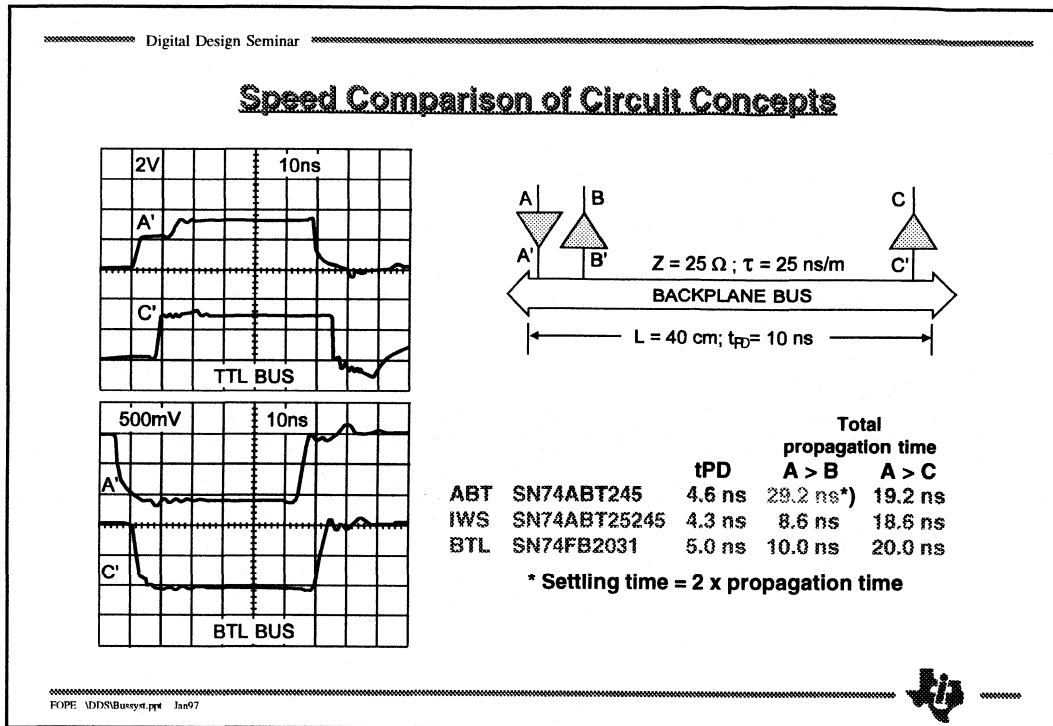All the circuits TI offers are bi-directional GTL to TTL converters. The designer can choose between 17- and 18-bit bus-width and select bus functions with and without registers and/or transparent latches. The SN74GTL16616 also includes a separate buffered path for the clock signal.



As a summary of the bus system section a comparison between three bus concepts is shown. To find out the bus speed, an investigation of the propagation delay times from input A to the outputs B and C is done:

Example 1:

ABT circuits are quite fast buffers with a max. propagation delay time of 4.6ns only. Because they are not able to switch a bus signal with the incident wave, we have to wait until the reflected wave travels back to the input B'. Now the overall max. delay time from input A to output B is 29.2ns.


Example 2:

The usage of the SN74ABT25245 IWS (Incident Wave Switching) driver enables incident wave switching. Here the propagation delay time from input A to output B is 8.6ns only and the speed limiting path is now from input A to output C with 18.6ns - still more than 10ns faster than example 1 with SN74ABT245.

Example 3:

On a backplane bus, BTL drivers show about the same speed as IWS drivers. With correct parallel line termination and the reduced voltage swing we get excellent wave-forms combined with very low noise.

Supply Current at Floating CMOS-Inputs

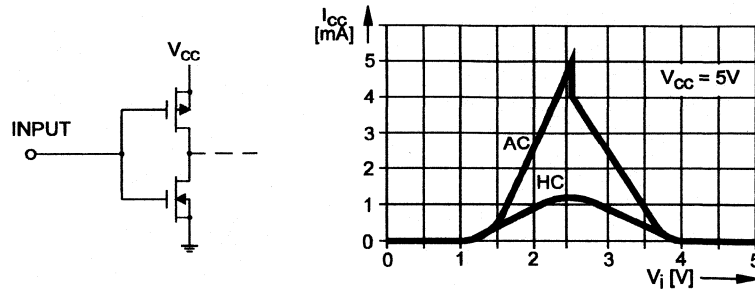

When the input voltage of a CMOS circuit is between the defined voltage levels (low or high) -e.g. floating-, the P- and N-Channel transistors conduct simultaneously. This results in increased supply current.



Besides the different bus concepts there are some problems that can be seen on most bus systems. One of these problems is a floating bus line which leads to an open input.

The diagram above shows an input of any standard CMOS or BiCMOS circuit. Normally this input sees only 0V (low) or 5V (high) and in this case one of the two transistors is ON and one is OFF. Hence nearly no supply current is flowing from V_{CC} to GND.

If CMOS inputs are connected to a floating bus line, any voltage between V_{CC} and GND can be observed. With the input voltage close to the threshold value, both transistors are partly switched ON and now supply current (I_{CC}) can flow from V_{CC} to GND.

The graphic shows this behaviour of HC and AC circuits: With an input voltage of 2.5V the supply current of a HC circuit can rise more than 1mA per input. Looking at a 32-bit bus with 10 modules the increase of I_{CC} here can be $32 \times 10 \times 1\text{mA} = 320\text{mA}$! Using Advanced CMOS (AC) circuits will result in a 5 times higher current, in this example $5 \times 320\text{mA} = 1.6\text{A}$.

Digital Design Seminar

Oscillation on a Floating Bus Line

INPUT (A)

BUS IN 3-STATE

OUTPUT (B)

$f = 60 \dots 80 \text{ MHz}$

$$\frac{\Delta V}{\Delta t} = \frac{\sum I_i}{C_B} \approx \frac{500 \mu\text{A}}{500 \text{ pF}} = 1 \text{ V}/\mu\text{s}$$

- ★ When a bus line is left floating, the line is charged by the input currents of the receivers attached to the bus up to the threshold voltage.
- ★ The feedback via the GND inductance L_{GND} causes an oscillation. The resulting output stage currents I_o of these circuits overload and destroy the devices.

FOPE \DDSBussyst.ppt Jan97

Another effect that can be seen on floating bus-lines is device oscillation:

When a bus line is left floating, it is charged by the leakage currents of all receivers-inputs attached to the bus-line (e.g. from L to H). When this leakage current charges the bus line above the threshold voltage, the output of the driver switches (e.g. from H to L). For this transition of the output a current spike is necessary and via the VCC and GND inductance L_{GND} the internal reference for the threshold voltage drifts away. The input voltage does not change, but the threshold changes and so the input of the driver reads a change in the logic input-level (e.g. back from H to L). Thus the output switches again (e.g. from L to H).

Under worse case conditions this behaviour can lead to a high frequency oscillation. The output stage currents I_o of the circuits involved overload the circuit and destroy the devices.

Digital Design Seminar

Bus Holders SN74ACT107x

- ★ Bus holders ensure valid logic levels in CMOS bus systems, when all drivers are inactive (3-state).
- ★ No pull-up resistors are required!
- ★ Integrated clamping diodes limit the under- and overshoots caused by line reflections and thus ensure system integrity.

Type	Function	Package
SN74ACT1071	10-Bit Bus Holder	16 Pin SOIC/SSOP
SN74ACT1073	16-Bit Bus Holder	20 Pin SOIC/SSOP

SN74ABTHxxx, SN74LVTHxxx,
SN74ALVCHxxx, SN74LVCHxxx

FOPE \DDSI\Busysyst.rpt Jan97


To address the problem of floating bus lines and open inputs TI made many investigations and look at various solutions to ease the design of bus systems.

One solution for floating bus lines is the Bus Hold circuit. This circuit holds the last valid logic level during the high impedance state and the floating bus line is held at a valid logic level. No other precautions have to be taken to avoid problems that arise from floating bus lines.

Bus hold circuits are included in the inputs of SN74ABTHxxx, SN74LVTHxxx, SN74ALVCHxxx and SN74LVCHxxx circuits. Ten or sixteen Bus-Hold circuits with integrated clamping diodes to V_{CC} as well as to GND are available as stand alone function under the device name SN74ACT1071 and SN74ACT1073.


Digital Design Seminar

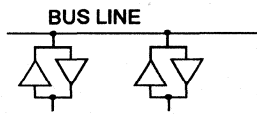Considerations of Floating Bus Lines (3-state)




★ Do nothing, if the duration of 3-state is $< 2 \dots 5 \mu\text{s}$ only.

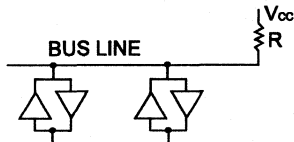★ Take no hardware precautions, but ensure no floating bus lines with bus protocol (e.g. PCI bus)



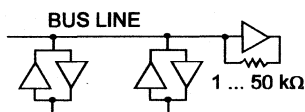★ Use pull up, pull down resistors or line termination networks to ensure defined voltage levels (high power dissipation!)



★ Terminate the bus line by a bus hold circuit which freezes the last active logic level.
No increase of supply current !

FOPE \DDSI\Busysta.ppt Jan97





Floating bus line normally only occur on bi-directional signal lines.

To avoid floating bus lines several actions can be implemented:

- ★ If the duration of the 3-state doesn't last longer than $2 \dots 5 \mu\text{s}$, the leakage currents can't charge the bus line into the threshold region.
- ★ With an intelligent bus protocol, long 3-state periods can be avoided. For example, the specification of the CPI bus claims: The last user of the bus has to drive the bus with any valid logic level, until the next module requests and gets the bus. This is an intelligent solution with low power consumption.
- ★ Any resistor network at the line-end, like pull-up or pull-down resistors or any line termination ensures defined logic levels during high impedance periods. This solution is not acceptable in low power environments.
- ★ Using bus-transceivers with integrated bus-hold cells or terminating the bus line by a bus hold circuit with integrated clamping diodes freezes the last active logic level. This is a good solution for low power systems.

Digital Design Seminar

Bus Conflicts

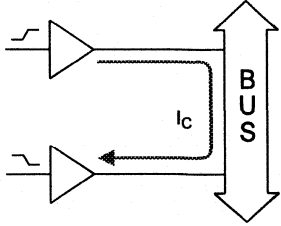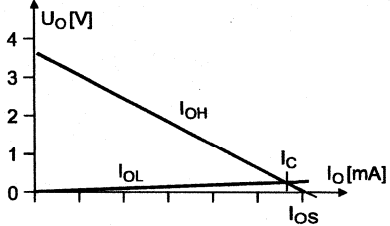



- ★ A bus conflict occurs when, from a timing mismatch, two line drivers apply different logic levels (voltages) to the bus at the same time.
- ★ The excessive output current $I_o (\approx I_{OS})$ causes a high power dissipation, which yields in a high chip temperature T_j .

$$T_j = T_a + P_{TOT} * R_{\theta ja}; (R_{\theta ja} = 80 \dots 100^\circ \text{ C/W})$$

Note: The chip temperature T_j must not exceed 150°C without dramatic reliability degradation (mechanical stress, etc.).

FOPE 'DDSBusyst.ppt Jan97



A bus conflict occurs when, from a timing mismatch, two line drivers apply different voltage levels to the bus at the same time. The excessive output current $I_o (\approx I_{OS})$ causes a high power dissipation, which yields in a high chip temperature T_j . According to the output characteristics the output that's driving a high-level is the "loser", but the designer can only observe a low-level voltage that's little bit higher than normal. In this situation the highest power dissipation can be observed in the output that's driving a high-level, because this output has a voltage drop of $(V_{OH} - V_{OL})_{typ.} \approx 3\text{V}$ and an output current flowing is in the range of $I_{OS} > 100\text{mA}$.

To find out whether a reliability problem could arise or not, a examination of the over all power dissipation is necessary. With the over all power dissipation P_{TOT} , the ambient temperature T_a and the thermal resistance of the package $R_{\theta ja}$, the chip temperature T_j can be calculated with the following formula:

$$T_j = T_a + P_{TOT} * R_{\theta ja}; (R = 80 \dots 100^\circ\text{C/W})$$

The chip temperature T_j must not exceed 150°C . Otherwise there is a risk of dramatic reliability degradation because of mechanical stress between the silicon, the metal of the lead-frame and the plastic of the package.

Bus Conflicts**Calculation of the Power Dissipation of a Line Driver**

$$P_{TOT} = P_Q + (P_S * t_s + P_O * 2t_p + P_C * t_C) * f * n$$

- P_Q = Quiescent power dissipation
 P_S = Average power dissipation caused by current spikes
 t_s = Duration of current spike
 P_O = Power dissipation caused by driving the transmission line
 t_p = Signal propagation time on the transmission line
 P_C = Power dissipation caused by the bus conflict
 t_C = Duration of the bus conflict
 f = Repetition rate
 n = Number of engaged outputs

The biggest contributors to the power dissipation are :


- 1) P_Q 2) P_C 3) P_O

Therefore short bus conflicts (duration < 50 ns, Duty-Cycle < 10%) are mostly uncritical when using (A)LS-, BiCMOS- and CMOS-circuits, but may be critical when using AS- and F-circuits.



To calculate the overall power dissipation, not only the power dissipation of the bus conflicts ($P_C \times t_C$) have to be taken into account, but also all the other sources like the quiescent power dissipation P_Q , the average power dissipation caused by the current spikes ($P_S \times t_s$) and the power dissipation caused by driving output loads (e.g. transmission line) P_O must be included into the calculation.

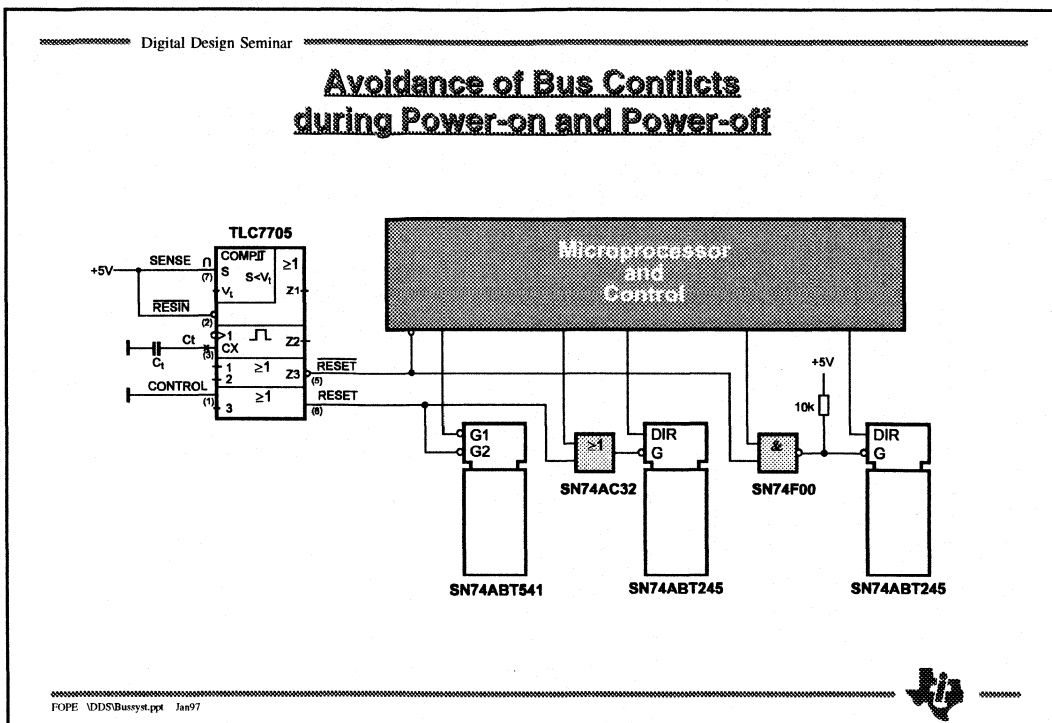Under typical conditions, bus conflicts that are shorter than 50ns with a duty-cycle of less that 10% are mostly uncritical when using LS, ALS, BiCMOS and CMOS circuits. It may be critical for AS or F circuits.




Bus conflicts don't occur only during normal operation. A good chance to generate bus conflicts for a long time is during power-up and power-down. Power supplies typically have settling times up to 100ms, while soft-start power supplies may even need more time to reach the final voltage. During the V_{CC} ramp-up, the different circuits start to work at different voltage levels and under worse case the bus drivers are already functional while the control logic connected to the "direction" and "enable" pins is still out of order. Under these circumstances very long bus-conflicts can occur and especially when using widebus devices this often leads to destroyed devices.

Using bus functions with two enable inputs allows us to connect one of these enable inputs to the system-reset line. In this case the bus drivers are in high impedance during the reset period and when using a supply voltage supervisor like the TLC7705 this reset signal is active during power-up and power down. Drivers with only one enable input can be expanded to two inputs using external gates.

Digital Design Seminar

Clock Distribution

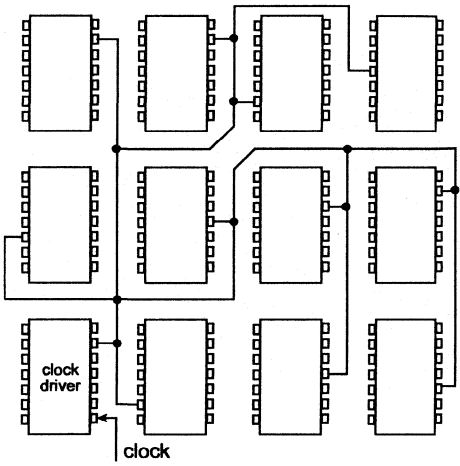Digital: Bad distribution of the Clock Signals



When drawing signal lines at random, each junction and line-end causes a point of discontinuity generating line reflections.

The signal is heavily distorted. Malfunction of the system is probable.

clock driver
clock

FOPE \DDSD\Busyst.ppt Jan97

Another issue in all synchronous systems such as bus systems is the clock distribution network. The clock signal is the most important signal in every synchronous system because it is the signal with the highest frequency and has to be routed to nearly every chip within the system. Clean clock signal slopes are essential.

Under these circumstances the clock distribution network in the figure above is a bad example. According to transmission line theory signal reflections occur at every branch of the wiring and a bad wave form will be the result. Because of this the above example can't even be used for slow systems.

Digital Design Seminar

Clock Distribution

Digital: Right Clock Signal Distribution

- ☞ Interconnecting the circuits in series provides a homogeneous line impedance (in ECL systems the interconnections between the various circuits are all made the same length to ensure constant impedance along the line).
- ☞ Line termination eliminates reflections.
- ☞ Termination impedance $1...2 \times Z_0$.
- ☞ Typ. Propagation time: 10...20 ns/m.
- ☞ Note: Take care of interconnect propagation time.
- ☞ Be careful with data-lines: watch for "Race Condition"


FOPE \DDSBussyst.ppt Jan97

The minimum requirement for a clock distribution network is to use signal lines with a defined beginning and defined end-point and without any branches. In this case we can implement parallel line termination to guarantee an excellent signal quality all along the signal trace. The above example is mostly a solution for slower systems, because the propagation delay time of the clock-signal along the clock-trace leads to an enormous skew: The slope arrives at different moments at the various clock inputs.

A special trap for designers is the "race condition". In the above example a data-line carries a signal from device A to device B. While new data is generated in A, and the new data-signal runs to device B along the data-line, the clock signal has to go a long way from the clock input of device A to the clock input of device B. If the data-signal arrives at device B before the clock-signal, then the new data is clocked into device B using the same slope that has generated this data. This is not what the designer usually expects and malfunction of the complete system will be the result.


Digital Design Seminar

Star-connected Clock Distribution

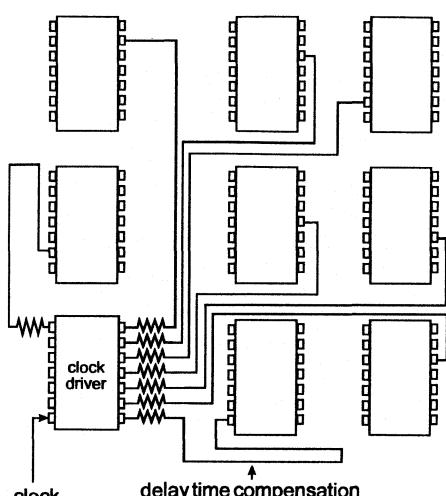

- ★ A star-connected network reduces skew caused by signal propagation delays.
- ★ Use clock driver with guaranteed low skew propagation delay, e.g. CDC208 (skew < 0.5 ns).
- ★ For lowest skew make all clock interconnecting lines of the same length.
- ★ Eliminate overshoots by matching the driver impedance to the line impedance by series resistors.

FOPE \DDSBu Syst.ppt Jan97



In most cases a star connected clock distribution network is the best solution for fast systems. To minimize the skew of the wiring the designer can choose equal length for all clock wires. Serial termination is the first choice for this layout, because these wires are point-to-point connections, which means that one output located at one end of the line drives one (or several) output(s) at the other end (or close to the other end) of the line.

If the board layout of the clock distribution network is made perfectly, the drivers of the clock signals should have the lowest skew possible. In this case the output skew is defined to be the difference of the propagation delay time between the slowest and the fastest driver within one clock driver package.

Texas Instruments offers a broad range of clock distribution circuits (CDC) that have guaranteed output skew values below 500ps.

Digital Design Seminar

Layout-Rules Digital: Distributed Clock Drivers

- ☞ Only a few lines from the central clock driver to distributed clock drivers using serial termination
- ☞ Short signal-lines from distributed clock drivers to clocked devices, no termination necessary

FOPE \DDSBusy.st.ppt Jan97

In large electronic systems with a huge number of clock inputs the clock distribution network can be designed like a tree. The above example shows one primary clock driver whose input is connected to the clock generator and whose five outputs feed the inputs of five secondary clock drivers. The signal traces between the primary and the five secondary clock drivers are point-to-point connections and should be serially terminated. If the length of the traces between the five secondary clock drivers and the clock inputs of the clocked circuits are short enough, no termination is necessary.


To calculate the overall skew of this clock distribution network another skew definition is necessary: The process skew. This type of skew ($t_{sk(pr)typ.} < 1ns$) guarantees a maximum difference in the propagation delay time between the fastest and the slowest driver in different packages. In above example the overall skew can be calculated in the following manner:

$$t_{sk(overall)} = t_{sk(0)} + t_{sk(pr)}$$

with $t_{sk(0)}$ = output skew of the primary clock driver

$t_{sk(pr)}$ = process skew of the five secondary clock drivers

Low-Skew Clock Driver

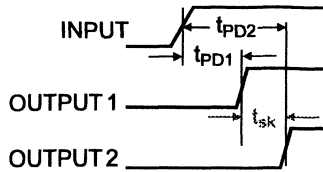

Output Skew

Skew between outputs of one circuit: $t_{sk(o)} \approx 0.5 \text{ ns}$,

Process Skew

Skew between outputs of various circuits of same type $t_{sk(pr)} \approx 1.0 \text{ ns}$,

Pulse Skew

Skew between rising and falling edge of outputs of one circuit: $t_{sk(p)} \approx 0.8 \text{ ns}$,

DEVICE DESCRIPTION

CDC203	HEX INV CLOCK DRIVER ($V_{CC} = 3.3 \text{ V}$)
CDC204(-7)	HEX INV CLOCK DRIVER
CDC208(-7)	DUAL 1 TO 4 CLOCK DRIVER
CDC209(-7)	DUAL 1 TO 4 CLOCK DRIVER
CDC303	OCTAL DIVIDE BY 2 CLOCK DRIVER
CDC304	OCTAL DIVIDE BY 2 CLOCK DRIVER
CDC305	OCTAL DIVIDE BY 2 CLOCK DRIVER
CDC328A	HEX CLOCK DRIVER W. SEL. PHASE
CDC329A	HEX CLOCK DRIVER W. SEL. PHASE
CDC330	DUAL 1 TO 3, 1 TO 4 DIVIDE BY 2
CDC337	QUAD 1:1 / QUAD 1:2 CLOCK DRIVER
CDC339	QUAD 1:1 / QUAD 1:2 CLOCK DRIVER
CDC340	1-LINE TO 8-LINE CLOCK DRIVER
CDC341	1-LINE TO 8-LINE CLOCK DRIVER
CDC391	1- TO 6-LINE CLOCK DRIVER
CDC392	CDC 391 WITH CMOS OUTPUTS
CDC536	3.3 V PLL CLK DRIVER
CDC582	3.3V PLL LVPECL CLK DRIVER
CDC586	3.3-V PLL CLK DRIVER
CDC2536	CDC536 WITH SER RESISTORS
CDC2582	CDC586 WITH DIFF. LVPECL INPUS
CDC2586	CDC586 WITH SERIES RESISTORS
CDC9841	PC MOTHERBOARD SYNT/DRV
CDC9842	PC MOTHERBOARD SYNT/DRV
CDC9843	PC MOTHERBOARD SYNT/DRV



Besides the output skew $t_{sk(o)}$ and the process skew $t_{sk(pr)}$, some clock drivers have a third type of skew: the pulse skew $t_{sk(p)}$. The pulse skew is defined to be the maximum difference in propagation delay time between the rising and the falling edge of a clock signal. If it is necessary to guarantee a maximum duty cycle (e.g. 45%) for the clock signal, devices with a specified pulse skew should be chosen.

Texas Instruments offers a broad range of clock distribution circuit (CDC) with various functionalities:

- ★ single drivers and several drivers connected to one clock input
- ★ inverting and non-inverting types
- ★ with and without built in dividers
- ★ supply voltage $V_{CC} = 5\text{V}$ and $V_{CC} = 3.3\text{V}$
- ★ clock drivers with and without PLL
- ★ application-specific clock drivers e.g. for PC motherboards

Bus Design Rules

- ★ Bus lines have very low line impedances ($Z_0 = 20...40 \Omega$).
- ★ Bus lines have to be terminated to prevent line reflections (signal distortion, circuit malfunctions due to undershoots).
- ★ Take care of propagation times ($\tau = 25 \text{ ns/m}$). Settling time of signals on TTL-type buses is $2 \times t_p$ (no incident wave switching).
- ★ Take care of control lines (clock, read, write, etc.).
- ★ Provide shielding between control lines and data/address lines.
- ★ A multiplexed data and address bus reduces design problems (50% less signal lines and 50% less line driver).
- ★ Driver output current is 100 mA/line. Provide adequate and low inductance GND return path (simultaneous switching)!
- ★ Rule of thumb: 25% of all backplane connector pins have to be GND lines!
- ★ Use multilayer boards with separate GND and V_{CC} plane for backplanes.




The above list shows a collection of bus design rules. Most of them have been already explained in detail on the previous pages.

One basic rule, not previously discussed, is the rule of thumb:

25% of all backplane connector pins have to be GND lines!


This huge number of GND pins is necessary to generate a low impedance and low inductance connection between the backplane and the modules. Otherwise it is not possible to get the necessary current, especially the peak values during current spikes, onto the modules. The GND lines should be distributed on the connector and not lumped together at one end (e.g. the bottom 3 rows). Otherwise the current path on the GND lines is too long from the backplane board to every location on the module and EMC problems can arise.

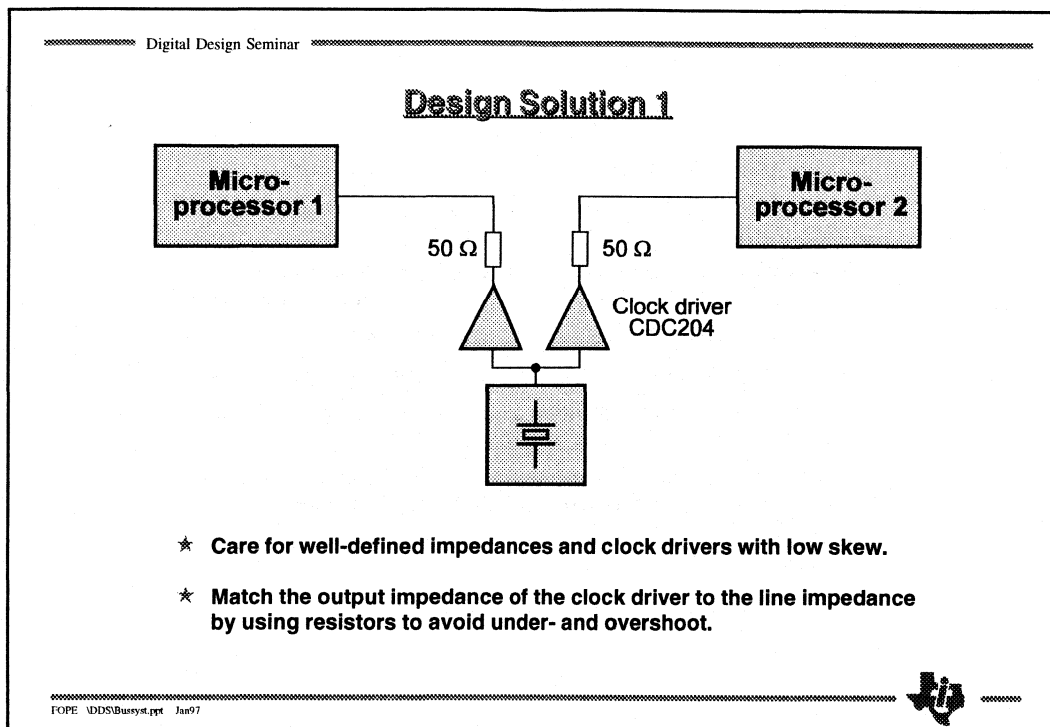

“Design Problem 1” had a bad clock distribution network. The clock driver was sitting close to microprocessor 1 and far away from processor 2. No line termination was included and therefore bad signal quality, caused by line reflections, was the result.

A clock distribution network in star-connection with correct line-termination leads to a reliable system.

Design Solution 2

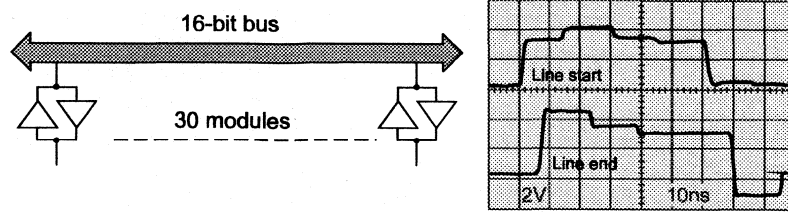

- ★ Signal integrity is now guaranteed by Incident Wave Switching.
- ★ System power dissipation is greatly reduced :

2 x ABT25245 transmitter	$I_{CC} = 20.5 \text{ mA}$
2 x ABT25245 receiver	$I_{CC} = 20.5 \text{ mA}$
56 x ABT25245 3-state	$I_{CC} = 28.0 \text{ mA}$
total	$I_{CC} = 69.0 \text{ mA}^*)$


*) Additional power consumption will be caused by required low impedance termination.
Recommended 60Ω 80Ω split termination on both line ends.



The designer of the backplane bus in "Design Problem 2" should have a closer look to the family of incident wave switching (IWS) driver SN74ABT25xxx. These drivers are able to switch the bus with the incident wave, so the signal quality on the backplane will be excellent. In addition, the current consumption of the drivers connected to the bus will drop from 6.5A down to 69mA!

..... Digital Design Seminar

Design Problem 3: A solution ?

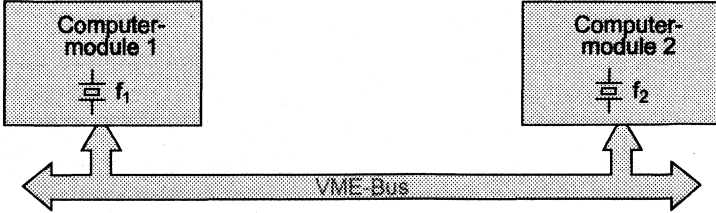


Computer-module 1 Computer-module 2

↑ ↑

← VME Bus →

- ★ The reduced clock rate in module 2 provides a few nanoseconds more settling time in the synchronization circuit. Thus reduces the probability of metastable state to a certain extent.
- ★ An evaluation of the real failure rate (1 failure/week? 1 failure/year) is now nearly impossible.
Therefore a careful circuit design (timing of the synchronization circuit) and the selection of suitable integrated circuits (SN74AS, SN74ABT, SN74F, SN74AC) is a must.

..... 

FOPE UDSBussy.ppt Jan97


The synchronization circuit of computer module 2 in the "Design Problem 3" had a mean time between failure (MTBF) rate less than one week. The reduced clock frequency of computer 2 increased the MTBF rate, but the designer didn't really know the actual value of his design (1 failure/week? 1 failure/year?). Therefore a careful circuit design (timing of the synchronization circuit, dual-rank synchronizer) and the selection of suitable integrated circuits (SN74AS, SN74ABT, SN74F, SN74AC) is essential to increase the MTBF rate into an uncritical region (e.g. 1000 years).


..... Digital Design Seminar

Advanced Logic Trends

..... GEBE 'DDSTrends.ppt Feb97



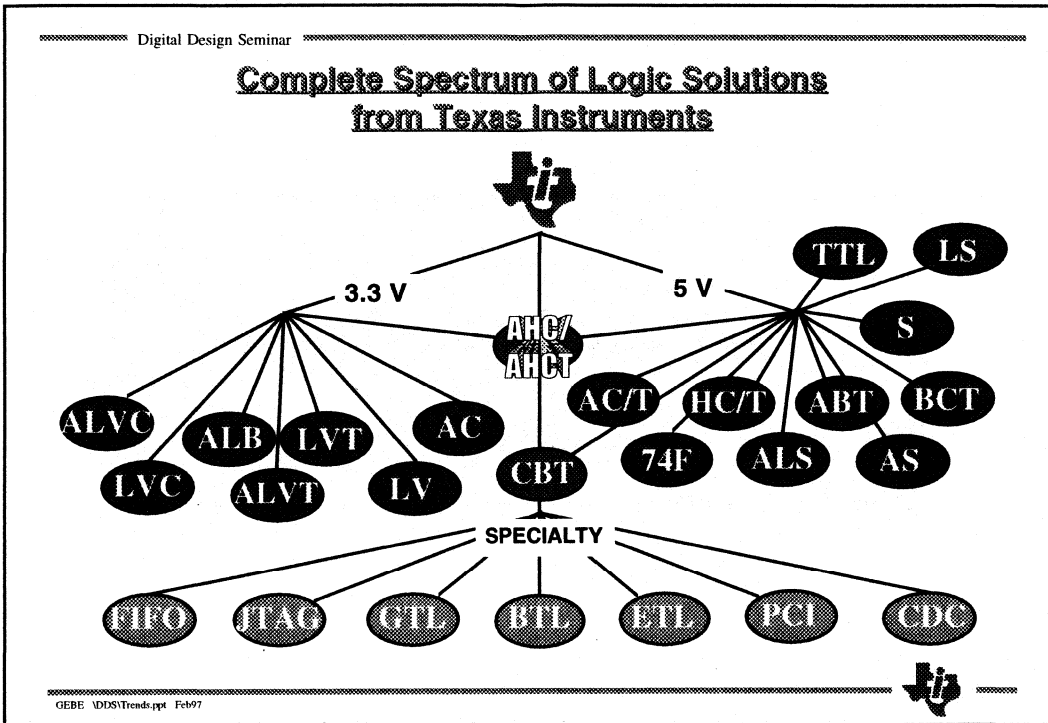


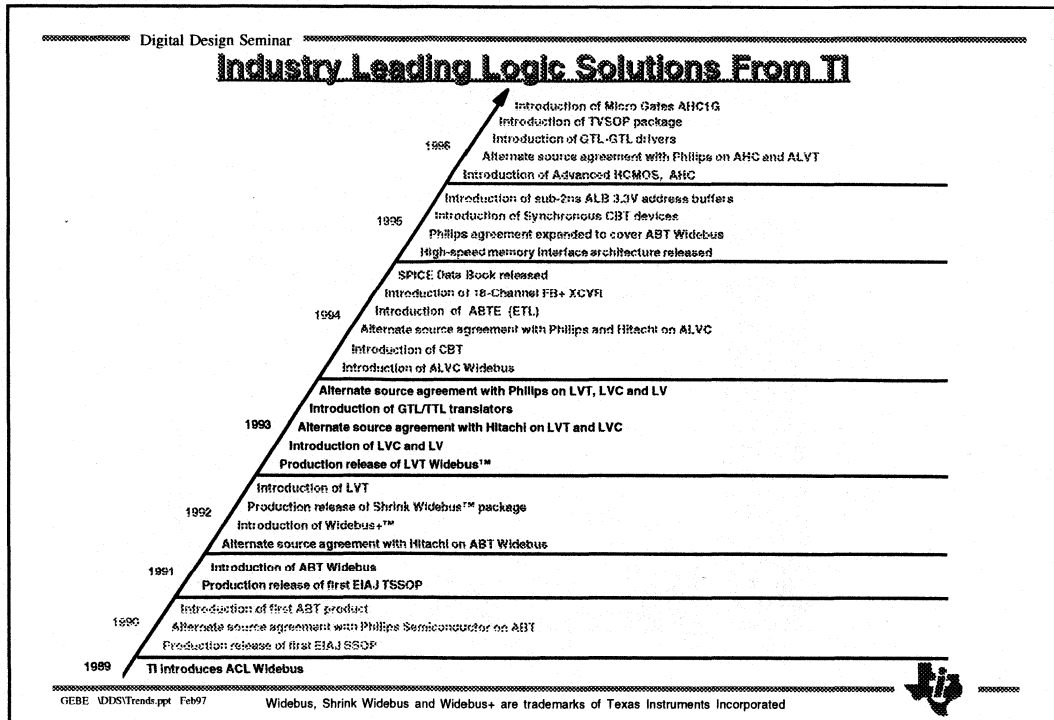

Digital Design Seminar

3.3V Logic - Worldwide Market Share

Year-to-Day as of 30. September 1996

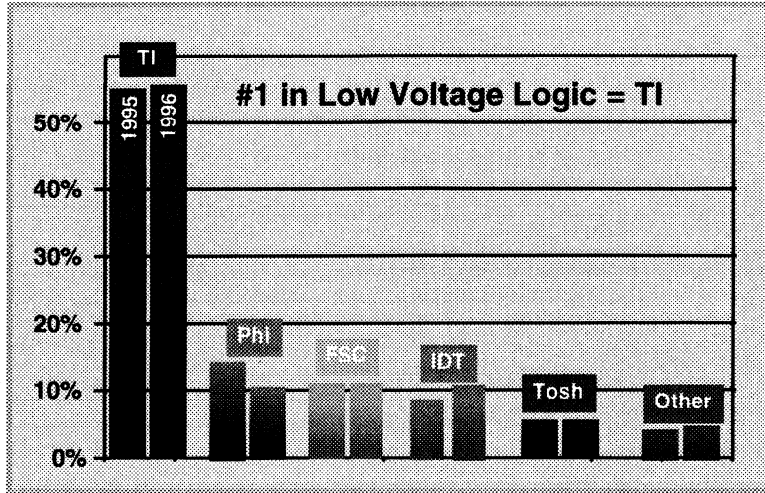


Source: Insight OnSite



GEBE VDDSVTrends.ppt Feb97


Digital Design Seminar

Moving to Low-Voltage Designs

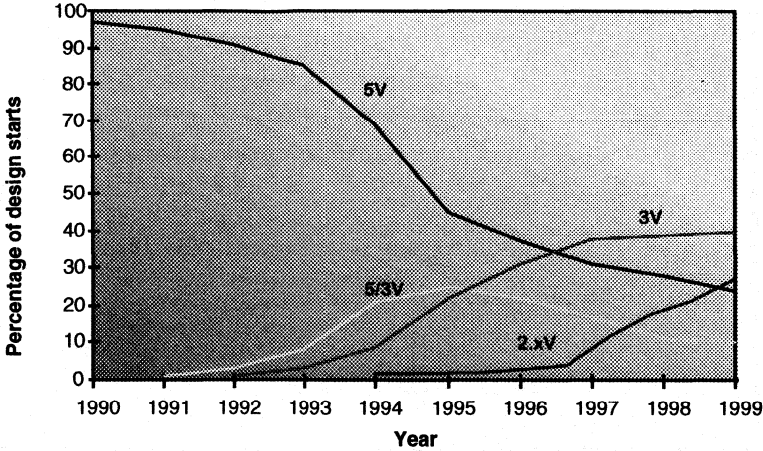

GEBE \DDSVTrends.ppt Feb97



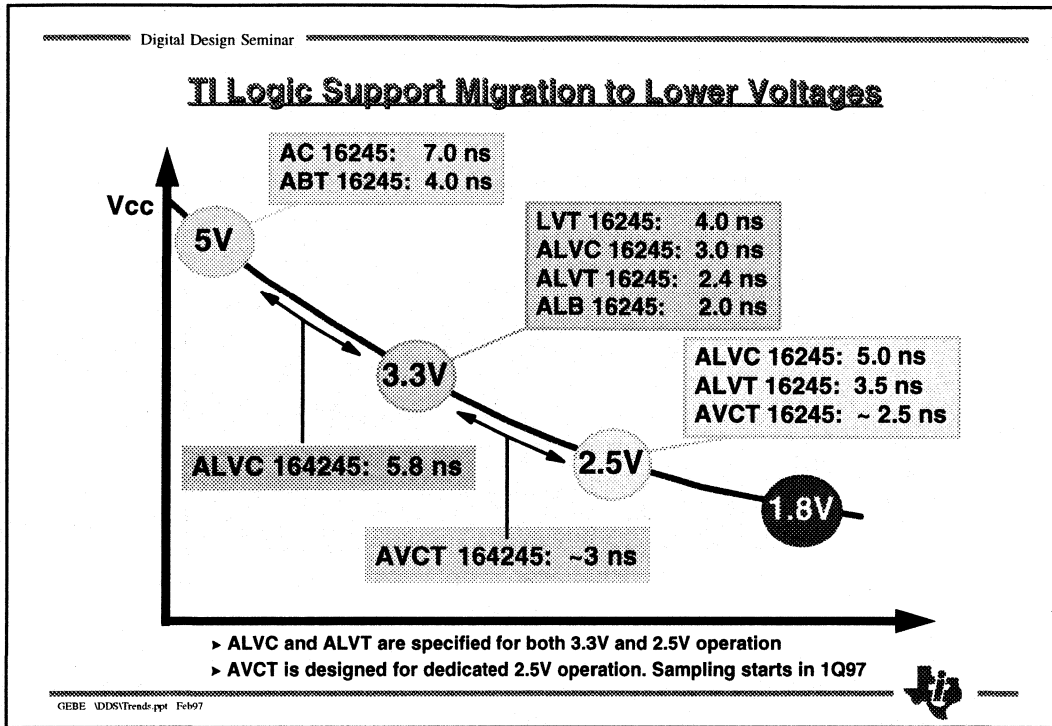


Digital Design Seminar

MicroGate Single gates in SOT-23 package

Standard Gates

Single Gate

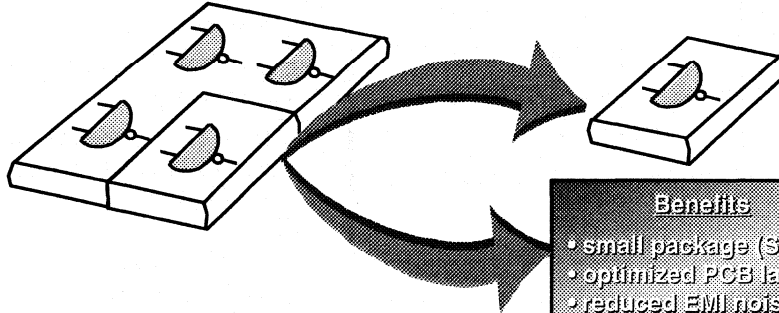


Benefits

- small package (SOT-23)
- optimized PCB layout
- reduced EMI noise
- enhancing ASIC functionality


GEBE ADISTrends.ppt Feb97



AHC/AHCT Microgate

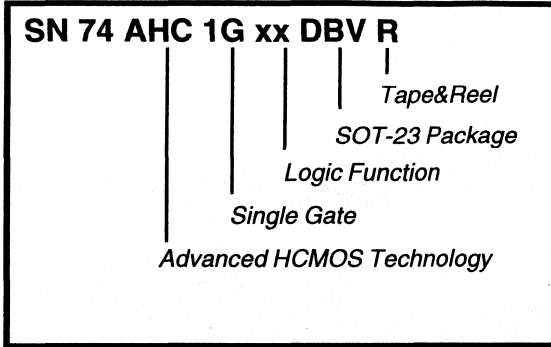

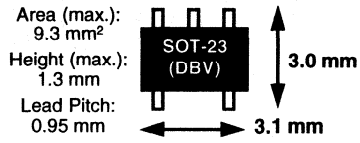- ◆ 3.5ns typ propagation delay
- ◆ +/-8mA output drive
- ◆ 20uA static current
- ◆ CMOS (AHC) and TTL (AHCT) compatible versions
- ◆ AHC versions compatible with Toshiba's TC7SHxx series
- ◆ Samples now




Cross-Reference (examples)

Texas Instruments	Toshiba
SN74AHC1G00DBV	TC7SH00F
SN74AHCT1G00DBV	----
SN74AHCU1G04DBV	TC7SHU04F



Advanced Low Voltage BICMOS (ALB): $T_{pd} \leq 2 \text{ ns!}$

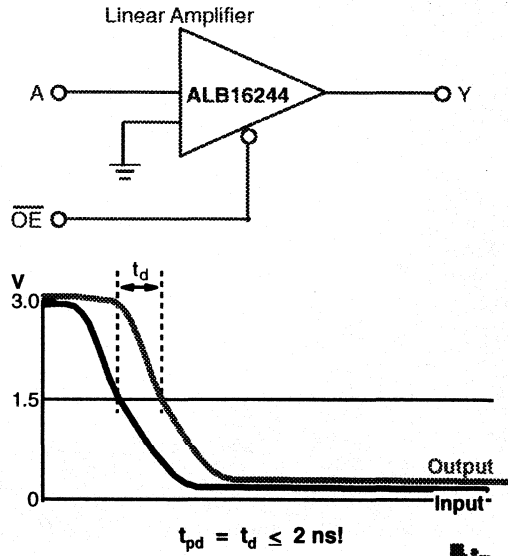- ★ New ALB product line from TI uses Advanced BICMOS technology; op-amp architecture
 - 2 ns prop delays (MAX!)
 - 3.3 V BICMOS process
 - Full 25 mA drive capability
 - '16244 and '16245 functions available soon
 - '16827 possible
- ★ Architecture limitations:
 - No hysteresis or buffering options possible (e.g. '240, '373, '646 ...)



Digital Design Seminar

Advanced Bus Interface Packaging


Bipolar	TTL	✓	✓						
	LS	✓	✓						
CMOS	S	✓	✓						
	ALS	✓	✓						
	F	✓	✓						
	AS	✓	✓						
	HC	✓	✓		✓*				
	HCT	✓	✓		✓*				
	LV	✓	✓		✓*				
	AHC	✓	✓		✓*	✓*			
	AHCT	✓	✓		✓*	✓*			
	AC	✓	✓		✓*	✓*	✓	✓	
BICMOS	ACT	✓	✓		✓*	✓*	✓	✓	
	LVC	✓	✓		✓*	✓*	✓	✓	✓*
	ALVC	✓	✓		✓*	✓*	✓	✓	✓*
Package example	BCT	✓	✓		✓*	✓*	✓	✓	✓*
	ABT	✓	✓		✓*	✓*	✓	✓	✓*
	LVT	✓	✓		✓*	✓*	✓	✓	✓*
Package Code	N/NT	DIP							
	D/DW	SOIC							
	DB	SSOP							
	PW	Thin SSOP							
	DGV	TVSOP							
	DL	SSOP				WIDEBUS			
	DGG	Thin SSOP							
	DGV	TVSOP							
	PN/PZ	TQFP							WIDEBUS+

* Selected functions

Widebus and Widebus+ are trademarks of Texas Instruments Inc.

GEBE VDSSTrends.ppt Feb97




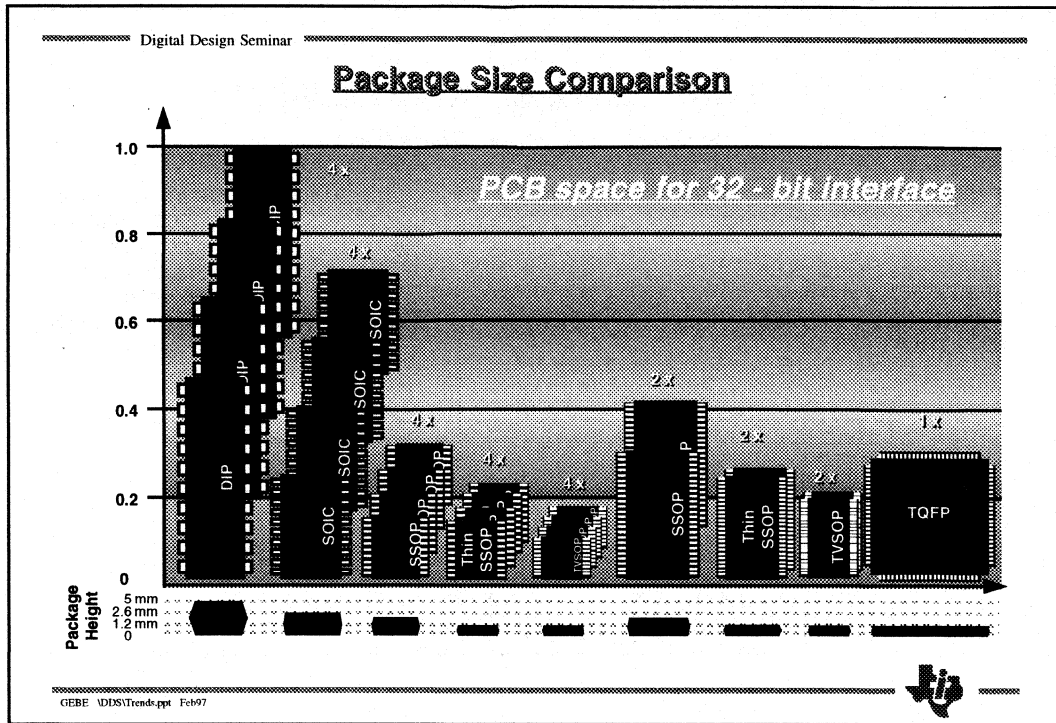

TVSOP: Dimensions and Pin Count

TVSOP = Thin Very Small Outline Packages

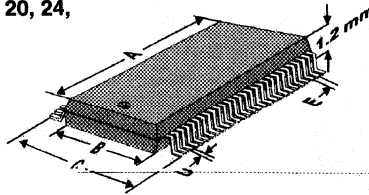- TVSOP is available in 14, 16, 20, 24, 48, 56, 80 and 100-pin types
- TVSOP has a lead pitch of 0.4 mm (16 mil) and a device height meeting the 1.2 mm PCMCIA



- All TVSOP packages have received JEDEC (Joint Electronics Device Engineering Council) registration under semiconductor package standard MO-194.

TVSOP Package	Typical Dimensions (in mm)					Area (mm ²)	% Smaller than SSOP	% Smaller than TSSOP	% Smaller than TQFP
	A	B	C	D	E				
14-Pin	3.60	4.40	6.40	0.18	0.40	23.00	52.4	29.3	
16-Pin	3.60	4.40	6.40	0.18	0.40	23.00	52.4	29.3	
20-Pin	5.00	4.40	6.40	0.18	0.40	32.00	43.0	24.0	
24-Pin	5.00	4.40	6.40	0.18	0.40	32.00	50.0	34.0	
48-Pin	9.80	4.40	6.40	0.18	0.40	63.00	61.9	38.0	
56-Pin	11.3	4.40	6.40	0.18	0.40	72.30	62.2	36.0	
80-Pin	17.0	6.10	8.10	0.18	0.40	137.8			30.0
100-Pin	20.8	6.10	8.10	0.18	0.40	168.5			35.0





Digital Design Seminar

Texas Instruments Mixed Signal and Logic Literature

Listed below is a collection of Texas Instruments' Mixed Signal and Logic Products technical documentation. The alphanumeric code is the literature number for each item listed. These documents can be ordered through a TI representative, an authorized distributor or the Product Information Center by referencing this literature number.

Document	Revision	Lit-Code	Document	Revision	Lit-Code
* Mixed Signal and Analog CD-ROM	1996	SLOD001	* AHC Selection Guide	1996	SCLBE01A
* Logic Application Report & Product CD-ROM	Jan97	SDZDE01A	* AHC MicroGate Product Information	1996	SCLTE01
* Mixed Signal & Analog Designer's Guide	Apr96	SLYU001	* Low Voltage Logic Selection Guide	1996	SCVBEO1A
* Logic Selection Guide	4Q96	SDYU001D	* CBT Crossbar Switch Selection Guide	1996	SCVBEO2A
* Data Converter Selection Guide	Oct96	SLABE05A	* GTL/ETL/BTL Backplane Selection Guide	1996	SCBBEO4
* Data Transmission Line Circuits Selection Guide	1996	SLLBE02	* FIFO Memories Selection Guide	1996	SCABEO1A
* Single Supply CMOS OpAmp Selection Guide	1996	SLOBE03	* CDC Clock Circuits Selection Guide	1996	SCBBEO5
* Rail-to-Rail OpAmp Selection Guide	1996	SLOBE02	* AHC,AHCT,HC,HCT,LV Data Book	1996	SCLD004
* Excalibur OpAmp Selection Guide	1996	SLOBE01A	* AC,ACT Data Book	1996	SCADE02
* TPIC Integrated Power Switches Selection Guide	1996	SLIBE01B	* ABT Data Book	1994	SCBDE08
* Intelligent Opto Sensors Selection Guide	1996	SOYBE03	* LVC,ALVC,LVT,LV,ALB Data Book	1996	SCBD003B
* MSP430 Selection Guide	1996	SLABE03A	* Widebus/Widebus+ Data Book	1995	SDWDE02
* Data Acquisition Circuits Data Book	1995	SLAD001	* BCT Data Book	1994	SCBD001B
* Data Transmission Line Circuits Data Book	1995/6	SLLD001A	* 74F Data Book	1994	SDFD001B
* Data Transmission Communication Controller	1996	SLLD003	* CDC Clock Circuits Data Book	1996	SCBTE07C
* Data Transmission Design Seminar Manual	1996	SLLDE01A	* GTL,ETL,BTL Backplane Data Book	1995	SCBDE10
* Power Supply Circuits Data Book	1996	SLVD002	* CBT Crossbar Switch Data Book	1995	SCDDE01
* Linear Circuits Power+ Products Data Book	1996	SLYD010A	* FIFO Memories Data Book	1996	SCAD003C
* Operational Amplifier and Comparators / Vol. A	1995	SLYD011	* FIFO Memories Designer's Handbook	1996	SCAA012A
* Operational Amplifier and Comparators / Vol. B	1995	SLYD012	* 3.3V FIFO Memories Data Book	1995	SCADE04
* Intelligent Opto Sensor Data Book	1996	SOYDE02B	* JTAG/Boundary Scan/IEEE1149.1 Data Book	1994	SCBDE09
* Wireless and Telecom Products Data Book	1996	SLWD001	* TNETA - ATM Network Data Book	1996	SDNDE02
			* Adv.Logic SPICE Models Data Book	1995	SCBD004A

GEBE \DDSVTrends.ppt Feb97



BELGIQUE/BELGIË

Brussels (02) 745 54 00

DEUTSCHLANDFreising (08161) 80-0 od. Nbst
Hannover (0511) 90 49 60
Stuttgart (0711) 34 03 0**EIRE**

Dublin (353) 1 47 54 19 4

ESPAÑA/PORTUGAL

Madrid (1) 372 80 51

FRANCE, MIDDLE EAST & AFRICA

Velizy Villacoublay (1) 30 70 10 01

HOLLAND

Amsterdam (020) 5 46 98 00

ITALIA

Agrate Brianza (Mi) (039) 68 421

MAGYARORSZÁG/HUNGARY

Budapest (1) 176 3733

SUOMI/FINLAND

Espoo (9) 43 54 20 33

SVERIGE, DANMARK & NORGE

Stockholm (8) 587 555 00

UNITED KINGDOM

Northampton (01604) 663000

BELGIQUE/BELGIË/BELGIUMEBV Elektronik: Tel: +32 2 716 00 10, Fax: +32 2 720 81 52
Eurodis Texim Electronics: Tel: +32 2 247 49 70, Fax: +32 2 215 81 02
SEI-Sonetech BV: Tel: +32 2 460 07 07, Fax: +32 2 460 12 00
SPOERLE ELECTRONIC: Tel: +32 2 725 46 60, Fax: +32 2 725 45 11**БЕЛОРУССИЯ/BELO RUSSIA**

Scan West: Tel: +7 017 226 9792, Fax: +7 017 226 9792

БЪЛГАРИЯ/BULGARIAEBV (Akermann Electronic): Tel: +359 2 540 078, Fax: +359 2 540 562
Macro Sofia: Tel: +359 2 708 140, Fax: +359 2 738 100
SEI-Elbatex: Tel: +359 2 802 041, Fax: +359 2 801 207**ČESKÁ REPUBLIKA/CZECH REPUBLIC**EBV GES-Electronics: Tel: +421 972 591 31/41/51, Fax: +42 1 972 591 61
Elbatex: Tel: +42 2 476 37 07, Fax: +42 2 476 37 08
Macro Weil s.r.o.: Tel: +42 2 311 21 82, Fax: +42 2 243 10 335
Setron: Tel: +42 2 687 10 40, Fax: +42 2 687 12 40
SPOERLE ELECTRONIC: Tel: +42 2 731 35 4, Fax: +42 2 731 35 5**DANMARK/DENMARK**Arrow Exatec A/S: Tel: +45 44 92 70 00, Fax: +45 44 92 60 20
Avnet Nortec A/S: Tel: +45 44 88 08 00, Fax: +45 44 88 08 88
EBV Elektronik: Tel: +45 39 69 05 11, Fax: +45 39 69 05 04
Jakob Hatteland Electronic A/S: Tel: +45 87 24 66 66, Fax: +45 87 24 66 60**DEUTSCHLAND/GERMANY**Avnet E2000: Tel: +49 89 45 11 00 1, Fax: +49 89 45 11 01 29
EBV Elektronik: Tel: +49 89 99 11 40, Fax: +49 89 99 11 44 22
Eurodis Enatechnik: Tel: +49 41 06 70 10, Fax: +49 41 06 70 12 68
SEI-Jermyn GmbH: Tel: +49 64 31 50 80, Fax: +49 64 31 50 82 89
SPOERLE ELECTRONIC: Tel: +49 61 03 30 40, Fax: +49 61 03 30 43 60**EIRE/IRELAND**Arrow Electronics: Tel: +353 1 459 5540, Fax: +353 1 459 5490
Avnet Lyco: Tel: +353 1 890 1000, Fax: +353 1 890 1010
Bloomer Electronics Ltd.: Tel: +44 1762 339818, Fax: +44 1762 330650
Macro Group Ireland: Tel: +353 1 676 6904, Fax: +353 1 676 0713**ESPAÑA/SPAIN**ATD Electronica: Tel: +34 1 304 15 34, Fax: +34 1 327 27 78
EBV Electronic: Tel: +34 1 804 32 56, Fax: +34 1 804 41 03
SEI-ADM Electronica: Tel: +34 1 530 41 21, Fax: +34 1 530 01 64
Sagitron: Tel: +34 1 416 94 41, Fax: +34 1 415 86 52**FRANCE**Arrow Electronique: Tel: +33 1 49 78 49 00, Fax: +33 1 49 78 05 96
Avnet EMG SA: Tel: +33 1 49 65 25 00, Fax: +33 1 49 65 27 39
EBV Electronic: Tel: +33 1 64 68 86 00, Fax: +33 1 64 68 27 67
SEI-3D: Tel: +33 1 64 47 29 29, Fax: +33 1 64 47 00 84
Tekelec Airtronic: Tel: +33 1 46 23 24 25, Fax: +33 1 45 07 21 91**ΕΛΛΑΔΑ/GREECE**

Atex Electronics: Tel: +30 1 90 22 003, Fax: +30 1 90 17 024

HOLLAND/NETHERLANDSEBV Elektronik: Tel: +31 3465 83010, Fax: +31 3465 83025
Eurodis Texim Electronics: Tel: +31 53 573 3333, Fax: +31 53 573 3888
SEI-Sonetech BV: Tel: +31 76 57 22 333, Fax: +31 76 57 22 395
SPOERLE ELECTRONIC: Tel: +31 30 609 1234, Fax: +31 30 603 5924**ITALIA/ITALY**Avnet-Adelsy SRL: Tel: +39 2 381 90 1, Fax: +39 2 380 02 988
EBV: Tel: +39 2 660 96 290, Fax: +39 2 660 17 020
SEI-Sonelco SpA: Tel: +39 2 660 261, Fax: +39 2 660 11 208
Silverstar-Celdis: Tel: +39 2 661 251, Fax: +39 2 661 04 275**ISRAEL**

TELSYS Ltd: Tel: +972 3 649 20 01, Fax: +972 3 649 74 07

LIETUVA/LITHUANIA

Macro: Tel: +370 7 764 937, Tel/Fax: +370 7 765 801

MAGYARORSZÁG/HUNGARYEBV LOMEX KFT: Tel: +36 1 272 06 07, Fax: +36 1 272 06 03
Elbatex: Tel: +36 1 269 90 93/94, Fax: +36 1 269 90 96
Macro Budapest Kft: Tel: +36 1 203 02 77, Fax: +36 1 203 03 41
Setron: Tel: +36 1 250 46 28/18, Fax: +36 1 168 67 86
SPOERLE ELECTRONIC: Tel: +36 1 270 62 75, Fax: +36 1 270 62 77**NORGE/NORWAY**Arrow-Tahonic A/S: Tel: +47 22 378 440, Fax: +47 22 370 720
Avnet Nortec A/S: Tel: +47 66 846 210, Fax: +47 66 846 545
Jakob Hatteland Electronic A/S: Tel: +47 53 763 000, Fax: +47 53 765 339**ÖSTERREICH/AUSTRIA**Avnet E2000: Tel: +43 1 911 28 47, Fax: +43 1 911 38 53
EBV Elektronik: Tel: +43 1 894 17 74, Fax: +43 1 894 17 75
SEI-Elbatex GmbH: Tel: +43 1 866 42 0, Fax: +43 1 866 42 202
SPOERLE ELECTRONIC: Tel: +43 1 318 72 70 0, Fax: +43 1 369 22 73**POLSKA/POLAND**Constans TI: Tel: +48 71 25 26 21, Fax: +48 71 25 44 39
EBV Semicon Components: Tel: +48 71 48 56 41, Fax: +48 71 48 56 41
Elbatex: Tel: +48 22 621 71 22, Fax: +48 22 623 06 05
Macropol Ltd.: Tel: +48 22 22 43 37, Fax: +48 22 22 91 36
Setron: Tel: +48 26 28 67 27, Fax: +48 26 21 15 40
SPOERLE ELECTRONIC: Tel: +48 22 640 03 49, Fax: +48 22 640 03 48**PORTUGAL**ATD Electronica: Tel: +351 1 471 4182, Fax: +351 1 471 5886
SEI-ADM Electronica: Tel: +351 2 973 6957, Fax: +351 2 973 6958**ROMANIA**Liviu Bejan: Tel: +401 686 93 12, Fax: +401 686 93 12
Macro: Tel: +40 1 634 31 29, Fax: +40 1 634 31 29**РОССИЯ/RUSSIA**Macro Petersburg: Tel: +7 812 531 1476, Fax: +7 812 327 8650
Scan Ltd.: Tel: +7 095 232 23 43, Fax: +7 095 938 22 47
SEI-Elbatex: Tel: +7 095 210 00 44, Fax: +7 095 956 10 78
Setron: Tel: +7 095 278 00 68, Fax: +7 095 278 00 68**SCHWEIZ/SUISSE/SWITZERLAND**Avnet E2000: Tel: +41 1 722 13 30, Fax: +41 1 722 13 40
EBV Elektronik: Tel: +41 1 74 561 61-30, Fax: +41 1 74 151 10
Eurodis Electronics AG: Tel: +41 1 843 31 11, Fax: +41 1 843 34 75
SEI-Elbatex AG: Tel: +41 56 437 51 11, Fax: +41 56 437 54 54
SPOERLE ELECTRONIC: Tel: +41 1 874 62 62, Fax: +41 1 874 62 00**SLOVENSKO/SLOVAKIA**Elbatex: Tel: +42 7 72 21 37, Fax: +42 7 72 21 39
Macro Components s.r.o.: Tel: +42 89 63 41 81, Fax: +42 89 63 41 09**SLOVENIA/CROATIA**EBV Elektronik: Tel: +386 61 133 0216, Fax: +386 61 133 0457
Elbatex: Tel: +386 61 159 71 98, Fax: +386 61 159 23 98**SOUTH AFRICA**

Pace Electronic Components: Tel: +27 11 9741211, Fax: +27 11 9741271

SUOMI/FINLANDArrow-Field Oy: Tel: +358 9 777 571, Fax: +358 9 798 853
Avnet Nortec Oy: Tel: +358 9 613 181, Fax: +358 9 692 232 6
Jakob Hatteland Oy: Tel: +358 9 351 615 21, Fax: +358 9 351 615 22**SVERIGE/SWEDEN**Arrow-TH:s Elektronik: Tel: +46 8 362 970, Fax: +46 8 761 3065
Avnet Nortec AB: Tel: +46 8 629 1400, Fax: +46 8 627 0280
Ericsson Standard Components AB: Tel: +46 8 757 4900, Fax: +46 8 752 9261
GB TopComp Electronics: Tel: +46 8 757 5300, Fax: +46 8 757 5353
Jakob Hatteland Electronic AB: Tel: +46 8 760 0140, Fax: +46 8 364 686**TURKIYE/TURKEY**

Empa A.S.: Tel: +90 212 599 30 50, Fax: +90 212 599 30 59

ΥΚΡΑΙΝΑ/UKRAINE

SEI-Elbatex: Tel: +38 44 227 22 62, Fax: +38 44 227 36 68

UNITED KINGDOMArrow-Jermyn: Tel: +44 1234 27 00 27, Fax: +44 1234 21 464
Avnet Access: Tel: +44 1462 48 08 88, Fax: +44 1462 48 85 67
Bloomer Electronics Ltd.: Tel: +44 1762 33 98 18, Fax: +44 1762 33 06 50
EBV Electronic: Tel: +44 1628 783688, Fax: +44 1628 783811
Macro Marketing Ltd.: Tel: +44 1628 60 60 00, Fax: +44 1628 66 68 73
SEI 2001 Electronic Comp.: Tel: +44 1438 74 20 01, Fax: +44 1438 74 20 02**IMPORTANT NOTICE:**

Texas Instruments (TI) reserves the right to make changes to or to discontinue any product or service identified in this publication without notice. TI advises its customers to obtain the latest version of the relevant information to verify, before placing orders, that the information being relied upon is current.

Please be advised that TI warrants its semiconductor products and related software to the specifications applicable at the time of sale in accordance with TI's standard warranty. TI assumes no liability for applications assistance, software performance, or third-party product information, or for infringement of patents or services described in this publication. TI assumes no responsibility for customers' applications or product designs.

E-PIC

TI SC European Product Information Center

MULTILINGUAL TECHNICAL HOTLINE:

Francais:	+33 (0) 1 30 70 11 64
English:	+44 - (0)1604 - 66 33 99
Italiano:	+33 (0) 1 30 70 11 67
Deutsch:	+49 (0)8161 80 33 11

E-mail	epic@ti.com
24 Hours FAXLINE:	+33 (0) 1 30 70 10 32

APPLICATION SUPPORT (Via MODEM):

BBS:	+33 (0) 1 30 70 11 99
INTERNET:	http://www.ti.com



**TEXAS
INSTRUMENTS**