

S-plane Explained

A (P)REVIEW OF LAPLACE TRANSFORMS AND HOW TO USE THEM IN EE122

- Introduction
- Motivation for s-plane analysis
- When I say 's-plane,' what do I mean?
- How to use the s-plane
 - Circuit analysis/design: the Integrator
 - Signal analysis/design: FM



Motivation for s-plane analysis

- Understanding circuits in another “domain” (the frequency domain)
 - The more ways we can understand our circuit, the better because...
- The time domain is hard for some things
 - filtering = convolution (Doh!)
- The s-plane (often) makes things easier
 - filtering = multiplication (Woohoo!)



Math behind the s-plane

The Laplace Transform of a time-domain function gives us a function of the complex frequency variable 's'

- The actual Laplace Transform*:

$$H(s) = \int_0^{\infty} h(t)e^{-st} dt$$

- $h(t)$ could be a signal, or a system

- As a signal: $h(t) = \sin(15t + 0.16)$

- As a system: $h(t) = \frac{v_{out}(t)}{v_{in}(t)}$

- $H(s)$: Laplace Transform of $h(t)$

- $s = \sigma + j\omega$: Complex Frequency Variable

*: not necessary for EE122, but interesting (maybe)



A note about transforms

- They make life easier (or should)
- If you've taken E40 (and/or Math 53), you have already used transforms
 - E40 uses phasor analysis of linear circuits
 - Complex impedances are just a tricky way of getting around differential equations so that we can take C as a “resistor” of value $1/j\omega C$.
Indeed, they are simply Laplace (or Fourier) transforms in disguise--as you will see.
 - Math 53 uses Laplace Transforms to solve differential equations




What do I mean when I say 's-plane'?

ANSWER: THE REAL (σ) AND IMAGINARY (ω) PARTS OF s ARE THE 'x' and 'y' ON A GRAPH

- Example:

- “Tent pole” plot of the $|H(s)|$ magnitude of a Chebychev filter's response to inputs of complex frequency 's'
- ω is what you usually think of as 'radian frequency' ($\omega=2\pi f$)
- σ is decay rate*

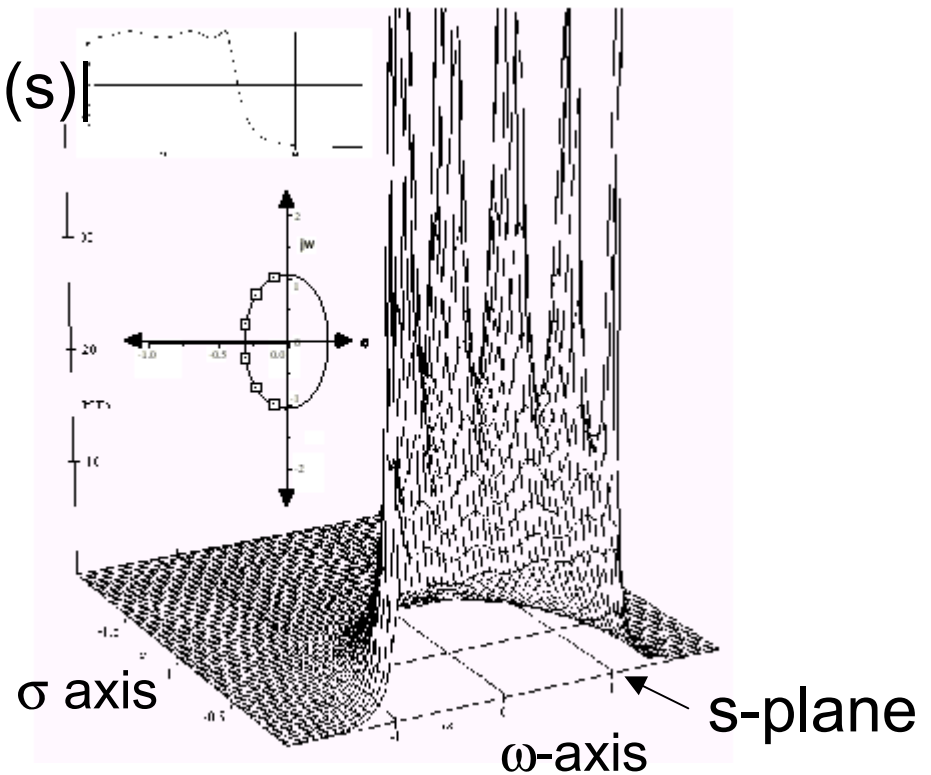

*: Not important for EE122, but used in stability analysis



Why should I use the s-plane?

**THIS IS THE SAME QUESTION AS:
'WHY IS THE LAPLACE TRANSFORM USEFUL?'**

- Turns differential equations (hard) into algebraic equations (easy)

$$Av_{out}(t) + B dv_{out}/dt = Cv_{in}(t) \Leftrightarrow (A + sB)v_{out} = Cv_{in}$$

$$\frac{v_{out}}{v_{in}} = H(s) = \frac{C}{A + sB}$$

- Turns convolution (hard) into multiplication (easy)

$$f(t) * h(t) = g(t) \Leftrightarrow F(s)H(s) = G(s)$$



How to use s-plane analysis

- Examples to follow:
 - Systems
 - Simple RC circuit
 - Integrator
 - Signals
 - Multiplication by a sinusoid: “Heterodyning”



RC circuit (simple)

- Straight from EE122 lecture notes:

Derivation :

$$v_{out}(t) = v_{in}(t) - iR$$

$$i = C dv_{out}/dt$$

$$v_{out}(t) + RC dv_{out}/dt = v_{in}(t)$$


"Magic" (Laplace Transform)

$$v_{out}(1 + sRC) = v_{in}$$


$$\frac{v_{out}}{v_{in}} = H(s) = \frac{1}{1 + sRC}$$

REVIEW: FIRST ORDER LOW-PASS
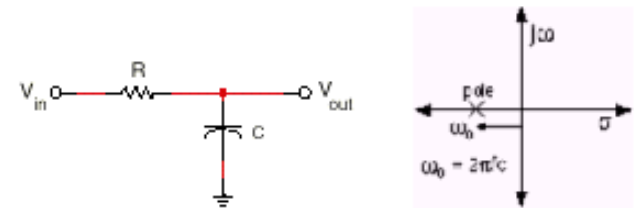
$$\frac{v_{out}}{v_{in}} = \frac{a_0}{s + \omega_0}$$



$$\omega_0 = 2\pi f_c = \frac{1}{RC}$$

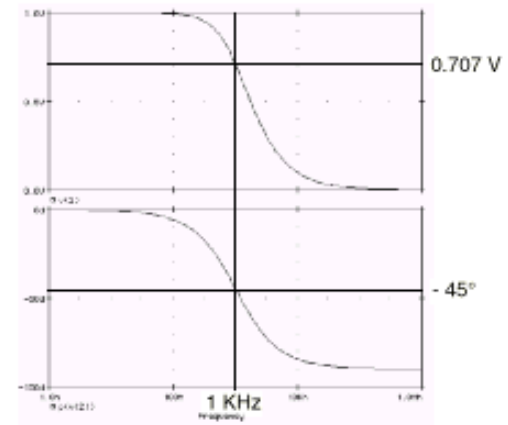

EE122, Stanford University, Prof. Greg Kovacs

5



EE122, Stanford University, Ross Venook

Integrator (slightly less simple)

AC Analysis :

$$v_{out}(t) = -(i_{in}(t) - i_C(t))R_2$$




$$i_{in}(t) = v_{in}(t) / R_1$$

$$i_C(t) = -Cdv_{out} / dt$$

$$v_{out}(t) = -(v_{in}(t) / R_1 + Cdv_{out} / dt)R_2$$

$$(R_1 + sR_1R_2C)v_{out} = -v_{in}R_2$$


$$\frac{v_{out}}{v_{in}} = |H(s)| = \frac{R_2}{sR_1R_2C + R_1}$$

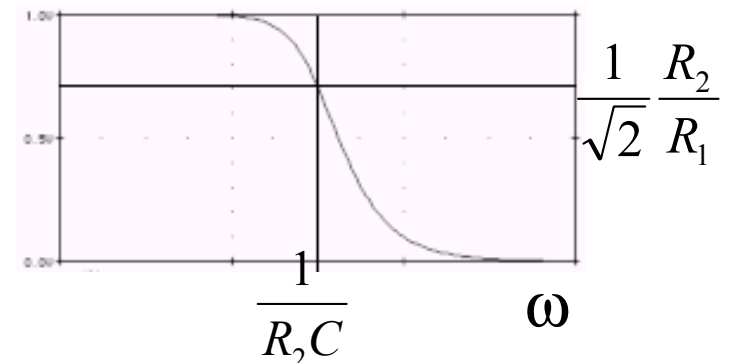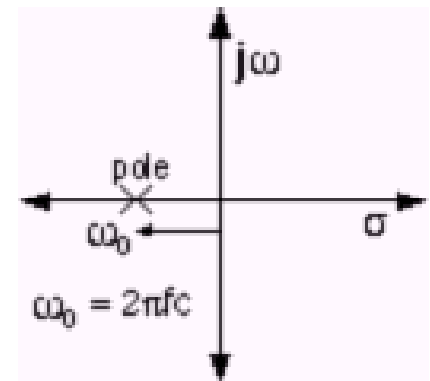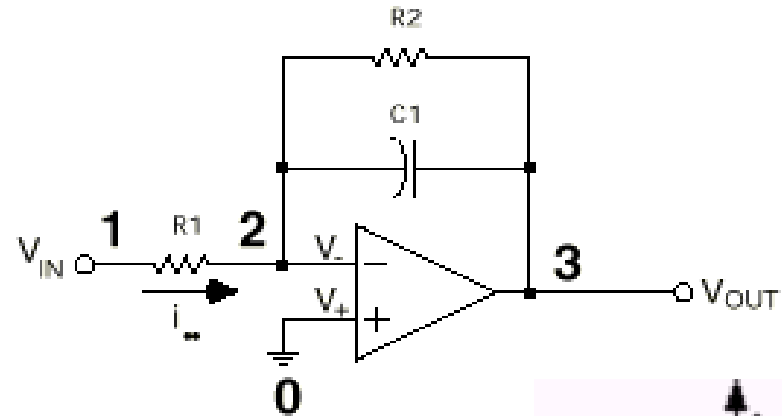

A familiar slide

POLES, ZEROS, AND CIRCUS TENTS?
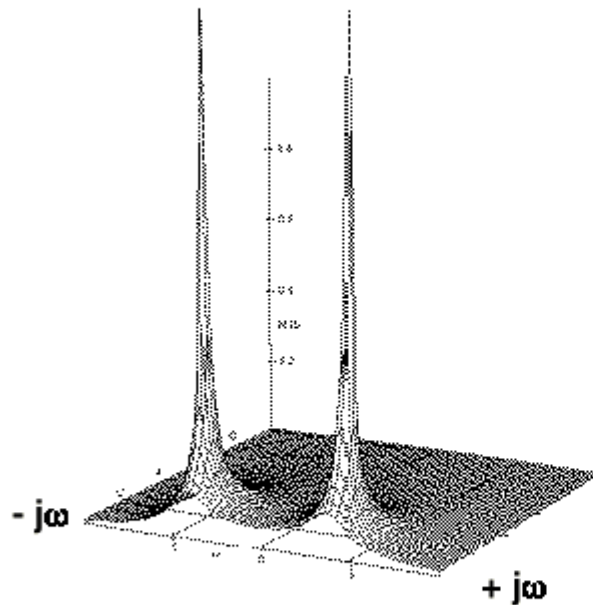
$$T(S) = \frac{A(S)}{B(S)} = \frac{(S - Z_1)(S - Z_2) \cdots (S - Z_m)}{(S - P_1)(S - P_2) \cdots (S - P_n)}$$



$$LPF(S) = \frac{A}{[S + (1+4j)][S + (1-4j)]}$$




Another familiar slide...

POLES OF 2nd ORDER SYSTEMS

$$\text{LPF}(S) = \frac{A}{S^2 + S\frac{\omega_0}{Q} + \omega_0^2}$$

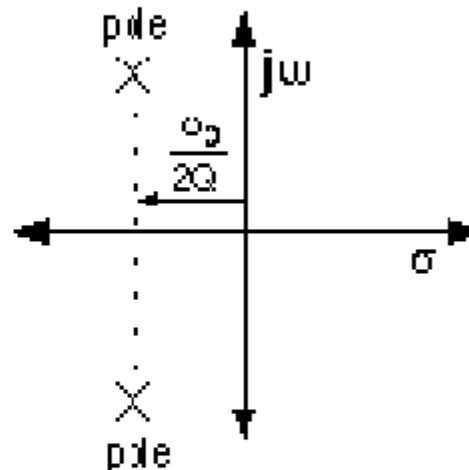POLE DISTANCE FROM $j\omega$ AXIS = $\frac{\omega_0}{2Q}$



FOR LEAST PEAKING
("MAXIMALLY-FLAT")


$$Q = \frac{1}{\sqrt{2}}$$

$$P_{1,2} = -\frac{\omega_0}{2Q} \pm j\omega_0\sqrt{1 - \frac{1}{(2Q)^2}}$$



A last familiar slide

EXAMPLE: 2nd ORDER HIGH-PASS

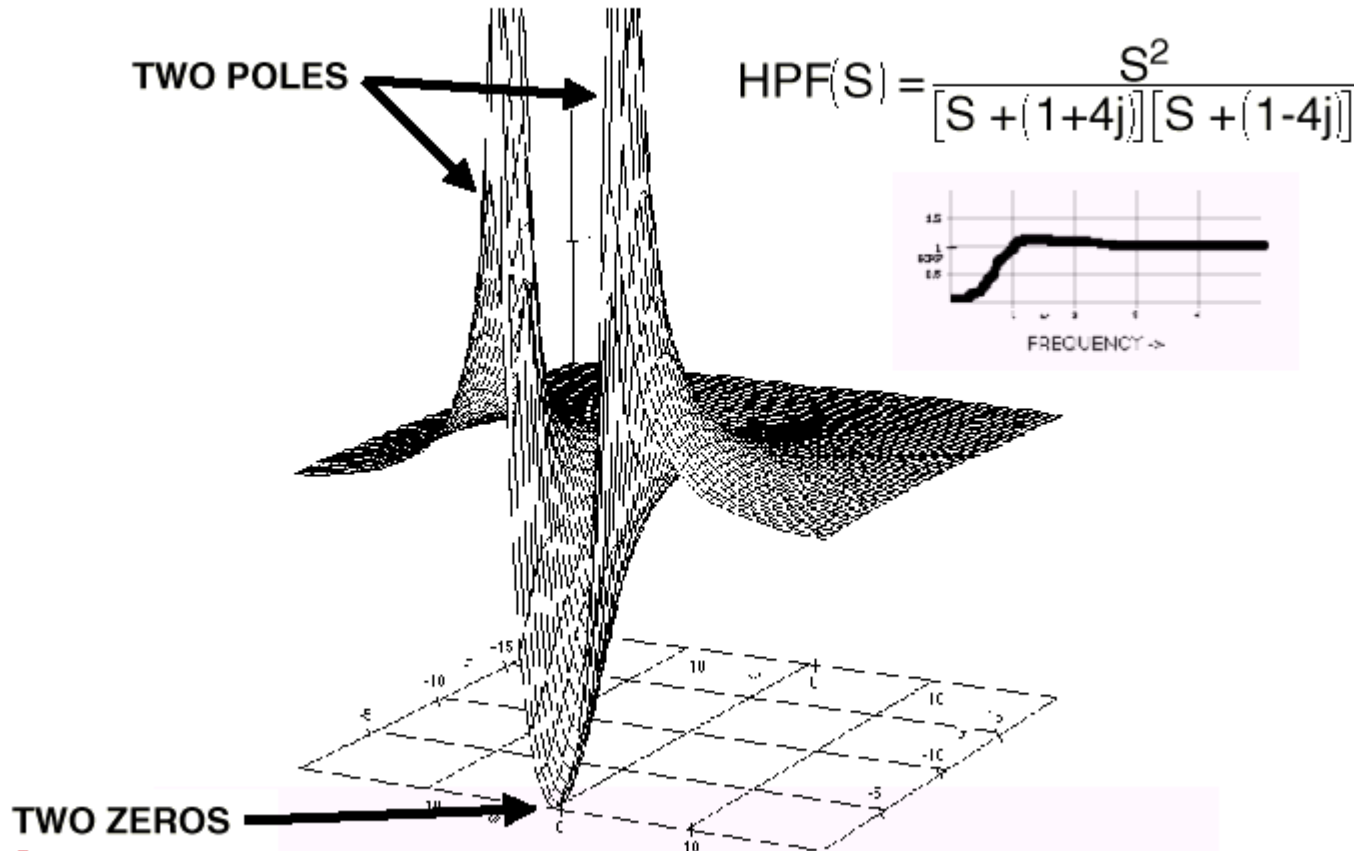

EE122, Stanford University, Prof. Greg Kovacs

8



EE122, Stanford University, Ross Venook


Heterodyning (for FM radio)

- Motivation: “Base-band” txn is trouble
 - Efficiency
 - $\lambda/4$ Antenna for kHz \sim length $>$ kilometers
 - Interference
 - All of the signals would muddle together
 - Hence, we need distinct ‘carrier frequencies’ (regulated by the FCC)
 - 92.3 MHz (KSJO)
 - 88.5 MHz (KQED)
 - 1070 kHz (KNX)
 - 710 kHz (KABC)
- FM
- AM




The “frequency domain”

- All base-band:

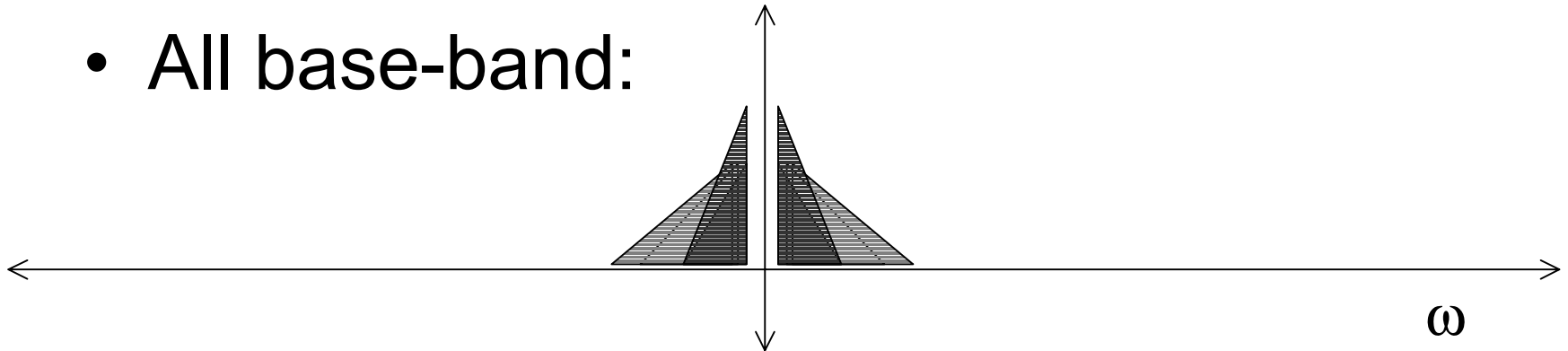

- Heterodyned

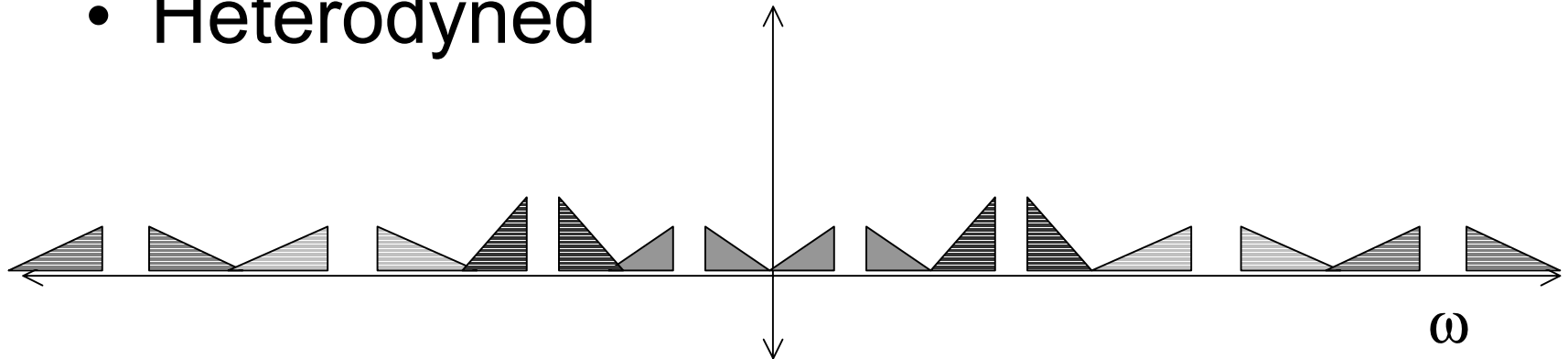

Back to heterodyning

**Because convolution in the time domain is multiplication in the frequency domain, when we multiply by a sinusoid in the time domain, it convolves the frequency content of our signal up to the frequency of the sinusoid.
(Whew! That was a mouthful)**

