

SEMICONDUCTOR DIODES AND TRANSISTORS

PROGRAMMED INSTRUCTION



MANUFACTURERS OF CATHODE-RAY OSCILLOSCOPES

VOLUME 3
TRANSISTORS

TEKTRONIX PUBLICATION 062-0067-00

SEMICONDUCTOR DIODES AND TRANSISTORS

VOLUME 3

TRANSISTORS

TEKTRONIX, INC.
P. O. BOX 500
BEAVERTON, OREGON

062-0067-00


SEVENTH PRINTING MARCH 1969

MARKETING TECHNICAL TRAINING

© 1964,1966, TEKTRONIX, INC.

ALL RIGHTS RESERVED

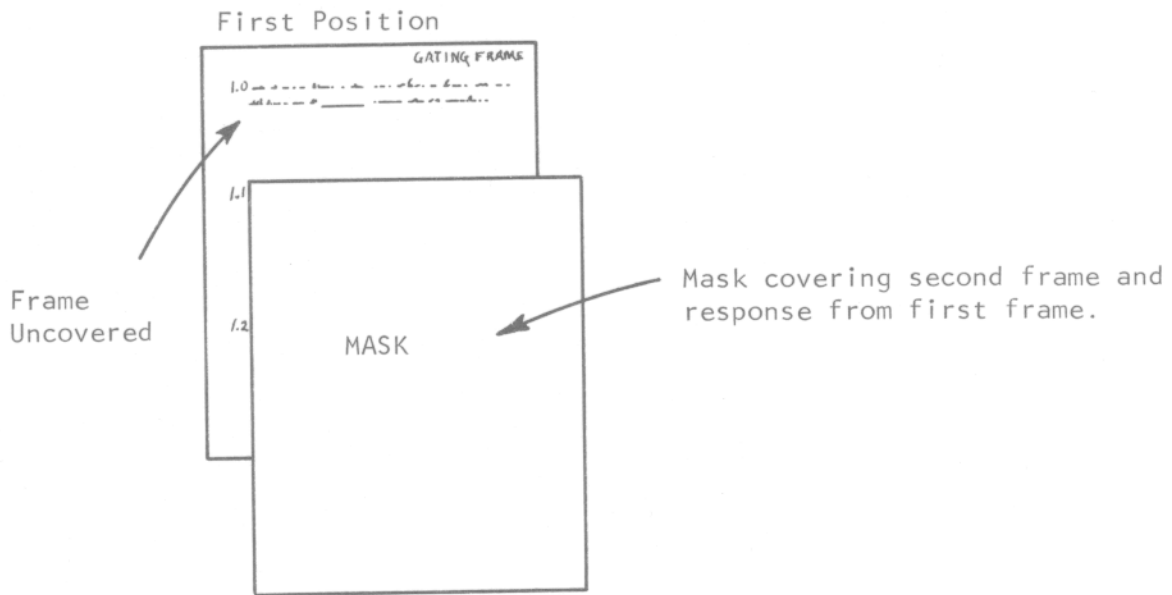This mask will help you as you go through this program.
Here is how to use it:




First Position:

Read the frame.
Write in your response.

Second Position:

Move the mask down. Check your response with the one printed in the box in the lower left hand corner of newly exposed frame. Read the newly exposed frame and write in your response. Slide the mask down again, and repeat this step.

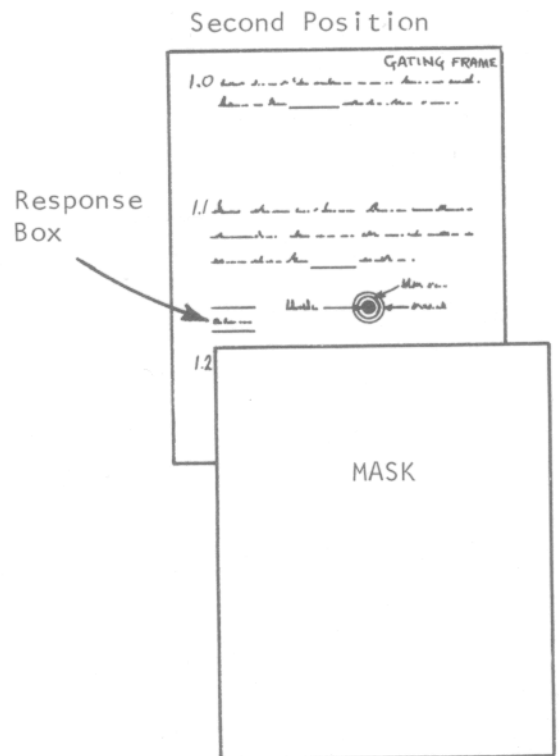

VOLUME 3 - TRANSISTORS

This volume is about the theory of operation of transistors, their characteristics, parameters and limiting factors. It discusses the operation of the transistor as an amplifier and as a switch. It further discusses methods of measuring the transistors characteristics and parameters and the effects of external energy and environment on the transistor.

PREREQUISITES:

This volume assumes the reader's successful completion of Semiconductor Diodes and Transistors - Volume 1 - Basic Semiconductors and Diodes, and Volume 2 - Diode Devices or their equivalent.

BROAD OBJECTIVES:

On successful completion of this volume, the reader will have gained knowledge of the theory and operation of junction transistors as amplifiers and switches and their characteristics, while preparing himself by meeting some of the prerequisites for volume 4 of this programed instruction series (Circuit Analysis 1 - Amplifiers).

SPECIFIC OBJECTIVES:

When the reader has successfully completed this volume, he will be able to do the following:

1. Recall that a forward biased PN junction has majority carriers crossing the junction and becoming minority carriers. Some carriers move well beyond the junction before recombining. The average time the carriers exist as minority carriers is termed "minority carrier lifetime".
2. Recall that a different degree of doping in the two sides of a PN junction results in some carriers diffusing through the opposite side without recombining.
3. Recall that doping one side of a PN junction lightly and making it very narrow results in much of the current being transported by diffusion.

4. Recall that the N or the P side of the junction can be doped lighter and made narrow to enhance current by diffusion.
5. Recall that two junctions can be formed in a single piece of semiconductor and the same action will take place at both junctions as when the basic diode is formed.
6. Recall that junction transistors are constructed by doping two junctions in a single piece of semiconductor, and that the center is doped much lighter than the ends to enhance diffusion current in the center.
7. Recall that the center portion of the transistor is made very narrow to enhance diffusion current in the center.
8. Name the three parts of the transistor and the paths of current carriers through the parts.
9. Recall that forward bias is applied to the emitter-base junction which results in the emitter injecting carriers into the base.
10. Recall that the collector junction is normally reversed biased and depends on minority carriers in the base for current.
11. Recall the current distribution in the transistor when conducting.
12. Recognize the symbol for common base d-c current gain. Recall the definition of common base d-c current gain and be able to apply it to the solution of a problem dealing with transistor d-c currents.
13. Recognize the symbol for common emitter d-c current gain. Recall the definition of common emitter d-c current gain and be able to apply it to the solution of a problem dealing with transistor d-c currents.
14. Recall the proper polarities for biasing both junctions of the transistor. Recall the effects of a varying emitter or base current on the collector current and for a given change, while will result in the larger change in collector current.
15. Recall that without injected carriers from the emitter there will be some collector current carried by thermally generated carriers. Recognize its

symbol as I_{CBO} and recall that its magnitude will vary with temperature changes.

16. Define I_{CEO} and recall its relative magnitude with respect to I_{CBO} .
17. Recognize the symbols for both an NPN and a PNP transistor, and be able to label the parts.
18. Recognize the common emitter configuration and recall its current gain capabilities with respect to unity.
19. Recall that both voltage gain and current gain are possible with a transistor in a common emitter configuration which makes possible a high power gain.
20. Recall the definition of the symbol h_{fe} , and recall that it does not take into account the circuit effects.
21. Recall the definition of the symbol h_{fb} , and recall that it does not take into account circuit effects.
22. Recall that voltage gain is possible with a transistor in a common base configuration and a corresponding power gain.
23. Recognize the common collector configuration and recall the magnitude of possible current and voltage gains with respect to unity.
24. Recall that the common collector configuration is also termed an "emitter follower".
25. Recall the definition of the symbol h_{fc} and its relative magnitude with respect to h_{fe} .
26. Recall the typical magnitude of input and output resistance of the common collector configuration.
27. Recall that the emitter follower finds use in situations requiring high output currents to drive capacitance.
28. Recognize the collector family of curves for a transistor, and recall how it is plotted. Recall that it allows a cross reference of the transistors voltage and currents.

29. Recall that h_{fe} may be calculated from data gained from the collector family of curves or plotted directly on the 575 Transistor-Curve Tracer, and be able to apply this in making a measurement of h_{fe} when given the curves and the point of measurement.
30. Construct a load line on the collector family of curves by recalling what determines the slope of the load line and how to construct it when given appropriate values.
31. Construct a load line on a collector family of curves and determine the quiescent operating point when given a circuit with component values and a collector family of curves.
32. Recall the definition of transistor saturation, $V_{CE}(\text{sat})$, $h_{FE}(\text{sat})$, and the bias condition at the collector junction at saturation.
33. Recall the bias conditions of the two junctions at saturation and that entering saturation increases the stored charge in the base of the transistor.
34. Given a circuit and collector family of curves, construct a load line, determine the static operating point base current, collector current, collector voltage and, given an applied signal current, determine circuit current gain.
35. Recognize avalanche breakdown on a collector family of curves, and recall that it relates to avalanche breakdown in the basic diode.
36. Recall the definitions and circuitry involved for B_{VCE0} , B_{VCB0} , and B_{VCER} , and that they are all temperature sensitive. Recall the curves on which each is measured when using a collector family of curves.
37. Recall the factors limiting the maximum power handling capability of a transistor and the terminology involved.
38. Recognize the symbols used and recall their meaning when using a thermal to electrical analogy to gain parameters for dealing with thermal problems in transistors.
39. Recognize the change in the thermal to electrical analogy that takes place when a heat sink and silicone lubricant are used to increase the power

dissipation capabilities of a transistor.

40. Solve a problem determining maximum steady state power dissipation when given θ_{SA} , θ_{JC} , θ_{CS} , T_A and T_{Jmax} .
41. Construct a maximum power curve on the collector family of curves of a transistor and recall the position of a load line for maximum output current swing.
42. Position a load line on the collector family of curves of a transistor for maximum output voltage swing.
43. Recall that very little power is dissipated by the transistor at cut-off or saturation, but that substantial power is dissipated in the area between these two limits which is termed the "active" or "transient" region.
44. Recall that when the transistor is acting as a switch, with its resting states at cut-off and saturation, it is possible for its load line to cross the maximum power hyperbola which allows greater power dissipation during switching than when a resting state occurs in the active region.
45. Recall that operating a transistor in the cut-off to saturated switching mode has the advantage of low resting state power dissipation, but the disadvantage of a larger stored charge which limits maximum repetition rate.
46. Recognize the symbols for the transistor switching parameters, and be able to define them. Recall what limits t_{on} and t_{off} of the transistor in the switching mode and a method of measuring the switching parameters.
47. Recall that the Tektronix Type 290 Transistor Switching Time Tester, or the Type 292 Semiconductor Tester in conjunction with a sampling system, may be used to check a transistor's switching times.
48. Recall the action of a speed-up capacitor when used to speed up a transistor switch, and be able to calculate the optimum value of speed-up capacitor given the voltage across the speed-up capacitor and the stored charge of the transistor.
49. Recall the meaning of current mode switching and that this mode reduces storage time which increases maximum possible repetition rate while sacri-

ficing maximum power dissipation with respect to the off to saturated mode.

50. Recall that current mode switching offers high speed, low noise, less critical transistor requirements, but more complicated design problems when compared to the off to saturated mode.
51. Recall that an avalanche switching transistor operates between cut-off and a point in the avalanche breakdown region and that the switching time can be on the order of fractional nanoseconds.
52. Recall that the main high frequency limiting factors of a transistor are junction capacitance transit time and the spreading out of carriers in the base.
53. Recognize the symbol for the cut-off frequency of a transistor in a common base configuration, and recall that it indicates the frequency at which low frequency h_{fb} has decreased to 0.707 of its low frequency value.
54. Recognize the symbol for cut-off frequency of the transistor in a common emitter configuration, and recall that it indicates the frequency at which h_{fe} has decreased to 0.707 of its low frequency value.
55. Recognize the symbols for output capacitance of the transistor in a common emitter and a common base configuration, and recall that they are related by the formula $C_{ob} = C_{oe} (1 + h_{fb})$.
56. Recall that high frequency construction calls for a thin, uniform width base and that the narrower the base, the less the transit time and spreading out of the carriers.
57. Define f_t as the frequency at which low frequency h_{fe} has decreased to unity, and recall that f_t gives information on the transistor beyond f_{hfe} .
58. Recognize the construction of the rate-grown and alloy type transistors, and recall their high frequency limitations.
59. Recognize the construction of the micro alloy and micro alloy diffused transistors and recall their frequency limitations. Recall that the micro alloy diffused is sometimes termed a drift field transistor.

60. Recognize the construction of the mesa and the epitaxial mesa, and recall the advantages gained from the epitaxial layer.
61. Recognize the construction of the planar transistor, and recall the definitions of the terms "surface passivated" and "double diffused".

The reader will know when he has met these objectives by correctly answering 90% of the questions in the self-test at the back of this program.

INSTRUCTIONS

The material in this program is presented in a series of numbered statements. Each numbered statement is termed a "frame" and each group of frames bearing the same number (3, 3.1, 3.2, etc.) is termed a "set". The answer to each frame is in a small box in the lower left hand corner of the following frame.

The material is presented in three types of frames within a set; the "gating frame", the "teaching frame", and the "criterion frame".

The first frame in each set is the gating frame. Cover the following frame which contains the answers with the mask provided. Read the frame carefully, studying any diagrams that are provided and fill in the blanks. Do not look at the answer until you fill in the blanks.

You must know something about the material to fill in the blanks in the gating frames as there is no clue given to the answer. If you can answer the gating frame and you are sure of the material, skip to the next gating frame and continue. The gating frames are designed to give the student that is familiar with the subject an indication of the information contained in the set and allow him to skip the set if he feels he knows the information covered.

If you cannot answer the gating frame, continue with the teaching frames in that set, covering the answers and filling in the blanks. You will find clues to the answers in the teaching frames or their diagrams.

The last frame in each set will have 2 (**) asterisks following the number. This is the criterion frame and once again, no clue is given to the answers. The preceding teaching frames should have provided the information needed to work the criterion frame. If your answer is wrong, go back and review the material in the teaching frames.

You may progress through the program at any speed you select. Don't miss an opportunity to review the material in a set if you can answer the gating frame but are a little hazy on the subject.

This is not a test. You are not being graded and you are not expected to be able to answer the gating frames unless you have the knowledge to let you skip a set. If you answer the teaching frames or the criterion frames incorrectly, don't be concerned, but go back and review the previous frame or frames as needed. Answer from the information presented and, if your answer does not match, review the material before going on.


If you would like to measure your progress, go to the back of the volume and do the self test without grading it before proceeding with the programed material. After completing the programed material, do the self test again and grade both attempts. This will give you an indication of the gains that you have made with this volume.

Do each set of the programed material in sequence, starting with Set 1.

If you are ready to proceed with the programed material, turn to the first gating frame - - - -


- 1 A generator with a very high internal resistance with respect to the external circuit can be considered to be a constant _____ generator, and a generator with a very low internal resistance with respect to the external circuit can be considered to be a constant _____ generator.

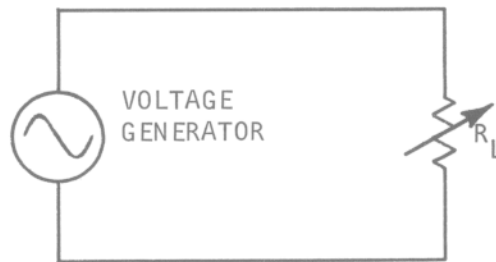- 1.1 The generator shown has zero internal resistance. Changes in the size of R_L have no effect on the voltage across R_L .




current
voltage

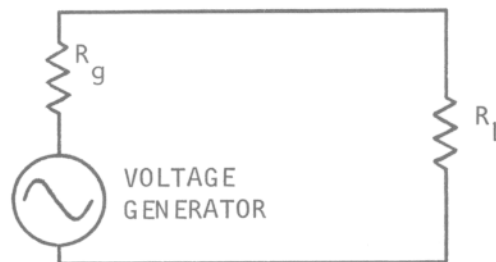- 1.2 The generator shown has a finite internal resistance represented by R_g . The generator voltage will be distributed between _____ and _____.




no answer needed

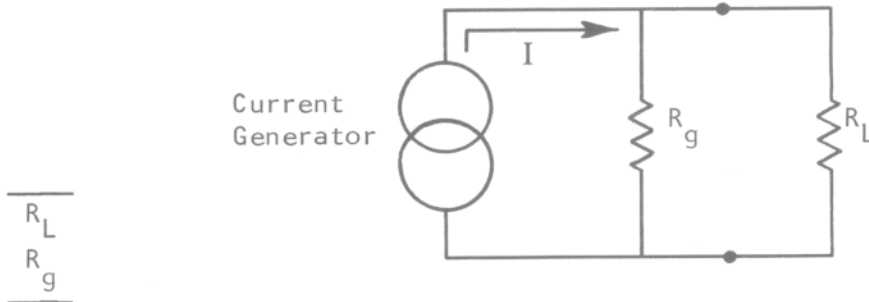1.3 A generator can also be shown as a current generator shunted by a resistance. The current supplied by the generator shown divides between _____ and _____.




 R_L
 R_g

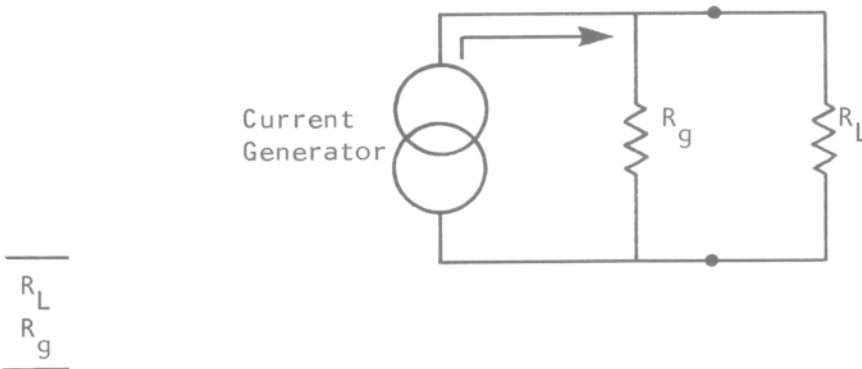1.4 If R_g in the diagram has a value approaching infinity, most of the generator current is in _____.



 R_L
 R_g

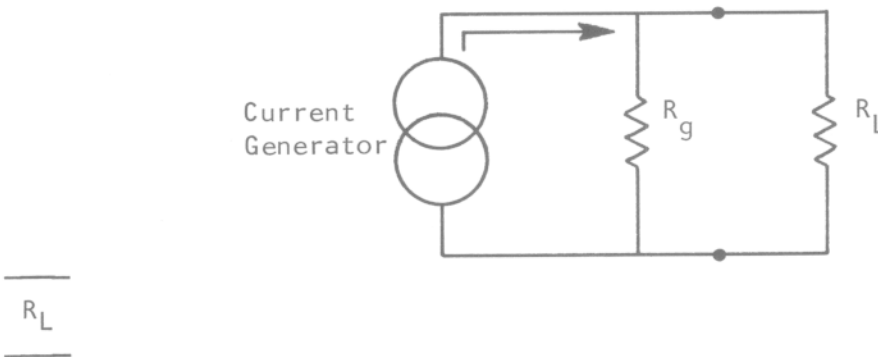1.5 If R_g in the diagram is not approaching infinity, but is very large with respect to R_L , most of the supplied current will flow in R_L .



 R_L

1.6 A generator with an internal resistance very large with respect to the external circuit can be considered a constant current generator (referring to magnitude).

no answer needed

1.7 A generator with an internal resistance or impedance very large with respect to the circuit it is supplying can be considered a constant _____ generator, since the _____ will change very little with changes in the load resistance or impedance.

no answer needed

1.8 A constant current generator has a very _____ internal impedance with respect to the circuit it is supplying.

current
current

1.9 A generator with a very low internal impedance with respect to the circuit it is supplying will have very little change in the output voltage with changes in the load.

high, large, etc.

1.10 A generator with a very low internal impedance with respect to the circuit it is supplying will supply a near constant* _____ with changes in the load. (* referring to magnitude)

no answer needed

1.11 A low impedance generator can be considered a _____* voltage generator if it is driving a circuit with a much higher impedance. (* referring to magnitude)

voltage

1.12** A low impedance generator will supply a near constant _____ magnitude if driving a high impedance circuit and a high impedance generator will supply a near constant _____ magnitude if driving a low impedance circuit.


constant

1.13 END OF SET

voltage
current

2 A circuit or device can be said to be essentially current or voltage driven or biased depending on the _____ of the driving generator with respect to the _____ of the circuit being driven.

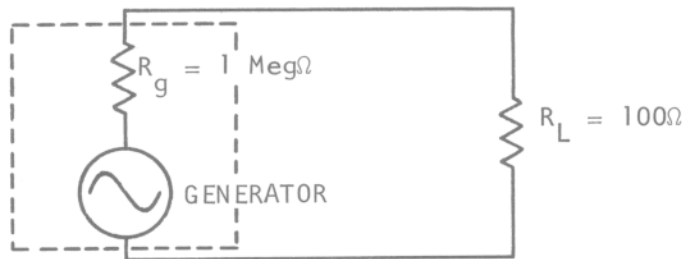2.1 In the circuit shown, the resistance of R_L must increase greatly to cause a significant change in the current in the circuit.



impedance
impedance

2.2 The generator shown can be considered to be a constant amplitude _____ generator.



no answer needed

- 2.3 Varying R_g will change the current in R_L . R_L is essentially current driven. (The current is changed which results in a voltage change.)



current

- 2.4 If the circuit or device to be driven changes its impedance when driven with voltage, it may be desirable to use a _____ impedance generator and essentially drive with current.

no answer needed


- 2.5 A d-c supply with a very high internal resistance with respect to its load is essentially ad-c _____ supply rather than a _____ supply.

high

2.6 For maximum transfer of power, the impedance of the generator or supply should be equal to the load impedance. This _____ the case when it is desired to drive with current or voltage.
(is, is not)

current
voltage

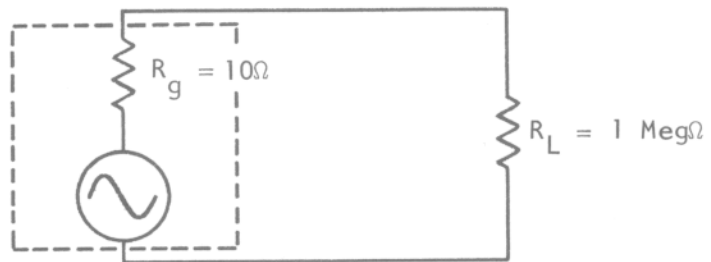2.7 The generator shown can be considered a constant* _____ generator. (* referring to magnitude)



is not

2.8 d-c biasing can be accomplished with a _____ supply as well as a voltage supply.

voltage

2.9 If the resistance of the biasing supply is very high with respect to the device to be biased, the device can be said to be biased with _____.

current

2.10 Using a much higher than needed voltage and adding a high value of series resistance results in a near constant _____ biasing supply. (NOTE: At Tektronix, this approach is typically referred to as long tailing.)

current

2.11 By using a large value of resistance in series with a high voltage to bias a device results in the series resistor having control of the _____ in the circuit.

current

2.12** Biasing and driving a circuit or device can be essentially current, voltage, or power depending on the relationship of the _____ in the circuit.

current

2.13 END OF SET

impedances

3 Forward biasing a junction results in some carriers traveling well beyond the junction before recombining. The average time they exist after crossing the junction is termed minority carrier _____.

3.1 Forward bias reduces the potential difference across a PN junction and results in majority carriers crossing the junction. Electrons in the N side and holes in the P side cross the junction when forward bias is applied. Once across the junction, these carriers are existing as _____ carriers.

lifetime

3.2 After crossing the junction, carriers must find imperfections in the covalent structure to accomplish recombination. With few _____ near the junction, some carriers must move well beyond the junction before recombining.

minority

3.3 After crossing the junction and before recombination occurs, the carriers are existing as _____.

imperfections

3.4 The longer the carriers exist as minority carriers, the more opportunity they will have to spread out in the opposite side before recombining. With few imperfections near the junction, the carriers will _____ out in the opposite side.

minority carriers

3.5 The average time that the carriers exist as minority carriers before recombining is termed minority carrier lifetime. The fewer the imperfections near the junction, the longer the _____ .

spread

3.6 If the minority carrier lifetime is long, some of the carriers will spread out through the entire opposite side of the junction without _____ .

minority carrier lifetime

3.7** Forward bias results in majority carriers crossing the junction. After crossing the junction, they exist as _____. The average time they exist after crossing the junction is termed _____ .

recombining

3.8

END OF SET


minority carriers
minority carrier lifetime

4 Applying forward bias to a PN junction with the P side doped much lighter than the N side results in some of the electrons recombining with holes in the P side, but some of the electrons will _____ through the P side without _____.

4.1 Electrons crossing the junction as a result of applied forward bias must find imperfections before they can recombine. If the electrons do not find imperfections, they will not _____.


diffuse
recombining

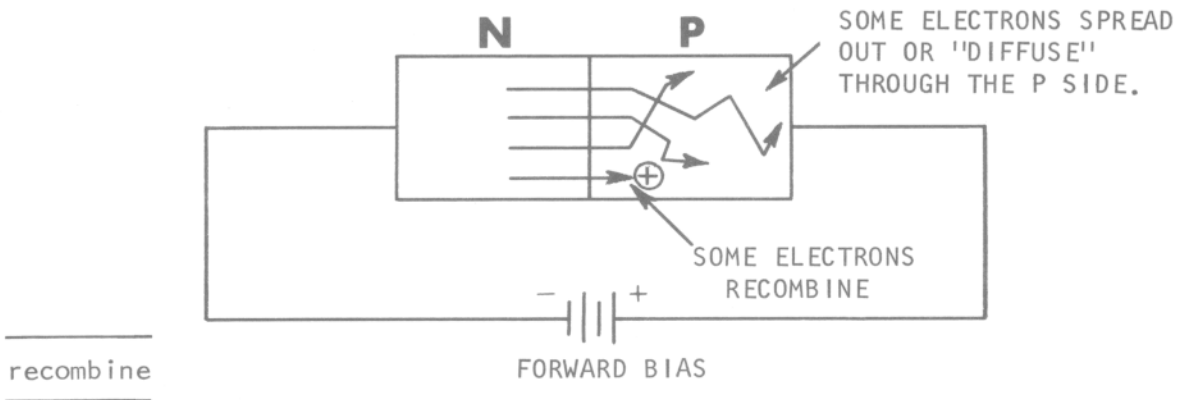4.2 Electrons injected into the P side as a result of applied forward bias, but unable to find _____, spread out or "diffuse" in the P side and do not recombine.



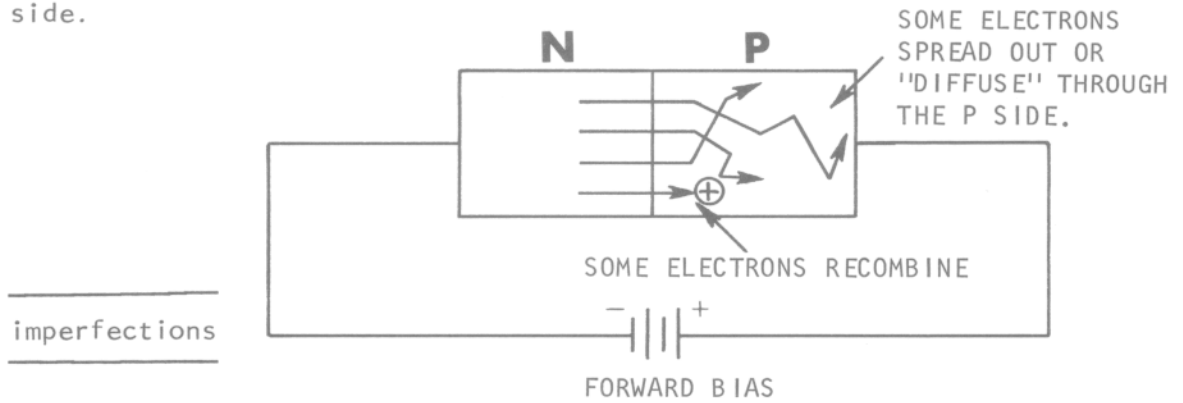4.3

Doping the P side much lighter than the N side results in many electrons injected into the P side by forward bias that cannot find imperfections to recombine. These electrons will _____ or spread out in the P side.




4.4

Doping the P side with less impurities than the N side, results in forward bias injecting electrons into the P side that cannot readily recombine. These electrons are existing as _____ carriers while in the P side.


diffuse

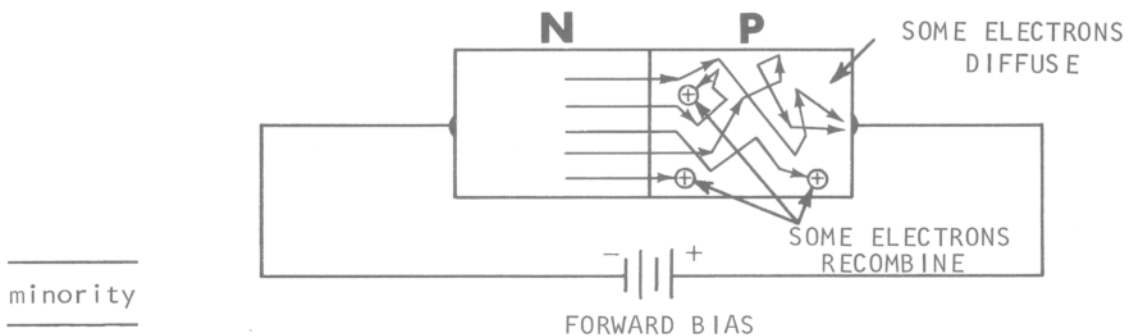4.5

Electrons crossing the junction (as a result of forward bias) that do not find imperfections, diffuse through the P side without recombining. Doping the P side with fewer imperfections than the N side results in some electrons _____ through the P side without _____.



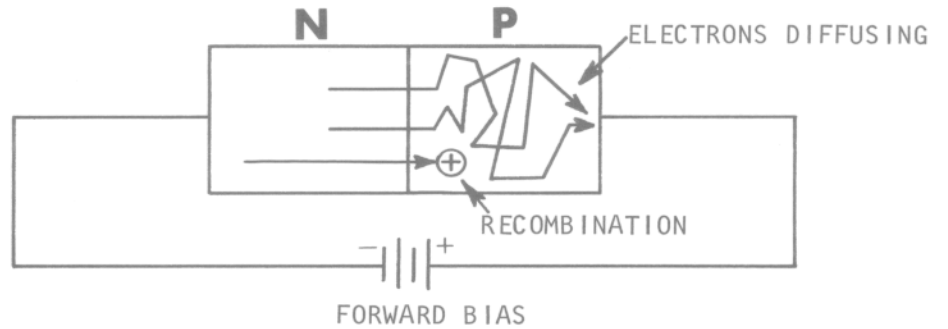4.6 Some electrons diffusing through the P side are attracted to the positive side of the bias source. Doping the P side much lighter than the N side results in some of the current in the external circuit being the result of _____ current in the diode.



_____ diffusing
recombining

4.7 Current transported by both recombination and _____ will result when electrons are injected into the P side and find insufficient imperfections to recombine.

_____ diffusion

4.8** Doping the P side much lighter than the N side results in injected electrons that _____ through the P side without _____.

_____ diffusion


4.9

END OF SET

diffuse
recombining


5 Doping the P side much lighter than the N side and making the P side very narrow results in most of the injected electrons diffusing through the P side without recombining.

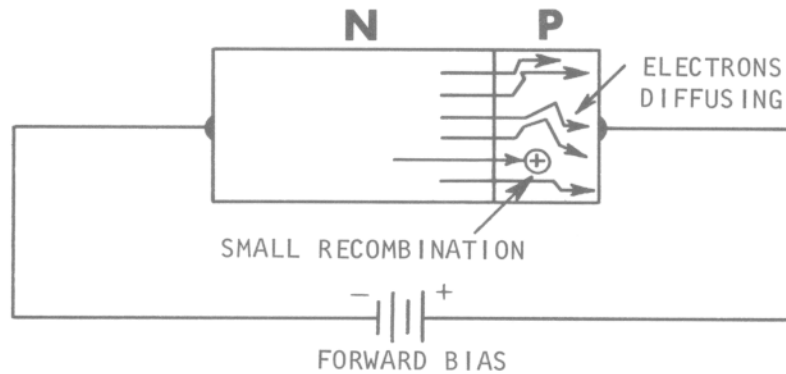5.1 Only a few of the electrons forced across the junction by applied forward bias find imperfections and recombine when the P side is doped much lighter than the N side.



lighter
narrow

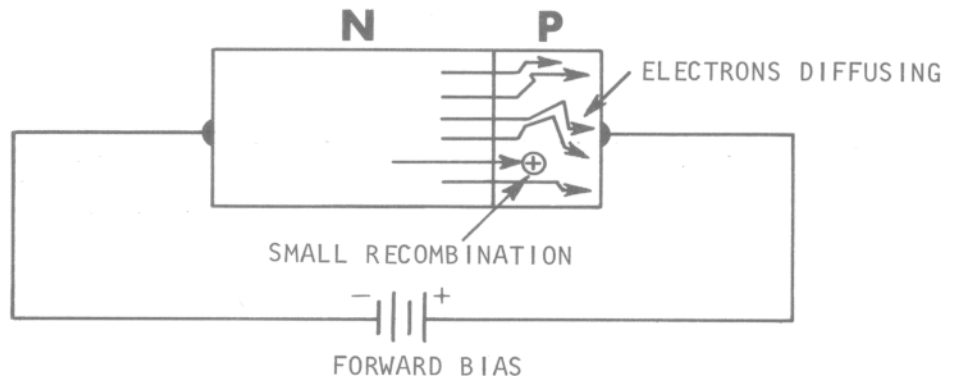5.2 The electrons forced across the junction by forward bias diffuse in the lightly doped P side. If the P side is made very narrow, most of the diffusing electrons pass through the P side without recombining.



recombine

5.3


Electron current in the external circuit results when electrons diffuse through the P side. The greater the number of diffusing electrons that cross the P material, the greater the external _____.

electrons recombining

5.4

Electrons forced across the junction by forward bias and diffusing through the P side are existing as minority carriers. Forward bias current is made up primarily of _____ when the P side is doped much lighter than the N side.

electron current

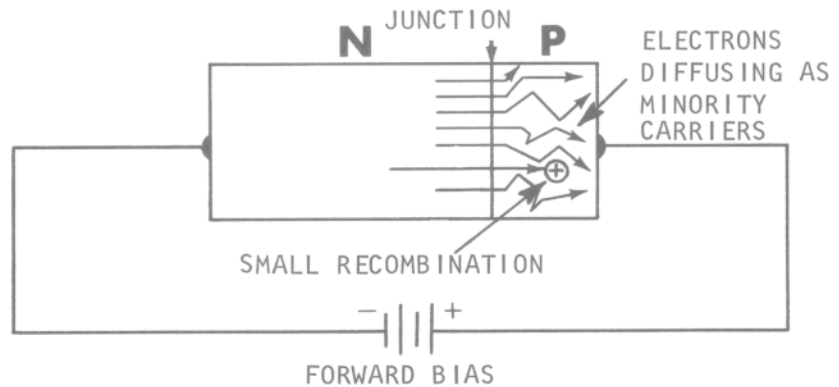

5.5**

Doping the P side much lighter than the N side and making the P side narrow results in most of the electrons that cross the junction _____ through the P side as _____ carriers.

minority carriers or diffusion current

5.6

END OF SET

diffusing
minority


6 Doping the N side of the junction much lighter than the P side and making the N side very narrow results in _____ diffusing through the _____ side when forward bias is applied.

6.1 Doping the N side much lighter than the P side of the junction results in more holes being injected into the N side than there are imperfections for recombination. If the holes do not find _____, they will not _____.


holes
N

6.2 Holes injected into the N side that do not find imperfections, _____ through the N side.

imperfections
recombine

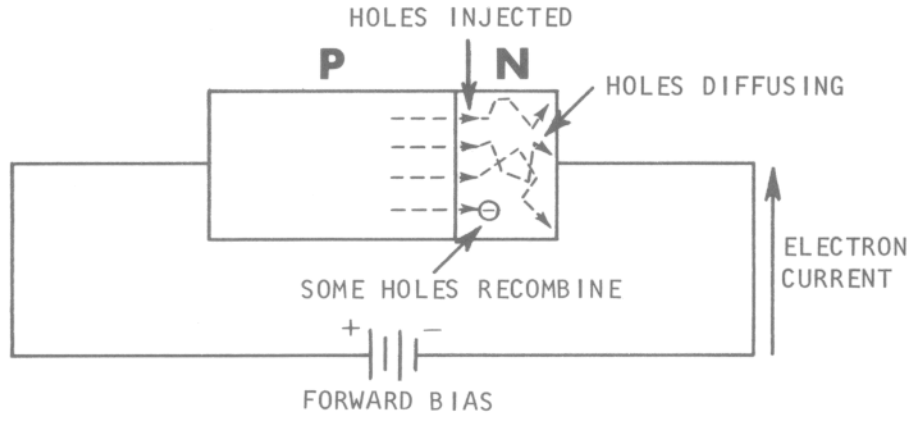


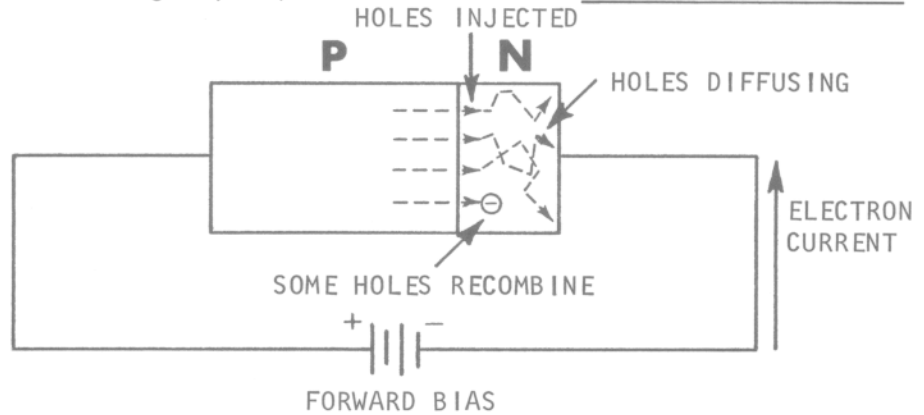6.3 If the N side is made very narrow, most of the injected holes will _____ across the lightly doped N side without _____.



diffuse

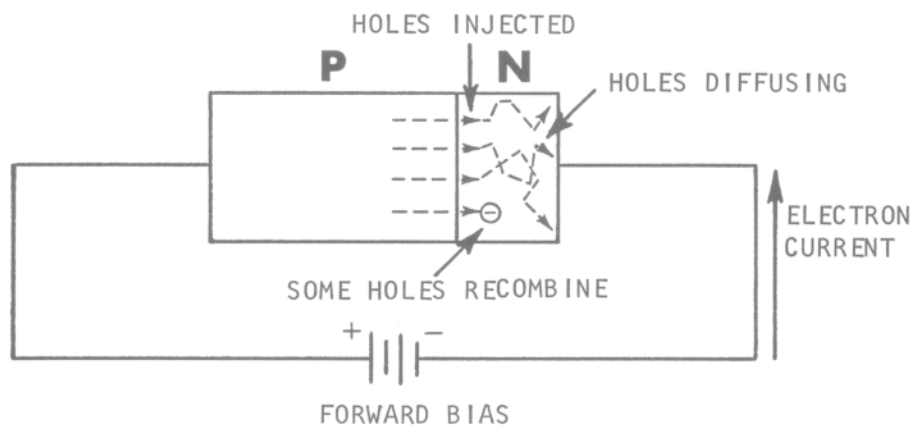6.4 Doping the N side much lighter than the P side and making the N side very narrow results in current by _____ of holes.



diffuse
recombining

6.5 Applying forward bias to a junction with a lightly doped, narrow N side, injects _____ into the N side that _____ through without _____.

diffusion

6.6***

The application of forward bias to a junction with a narrow and lightly doped N side results in current made up primarily of _____ that _____ through the N side.

holes
diffuse
recombining


6.7

END OF SET

holes
diffuse


7 Two junctions can be formed in a single piece of semiconductor material in either a _____ or _____ arrangement. Forming two junctions in the same semiconductor results in holes and electrons at each junction, _____ until a state of _____ exists at both junctions.

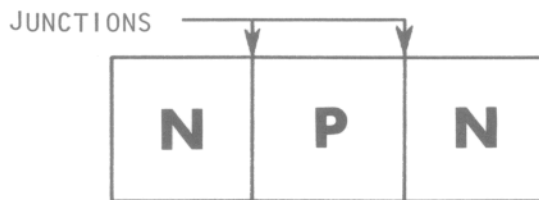7.1 If a piece of semiconductor has the two ends doped with N type impurities and the center with P type impurities, there will be two distinct _____ in the material.




 PNP or NPN
 recombining
equilibrium or balance

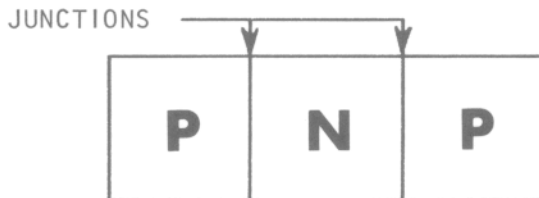7.2 Doping the two ends of the semiconductor with P type impurities and the center with N type impurities will also result in two distinct _____ in the material.




junctions

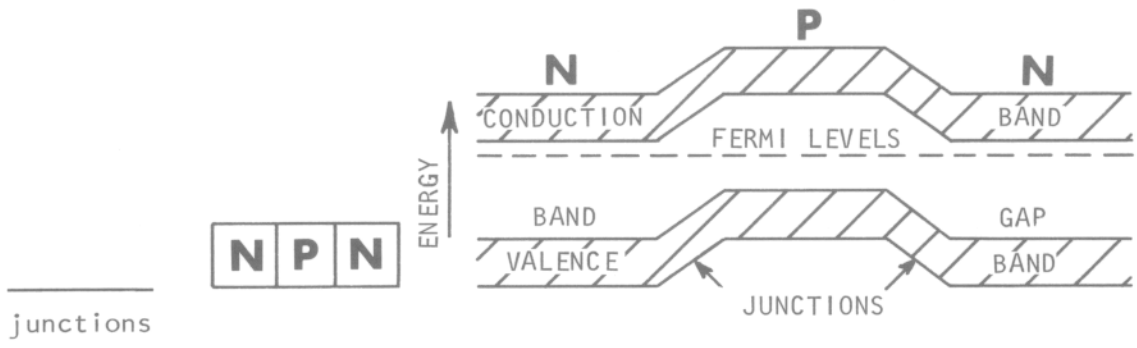7.3 With two junctions formed in the same semiconductor, recombination occurs at both junctions until the fermi levels line up. The alignment of the fermi levels indicates a state of _____.



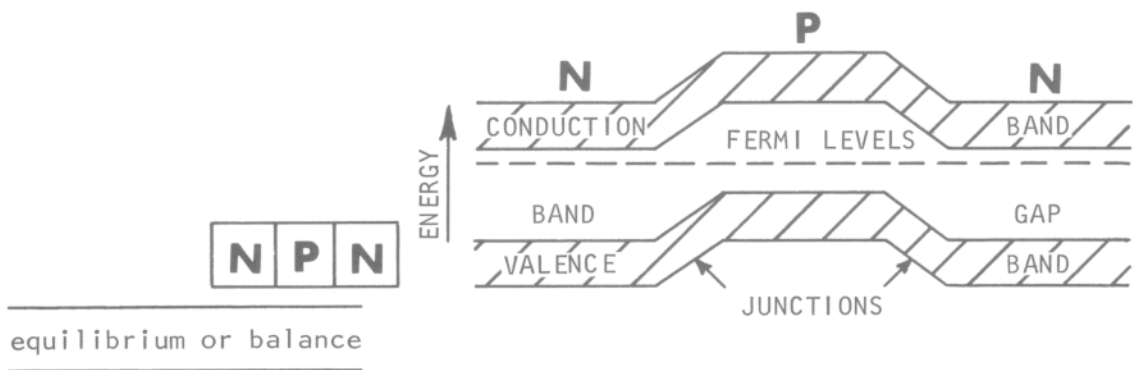7.4 With no external energy applied to a semiconductor containing two junctions, a potential difference exists across both junctions. The _____ must be overcome to have current.



7.5 When two junctions are formed in one piece of semiconductor, the same action occurs at both junctions as when a single _____ is formed.

potential difference

7.6** When two junctions are formed in a single piece of semiconductor,
_____ occurs at both junctions until a state of _____
exists across both junctions.


junction

7.7 END OF SET

recombination
equilibrium or balance

8 Junction transistors are manufactured by forming two junctions in a single semiconductor, The center is doped much _____ than the ends (heavier, lighter) to enhance _____ current in the center.

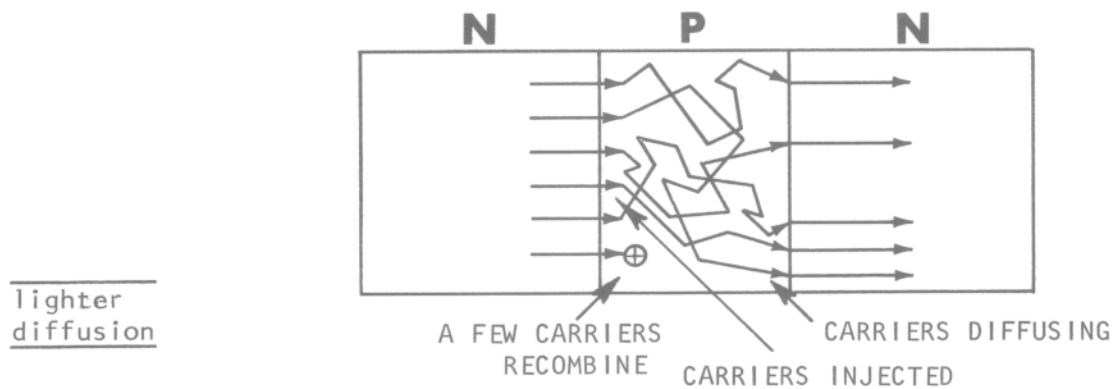8.1 A junction transistor functions by one end injecting carriers into the center portion and these carriers traveling as minority carriers through the center portion. Current in junction transistors relies on _____ current in the center portion.



8.2 Diffusion results when majority carriers are forced across the junction and are not able to find imperfections to recombine. Carriers forced across a junction that cannot imperfections, cannot _____ and, therefore, exist as _____ carriers.

diffusion (minority carrier)


8.3 Diffusing carriers are majority carriers that have been forced across a junction and are existing as minority carriers in the opposite side. Diffusing carriers unable to find _____ are existing as _____ carriers.

recombine
minority

8.4 The center of the junction transistor is doped much lighter than the ends to enhance diffusion of carriers in the center portion. Carriers forced into the center portion will exist as _____ carriers and will _____ through the center portion.

imperfections
minority

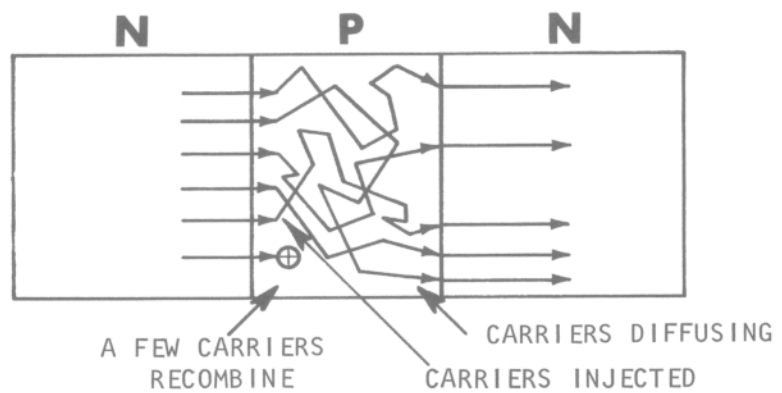8.5 With the center portion doped much lighter than the ends, some carriers will recombine in the center portion, but most of the carriers will _____ through the center.



minority
diffuse

8.6** Junction transistors are constructed by forming _____ (#) junctions in the one piece of semiconductor. The center is doped much lighter than the ends to enhance _____ in the center.

diffuse

8.7 END OF SET

2
diffusion

9 Junction transistors are manufactured by forming two junctions in a single piece of semiconductor. The width of the center portion between the two junctions is made very _____ to further enhance _____ by reducing _____.

9.1 Junction transistors are made by doping the two ends of a semiconductor different than the center and forming two distinct _____.



 narrow, thin, etc.
 diffusion
 recombination

9.2 The center of the semiconductor is doped much lighter than the ends to enhance diffusion in the center. The wider the center portion, the more carriers will recombine and the less will _____.

 junctions

9.3 The aim in junction transistors is to cause many of the carriers injected into the center portion to diffuse across the center region. The _____ the center portion for given doping levels, the more (wider, narrower) carriers will diffuse across.

_____ diffuse _____

9.4 Doping the center lightly results in a long minority carrier lifetime and enhances _____ of carriers.

_____ narrower _____

9.5 The transistor utilizes diffusion of carriers through the center portion of the device. The center portion is made very _____ to reduce recombination and increase _____.



_____ diffusion _____

9.6 The center of the transistor is doped much lighter than the ends to enhance diffusion in the center. The center is made very narrow to enhance carrier _____ and to reduce recombination.

narrow, thin, etc.
diffusion

9.7 Light doping in the center results in a long minority carrier lifetime and less carrier _____.

diffusion

9.8** The center portion of a junction transistor is made very _____ to enhance carrier _____ and reduce carrier _____.


recombination

9.9 END OF SET


narrow, thin, etc.
diffusion
recombination

10 That part of the transistor considered the source of current carriers is termed the _____ and the center part, the _____. The remaining part is termed the _____. The current carriers move through the parts of the transistor in _____ order as/than just stated.
 (the same, a different)

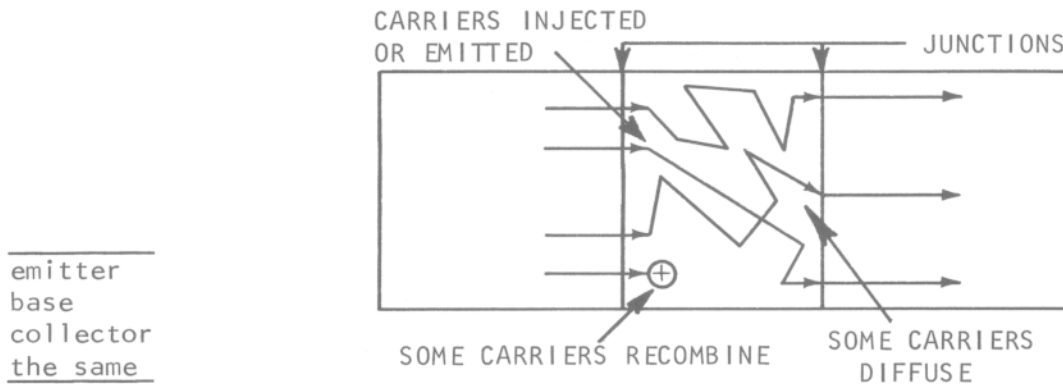10.1 The transistor works on the principle of one end of the device injecting or emitting carriers into the center portion. Once injected, the carriers either recombine or _____ through the center portion.




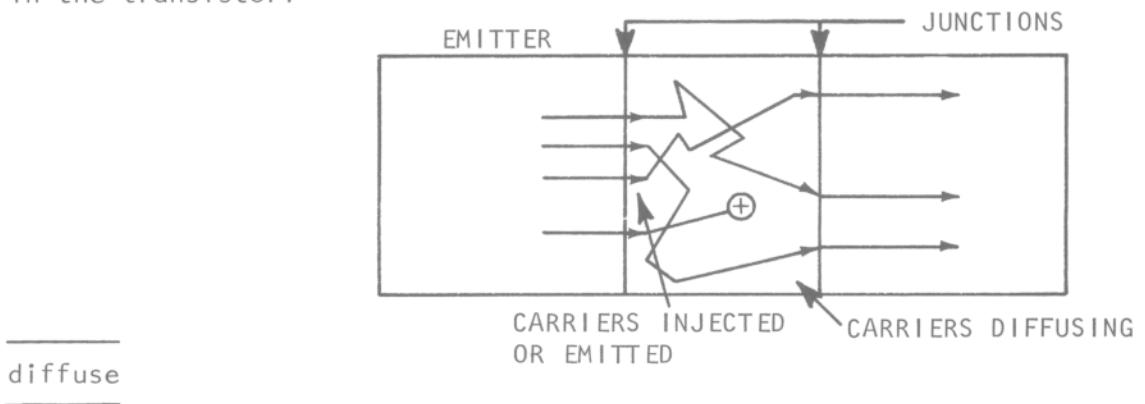10.2 Since one end injects or emits carriers into the center portion, it is called the _____ and is considered the source of current carriers in the transistor.



diffuse

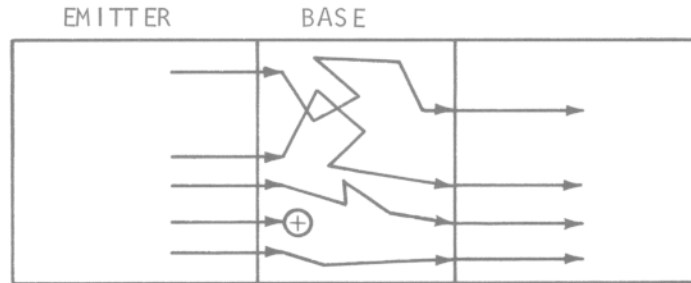10.3 The center portion of the transistor is termed the base. The emitter injects carriers into the _____.




_____ emitter

10.4 The emitter injects carriers into the base. Some of the carriers recombine but, due to the base being made very thin, most of them _____ through the base.

_____ base

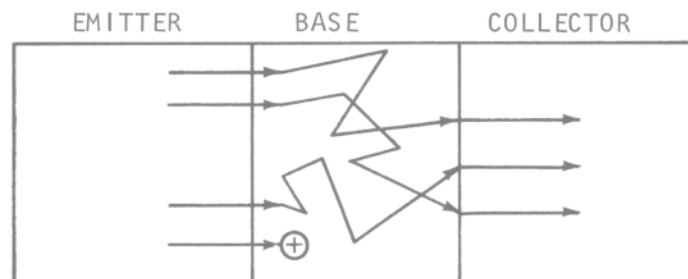10.5 The carriers that diffuse through the base are collected by the remaining end of the transistor. The three parts of the transistor are the emitter, base and the _____.



_____ diffuse

10.6 The emitter injects carriers into the base; the injected carriers diffuse through the base, and those that do not recombine are collected by the _____.

collector

10.7 Those carriers that recombine in the base become base lead or simply base current. Base lead current is $\frac{\text{_____}}{\text{(recombination, diffusion)}}$ current.

collector

10.8** Carriers are injected by the emitter into the _____ and diffuse to the _____. Those carriers that recombine in the base become _____ lead current.

recombination

10.9 END OF SET

base
collector
base

11 The emitter-base junction can be forward biased by a current or voltage source. A high resistance d-c source with respect to the d-c resistance of the emitter base junction will be essentially a d-c _____ source and a low resistance d-c source will be essentially a d-c _____ source.

11.1 The emitter-base junction must be forward biased to have current. To accomplish this, the current through the junction or the voltage across the junction can be controlled for biasing purposes.

current
voltage

11.2 A high resistance d-c source (with respect to the emitter-base junction) will essentially control the junction _____ for biasing purposes.

no answer needed

11.3 A low resistance d-c source (with respect to the emitter-base junction) will essentially control the junction _____ for biasing purposes.

current

11.4 A vacuum tube has the controlling circuit reversed biased* and uses a d-c voltage source normally for biasing purposes *(grid made negative with respect to the cathode).

voltage

11.5 A transistor has the emitter-base junction (its controlling circuit) forward biased in most cases and the junction resistance varies with voltage changes.

no answer needed

11.6 It is common to find a high resistance d-c source used to bias a transistor's emitter-base junction since it is a
biased junction. (forward, reverse)

no answer needed

11.7 Controlling the in the emitter-base junction of a transistor for biasing purposes is common, since the emitter-base junction is normally biased.

forward

11.8 Forward biasing a junction with current requires that the current source force majority carriers to cross the junction to recombine.

current
forward

11.9 When a biasing source is shown or referred to in this program, it can be either a voltage or current source, depending on its internal

_____.

no answer needed

11.10 Forward biasing the emitter base junction can refer to forcing current with a current source or voltage with a voltage source. In either case, the junction potential difference must be _____.
(increased, reduced)

resistance (impedance)

11.11** Forward bias applied to the emitter-base junction can be essentially a current or voltage source depending on its internal _____ with respect to the emitter-base d-c resistance. A high resistance source will be essentially a _____ biasing source.


reduced

11.12 END OF SET

resistance
current


12 The potential difference at the emitter-base junction must be reduced for the emitter to inject carriers into the base. This is done by applying _____ bias to the emitter-base junction. Those injected carriers that _____ recombine, diffuse through the base. Those carriers that do recombine make up what is termed _____ current.

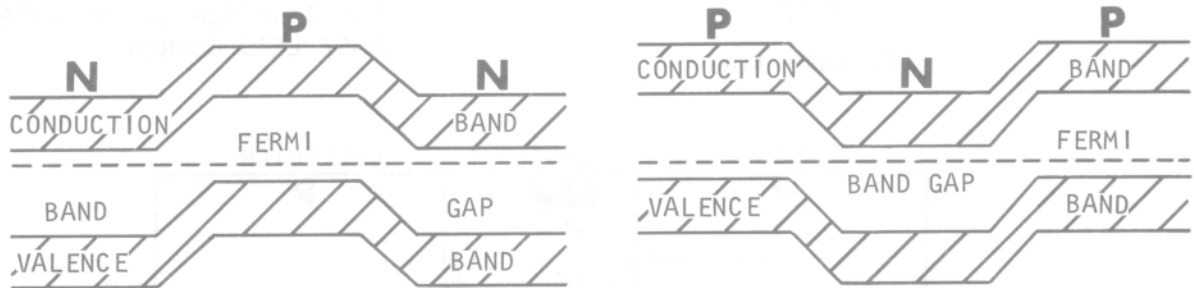12.1 Recombination occurs at both junctions until the fermi levels line up after two junctions are formed in a single piece of semiconductor. The fermi levels line up indicating a state of _____.



forward
do not
base

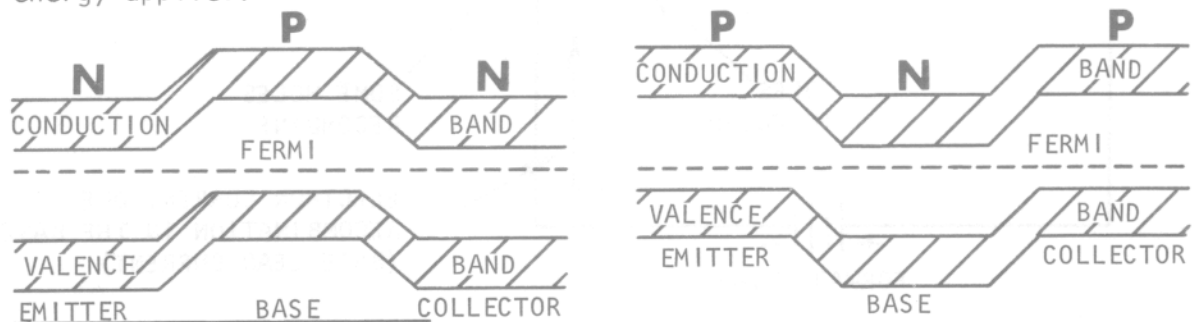12.2 Both junctions are at equilibrium with no external energy applied. The emitter _____ injecting carriers into the base without external energy applied.



equilibrium, balance, etc.

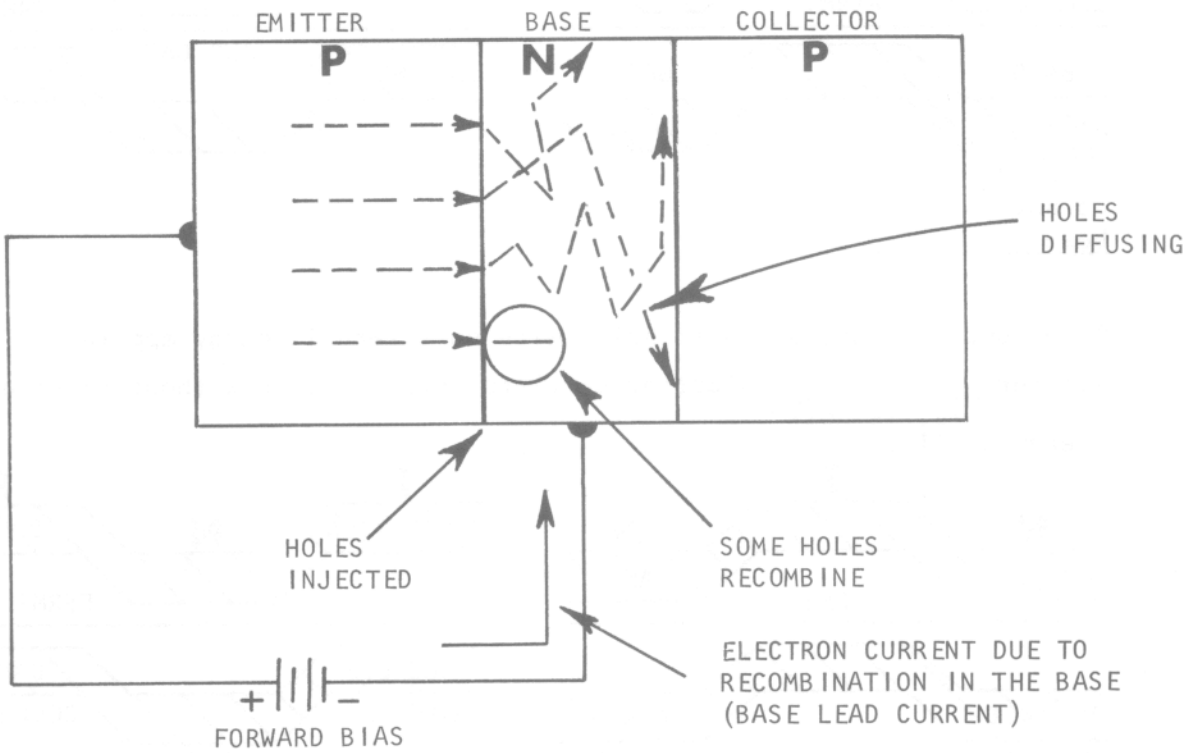
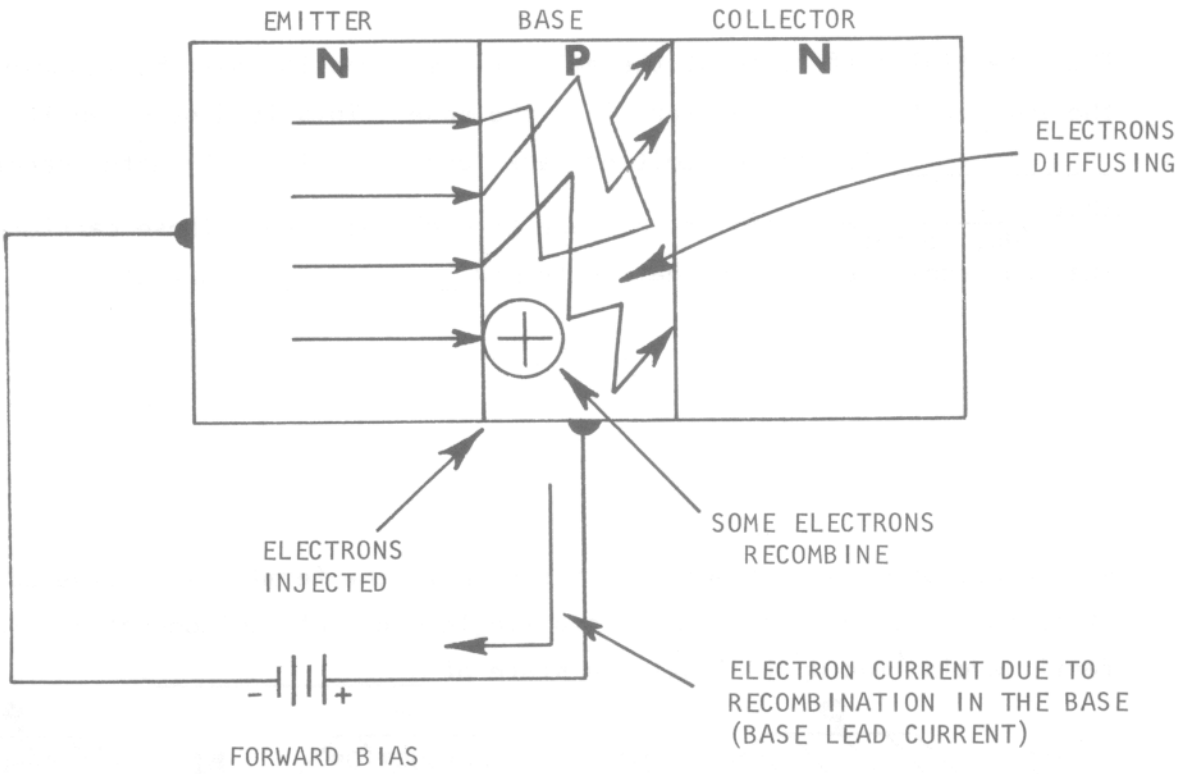


FIGURE 12

12.3 Forward bias applied reduces the potential difference between emitter and base, allowing majority carriers to move across the junction. Majority carriers become minority carriers, and those that do not recombine _____ through the base as shown in figure 12.

_____ is not _____

12.4 Forward bias injects many carriers into the base that cannot find imperfections and recombine. This is a result of the base being doped much lighter than the _____.

_____ diffuse _____

12.5 Figure 12 shows both a PNP and an NPN transistor with forward bias applied, emitter to base. For both PNP and NPN transistors, the emitter-base junction is _____ biased to inject carriers into the base.

_____ emitter _____

12.6 The carriers that do recombine make up base lead current. This current is generally referred to simply as _____ current.

_____ forward _____

12.7 The term base current refers to the current in the base lead as a result of carrier _____ in the base.

base

12.8 Carriers injected into the base that do not recombine exist as minority carriers and _____ through the base.

recombination

12.9** Injection of majority carriers from the emitter into the base is accomplished by application of _____ to the emitter-base junction. Injected carriers that do not recombine, _____ through the base as _____ carriers. Carriers that recombine in the base result in a current in the base connecting lead that is termed _____ current.

diffuse

12.10 END OF SET

forward bias
diffuse
minority
base

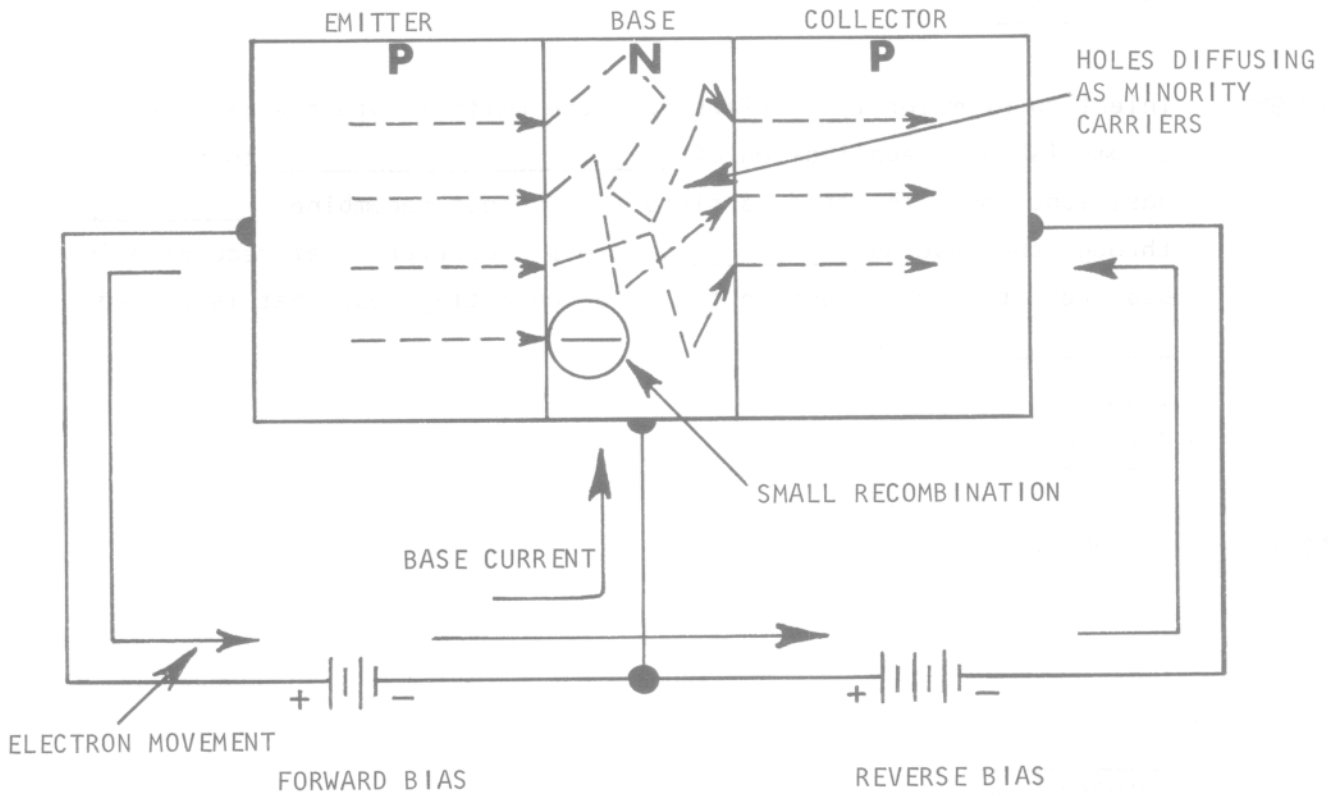
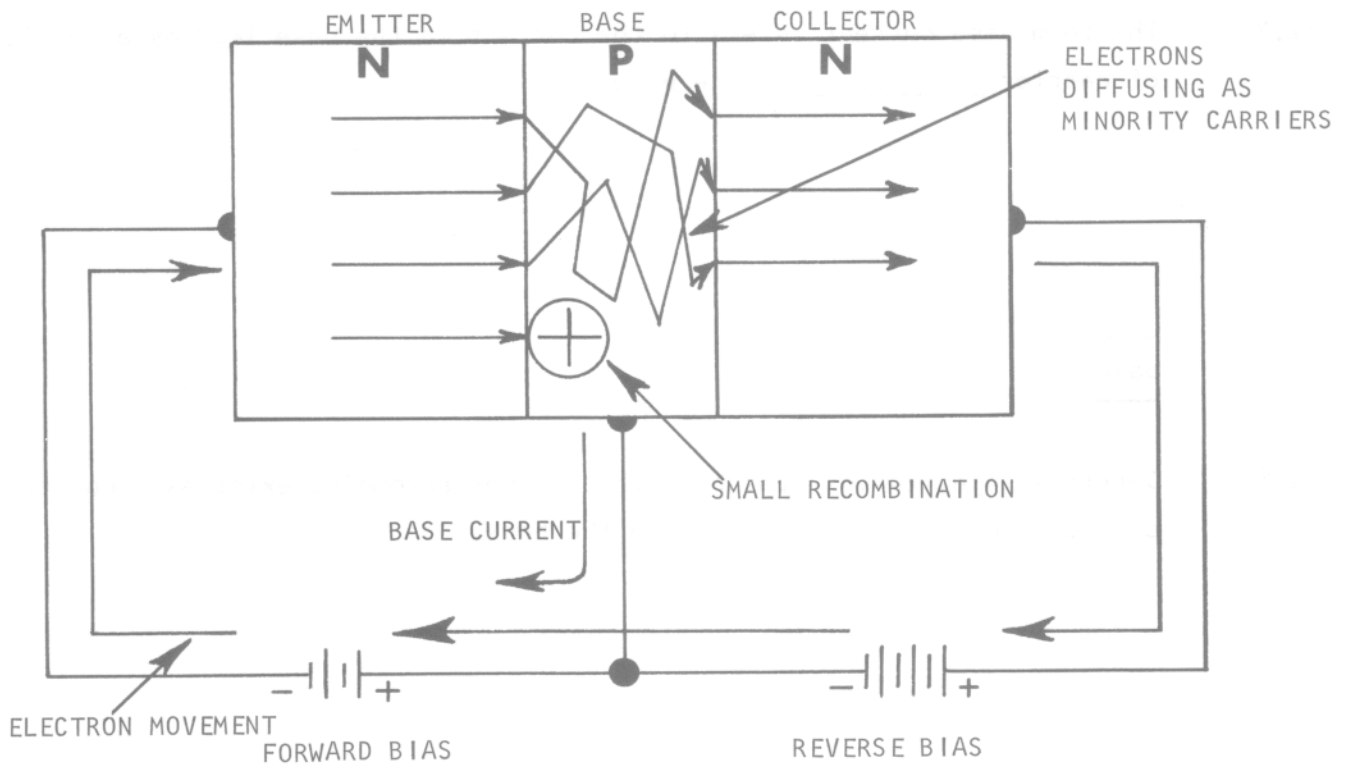


FIGURE 13

13 The collector to base junction of a transistor is _____ biased and its current depends on minority carriers present due to thermal energy or carriers that are injected into the base from the _____ that do not recombine.

13.1 The carriers injected into the base that do not recombine are existing as minority carriers. In order to collect them, the collector-base junction is _____ biased, as shown in figure 13.

reverse
emitter

13.2 Figure 13 shows both a NPN and a PNP transistor with biasing. Reverse biasing the collector-base junction causes this junction's current to be dependent on the number of minority carriers available in the _____.

reverse

13.3 Collector current is dependent on minority carriers in the base. Varying the number of injected minority carriers will vary the _____ in the collector junction.

base

13.4 The magnitude of the current in the reverse biased collector junction is dependent on the number of _____ carriers available in the base.

current

13.5 Reverse bias to the majority carriers will accelerate minority carriers across the junction if they enter the transition region.

minority

13.6 Without injected carriers from the emitter, the collector current is limited by the number of minority carriers in the base as a result of _____ energy.

no answer needed

13.7 The carriers injected from the emitter into the base that do not recombine are existing as _____ carriers in the base.

heat, thermal, etc.

13.8 The diffusing carriers in the base, injected by the emitter, provide a supply of minority current carriers for the _____ junction.

minority

13.9** The collector-base junction is _____ biased; its current magnitude is governed by the _____ carriers in the base as a result of heat energy or injection from the _____.


collector

13.10 END OF SET


reverse
minority
emitter

14 Base current is the result of _____ in the base and collector current is made up of carriers that _____ through the base. The emitter current in a transistor is the sum of _____ and _____ current.

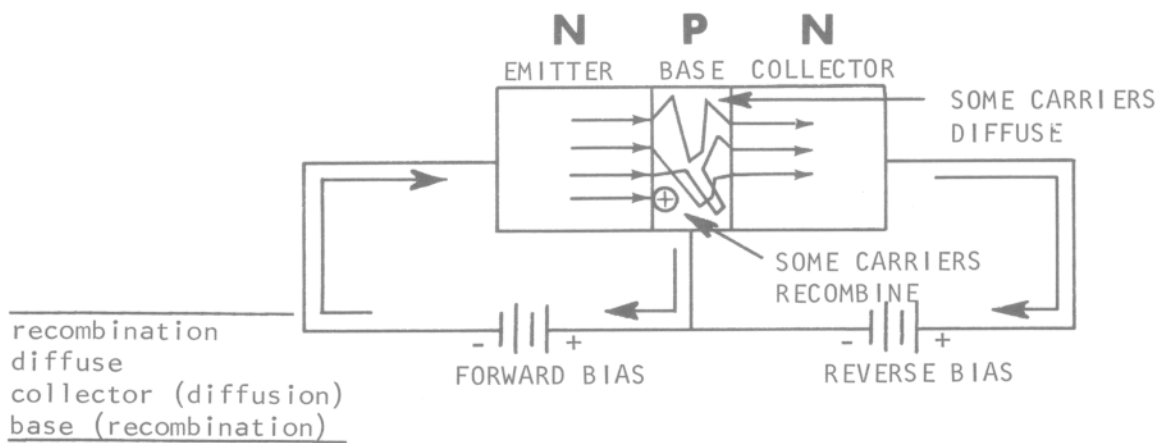
14.1 Forward biasing the emitter-base junction injects carriers into the base. Some carriers recombine and the rest _____ through the base.



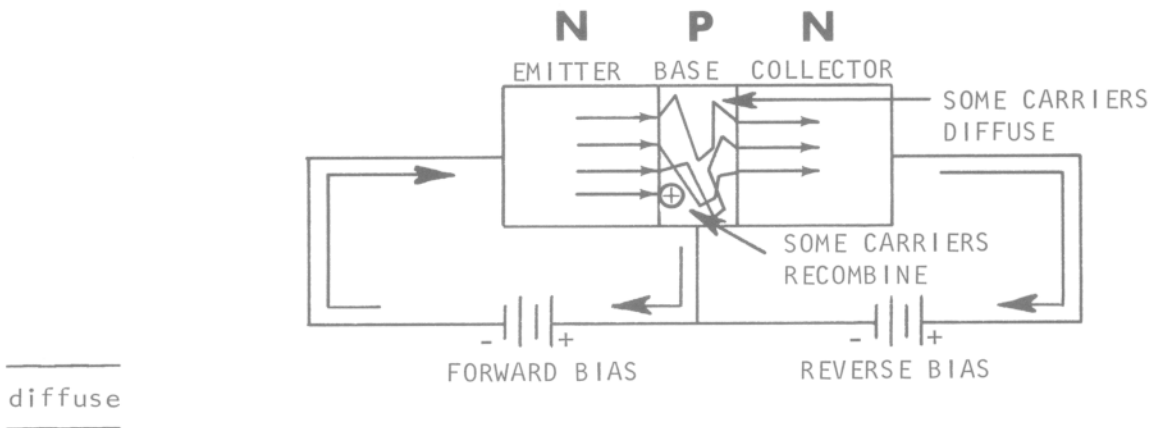14.2 Those injected carriers that do not recombine in the base and become base lead current diffuse through the base to the _____.



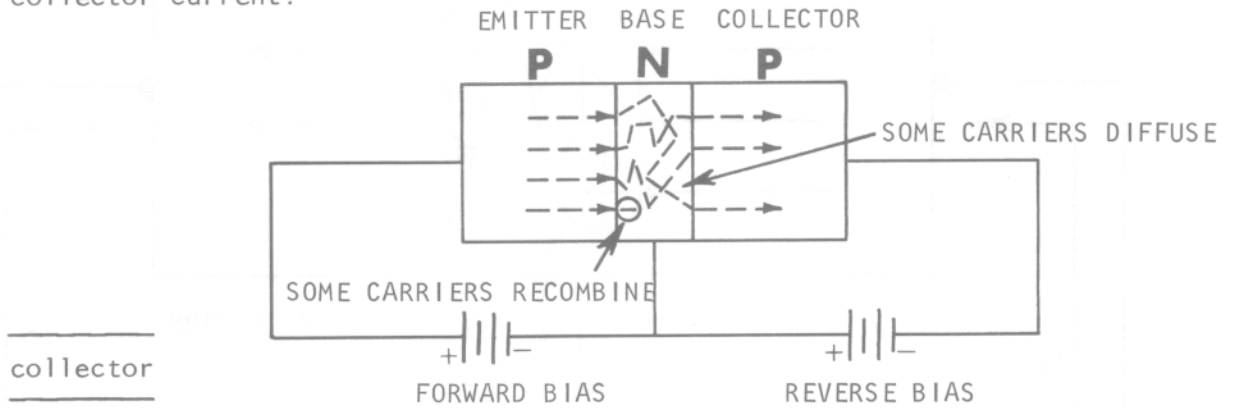14.3 The carriers injected into the base from the emitter either recombine and become base lead current or _____ to the collector and become collector current.



14.4 Base current is defined as the current in the base lead as a result of carrier _____.

diffuse

14.5 Collector current is the current in the collector lead that has _____ across the base.

recombination


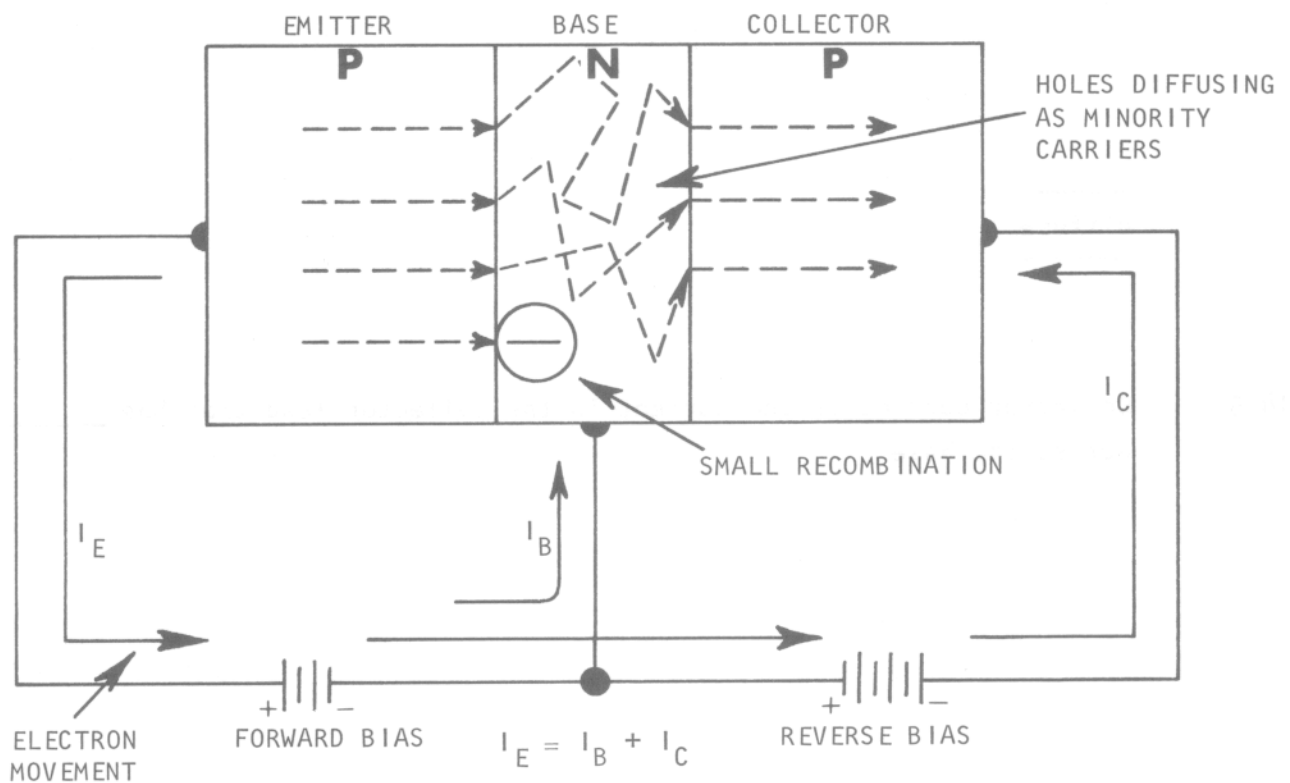
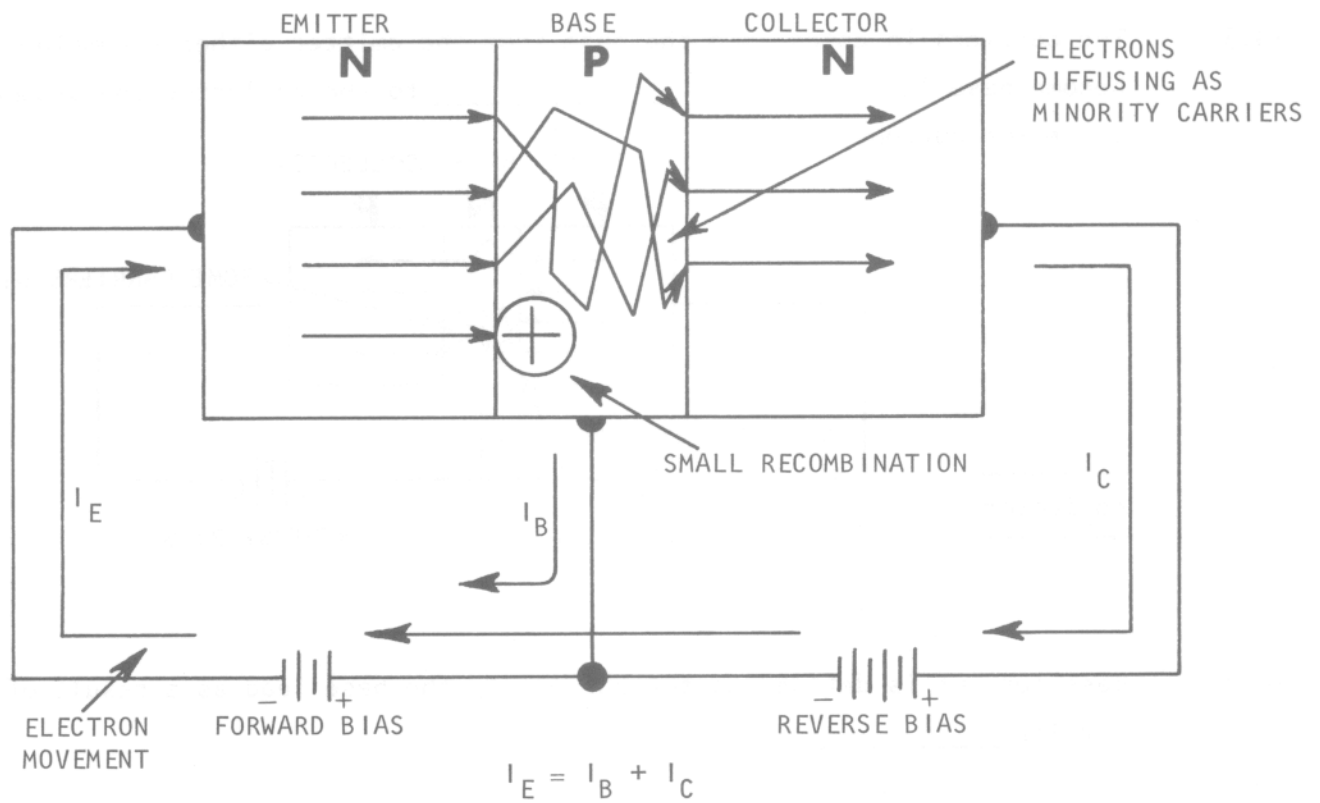


FIGURE 14

14.6 The sum of the carriers diffusing to the collector and the carriers that recombine in the base is equal to the _____ current.

diffused

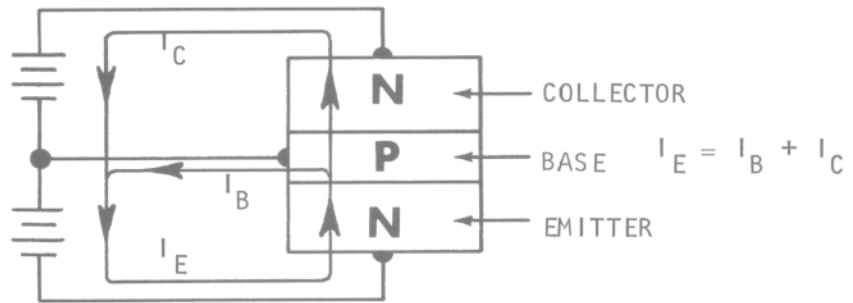

14.7 Figure 14 shows both a NPN and a PNP transistor indicating currents. I_E (d-c emitter current) is equal to the sum of I_C (d-c collector current) and I_B (d-c base current). $I_C = 20$ ma, $I_B = 1$ ma, $I_E =$ _____.

emitter

14.8** $I_E = 50$ ma, $I_B = 2$ ma, therefore $I_C =$ _____. I_B refers to the current in the base lead as a result of carrier _____ in the base.

21 ma


14.9

END OF SET

48 ma
recombination


15 The d-c current in the collector (I_C) can be calculated by taking the product of d-c emitter current (I_E) and the d-c current gain factor, emitter to collector. This factor is referred to as _____ or _____.

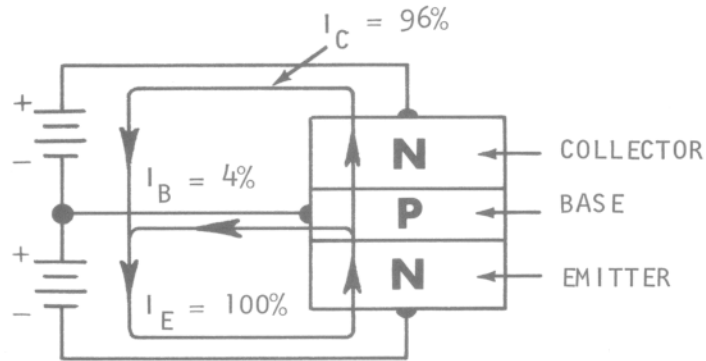15.1 The d-c current in the collector (I_C) is a percentage of the current in the emitter. In the diagram, collector current is _____% of emitter current.



alpha
 h_{FB}

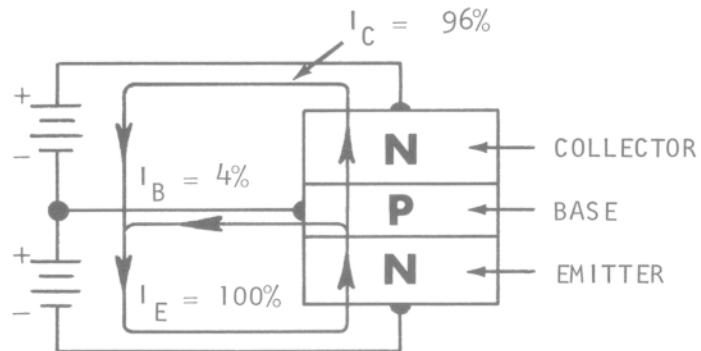15.2 If the current in the emitter (I_E) in the diagram is 10 milliamperes, the current in the collector (I_C) is _____ milliamperes.



15.3 The product of emitter current and the percentage of the emitter current that flows in the collector will give the value of _____ current.

9.6

15.4 If 92% of the emitter current flows in the collector, and the emitter current is 5 milliamps, the collector current is _____ milliamps.

collector

15.5 The d-c current gain from emitter to collector will be less than unity and the collector current will be _____ than the emitter current.
(more, less)

4.6

15.6 The fraction of emitter current that flows in the collector is called d-c alpha. The d-c current gain factor, emitter to collector, is termed d-c _____.

less

15.7 The symbol that indicates d-c alpha is h_{FB} and this is the current gain from _____ to collector.

alpha

15.8 The h in the symbol for d-c current gain stands for "hybrid" and simply indicates that it is a hybrid parameter.

emitter

15.9 The term "hybrid" indicates an approach to analyzing transistor circuits and the h indicates that the particular parameter so designated can be used with the _____ approach.

no answer needed

15.10 The "F" in the d-c current gain symbol indicates "forward d-c current gain" and the "B" indicates the common point for measurement.

hybrid

15.11 The symbol " h_{FB} " indicates hybrid forward current gain from emitter to collector since the B indicates that the _____ is the common point.

no answer needed

15.12 The product of "d-c alpha" or " h_{FB} " and the emitter current will give the value of collector current. If alpha is 0.97 and emitter current is 2 milliamps, collector current is _____ milliamps.

base

15.13 The symbol h_{FB} represents the d-c current gain factor of a transistor, from emitter to collector. h_{FB} will always be less than _____.

1.94

15.14** The symbol for d-c current gain emitter to collector is _____ and the product of d-c current gain and emitter current is equal to _____.


one, unity, etc.

15.15 END OF SET


h_{FB}
collector current (I_C)

16 The product of the d-c base current (I_B) and the d-c current gain factor from base to collector will give the value of _____ current. This current transfer factor is given the symbol _____ and called "d-c _____".

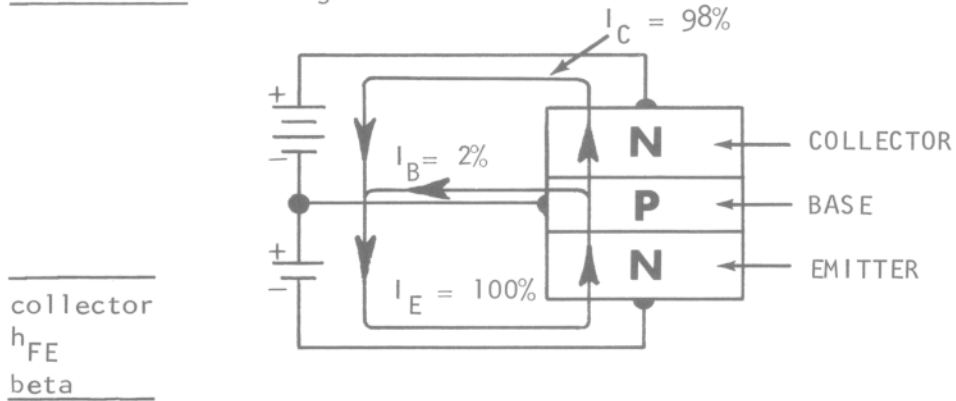
16.1 The collector current in the diagram is 98% of emitter current. The base current is 2% of emitter current. This means the collector current is _____ # times greater than base current.



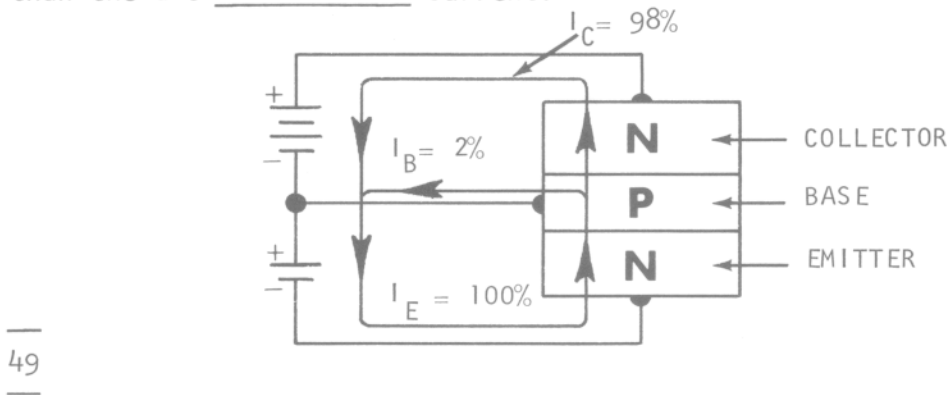16.2 The d-c current gain, base to collector, of the transistor in the diagram is 49. This means that the d-c collector currents is 49 times greater than the d-c _____ current.



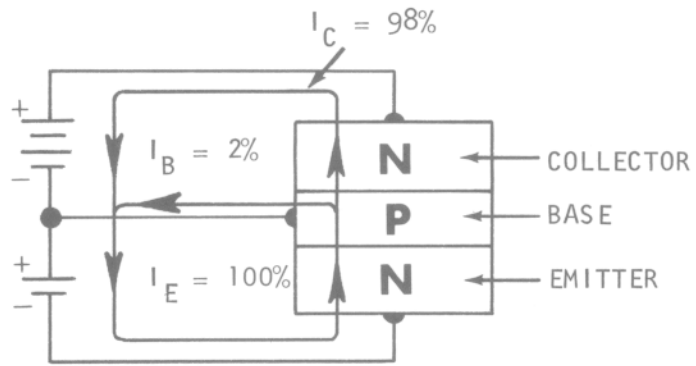16.3 If the base current in the diagram is 10 milliamps, the collector current is _____ milliamps.



base

16.4 The symbol given the d-c current gain factor is h_{FE} and is termed "d-c beta". $I_B \times h_{FE} =$ _____.

490

16.5 " h_{FE} " indicates hybrid forward d-c current gain, base to collector, since the E indicates that the _____ is the common point.

 I_C

16.6 If a transistor has an h_{FE} or d-c "beta" of 60 and a d-c base current of 15 milliamps, the collector d-c current will be _____ milliamps.

emitter

16.7 h_{FE} or d-c beta can be found by dividing the d-c collector current by the d-c base current. _____ = $\frac{I_C}{I_B}$
(symbol)

900

16.8** The d-c current gain factor, base to collector, is given the symbol _____. The product of _____ and d-c base current will give the value of d-c collector current.


 h_{FE}

16.9 END OF SET

 h_{FE}
 h_{FE}

17 The emitter base junction of a transistor is the controlling circuit and changes in emitter-base current or voltage will be accompanied by a change in the _____ current. A change in the base-emitter _____ will have the more linear effect.

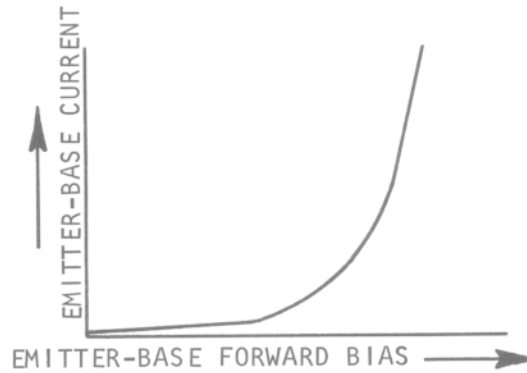17.1 The emitter-base junction of a transistor has a voltage versus current curve resembling that of a conventional diode.



collector current

17.2 Once the potential difference of the emitter-base junction has been reduced, majority carriers cross the junction.

no answer needed

17.3 Due to the difference in the doping levels in the emitter and the base, only a few of the carriers from the emitter find imperfections and accomplish _____.

no answer needed

17.4 Those carriers that do not recombine, _____ to the collector and become collector current.


recombination

17.5 A change in the emitter-base junction voltage will change the number of carriers injected from the emitter and thus change the number diffusing to the _____.


diffuse

17.6 The emitter-base junction EI curve shows that the current does not change linearly with changes in applied forward voltage.

collector

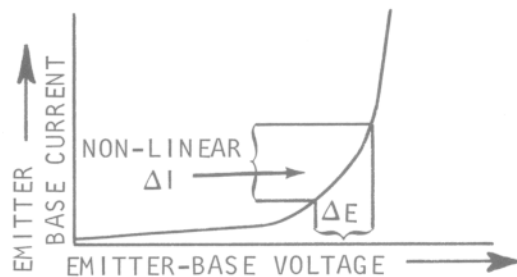

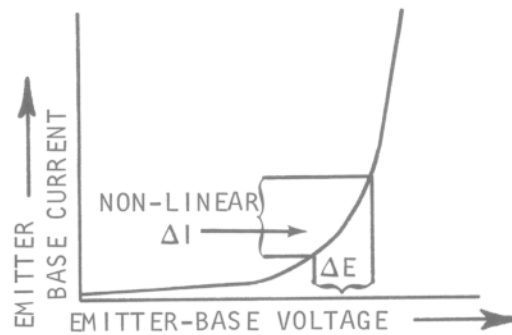17.7 When the applied forward voltage on the emitter-base junction is varied to change the current, the resultant change is non-_____.



no answer needed

17.8 Since driving the emitter-base junction with voltage results in a non-linear result, it is common to find transistors driven with _____ sources.

linear

17.9 Driving the transistors emitter-base junction with a high impedance source is essentially _____ drive.

(current, voltage)

current

17.10 Current driving the emitter base junction allows linear changes to be accomplished. This requires a impedance input generator.
(high, low)

current

17.11** The emitter base junction is typically driven to give
(voltage, current)
the most linear change in the transistor currents.

high

17.12 END OF SET

current

18 Carriers are injected from the emitter into the base when the emitter-base junction is forward biased. The collector junction is _____ biased and depends on the injected carriers in the base for current. A change in emitter or base current will be accompanied by a change in collector current. For a given change in emitter and base current, varying _____ current will have the largest effect on collector current.

18.1 The emitter-base junction is normally forward biased. Since the base is doped much lighter than the emitter, only a few of the injected carriers find imperfections and recombine. The remaining carriers diffuse in the base as _____ carriers.

reverse
base

18.2 The collector junction is reverse biased and depends on minority carriers for current. There are a few minority carriers present in the base at room temperature due to heat energy, but most minority carriers in the base have been injected from the _____.

minority

18.3 The number of minority carriers present in the base can be changed by varying either emitter or base current. Varying the number of _____ carriers in the base will vary collector current.

emitter

18.4 Consider that the base is doped with only one tenth as many imperfections as the emitter. Ten units of current flowing in the emitter will inject ten units of current into the base; one unit recombines in the base and the remaining nine units will _____ to the collector.

minority

18.5 With the base doped one tenth as much as the emitter, increasing the emitter current by ten units of current will increase the base current by one unit and the collector current by _____ units.

diffuse

18.6 If a ten unit change in the emitter current results in a nine unit change in collector current, the a-c signal current gain, emitter to collector, is less than _____.

nine

18.7 Increasing the base current (of the same transistor as frame 18.6) by one unit of current causes an increase of ten units to be injected into the base from the emitter. One unit recombines in the base while the other nine add to _____ current.

one, unity

18.8 The a-c signal current gain, base to collector, of the transistor in frame 18.7 is _____.

collector

18.9 The current gain, emitter to collector, will always be _____ (greater, less) than one, while the current gain, base to collector, can be _____ (greater, less) than one.

nine

18.10** A change in _____ or _____ current will be accompanied by a change in collector current. For the same amount of variance, a change in _____ current will be accompanied by the largest change in collector current.

less
greater

18.11 END OF SET

emitter
base
base

19 With the collector-base junction reverse biased, there will be some collector current flow (I_{CBO}) without the emitter injecting carriers into the base. This current is made up of _____ and, for a given bias, will vary with a change in _____.

19.1 At room temperature, there are some holes in the N material and some free electrons in the P material as a result of heat energy forming hole-electron pairs. These are _____ carriers.

minority carriers

temperature

19.2 The emitter-base junction is forward biased (in the majority of applications) to the majority carriers and this opposes the movement of _____ carriers across the emitter-base junction.


minority

19.3 The collector-base junction is reversed biased (in most applications) to the majority carriers and enhances the movement of _____ carriers across the collector junction.

minority

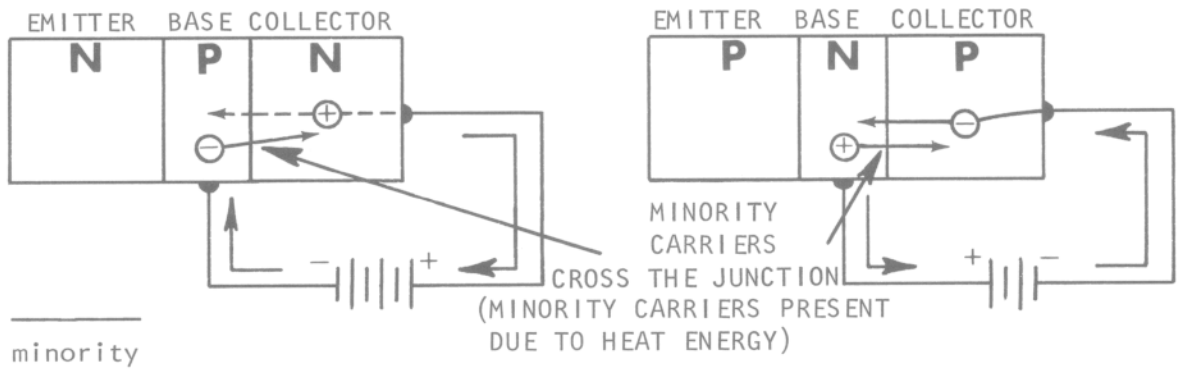
19.4

There will be some current in the collector circuit when it is reverse biased (even if the emitter is open), because of the minority carriers present due to _____.



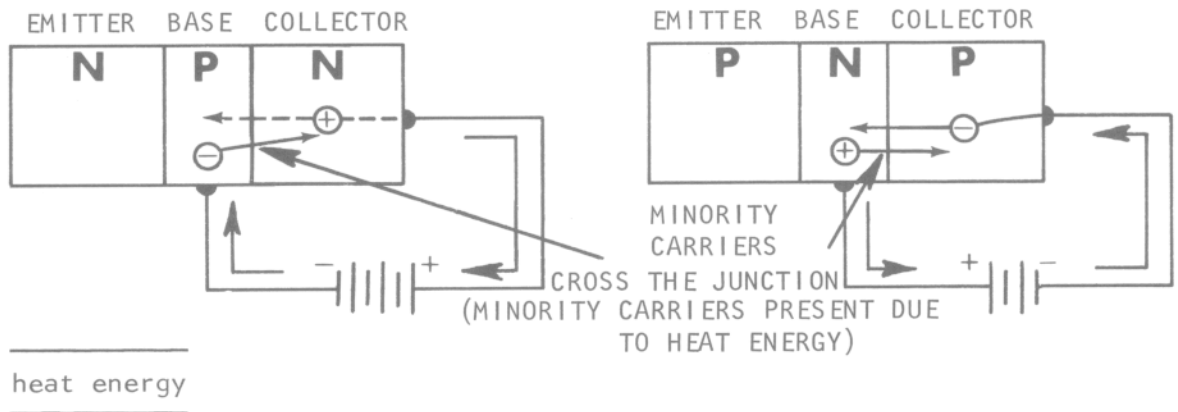
19.5

The current in the diagram is temperature dependent as a change in temperature changes the number of _____ carriers available.



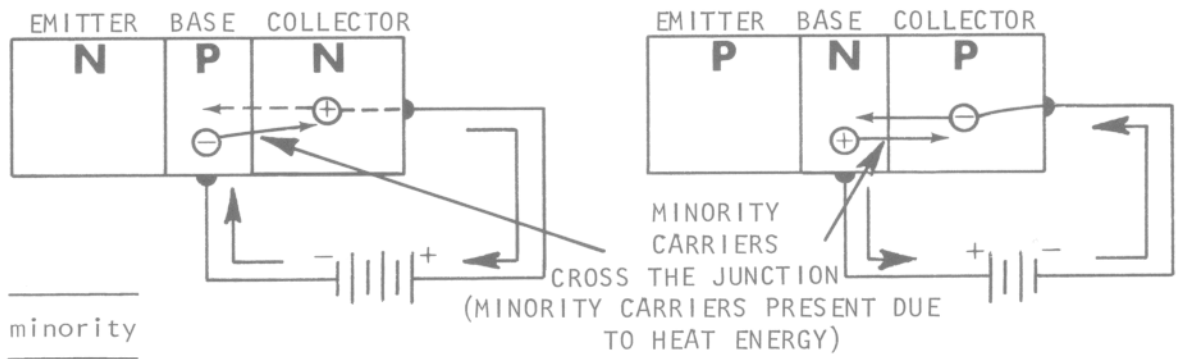19.6

The current in the diagram is given the symbol I_{CB0} indicating d-c current between collector and base with the emitter open. I_{CB0} is the result of "hole - _____".



19.7 In the symbol I_{CB0} , the capital I indicates d-c current, the subscripts CB indicate that the current is between collector and base, and the subscript 0 indicates that the remaining element, the _____, is open circuited.

electron pairs

19.8 I_{CB0} is the current at the collector junction carried by _____ carriers present as a result of thermal energy. I_{CB0} will flow with the emitter lead _____ circuited.

emitter

19.9** There is current in the collector junction when it is reverse biased, even if the _____ lead is open circuited. This current is given the symbol _____. A change in temperature will change the magnitude of _____.

minority
open

19.10 END OF SET

emitter

I_{CB0}
 I_{CB0}

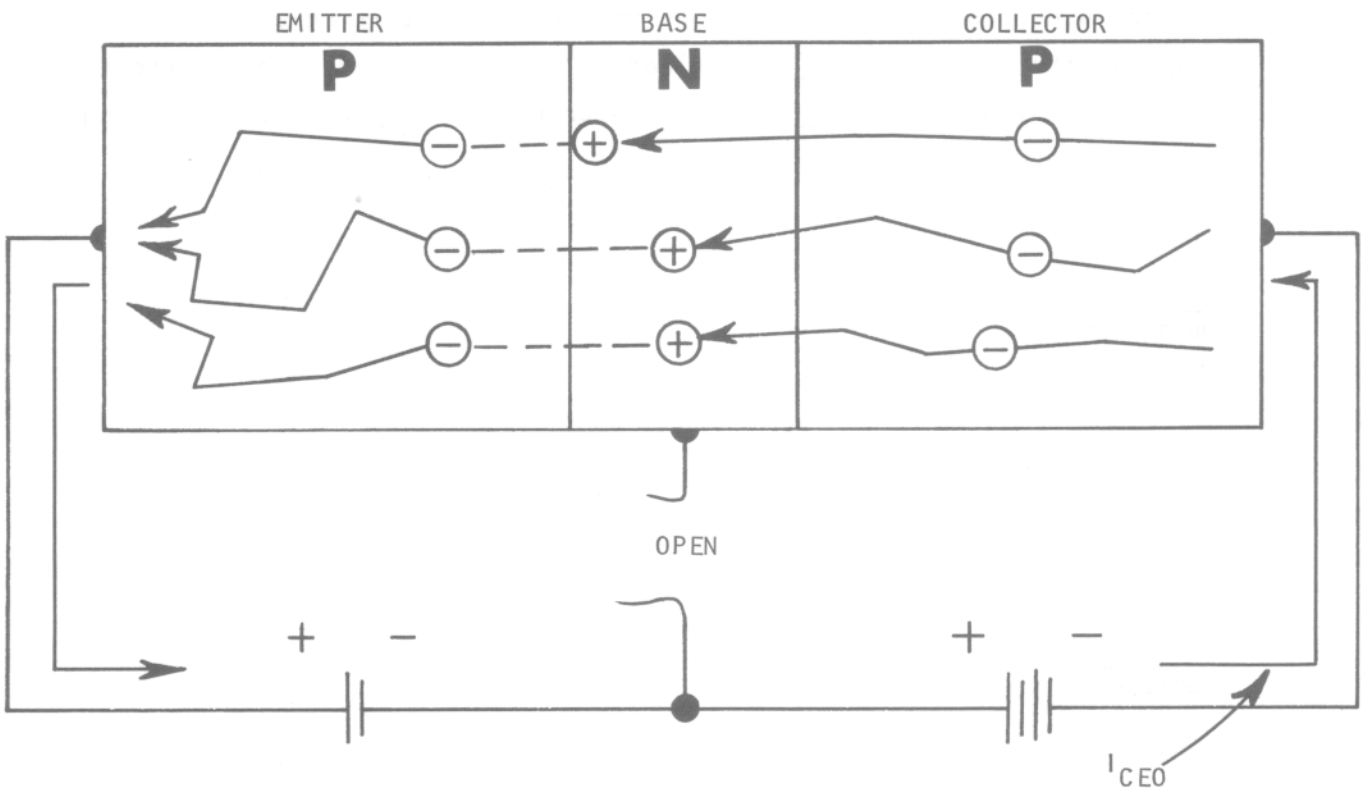
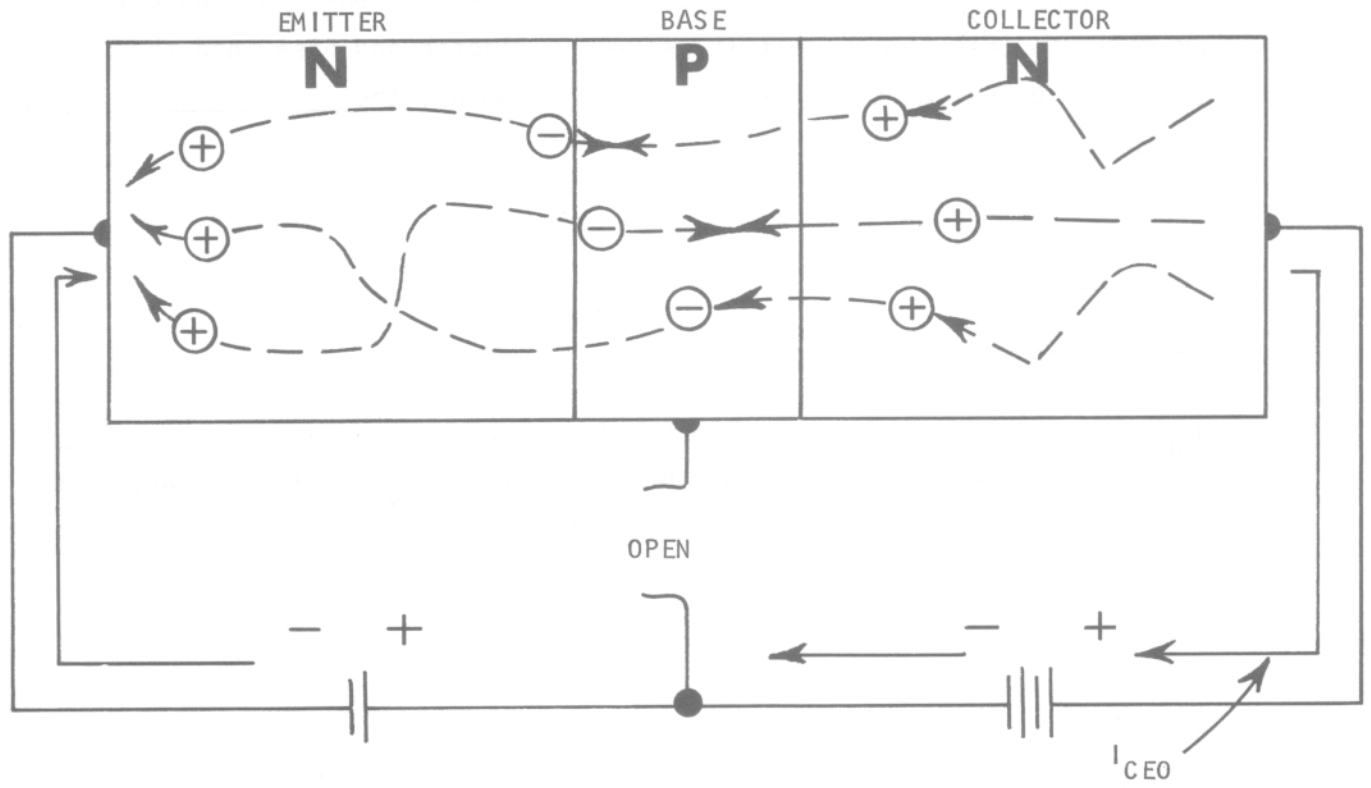


FIGURE 20

20 With bias voltages applied, there is some collector current with the base lead open circuited. This current is made up of minority carriers and is given the symbol _____. It is approximately equal to _____
 $\times I_{CBO}$.

20.1 Figure 20 shows both an NPN and a PNP transistor with bias supplies, but with the base lead open circuited. The current is made up of _____ carriers.

$$\frac{I_{CEO}}{h_{FE}}$$

20.2 Opening the base lead as shown in figure 20 results in minority carriers crossing both junctions. With the base doped much lighter than the emitter, many minority carriers are injected into the base from the emitter with the condition in figure 20.

_____ minority _____

20.3 I_{CBO} is limited by the carriers present due to heat energy. With the condition in figure 20, the number of minority carriers in the base is increased by approximately d-c beta or _____ (symbol).

_____ no answer needed _____

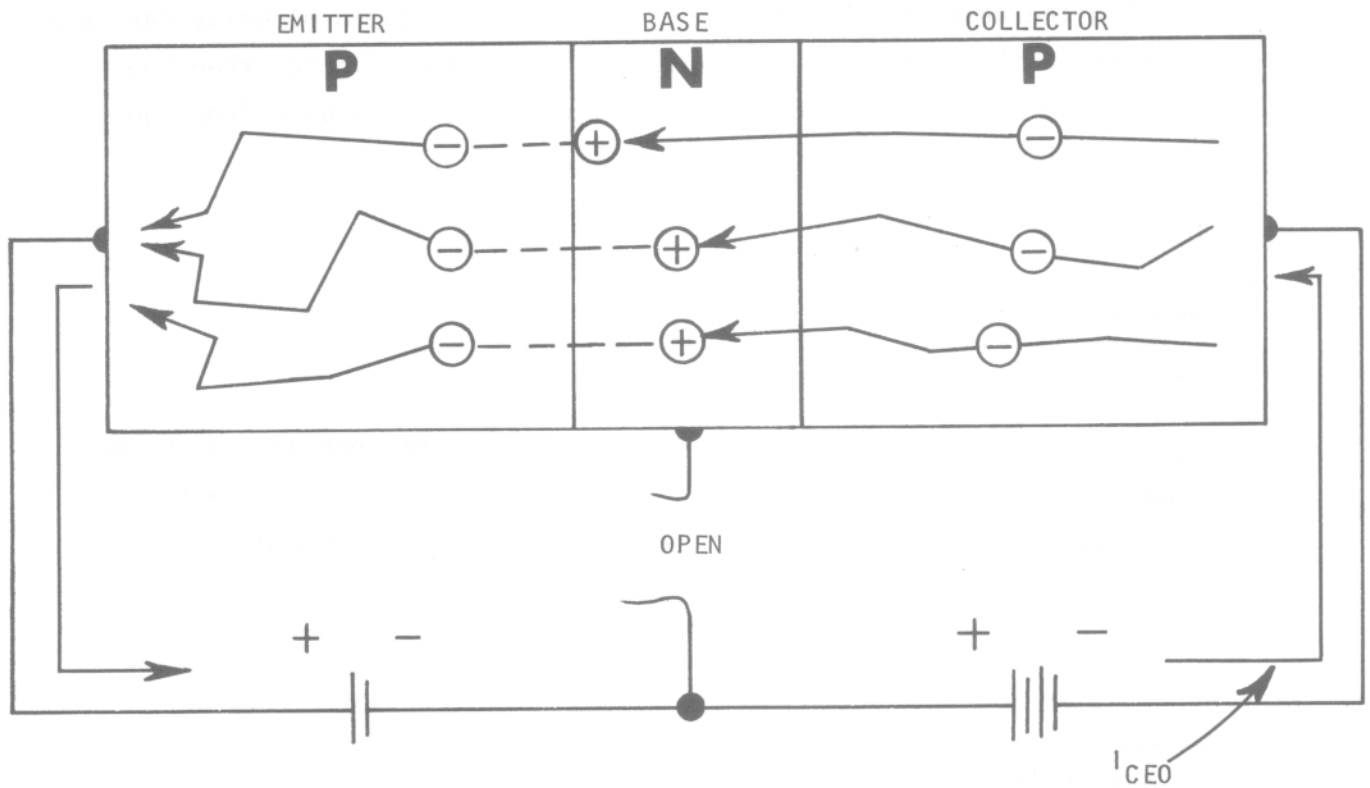
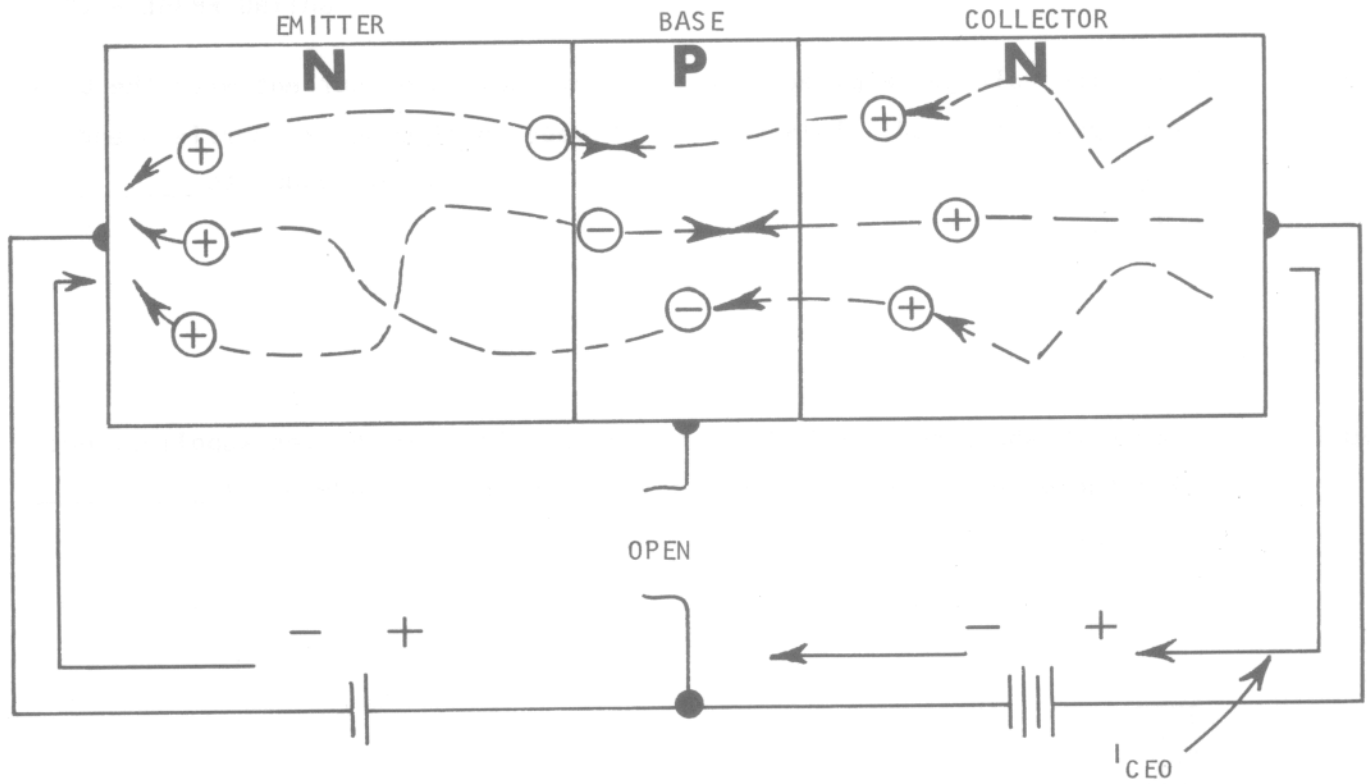


FIGURE 20

20.4 The minority carriers in the base are increased by approximately the d-c current gain of the transistor when the condition in figure 20 exists. There will be more _____ carriers available in the base than for the I_{CBO} condition.

 h_{FE}

20.5 The current in figure 20 is between collector and emitter with the base lead open. It is given the symbol I_{CEO} . I_{CEO} will be _____ than I_{CBO} .
(larger, smaller)

minority

20.6 The current termed I_{CBO} is magnified by $\approx h_{FE}$ with the conditions in figure 20. $I_{CBO} \times h_{FE} \approx$ _____.

larger

20.7** I_{CEO} indicates d-c current between _____ and _____ with the base lead open circuited. It is approximately equal to the product of I_{CBO} and _____.



 I_{CEO}

20.8

END OF SET

collector
emitter
 h_{FE}


21

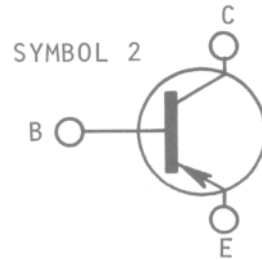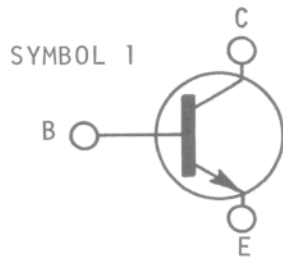

Symbol 1 is for a/an _____ transistor, and symbol 2 is for a/an _____ transistor. E indicates the _____.

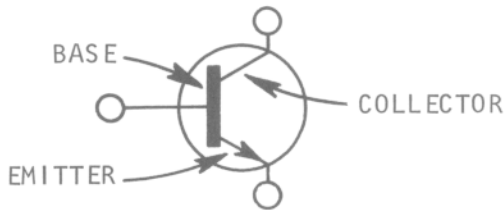21.1

The solid vertical line in the transistor symbol indicates the base. The line (without the arrow head) intersecting the base at an angle indicates the _____.



NPN
PNP
emitter


21.2

The line containing an arrow head that intersects the base at an angle indicates the _____.




collector

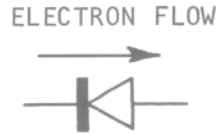21.3 In an NPN transistor, the carriers are electrons injected from the emitter into the base. In the diode symbol, electrons flow _____ the symbol arrow point as shown in the diagram.
 (out of, into)




_____ emitter _____

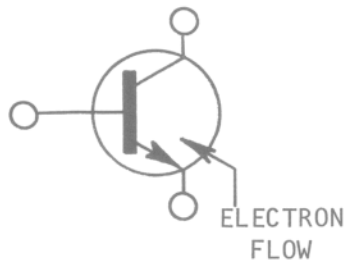21.4 The emitter-base of a transistor is a PN junction and in the symbol electrons will flow _____ the tip of the arrow.
 (into, out of)




_____ into _____

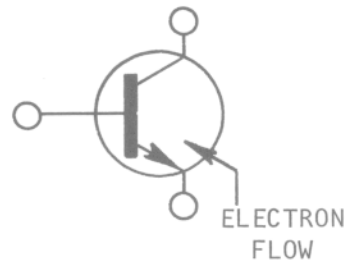21.5 The symbol shown has electrons flowing into the tip of the arrow. The arrow indicates that electrons are flowing from the emitter into the _____.




_____ into _____

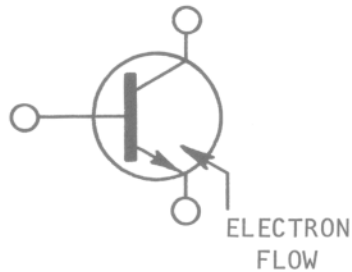21.6 An NPN transistor has the emitter injecting electrons into the base. The symbol shown must be a/an _____ transistor.





base

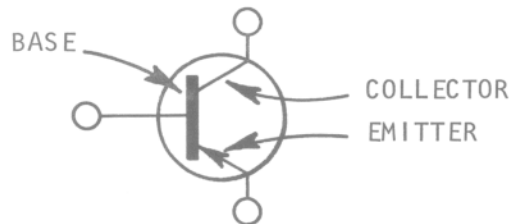21.7 The emitter of a PNP transistor injects holes into the base. Holes move in the direction that the arrow is pointing in a diode symbol. The transistor shown must be a/an _____ transistor.




NPN

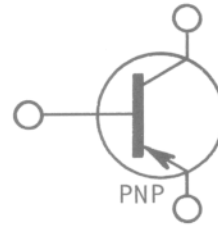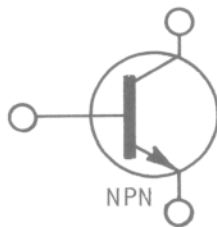21.8 PNP transistors have the emitter arrow pointing _____ the base and NPN transistors have their emitter arrow pointing _____ the base.



PNP

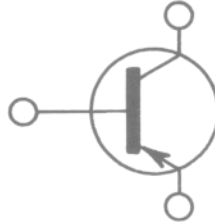21.9** The symbol shown is a/an _____ transistor. If the emitter arrow were pointing the other way, it would be the symbol for a/an _____ transistor. The part of the symbol containing the arrowhead indicates the _____.




toward
away from

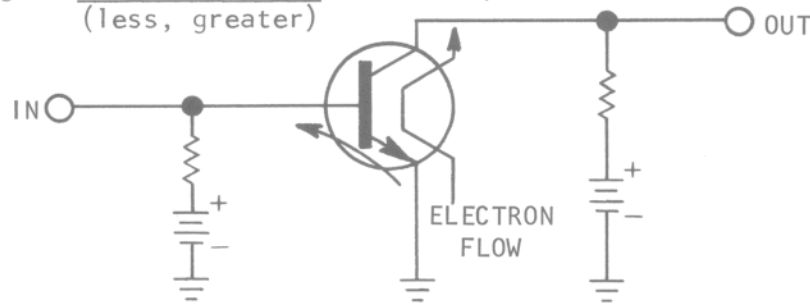
21.10 END OF SET

PNP
NPN
emitter

22 The transistor in the diagram is a/an _____ type and is in a common _____ configuration. A transistor in this configuration will give current gain _____ than unity.
(less, greater)



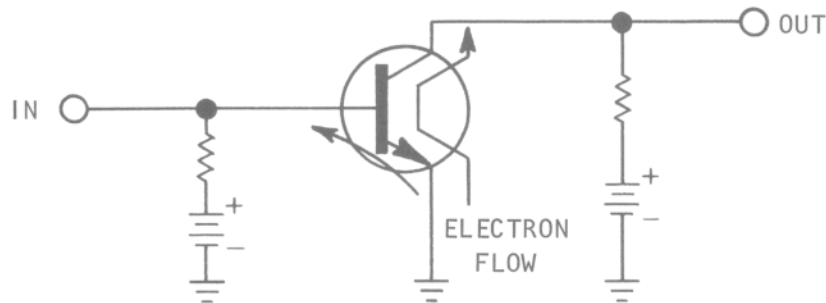22.1 The transistor in the diagram has the arrow indicating the emitter pointing away from the base. Electrons flow _____ the arrow in the symbol.
(with, against)




NPN
emitter
greater

22.2 Electrons are injected into the base from the emitter in an NPN transistor. The diagram shown is a/an _____ transistor.




against

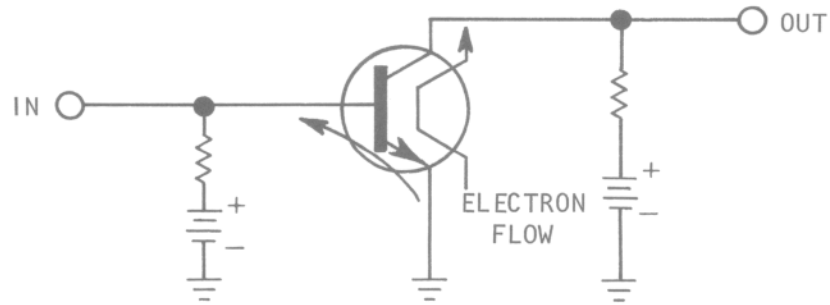22.3 Grounding the emitter makes it common to both the input and output circuits. The transistor in the diagram has its emitter _____ to both the input and output circuits.



PNP

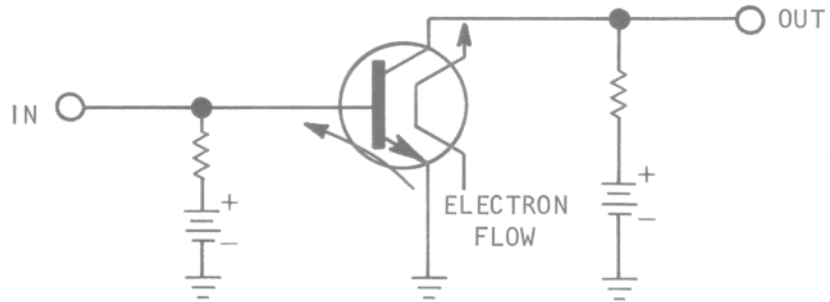22.4 The grounded or common emitter circuit has the transistors' _____ as its input point, and the transistors' _____ as its output point.



common


22.5 A small change in input (base) current in the common emitter circuit will be accompanied by a _____ change in output (collector) current.
(larger, smaller)

base
collector

22.6 It is possible for the common emitter configuration to give a current gain greater than unity. The output (collector) current change can be larger than the change in the _____ current.

larger

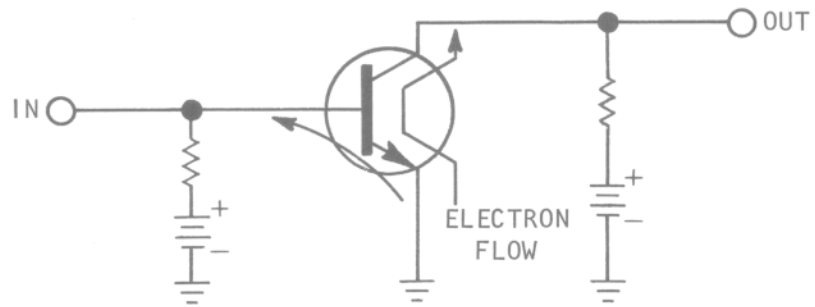22.7** The transistor in the diagram is an NPN type. The emitter injects _____ into the base. The current gain of this common _____ configuration can be greater than unity.



input (base)

22.8 END OF SET


electrons
emitter

23 Voltage gain along with current gain can be accomplished with the common _____ configuration making possible a high power gain.

23.1 The common emitter configuration allows a current gain greater than unity. The signal current in the output can be _____ than the signal current in the input.

_____ emitter _____

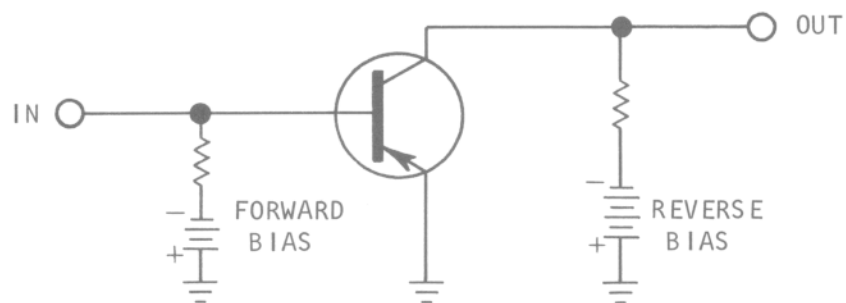
23.2 The emitter junction is forward biased while the collector junction is _____ biased in most amplifier configurations.



_____ greater, larger, etc. _____

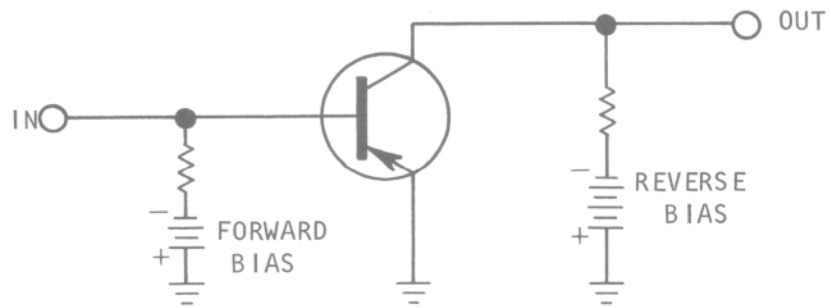23.3


Forward bias is necessary at the emitter junction for carrier injection into the base. The emitter junction has a low impedance because it is _____ biased.



reverse

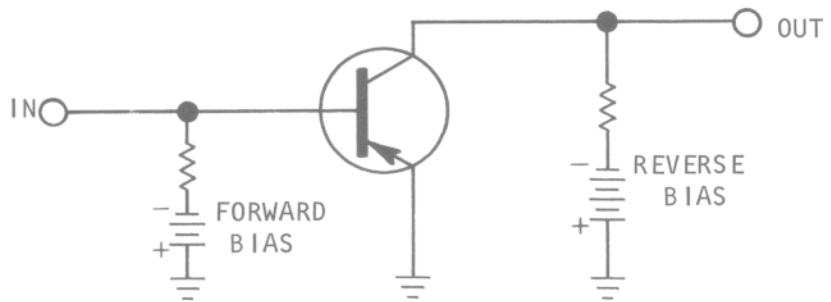23.4


The collector junction offers a higher impedance than the emitter junction because the collector junction is _____ biased.



forward

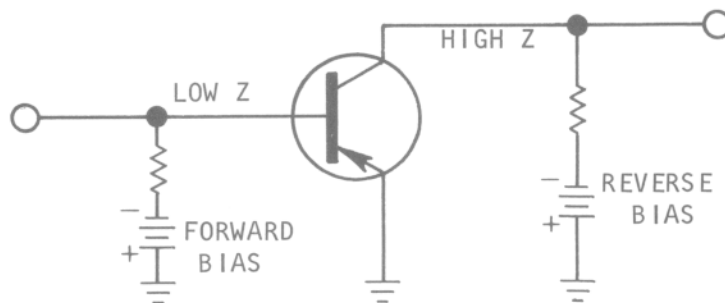23.5

By ohms law, a current through a high impedance will develop a larger voltage than the same current through a low impedance. There is a higher impedance at the _____ junction than at the _____ junction.



reverse

23.6 Voltage gain is possible with the common emitter configuration. Since the _____ is a higher impedance circuit, the current in the collector circuit develops a larger voltage than at the base.

collector
emitter

23.7 A small voltage change applied to the base to emitter circuit of a common emitter configuration can cause a larger voltage change at the _____.

collector

23.8 The common emitter configuration offers a high power gain because both current and _____ gain are possible.

collector

23.9** The common emitter configuration offers both _____ and _____ gain, making possible a large power gain.

voltage

23.10 END OF SET

current
voltage

24 The small signal, a-c current gain of the transistor in a common emitter configuration is given the symbol _____. This parameter _____ include circuit effects on current gain.
(does, does not)

24.1 Small signal indicates that the transistor will operate only over a small portion of its possible operating range. Forcing a transistor to operate to the extremes of its operating range of currents and voltages _____ considered small signal.
(is, is not)

_____ h_{fe} _____
does not

24.2 Small signal characteristics are expressed by small or incremental changes. The small signal current gain indicates the amount that a/an _____ current change will be amplified.

_____ is not _____

24.3 The common emitter configuration has the _____ as its input and the collector as its output with the _____ common to both.

_____ small, incremental _____

24.4 A change in the base current of a common emitter configuration will be accompanied by a larger current change in the _____ circuit.

base
emitter

24.5 Varying the voltage on the collector junction will also cause a change in collector current. The effect of a collector voltage change on collector current will be much smaller than the effect of a/an _____ current change on collector current.

collector

24.6 In order to gain an accurate measurement of the control of input current on the output current, the output _____ must be held constant.

input (base)

24.7 The current gain of the transistor in a common emitter configuration can be measured by varying the input current, noting the change in output current while holding output _____ constant.

voltage

24.8 The symbol h_{fe} indicates the small signal, a-c current gain of the transistor in a common _____ configuration.

_____ voltage _____

24.9 The transistor current gain parameter, h_{fe} is referred to as small signal "beta". The small signal current gain from base to collector is called _____.

_____ emitter _____

24.10 h_{fe} may be calculated by dividing the change in collector current by the applied change in base current while holding collector voltage constant.

$$h_{fe} = \frac{\Delta I_c}{\Delta I_b} \bigg|_{\Delta V_{ce} = 0}$$

Δ = Incremental change

I_c = Collector current

I_b = Base current

V_{ce} = Voltage _____ to emitter

_____ beta _____

24.11 h_{fe} is the current gain of the transistor only when placed in a common emitter configuration. The effects of the _____ will also have to be taken into account when calculating total circuit current gain.

collector

24.12

$$h_{fe} = \frac{\Delta I_c}{\Delta I_b} \bigg|_{\Delta V_{ce} = 0}$$

The current gain parameter h_{fe} _____ take into account losses encountered in the circuit.

circuit

24.13** The symbol h_{fe} indicates a transistor current gain parameter. It _____ be used with a transistor in a common base configuration.
(would, would not)
It _____ take into account the effects of the circuit on current gain.
(does, does not)


does not

24.14 END OF SET

would not
does not


25 A transistor in a common base configuration will give a current gain _____ . The small signal, a-c current gain of the transistor in a common base configuration is given the symbol _____. This parameter _____ take into account (does, does not) the effects of the circuit on current gain.

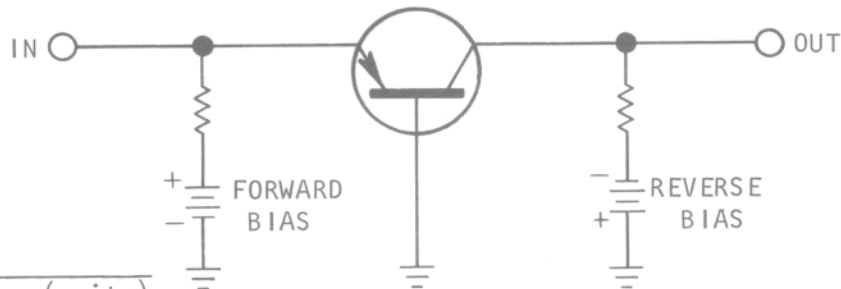25.1 The common base configuration has the emitter as the input, the collector as the output, and the _____ common to both.




less than one (unity)
 h_{fb}
 does not

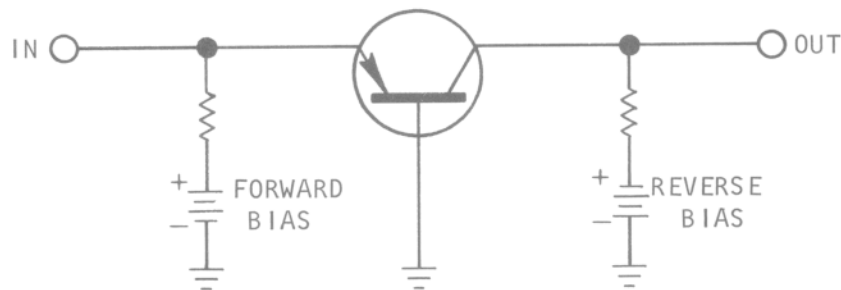25.2 Comparing the common base to the common emitter, the emitter junction is _____ biased in both and the collector junction is _____ biased in both. Only the configuration or orientation of the transistor is different.



base

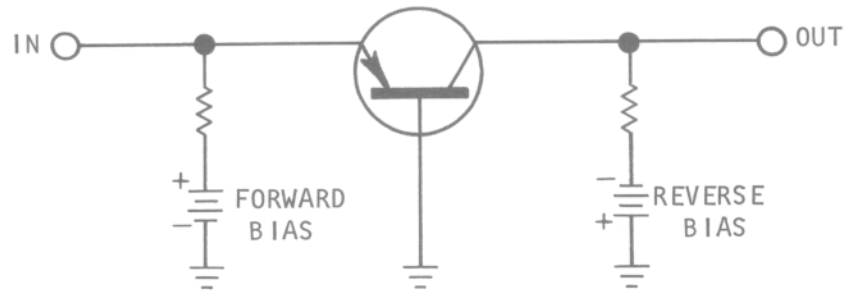25.3 A change in the emitter (input) current in the circuit in the diagram will result in a _____ change in the collector (output) circuit.
 (larger, smaller)



forward
reverse

25.4 The output current will always be smaller than the input current in a common _____ configuration.

smaller

25.5 The current gain of the common base configuration can be said to be less than one (unity), since the output current will be _____ than the input current.

base

25.6 A change in the emitter current will be accompanied by a change in the collector current. A change in the voltage on the collector junction will also result in a change in _____ current.

less, smaller, etc.

25.7 To make an accurate measurement of the relation of a varying emitter current to collector current, the collector _____ must be held constant.

collector

25.8 The small signal, a-c current gain of the transistor in a common base configuration is referred to as small signal "alpha" and given the symbol h_{fb} . This parameter _____ take into account the effects of the circuit on current gain.
(does, does not)

voltage

25.9 h_{fb} can be calculated by dividing the output current by the input current while holding the output _____ constant.

$$h_{fb} = \frac{\Delta I_c}{\Delta I_e} \bigg|_{\Delta V_{cb} = 0}$$

Δ = Incremental change
 I_c = Collector current (output)
 I_e = Emitter current (input)
 V_{cb} = Voltage collector to base (output)

does not

25.10** The small signal current gain of the transistor in a common base configuration is given the symbol _____. This current gain parameter _____ be used for a transistor in a common emitter configuration. The effects of the circuit _____ taken into account by this parameter. (would, would not) (are, are not)

_____ voltage _____

25.11 END OF SET

_____ h_{fb} _____
would not
are not

- 26 Since the collector junction is a _____ impedance circuit and the emitter junction is a _____ impedance circuit, voltage gain can be accomplished with the common base configuration and a corresponding _____ gain.
- 26.1 Common base current gain is less than unity. The current in the collector (output) circuit will be _____ than the current in the emitter (input) circuit.
- _____
- high
low
power
- 26.2 Reverse biasing the collector results in a high impedance collector circuit with respect to the low impedance, _____ biased emitter circuit.
- _____
- less
- 26.3 The product of collector impedance and collector current can be greater than the product of emitter current and emitter impedance. This indicates that voltage gain is possible.
- _____
- forward

26.4 Although current gain is less than unity in the common base configuration, voltage gain greater than unity is possible and a corresponding _____ gain may be realized.

_____ no answer needed _____

26.5 The product of current gain (less than unity) and voltage gain (greater than unity) will give the _____ gain.

_____ power _____


26.6** Power gain is possible with the common base configuration although the current gain is _____ since there is the possibility of _____ gain.

_____ power _____

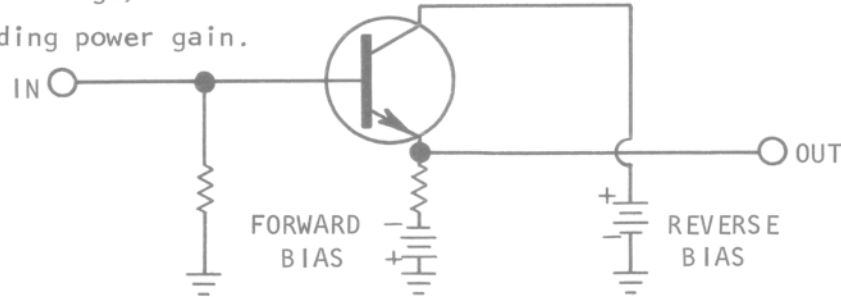
26.7 END OF SET

_____ less than unity
voltage _____

- 27 The transistor shown is in a common _____ configuration. _____ gain is possible with this configuration with a _____ (Current, Voltage) corresponding power gain.




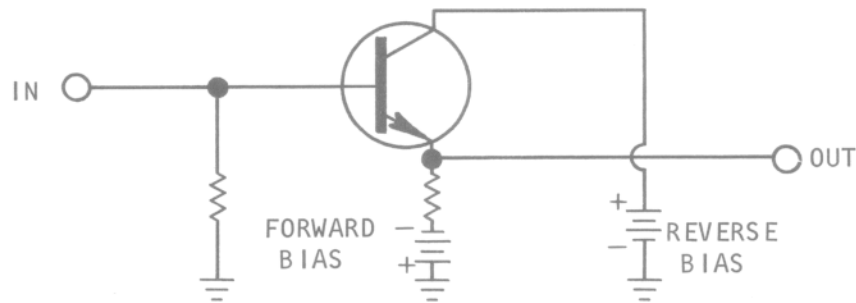- 27.1 The _____ serves as the input, the _____ serves as the output, and the _____ is common to both in this configuration.




collector
Current

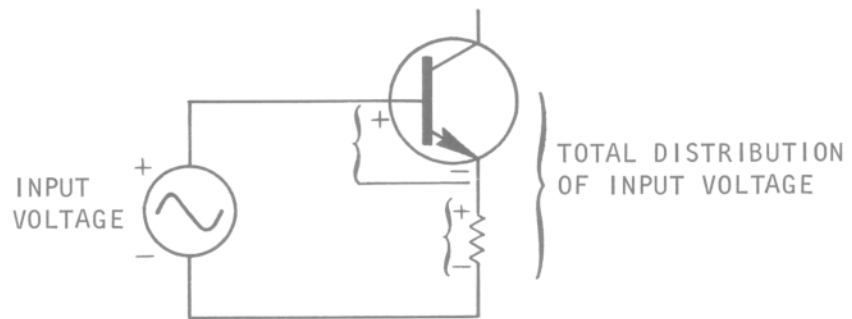- 27.2 The input signal voltage is applied at the base and will be distributed across the emitter-base junction and the resistance in the emitter circuit.



base
emitter
collector

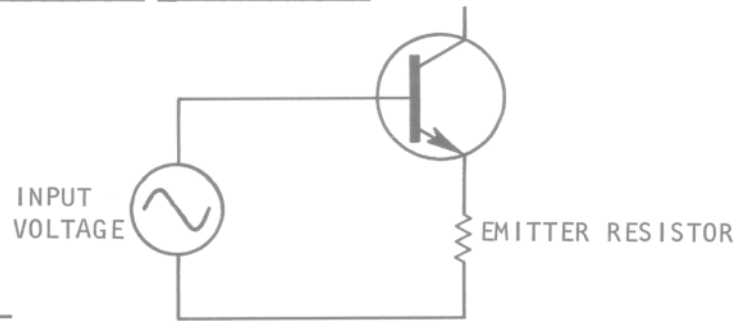27.3 If the emitter resistor has a high resistance with respect to the resistance of the emitter-base junction, most of the input voltage will be across the _____.



no answer needed

27.4 Since the voltage across the emitter resistor is only part of the input voltage, the voltage across the emitter resistor will always be less than the input voltage.

emitter resistor

27.5 Signal voltage at the emitter can never be equal to or larger than the applied signal voltage at the _____ terminal of a transistor in the common collector configuration.

no answer needed

27.6 The emitter is the output point and the base is the input point. Since the emitter signal voltage can never equal the base signal voltage, the voltage gain is less than _____.

base

27.7 The emitter current is the sum of base and collector current. The _____ handles the greatest amount of current in the transistor.

one, unity


27.8 The current gain of a transistor in a common collector configuration is greater than unity. The current in the emitter is greater than the current in the _____.

emitter

27.9 The voltage gain of a common collector configuration is less than unity. Power gain is possible, however, as this configuration yields _____ gain.

base (input)

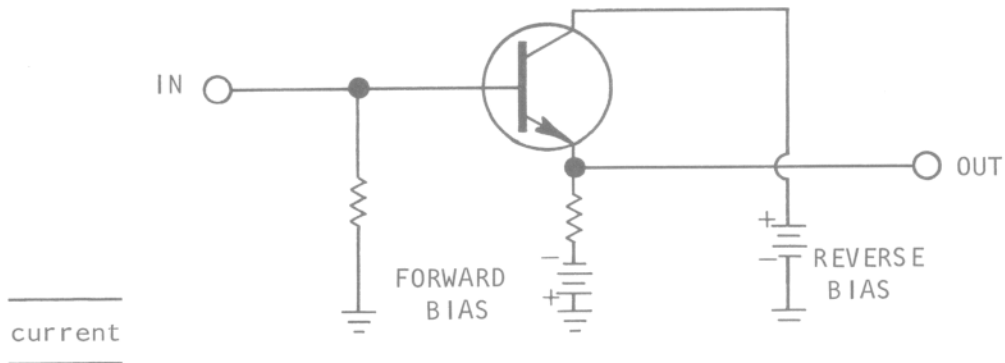27.10 Since the emitter current is equal to collector current plus base current of the transistor in the diagram, its current gain can be greater than _____.



27.11 The common collector configuration has the largest potential current gain of the three transistor configurations, since the input is at the lowest current point on the transistor while the output is taken from the _____ current point.

_____ one, unity

27.12** The common collector configuration can yield power gain even though its voltage gain is less than unity, since _____ gain is possible.


_____ highest, largest, etc.

27.13 END OF SET


—
current
—

28 The common collector configuration is also referred to as an emitter _____ since the emitter will _____ the base.

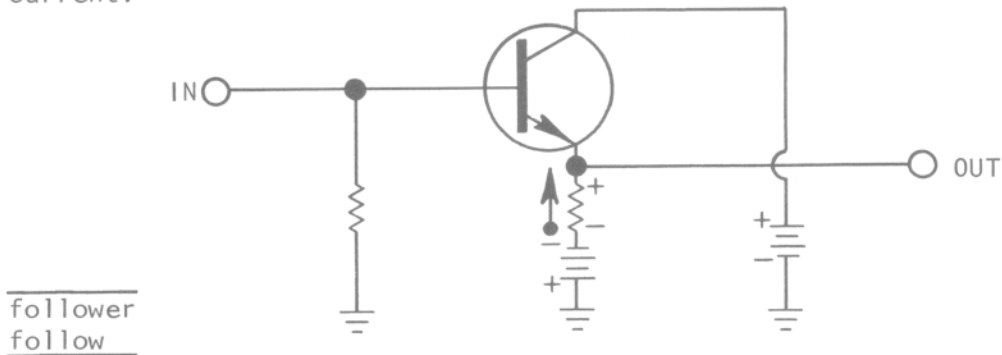
28.1 An increase in base current will be accompanied by an increase in collector and emitter currents. In the transistor shown, an increase in input current will be accompanied by an _____ in the output current.



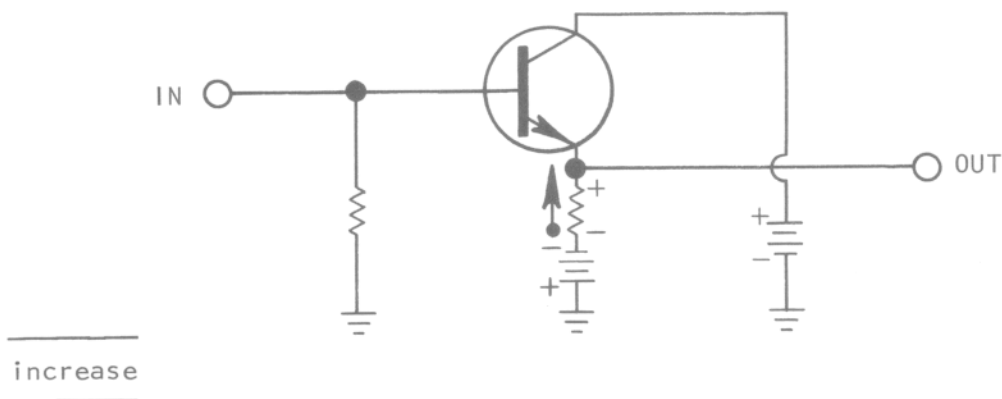28.2 A positive voltage change on the base will be accompanied by an increase in base current and an increase in collector and _____ current.



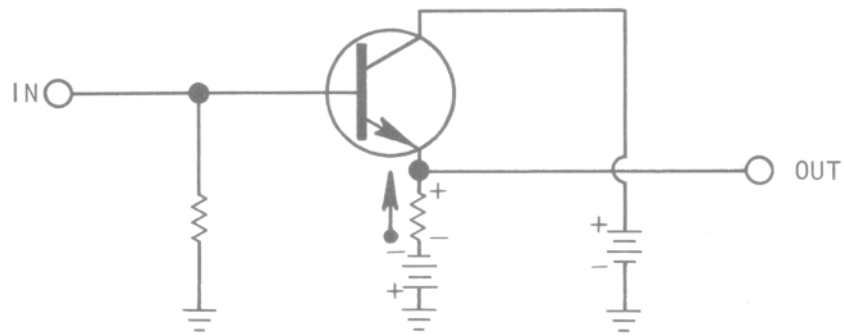28.3 A positive voltage change on the base will cause an increase in emitter current and a positive _____ change at the emitter.



emitter

28.4 The voltage and current changes at the emitter will follow the changes at the base. The _____ follows the _____.

voltage

28.5 The voltage changes at the emitter of an emitter follower configuration can never be larger than the voltage changes at the base. The current changes at the emitter, however, can be much larger than the current changes at the _____.

emitter

base

28.6** The emitter changes follow the base changes in the common collector configuration. This configuration is commonly referred to as an _____
_____.

base (input)

28.7 END OF SET

emitter follower

29 The small signal, low frequency current gain parameter for the transistor in a common collector configuration is given the symbol _____. It is equal to $h_{fe} +$ _____.

29.1 A change in base current in an emitter follower will give a collector current change equal to $h_{fe} \times \Delta I_B$. The change in emitter current is equal to the sum of the collector current change and the _____ current change.

$$\frac{h_{fc}}{1}$$

29.2

$$\Delta I_E = \Delta I_C + \Delta I_B$$

$$\Delta I_C = h_{fe} \Delta I_B$$

$$\Delta I_E = h_{fe} \Delta I_B + \Delta I_B$$

$$\Delta I_E = (h_{fe} + 1) \Delta I_B$$

$$\Delta I_E = h_{fc} \Delta I_B$$

h_{fc} is the same as _____

 base

29.3 Since h_{fc} is the same as $h_{fe} + 1$, the potential current gain is greatest for the common _____ configuration.

$$\frac{h_{fe} + 1}{}$$

29.4** Emitter follower small signal current gain parameter is given the symbol _____. It has the same value as _____.

_____ collector

29.5 END OF SET

$$\frac{h_{fc}}{h_{fe} + 1}$$

30 The common collector configuration offers a high _____ resistance and a low _____ resistance.

30.1 The output from the common collector (emitter follower) configuration is taken at the emitter. The emitter is a _____ current point with respect to the other transistor terminals.

input

output

30.2 The input to an emitter follower is applied at the base, a _____ current point with respect to the other transistor terminals.

high

30.3 Since the emitter follows the base, some of the input voltage change is, in effect, cancelled due to the emitter moving in a/the _____ polarity direction as/than the base.

low

30.4 In comparing the common collector to the common emitter configuration, it will take a greater voltage change at the base to cause the same current change in the common collector configuration.

same

30.5 The requirement of a larger voltage change to cause the same current change indicates the input resistance is greater in the emitter follower than in the common emitter configuration.

no answer needed

30.6 The output point of the emitter follower has nearly the same voltage change as at the input, but a much larger current change. This indicates a much lower resistance at the output than the input.

greater

30.7** The emitter follower offers a high resistance and a low resistance.

lower

30.8

END OF SET

input
output

31 The emitter follower configuration with its high input resistance and low output resistance finds use in applications requiring high output _____ to drive capacitance.

31.1 The emitter follower input resistance is made large by the negative feedback (emitter following the base) from the emitter. The base is a high resistance, _____ current point.
(high, low)

current

31.2 The emitter has a low resistance and is a _____ current point.
(high, low)
Taking the output at the emitter allows high output currents, with respect to other points in the emitter follower circuit.

low

31.3 The emitter follower finds much use as an impedance matching circuit that also offers _____ gain greater than unity.
(current, voltage)

high

31.4 Since the emitter follower offers a high output current, it is often used to drive circuits with high input capacitance. The emitter follower can provide current to charge _____ that would load down the output of other configurations.

current

31.5 The emitter follower configuration offers a high input resistance and a low output resistance and is able to drive a larger _____ than most configurations for the same loading.

capacitance



31.6** The _____ configuration is noted for high input resistance and low output resistance and its ability to drive capacitance because it can supply a high output _____.

capacitance

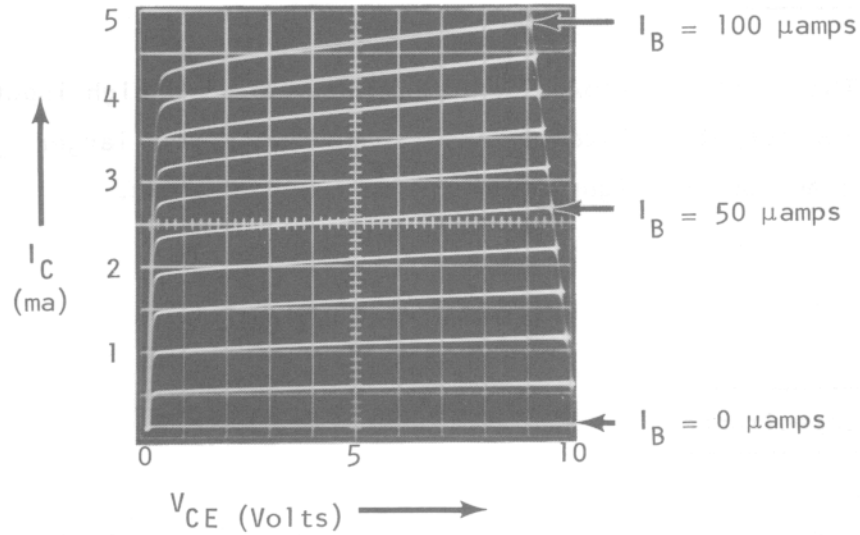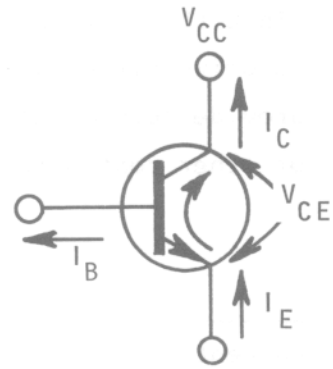
31.7 END OF SET

common collector (emitter follower)
current

V_{CC} = COLLECTOR SUPPLY VOLTAGE
 I_B = d-c BASE CURRENT
 I_C = d-c COLLECTOR CURRENT
 I_E = d-c EMITTER CURRENT
 V_{CE} = d-c VOLTAGE, COLLECTOR TO EMITTER



COLLECTOR FAMILY OF CURVES

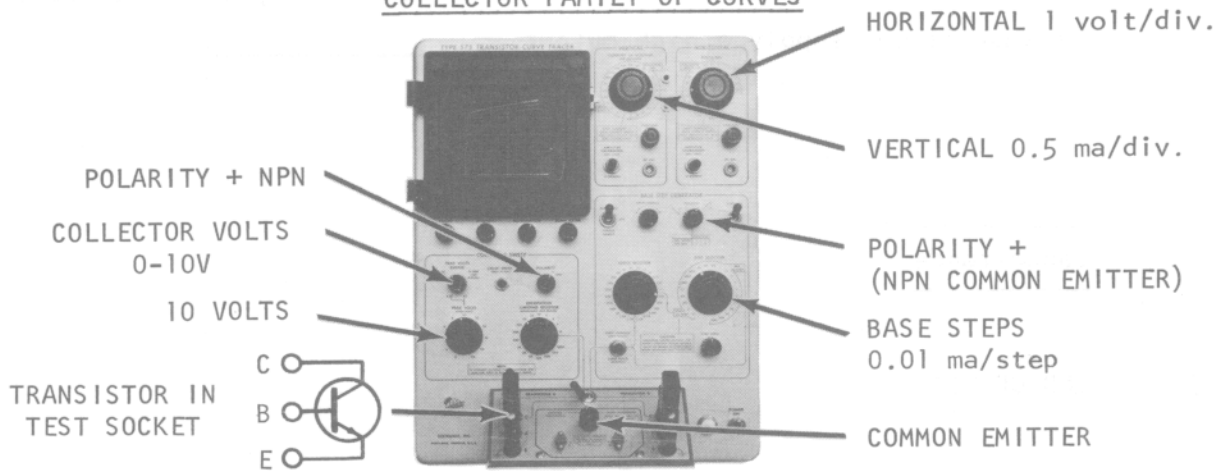

TEST SETUP

TEKTRONIX TYPE 575 TRANSISTOR-CURVE TRACER
 TOP PHOTO TAKEN WITH TYPE C-12 OSCILLOSCOPE CAMERA

FIGURE 32

32 A chart such as the one in figure 32 shows the transistor's characteristics over a range of currents and voltages. The "collector _____ of curves" shown is for the common _____ configuration. Each curve represents a value of _____ current and allows a cross reference of the transistor's currents and voltages.

32.1 The horizontal scale in figure 32 is in units of collector to emitter voltage. _____ current is plotted vertically.

family
emitter
base



32.2 Each individual curve on the chart in figure 32 is for a given value of base current. Another way of stating this is to say that _____ current is the running parameter.

Collector

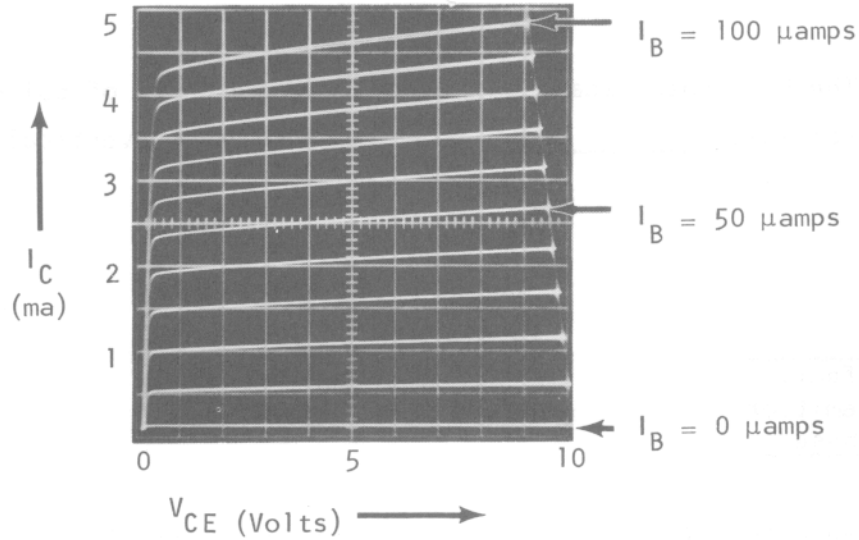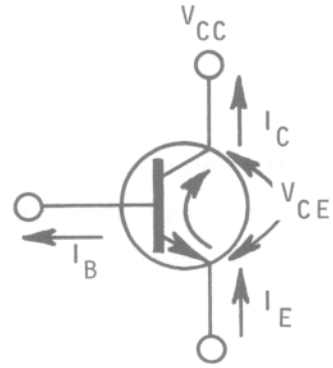
32.3 The chart in figure 32 is called a collector family of curves. The voltages and currents in the collector circuit are shown at several values of _____ current resulting in a group or family of curves.

base

V_{CC} = COLLECTOR SUPPLY VOLTAGE
 I_B = d-c BASE CURRENT
 I_C = d-c COLLECTOR CURRENT
 I_E = d-c EMITTER CURRENT
 V_{CE} = d-c VOLTAGE, COLLECTOR TO EMITTER



COLLECTOR FAMILY OF CURVES

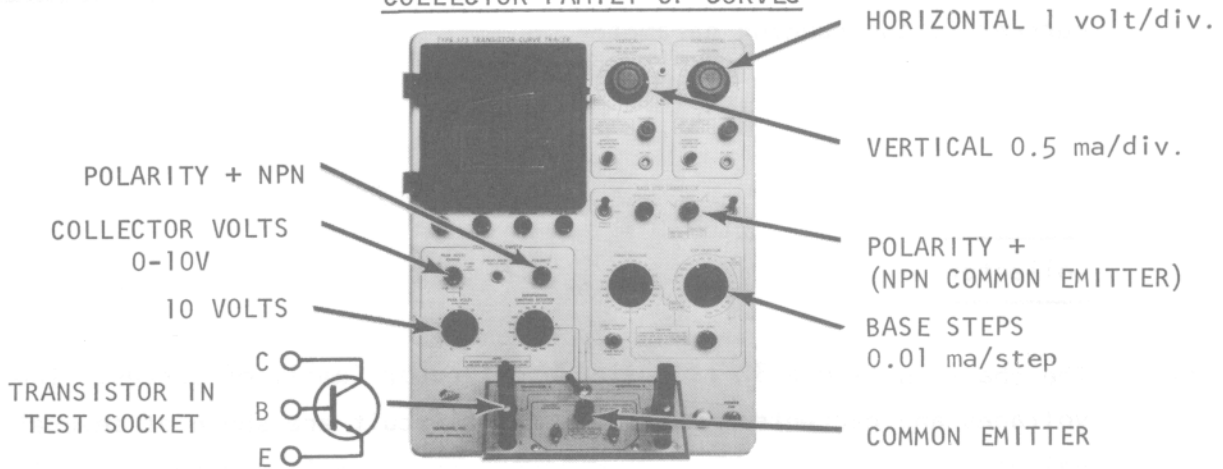

TEST SETUP

TEKTRONIX TYPE 575 TRANSISTOR-CURVE TRACER
 TOP PHOTO TAKEN WITH TYPE C-12 OSCILLOSCOPE CAMERA

FIGURE 32

32.4 A given point on a base current curve gives a cross reference of collector current and collector _____.

_____ base _____

32.5 The base current in the collector family of curves in figure 32 varies between zero and 100 μ amps. The base current curve near the bottom of the chart indicates _____ base current.

_____ voltage _____



32.6 According to the chart in figure 32, for a given value of V_{CE} , an increase in base current results in a/an _____ in collector current.
(increase, decrease)

_____ zero _____


32.7 Each curve in the chart in figure 32 indicates a given value of base current. The slope of the base current curve indicates the effect of _____ voltage on collector current.

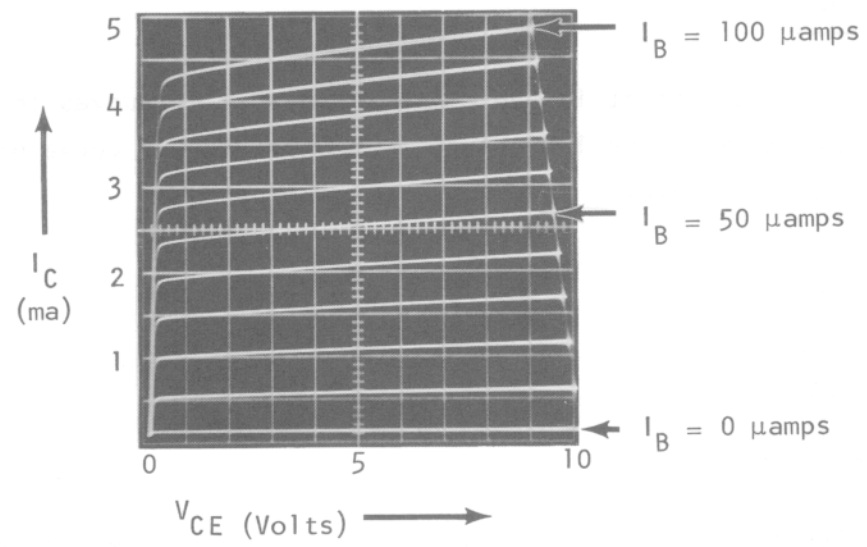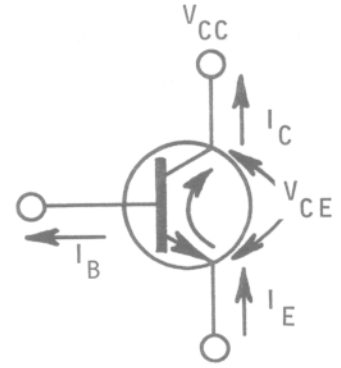_____ increase _____

V_{CC} = COLLECTOR SUPPLY VOLTAGE
 I_B = d-c BASE CURRENT
 I_C = d-c COLLECTOR CURRENT
 I_E = d-c EMITTER CURRENT
 V_{CE} = d-c VOLTAGE, COLLECTOR TO EMITTER



COLLECTOR FAMILY OF CURVES

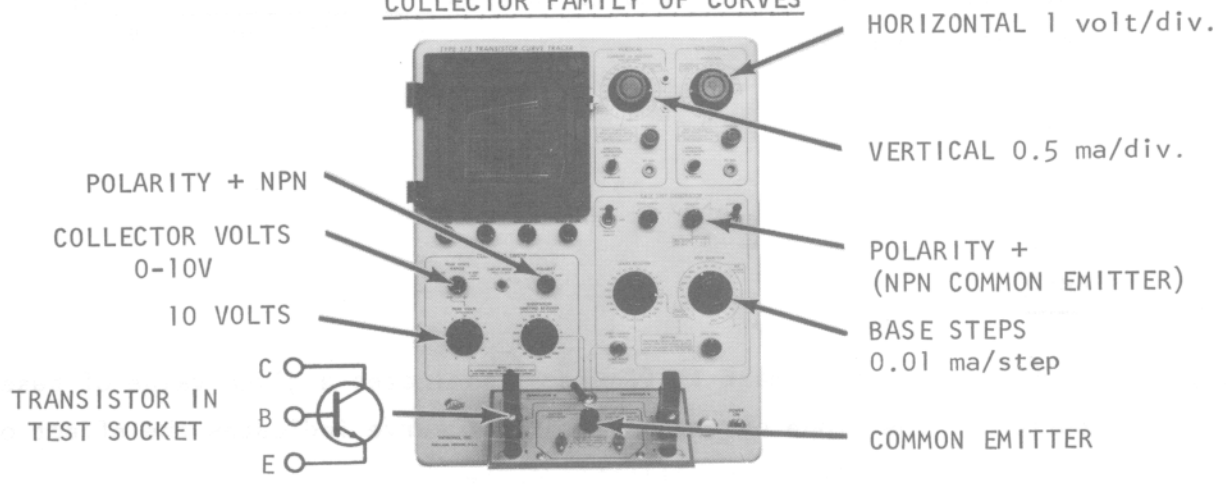

TEST SETUP

TEKTRONIX TYPE 575 TRANSISTOR-CURVE TRACER
 TOP PHOTO TAKEN WITH TYPE C-12 OSCILLOSCOPE CAMERA

FIGURE 32

32.8 An increase in collector voltage causes a/an _____ in collector current for a given value of base current as shown by the curves in figure 32.

collector

32.9 Each curve in the collector family of curves in figure 32 represents a value of base current. When base current (I_B) is 60 μ amps and collector voltage (V_{CE}) is 5 volts, collector current (I_C) is _____ ma.

increase

32.10 Any point along a base current curve gives a cross reference of collector current and voltage. The 30 μ amp base current curve crosses the 1.6ma collector current point at _____ volts of collector voltage.

3

32.11 From the collector family of curves in figure 32, with a collector voltage of 7 volts and a collector current of 3.5ma, there is _____ μ amps of base current.


5

32.12** The collector family of curves for a common emitter configuration is a plot of _____ voltage versus _____ current for different values of _____ current, allowing a cross reference of the transistor's voltages and currents.



—
70
—

32.13 END OF SET

collector
collector
base

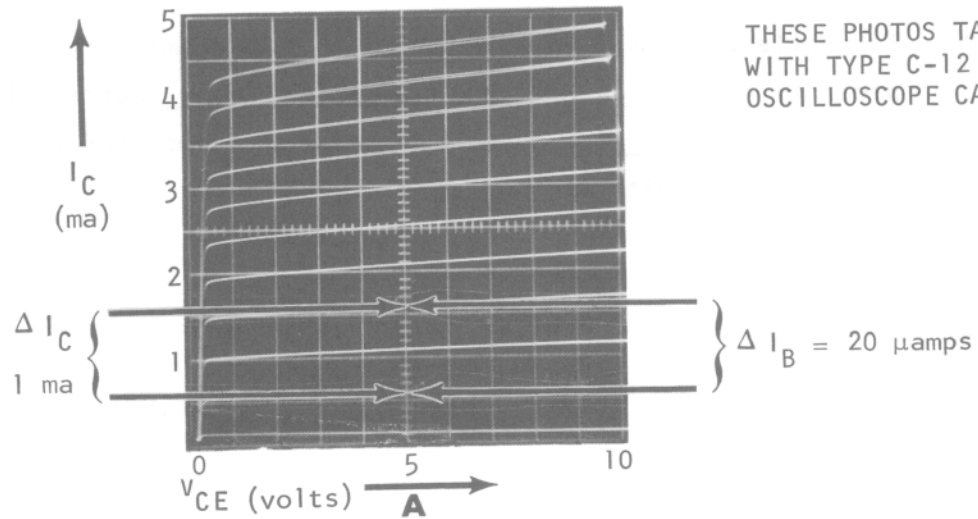

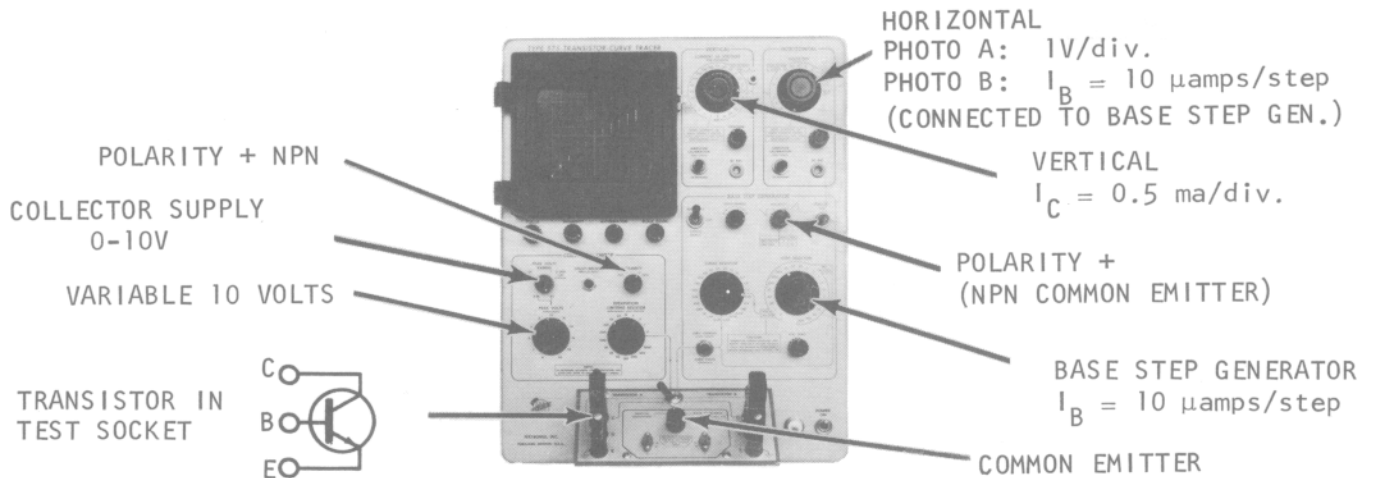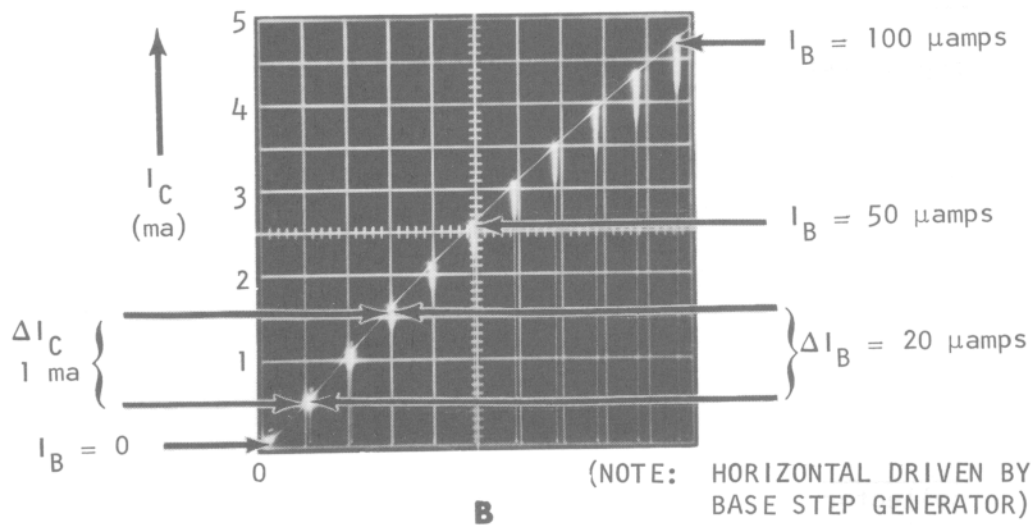THESE PHOTOS TAKEN WITH TYPE C-12 OSCILLOSCOPE CAMERA



TEST SETUP

TEKTRONIX TYPE 575 TRANSISTOR-CURVE TRACER
FIGURE 33

33 h_{fe} may be calculated from data gained from the collector family of curves of the transistor. It may also be calculated from data gained by plotting collector current versus _____ current directly on the 575 Transistor-Curve Tracer.

33.1 h_{fe} can be calculated from data gained by varying base current while holding collector voltage constant and noting the change in collector current.


_____ base _____

33.2 To hold collector voltage constant on a collector family of curves, the measurements are made along only one vertical line indicating collector voltage.



_____ no answer needed _____

33.3 The measurements made on the collector family of curves in figure 33 are made along the vertical line indicating _____ volts of V_{CE} .

_____ no answer needed _____

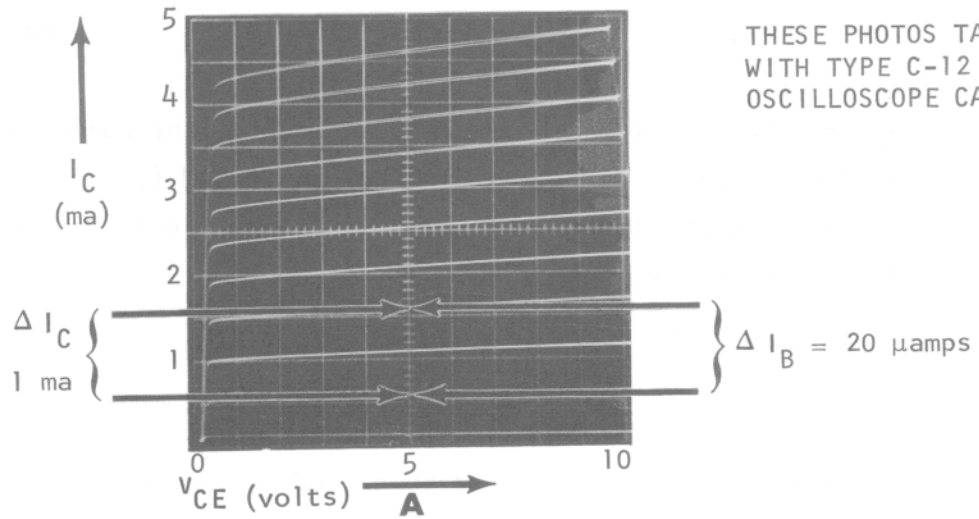

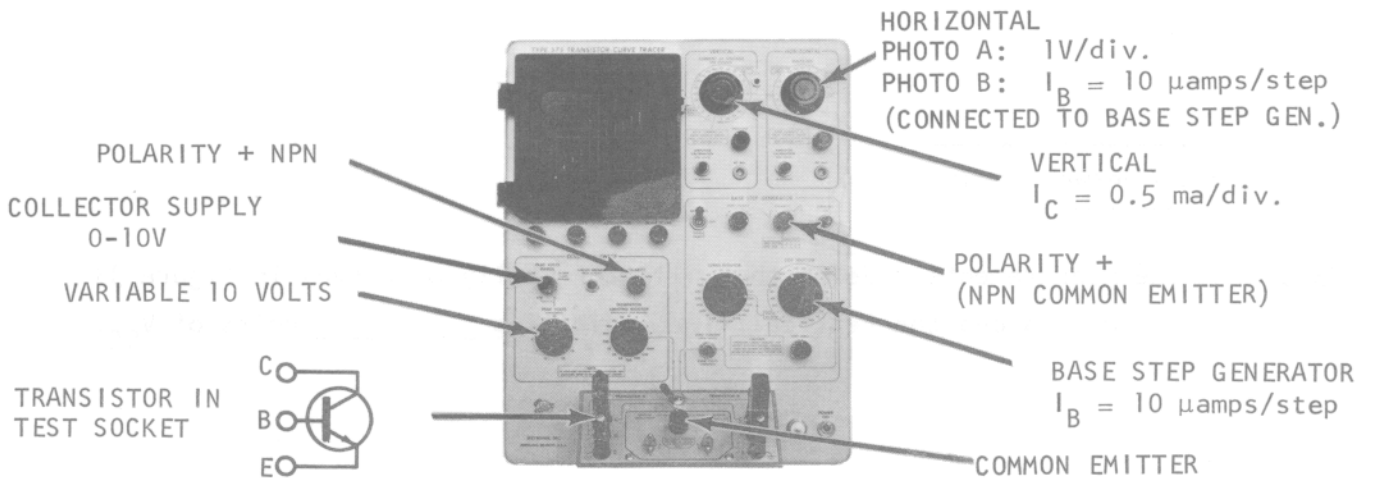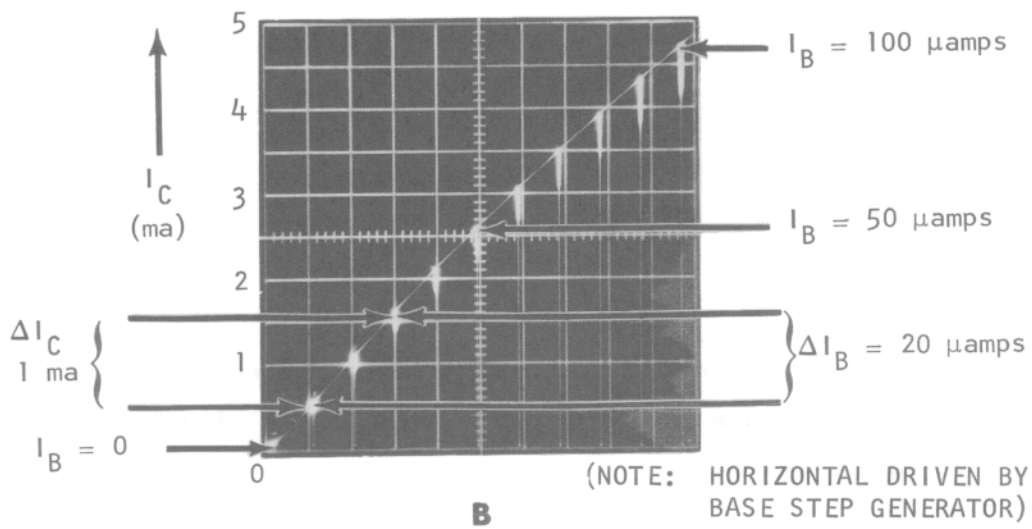THESE PHOTOS TAKEN WITH TYPE C-12 OSCILLOSCOPE CAMERA



TEST SETUP

TEKTRONIX TYPE 575 TRANSISTOR-CURVE TRACER
FIGURE 33

33.4 The assumed change in base current in figure 33 is _____ μ amps. This is accompanied by a change in collector current (along the 5 volt V_{CE} line) of _____ ma.

—
5
—

33.5

$$h_{fe} = \left. \frac{\Delta I_C}{\Delta I_B} \right|_{\Delta V_{CE} = 0}$$

At the point selected for measurement on the collector family of curves in figure 33, $h_{fe} =$ _____.

—
20
1
—

33.6


In the second display in figure 33, base current is plotted directly against collector current and the slope of the line indicates h_{fe} . Each step represents _____ μ amps of base current.

$$\frac{\Delta I_C}{\Delta I_B} = \frac{\Delta I \text{ ma}}{\Delta 20 \mu a} = 50$$



33.7

Photo B in figure 33 is a direct plot of base current versus collector current. The horizontal scale is not given a dimension because each step in the display corresponds to a given value of base current.

—
10
—

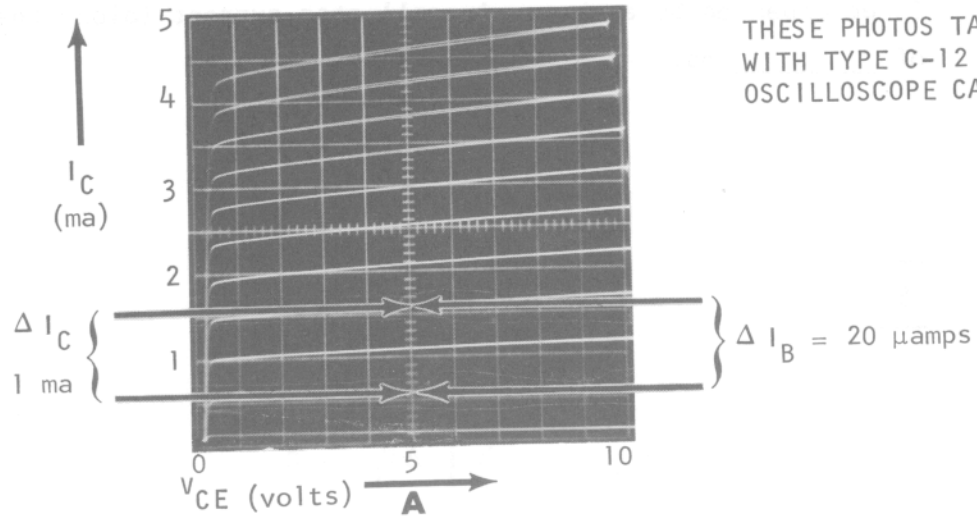

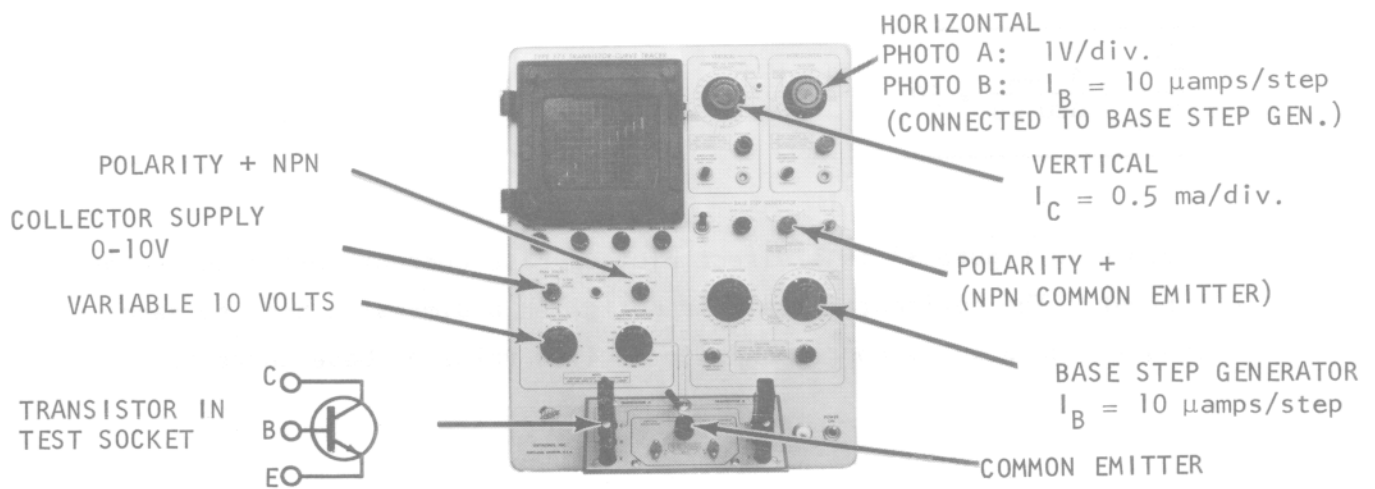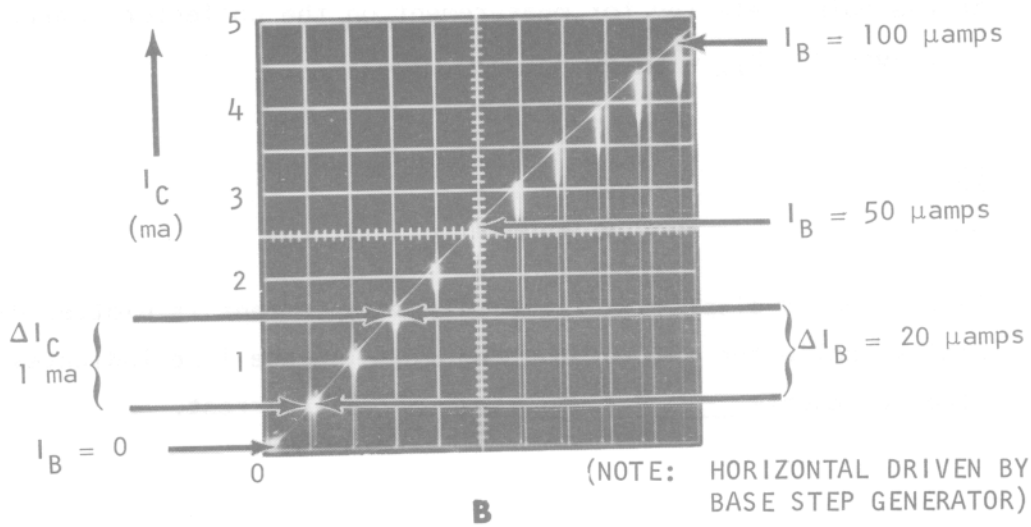THESE PHOTOS TAKEN
WITH TYPE C-12
OSCILLOSCOPE CAMERA



TEST SETUP

TEKTRONIX TYPE 575 TRANSISTOR-CURVE TRACER
FIGURE 33

33.8 Photo B in figure 33 provides a plot collector current versus _____ instead of collector voltage as shown in photo A.

no answer needed

33.9 The measurement used to determine h_{fe} from the collector family of curves in figure 33 was made between a base current of 10 and 30 μ amps. To gain the same results from photo B in figure 33, the measurements should be made between _____ and _____ μ amps of base current.




base current

33.10 Making these same measurements at a different point on the curves in figure 33 will result in a different value of _____.

10
30

33.11 h_{fe} will change with the selected point of operation of the transistor. The slope of the line indicating h_{fe} in photo B of figure 33 is not straight because _____ has different values at different points of operation.

 h_{fe}

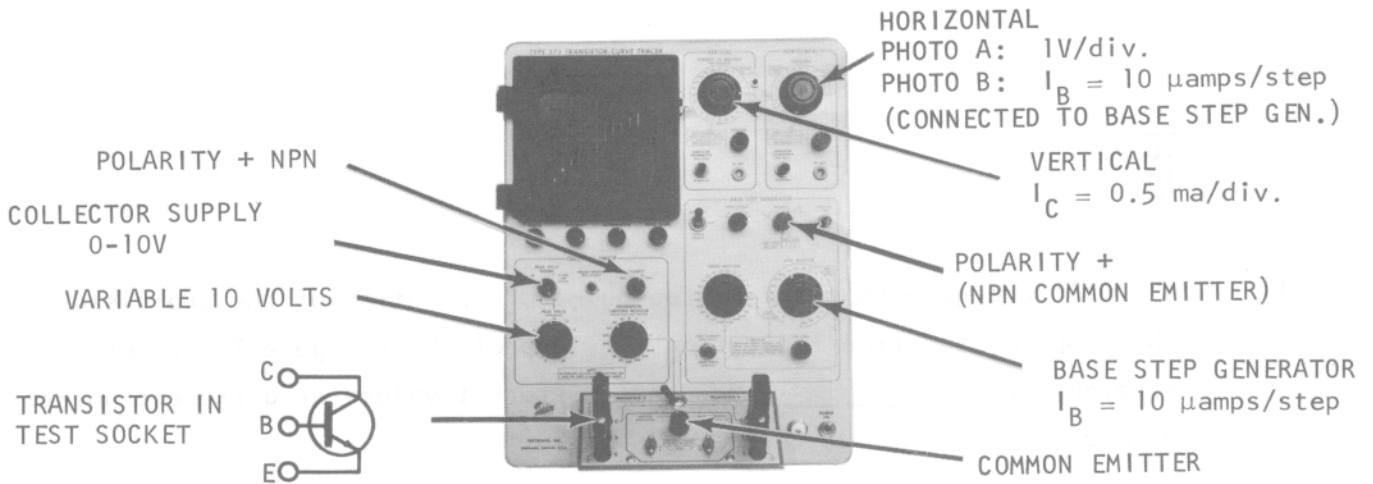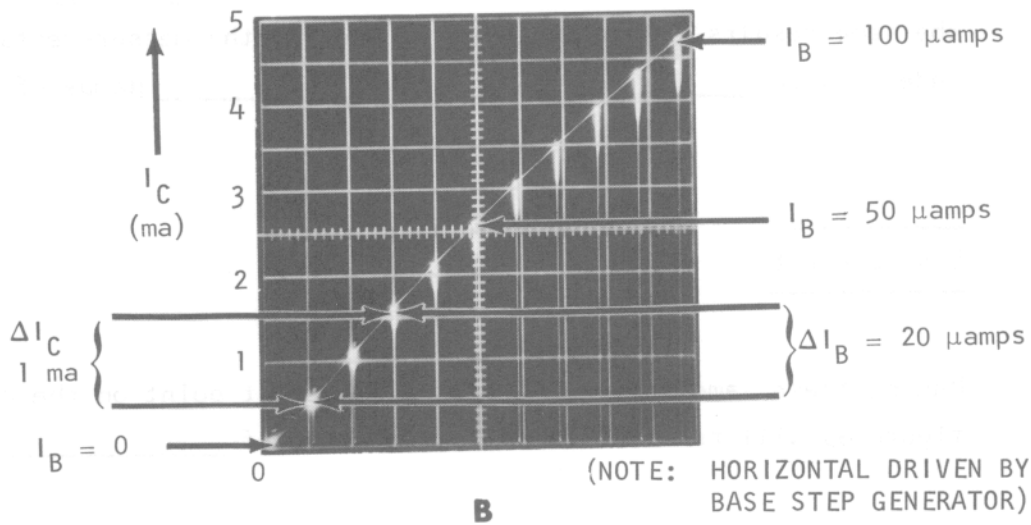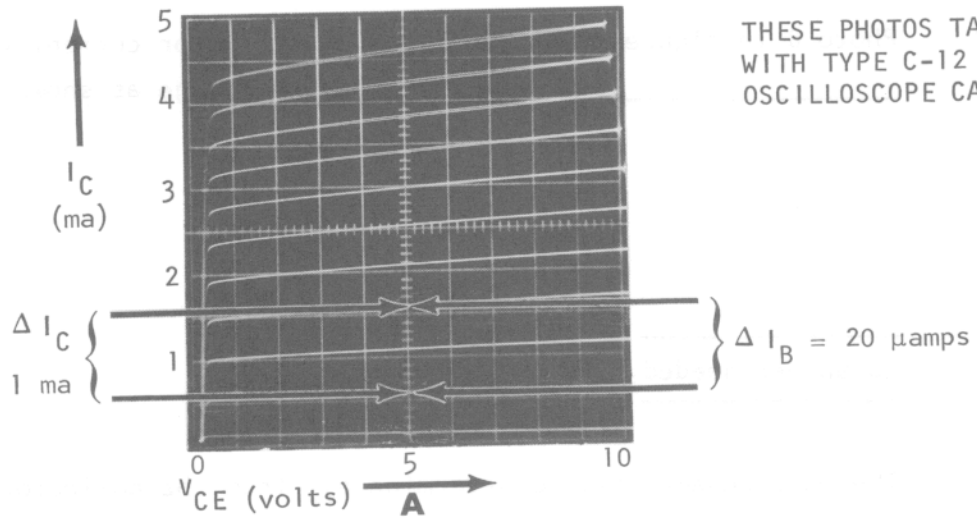

TEST SETUP

TEKTRONIX TYPE 575 TRANSISTOR-CURVE TRACER
FIGURE 33

33.12 Make a few measurements of h_{fe} at different points on the curves in figure 33.

 h_{fe}

33.13 To have the transistor whose curves are shown in figure 33 operate with a collector current of 2.5 ma and a collector voltage of 4 volts, there must be _____ μ a of base current.


no answer needed

33.14** h_{fe} may be found from the collector _____ of curves. When base current is plotted directly against collector current on the 575, the slope of the line indicates _____.


50

33.15 END OF SET

family
 h_{fe}

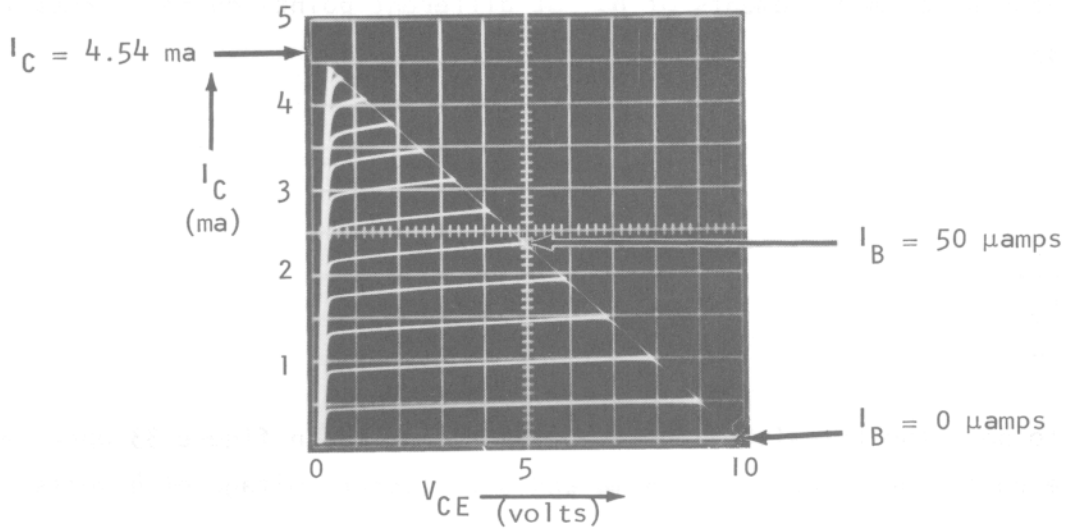

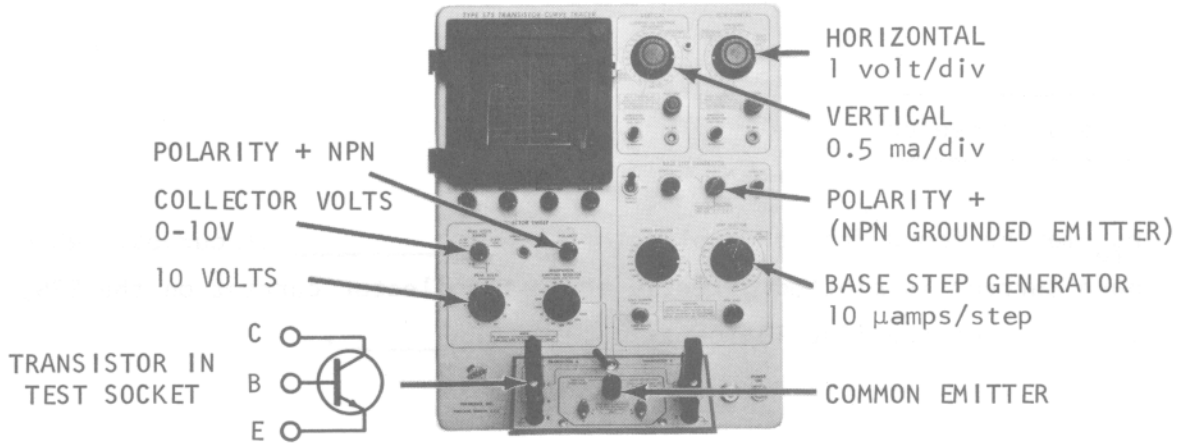COLLECTOR FAMILY OF CURVES
WITH 2.2K LOAD LINE



TEST SETUP

TEKTRONIX TYPE 575 TRANSISTOR-CURVE TRACER
TOP PHOTO TAKEN WITH TYPE C-12 OSCILLOSCOPE CAMERA

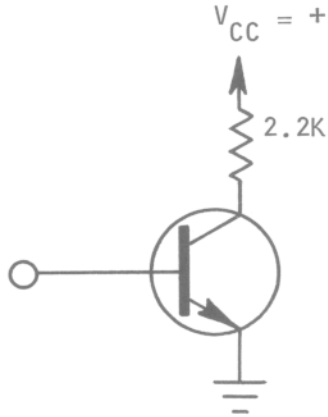


FIGURE 34

34 To gain information on the operation of the transistor in a circuit, a load line may be drawn on the collector family of curves. The slope of the d-c load line is determined by the _____ in series with the transistor.

34.1 With supply voltages applied to the transistor and the transistor non-conducting, the full collector supply voltage appears across the transistor. One limit of the transistor's operation is the collector _____.


_____ resistance

34.2 Considering that the transistor is short circuited, the amount of current flowing is governed by the value of collector supply voltage and the total series resistance. One limit of the transistor's operation may be found by dividing the collector supply voltage by the total _____.


_____ supply voltage

34.3 Figure 34 shows a transistor with a resistance in series to the collector supply. The slope of the line on the collector family of curves is determined by the _____.

_____ series resistance

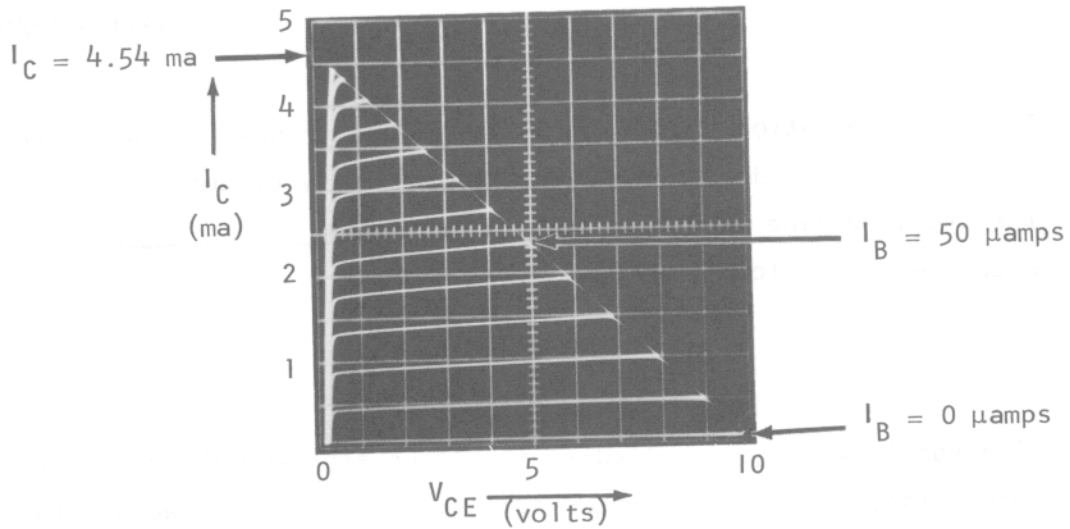

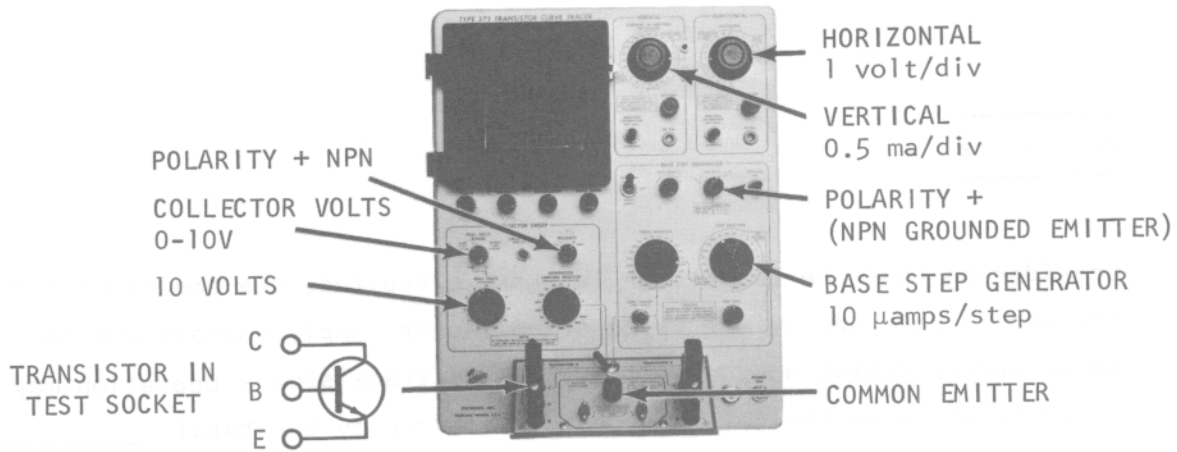COLLECTOR FAMILY OF CURVES
WITH 2.2K LOAD LINE



TEST SETUP

TEKTRONIX TYPE 575 TRANSISTOR-CURVE TRACER
TOP PHOTO TAKEN WITH TYPE C-12 OSCILLOSCOPE CAMERA

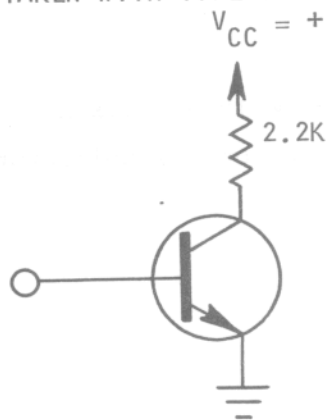


FIGURE 34

34.4 The load line in figure 34 intersects the base line at 10 volts on the collector family of curves. If the transistor is non-conducting, there will be _____ volts, collector to emitter.

resistor

34.5 Considering that the transistor is a short circuit, current is limited by the series resistance in the circuit; in the case in figure 34, _____K ohms.

10


34.6 With the transistor shorted, the full supply voltage is across the series resistance. With the transistor in figure 34 shorted, there are _____ volts across 2.2K ohms.

2.2


34.7 With the transistor shorted, the current flow is calculated by dividing the voltage across the series resistance by the resistance. With the transistor in figure 34 shorted, the current is _____m amps.

$$I = \frac{V_R}{R} = \frac{10V}{2.2K} = \frac{?}{}$$

10

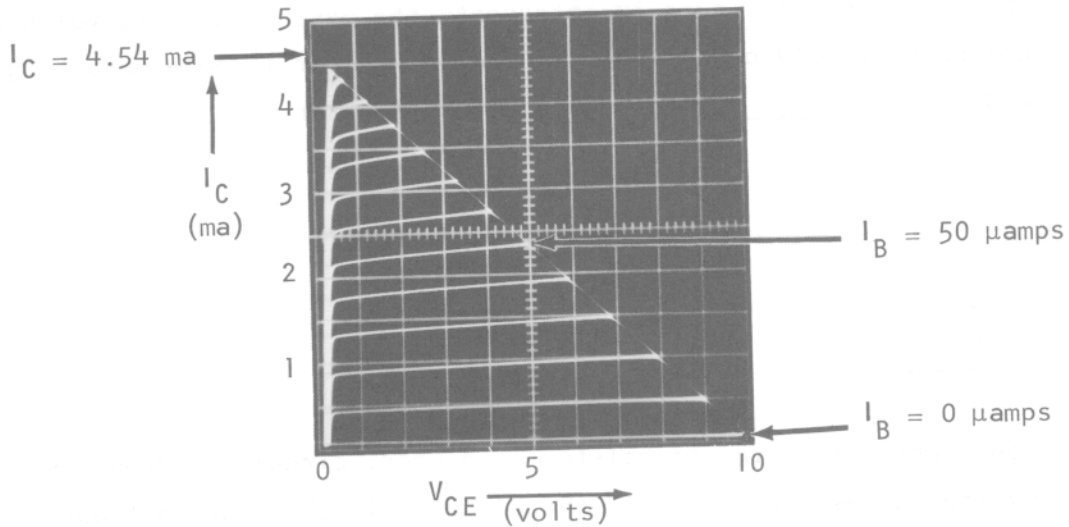

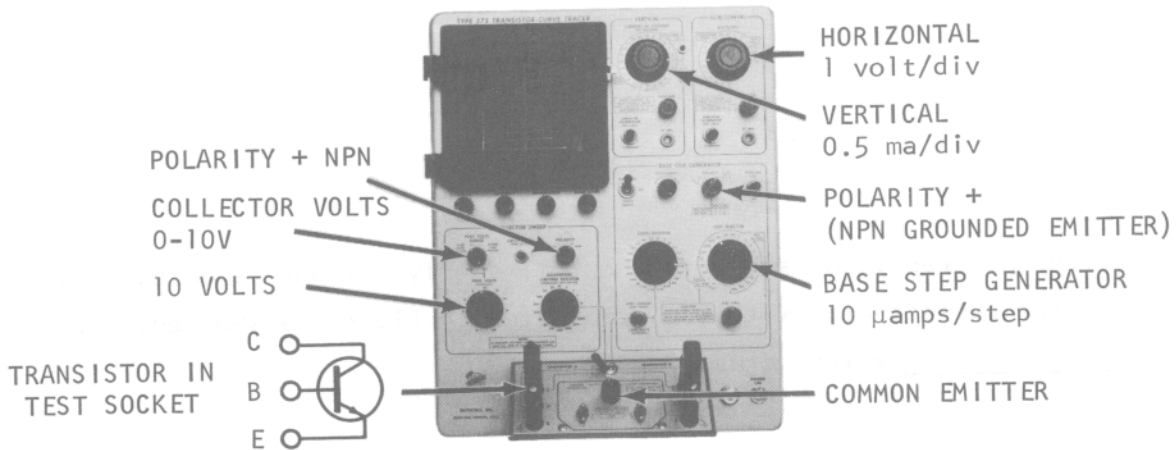COLLECTOR FAMILY OF CURVES
WITH 2.2K LOAD LINE



TEST SETUP

TEKTRONIX TYPE 575 TRANSISTOR-CURVE TRACER
TOP PHOTO TAKEN WITH TYPE C-12 OSCILLOSCOPE CAMERA

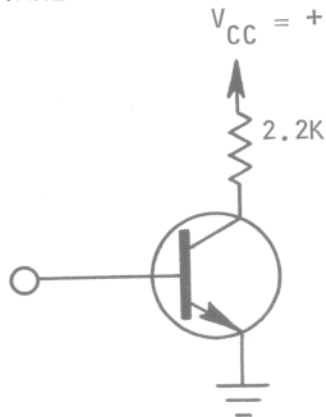


FIGURE 34

34.8 The load line is constructed between the two extremes calculated in the previous frames and shown in figure 34. The extremes are _____ m amps and _____ volts.

4.54

34.9 Construct a load line on the collector family of curves in figure 34 for the same circuit if the collector supply were 5 volts instead of 10.

4.54
10

34.10 The load line constructed in frame 34.9 _____ parallel to the load line for a supply voltage of 10 volts.
(is, is not)

THE LOAD LINE SHOULD EXTEND BETWEEN
2.27ma on the vertical scale and
5 volts on the horizontal scale.

34.11 The slope of the load line does not change when a different supply voltage is used, since the slope is determined by the value of _____.



is

34.12** The d-c load line is constructed between the two extremes of d-c operation. These two extremes are found by considering the transistor is first _____ then _____. The slope of the d-c load line is determined by the series _____.

resistance

34.13 END OF SET

open, shorted (any order)
resistance

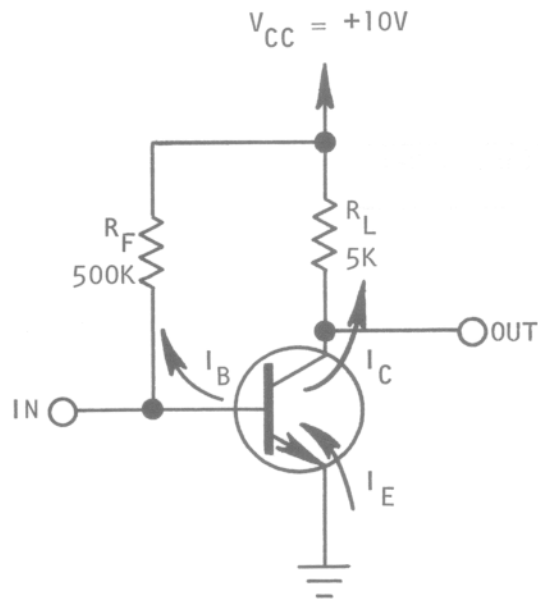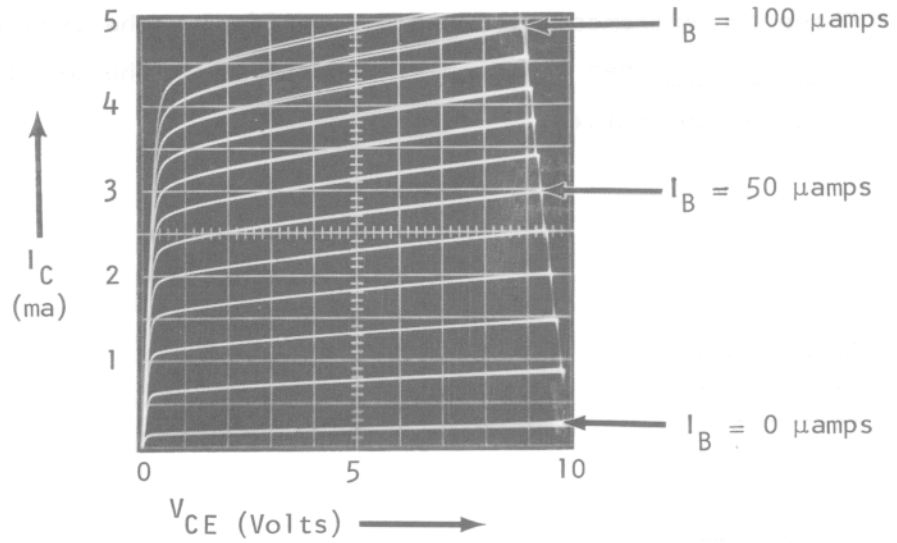

TEST SETUP

TEKTRONIX TYPE 575 TRANSISTOR-CURVE TRACER
 TOP PHOTO TAKEN WITH TYPE C-12 OSCILLOSCOPE CAMERA

- R_L = COLLECTOR LOAD RESISTOR
- R_F = BASE BIASING RESISTOR
- V_{CC} = COLLECTOR SUPPLY VOLTAGE

FIGURE 35

35 Construct a d-c load line for the circuit in figure 35. R_F sets the operating point base current at a value of _____ μ amps.

35.1 Consider that the transistor in figure 35 is open circuited. The voltage across the transistor will be the collector supply voltage or _____ volts.

_____ load line on following page _____
20

35.2 One extreme of the transistor's operation is the supply voltage. To find the other extreme, consider that the transistor is _____ circuited.

—
10
—

35.3 With the transistor in figure 35 short circuited, the current is limited by R_L . The full supply voltage will be dropped across R_L and the current will be _____ ma.

—
short
—

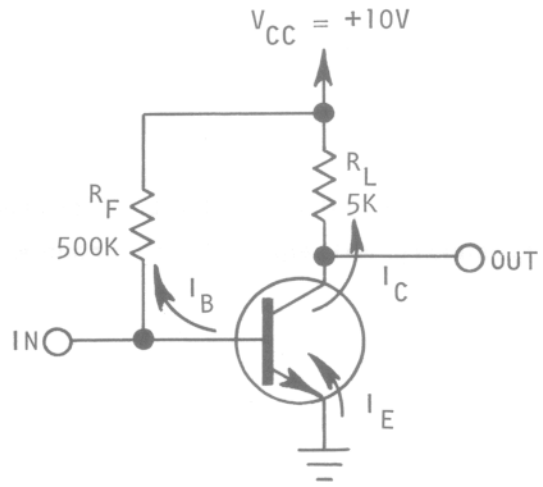
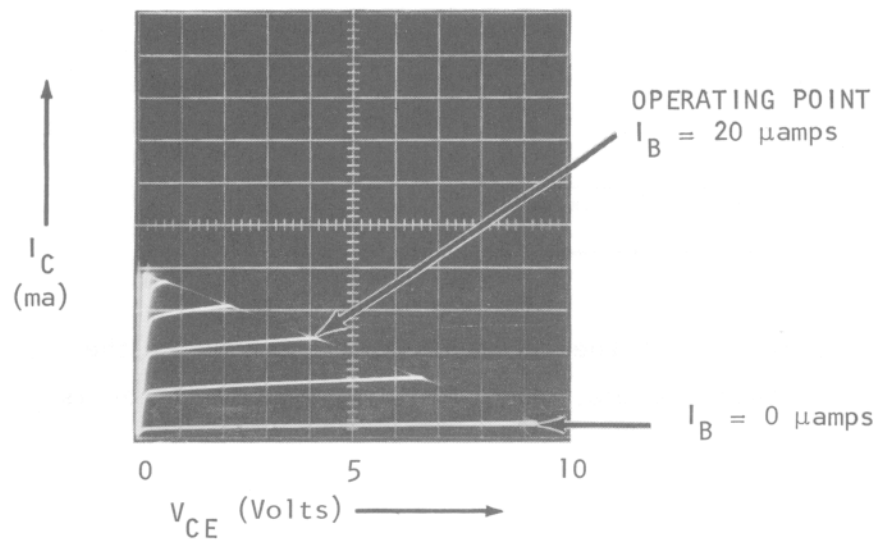
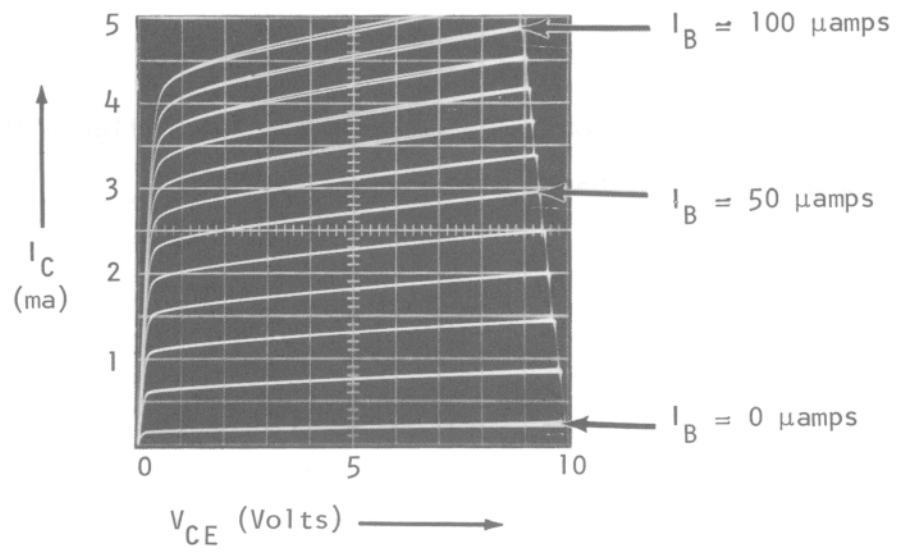


FIGURE 35-A

35.4 The two extremes for the transistor in figure 35A are: (1) 10 volts V_{CE} with zero collector current and, (2) _____ ma I_C with zero collector volts. A line connecting these points is the d-c load line.

$$\frac{10V}{5K} = 2 \text{ ma}$$

35.5 Since the voltage, base to emitter, is a very small value (a few tenths of a volt), consider that the full supply voltage is across R_F . The current through R_F is then _____.

$$\frac{V_{RF}}{R_F} = \frac{10V}{500K} = \underline{\quad ? \quad}$$

2

35.6 The current through R_F is I_B of the transistor. I_B is _____ for the transistor in figure 35-A.

$$\frac{10V}{500K} = 20 \text{ } \mu\text{amps}$$

35.7 The static (no applied signal) operating point of the transistor in figure 35-A is indicated by the point at which the 20 μ amp base current curve intersects the load line. The collector current at this point is about _____.

20 μ amps

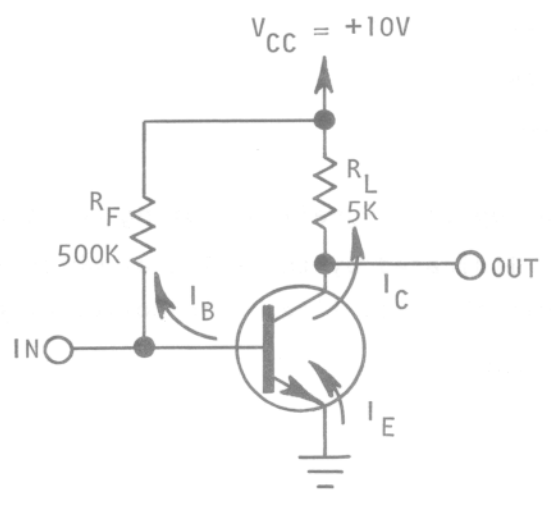
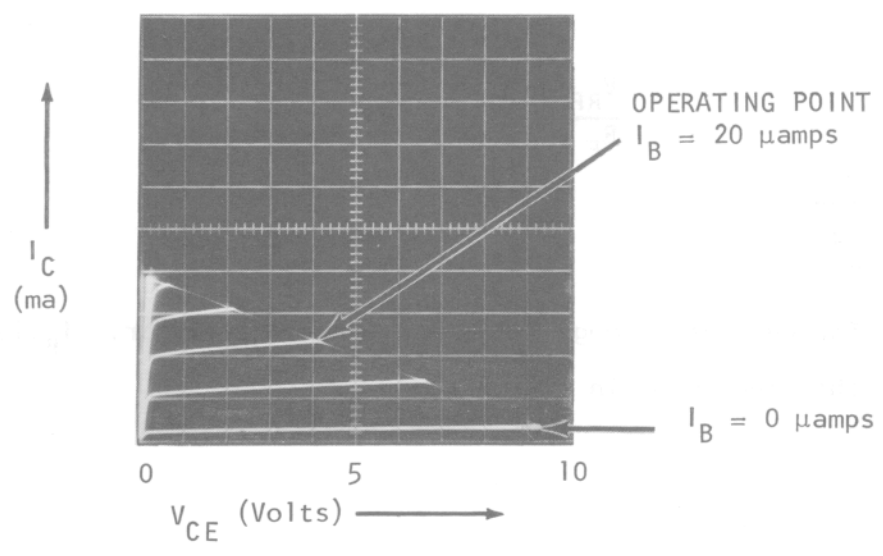
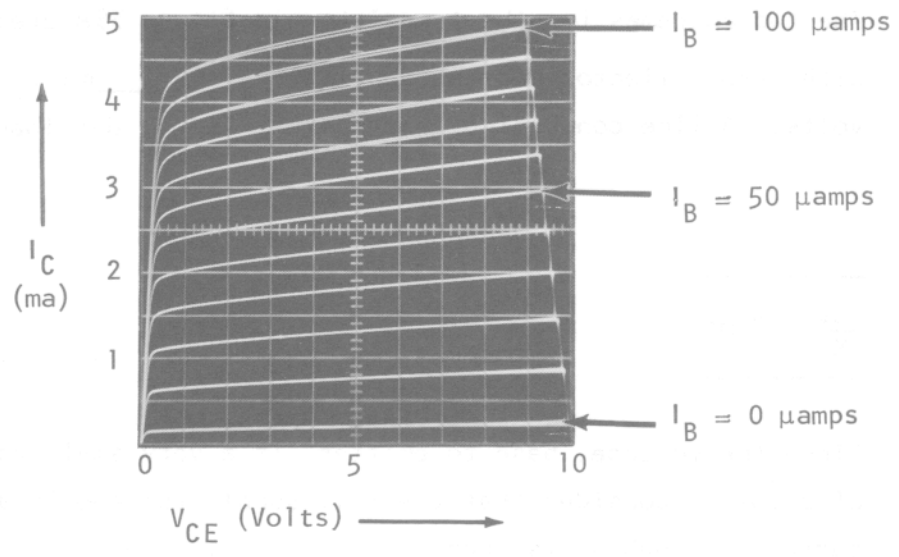


FIGURE 35-A

35.8 Figure 35-A shows the load line and operating point for the circuit in figure 35. The collector voltage at the operating point is about _____ volts.


1.15ma

35.9 The static or no input signal conditions of the transistor in figure 35-A are: $I_B =$ _____, $I_C =$ _____, and $V_{CE} =$ _____.



4.2V

35.10 Since I_E is the sum of collector and base current, the emitter current at the static operating point in figure 35-A is _____ ma.

20 μ amps
1.15 ma
4.2 volts

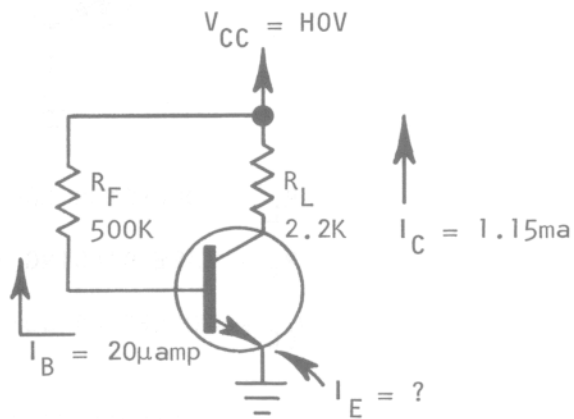

Turn to figure 35C for answer

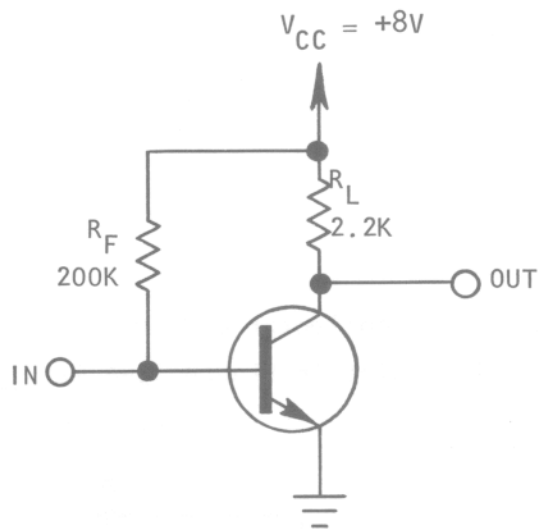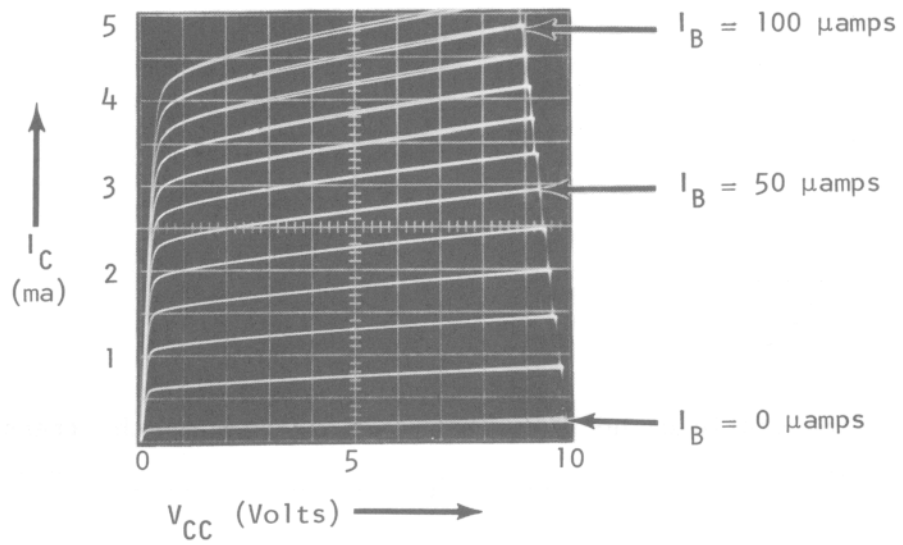

R_L = COLLECTOR LOAD RESISTOR

R_F = BASE BIASING RESISTOR

V_{CC} = COLLECTOR SUPPLY VOLTAGE

FIGURE 35-B

36 A transistor is termed in _____ when the collector junction becomes forward biased. The collector to emitter voltage at which this occurs is given the symbol _____. The current gain at saturation is given the symbol _____.

36.1 In most small signal amplifier applications, the transistor remains in the most linear portion of its operating characteristics. This falls somewhere between the non-conducting or cut-off state, and the condition where the collector junction becomes forward biased which is termed saturation.

saturation
 $V_{CE} \text{ (sat)}$
 $h_{FE} \text{ (sat)}$

36.2 In the cut-off state, the only current flowing is the result of hole-electron pairs and perhaps some surface leakage current. The transistor offers a very high resistance (near open circuit) and the voltage across the transistor approaches the collector supply voltage.

no answer needed

36.3 As the base current is increased, collector current increases and added voltage is dropped across the series resistance in the circuit. As base current increases, the voltage across the transistor _____ (increases, decreases).

no answer needed

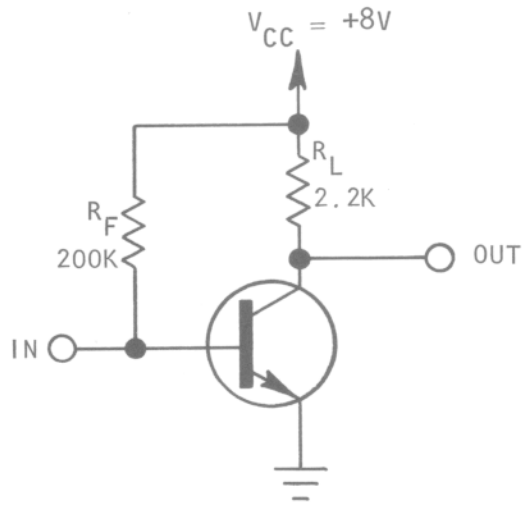
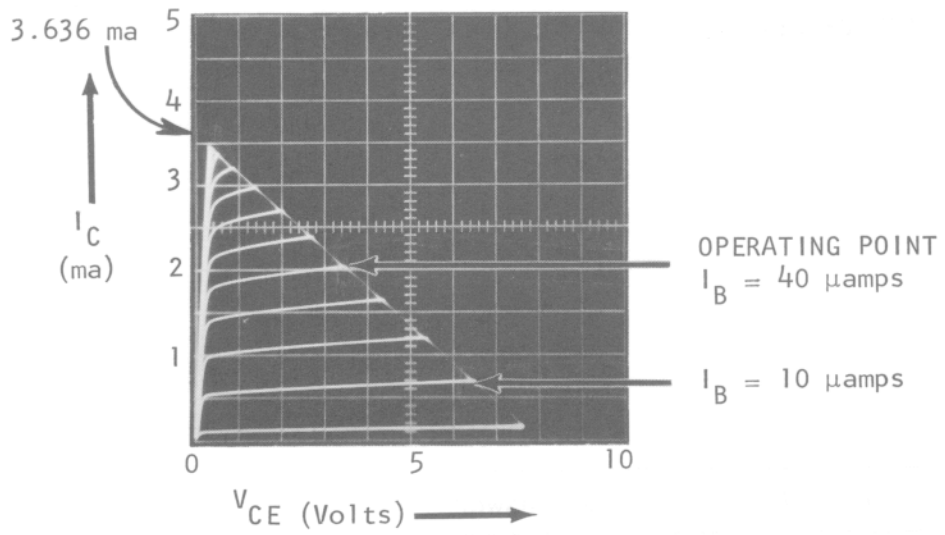
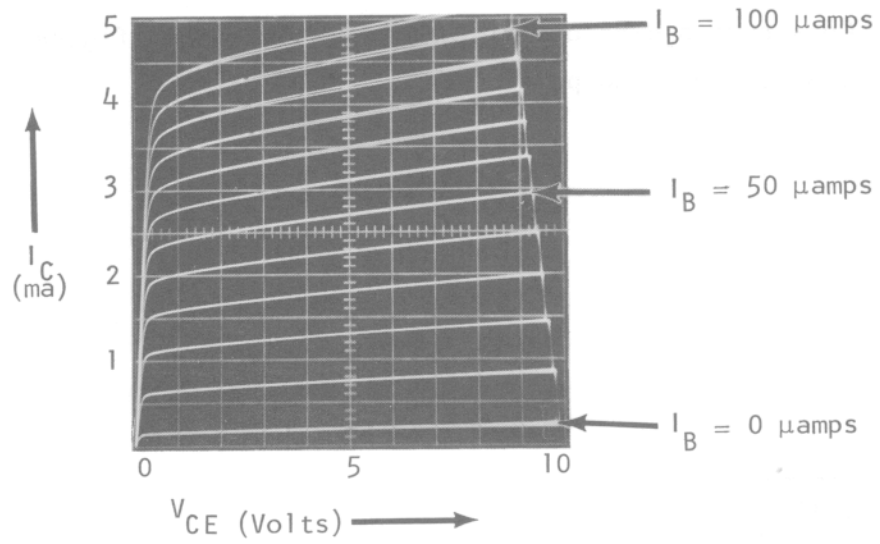


FIGURE 35-C

36.4 Changes in collector voltage have only a small effect on collector current as long as the collector junction is reverse biased. When the collector junction becomes forward biased, the transistor is said to be in _____.

_____ decreases _____

36.5 When the collector junction becomes forward biased, collector current is reduced as shown in figure 36. The sharp change occurs at approximately _____ volts, V_{CE} , when $I_B = 100 \mu\text{amps}$.

_____ saturation _____



36.6 The transistor in the common emitter configuration starts to enter saturation when the voltage collector to emitter (V_{CE}) is equal to the voltage, base to emitter (V_{BE}). On the $100 \mu\text{amp}$ base current curve in figure 36, $V_{BE} = V_{CE} =$ _____ volts when the transistor enters saturation.

_____ 0.3 _____


36.7 The collector to emitter voltage at the point the transistor enters saturation is given the symbol $V_{CE}(\text{sat})$. _____ is given at a specified value of I_B and I_C in manufacturers specifications.

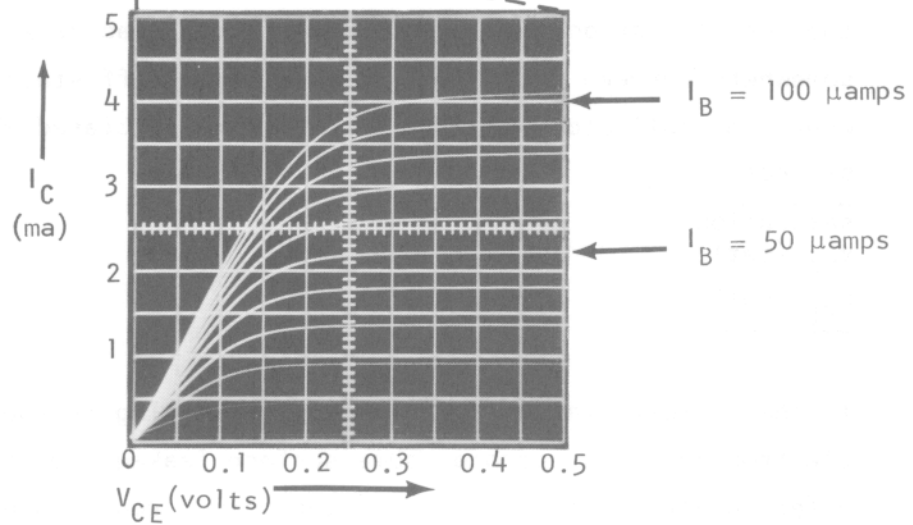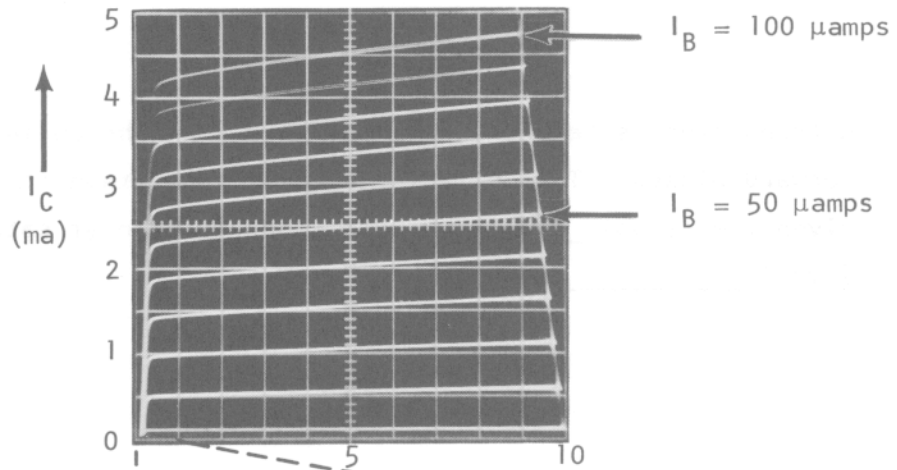_____ 0.3 _____

THESE PHOTOS TAKEN
WITH TYPE C-12
OSCILLOSCOPE CAMERA



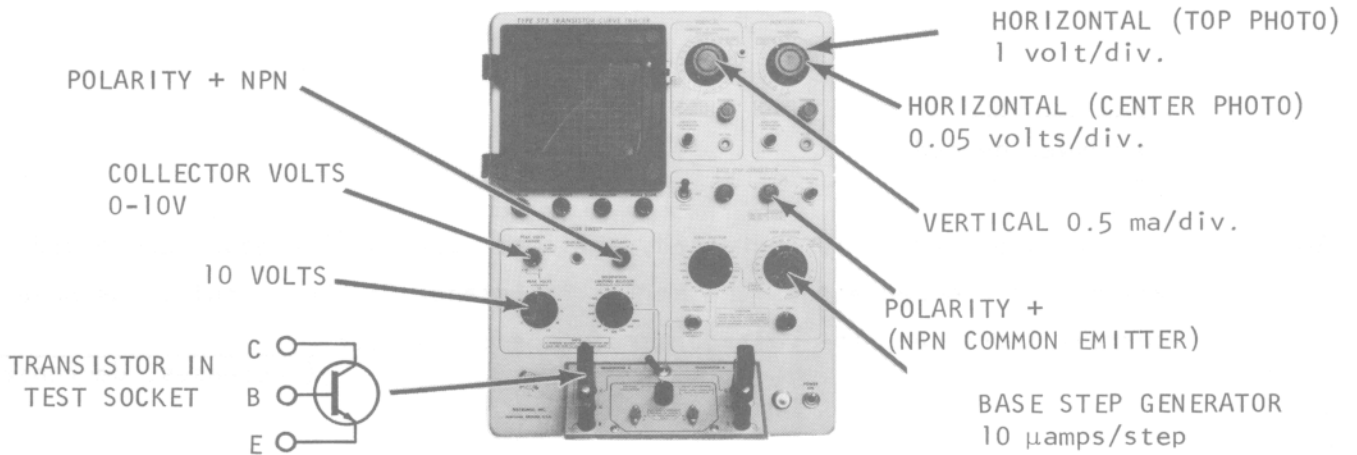COLLECTOR FAMILY OF CURVES
EXPANDED AREA AROUND SATURATION



TEST SETUP

TEKTRONIX TYPE 575 TRANSISTOR-CURVE TRACER

Figure 36

36.8 In figure 36, $V_{CE}(\text{sat}) \approx 0.3$ volts at $I_B = 100 \mu\text{amps}$ and $I_C = 4 \text{ ma}$. When $I_B = 90 \mu\text{amps}$ and $I_C = 3.5\text{ma}$, $V_{CE}(\text{sat}) \approx$ _____.

 $V_{CE}(\text{sat})$

36.9 $h_{FE}(\text{sat})$ is the current gain of the transistor at saturation.
 $h_{FE}(\text{sat}) = \frac{I_C(\text{sat})}{I_B(\text{sat})}$. On the $100 \mu\text{amp}$ base current curve in figure 36, $h_{FE}(\text{sat}) =$ _____.

 $0.25V$



36.10** The current gain at saturation is given the symbol $h_{FE}(\text{sat})$. When the collector junction is reverse biased, the transistor _____ in saturation and V_{CE} is _____ than $V_{CE}(\text{sat})$. (is, is not)
 (less, greater)

 40

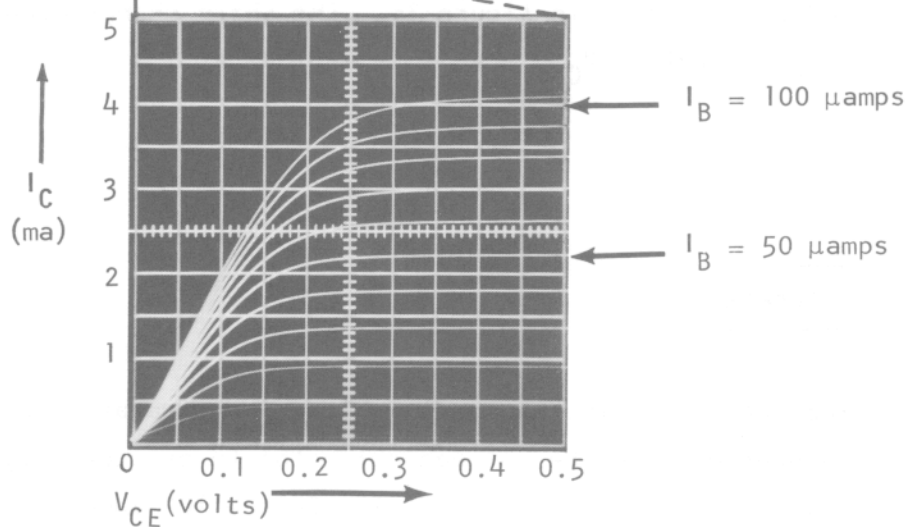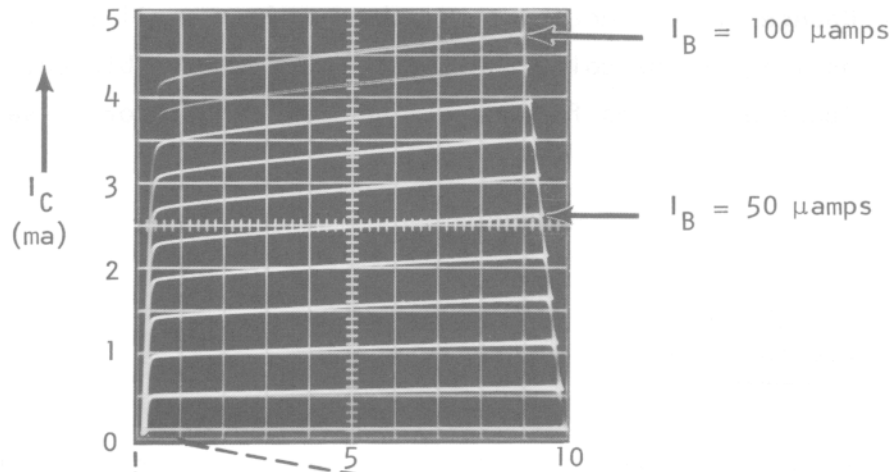
36.11 END OF SET

 is not
 greater

THESE PHOTOS TAKEN WITH TYPE C-12 OSCILLOSCOPE CAMERA



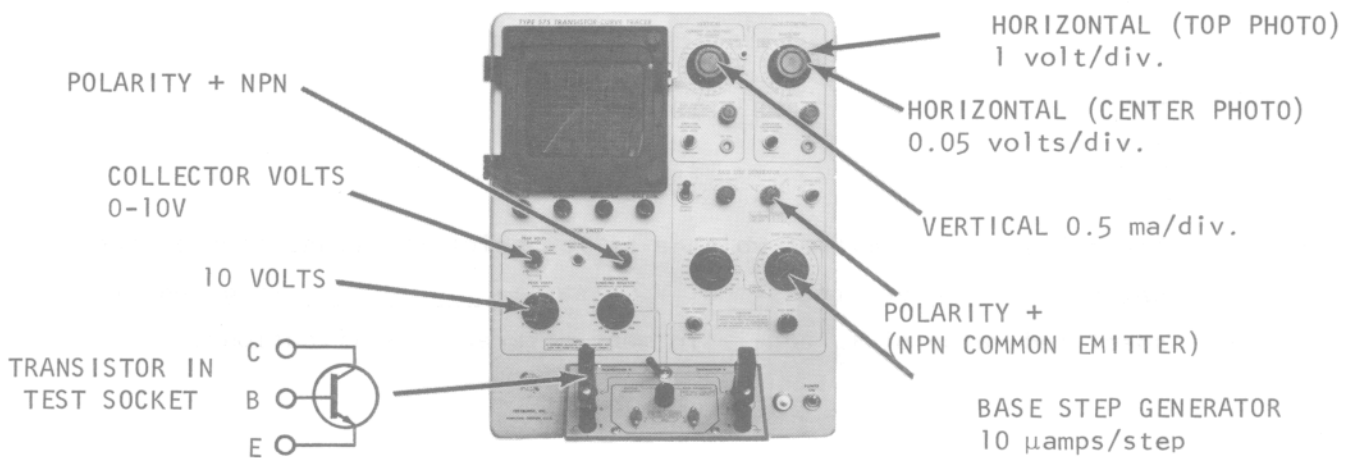COLLECTOR FAMILY OF CURVES
EXPANDED AREA AROUND SATURATION



TEST SETUP

TEKTRONIX TYPE 575 TRANSISTOR-CURVE TRACER

Figure 36

37 A transistor in saturation has both the emitter and collector junctions _____ biased. The injection of minority carriers into the base from the collector when the transistor enters saturation increases the _____ in the base. This must be removed in order to turn _____ the transistor.

37.1 Carriers injected into the base recombine or diffuse to the collector. Once injected and until they recombine in the base or move into the collector circuit, they are existing as _____ carriers in the base.

forward
stored charge
off

37.2 Carriers injected into the base from the emitter represent a charge in the base during their diffusion to the collector.

minority

37.3 To turn on a transistor, the charge of minority carriers must be established in the base. To turn off a conducting transistor, this stored _____ must be removed.

no answer needed

37.4

A period of time is required to turn on a non-conducting transistor to establish the _____ of minority carriers in the _____ before collector current can reach its final value.

_____ charge _____

37.5

Once the transistor is in full conduction, removal of the stored charge of minority carriers in the base is required to turn it off.

_____ charge
base _____

37.6

It takes a period of time to remove the stored charge when turning off a conducting transistor. The greater the magnitude of stored charge, the more _____ is required to remove it.

_____ no answer needed _____

37.7

When the transistor is driven into saturation, the collector injects carriers into the base as a result of becoming forward biased. The number of minority carriers in the base is increased and the collector current is decreased.

_____ time _____

37.8 Until the carriers in the base recombine or move into the collector, they are existing as a stored charge in the base. The extra injected carriers forced into the base in saturation represent an increase in the _____ in the base.

no answer needed

37.9 A transistor driven into saturation has a larger stored charge in its base than when in an un-saturated condition. The deeper the transistor is driven into _____, the greater the stored charge.

stored charge

37.10 Since the stored charge represents a supply of minority carriers, the stored charge must be removed before the transistor can be turned _____.

saturation

37.11** The collector becoming forward biased as the transistor enters saturation results in an increase in the _____ in the base of the transistor which must be removed to turn the transistor _____.

off

37.12

END OF SET

stored charge
off



V_{CE} →

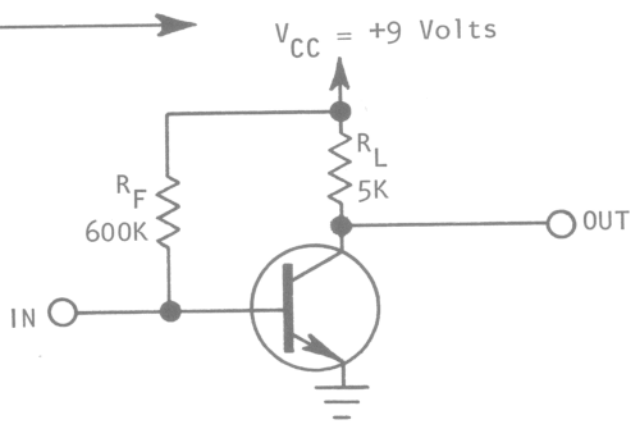


FIGURE 38

38 Construct a load line; determine the operating point base current, collector voltage and collector current for the circuit in figure 38. With an applied signal current of 10 μ amps peak to peak, what signal current is flowing in the output circuit and what is circuit current gain?

38.1 One extreme of the transistor's operating range is the supply voltage. The load line will intersect the zero collector current line at _____ volts of collector voltage in figure 38.


answers on following page

38.2 The second extreme of the transistor's operation is determined by the series resistance in the paths of emitter and collector current. The load line intersects the zero collector voltage line at _____ma of collector current in figure 38.

9

38.3 Operating or quiescent point base current is determined by the base biasing resistor, R_F . The operating point base current in figure 38 is _____ μ amps.

1.8

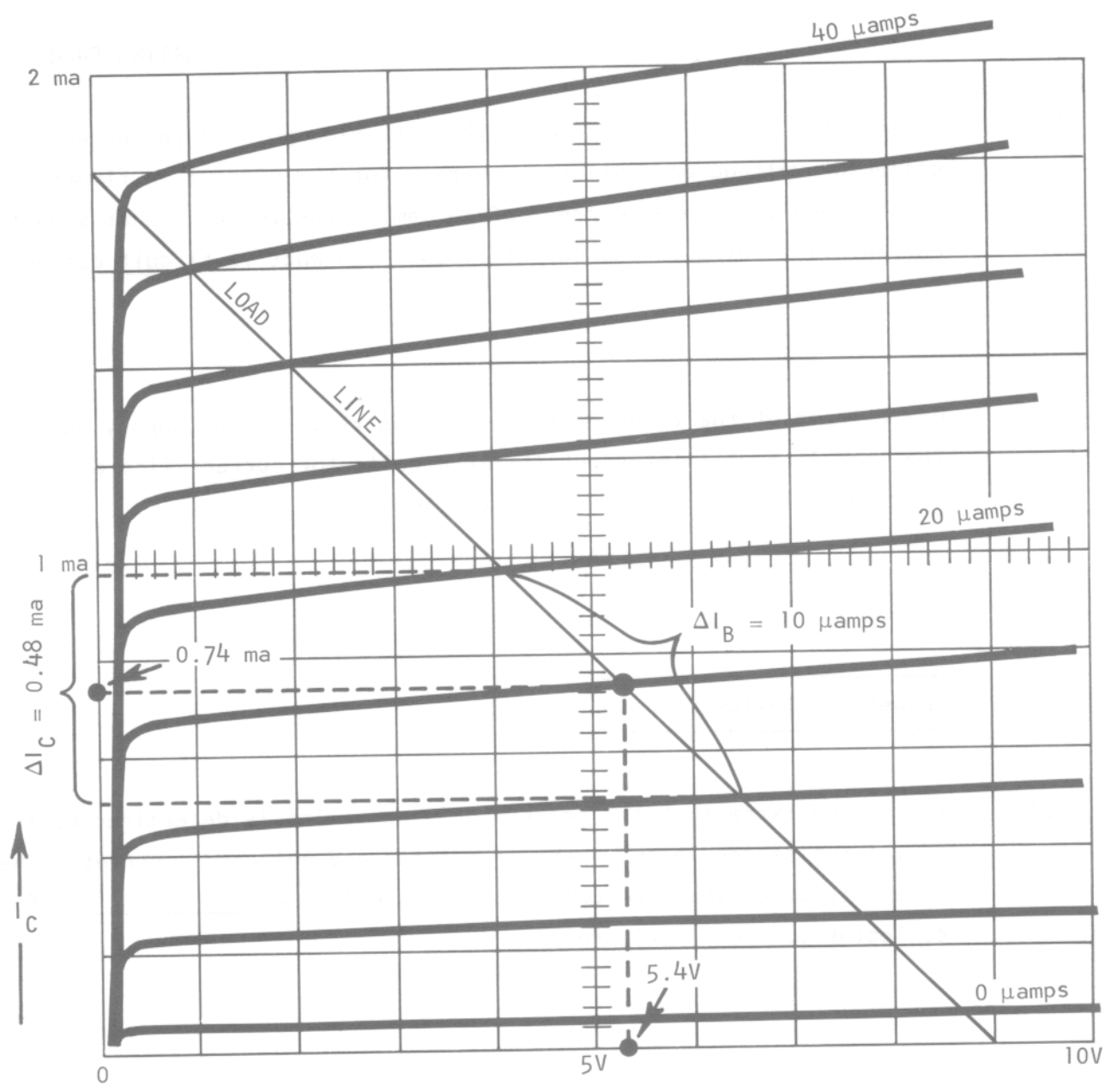

V_{CE} → $V_{CC} = +9 \text{ Volts}$

$A_i = \text{CURRENT GAIN}$

$$A_i = \frac{\Delta I_C}{\Delta I_B} \text{ (ALONG THE LOAD LINE)}$$

$$A_i = \frac{0.48 \text{ ma}}{10 \mu\text{amps}}$$

$$A_i = 48$$

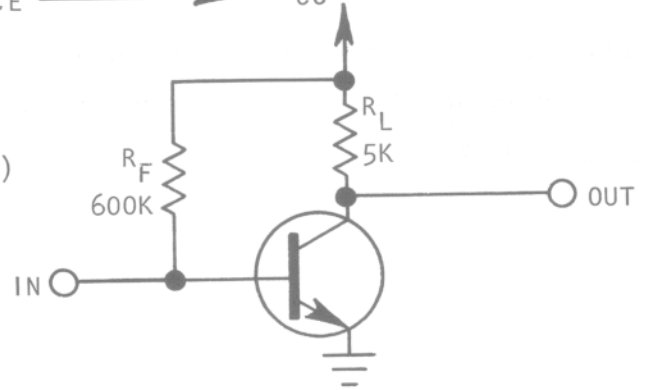


FIGURE 38-A

38.4 The operating point base current curve intersects the load line at the operating point. In figure 38-A, operating point collector current is _____ and collector voltage is _____.

$$\frac{9 \text{ Volts}}{600\text{K}} = 15 \mu\text{amps}$$

38.5 h_{fe} gives the current gain of the transistor, but disregards the circuit. Making a current gain measurement along the load line gives the current gain of the _____.

$$\frac{0.74\text{ma}}{5.4 \text{ Volts}}$$

38.6 With an input signal current of 10 μamps peak to peak, the base current will vary 5 μamps above and below the operating point. In figure 38-A it varies between _____ μamps and _____ μamps of base current.

_____ circuit _____

38.7 If the applied change in base current is assumed to take place along the load line, the change in circuit collector current can be found. In figure 38-A, the change in collector current for an input change of 10 μamps base current is _____ ma.

_____ 10 _____
_____ 20 _____

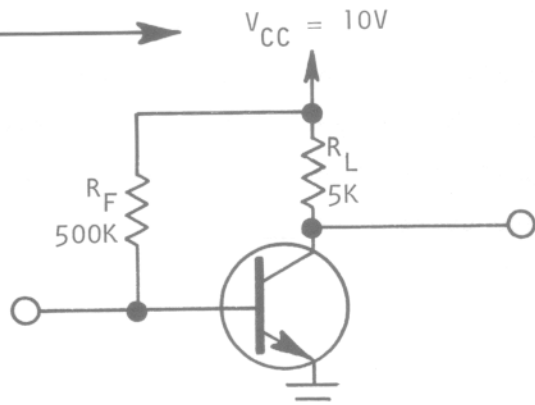
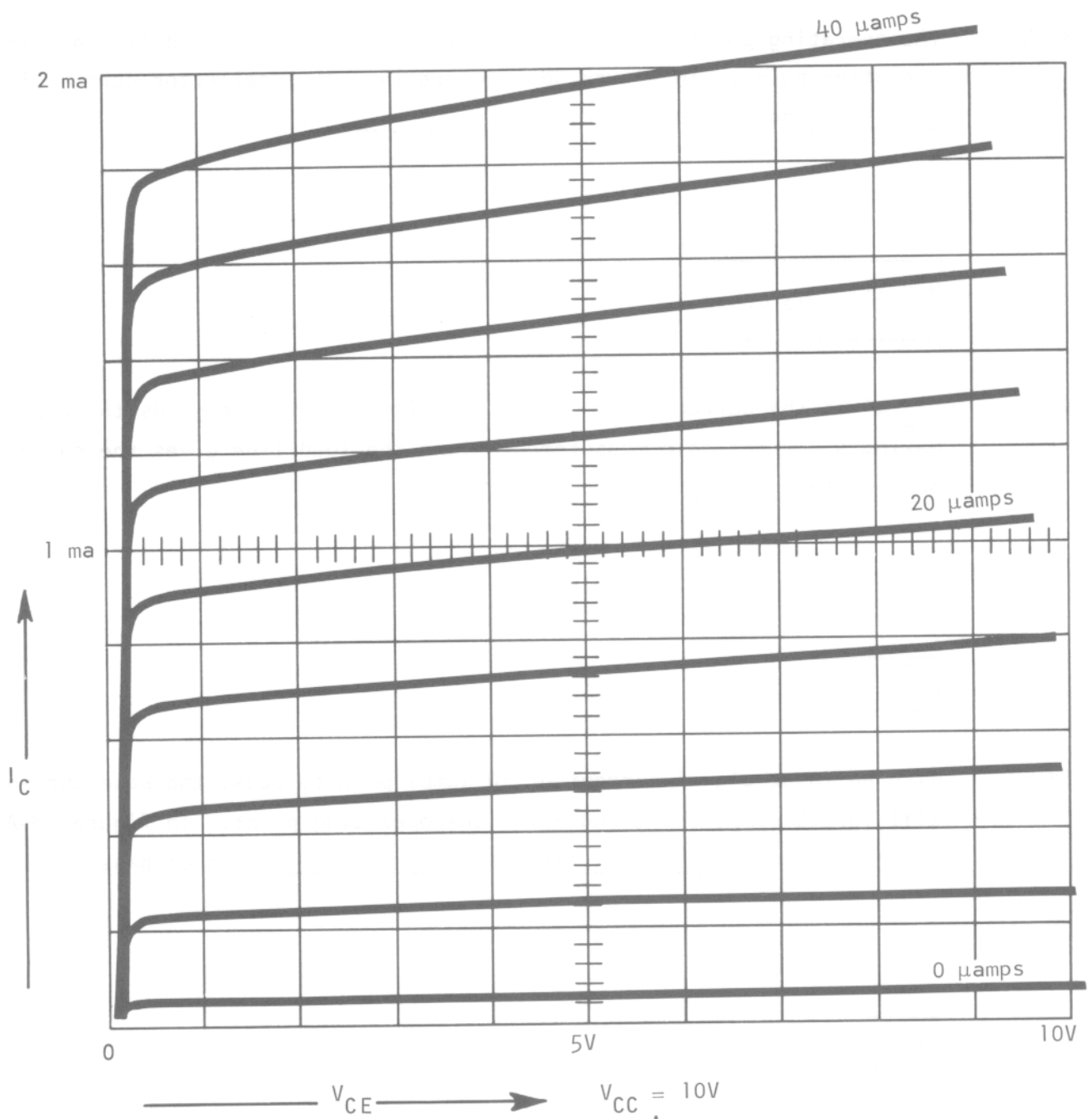


FIGURE 38-B

38.8 Dividing the change in collector current by the applied change in base current along the load line gives the circuit current gain . In figure 38-A, circuit current gain is _____.


$$\frac{0.48 \text{ ma}}{10 \text{ } \mu\text{amps}} = 48$$

38.9** Construct a load line; determine the operating point base current, collector current, and collector voltage for the circuit in figure 38-B.

$$\frac{0.48 \text{ ma}}{10 \text{ } \mu\text{amps}} = 48$$

38.10 END OF SET

answer on following page

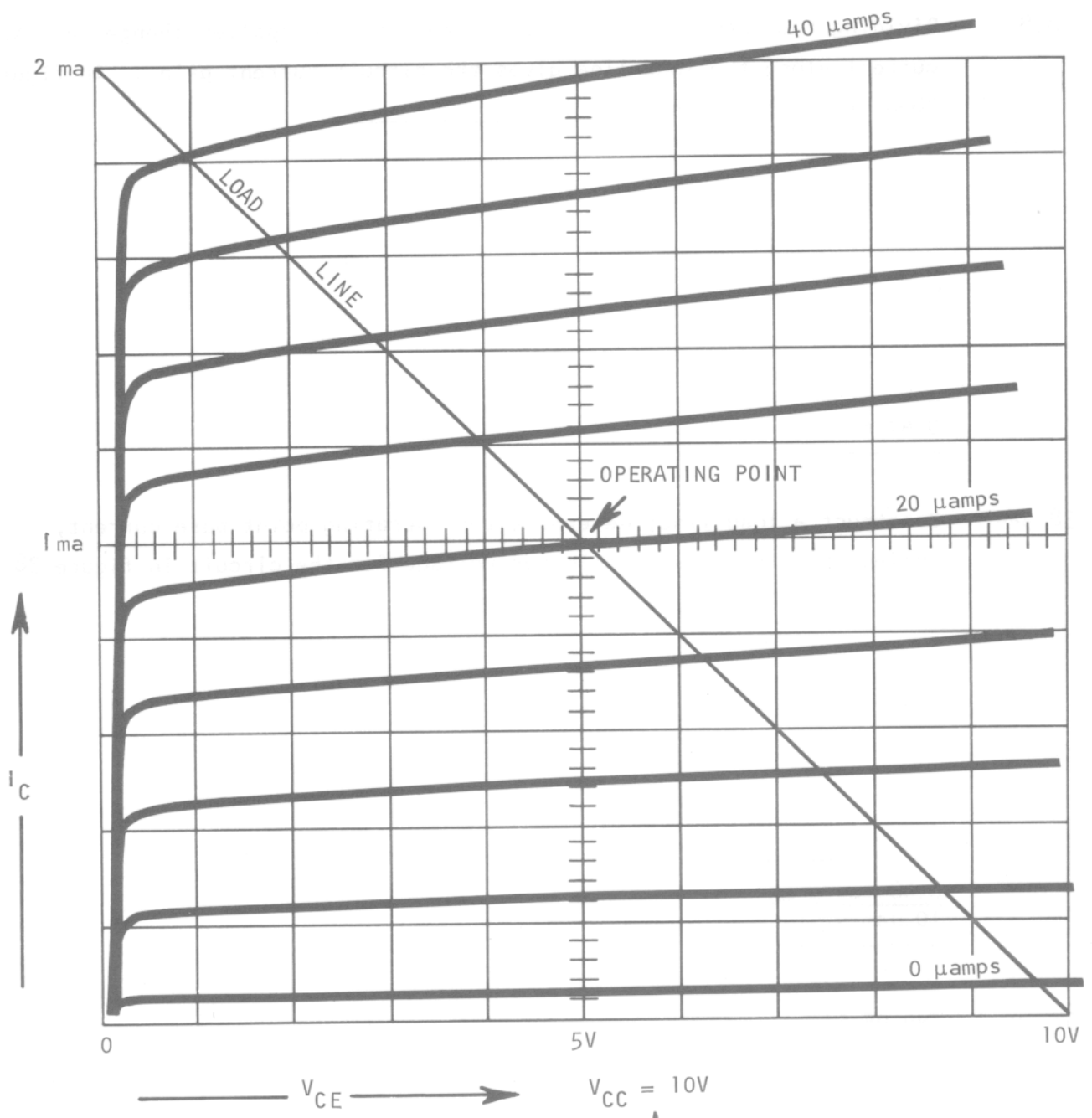

OPERATING POINT

$I_B = 20\ \mu\text{amps}$

$I_C = 1\ \text{ma}$

$V_{CE} = 5\ \text{Volts}$

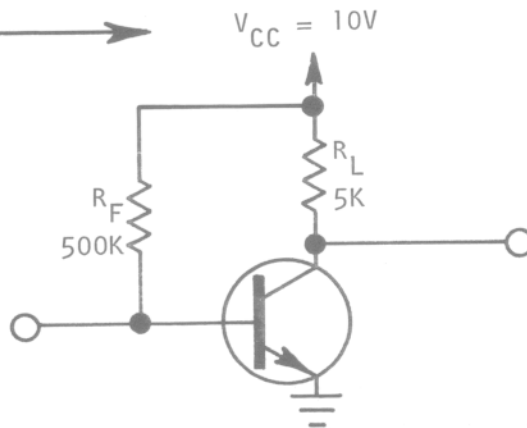


FIGURE 38-C

39 The transistors collector junction is normally reversed biased except when driven into saturation. Too large a reverse bias can result in the collector entering a condition termed _____ . This is caused by the _____ of carriers due to the high value of reverse bias.

39.1 At room temperature, there are minority carriers present in all parts of the transistor. _____ bias on the collector junction results in any minority carriers that enter the transition region, crossing the junction.


 avalanche breakdown
 acceleration or multiplication

39.2 A high value of reverse bias accelerates the carriers to great speeds. The accelerated carriers strike other atoms in the structure, freeing more carriers which are also _____ by the high reverse bias.


 reverse

39.3 The multiplication of carriers at high values of reverse bias causes the collector to go into a reverse breakdown condition.

 accelerated

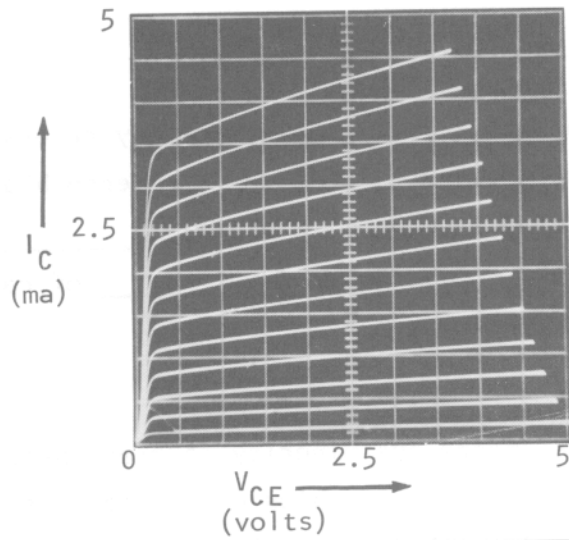

A

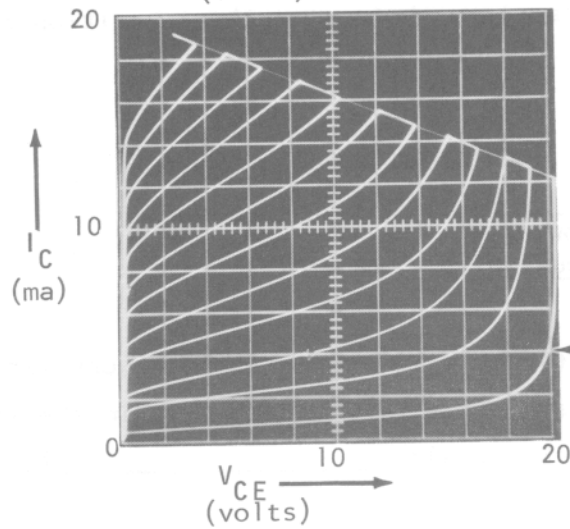

B

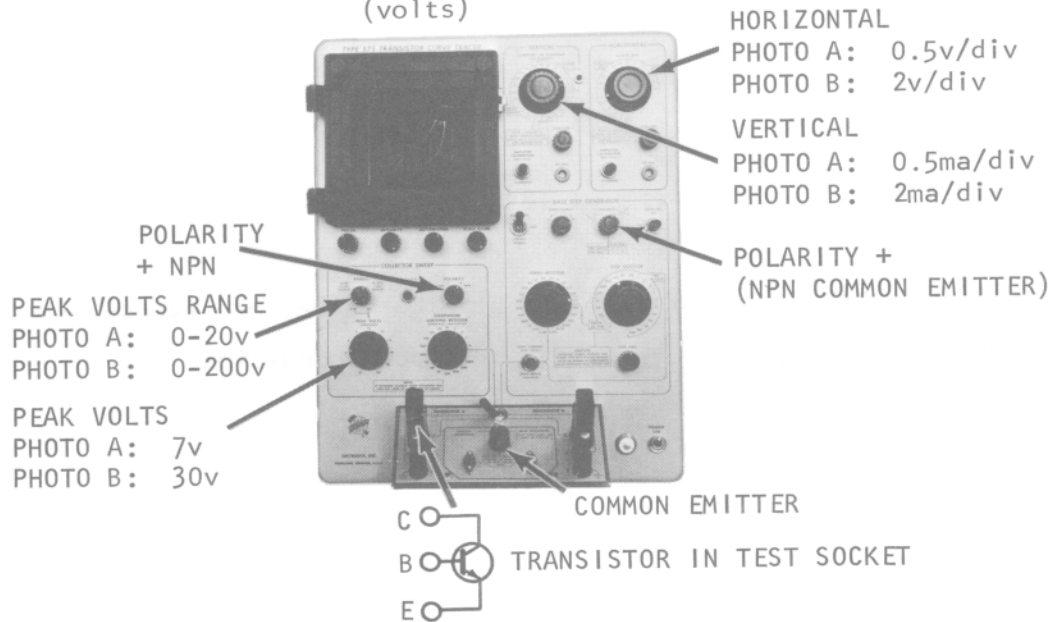


FIGURE 39

39.4 The multiplication of carriers in the reverse breakdown mode is termed avalanche. Avalanche breakdown occurs at high values of collector _____ voltage.

no answer needed

39.5 Figure 39 shows a collector family of curves in the top photo. The second photo is a collector family of curves for the same transistor, but includes the area around collector _____.

reverse

39.6 When the breakdown voltage is reached, collector current increases greatly. For zero I_B in figure 39, avalanche breakdown occurs at approximately _____ volts of V_{CE} .

avalanche breakdown

39.7 When the breakdown voltage of the collector junction is exceeded, the collector enters a condition termed _____ or reverse breakdown. This is a result of the multiplication of carriers on impact of accelerated carriers.

39.8 Avalanche breakdown in the collector of a transistor is the same as discussed for the basic diode. The orientation of the transistor can effect the voltage point at which breakdown occurs, however, due to the influence of transistor gains.

avalanche

39.9 A transistor in avalanche breakdown has _____ action occurring at the collector junction as the basic diode when in avalanche breakdown.
(the same, a different)

no answer needed

39.10** When the transistor enters _____ breakdown, the current increases greatly. This is a result of the _____ of carriers by accelerated carriers striking atoms in the structure.

the same

39.11 END OF SET

avalanche
multiplication, etc.

40 The symbol _____ indicates breakdown voltage, collector to emitter, with the base lead open; the symbol _____ indicates breakdown voltage, collector to base, with the emitter lead open; and the symbol _____ indicates breakdown voltage, collector to emitter, with a specified resistance from base to emitter. They are all given at a specified temperature.

40.1 The configuration affects the voltage point at which the transistor starts to break down. The manufacturer lists several breakdown voltages for several _____.

BV_{CEO}
 BV_{CBO}
BV_{CER}

40.2 A change in temperature will change the voltage requirements to cause breakdown. When a breakdown voltage is specified, the _____ should also be stated.

 configurations


40.3 Without injected carriers from the emitter and the reverse voltage applied directly between collector and base, the breakdown voltage is determined by the characteristics of the collector base junction (and the temperature).

 temperature

40.4 The common base configuration finds the situation in frame 40.3, if the emitter lead is open circuited. The breakdown voltage is determined by the point at which the collector diode starts to avalanche.

no answer needed

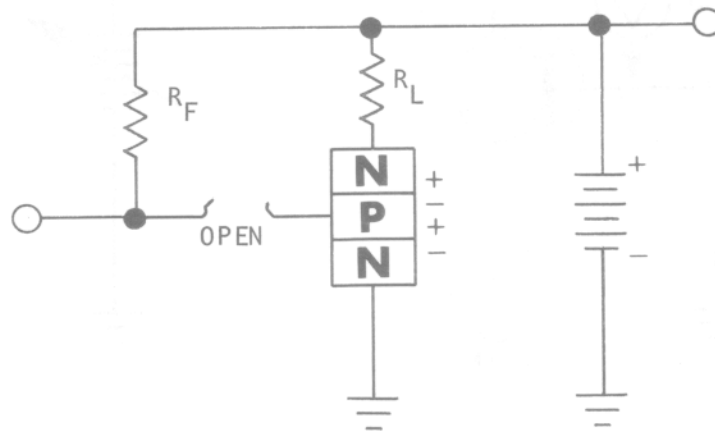
40.5 The common emitter configuration has the collector supply voltage applied across both junctions when the base lead is open circuited. Although this reverse biases the collector junction, it _____ biases the emitter junction.



no answer needed


40.6 Voltage applied from collector to emitter with the base lead open circuited will reverse bias one junction and forward bias the other. This will _____ the number of minority carriers in the base.
(increase, decrease)

forward

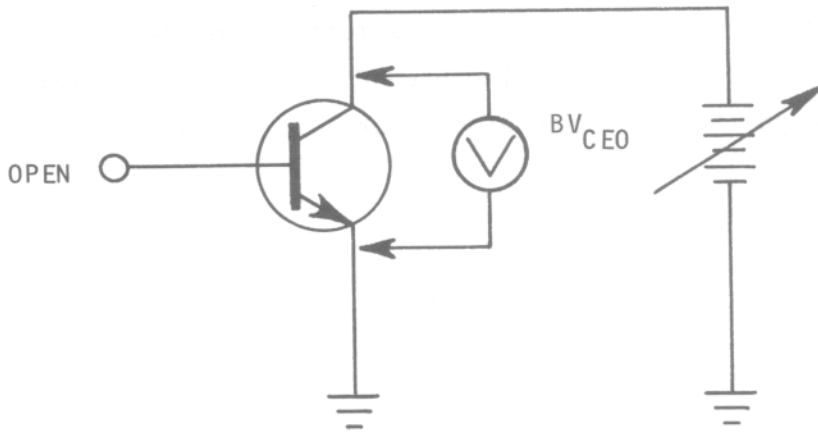


BV_{CE0}

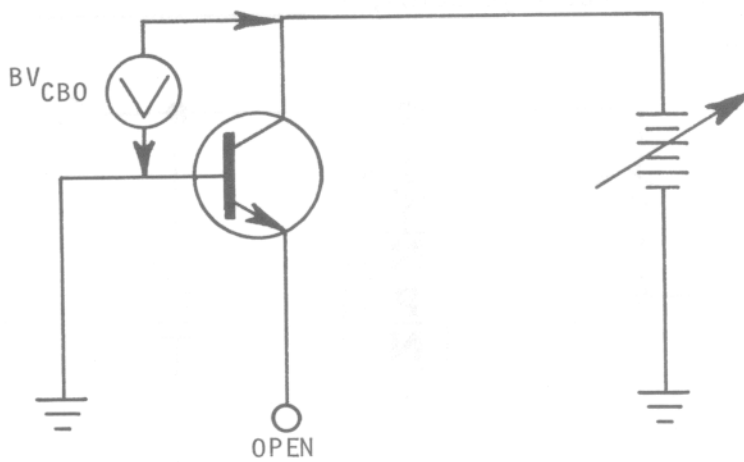BREAKDOWN VOLTAGE,
COLLECTOR TO EMITTER,
WITH THE BASE LEAD
OPEN ($I_b = 0$)



BV_{CBO}

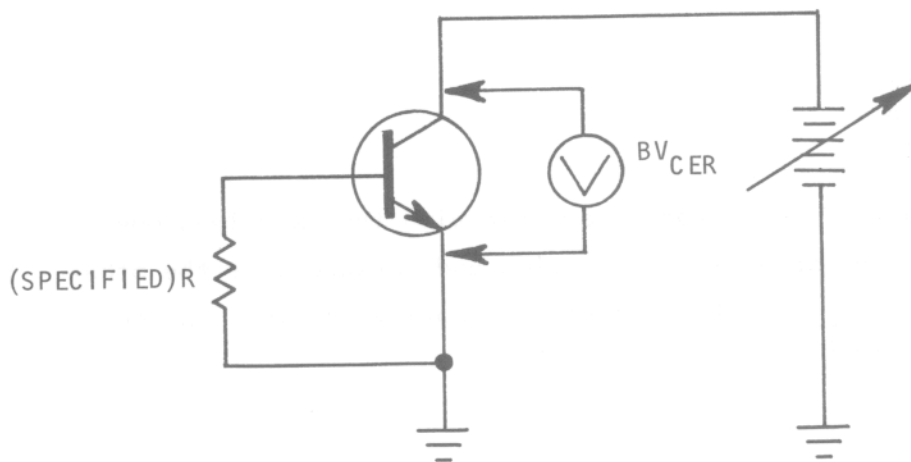BREAKDOWN VOLTAGE,
COLLECTOR TO BASE,
WITH THE EMITTER LEAD
OPEN ($I_e = 0$)



BV_{CER}

BREAKDOWN VOLTAGE,
COLLECTOR TO EMITTER,
WITH A SPECIFIED
VALUE OF RESISTOR BE-
TWEEN BASE AND EMITTER

FIGURE 40-A

40.7 The action of the emitter junction when the voltage is applied, collector to emitter rather than collector to base, reduces the voltage required to cause the transistor to enter a breakdown condition.

increase

40.8 A transistor in a common base configuration will break down at _____ collector voltage as/than a transistor in a common (a different, the same) emitter configuration.


no answer needed

40.9 Figure 40-A shows three possible configurations and the breakdown voltage symbols. BV_{CE0} indicates that the breakdown voltage was measured with the _____ lead open circuited.

a different


40.10 Biasing the transistor to allow zero base lead current, allows the measurement of the breakdown voltage whose symbol is _____.

base

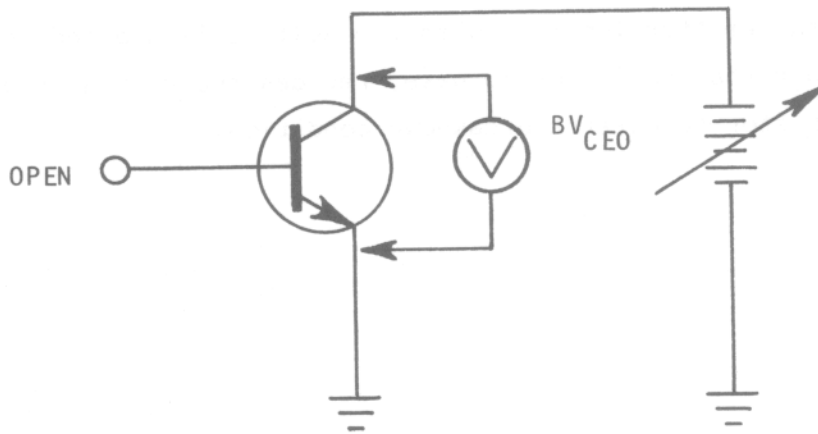


BV_{CEO}

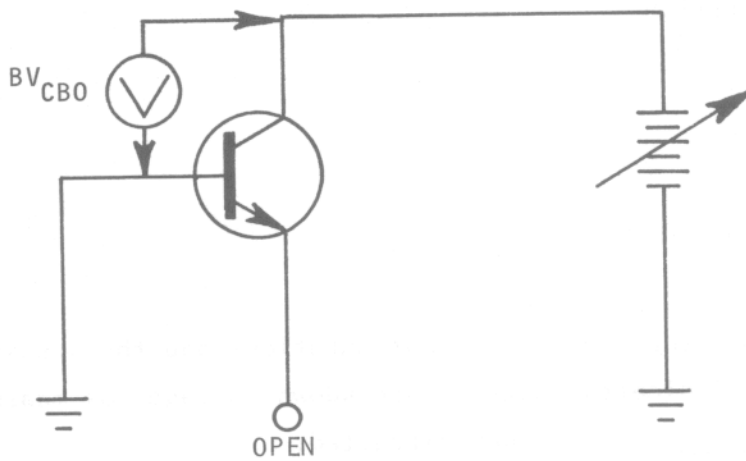BREAKDOWN VOLTAGE,
COLLECTOR TO EMITTER,
WITH THE BASE LEAD
OPEN ($I_b = 0$)



BV_{CBO}

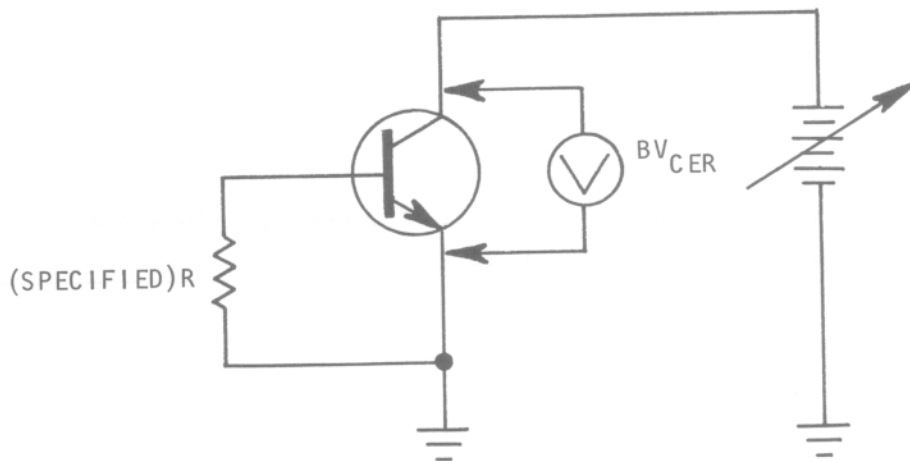BREAKDOWN VOLTAGE,
COLLECTOR TO BASE,
WITH THE EMITTER LEAD
OPEN ($I_e = 0$)



BV_{CER}

BREAKDOWN VOLTAGE,
COLLECTOR TO EMITTER,
WITH A SPECIFIED
VALUE OF RESISTOR BE-
TWEEN BASE AND EMITTER

FIGURE 40-A

40.11 BV_{CBO} is measured with the _____ lead open. BV_{CBO} breakdown occurs between collector and _____, as shown in figure 40-A.

 BV_{CEO}

40.12 BV_{CEO} is aided by the gain of the transistor and occurs at a _____ (lower, higher) voltage than BV_{CBO} for the same transistor.




emitter
base

40.13 BV_{CER} is an attempt to specify a breakdown voltage that will be closer to the conditions encountered in an actual circuit. BV_{CER} is given with a specified value of resistance between _____ and _____ as shown in figure 40-A.

lower

40.14 On a common emitter collector family of curves, the open base lead condition is represented by the _____ base current curve.

base
emitter

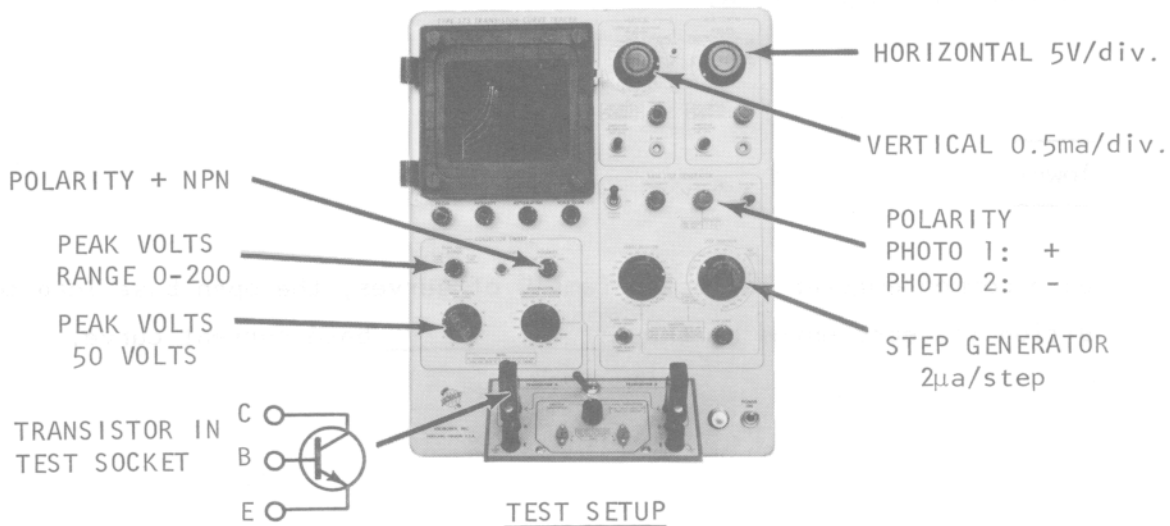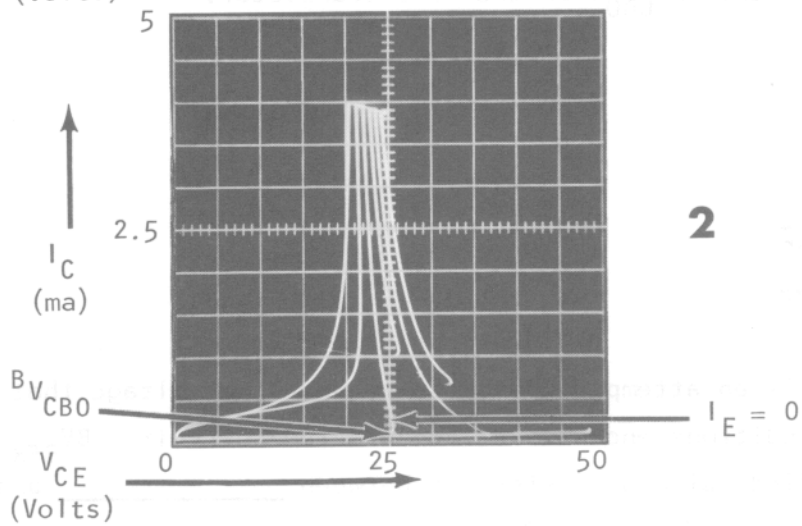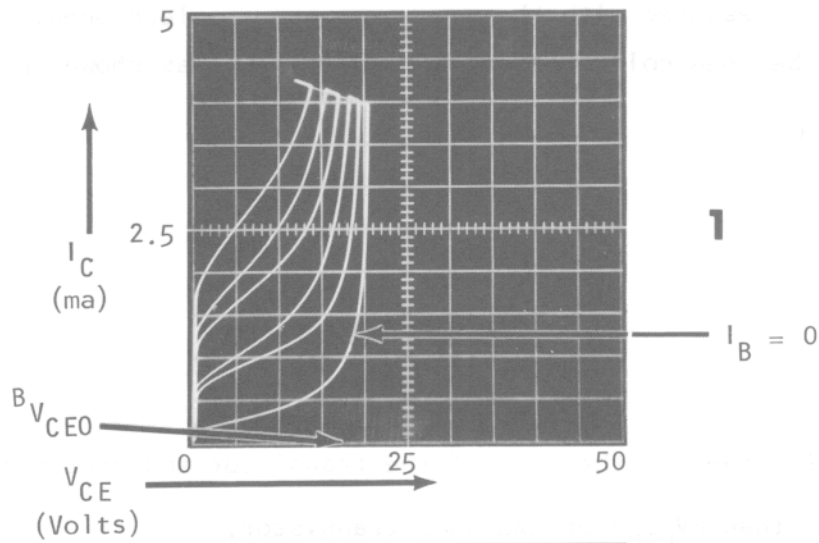

TEKTRONIX TYPE 575 TRANSISTOR-CURVE TRACER
 PHOTOS 1 AND 2 TAKEN WITH TYPE C-12 OSCILLOSCOPE CAMERA
 FIGURE 40-B

40.15 On a common emitter collector family of curves, reverse biasing the emitter base junction sufficiently to reduce emitter current to zero is the same as opening the _____ lead.

zero

40.16 In figure 40-B (photo 2), the line marked $I_E = 0$ indicates that sufficient reverse base current is applied to reduce the emitter current to zero. This is the same as opening the _____ lead.




emitter

40.17 Figure 40-B (photo 1) is a collector family of curves for a common emitter configuration. The sharp increase in current at high values of V_{CE} indicates _____ breakdown is occurring.

emitter

40.18 In figure 40-B (photo 2), reverse biasing current is being applied to reduce emitter current. BV_{CBO} is measured on the _____ emitter current curve.

avalanche

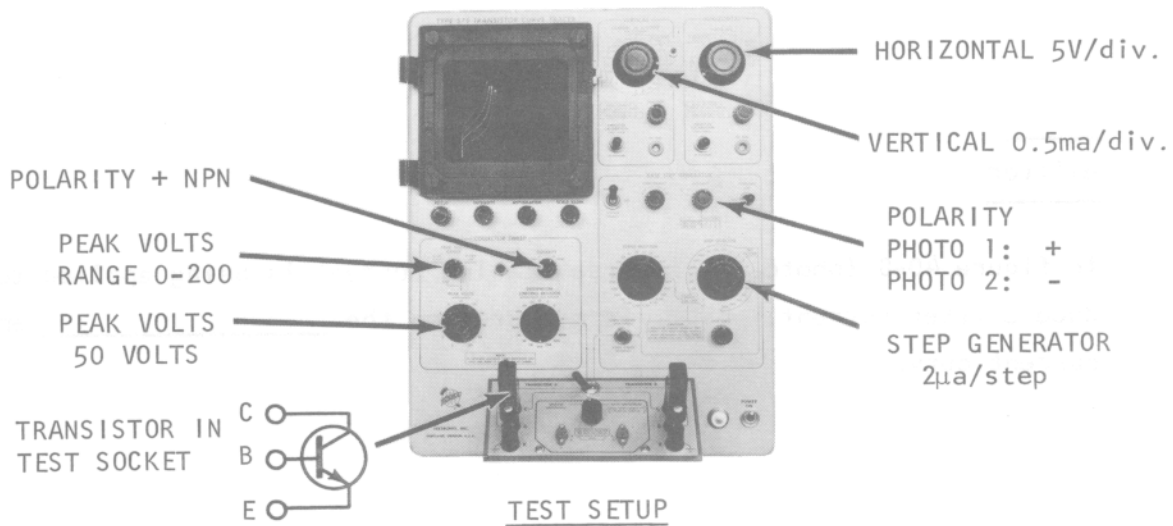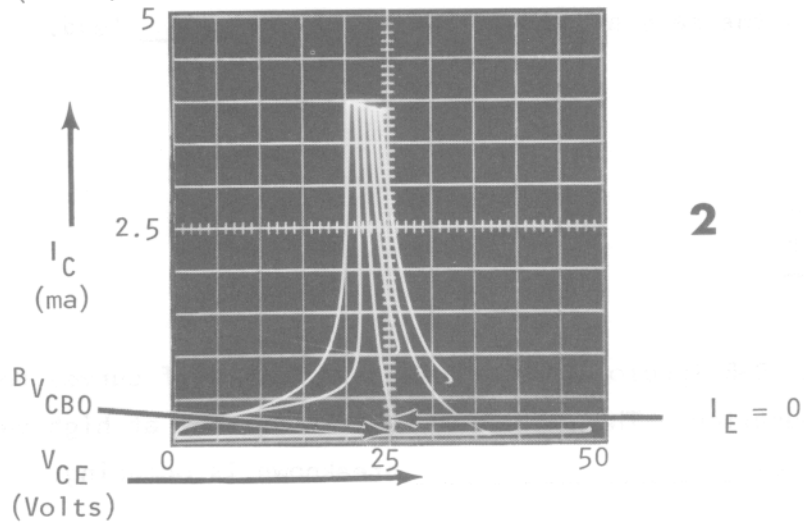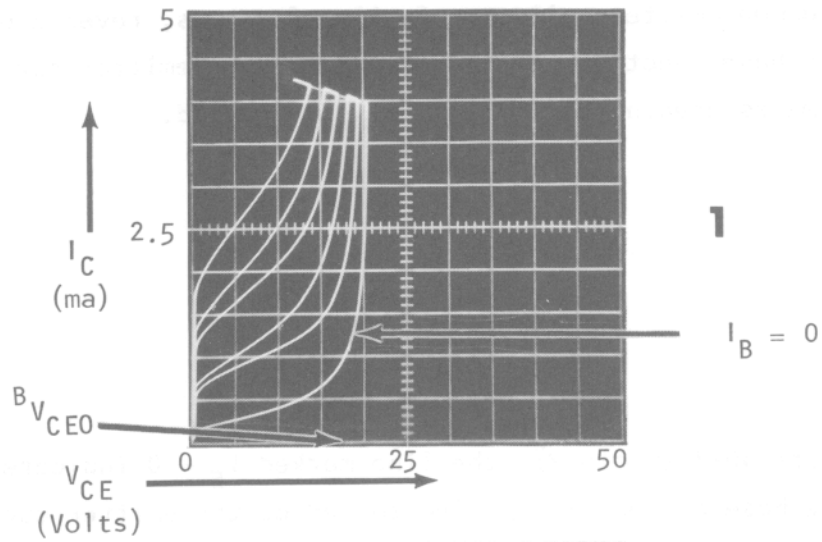

TEKTRONIX TYPE 575 TRANSISTOR-CURVE TRACER
 PHOTOS 1 AND 2 TAKEN WITH TYPE C-12 OSCILLOSCOPE CAMERA
 FIGURE 40-B

40.19 In figure 40-B (photo 2), BV_{CBO} is measured on the base current curve that is marked $I_E = 0$. This curve indicates that sufficient reverse base current has been applied to oppose any minority or leakage current and simulates an open _____ circuit.

zero

40.20** The symbol BV_{CEO} indicates _____ ;
the symbol BV_{CBO} indicates _____ ;
the symbol BV_{CER} indicates _____ .
_____ should be stated when these values are given.
(Note: Define the symbols above.)

emitter

40.21 END OF SET

breakdown voltage collector to emitter with the base lead open
breakdown voltage collector to base with the emitter lead open
breakdown voltage collector to emitter with a specified resistor from
base to emitter
temperature

41 Maximum power handling capabilities of the transistor are limited by the maximum temperature that the junctions can reach without harm, the surrounding air temperature and the total _____ from junction to surrounding air.

41.1 As with the basic diode, the transport of carriers results in carriers changing energy bands and giving off energy in the form of _____ and _____.

thermal resistance

41.2 The majority of the energy given off at the transistor's junctions is in the form of heat. The more power dissipated at the junction, the more _____ is given off.

heat
light

41.3 The power ($I \times E$) dissipated by a junction results in the generation of heat and raises the junction _____ above that of its surroundings.

heat (energy)

41.4 The junction can reach an operating temperature at which it is harmed if too much power is dissipated. Moving some of the generated heat away from the junction allows _____ power to be dissipated.
(more, less)

temperature

41.5 The collector junction dissipates the greater amount of power of the two junctions in most cases. The smaller amount of heat will be generated at the _____ junction.

more

41.6 The transistor is normally mounted in a case and this offers opposition to the transfer of _____ from the junction to the surrounding air.

emitter

41.7 The greater the amount of heat that can be moved from the junction to the surrounding air, the more power can be dissipated for the same surrounding air (ambient) temperature. The lower the surrounding air (ambient) temperature, the _____ power a given transistor can dissipate.
(more, less)

heat

41.8 The difference between the ambient (surrounding air) temperature and the maximum temperature at which the junction can operate, is the allowable rise in junction temperature due to dissipating power.

more

41.9 The opposition offered in the path of heat transfer from the junction to the surrounding air is termed "thermal resistance". The higher the thermal resistance, the (more, less) heat will be transferred.

no answer needed

41.10 The maximum allowable junction temperature (T_{JMAX}), the ambient temperature (T_A), and the opposition offered in the path of heat transfer from the junction to surrounding air which is termed _____, limits the maximum power dissipation.

less

41.11 Total thermal resistance may be the sum of several individual thermal resistances. For example, thermal resistance junction to the case and thermal resistance from the case to the surrounding air would add to give _____ thermal resistance, junction to ambient.



thermal resistance

41.12** Thermal resistance, maximum _____ (T_{JMAX}), and
_____ (T_A) limit the amount of power
the transistor can dissipate.

total

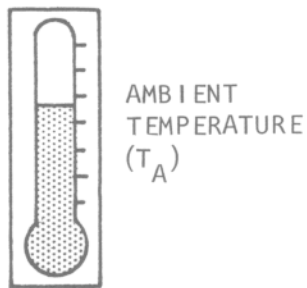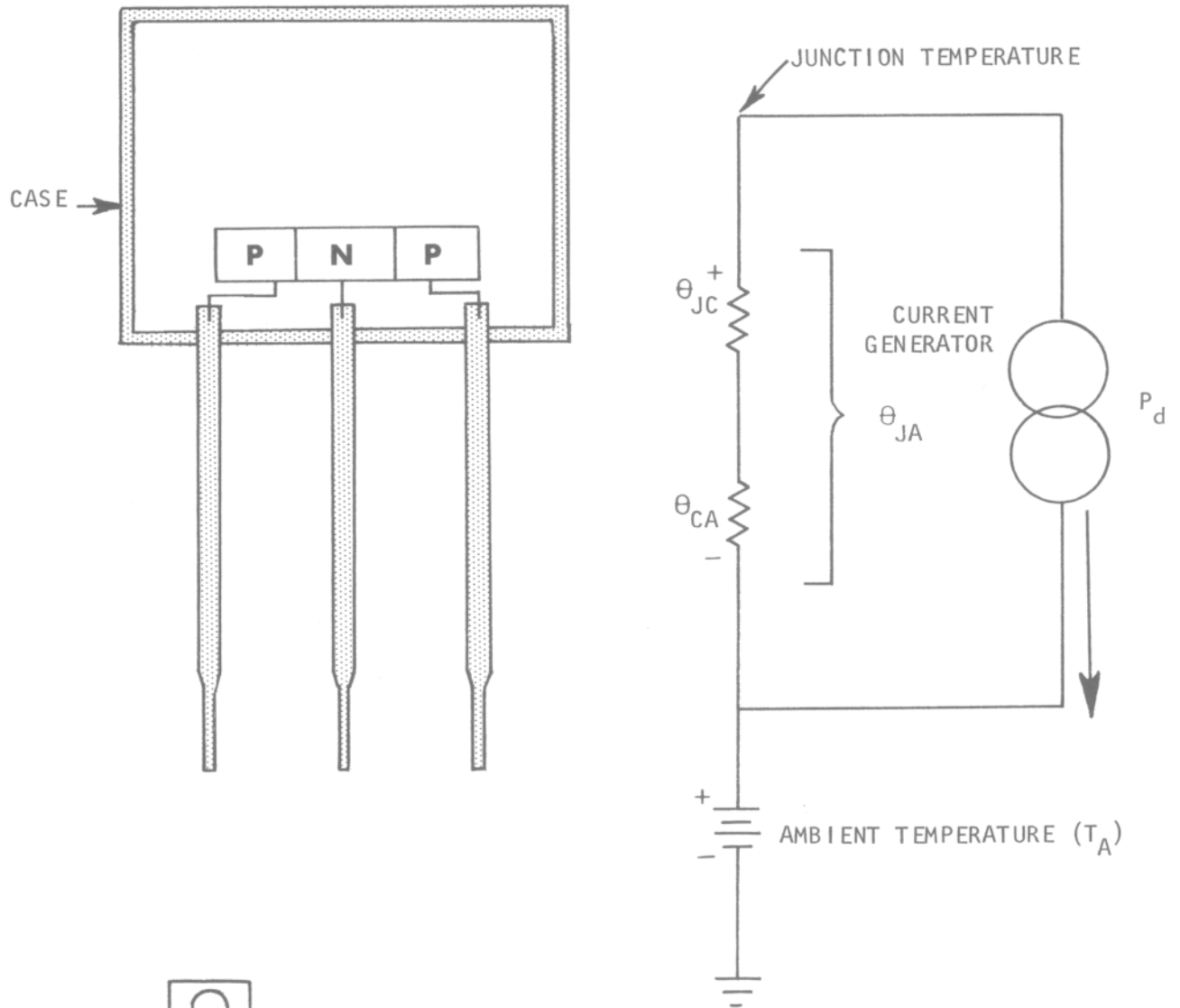41.13 END OF SET

junction temperature
ambient (surrounding air) temperature



<u>THERMAL</u>	=	<u>ELECTRICAL EQUIVALENT</u>
AMBIENT TEMPERATURE	=	VOLTAGE
THERMAL RESISTANCE	=	RESISTANCE
POWER DISSIPATION	=	CURRENT
JUNCTION TEMPERATURE	=	VOLTAGE

THERMAL TO ELECTRICAL ANALOGY
FIGURE 42

42 The symbol for total thermal resistance, junction to ambient, is _____ . When dealing with a transistor that is not connected thermally to an external heat sink, _____ (#) thermal resistances add to give the total and their symbols are _____ and _____ . Thermal resistance is expressed in _____ .

42.1 Thermal resistance is given the symbol θ . The subscripts indicate between what two points the opposition to heat transfer exists. θ_{JA} indicates thermal resistance, _____ to ambient (surrounding air).




θ_{JA}
two
 θ_{JC}
 θ_{CA}
degrees centigrade per watt ($^{\circ}\text{C}/\text{W}$)

42.2 When the transistor is in a case and depends on radiation of heat to the surrounding air from the case, two thermal resistances add to give total thermal resistance. Thermal resistance, junction to case (θ_{JC}), and thermal resistance, case to ambient (θ_{CA}), add to give _____ .

junction

42.3 Figure 42 shows the transistor and the thermal considerations in electrical terms. Thermal resistance is analogically compared with electrical resistance, power dissipation at the junction with electrical current, and ambient temperature with electrical _____ .

total thermal resistance (θ_{JA})

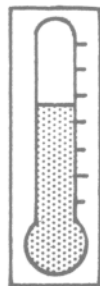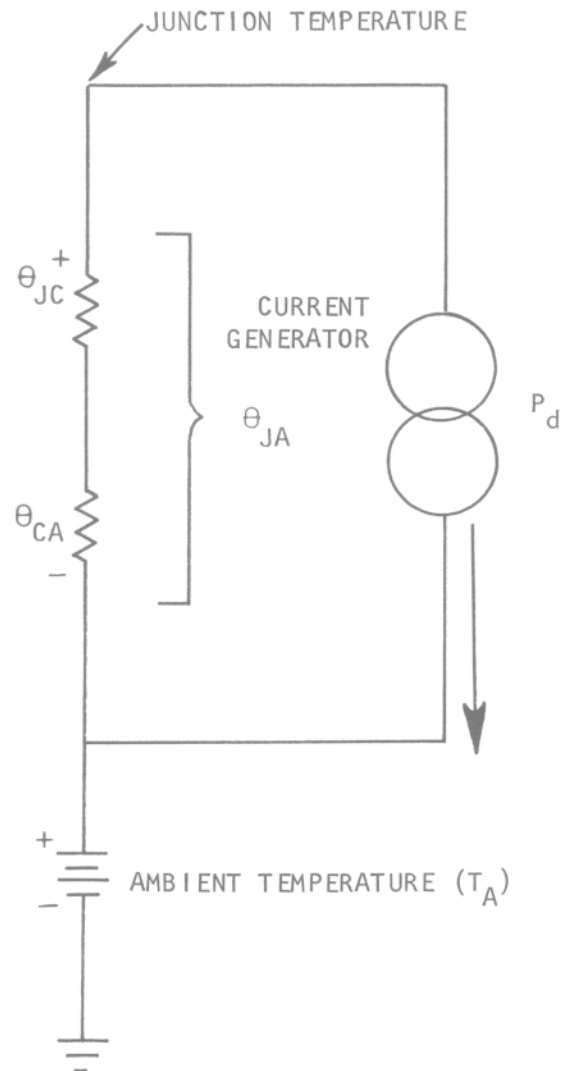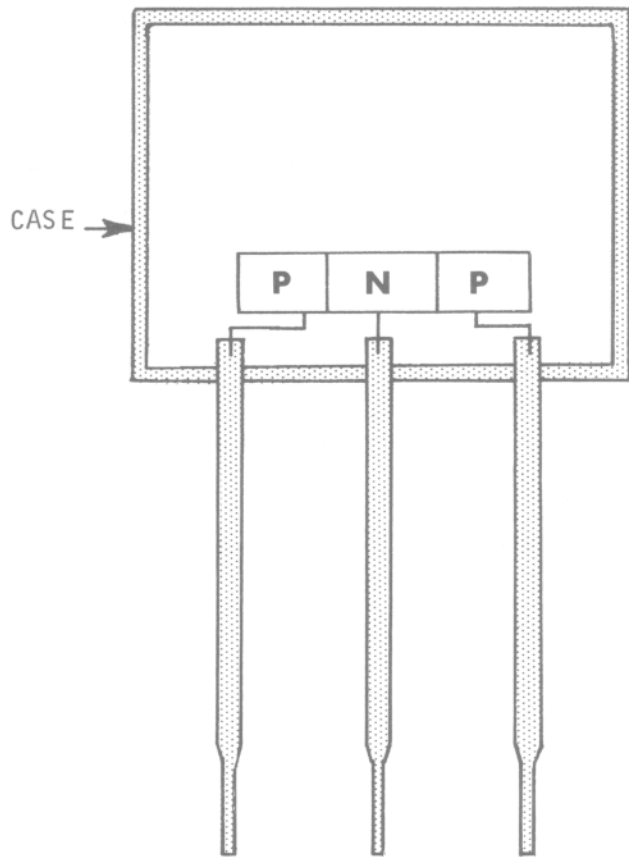

AMBIENT
TEMPERATURE
(T_A)

<u>THERMAL</u>	=	<u>ELECTRICAL EQUIVALENT</u>
AMBIENT TEMPERATURE	=	VOLTAGE
THERMAL RESISTANCE	=	RESISTANCE
POWER DISSIPATION	=	CURRENT
JUNCTION TEMPERATURE	=	VOLTAGE

THERMAL TO ELECTRICAL ANALOGY

FIGURE 42

42.4 θ_{JC} indicates thermal resistance, junction to _____, and θ_{CA} indicates thermal resistance, case to _____.

voltage

42.5 The product of thermal resistance total and the power dissipation will give a temperature (voltage in the analogy) that will add to _____ temperature which is also analogically compared to a voltage and this sum gives junction temperature.

case
ambient

42.6 Thermal resistance is expressed in degrees centigrade per watt ($^{\circ}\text{C}/\text{W}$). This indicates the rise in junction temperature with power dissipation at the junction in degrees centigrade per _____.

ambient

42.7 Connecting the transistor thermally to an external heat sink (such as the chassis) is termed "heat sinking" the transistor. Heat sinking will _____ total thermal resistance.
(raise, lower)

watt

42.8 Total thermal resistance ($^{\circ}\text{C}/\text{W}$) times the power dissipation (P_d in watts) gives the rise in junction temperature (ΔT_J). The rise in junction temperature added to the ambient temperature (T_A) gives the operating temperature of the junction (T_J). $P_d \theta_{JA} + T_A = \underline{\hspace{2cm}}$



lower

42.9** Thermal resistance (θ_{JC}) added to thermal resistance (θ_{CA}) gives thermal resistance (θ_{JA}) when no separate heat sink is involved. Thermal resistance is expressed in $^{\circ}\text{C}/\underline{\hspace{2cm}}$.

operating temperature of the junction (T_J)

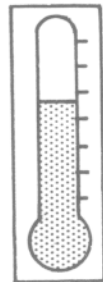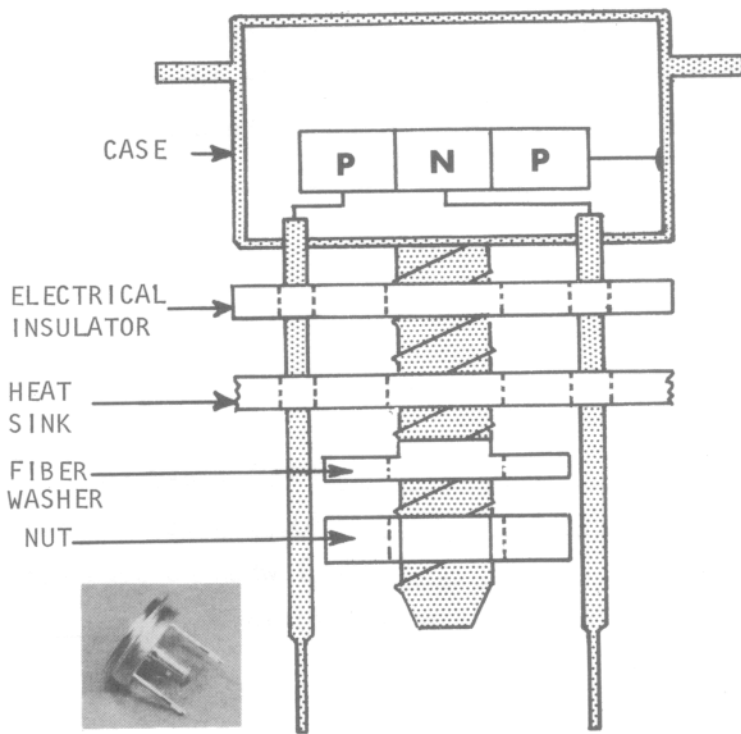
42.10 END OF SET

junction to case
case to ambient
junction to ambient
watt



AMBIENT TEMPERATURE (T_A)

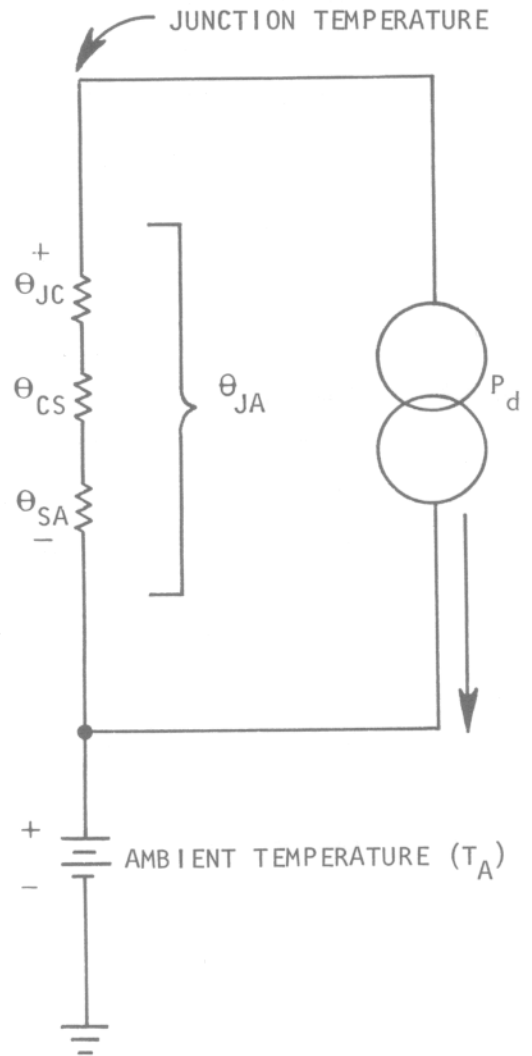NOTE: When a heat sink is used, θ_{CS} and θ_{SA} replace θ_{CA} . The sum of θ_{CS} and θ_{SA} is always much lower than θ_{CA} .



JUNCTION POWER DISSIPATION = CURRENT
 OPPOSITION TO HEAT TRANSFER = RESISTANCE
 AMBIENT TEMPERATURE = VOLTAGE
 JUNCTION TEMPERATURE = VOLTAGE

INSULATING WASHER	TYPICAL THERMAL RESISTANCE, (θ_{CS}) IN °C/W	
	DRY	W/SILICON LUBRICANT
NONE	0.2	0.1
TEFLON	1.45	.8
MICA	0.8	0.4
ANODIZED ALUMINUM	0.4	0.35

THERMAL TO ELECTRICAL ANALOGY WHEN USING A SEPARATE HEAT SINK

FIGURE 43

43 When a heat sink is used to increase power dissipating capabilities, _____ (#) thermal resistances add to give θ_{JA} . Their symbols are _____, _____, and _____. _____ lubricant will reduce θ_{JA} .

43.1 Using a separate heat sink replaces the rather large thermal resistance, case to ambient (θ_{CA}), with two thermal resistances whose sum is much less than θ_{CA} . θ_{CA} has a _____ value than the thermal resistances that replace it when a heat sink is used.

 θ_{JC}
 θ_{CS}
 θ_{SA}
silicone



43.2 Higher power handling transistors generally have the collector connected directly to the case to aid in heat transfer. This, in most cases, requires that the case be insulated electrically from the heat sink. The electrical insulator used should have good _____ conductivity.

 larger

43.3 Figure 43 shows a power transistor with an external heat sink and the equivalent thermal considerations in an electrical analogy. Once again power dissipation (P_d) is expressed analogically as electrical

_____.

 heat (thermal)

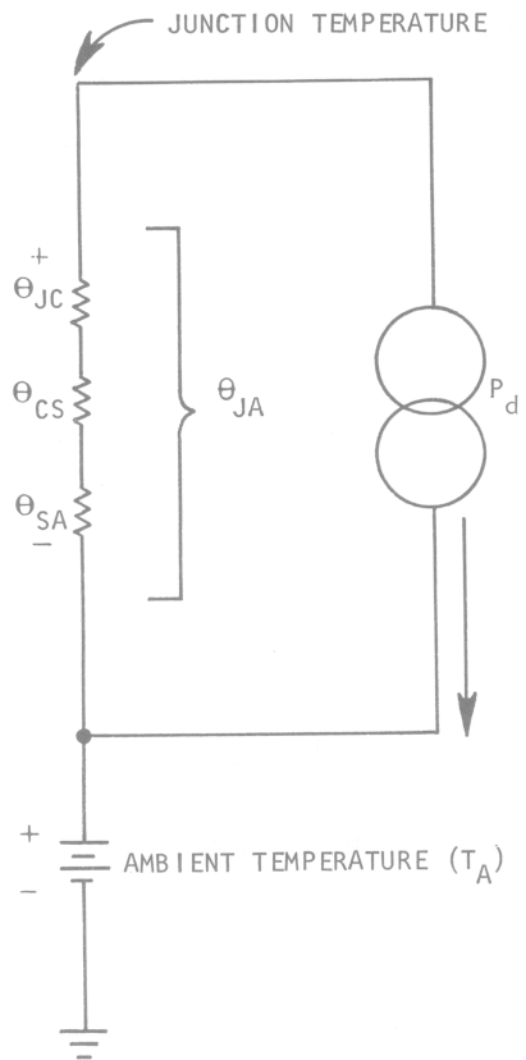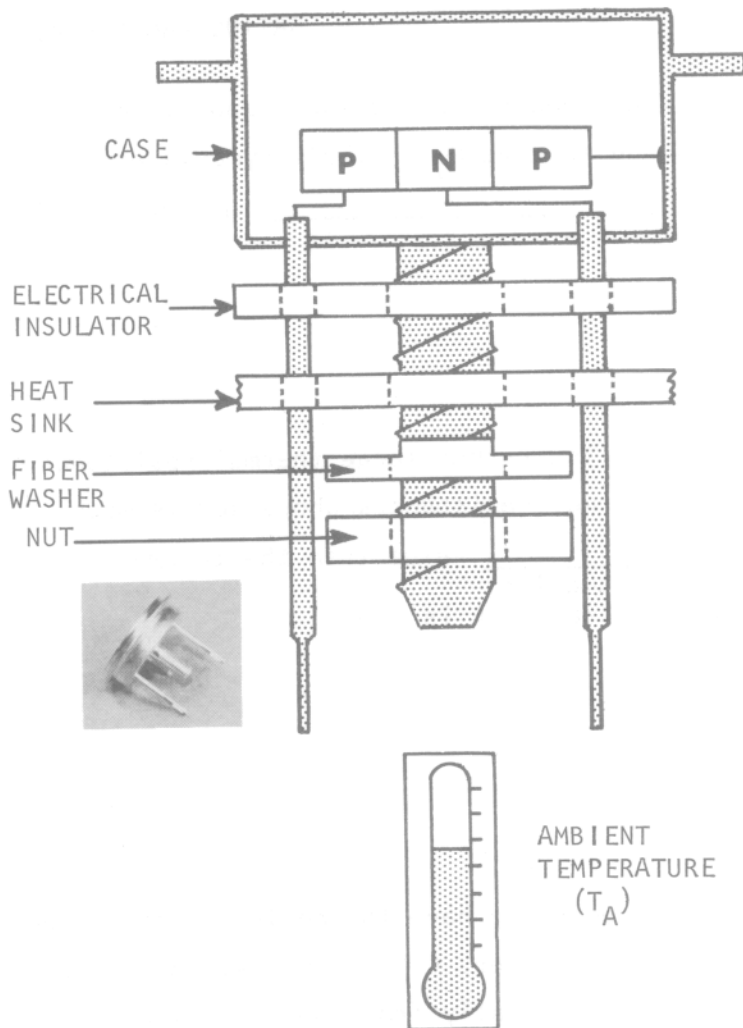

NOTE: When a heat sink is used, θ_{CS} and θ_{SA} replace θ_{CA} . The sum of θ_{CS} and θ_{SA} is always much lower than θ_{CA} .

JUNCTION POWER DISSIPATION = CURRENT
 OPPOSITION TO HEAT TRANSFER = RESISTANCE
 AMBIENT TEMPERATURE = VOLTAGE
 JUNCTION TEMPERATURE = VOLTAGE

INSULATING WASHER	TYPICAL THERMAL RESISTANCE, (θ_{CS}) IN °C/W	
	DRY	W/SILICON LUBRICANT
NONE	0.2	0.1
TEFLON	1.45	.8
MICA	0.8	0.4
ANODIZED ALUMINUM	0.4	0.35

THERMAL TO ELECTRICAL ANALOGY WHEN USING A SEPARATE HEAT SINK

FIGURE 43

43.4 There is opposition to the transfer of heat from the case to the heat sink. This thermal resistance is given the symbol _____ as shown in figure 43.

current

43.5 θ_{CS} is the thermal resistance, case to heat sink. θ_{SA} is thermal resistance, _____ to ambient. $\theta_{JC} + \theta_{CS} + \theta_{SA} = \underline{\hspace{2cm}}$.



 θ_{CS}

43.6 The sum of the three thermal resistances is total thermal resistance when an external heat sink is used. The product of total thermal resistance and the power dissipation gives the rise in junction temperature above _____ (T_A). (Each individual thermal resistance contributing to the temperature rise)

heat sink
 θ_{JA}

43.7 θ_{CS} and θ_{SA} replace θ_{CA} when an external heat sink is used. Coating the insulating washer (between the case and the heat sink) with silicone lubricant will _____ θ_{CS} as shown in figure 43.
(increase, decrease)

ambient temperature

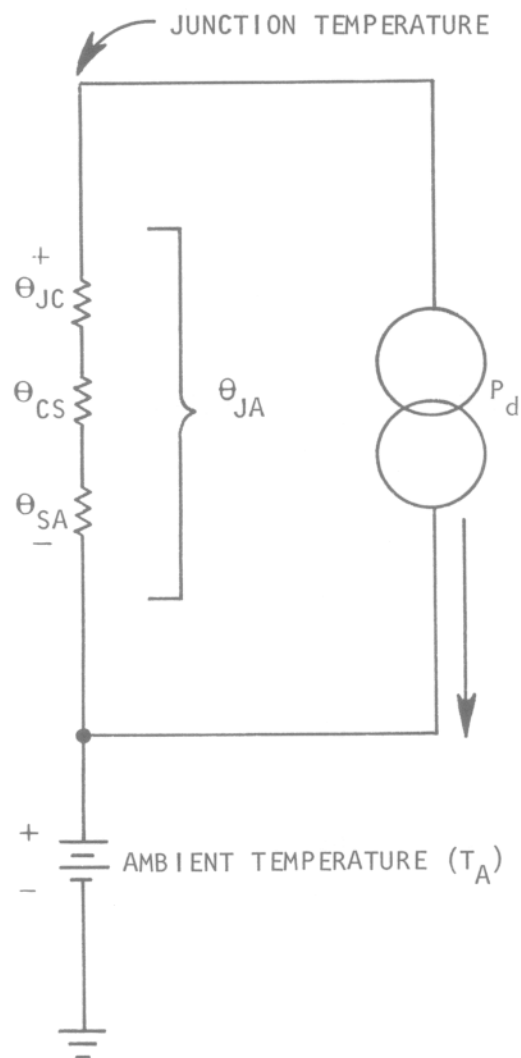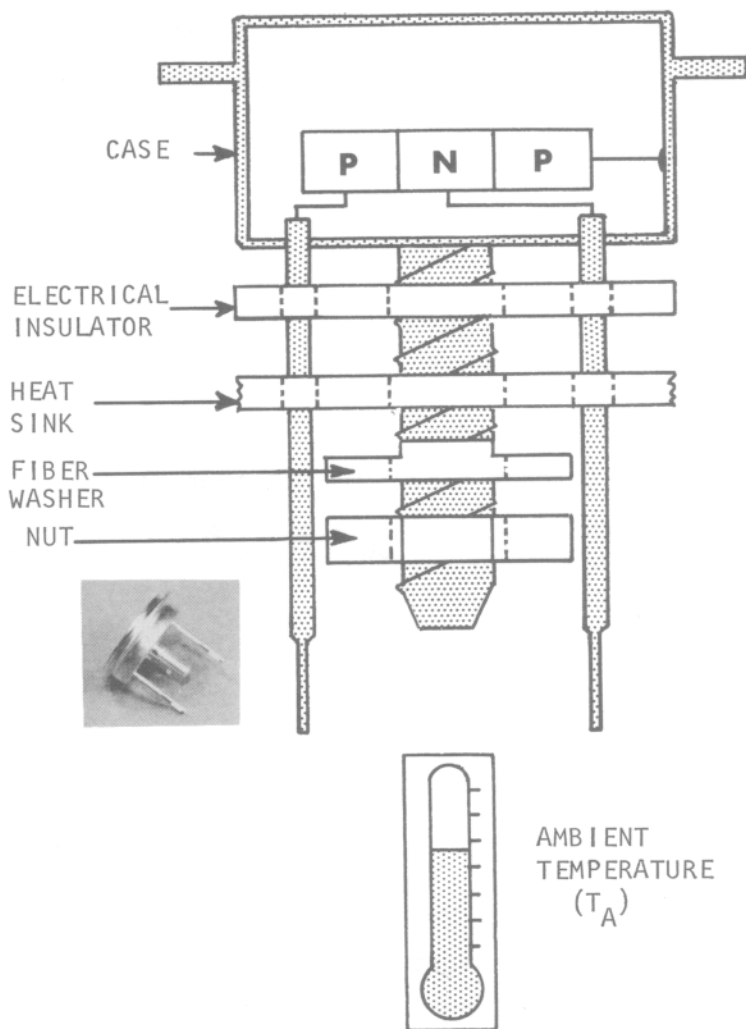

NOTE: When a heat sink is used, θ_{CS} and θ_{SA} replace θ_{CA} . The sum of θ_{CS} and θ_{SA} is always much lower than θ_{CA} .

JUNCTION POWER DISSIPATION = CURRENT
 OPPOSITION TO HEAT TRANSFER = RESISTANCE
 AMBIENT TEMPERATURE = VOLTAGE
 JUNCTION TEMPERATURE = VOLTAGE

INSULATING WASHER	TYPICAL THERMAL RESISTANCE, (θ_{CS}) IN °C/W	
	DRY	W/SILICON LUBRICANT
NONE	0.2	0.1
TEFLON	1.45	.8
MICA	0.8	0.4
ANODIZED ALUMINUM	0.4	0.35

THERMAL TO ELECTRICAL ANALOGY WHEN USING A SEPARATE HEAT SINK

FIGURE 43

43.8 As shown in figure 43, silicone lubricant will reduce θ_{CS} even if no insulating washer is used. Reducing θ_{CS} also reduces _____.

decrease

43.9** The sum of θ_{JC} , _____ and _____, is the total thermal resistance when an external heat sink is used. _____ lubricant reduces the total thermal resistance.

 θ_{JA}

43.10 END OF SET

 θ_{CS}
 θ_{SA}
silicone

44

GIVEN:

$$\theta_{SA} = 3.2^\circ\text{C/watt}$$

$$\theta_{JC} = 1.2^\circ\text{C/watt}$$

$$\theta_{CS} = 0.6^\circ\text{C/watt}$$

$$T_A = 50^\circ\text{C}$$

$$T_{J\text{max}} = 150^\circ\text{C}$$

The maximum steady state power the transistor can dissipate is _____.

44.1

The sum of the individual thermal resistances is the total thermal resistance. $\theta_{JC} + \theta_{CS} + \theta_{SA} = \theta_{JA} =$ _____ $^\circ\text{C/watt}$ with the values given in frame 44.

20 watts

44.2

Given an ambient temperature (T_A) of 50°C , and a maximum allowable junction temperature ($T_{J\text{max}}$) of 150°C , the allowable change in junction temperature due to power dissipation is found by subtracting T_A from $T_{J\text{max}}$. $T_{J\text{max}} - T_A =$ allowable $\Delta T_J =$ _____ $^\circ\text{C}$.

—

5

—

44.3

The product of power dissipation and total thermal resistance must not exceed the maximum allowable change in junction temperature. Rearranging formula:

$$P_d^{\text{max}} \theta_{JA} = T_{J\text{max}} - T_A$$

$$P_d(\text{max}) = \frac{\quad?}{\quad}$$

100

44.4

Since $P_d(\max) = \frac{T_{J\max} - T_A}{\theta_{JA}}$

$P_d(\max)$ for the problem in frame 44 = $\frac{150^\circ\text{C} - 50^\circ\text{C}}{5^\circ\text{C/watt}} = \underline{\hspace{2cm}} ?$

$\frac{T_{J\max} - T_A}{\theta_{JA}} = \underline{\hspace{2cm}}$

44.5

To find the maximum allowable power dissipation for a given ambient temperature, divide the allowable change in junction temperature by the total thermal resistance. $P_d(\max) = \underline{\hspace{2cm}}$

20 watts

44.6**

$\theta_{JC} = 2.1^\circ\text{C/watt}$

$\theta_{CS} = 0.8^\circ\text{C/watt}$

$\theta_{SA} = 5.1^\circ\text{C/watt}$

$T_A = 70^\circ\text{C}$

$T_{J\max} = 150^\circ\text{C}$


$P_d(\max) = \underline{\hspace{2cm}} ?$

$\frac{T_{J\max} - T_A}{\theta_{JA}}$

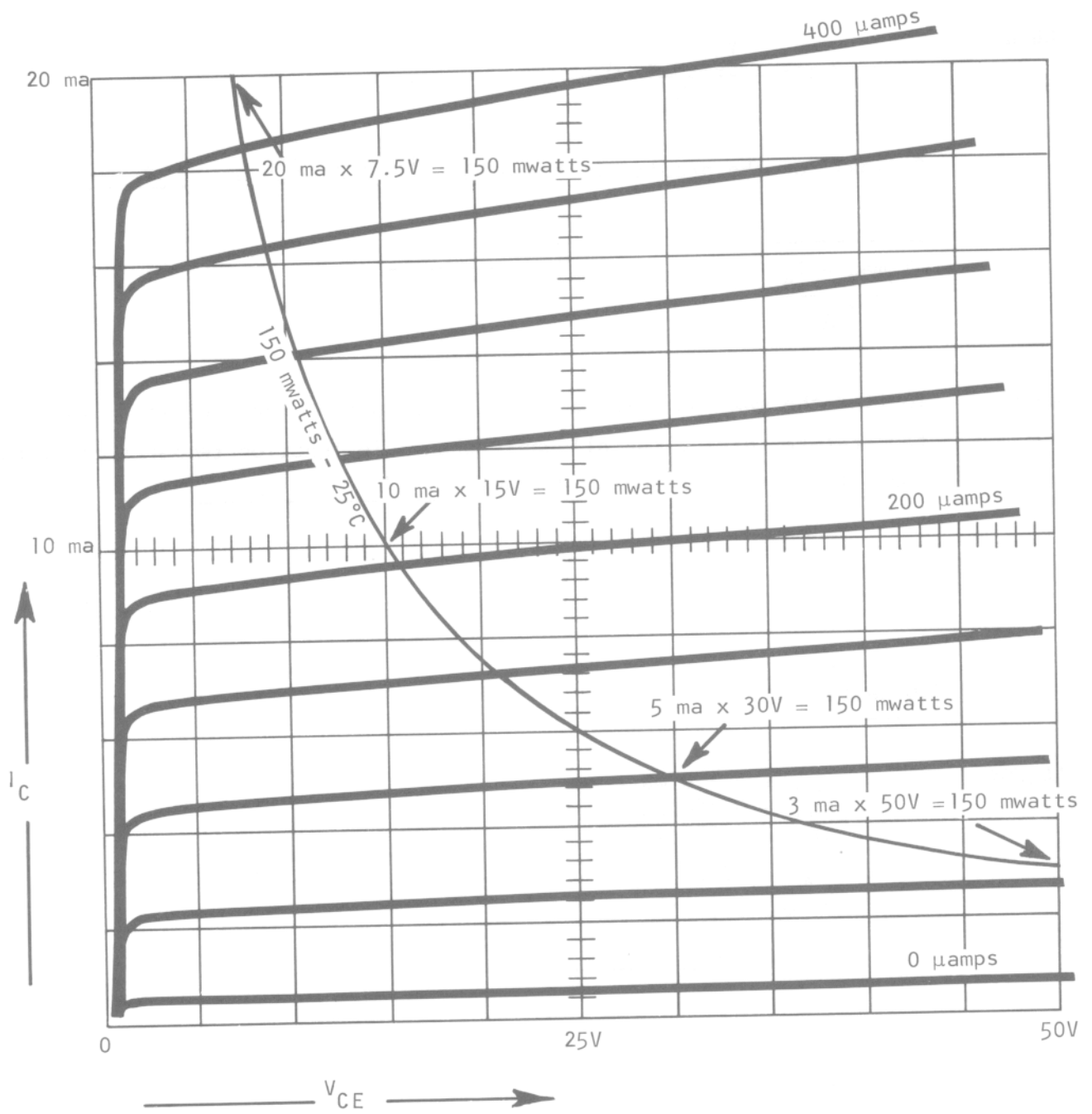44.7

END OF SET

$P_d(\max) = \frac{T_{J\max} - T_A}{\theta_{JA}} = \frac{150^\circ\text{C} - 70^\circ\text{C}}{2.1^\circ\text{C/watt} + 0.8^\circ\text{C/watt} + 5.1^\circ\text{C/watt}} = 10 \text{ watts}$




COLLECTOR FAMILY OF CURVES WITH A MAXIMUM
 POWER CURVE - 150 mwatts - 25°C

FIGURE 45

- 45 The maximum power curve is constructed by connecting all points of _____ on the collector family of curves. For maximum safe output power, the load line should be _____ to the maximum power curve on the collector family of curves. For maximum current and power, the load line also intersects the maximum _____ point. _____ (T_A) must be specified.
- 45.1 When maximum power dissipation is given by the manufacturer or calculated using thermal resistance, it can be plotted on the collector family of curves as shown in figure 45. The curve that results connects all points of maximum power dissipation at a given _____.
- _____
- maximum power
tangent
current
temperature
- 45.2 The maximum power dissipation of the transistor in figure 45 is 150 mwatts at a temperature of 25°C. At a higher temperature, the maximum power dissipation is _____ than this value.
(less, more)
- _____
- temperature
- 45.3 In figure 45, the area below and to the left of the maximum power curve is the safe operating area at 25°C. The area above and to the right of the maximum power curve is the un-_____ area.

less

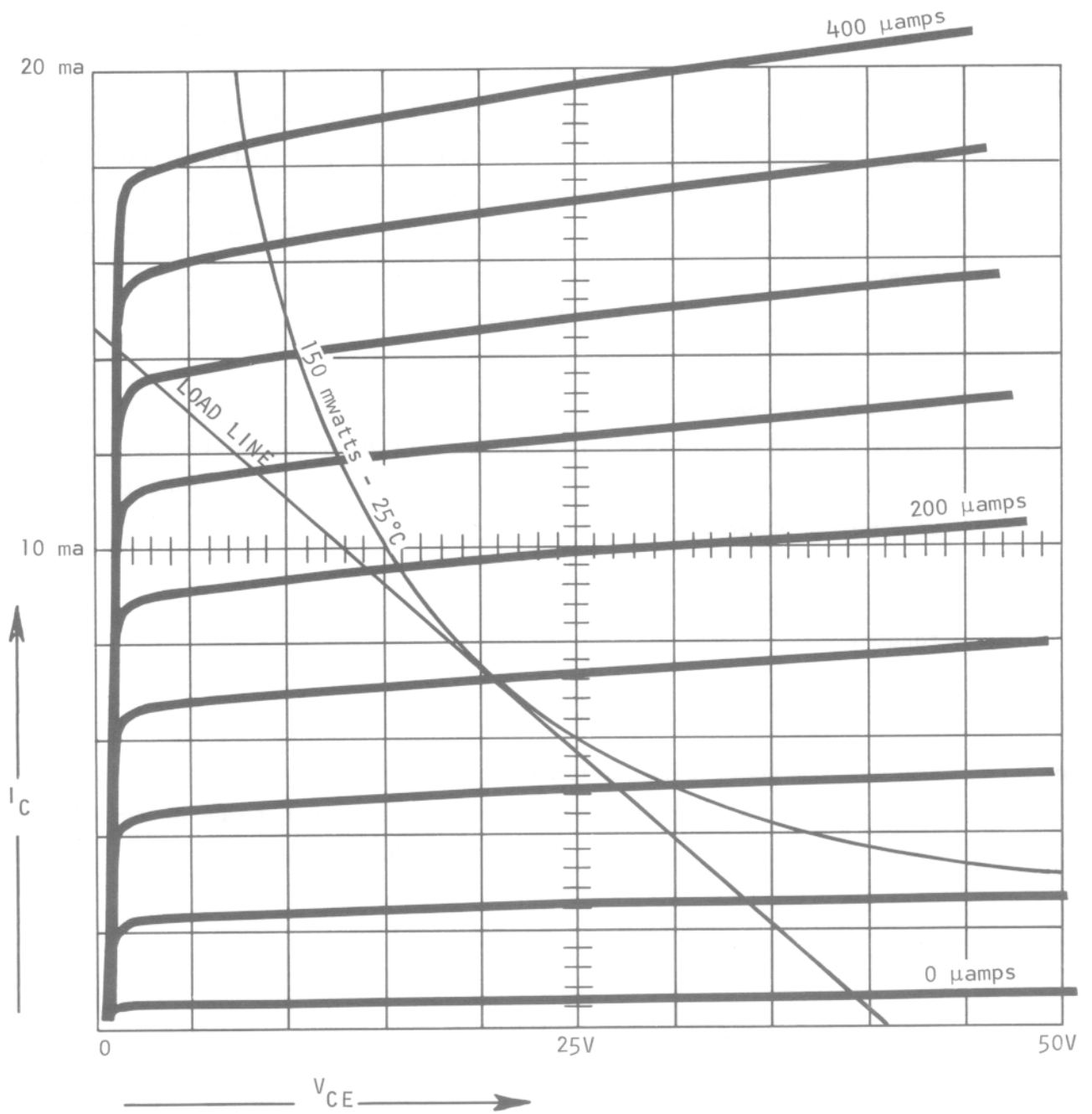

COLLECTOR FAMILY OF CURVES WITH MAXIMUM
POWER CURVE AND LOAD LINE FOR MAXIMUM
LINEAR POWER

FIGURE 45-A

45.4 A load line that is tangent to the maximum power curve and passes through the linear region of the curves will handle maximum _____ power.


safe

45.5 Figure 45-A shows a load line constructed tangent to the maximum power curve for maximum linear power. This load line _____ allow maximum possible current swing.
(will, will not)

linear

45.6 To allow maximum current swing along with maximum power, the load line should intersect the maximum rated forward _____ point and be tangent to the maximum _____ curve.

will not

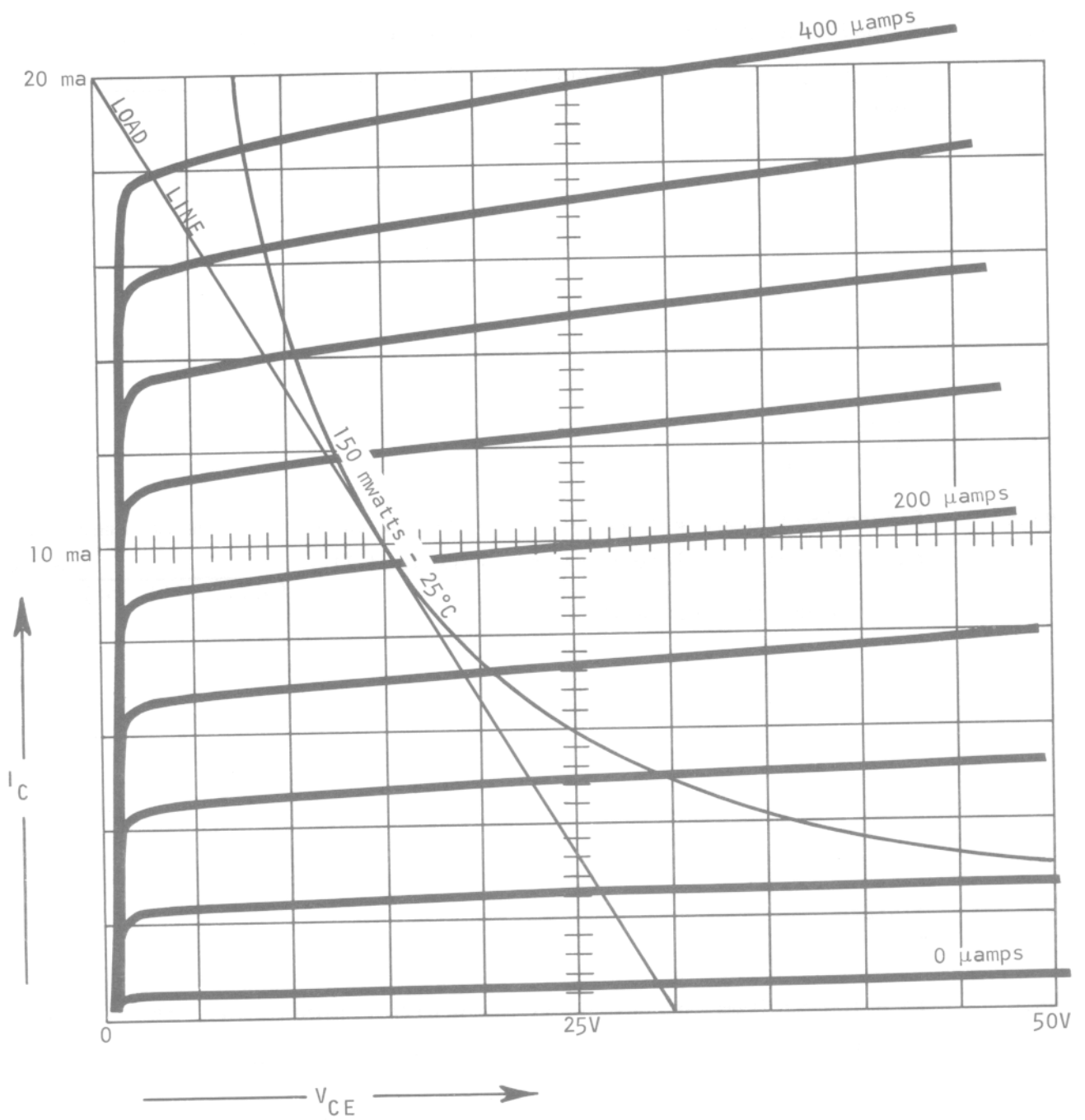

COLLECTOR FAMILY OF CURVES WITH MAXIMUM
 POWER CURVE AND LOAD LINE FOR MAXIMUM POWER
 WITH MAXIMUM POSSIBLE CURRENT SWING

FIGURE 45-B

45.7 Figure 45-B shows a load line tangent to the maximum power curve. The transistor in figure 45-B is rated at a maximum forward current of 20 mamps. The load line is designed to give maximum power and _____ swing.

current
power

45.8 The load line for maximum current should be constructed from the maximum current point to a point _____ to the maximum power curve.


current

45.9** The maximum power curve is constructed by connecting all the maximum _____ points together. A load line allowing maximum current swing and maximum power should intersect the _____ point and be _____ to the maximum power curve.

tangent

45.10 END OF SET

power
maximum current
tangent

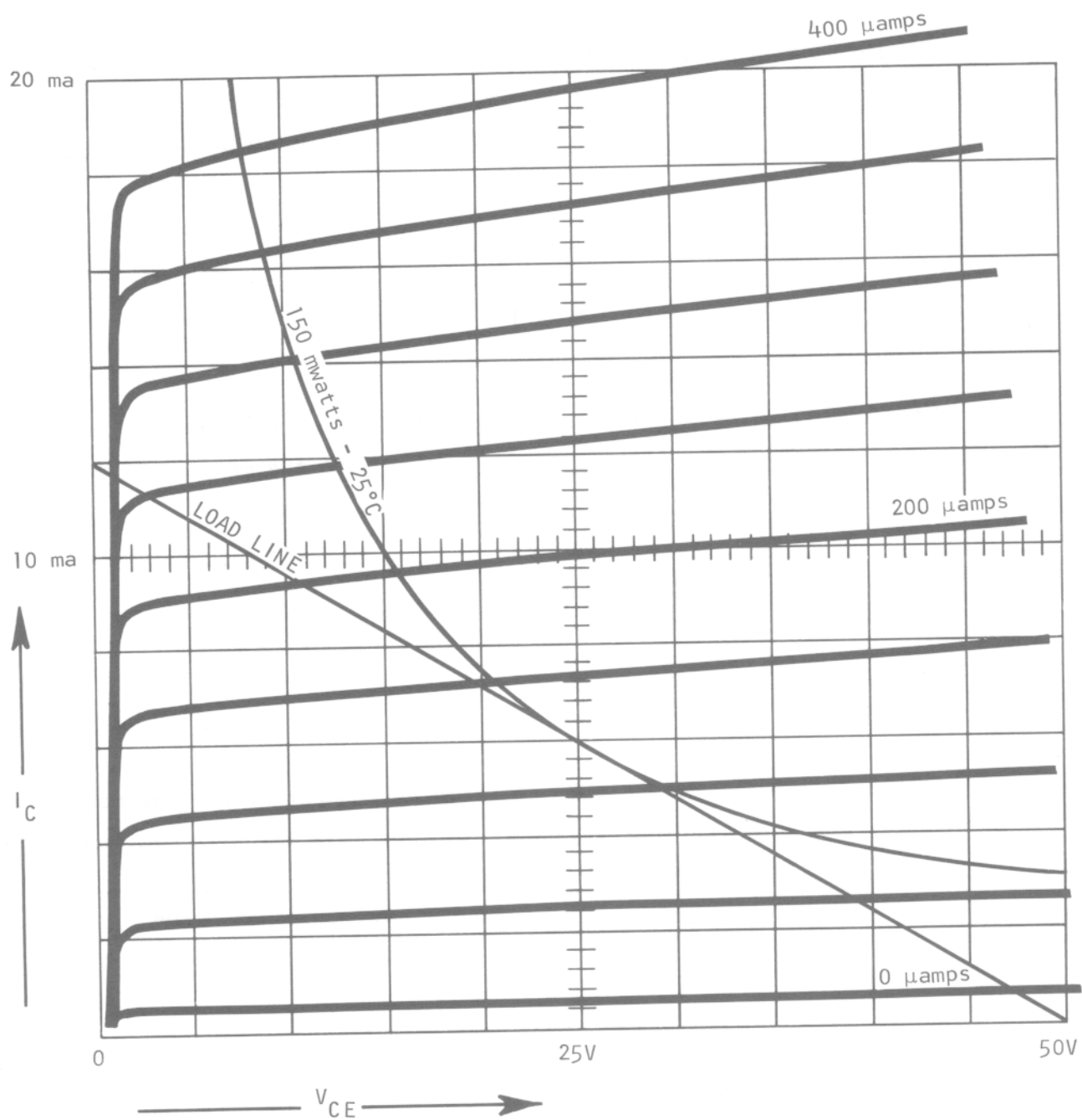

COLLECTOR FAMILY OF CURVES WITH A MAXIMUM
POWER CURVE AND A LOAD LINE FOR MAXIMUM POWER
WITH MAXIMUM POSSIBLE VOLTAGE SWING

FIGURE 46

46 The load line, to insure maximum power and maximum possible voltage swing, should be _____ to the maximum power curve and intersect the maximum _____ point on the collector family of curves.

46.1 To insure maximum power, the load line should be tangent to the maximum power curve. To insure maximum possible voltage swing, the load line should also intersect the maximum _____ point.

tangent
voltage

46.2 The maximum power curve is constructed by joining together all points on the collector family of curves equal to maximum power. The area to the left and below the maximum power curve is the _____ area.

voltage

46.3 In figure 46, the load line is tangent to the maximum power curve. The maximum voltage of this transistor is 50 volts. The load line is constructed for maximum power and maximum voltage swing.

safe

46.4 The load line must not cross the maximum power dissipation curve. It is, therefore, placed _____ to the maximum power dissipation curve.

voltage

46.5 To insure maximum possible voltage swing, the load line should also intersect the maximum _____ point.

tangent

46.6** The load line for maximum power and voltage swing should be _____ to the maximum power curve and intersect the maximum _____ point.

voltage

46.7 END OF SET

tangent
voltage

47 Only a small amount of power is dissipated when the transistor is at the extremes of its operation. The extremes of the transistor's operation are termed _____ and _____. The most power is dissipated in the "_____" region between these two points (also known as the transient region).

47.1 A transistor in saturation has very little voltage across it, but a relatively large current flowing which results in a small power dissipation.

saturation
cut-off
active

47.2 At the opposite extreme of its operation, the transistor is "cut-off" and very little current is flowing. Although there may be a large voltage across the transistor at cut-off, there is very little _____ dissipation.

no answer needed

47.3 At the two extremes of its operation, the transistor dissipates very little power. The power is dissipated between _____ and _____.

power

47.4 The area between saturation and cut-off is termed the active region. The majority of the power is dissipated in the _____ region.

saturation
cut-off

47.5 The active region is also termed the transient region. The transistor dissipates the greatest amount of power in the _____ or _____ region.

active

47.6** Very little power is dissipated at the extremes of the transistor's operation. The power is dissipated mainly in the _____ or _____ region.

active
transient

47.7 END OF SET

active
transient

48 The transistor, acting as a switch, _____ have its load line
 (may, may not)
 cross over the maximum power curve if it has its resting states at the
 extremes of the transistor's operation (saturation and cut-off) and not
 in the active region. This will allow the switching of _____
 (less, more)
 power than if the transistor rests in the active region.

48.1 With the transistor operating as a switch in either the on or off con-
 dition, it may have its resting states at saturation and cut-off. Very
 little power is dissipated at _____ and _____.


 may
 more

48.2 When the transistor is switched from saturation to cut-off or vice-versa,
 it will make an excursion through the _____ region.

 saturation
 cut-off

48.3 Power will be dissipated during the excursion through the active region.
 The greater the amount of time spent in the active region, the
 _____ power will be dissipated.
 (more, less)

 active or transient

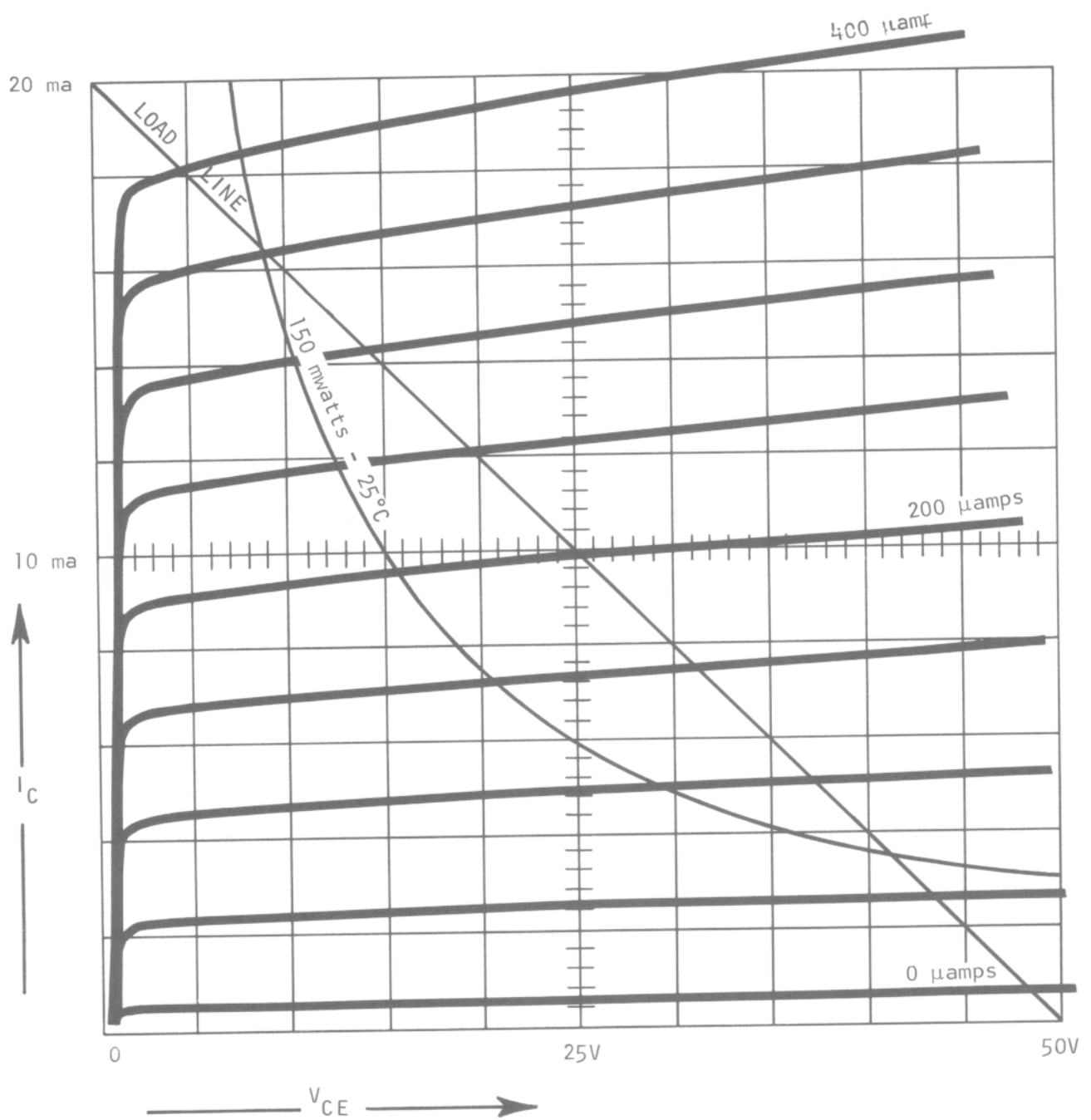

at 25°C $\left\{ \begin{array}{l} B_{VCE0} = 50V \text{ (maximum voltage)} \\ I_C(\text{max}) = 20\text{ma (maximum forward current)} \end{array} \right.$

TOTAL POSSIBLE POWER SWING = 1,000 mwatts

$$I_C(\text{max}) \times V_{CE}(\text{max}) = 20\text{ma} \times 50V = 1,000 \text{ mwatts}$$

FIGURE 48

48.4 If the transistor does not spend too much time in the active region during its excursion and does not enter the active region too many times per second, the load line can be constructed between the maximum _____ and _____ points as shown in figure 48.

more

48.5 Operating the transistor as a switch between saturation and cut-off allows _____ transistor power dissipation (during the transition) (greater, less) than when the transistor has a resting state in the active region.


current
voltage

48.6 Figure 48 shows the construction of a load line for a transistor switch operating between cut-off and _____. This allows _____ output power than when the transistor rests in the active (greater, less) region.

greater

48.7 The total possible power excursion in figure 48 is 1,000 mwatts since the transistor can make a transition from approximately 50V to 20ma and vice-versa. The maximum transistor power dissipation when the transistor rests in the active region is 150 mwatts.

saturation
greater

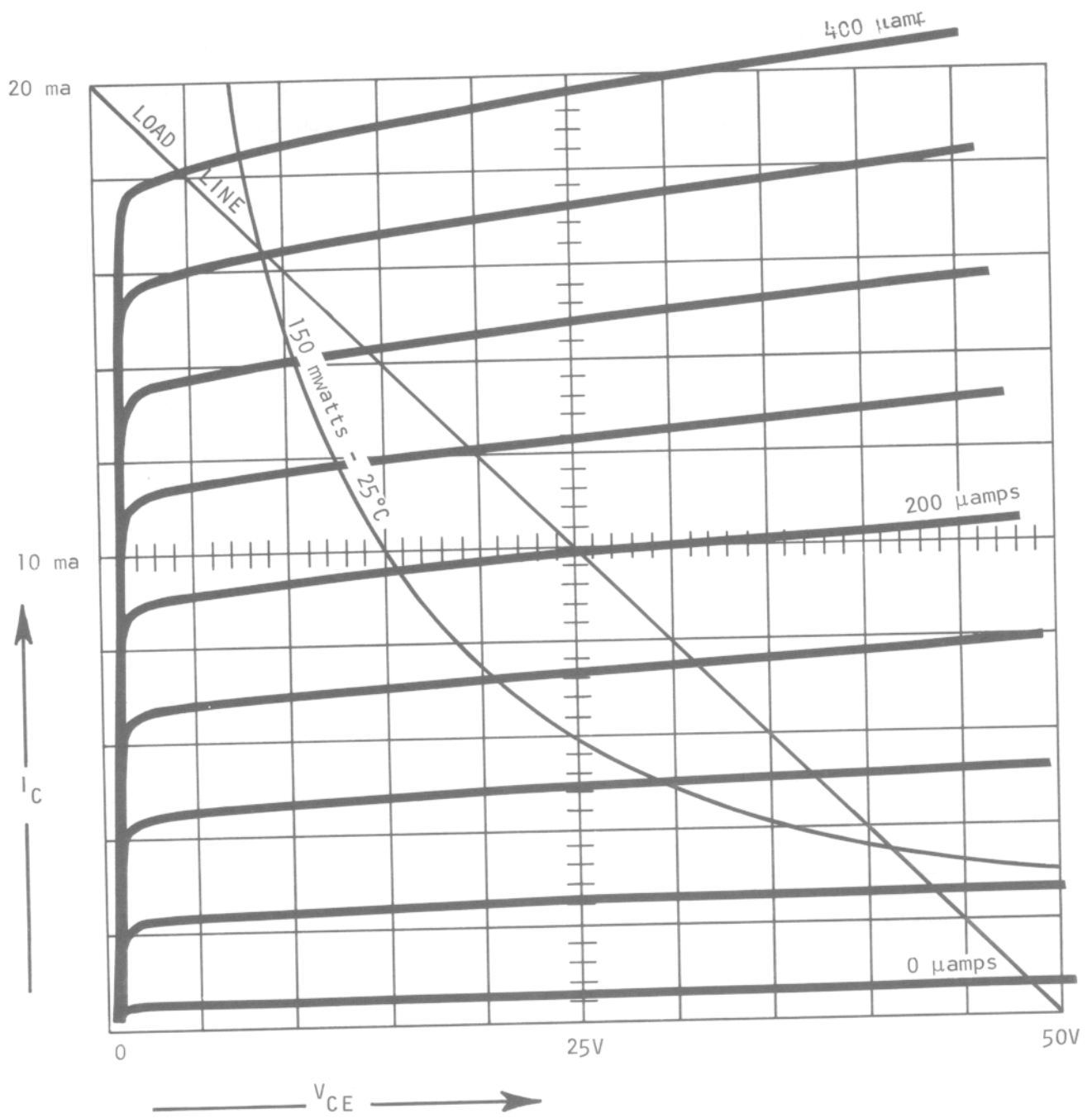

at 25°C $\left\{ \begin{array}{l} B_{VCE0} = 50V \text{ (maximum voltage)} \\ I_C(\text{max}) = 20\text{ma (maximum forward current)} \end{array} \right.$

TOTAL POSSIBLE POWER SWING = 1,000 mwatts
 $I_C(\text{max}) \times V_{CE}(\text{max}) = 20\text{ma} \times 50V = 1,000 \text{ mwatts}$

FIGURE 48

48.8 If the transistor in figure 48 had a resting state in the active region, the load line _____ cross over the 150 mwatt curve.
(could, could not)

no answer needed

48.9 Operating in the cut-off to saturated switching mode allows greater power dissipation (and as a result, greater output power), as long as the transistor does not spend too much time in the _____ region.

could not

48.10** Operating the transistor as a switch with one of its resting states in the active region _____ allow the load line to cross the maximum steady state power curve. This allows _____ power dissipation and output power than the cut-off to saturated mode of operation for the same switching rate.

active or transient

48.11 END OF SET

does not
less

49 Operating a transistor in the cut-off to saturated switching mode has the advantage of low resting state power dissipation, but has the disadvantage of limiting _____ rate because of the larger _____ in the base as a result of driving the transistor into saturation.

49.1 When the transistor has its resting states at saturation and cut-off, there is little power dissipated when the transistor is at rest. When the transistor is saturated, the collector junction is _____ biased.

repetition
stored charge

49.2 The collector becomes forward biased when the transistor enters saturation. The collector injects carriers into the base when it enters _____ and becomes _____ biased.

forward

49.3 The collector, becoming forward biased and injecting carriers into the base, results in an increase in the number of carriers stored in the base of the transistor. This increase in base stored charge is a result of the transistor entering _____.

saturation
forward

49.4 On entering saturation, the stored charge in the base of the transistor is increased. The deeper the transistor is driven into saturation, the greater the _____ in the base.

saturation

49.5 As with the basic diode, the stored charge must be removed before the transistor may be turned off. It takes a period of time to remove the _____.

stored charge

49.6 Since it takes a period of time to remove the stored charge, the total switching time of the transistor is _____ when the transistor rests in saturation rather than the active region.
(increased, decreased)

stored charge

49.7 An increase in total switching time of the transistor will _____ the maximum number of times the transistor can switch between its resting states per second.
(increase, decrease)

increased

49.8 The maximum repetition rate of the transistor is the maximum number of times per second that it can switch from one resting state to the other and back again. Maximum repetition rate is reduced when the transistor is driven into _____.

decrease

49.9 The deeper the transistor is driven into saturation, the lower the maximum _____.

saturation

49.10** The disadvantage of operating in the cut-off to saturated switching mode, is the increase in the _____ in the base which limits maximum _____.

repetition rate

49.11 END OF SET

stored charge
repetition rate

50 In dealing with a transistor switch, the turn on time (t_{on}) is equal to the sum of _____ and _____ and the turn off time (t_{off}) is equal to the sum of _____ and _____. There is some current flow in the off state and some voltage across the transistor in the _____ state.

50.1 An ideal switch is one that allows zero current when open, infinite current when closed, and the ability to turn on and off in zero time. A transistor gives _____ of these qualities.
(all, none)

delay time (t_d)
 rise time (t_r)
 storage time (t_s)
 fall time (t_f)
 on

50.2 When the transistor is off, there is some current, due mostly to hole-electron pairs as formed by heat energy. The transistor in its off state will offer a high, but not a/an _____ resistance.

none

50.3 When the transistor is on and saturated, there will still be some voltage across the transistor which is given the symbol $V_{CE(sat)}$. In the on condition, the transistor will not be a/an _____ circuit.

infinite

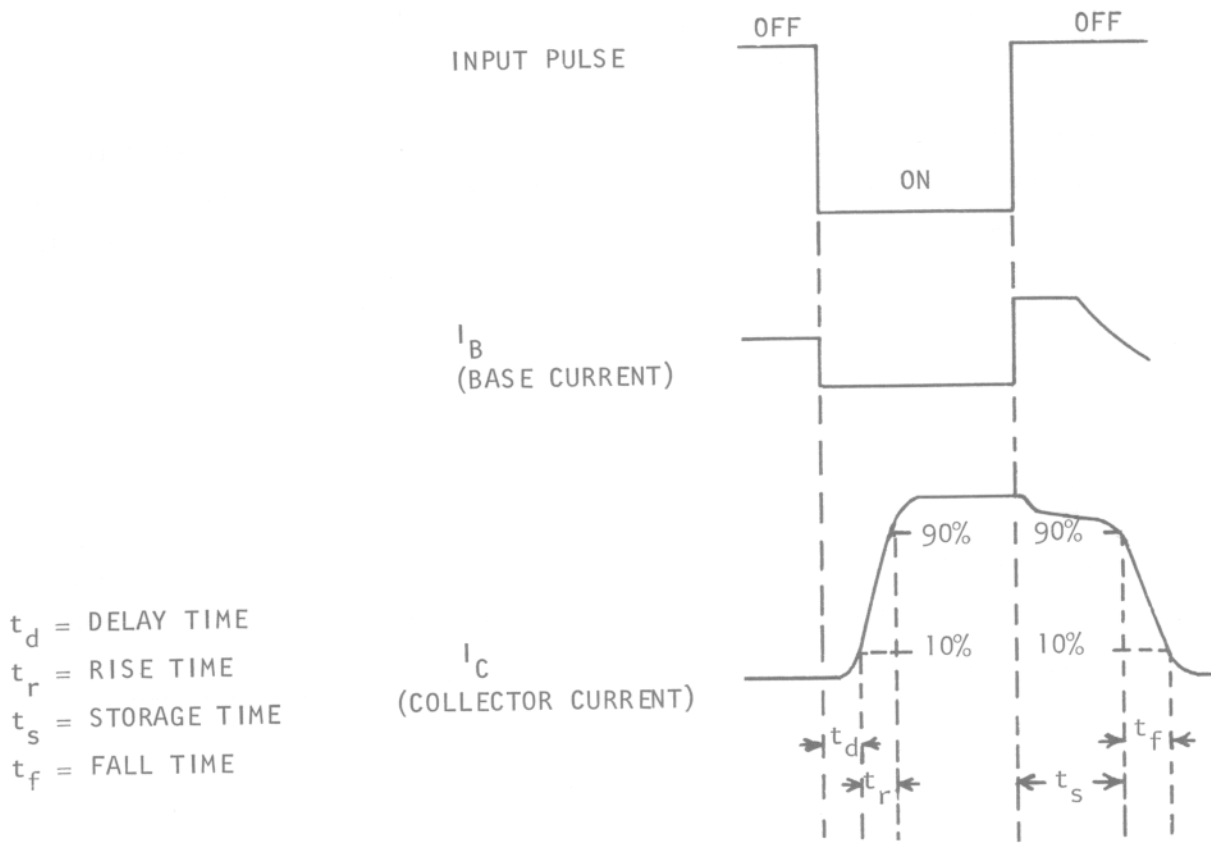
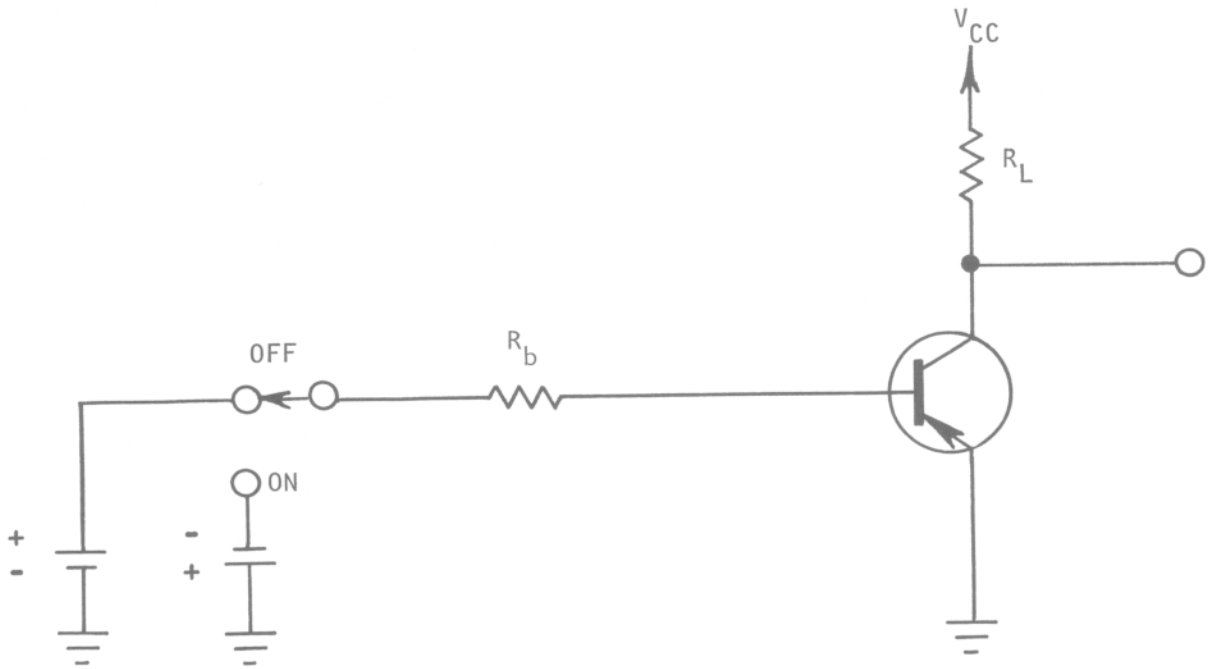


FIGURE 50

50.4 When the transistor is turned on, it will take a period of time for the stored charge to be established and for the recombination and diffusion to reach an equilibrium rate. In other words, it will take a period of time for the injected carriers to move across the base to the collector. When a change is instigated at the emitter junction, there is some _____ before the change occurs in the collector.

_____ zero resistance (short)

50.5 Figure 50 shows a transistor in a circuit to check its switching characteristics. The time between the instigation of the input change and the point that collector current has changed, 10% of its total excursion, is termed _____ time (t_d).


_____ time (delay)

50.6 Delay time (t_d) is the time it takes to move carriers into the _____ to establish the stored charge of _____ carriers.
(minority, majority)

_____ delay

50.7 In figure 50, the time between the points on the leading edge of the waveform where collector current has changed from 10% to 90% of its total excursion is termed _____ time.

_____ base
minority

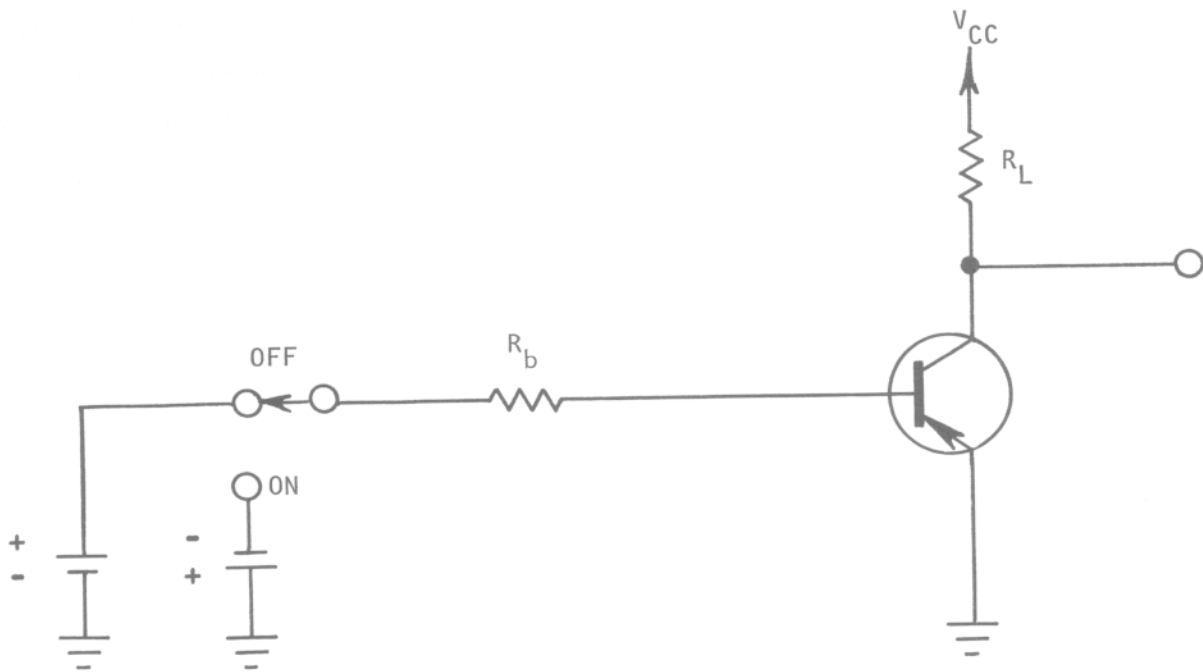

t_d = DELAY TIME
 t_r = RISE TIME
 t_s = STORAGE TIME
 t_f = FALL TIME

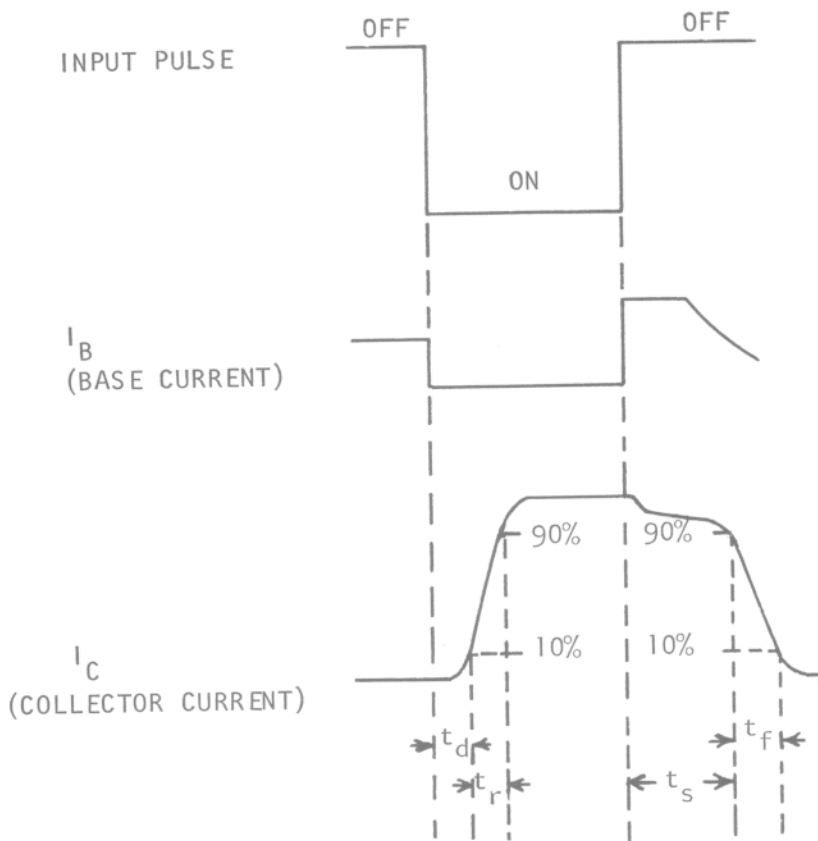


FIGURE 50

50.8 Rise time is determined by the charge control time constant in the base, governed by minority carrier lifetime. The sum of delay time (t_d) and rise time (t_r) is the transistor's _____ time (t_{on}).

rise

50.9 In figure 50, the time between the fall of the input pulse and the point that collector current falls to 90% of its maximum value is termed _____ time (t_s).


turn on

50.10 Storage time is increased when the forward biased collector injects carriers into the base when the transistor enters _____.

storage

50.11 Holding the transistor out of saturation will reduce _____ time.

saturation

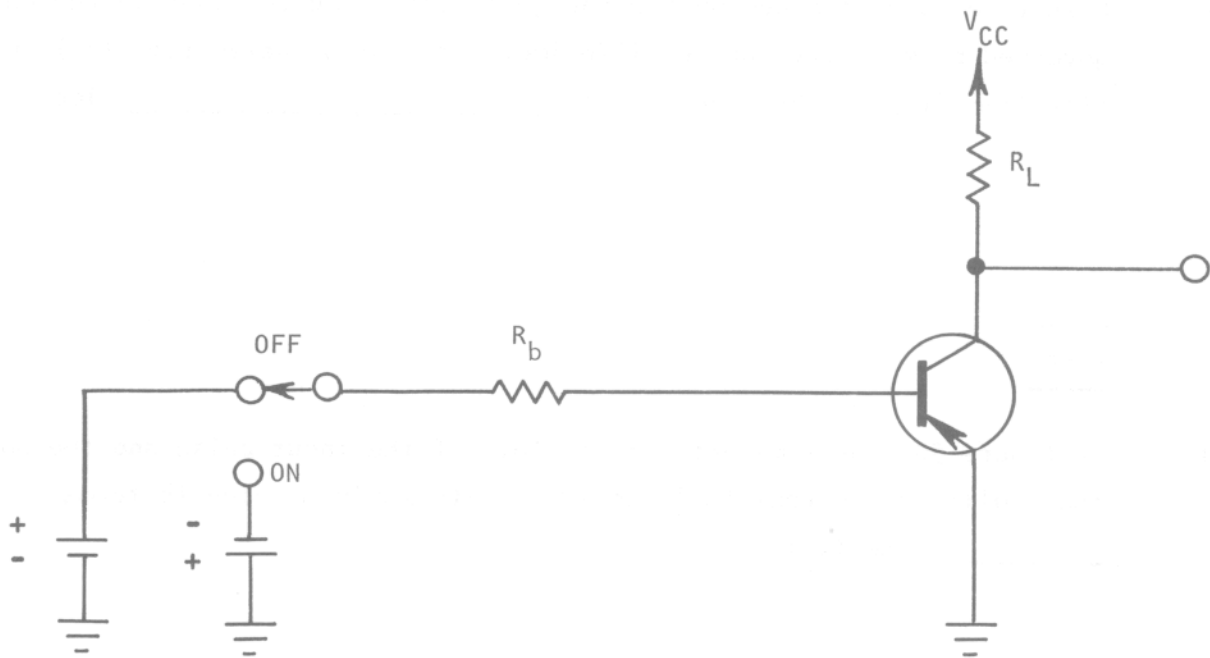

- t_d = DELAY TIME
- t_r = RISE TIME
- t_s = STORAGE TIME
- t_f = FALL TIME

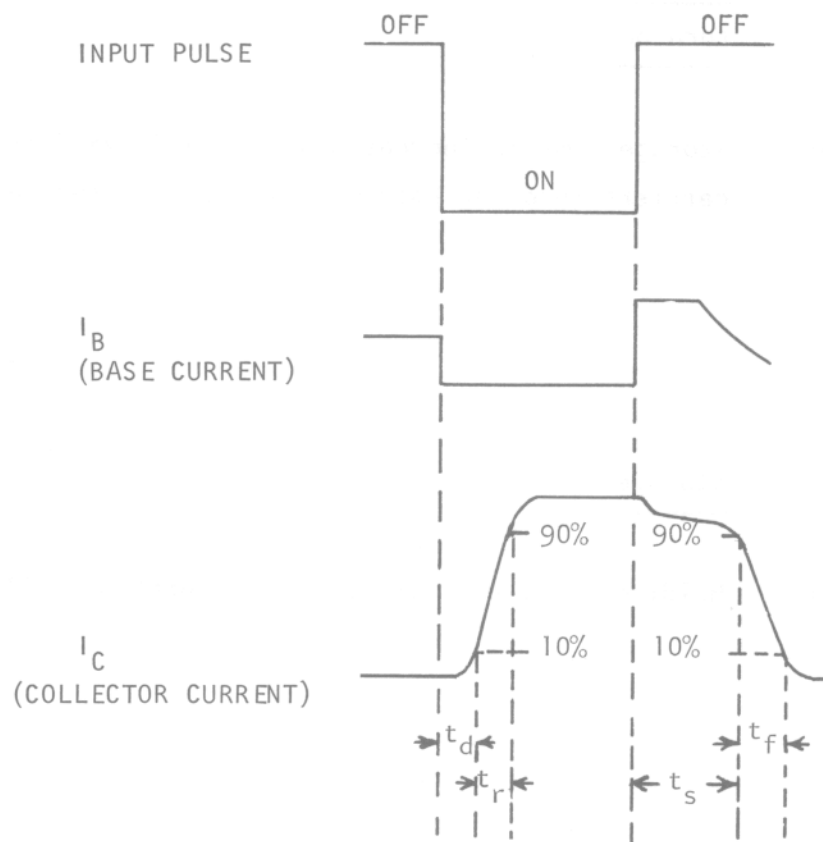


FIGURE 50

50.12 The time between 90% and 10% on the falling portion of the collector current waveform in figure 50 is termed _____ time (t_f).

_____ storage (switching) _____

50.13 The sum of storage time (t_s) and fall time (t_f) gives the transistors _____ time (t_{off}).

_____ fall _____

50.14 Turn off time (t_{off}) = storage time (t_s) + fall time (t_f) and turn on time (t_{on}) = delay time (t_d) + rise time (t_r).

$$t_{off} - t_f = \underline{\hspace{2cm}}$$

_____ turn off _____

50.15** $t_s + t_f = \underline{\hspace{2cm}}$ and $t_d + t_r = \underline{\hspace{2cm}}$

The transistor is less than an ideal switch as there is some _____ in the off state and some _____ across the transistor in the on state.

_____ storage time (t_s) _____

50.16

END OF SET

turn off time (t_{off})
turn on time (t_{on})
current
voltage

51 The switching times of fast transistors may be checked using the Tektronix Type 290 Transistor Switching Time Tester or the Type 292 Semiconductor Tester in conjunction with a sampling system. The _____ checks the transistor in a specific configuration while the _____ allows the circuit to be inserted with the transistor.

51.1 The manual switch used in the previous set is not fast enough to give accurate readings of switching times. In practice, electrically driven switches are used.


290
sampling
567

51.2 The 290 Switching Time Tester provides a circuit, bias voltages, and input and output jacks along with facilities to drive the input of the transistor. The output is monitored with a sampling oscilloscope. Both the input driving signal and the transistor's output may be monitored.


no answer needed

51.3 The input pulse and the transistor's output can be monitored and measurements taken of switching times exactly as in set 50 when the 290 and a sampling system are used. These measurements are similar to the diode switching time measurements made in volume 2 of this series.

no answer needed

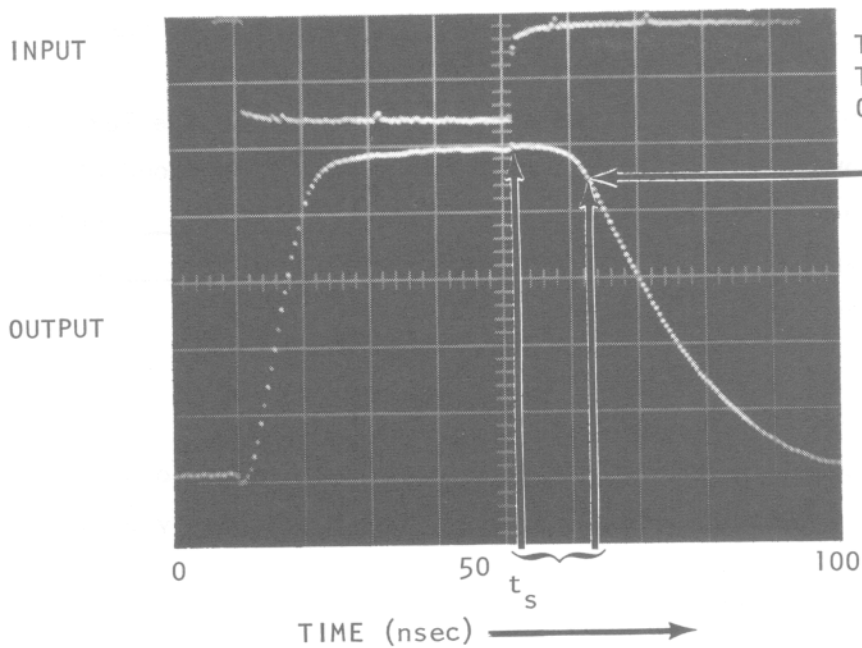

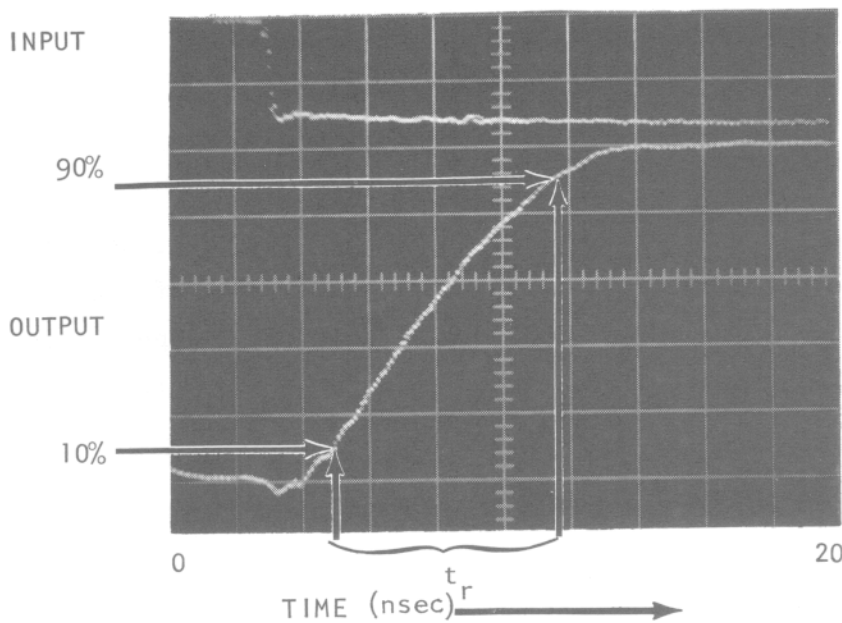TOP PHOTOS TAKEN WITH A
TYPE C-12 OSCILLOSCOPE
CAMERA



TEST SET-UP

TEKTRONIX TYPE 661 SAMPLING
OSCILLOSCOPE, 4S1 DUAL TRACE
SAMPLING VERTICAL, 5T1A
TIMING UNIT, TYPE 109 PULSE
GENERATOR, AND TYPE 290
TRANSISTOR SWITCHING
TIME TESTER

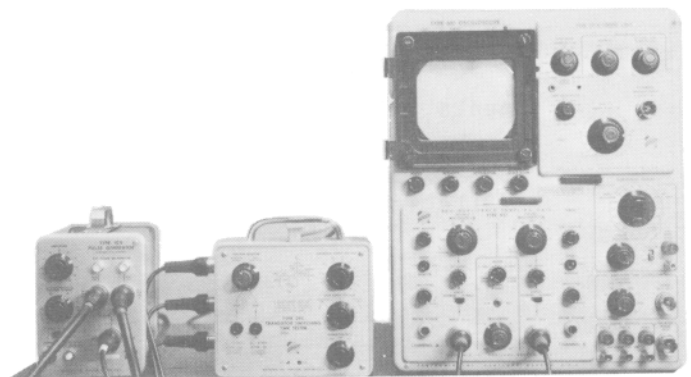
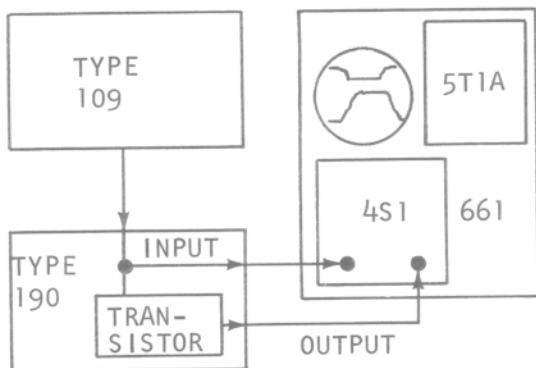


FIGURE 51

51.4 Figure 51 shows the 290 being used with the Tektronix Type 661 sampling oscilloscope. It should be remembered that the risetime considerations, when making measurements as discussed in volume 2, are valid for these measurements as well.

no answer needed

51.5 The dual trace ability allows the observance of the input and output pulse, simultaneously. The risetime measurement in figure 51 is approximately _____ nsec.

no answer needed

51.6 The storage time in figure 51 is approximately _____ nsec.

7

51.7 The 290 Transistor Switching Time Tester can be used in conjunction with a sampling system and a pulse generator to make the measurements described in set 50. This allows measurement of fractional nanosecond switching times.

11



TEKTRONIX TYPE 292 SEMICONDUCTOR TESTER
AND ACCESSORIES

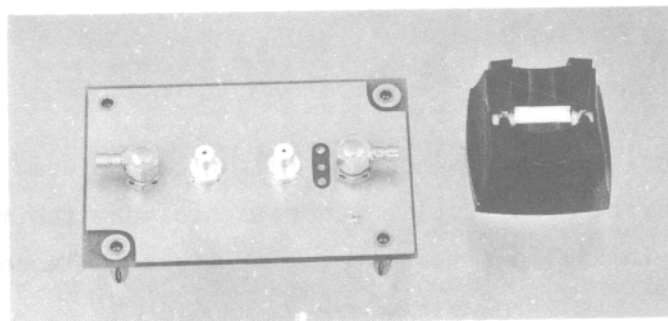


FIGURE 51-A

51.8 The Type 292 Semiconductor Tester (shown in figure 51-A) allows the circuit for the transistor to be selected and built while maintaining the transistor in an optimum measurement environment.

no answer needed

51.9 The Type 292 does not limit the measurements to a specified circuit, but allows the measurement circuit to be fabricated on special test fixtures provided.


no answer needed

51.10 The Type 292 does not limit the switching time measurements to a specified _____.

no answer needed

51.11 The Type 292 (shown in figure 51-A) can be used for diode measurements as well as _____ measurements.

circuit

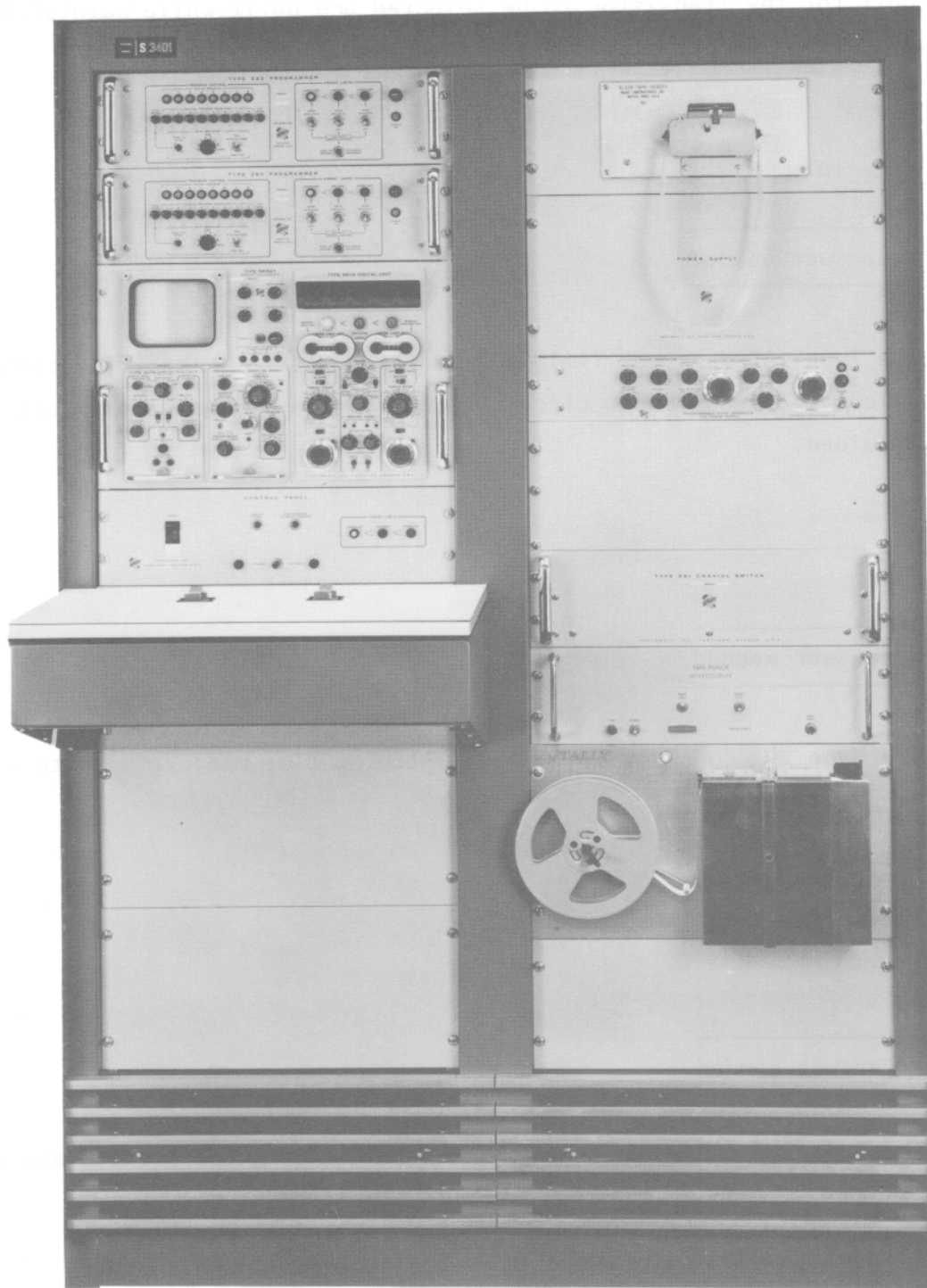

TEKTRONIX TYPE S-3401 SYSTEM

FIGURE 51-B

51.12 For transistor manufacturers, the system of measurement becomes more complex. A great number of measurements must be made in a short period of time. Figure 51-B shows a programmed measurement system for transistors (and other semiconductor devices).

transistor

51.13 The system in figure 51-B is the Tektronix S-3401 system. This is a programable, computer type system that can be used for rapid, sequential measurements of fast transistors. (Also, other semiconductor devices and integrated circuits.)

no answer needed

51.14** The Type _____ Transistor Switching Time Tester or the Type _____ Semiconductor Tester may be used in conjunction with a pulse generator and sampling system to check fast transistor switching times.

no answer needed

51.15 END OF SET

52 A _____ capacitor will reduce the time involved in establishing the base charge when turning on a transistor and removing the base charge when turning off a conducting transistor. The optimum value of speed-up capacitor may be found by dividing the transistor's stored charge by the value of _____ on the speed-up capacitor.

52.1 The stored charge in the base of a transistor must be established to turn on a transistor and must be removed to turn the transistor off. Sufficient current must be supplied to establish and remove the _____ to turn a transistor on and off.

speed-up
voltage

52.2 A capacitor connected across the resistance in the input circuit of a transistor will speed up the establishment of the base charge when turning the transistor on and speed up the removal of the stored charge when turning the conducting transistor off.

stored charge
base charge

52.3 The output resistance of the driving source must be low for best effect of the added capacitor. Since the capacitor speeds up the switching time, it is referred to as a _____ capacitor.

no answer needed

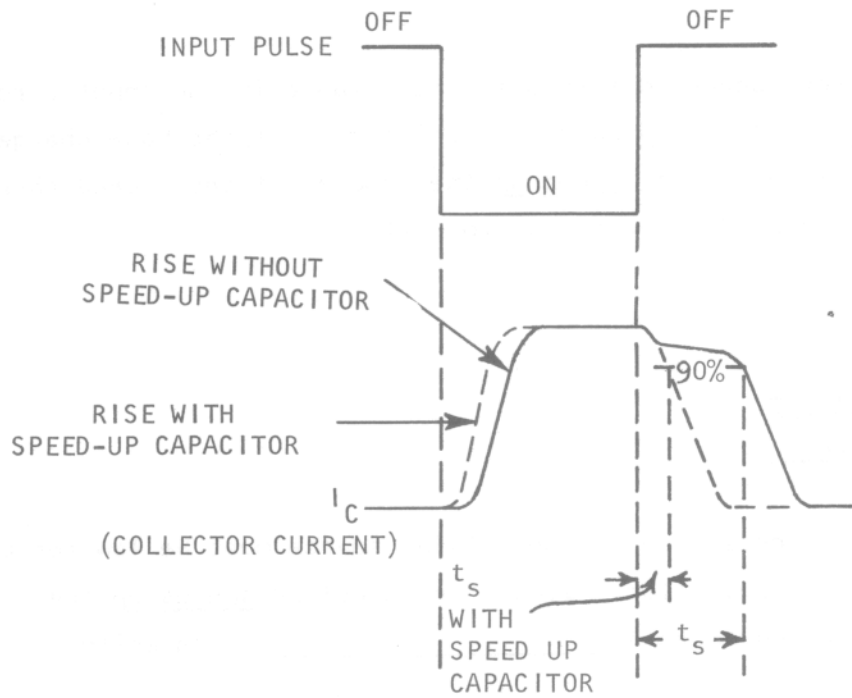
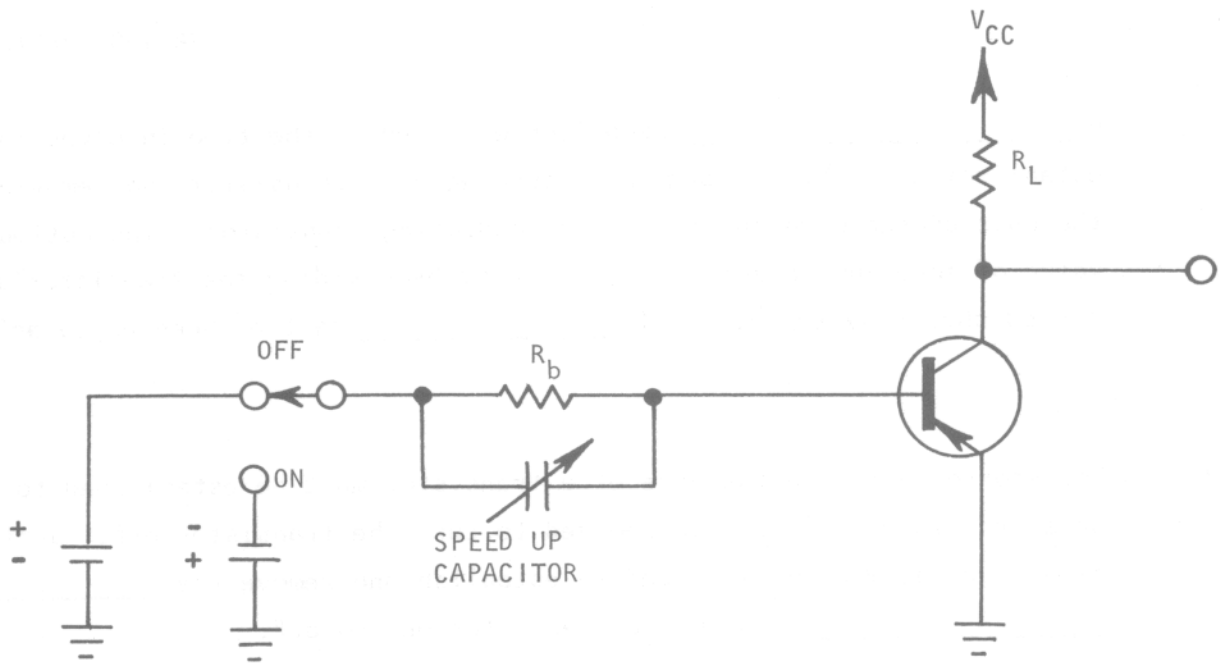


FIGURE 52

52.4 Figure 52 shows the added speed-up capacitor and its effect on the output waveform. The optimum value of speed-up capacitor to accomplish this will have a charge equal to the transistor's _____ charge.

_____ speed-up _____

52.5 The charge on the speed-up capacitor speeds up the establishment and removal of the stored charge when the speed-up capacitor is of optimum value. While observing the transistor's switching characteristics on the 290 Switching Time Tester or the 292 Semiconductor Tester, the speed-up capacitor can be adjusted for minimum switching _____.

_____ stored or base _____

52.6 Letting Q_s indicate total transistor stored charge, and Q_c indicate the charge on the speed-up capacitor, Q_c should be approximately equal to _____ for optimum speed-up action.

_____ times _____

52.7 $Q_c \cong Q_s$ for optimum speed-up operation.

$Q_c = CE$ where C is the capacity of the speed-up capacitor and E is the voltage across the capacitor. $Q_c = Q_s = CE$

$$\frac{Q_s}{E} = \frac{?}{_____}$$

_____ Q_s _____

52.8

The optimum value of speed-up capacitor is found by dividing the transistor's stored charge by the voltage on the speed-up capacitor. When this value of capacitor is used, the charge on the capacitor will equal the transistor's _____.

 C (value of speed-up capacitors)

52.9**

A speed-up capacitor across the input driving resistance will reduce _____ times. The optimum value of speed-up capacitor is equal to the transistor's _____ divided by the voltage on the speed-up capacitor.

 stored charge

52.10

END OF SET

 switching
 stored charge (Q_s)

53 An obvious method of reducing saturated mode storage time is to keep the transistor out of saturation. This is termed _____ switching and the transistor operates between cut-off and the _____ region. Current mode switching allows _____ transistor power dissipation than saturated mode switching.
(more, less)

53.1 Not allowing the collector to become forward biased will prevent the collector from injecting carriers into the base. The collector voltage must be held _____ than $V_{CE(sat)}$ to accomplish this.
(less, greater)


current mode
active
less

53.2 Zener or avalanche diodes are sometimes used to catch the collector voltage and hold it above $V_{CE(sat)}$. This prevents the transistor from entering _____.

greater

53.3 When the transistor is held out of saturation, it switches from cut-off to a high current point and this is termed _____ mode switching.

saturation

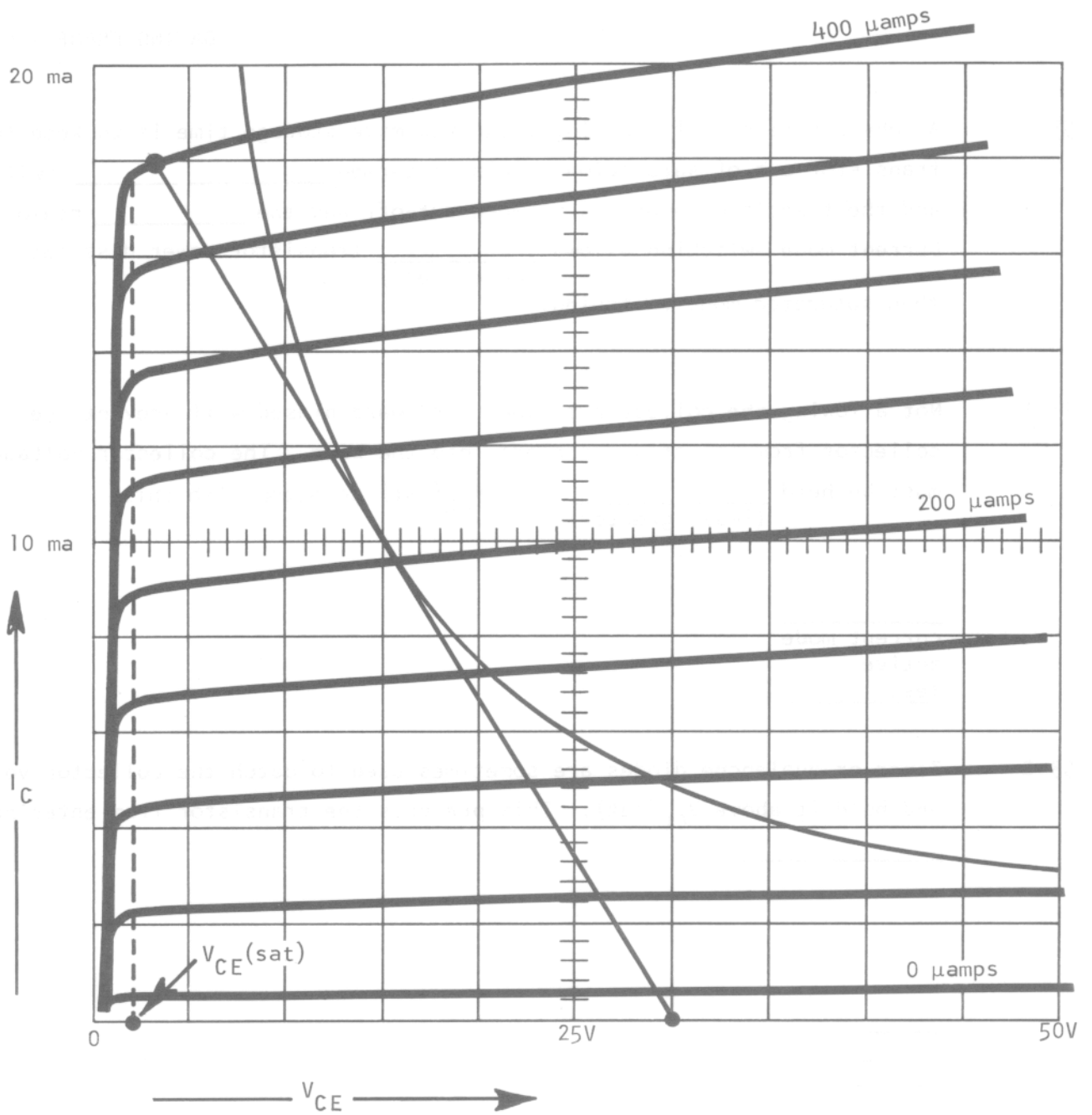

CURRENT MODE SWITCHING
CUT-OFF TO ACTIVE REGION

FIGURE 53

53.4 Current mode switching has the transistor switching between cut-off and the _____ region. This switching mode allows _____ transistor power dissipation during switching than the off to saturated switching mode.

current

53.5 Figure 53 shows the load line for current mode switching. The collector voltage is caught in the active region and not allowed to go below _____.

active
less

53.6 In figure 53, the on resting state is held below the maximum power curve. A disadvantage of current mode switching is the reduction in _____ dissipation capabilities with reference to the cut-off to _____ switching mode.

 V_{CE} (sat)

53.7** Transistor storage time can be reduced by holding the transistor out of _____. This switching mode is termed _____ mode switching. This mode can allow the transistor to dissipate _____ power during switching than the saturated mode.

power
saturated

53.8

END OF SET

saturation
current
less

54 Current mode switching offers _____ speed, _____ noise, _____ critical transistor requirements and _____ complicated d-c design problems than the saturated switching mode.

(higher, lower)

(higher, lower)

(more, less)

(more, less)

54.1 Current mode switching reduces the storage time which reduces total switching time over the saturated switching mode. Current mode switching offers a _____ maximum repetition rate than the saturated mode.

(higher, lower)

high
low
less
more

54.2 When the transistor enters saturation, both the emitter and collector inject carriers into the base resulting in an increase in the noise level. The current mode switch does not enter saturation and generates _____ noise than the saturated mode.

(more, less)

higher

54.3 $V_{CE}(\text{sat})$, $h_{FE}(\text{sat})$, breakdown voltage from emitter to base, thermal and leakage currents are less critical with the current mode, since the transistor does not enter _____.

less

54.4 The transistor must remain out of saturation under worst case conditions, using the current switching mode. This increases the complexity of the d-c design considerations over the _____ mode.

saturation

54.5 Since the current mode switch has a resting state in the _____ region, care must be taken that maximum power is not exceeded.

saturated

54.6** The advantages of current mode switching over saturated mode switching are _____ switching speed, _____ critical transistor parameters. The disadvantages are _____ resting state power dissipation and _____ complicated d-c design considerations than the off to saturated mode.

active

54.7 END OF SET

faster
less
less
higher
more

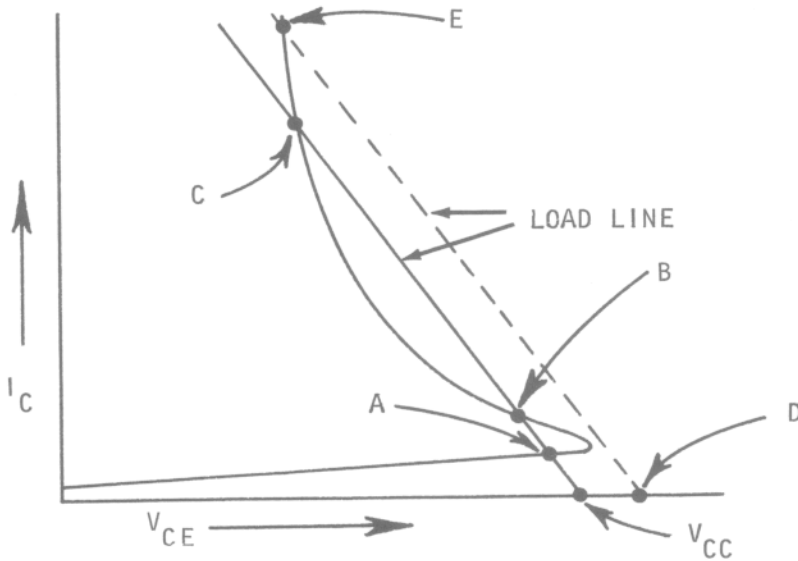
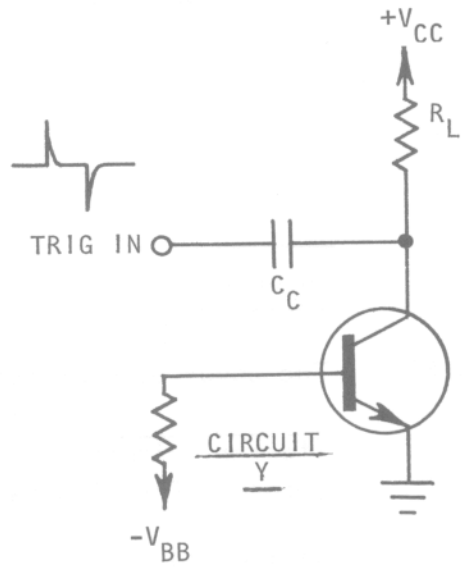
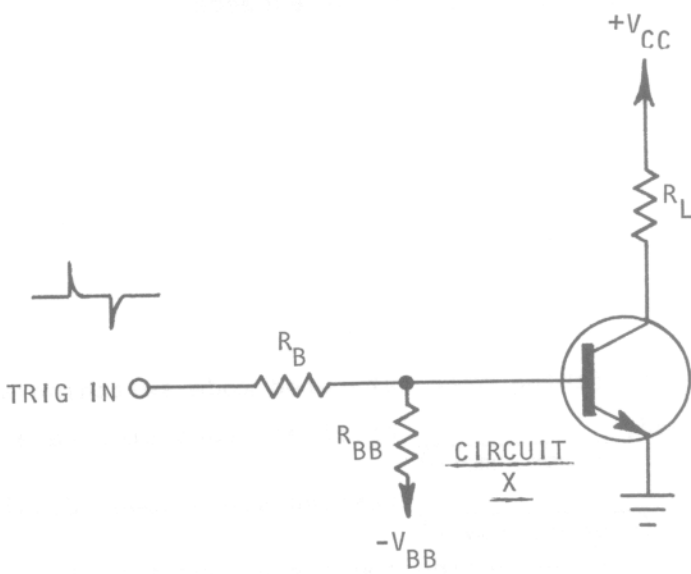
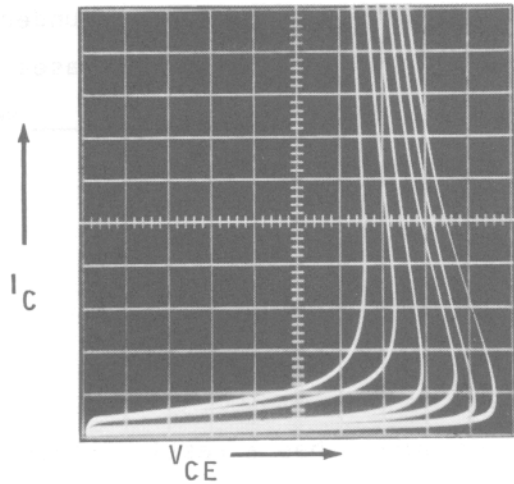


FIGURE 55

55 The avalanche switching mode has the transistor switching between cut-off and a point in the _____ region. The switching time can be on the order of fractional _____ seconds. Avalanche switching can be triggered in the base or _____ circuit.

55.1 One resting state of an avalanche switching transistor is just out of avalanche breakdown and the other is in the _____ breakdown region.

 avalanche breakdown
 nano
 collector _____.

55.2 The action of causing the transistor to switch states is termed triggering and the applied energy to cause switching is termed a _____.

 avalanche

55.3 Figure 55 shows transistors biased for avalanche switching. V_{CC} is very near the _____ voltage point.

 trigger

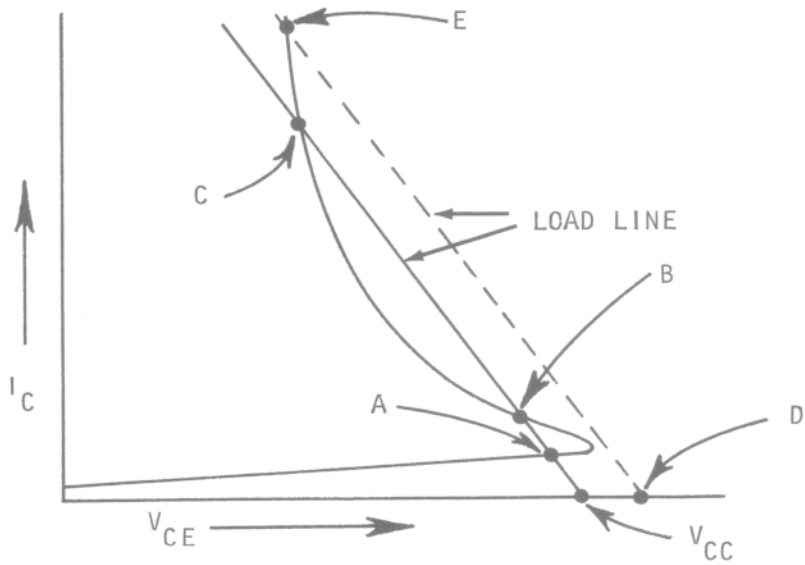
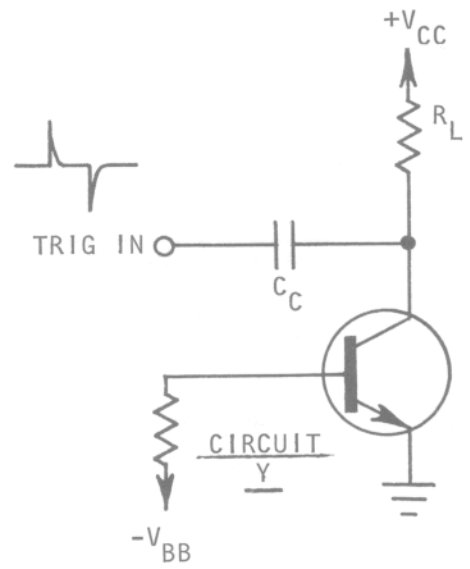
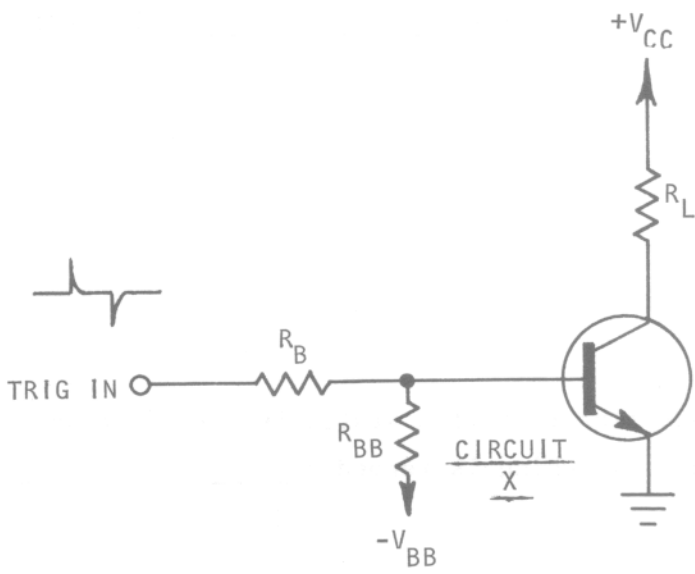
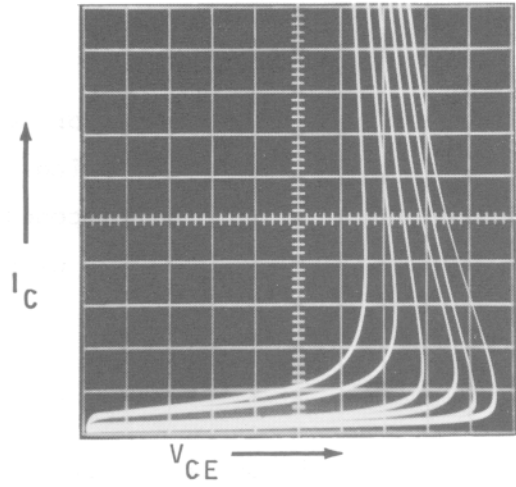


FIGURE 55

55.4 The transistors in figure 55 must operate on the load line. The transistor can operate only at points A, B and C with the load line and value of _____ shown.

_____ avalanche breakdown _____

55.5 Consider the transistor in circuit X in figure 55 as operating at point A on the curve. Forcing more current with V_{CC} constant will cause the operating point to shift to B and then to _____.

_____ V_{CC} _____

55.6 The input trigger in circuit X increases the current causing the transistor to switch to point C on the load line. This transition can take place in a fraction of a nanosecond. Avalanche switching can give a very _____ switching time.

_____ C _____

55.7 A trigger is needed to return the transistor to point A. The avalanche switching mode shown in figure 55 is bi-stable, meaning the transistor has _____ (#) stable states.

_____ fast _____

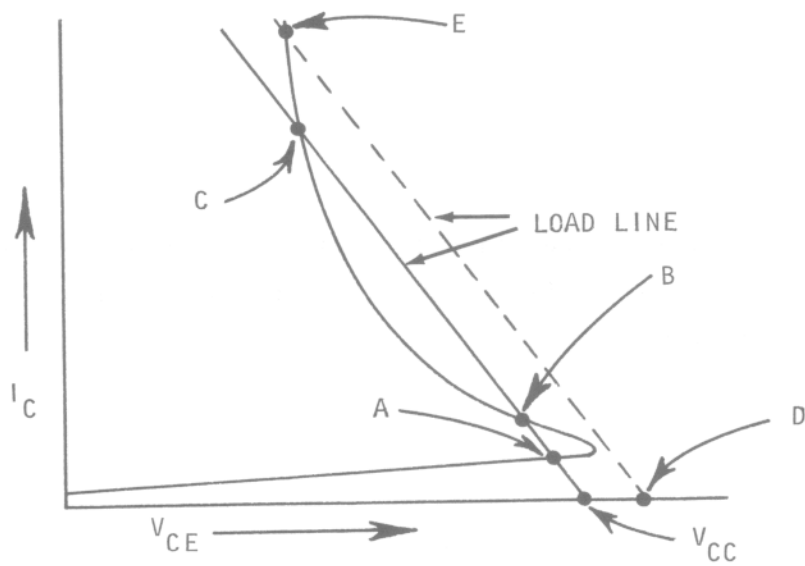
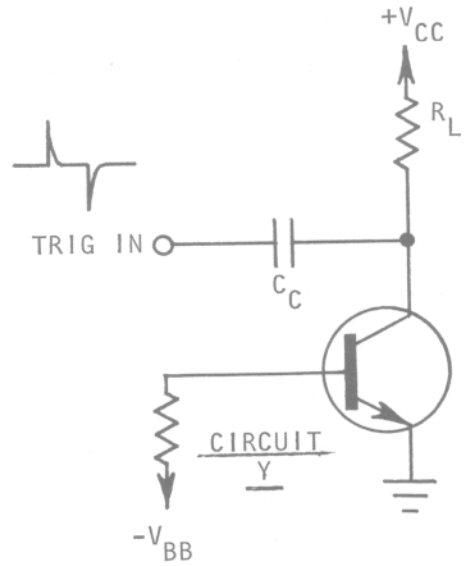
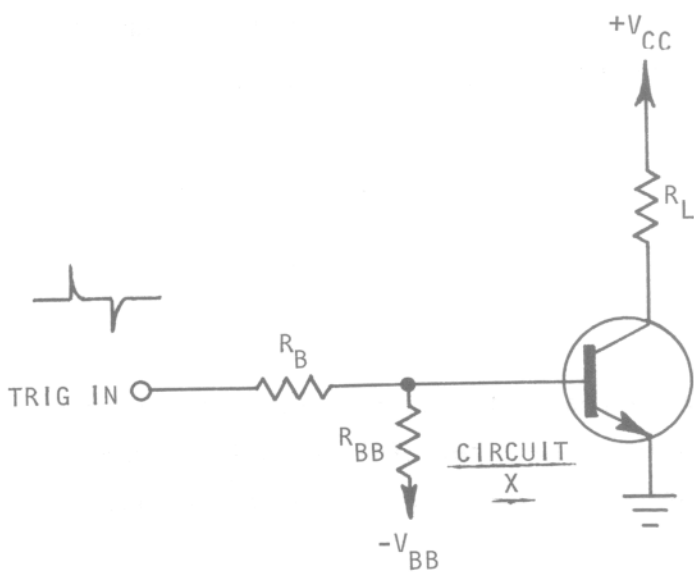
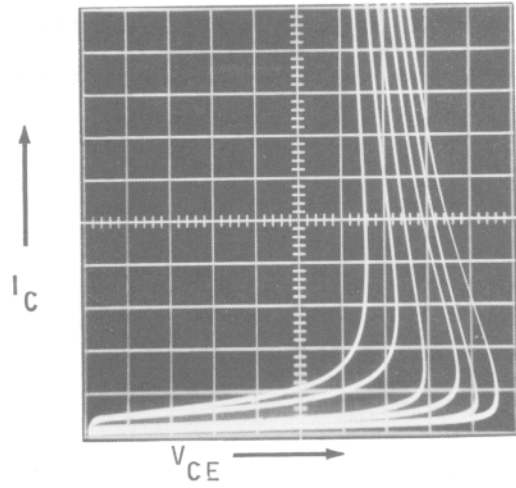


FIGURE 55

55.8 The circuit Y in figure 55 has the trigger applied to the collector. The trigger will increase or decrease the collector voltage depending on its polarity.

—
two
—

55.9 With circuit Y operating at point A in figure 55, a positive going trigger will increase the applied collector voltage and the load line will move to point D. At that instant, the only point on the load line that the transistor can exist is at point _____.

—————
no answer needed
—————

55.10 Once triggered to point E in figure 55, the transistor in circuit Y will rest at point _____ when the trigger is no longer present.

—
E
—

55.11 In order to move back to point A from point C, the collector must be triggered in the opposite polarity. Circuit Y in figure 55 is _____-stable and switches between resting points _____ and _____.

—
C
—

55.12 Avalanche mode switching can be accomplished in fractional nanoseconds, allowing very fast rising outputs. The collector supply voltage is near the _____ voltage.

bi
A
C

55.13** The two resting states of an avalanche switching transistor are just below the _____ point and in the _____ region. Fractional _____ second risetimes are possible with this switching mode.

avalanche breakdown

55.14 END OF SET

avalanche breakdown
avalanche breakdown
nano

56 The main high frequency limiting factors in the transistor are collector and emitter junction _____, base _____ time, and the spreading out of the carriers in the _____.

56.1 Carriers injected from the emitter into the base are existing as minority carriers in the base. They must diffuse the entire _____ thickness to reach the collector.

_____ capacitance
transit
base _____

56.2 As the applied frequency is increased, a frequency will be reached where the time involved in the transit of the carriers across the base causes phase shift and loss of gain. The greater the transit time, the _____ the frequency at which phase shift and loss of gain occur.
(lower, higher)

base

56.3 There is capacitance across the collector and emitter junctions. This capacitance will change with the amount of current and the voltage across the junction. This capacitance shunts the junction and, as frequency is increased, will have _____ effect.
(a greater, less)

lower

56.4 The collector junction is reverse biased and the emitter junction is forward biased in amplifier configurations. The _____ junction will have the highest resistance.

a greater


56.5 The effects of collector junction capacitance will occur at a lower frequency than the effects of emitter junction capacitance as collector junction capacitance is shunting a _____ resistance.
(higher, lower)

collector

56.6 The carriers, on entering the base, spread out or diffuse in the base. They strike atoms in the structure and bound off, taking an erratic path in the base. Carriers do not travel in a direct route from emitter to _____ through the _____.

higher

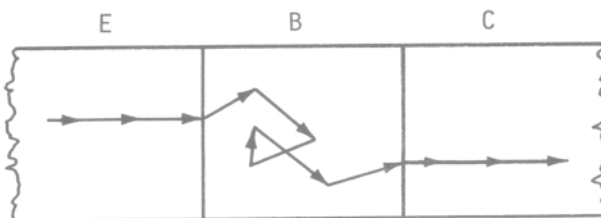56.7 The diagram shows a typical path a current carrier might take in its transit through the base. Several carriers entering the base at the same time could well arrive at the collector at _____ times.



collector
base

56.8 The wider the base, the _____ opportunity the carriers will have
(more, less)
to spread out and arrive at the collector at _____ times.

different

56.9** High frequency operation in transistors is limited mainly by the
_____ at the collector and emitter junctions, the time of
_____ in the base, and the _____ out of the carriers
in the base.

more
different

56.10 END OF SET

capacity
transit
spreading

57 _____ is the symbol for the cut-off frequency of the transistor in a common base configuration. This indicates the frequency at which _____ has fallen to 0.707 of its low frequency value.

57.1 h_{fb} is the small signal, a.c. current gain of the transistor in a common base configuration. Due to factors already discussed, h_{fb} will decrease with an increase in frequency.


$$\frac{f_{hfb} \text{ or } f_{\alpha_b}}{h_{fb}(\alpha)_b}$$

57.2 A frequency will be reached at which h_{fb} has decreased to 0.707 of its low frequency value. The frequency at which this occurs is given the symbol f_{hfb} or f_{α_b} . This is usable with the common _____ configuration.

_____ decrease _____

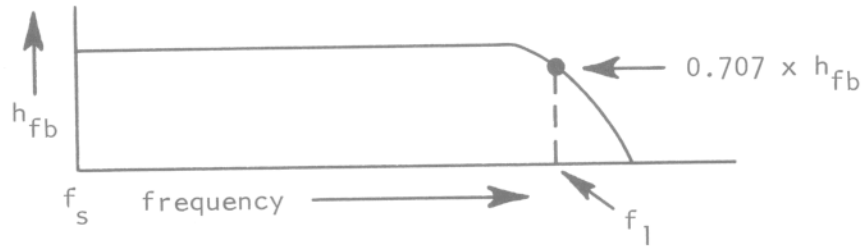57.3

In the diagram, h_{fb} is plotted vertically and frequency is plotted _____ on the base line. f_1 is given the symbol _____ and indicates the common base cut-off frequency of the transistor.



base

(NOTE: f_s = standard frequency, usually 1kc)

57.4**

f_{hfb} or $f_{\alpha b}$ indicates the _____ at which h_{fb} falls to _____ of its low frequency value. This is the cut-off frequency of the transistor in a common _____ configuration.

horizontally
 f_{hfb} or $f_{\alpha b}$

57.5

END OF SET

frequency
0.707
base

58

_____ is the symbol for the cut-off frequency of the transistor in a common emitter configuration. This indicates the frequency at which _____ has diminished to 0.707 of its low frequency value. For a given transistor, this frequency will be much _____ than f_{hfb} .

58.1

h_{fe} , the small signal, a-c current gain of the transistor in a common emitter configuration will decrease at the higher frequencies. The cut-off point is considered to be the point at which h_{fe} has decreased to _____ of its low frequency value.

_____ f_{hfe} or f_{α_e}
 h_{fe}


 lower

58.2

The frequency at which h_{fe} has decreased to 0.707 of its low frequency value is given the symbol f_{hfe} or f_{α_e} . This frequency is usable with the common _____ configuration.

_____ 0.707 _____

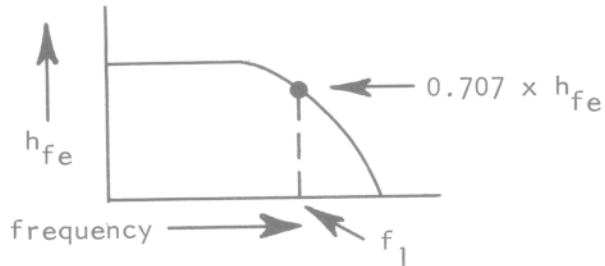58.3 In the diagram, h_{fe} is plotted vertically and frequency is plotted horizontally. f_1 is given the symbol _____ and indicates the common emitter cut-off frequency of the transistor.



_____ emitter

(NOTE: f_s = frequency standard, usually 1kc)

58.4 The relationship of f_{hfe} and f_{hfb} is expressed as $f_{hfe} = f_{hfb} (1 + h_{fb})$. Consider a transistor with an $h_{fb} = -0.98$ and an h_{fe} of 49. If the transistor has an f_{hfb} of 10 megacycles, h_{fe} will fall to 0.707 of its low frequency value at _____ cycles.

$$f_{hfe} = f_{hfb} (1 + h_{fb})$$

(NOTE: h_{fb} is always a negative quantity)

_____ f_{hfe} or f_{α_e}

58.5 f_{hfe} will occur at a much lower frequency than f_{hfb} . For a given transistor, the common emitter configuration will have its gain reduced to 0.707 of its low frequency value at a _____ frequency than the common base configuration.

$$f_{hfe} = f_{hfb} (1 + h_{fb}) = 10^7 1 + (-0.98) = 10^7 \times 0.02 = 200K$$

58.6 Consider a transistor with an $h_{fb} = -0.96$ and an $f_{hfe} = 500K$ cycles.

$$f_{hfb} = \underline{\hspace{2cm}}$$

(NOTE: h_{fb} is always a negative quantity)

lower

58.7** f_{hfe} is the symbol for the transistor's cut-off frequency in a common _____ configuration. This is the frequency at which _____ has fallen to _____ of its low frequency value. For given transistor, f_{hfb} will be a _____ frequency than f_{hfe} .
(higher, lower)

$$f_{hfb} = \frac{f_{hfe}}{1+h_{fb}} = \frac{500 \times 10^3}{0.04} = 12.5 \text{ megacycles}$$

58.8 END OF SET

emitter
 h_{fe}
0.707
higher

59 C_{ob} is the symbol given the output capacitance of a transistor in a common _____ orientation and C_{oe} is the symbol given the output capacitance of a transistor in a common _____ orientation. They are related as shown by the formula $C_{ob} = \underline{\hspace{2cm}}$.

59.1 In the symbol C_{ob} , the C indicates capacitance, the o indicates output, and the _____ indicates common base.

_____ base
 emitter
 $C_{oe} (1+h_{fb})$

59.2 In the symbol C_{oe} , the C indicates capacitance, the o indicates output, and the e indicates common _____.

_____ b

59.3 The relationship between C_{ob} and C_{oe} is expressed by the formula

$$C_{ob} = C_{oe} (1+h_{fb}). \text{ If } h_{fb} = -0.98 \text{ and } C_{oe} = 200 \text{ picofarads,}$$

$$C_{ob} = \underline{\hspace{2cm}}.$$

(Note: h_{fb} is always a negative quantity.)

emitter

59.4 C_{oe} will be much larger than C_{ob} for a given transistor and set of conditions. It has already been shown that the common _____ configuration current gain will fall off to 0.707 of its low frequency value at a lower frequency than the common _____ configuration.

$$\underline{C_{ob} = 200\text{pf} (1-0.98) = 200\text{pf} \times 0.02 = 4\text{pf}}$$

59.5 $C_{ob} = C_{oe} (1+h_{fb})$

$$C_{ob} = 9\text{pf}$$

(Note: h_{fb} is always a negative quantity.)

$$h_{fb} = -0.97$$

$$C_{oe} = \underline{\hspace{2cm}}$$

emitter
base

59.6** The output capacitance of the common emitter configuration has the symbol _____ and, the output capacitance of the common base configuration has the symbol _____. Their relationship is expressed by the formula $C_{ob} = \underline{\hspace{2cm}}$.

$$\underline{C_{oe} = \frac{C_{ob}}{1+h_{fb}} = \frac{9\text{pf}}{0.03} = 300\text{pf}}$$

59.7

END OF SET


$$\frac{C_{oe}}{C_{ob} C_{oe} (1+h_{fb})}$$

60 High frequency construction calls for a _____ but uniform base width. The narrower the base, the less the _____ time and the less time the carriers have to _____ out in the base.

60.1 The narrower the base thickness between the emitter and the collector, the less the transit time for a given minority carrier lifetime. Making the base very narrow increases the frequency at which _____ shift becomes a problem.

narrow
transit
spread

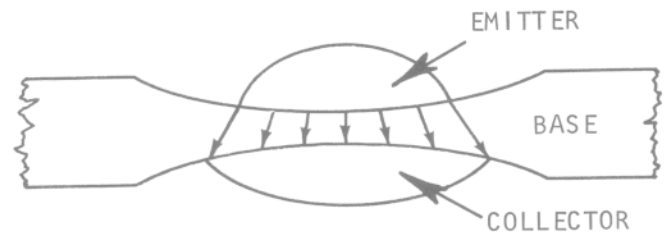60.2 The thin base should also have a uniform thickness. The transistor in the diagram has high frequency problems built in, since it takes some of the carriers longer than others to move through the base.



phase

60.3 Making the base narrow reduces the time the carriers spend in the base. The carriers will spread out less in a _____ base with a short transit time.

_____ no answer needed _____

60.4 Transit time and spreading out of the carriers are reduced with a narrow base. A uniform, narrow width further improves the high _____ characteristics.

_____ narrow, thin, etc. _____

60.5 High frequency transistors will have a different structure than low frequency or general purpose types. The desired characteristics will govern the _____ of the transistor.

_____ frequency _____

60.6** High frequency operation dictates a narrow _____ with uniform width. This reduces _____ time and the spreading out of the carriers in the _____.

_____ structure, construction, etc. _____

60.7

END OF SET

base
transit
base

62 A narrow, uniform width base is the aim in construction of high frequency transistors. The rate grown transistor has limited high frequency characteristics. The alloy type transistor gives a/an _____ (increase, decrease) in f_{hfb} over the rate grown. Typical f_{hfb} for the alloy transistor is _____ megacycles.

62.1 The rate grown transistor is manufactured by pulling a seed crystal from a container of molten materials. The crystal is said to be _____ in the process.

increase
1 to 10

62.2 Changing the rate at which the crystal is grown is one method of forming the N and P type regions. Different amounts of dopent impurities enter the crystal when the growing _____ is changed.

grown

62.3 The rate grown crystal is cut up and makes a number of transistors. Changing the _____ of growing forms the N and P regions as shown in the cross section in figure 62.

rate

62.4 The base could be made thinner in the rate grown process, but the problem is both in getting a uniform width and attaching a wire to the base. The base should be thinner than the _____ that must be attached.

rate

62.5 The alloy transistor is constructed by alloying two dots of material to the sides of a very thin crystal wafer. The dots should give an impurity concentration _____ the thin wafer.
(opposite of, same as)


wire, lead, etc.

62.6 Figure 62 shows a cross section of the alloy transistor. The dots become the emitter and collector contacts and the crystal wafer becomes the _____.


opposite of

62.7 The alloying process makes possible a much thinner base between the emitter and collector with the ability to connect a wire to the crystal wafer for an electrical connection to the _____.

base

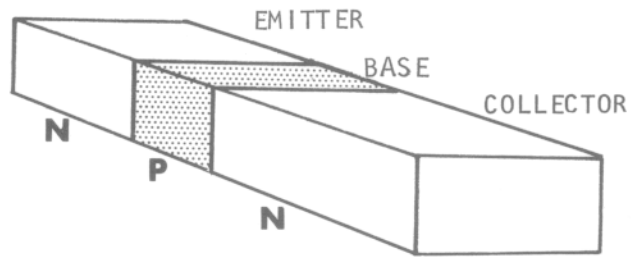

RATE GROWN

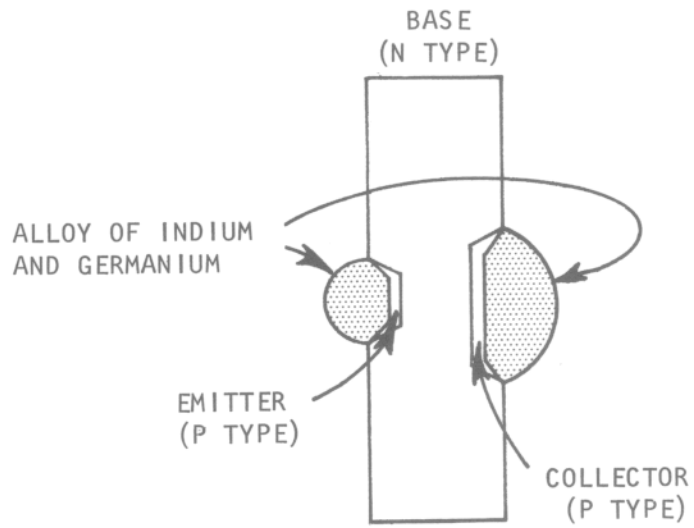

ALLOY

FIGURE 62

62.8

It is difficult to gain uniformity if the base is made too thin in the alloy transistor. Typical f_{hfb} for the alloy transistor is from 1 to 10 megacycles. This is an increase in f_{hfb} over the _____ transistor.

base

62.9**


The rate grown transistor is rugged and useful at the _____ frequencies. The alloy type gives a/an _____ in f_{hfb} with respect to the rate grown type. Typical f_{hfb} for the alloy type is _____ to _____ megacycles.

rate grown


62.10

END OF SET

lower
increase
1
10

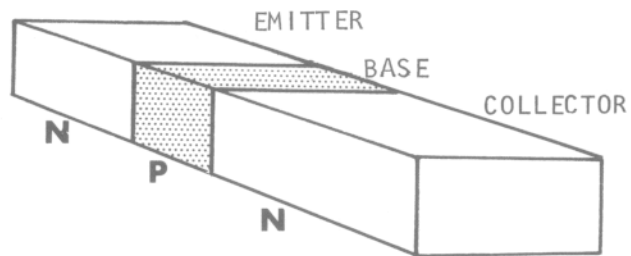

RATE GROWN

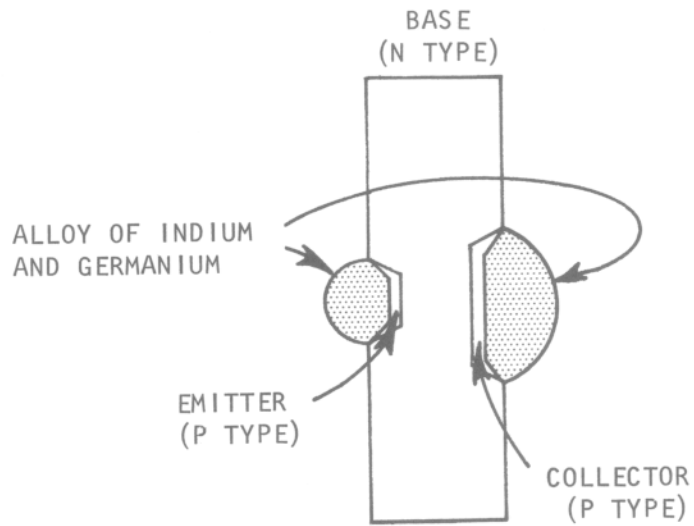

ALLOY

FIGURE 62

63 The micro-alloy is a variation of the _____ type transistor. To obtain a very thin, uniform base, the center of the wafer is etched very thin before the dots are applied and _____. This gives the characteristics of a/an _____ transistor with a thinner base. An increase of f_{hfb} to _____ megacycles is typical. A further improvement in f_{hfb} to _____ megacycles can be obtained with the micro-alloy diffused. This transistor gives the effect of a built-in electric _____ in the base. The micro-alloy diffused is also called a drift _____ transistor.

63.1 In order to get a thinner base and yet not make the device too fragile, the center of the wafer is etched very thin. Etching is the process of concentrating a stream of acid on the two sides and removing some of the material. The outer edges, not being etched, gives the device _____.

 alloy
 alloyed
 alloy
 40
 200
 field
field

63.2 The dots are applied to the thin portion of the wafer and when alloyed, give a very thin base. The dots should give an impurity concentration _____ as/to the etched wafer as shown in figure 63.

 (the same, opposite)

 strength, rigidity, etc.

63.3 The micro-alloy gives the characteristics of an alloy transistor with a much thinner _____. An increase in f_{hfb} to 40 megacycles is typical. This is _____ than the alloy transistor.
(higher, lower)

_____ opposite

63.4 A further variation of the alloy is the micro-alloy diffused or drift field transistor. In this type, the dopants are diffused into the wafer. Diffusion doping is the process of heating the wafer while surrounding it with the impurities in the form of a gas. The impurities _____ into the wafer during the process.


_____ base
higher

63.5 The diffused wafer is then etched, predominately on the collector side. This places the heavier doped portion of the base nearest the emitter when the dots are applied and alloyed. The doping will appear to be graduated heavy to light from _____ to _____.


_____ diffuse, spread, etc.

63.6 The graduated doping in the base gives the effect of an electric accelerating field in the base. The diffusing carriers will be accelerated reducing both _____ time and the amount that the carriers _____ out in the base.

_____ emitter
collector

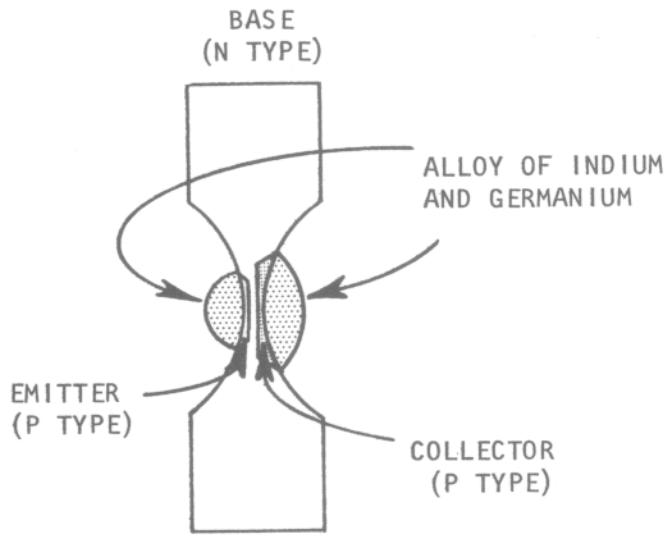

MICRO-ALLOY

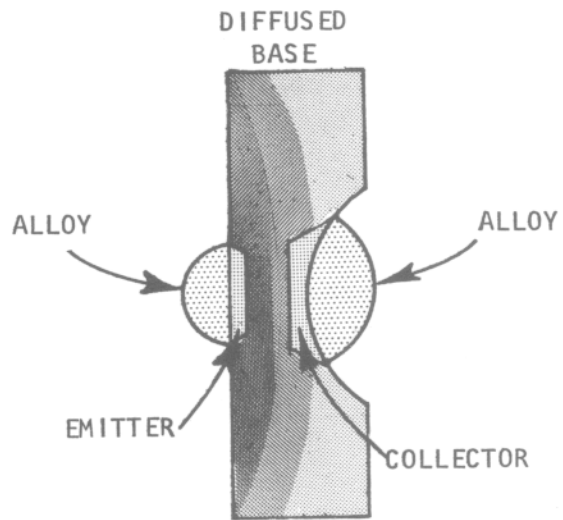

MICRO-ALLOY DIFFUSED

FIGURE 63

63.7 The effective electric field in the micro-alloy diffused base increases the frequency limits. An extension of f_{hfb} to 200 megacycles can be obtained with this construction. Another name commonly used for the micro-alloy diffused is "drift field" transistor.

transit
spread

63.8 The micro-alloy diffused or _____ transistor has an effective accelerating electric _____ built into the base.


no answer needed

63.9 Figure 63 shows the cross section of the drift field transistor. Base doping is heaviest near the _____.


drift field
field

63.10** The wafer is etched very thin before the dots are placed and alloyed to form a _____ transistor. This gives the characteristics of an alloy transistor with an extension of f_{hfb} to _____ megacycles. The micro-alloy diffused gives an extension of f_{hfb} to _____ megacycles by graduated doping in the base. It is also called a _____ transistor.

emitter

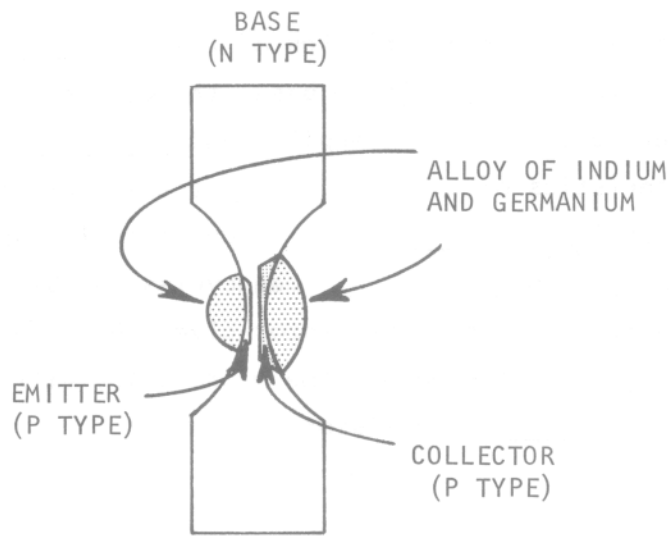

MICRO-ALLOY

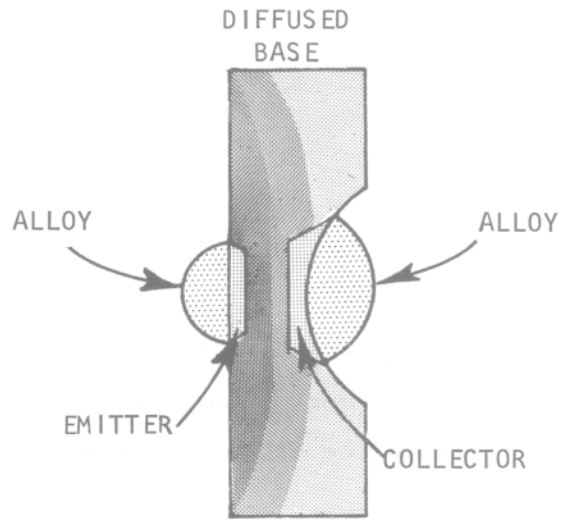

MICRO-ALLOY DIFFUSED

FIGURE 63

63.11


END OF SET

micro-alloy


40

200

drift field

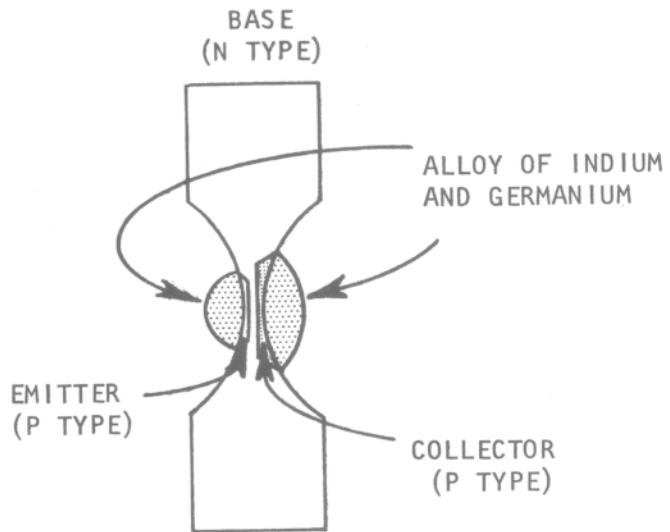

MICRO-ALLOY

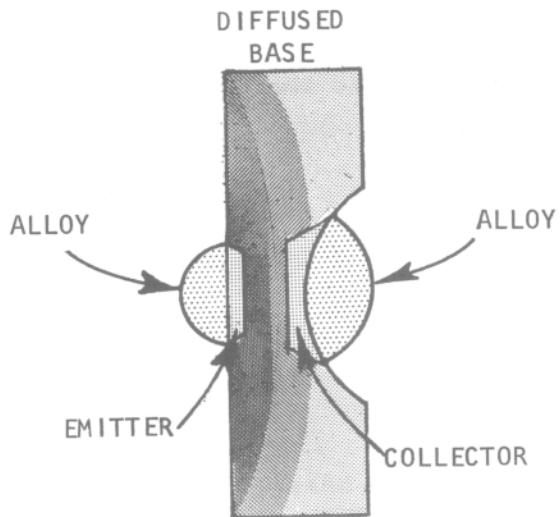

MICRO-ALLOY DIFFUSED

FIGURE 63

64 The aim in construction of the mesa transistor is a very narrow base, low collector junction _____, while maintaining the collector large to dissipate _____. The epitaxial mesa has an epitaxial layer that makes up the flat topped peak. The epitaxial layer allows high _____, while the collector is a low resistance material for a low _____.

64.1 The mesa construction starts with a thin layer of dopent being diffused into a basic wafer. The diffusing dopent is opposite to the dopent in the basic wafer. The thin diffused layer and the basic wafer will form a _____.

_____ capacitance
 _____ heat, (power)
 B_{VCBO}
 $V_{CE(sat)}$

64.2 The thin diffused layer becomes the base. A non-rectifying contact is connected to the layer for electrical connection. The basic pellet should be doped _____ than the diffused layer.
 (heavier, lighter)

_____ junction

64.3 The emitter is alloyed into the base (or an aluminum stripe is used) to form the emitter. The alloyed emitter (or the aluminum stripe) and the diffused layer will form the second _____.

_____ heavier _____

64.4 The top of the wafer is etched away except that portion containing the base lead and the emitter. This leaves a flat topped peak or _____ as shown in figure 64.


_____ junction _____

64.5 The area around the collector junction is etched away to reduce collector junction capacitance, while leaving the rest of the wafer to dissipate the _____ generated by power dissipation. Etching away part of the junction effectively reduces the area of the plates of the _____ at the junctions.


_____ mesa _____

64.6 The mesa has an increase in f_{hfb} into the hundreds of megacycles. The low resistance of the collector allows a low value of $V_{CE(sat)}$. The low resistance collector results in a low value of collector to base breakdown voltage, _____ (symbol).

_____ capacitance _____

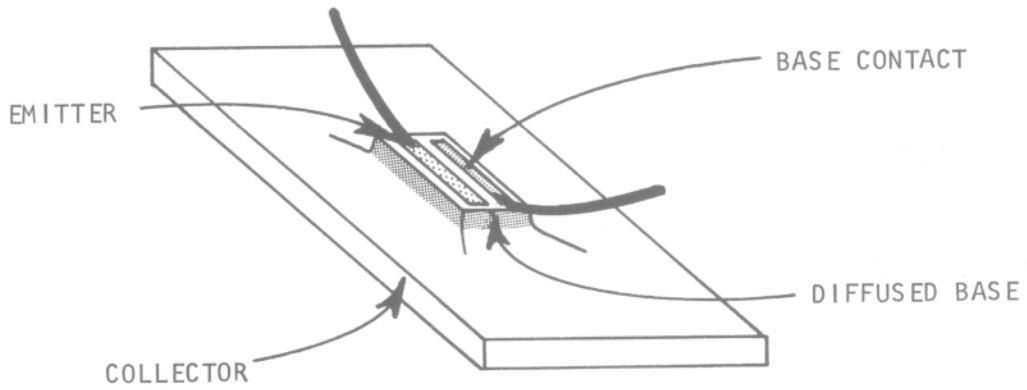

MESA

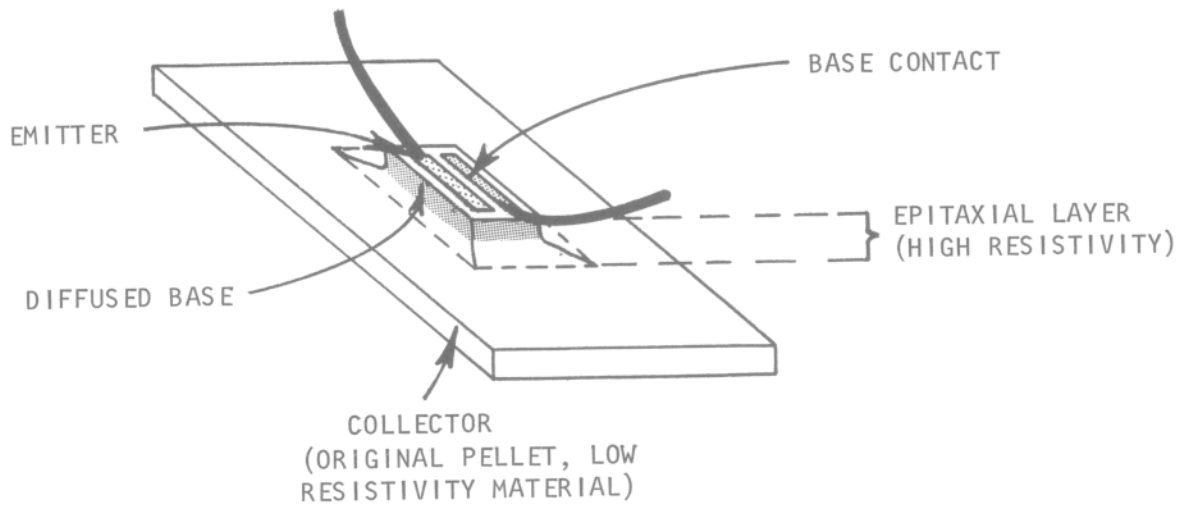

EPITAXIAL MESA

FIGURE 64

64.7

An epitaxial layer refers to the process of passing a gas over a structure until the gas has deposited a layer of solidified material on top of the original structure. The epitaxial mesa utilizes an _____ layer.

BV_{CBO}

64.8

The epitaxial mesa has the same characteristics as the mesa with the added advantage of a higher value of BV_{CBO}. The _____ layer makes possible the higher breakdown voltage capability.

epitaxial

64.9


The epitaxial mesa is constructed by first depositing a high resistivity epitaxial layer on a basic low resistant crystal pellet. The base is diffused into the epitaxial layer and the rest of the construction is the same as the _____.

epitaxial


64.10

The diffused base and the remainder of the epitaxial layer form the collector junction. The rest of the pellet or wafer serves to dissipate heat. The high resistance epitaxial layer at the collection junction allows a higher value of collector breakdown voltage.

mesa

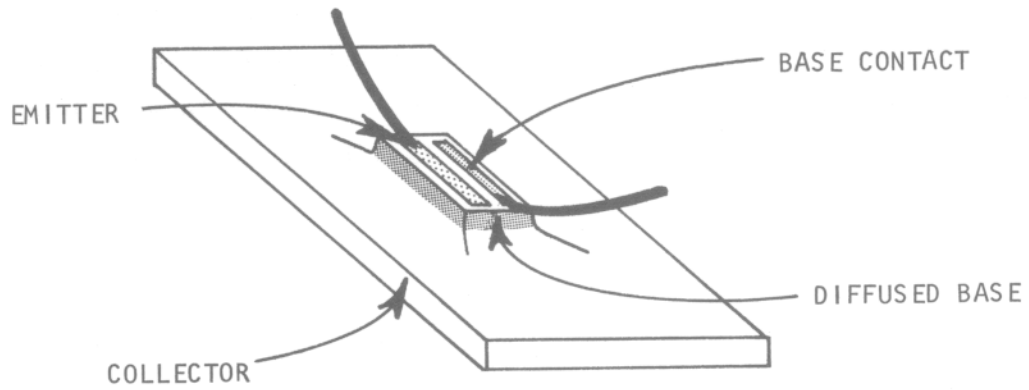

MESA

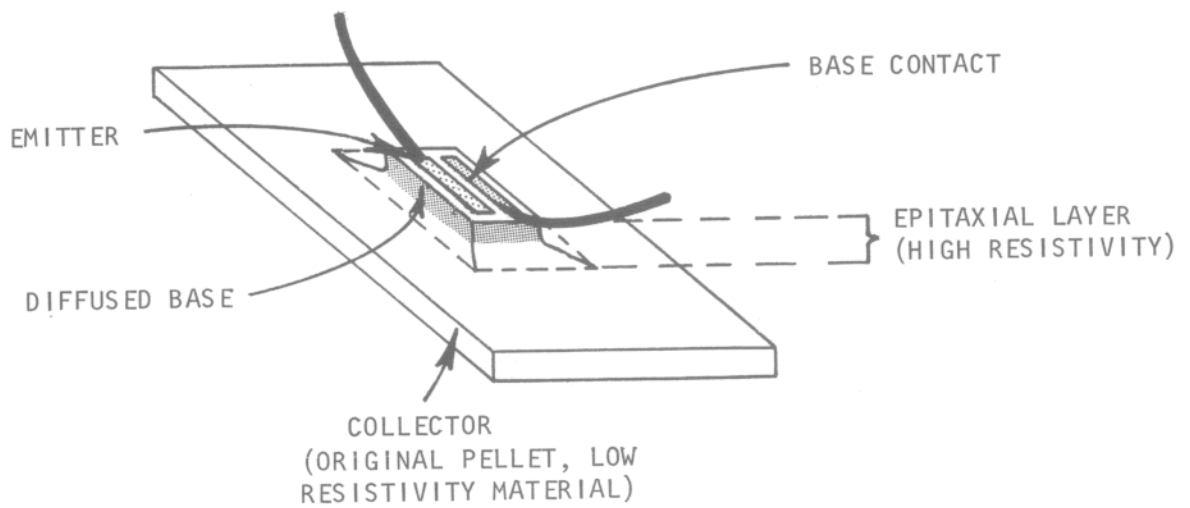

EPITAXIAL MESA

FIGURE 64

65 The planar transistor does not need the flat topped peak of the mesa, as _____ is used to mask the basic pellet and allow controlled diffusion. Selected portions for the emitter and base are cut through the protection to allow _____. The junctions are protected immediately on being formed and are said to be surface _____.

65.1 The planar transistor is made by diffusing both the emitter and base into the basic crystal wafer. The planar is a double _____ transistor.


silicon dioxide
diffusion
passivated

65.2 A layer of silicon dioxide is grown on the surface of the basic crystal wafer. Diffusion cannot occur through the _____.


diffused

65.3 Holes can be cut through the silicon dioxide and allow well controlled diffusion of the emitter and base as shown in figure 65. The original pellet becomes the _____.

silicon dioxide

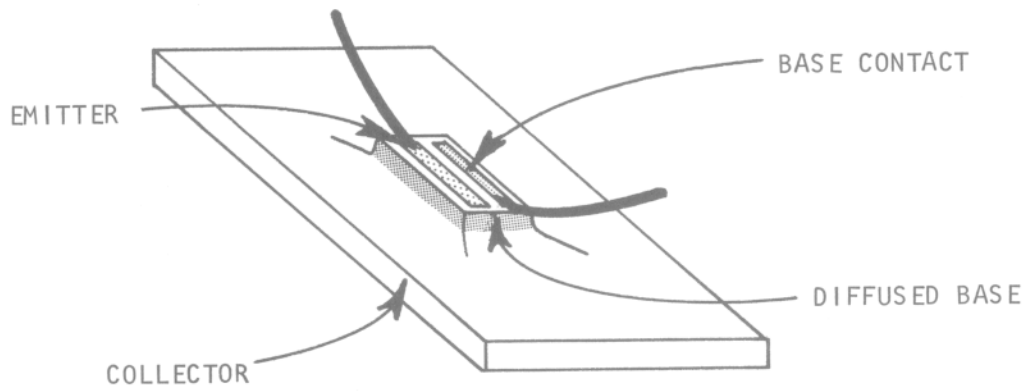

MESA

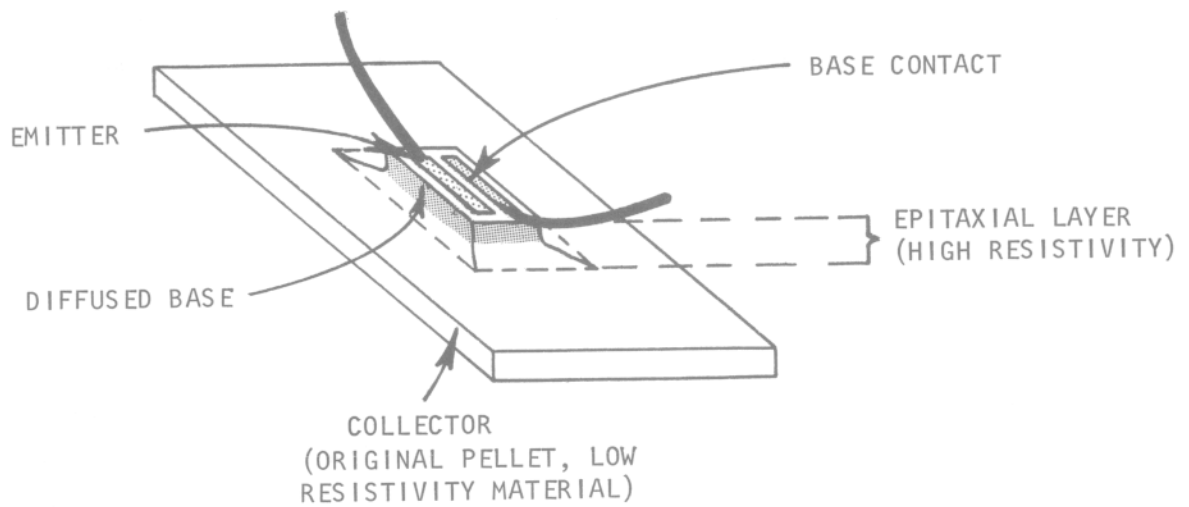

EPITAXIAL MESA

FIGURE 64

65.4 The silicon dioxide masks the remainder of the collector area and keeps the junction confined to the selected area. This maintains low junction capacitance and the mesa is not necessary. The _____ mask does much the same job as etching the mesa.

collector

65.5 Since the silicon dioxide is replaced immediately over the junction after it is formed, the junction is protected from the surrounding environment and is said to be surface passivated. The _____ transistor is double-diffused and surface _____.

silicon dioxide

65.6 The emitter and base contacts in figure 65 are termed ohmic contacts. This indicates that they are passive or non-rectifying contacts. The junctions are active internally, but are surface _____.

planar
passivated


65.7** The mesa or flat topped peak is not needed in the planar because _____ is used to mask the device and allow controlled diffusion. Holes are cut through the surface protection for selected _____ of a given area for the emitter and base. The junctions are surface _____.

passivated

65.8

END OF SET

silicon dioxide
diffusion
passivated

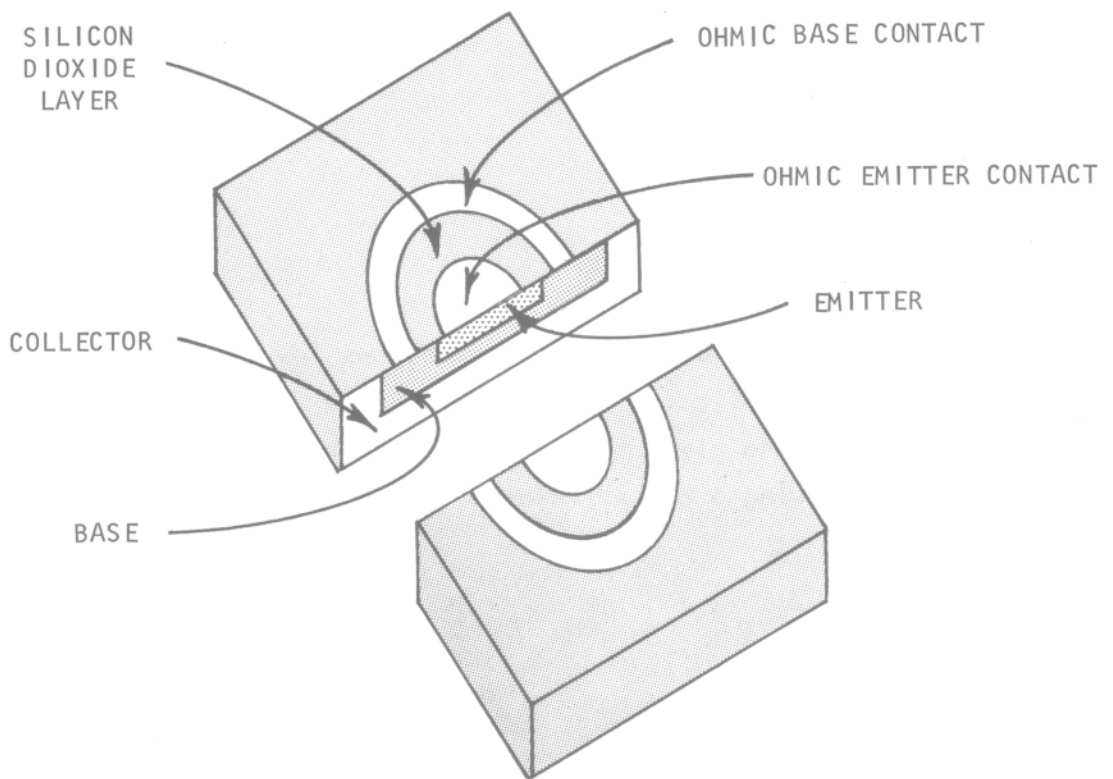

PLANAR

FIGURE 65

SELF TEST

Read each question carefully, studying any diagrams provided and select the most correct answer.

1. Forward biasing a PN junction results in majority carriers crossing the junction and becoming minority carriers. The average time the carriers exist after crossing the junction and before recombining is termed _____.
 - a. half life of the material
 - b. minority carrier lifetime
 - c. transit time
 - d. recombination time

2. Applying forward bias to a PN junction with one side doped much lighter than the other, results in some carriers failing to recombine and diffusing through the lightly doped side as _____ carriers.
 - a. heat
 - b. bias
 - c. majority
 - d. minority

3. Doping one side of a PN junction much lighter and making it very narrow results in much of the forward bias current in the external circuit being the result of _____ current in the diode.
 - a. diffusion
 - b. majority carrier
 - c. photon
 - d. phonon

4. Forward bias current transported by diffusion of carriers results when the _____ side of the junction is doped much lighter than the opposite side.
 - a. N
 - b. P
 - c. either N or P
 - d. none of the above

5. When two junctions are formed in a single piece of semiconductor, recombination occurs at both junctions until a state of _____ exists at both junctions and carrier movement across the junctions _____.
 - a. pandimonium, starts
 - b. balance, stops
 - c. equilibrium, starts
 - d. reverse bias, reverses

6. Junction transistors are constructed by doping two junctions in a single piece of semiconductor with the two ends _____ doped and the center _____ doped.

- a. lightly, heavily
- b. heavily, heavily
- c. heavily, lightly
- d. lightly, lightly

7. The center portion of a junction transistor is made narrow to enhance the transport of carriers by _____ in the center portion.

- a. photon
- b. majority carrier
- c. only electron
- d. diffusion

8. The center portion in the diagram is termed the _____ and the right hand portion the _____.



- a. base, collector
- b. collector, base
- c. gate, collector
- d. gate, anode

9. Injection of carriers from the emitter into the base is accomplished by application of _____ to the emitter-base junction.

- a. thermal energy
- b. reverse bias
- c. forward bias
- d. series resistance

10. The collector junction is normally _____ biased and depends on _____ carriers in the base for current.



- a. reverse, minority
- b. forward, majority
- c. forward, minority
- d. reverse, majority

11. The emitter current is the sum of _____ and _____ current in the _____.
- recombination, diffusion, base
 - collector, diffusion, base
 - base, collector, transistor
 - either a or c
 - base, recombination, collector
 - either b or e
12. h_{FB} is the symbol for _____ current gain from the _____ to the _____ of the transistor.
- small signal, emitter, collector
 - d-c, base, collector
 - small signal, base, collector
 - d-c, emitter, collector
13. The product of d-c current gain, _____ (symbol), and the d-c base current will give the value of _____ current.
- h_{FE} , collector
 - h_{FB} , collector
 - h_{FE} , emitter
 - h_{FB} , emitter
14. A variation in base or emitter current will be accompanied by a change in collector current. For a given change in base or emitter current, a change in _____ current will result in the greatest change in collector current.
- base
 - emitter
15. I_{CBO} indicates current between _____ and _____, with the _____ open circuited.
- emitter, collector, base
 - collector, emitter, base
 - collector, base, emitter
 - emitter, base, collector
16. I_{CBO} is made up of carriers present as a result of _____ and will vary with a change in _____.
- thermal energy, forward bias
 - reverse bias, thermal resistance
 - forward bias, temperature
 - thermal energy, temperature
 - reverse bias, capacitance

17. I_{CEO} is the current between _____ and _____ with the _____ open circuited.
- collector, emitter, base
 - collector, base, emitter
 - emitter, base, collector
 - collector, emitter, emitter

18. $I_{CEO} \approx$ _____ $\times I_{CBO}$.
- h_{FB}
 - h_{FE}
 - ambient temperature
 - thermal resistance

19.

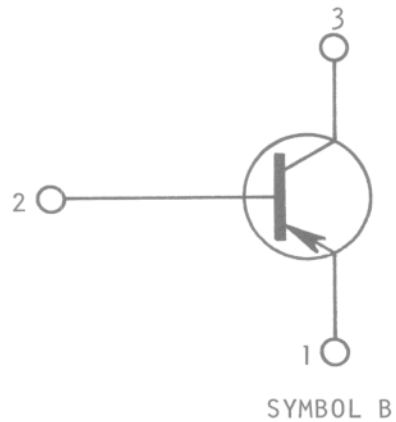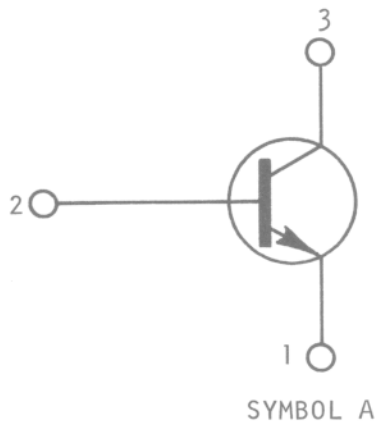

Symbol B is a/an _____ transistor and point 2 indicates the _____ lead.

- NPN, base
 - PNP, base
 - PNP, emitter
 - NPN, emitter
20. A transistor in a common emitter configuration has a greater possible current gain than _____.
- a transistor in a common base configuration
 - a transistor in a common collector configuration
 - unity
 - any of the above
 - either a or c

21. A transistor in a common _____ configuration can yield the highest possible power gain of the three configurations.
- a. emitter
 - b. base
 - c. collector
22. A transistor in a common _____ configuration cannot offer a current gain greater than unity.
- a. collector
 - b. emitter
 - c. base
23. A transistor in a common _____ configuration cannot offer a voltage gain greater than unity.
- a. collector
 - b. emitter
 - c. base
24. h_{fe} is the _____, a-c current gain of the transistor in a common _____ configuration.
- a. direct current, base
 - b. small signal, emitter
 - c. direct current, emitter
 - d. small signal, base
25. The small signal, a-c, current gain of the transistor in a common base configuration is given the symbol _____ and _____ include circuit effects.
- a. h_{fb} , does not
 - b. h_{fc} , does not
 - c. h_{fb} , does
 - d. h_{fe} , does
 - e. h_{fc} , does not
26. Power gain is possible with the common base configuration, although _____ gain is less than unity, since _____ gain greater than unity is possible.
- a. voltage, current
 - b. current, voltage

27. Power gain is possible with the common collector configuration, although _____ gain is less than unity, since _____ gain greater than unity is possible.
- current, voltage
 - voltage, current
28. Emitter follower is another name given a transistor in a common _____ configuration.
- emitter
 - collector
 - base
29. h_{fc} is the small signal, low frequency current gain of the transistor in a common _____ configuration and is approximately equal to _____.
- base, $h_{fb} + 1$
 - emitter, $h_{fe} + 1$
 - collector, $h_{fb} + 1$
 - collector, $h_{fe} + 1$
30. The emitter follower offers a _____ input resistance and a _____ output resistance.
- low, low
 - high, high
 - high, low
 - low, high
31. A transistor in a common _____ configuration has a very low output resistance is able to supply large output _____.
- collector, currents
 - emitter, voltages
 - base, voltages
 - base, currents
32. The slope of a d-c load line constructed on a collector family of curves is determined by the _____ in _____ the transistor.
- reactance, series with
 - resistance, series with
 - current, the base of
 - current, the collector of

33. The d-c load line is constructed between the maximum _____ point and the maximum _____ point on the collector family of curves set by the series resistance and the total supply _____.
- voltage, current, current
 - voltage, current, voltage
 - voltage, current, resistance
 - resistance, current, voltage
34. The transistor is termed in saturation when the collector becomes _____. The collector voltage at this point is given the symbol _____.
- cut-off, V_{CC}
 - forward biased, BV_{CBO}
 - reversed biased, $V_{CE(sat)}$
 - forward biased, $V_{CE(sat)}$
 - fully saturated, $BV_{CBO(sat)}$
35. Saturation in a transistor results in an increase in the _____ in the base as a result of the collector junction becoming _____ biased.
- stored charge, reverse
 - depletion region, forward
 - depletion region, reverse
 - stored charge, forward
36. Avalanche breakdown occurs at high _____ collector voltages due to the _____ of carriers at the collector junction.
- forward, acceleration
 - reverse, recombination
 - reverse, multiplication
 - forward, multiplication
37. Changing the transistor's configuration will change the collector voltage point at which avalanche breakdown occurs. BV_{CBO} indicates the breakdown voltage, _____ to _____ with the _____ d-c open circuited.
- collector, base, emitter
 - collector, emitter base
 - emitter base, collector
 - collector, ground, emitter

38. BV_{CEO} indicates the breakdown voltage, _____ to _____ with the _____ d-c open circuited.
- base, emitter, collector
 - collector, emitter, base
 - collector, base, emitter
 - collector, ground, emitter
39. BV_{CER} is the breakdown voltage, _____ to _____ with a specified value of resistance between _____ and _____.
- collector, emitter, collector, base
 - collector, base, base, emitter
 - collector, emitter, base, emitter
 - collector, emitter, collector, emitter
40. Maximum steady state power dissipation in a transistor is limited by the maximum allowable junction _____, surrounding air _____, and the total _____, junction to ambient.
- temperature, temperature, thermal resistance
 - current, temperature, temperature gradient
 - voltage, temperature, thermal resistance
 - temperature, temperature, temperature gradient
41. θ_{JA} is the symbol for thermal resistance, _____ to _____ and is measured in _____.
- jacket, ambient, °C/watt
 - junction, area, watts/°C
 - junction, ambient, watts/°C
 - junction, ambient, °C/watt
42. $\theta_{JC} + \theta_{CS} + \text{_____} = \theta_{JA}$ when a separate _____ sink is used with a transistor.
- θ_{SC} , heat
 - θ_{CA} , conductance
 - θ_{CA} , heat
 - θ_{SA} , heat
43. _____ lubricant reduces thermal resistance, case to _____ and as a result, reduces total thermal resistance.
- Germanium, heat sink
 - Silicone, heat sink
 - Gallium, heat sink
 - Gallium, ambient

44. $\theta_{JC} = 1.8^\circ\text{C/watt}$
 $\theta_{SA} = 3.6^\circ\text{C/watt}$
 $\theta_{CS} = 0.6^\circ\text{C/watt}$
 $T_A = 60^\circ\text{C}$
 $T_{Jmax} = 150^\circ\text{C}$

$$P_{max} = \frac{T_{J(max)} - T_A}{\theta_{JA}}$$

The maximum steady state power the transistor can dissipate with the thermal characteristics listed above is _____.

- a. 1.5 watts
 - b. 30 watts
 - c. 15 watts
 - d. 3 watts
45. For maximum linear power operating in the active region, the load line should be placed _____.
- a. tangent to the maximum power curve in the most linear region of curves.
 - b. from BV_{CBO} to a point tangent to the maximum power curve
 - c. from $I_C(\text{max})$ to a point tangent to the maximum power curve
 - d. $I_C(\text{max})$ to $V_{CE}(\text{max})$
46. Answer d in question 45 will allow _____ for a given transistor.
- a. maximum linear power
 - b. maximum power with maximum current swing in the linear region
 - c. maximum power for low repetition rate switching
 - d. maximum power for high repetition rate switching
47. Little power is dissipated at cut-off and _____ while most of the power is dissipated in the _____ region of the transistor's characteristics.
- a. transient, active
 - b. depletion, transient
 - c. saturation, active
 - d. saturation, depletion
48. _____ power can be dissipated during switching with the transistor is operated as a cut-off to saturated, low rep-rate switch and the load line can _____ the maximum power curve on a collector family of curves.
- a. less, not cross over
 - b. more, be tangent to
 - c. more, be in the safe area below
 - d. more, cross over

49. The off to saturated switching mode offers _____ resting state power, but limited repetition rate due to increased _____.
- low, storage time
 - high, storage time
 - maximum, transit time
 - low, transit time
50. A transistor switch turn on time (t_{on}) is equal to the sum of _____ and _____, and the transistors turn off time is equal to the sum of _____ and _____ when using the switching parameters.
- rise time, transit time fall time, response time
 - rise time, transit time storage time, fall time
 - rise time, delay time storage time, fall time
 - rise time, interface time storage time, recovery time
51. A capacitor used to reduce switching time in a transistor switching configuration, by aiding in the establishment and removal of the stored charge is referred to as a _____ capacitor.
- switching filter
 - speed up
 - charge chopper
 - time chopper
52. The charge on the capacitor mentioned in question 51 should be _____ the transistors stored charge for an effective increase in switching time.
- equal to
 - less than
 - ten times
 - one tenth of
53. _____ switching offers faster switching times than the saturated mode, but sacrifices _____.
- cut-off, flexibility
 - current mode, less critical transistor specification
 - voltage mode, power
 - current mode, power capabilities
54. A/an _____ switching transistor has the transistor switching in the collector breakdown region and can offer rise times in the fractional _____ second region.
- avalanche, nano
 - avalanche, micro
 - current mode, nano
 - current mode, micro
 - avalanche, milli

55. The three main high frequency limiting factors in transistors are _____, _____, and _____.
- doping ratio, junction capacity, storage time
 - junction capacity, base transit time, thermal resistance
 - base transit time, spreading of carriers in the base, junction capacity
 - emitter transit time, spreading of carriers in the base, junction capacity
56. _____ is the symbol for the cut-off frequency of a transistor in a common base configuration and indicates the frequency at which _____ falls to 0.707 of its low frequency value.
- f_{hfe} , h_{fe}
 - f_t , h_{fb}
 - f_{hfb} , h_{fb}
 - f_{α_b} , h_{fe}
57. C_{ob} is the symbol for the output capacitance of a transistor in a common _____ orientation. C_{oe} is the symbol for the output capacitance of a transistor in a common _____ orientation.
- base, emitter
 - emitter, base
58. A _____ base and _____ junction capacity is the aim in high frequency transistors.
- heavily doped, low
 - lightly doped, diffused
 - narrow, low
 - narrow, variable
59. f_t is the symbol for the frequency at which _____ falls to _____.
- h_{fe} , unity
 - h_{fb} , 0.707 of low frequency value
 - h_{fe} , 0.707 of low frequency value
 - h_{fb} , unity

60. f_{hfe} indicates the cut-off (_____) of the transistor in a common _____ configuration.

- a. $h_{fe} = \text{unity}$, emitter
- b. low frequency $h_{fe} \times 0.707$, base
- c. $h_{fe} = \text{unity}$, base
- d. low frequency $h_{fe} \times 0.707$, emitter

29. d

30. c

59. a

60. d

ANSWERS TO SELF TEST

1. b
2. d
3. a
4. d
5. b
6. c
7. d
8. a
9. c
10. a
11. d
12. d
13. a
14. a
15. c
16. d
17. a
18. b
19. b
20. e
21. a
22. c
23. a
24. b
25. a
26. b
27. b
28. b
29. d
30. c

31. a
32. b
33. b
34. d
35. d
36. c
37. a
38. b
39. c
40. a
41. d
42. d
43. b
44. c
45. a
46. c
47. c
48. d
49. a
50. c
51. b
52. a
53. d
54. a
55. c
56. c
57. a
58. c
59. a
60. d